

Lectur 22


RF and Microwave Circuit Design Γ-Plane and Smith Chart Analysis

In this lecture you will learn:

- Γ-plane and Smith Charts
- Stub tuning
- Quarter-Wave transformers

ECE 303 – Fall 2005 – Farhan Rana – Cornell University

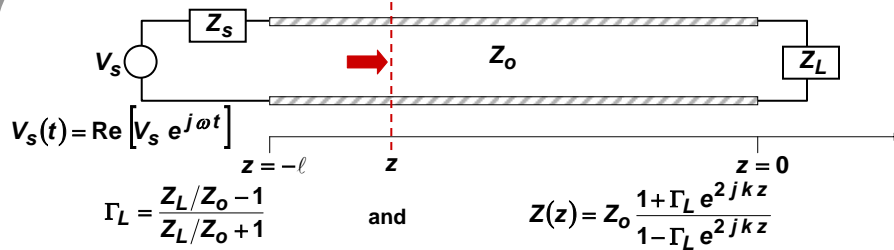Impedance Transformations in Transmission Lines



Define a position dependent reflection coefficient as:

$$\Gamma(z) = \Gamma_L e^{2jkz}$$

→ $\Gamma(z)$ is a complex number of magnitude never greater than unity

Define a normalized impedance as:

$$Z_n(z) = \frac{Z(z)}{Z_0} = R_n(z) + j X_n(z)$$

→ Normalized resistance

→ Normalized reactance

Then:

$$Z_n(z) = \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \quad \text{or} \quad \Gamma(z) = \frac{Z_n(z) - 1}{Z_n(z) + 1}$$

ECE 303 – Fall 2005 – Farhan Rana – Cornell University

Γ -Plane (Complex Plane)

$$\Gamma(z) = \Gamma_L e^{2jkz}$$



$\Gamma(z)$ completes one full revolution in the complex plane when its phase goes through 2π

$$2kz = 2\pi$$

$$\Rightarrow z = \frac{\lambda}{2}$$

$$Z_n(z) = \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

Therefore, impedance is periodic with distance z with a period equal to half-wavelength

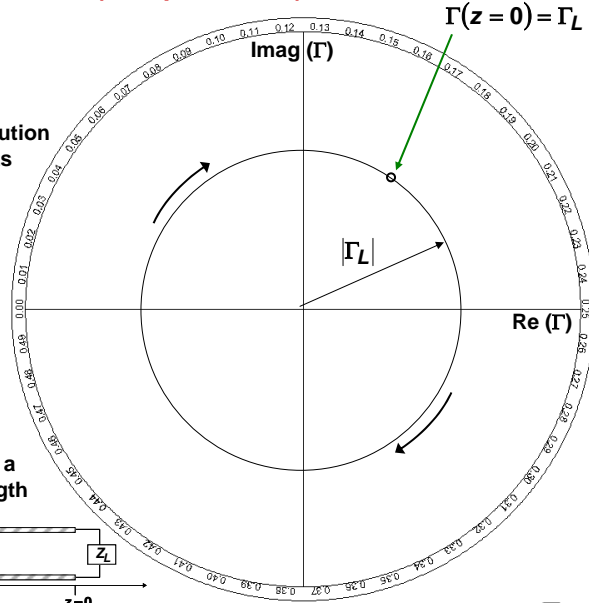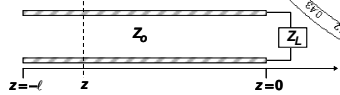



ECE 303 - Fall 2005 - Farhan Rana - Cornell University

Γ -Plane with Normalized Reactance Curves

$$\begin{aligned} Z_n(z) &= \frac{Z(z)}{Z_0} \\ &= R_n(z) + jX_n(z) \\ &= \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \end{aligned}$$

The red curves indicate the values of the normalized reactance $X_n(z)$ on the Γ -plane

From the curves one can read-off the values of $X_n(z)$

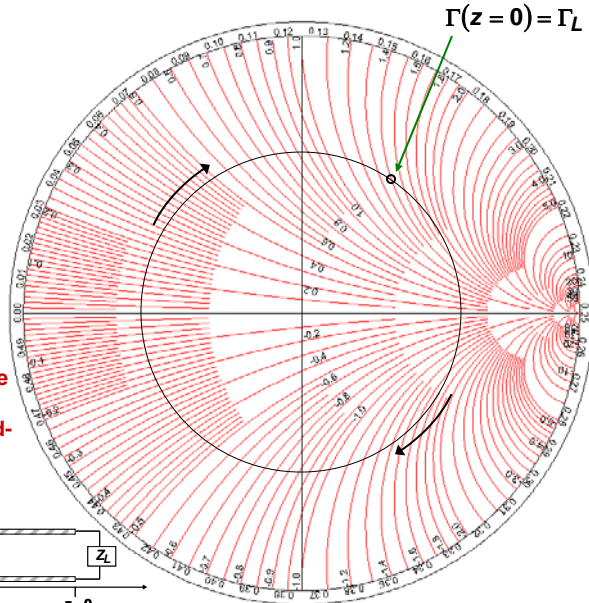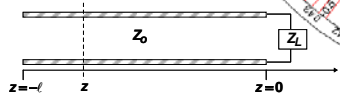


ECE 303 - Fall 2005 - Farhan Rana - Cornell University

Γ-Plane with Normalized Resistance Curves

$$\begin{aligned} Z_n(z) &= \frac{Z(z)}{Z_0} \\ &= R_n(z) + jX_n(z) \\ &= \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \end{aligned}$$

The blue curves indicate the values of the normalized resistance $R_n(z)$ on the Γ -plane

From the curves one can read-off the values of $R_n(z)$

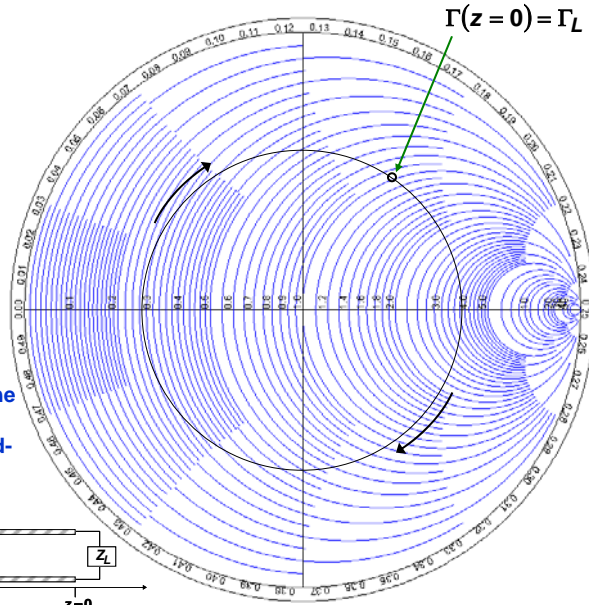


ECE 303 – Fall 2005 – Farhan Rana – Cornell University

Γ-Plane with Normalized Resistance and Reactance Curves The Smith Chart

$$\begin{aligned} Z_n(z) &= \frac{Z(z)}{Z_0} \\ &= R_n(z) + jX_n(z) \\ &= \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \end{aligned}$$


The **Smith Chart** enables one to read-off values of both the normalized resistance $R_n(z)$ and the normalized reactance $X_n(z)$ values on the Γ -plane

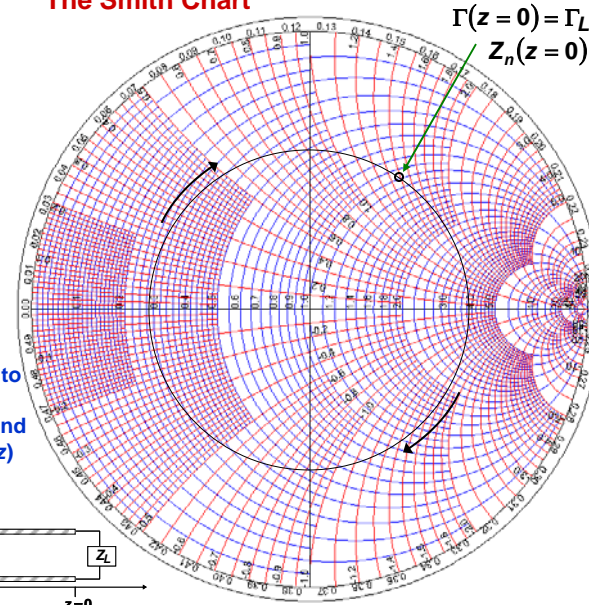

ECE 303 – Fall 2005 – Farhan Rana – Cornell University

Load Matching for Maximum Power

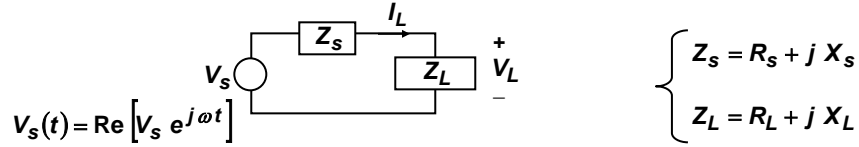In many microwave and RF circuits it is HIGHLY desirable to be able to transfer maximum possible time-average power to a load impedance:



What is the time-average power delivered to the load?


$$\begin{aligned} \langle P_L(t) \rangle &= \langle V_L(t) I_L(t) \rangle = \frac{1}{2} \text{Re} [V_L I_L^*] = \frac{1}{2} \text{Re} \left[V_s \frac{Z_L}{Z_s + Z_L} \left(\frac{V_s}{Z_s + Z_L} \right)^* \right] \\ &= \frac{1}{2} \frac{|V_s|^2}{|Z_s + Z_L|^2} \text{Re} [Z_L] = \frac{|V_s|^2}{2} \frac{R_L}{(R_s + R_L)^2 + (X_s + X_L)^2} \end{aligned}$$

Maximum time-average power delivered to the load:

$$\Rightarrow \langle P_L(t) \rangle \text{ is maximized when: } \begin{cases} R_L = R_s & X_L = -X_s \\ \text{or} \\ Z_L = Z_s^* \end{cases} \Rightarrow \langle P_L(t) \rangle_{\max} = \frac{|V_s|^2}{8 R_s}$$


ECE 303 - Fall 2005 - Farhan Rana - Cornell University

Load Matching in Transmission Lines

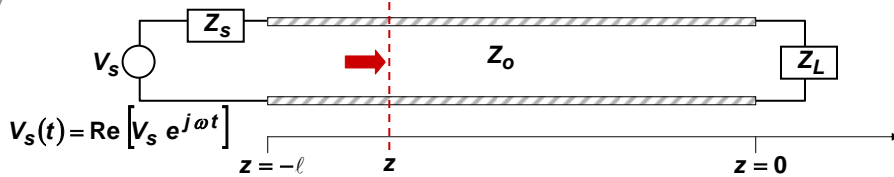

$$Z_n(z) = \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \quad Z(z) = Z_0 \quad Z_n(z) = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

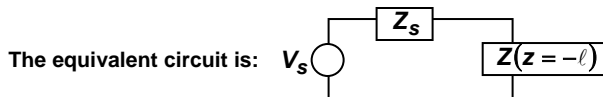How does one get the maximum time-average power delivered to the load?




Power delivered to the load Z_L will be maximized if power delivered to the transformed impedance $Z(z = -l)$ is maximized

\Rightarrow Must have the impedance $Z(z = -l)$ matched to the source impedance Z_s , i.e.

$$Z(z = -l) = Z_s^*$$

ECE 303 - Fall 2005 - Farhan Rana - Cornell University

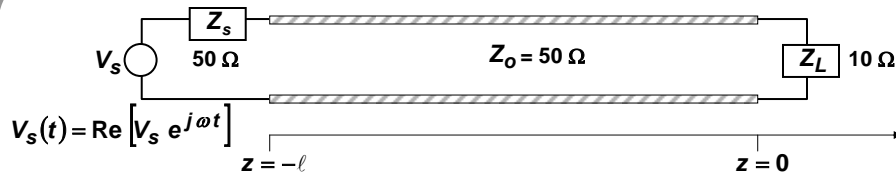Example: Load Matching in Transmission Lines - I



Suppose: $Z_0 = 50 \Omega$ $Z_L = 10 \Omega$ $Z_s = 50 \Omega$

How does one get the maximum time-average power delivered to the load?

Need $Z(z = -\ell)$ matched to the source impedance $Z_s = 50 \Omega$

STEP 1: First find Γ_L

$$\Gamma_L = \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} = \frac{2}{3} = -0.667$$

STEP 2: Find " ℓ " such that the impedance $Z(z = -\ell)$ has a real part of 50Ω

$$Z(z = -\ell) = 50 + jX(z = -\ell) \Rightarrow Z_n(z = -\ell) = 1.0 + jX_n(z = -\ell)$$

ECE 303 - Fall 2005 - Farhan Rana - Cornell University

Example: Load Matching in Transmission Lines - II

Find the desired " ℓ " using Smith Chart


$$Z_n(z = 0) = 0.2$$

$$\Gamma(z = 0) = \Gamma_L = -0.667$$

$$Z_n(z = -\ell) \approx 1.0 + j1.8$$


$$\Rightarrow \ell \approx 0.183 \lambda$$

$$Z(z = -\ell) \approx (1.0 + j1.8) Z_0 \approx 50 + j90$$

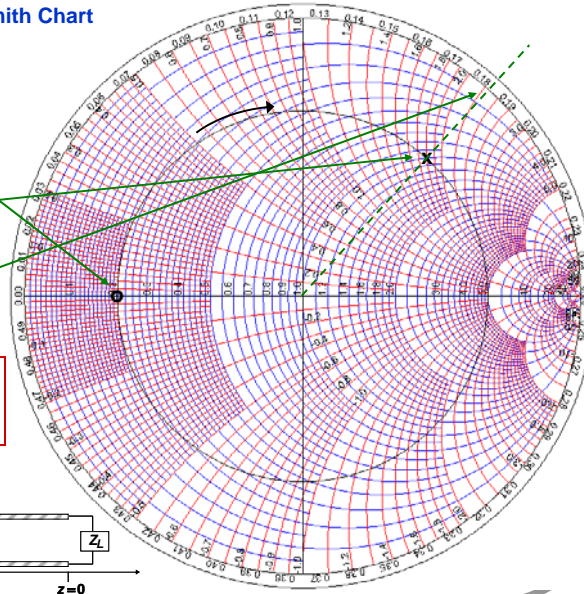


ECE 303 - Fall 2005 - Farhan Rana - Cornell University

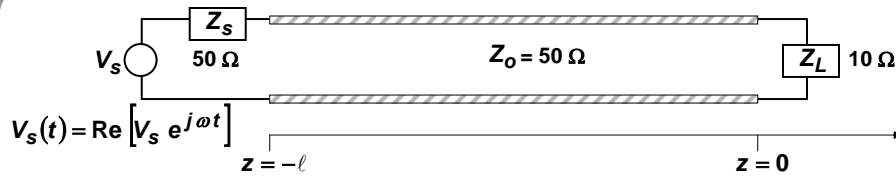Example: Load Matching in Transmission Lines - III



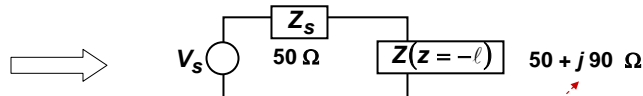So if $\ell = 0.183 \lambda$ then the equivalent circuit is:



But we have a problem !

We have been able to match the real part of the impedance to the source but we ended up with an unwanted reactive term


How do we get rid of this unwanted reactance?

Answer: Use "stub tuners"

ECE 303 - Fall 2005 - Farhan Rana - Cornell University



Stub Tuners in Microwave Circuits

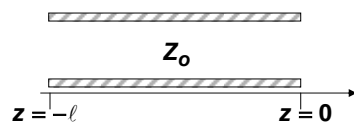Stub tuners, as the name suggests, are short stubs of transmission lines that are used to cancel out unwanted reactances in microwave circuits




$$Z(z = -\ell) = jX = -Z_0 j \cot(k\ell)$$

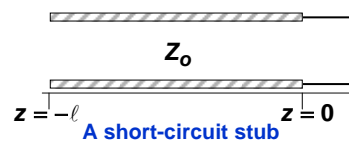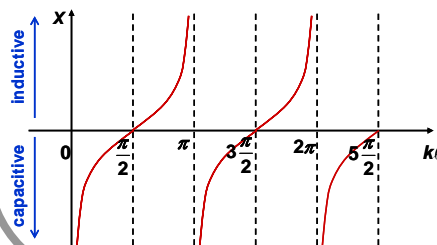It has a capacitive impedance for short lengths and is used to cancel unwanted inductive reactances




$$Z(z = -\ell) = jX = Z_0 j \tan(k\ell)$$

It has an inductive impedance for short lengths and is used to cancel unwanted capacitive reactances

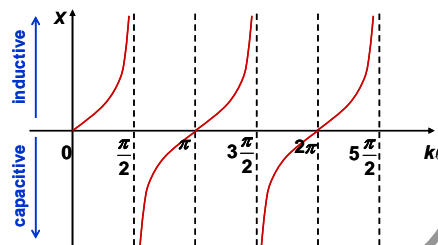

ECE 303 - Fall 2005 - Farhan Rana - Cornell University

Load Matching Using Series Stub Tuners

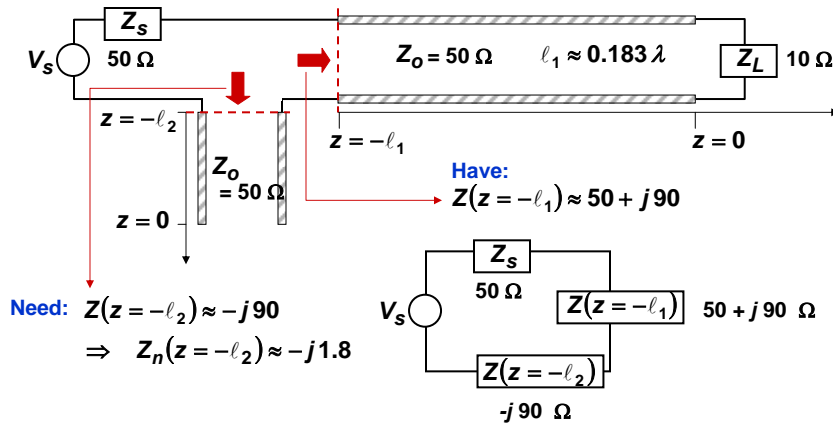

What length l_2 of the stub must be chosen to get a reactance of $-j90$?

$$Z(z = -l_2) = -Z_o j \cot(k l_2) = -j90$$

$$\Rightarrow k l_2 \approx 0.50$$

$$\Rightarrow l_2 \approx .08 \lambda$$

Load Matching Using Stub Tuners: Smith Chart

Open-Circuit stub tuner on a Smith Chart


$$Z_n(z = 0) = \infty$$

$$\Gamma(z = 0) = \Gamma_L = +1$$

$$Z(z = -l_2) \approx -j90$$

$$\Rightarrow Z_n(z = -l_2) \approx -j1.8$$

$$\Rightarrow l_2 \approx 0.08 \lambda$$

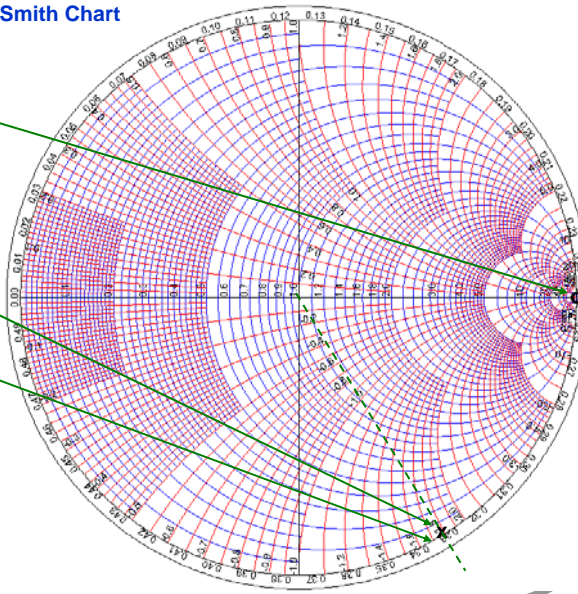



Admittances and Normalized Admittances on Smith Charts

$$\begin{aligned} Z_n(z) &= \frac{Z(z)}{Z_o} \\ &= R_n(z) + jX_n(z) \\ &= \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \end{aligned}$$

$$Y_o = \frac{1}{Z_o}$$


$$Y(z) = \frac{1}{Z(z)}$$

$$\begin{aligned} Y_n(z) &= \frac{Y(z)}{Y_o} = \frac{1}{Z_n(z)} \\ &= \frac{1 - \Gamma(z)}{1 + \Gamma(z)} \end{aligned}$$

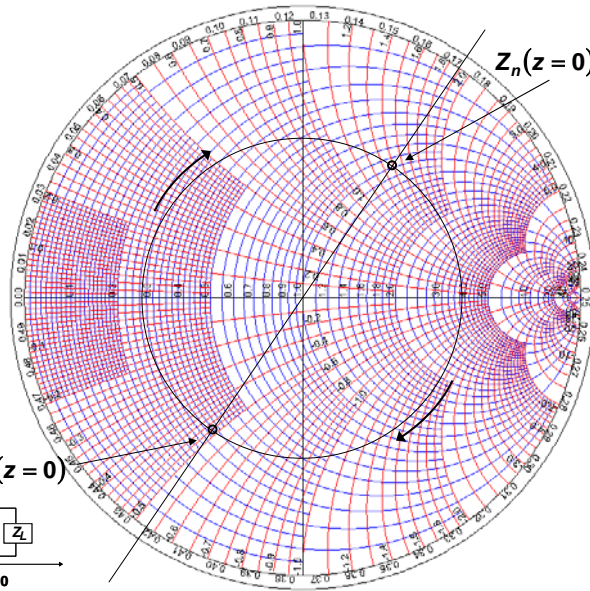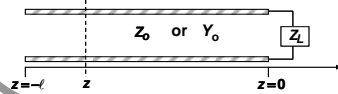

ECE 303 - Fall 2005 - Farhan Rana - Cornell University

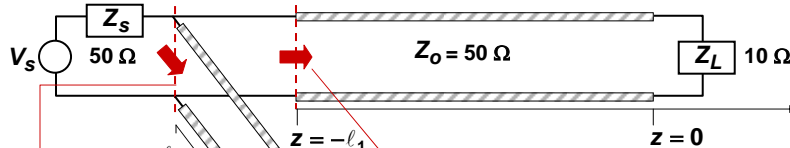Load Matching Using Parallel Stub Tuners - I



Need:


$$Y(z = -l_2) = \frac{1}{Z(z = -l_2)} = +jD$$

$$\Rightarrow Y_n(z = -l_2) = \frac{1}{Z_n(z = -l_2)} = +j50D$$

Need:

$$Y(z = -l_1) = \frac{1}{Z(z = -l_1)} = \frac{1}{50} - jD$$
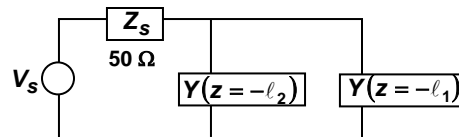
$$\Rightarrow Y_n(z = -l_1) = \frac{1}{Z_n(z = -l_1)} = 1 - j50D$$



It is more useful here to work with admittances rather than impedances when one uses parallel stubs since admittances of circuit elements in parallel add

ECE 303 - Fall 2005 - Farhan Rana - Cornell University

Load Matching Using Parallel Stub Tuners - II


$$Z_n(z=0) = \frac{10}{50} = 0.2$$

$$\Gamma(z=0) = \Gamma_L = -0.667$$

$$Y_n(z=0) = \frac{1}{Z_n(z=0)} = 5.0$$

$$Y_n(z=-l_1) = \frac{1}{Z_n(z=-l_1)} = 1.0 - j1.8$$


$$\Rightarrow l_1 \approx 0.067 \lambda$$

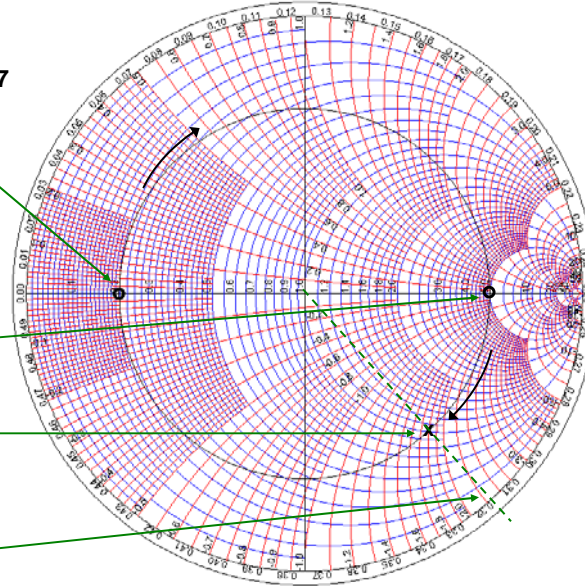

ECE 303 - Fall 2005 - Farhan Rana - Cornell University

Load Matching Using Parallel Stub Tuners - III

So what do we have so far:

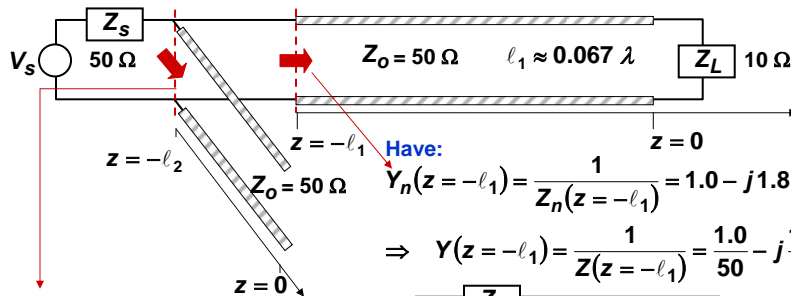


Have:

$$Y_n(z=-l_1) = \frac{1}{Z_n(z=-l_1)} = 1.0 - j1.8$$

$$\Rightarrow Y(z=-l_1) = \frac{1}{Z(z=-l_1)} = \frac{1.0}{50} - j \frac{1.8}{50}$$

Need:
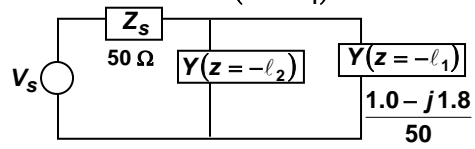
$$Y(z=-l_2) = \frac{1}{Z(z=-l_2)} = +j \frac{1.8}{50}$$



What length l_2 of the stub must be chosen to get a reactance of $+j 1.8/50$?

$$Y(z=-l_2) = \frac{1}{Z(z=-l_2)} = j \frac{\tan(k l_2)}{Z_0} = j \frac{1.8}{50}$$

$$\Rightarrow k l_2 \approx 1.064 \quad \Rightarrow l_2 \approx 0.17 \lambda$$

ECE 303 - Fall 2005 - Farhan Rana - Cornell University

Load Matching Using Parallel Stub Tuners - IV

Open-Circuit stub tuner on a Smith Chart


$$Z_n(z=0) = \infty$$

$$\Gamma(z=0) = \Gamma_L = +1$$

$$Y_n(z=0) = \frac{1}{Z_n(z=0)} = 0$$


$$Y_n(z=-l_2) = \frac{1}{Z_n(z=-l_2)} = +j1.8$$

$$\Rightarrow l_2 \approx 0.17 \lambda$$

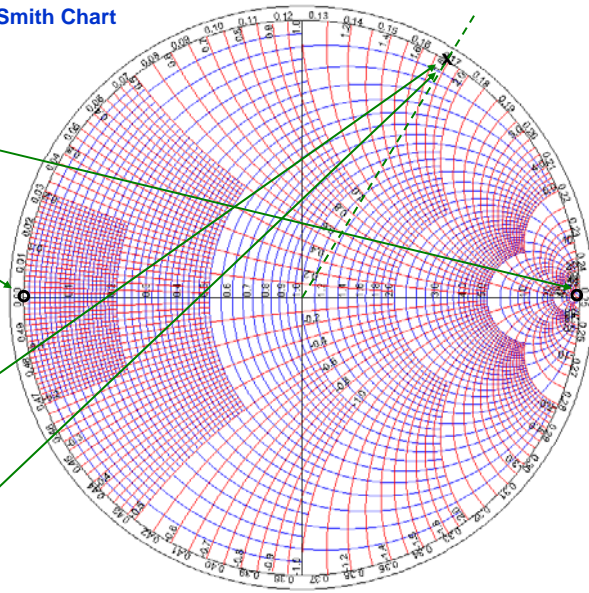


ECE 303 - Fall 2005 - Farhan Rana - Cornell University

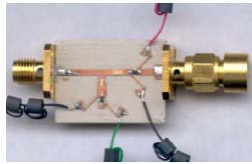
Stubs in Microwave Circuits: Some Pictures



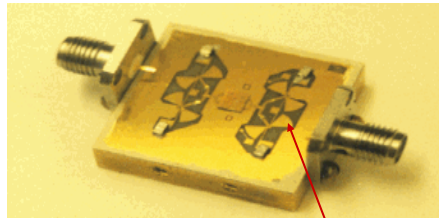
Photograph of an 10 GHz electronic single-stub tuner with varactor diode tuning elements



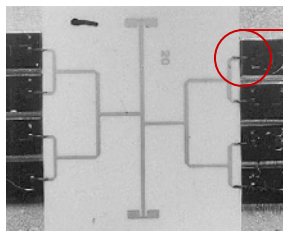A GaN amplifier chip with radial stubs for 10 GHz operation



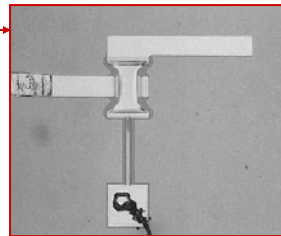
20 GHz micro-fabricated reconfigurable stub tuner



20 GHz micro-fabricated MEMS-switched stub tuner

ECE 303 - Fall 2005 - Farhan Rana - Cornell University

Quarter-Wave Transformer

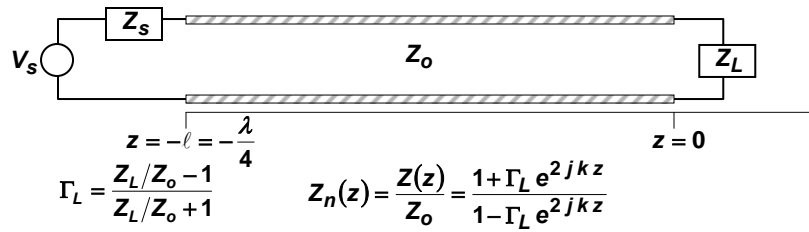

Suppose the length ℓ of the transmission line is quarter-wavelength:

$$\ell = \frac{\lambda}{4} \Rightarrow k\ell = \frac{\pi}{2}$$

$$\Rightarrow Z_n(z=0) = \frac{Z_L}{Z_o} = \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

$$\Rightarrow Z_n\left(z = -\ell = -\frac{\lambda}{4}\right) = \frac{1 + \Gamma_L e^{-2jk\ell}}{1 - \Gamma_L e^{-2jk\ell}} = \frac{1 - \Gamma_L}{1 + \Gamma_L} = \frac{1}{Z_n(z=0)} = \frac{Z_o}{Z_L}$$

A quarter-wavelength long transmission line inverts the normalized impedance

$$\text{Actual impedance at } z = -\lambda/4 : Z\left(z = -\frac{\lambda}{4}\right) = Z_o Z_n\left(z = -\frac{\lambda}{4}\right) = \frac{Z_o^2}{Z_L}$$

ECE 303 - Fall 2005 - Farhan Rana - Cornell University

Quarter-Wave Transformer: On a Smith Chart

Suppose:


$$Z_L = 50 + j50$$

$$Z_o = 50$$

$$\Rightarrow Z_n(z=0) = \frac{Z_L}{Z_o} = \frac{1 + \Gamma_L}{1 - \Gamma_L} = 1.0 + j1.0$$

$$\Rightarrow Z_n\left(z = -\frac{\lambda}{4}\right) = \frac{1}{Z_n(z=0)} = 0.5 - j0.5$$

$$Z\left(z = -\frac{\lambda}{4}\right) = Z_o Z_n\left(z = -\frac{\lambda}{4}\right) = 25 - j25$$

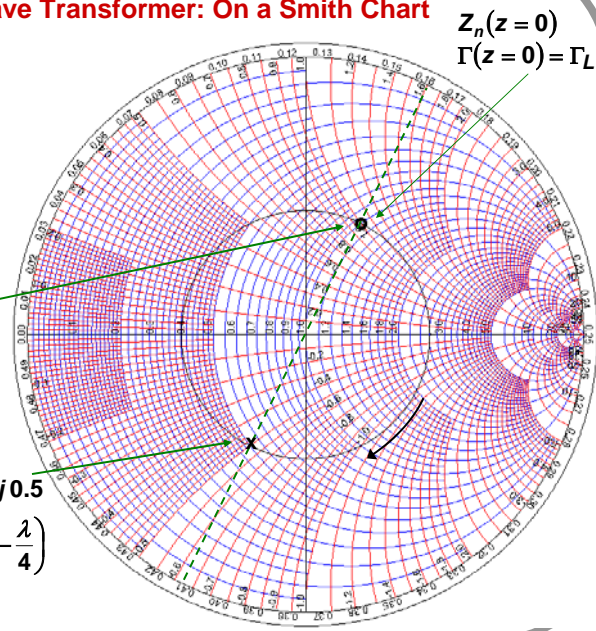

ECE 303 - Fall 2005 - Farhan Rana - Cornell University