 


Lecture 10


MOSFET Characteristics and Small Signal Circuit Models

In this lecture you will learn:



- The operation of the MOS transistor
- Small signal circuit models of the MOS transistor



A NMOS Transistor: A Review

 


NMOS Transistor: A Review

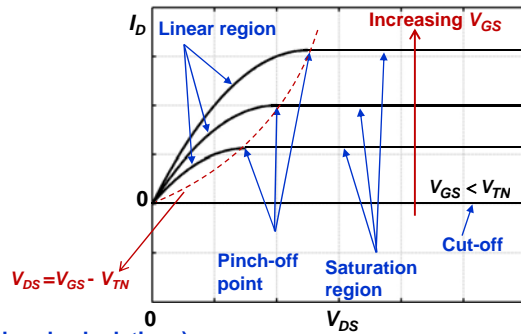 

Simplified current model (good for hand calculations):

$$I_D = \begin{cases} 0 & \text{For } V_{GS} < V_{TN} \\ k_n \left[V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right] V_{DS} & \text{For } 0 \leq V_{DS} \leq V_{GS} - V_{TN} \\ \frac{k_n}{2} (V_{GS} - V_{TN})^2 & \text{For } 0 \leq V_{GS} - V_{TN} \leq V_{DS} \end{cases} \quad \left. \vphantom{\begin{cases} 0 \\ k_n \left[V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right] V_{DS} \\ \frac{k_n}{2} (V_{GS} - V_{TN})^2 \end{cases}} \right\} k_n = \frac{W}{L} \mu_n C_{ox}$$

NFET Voltage Amplifier and Inverter

 

We need to find the relation between the output and the input voltage

1) $V_{IN} < V_{TN}$

The FET is in cut-off regime and $I_D = 0$ and consequently $V_{OUT} = V_{DD}$



2) $V_{IN} > V_{TN}$

The FET is turned on and $I_D \neq 0$ and consequently $V_{OUT} = V_{DD} - I_D R < V_{DD}$

$V_{OUT} > V_{IN} - V_{TN}$ (Saturation)

$V_{OUT} < V_{IN} - V_{TN}$ (Linear)

  
NFET Voltage Amplifier and Inverter: A Graphical Solution



$$I_D = \frac{V_{DD} - V_{OUT}}{R}$$

$$I_D = \begin{cases} 0 & \text{For } V_{IN} < V_{TN} \\ k_n \left[V_{IN} - V_{TN} - \frac{V_{OUT}}{2} \right] V_{OUT} & \text{For } 0 \leq V_{OUT} \leq V_{IN} - V_{TN} \\ \frac{k_n}{2} (V_{IN} - V_{TN})^2 & \text{For } 0 \leq V_{IN} - V_{TN} \leq V_{OUT} \end{cases} \quad \left\{ k_n = \frac{W}{L} \mu_n C_{ox} \right.$$

 NFET Voltage Amplifier and Inverter: Transfer Curve




1) Assume the FET is in the saturation regime:

$$I_D = \frac{k_n}{2} (V_{IN} - V_{TN})^2$$

$$I_D = \frac{V_{DD} - V_{OUT}}{R}$$

Answer is:
 
$$V_{OUT} = V_{DD} - \frac{Rk_n}{2} (V_{IN} - V_{TN})^2$$




But the assumption that the FET is in saturation is only valid provided that:

$$V_{DS} > V_{GS} - V_{TN}$$

$$\Rightarrow V_{OUT} > V_{IN} - V_{TN}$$

 NFET Voltage Amplifier and Inverter: Transfer Curve




2) Now assume the FET is in the linear regime:

$$I_D = k_n \left[V_{IN} - V_{TN} - \frac{V_{OUT}}{2} \right] V_{OUT}$$

$$I_D = \frac{V_{DD} - V_{OUT}}{R}$$

 Answer can be found by solving the above two equations for V_{OUT} vs V_{IN}




A high input voltage produces a low output voltage

A low input voltage produces a high output voltage

The device can therefore be used as a logical inverter!

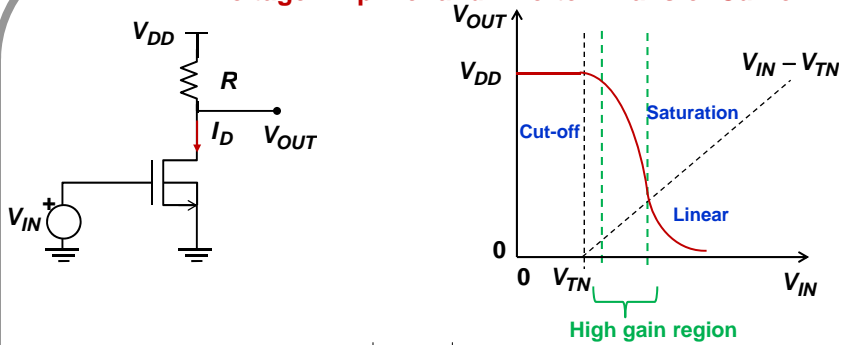NFET Voltage Amplifier and Inverter: Transfer Curve




In the high gain region, the slope $\left| \frac{dV_{OUT}}{dV_{IN}} \right|$ can be much larger than unity!

This means a small change in the input voltage will produce a large change in the output voltage

The circuit can therefore be used as a voltage amplifier!

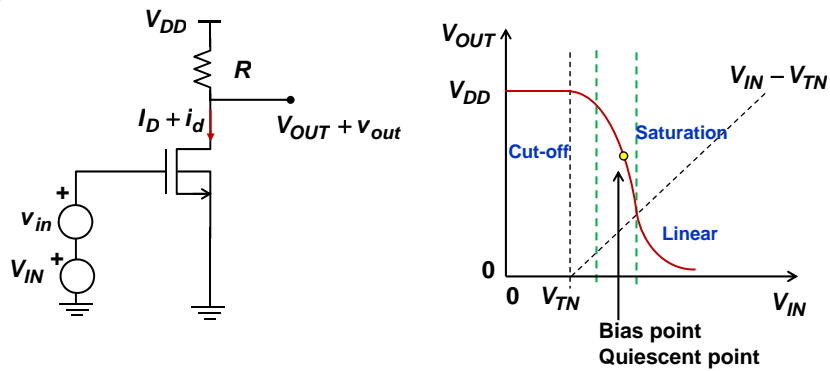NFET Common Source (CS) Voltage Amplifier




We need better techniques to calculate the voltage gain of such amplifier circuits

We need small signal models of the FETs!


NFET Model with Channel Length Modulation Included

We will often use the following current model:
 
$$I_D = \begin{cases} 0 & \text{For } V_{GS} < V_{TN} \\ & \text{(Cut-off region)} \\ k_n \left[V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right] V_{DS} (1 + \lambda_n V_{DS}) & \text{For } 0 \leq V_{DS} \leq V_{GS} - V_{TN} \\ & \text{(Linear region)} \\ \frac{k_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS}) & \text{For } 0 \leq V_{GS} - V_{TN} \leq V_{DS} \\ & \text{(Saturation region)} \end{cases}$$




NFET Small Signal Model – Part I

 


$$\begin{aligned} i_D &= I_D + i_d \\ &= I_D + \frac{\partial I_D}{\partial V_{GS}} v_{gs} \\ &= I_D + g_m v_{gs} \end{aligned}$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$


Transconductance

 

NFET Small Signal Model – Part II

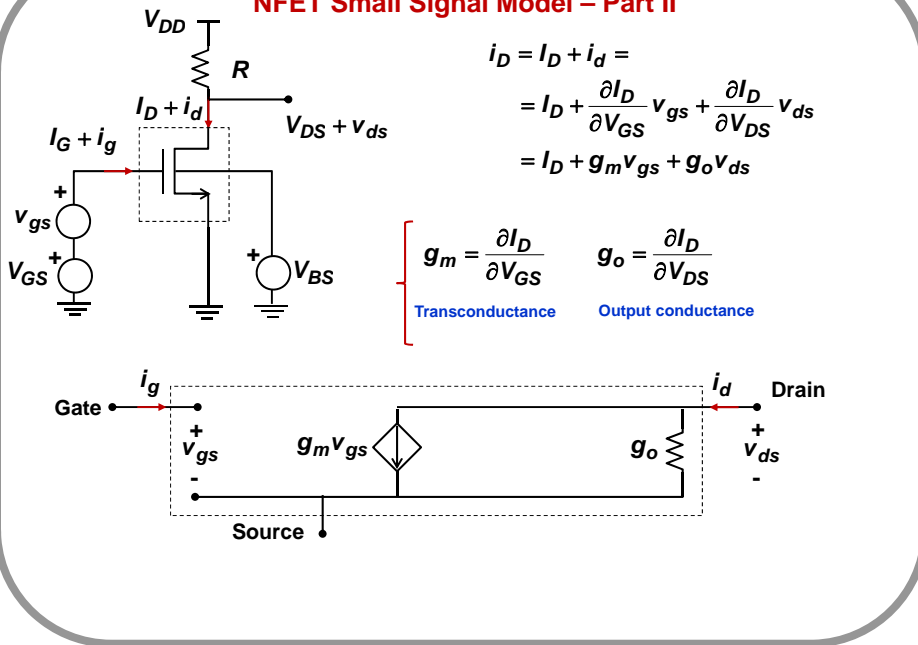


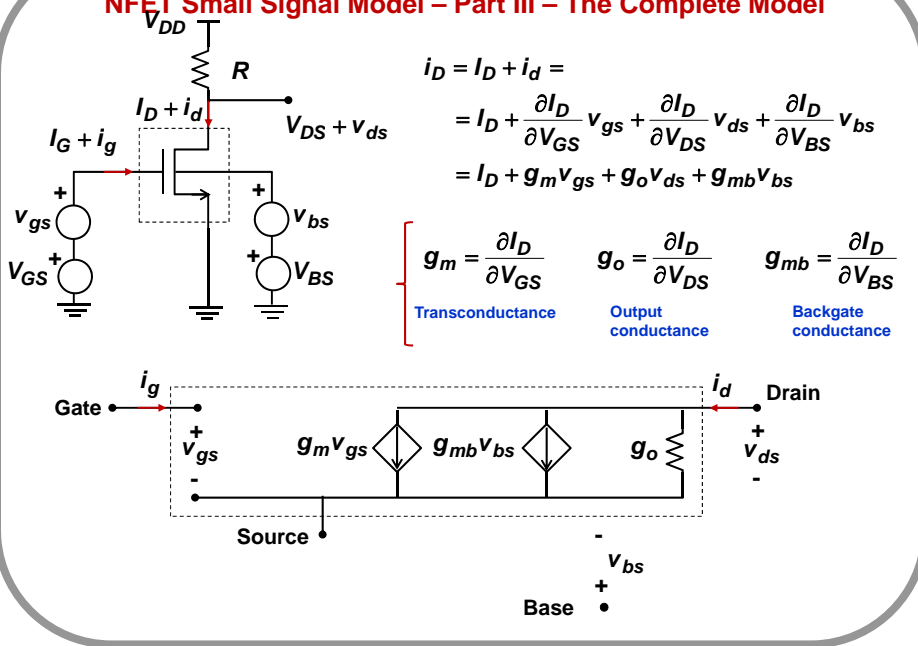NFET Small Signal Model – Part III – The Complete Model



NFET Model
 
$$I_D = \begin{cases} 0 & \text{For } V_{GS} < V_{TN} \\ & \text{(Cut-off region)} \\ k_n \left[V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right] V_{DS} (1 + \lambda_n V_{DS}) & \text{For } 0 \leq V_{DS} \leq V_{GS} - V_{TN} \\ & \text{(Linear region)} \\ \frac{k_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS}) & \text{For } 0 \leq V_{GS} - V_{TN} \leq V_{DS} \\ & \text{(Saturation region)} \end{cases}$$



$$g_m = \frac{\partial I_D}{\partial V_{GS}} \quad \text{Transconductance}$$

$$g_o = \frac{\partial I_D}{\partial V_{DS}} \quad \text{Output conductance}$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} \quad \text{Backgate conductance}$$


NFET: Transconductance

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

Saturation: $g_m = \frac{\partial I_D}{\partial V_{GS}} = k_n (V_{GS} - V_{TN}) (1 + \lambda_n V_{DS}) = \sqrt{2k_n I_D (1 + \lambda_n V_{DS})}$

Linear: $g_m = \frac{\partial I_D}{\partial V_{GS}} = k_n V_{DS} (1 + \lambda_n V_{DS})$

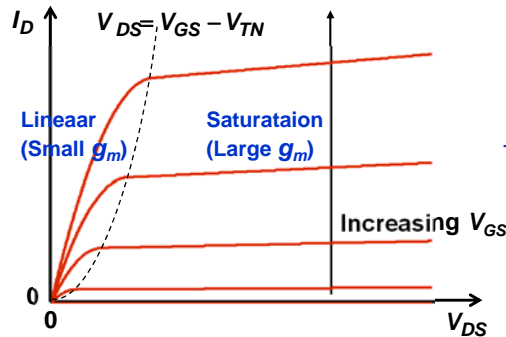Increases only as the square-root of the current



To achieve large g_m operate in the saturation region


NFET: Transconductance

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

Saturation: $g_m = \frac{\partial I_D}{\partial V_{GS}} = k_n (V_{GS} - V_{TN})(1 + \lambda_n V_{DS}) = \sqrt{2k_n I_D (1 + \lambda_n V_{DS})}$

Linear: $g_m = \frac{\partial I_D}{\partial V_{GS}} = k_n V_{DS} (1 + \lambda_n V_{DS})$

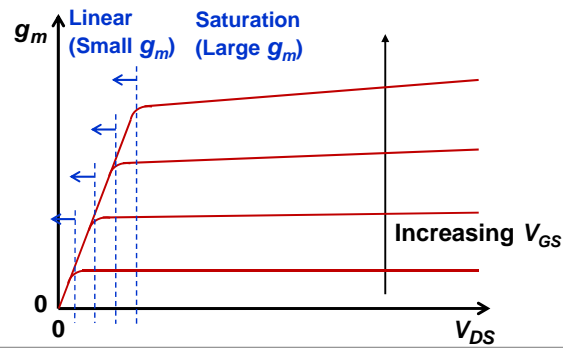Increases only as the square-root of the current




NFET: Output Conductance

$$g_o = \frac{\partial I_D}{\partial V_{DS}}$$

Saturation: $g_o = \frac{\partial I_D}{\partial V_{DS}} = \frac{k_n}{2} (V_{GS} - V_{TN})^2 \lambda_n = \lambda_n I_D$

 Linear: $g_o = \frac{\partial I_D}{\partial V_{DS}} = \lambda_n I_D + k_n (V_{GS} - V_{TN} - V_{DS})(1 + \lambda_n V_{DS})$




NFET: Output Conductance

$$g_o = \frac{\partial I_D}{\partial V_{DS}}$$

Saturation: $g_o = \frac{\partial I_D}{\partial V_{DS}} = \frac{k_n}{2} (V_{GS} - V_{TN})^2 \lambda_n = \lambda_n I_D$

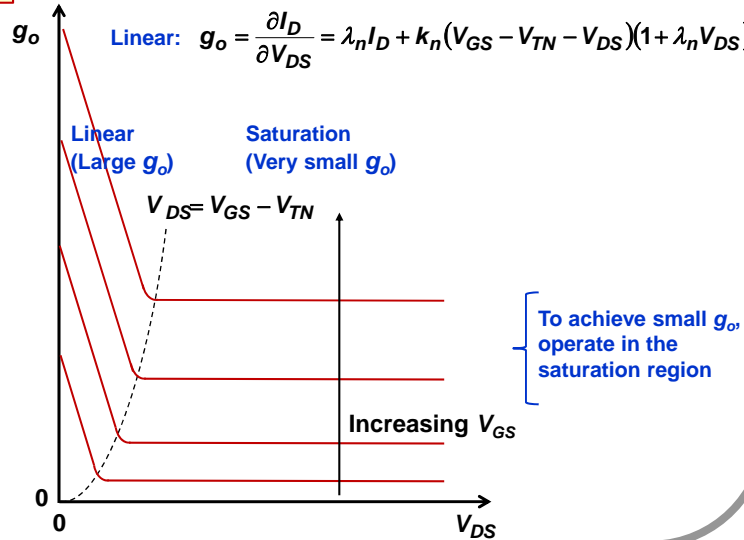Linear: $g_o = \frac{\partial I_D}{\partial V_{DS}} = \lambda_n I_D + k_n (V_{GS} - V_{TN} - V_{DS})(1 + \lambda_n V_{DS})$



NFET: Backgate Conductance

Recall that the threshold voltage depends on the source-to-bulk voltage V_{SB} :

$$V_{TN} = V_{TN}(V_{SB} = 0) + \gamma_n (\sqrt{-2\phi_p + V_{SB}} - \sqrt{-2\phi_p})$$


$$\gamma_n = \frac{\sqrt{2 \epsilon_s q N_a}}{C_{ox}} = \text{Backgate effect (or the body effect) parameter}$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} = \frac{\partial I_D}{\partial V_{TN}} \frac{\partial V_{TN}}{\partial V_{BS}}$$

Saturation: $g_{mb} = \frac{\partial I_D}{\partial V_{TN}} \frac{\partial V_{TN}}{\partial V_{BS}} = - \frac{\partial I_D}{\partial V_{GS}} \frac{\partial V_{TN}}{\partial V_{BS}} = g_m \frac{\gamma_n}{2\sqrt{-2\phi_p - V_{BS}}}$

Linear: $g_{mb} = \frac{\partial I_D}{\partial V_{TN}} \frac{\partial V_{TN}}{\partial V_{BS}} = - \frac{\partial I_D}{\partial V_{GS}} \frac{\partial V_{TN}}{\partial V_{BS}} = g_m \frac{\gamma_n}{2\sqrt{-2\phi_p - V_{BS}}}$

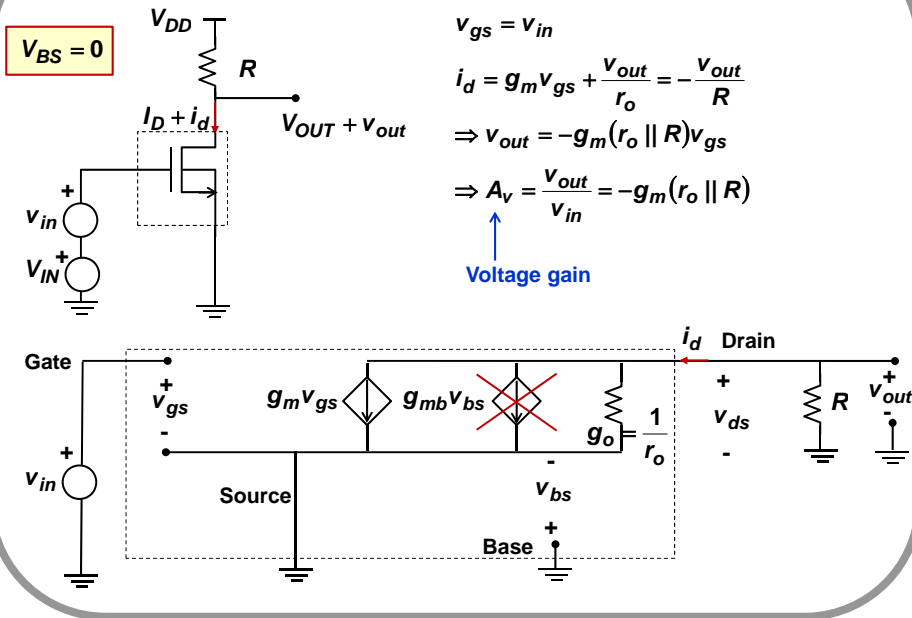NFET Common Source (CS) Voltage Amplifier





A Note on Small Signal Modeling

When making a small signal model out of a complicated nonlinear signal remember that:

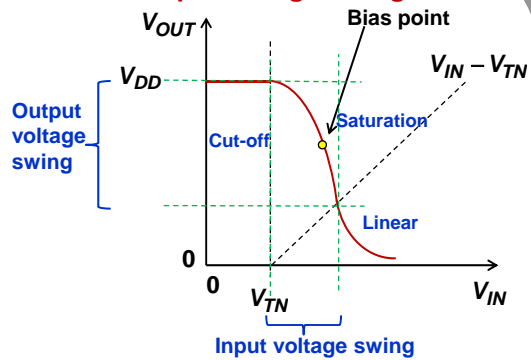 - 1) All DC voltage sources in the circuit become short circuits
- 2) All DC current sources in the circuit become open circuits

NFET CS Amplifier: Limits of Output Voltage Swing





Minimum output voltage and maximum input voltage:

If the output voltage becomes too small (happens when the input voltage becomes too large), the FET will go into the **linear region** (in the linear region the gain is small)

Maximum output voltage and minimum input voltage:

If the input voltage becomes too small the FET will go into **cut-off**

The Diode-Connected NFET

  


The gate and the drain of the FET are tied together

Since:

$$\begin{aligned} V_{DG} &= 0 \\ \Rightarrow V_{DS} &= V_{GS} \\ \Rightarrow V_{DS} &> V_{GS} - V_{TN} \end{aligned}$$

\Rightarrow The FET is always operating in saturation when not in cut-off (i.e. provided $V_{GS} > V_{TN}$)

The Diode-Connected NFET

 

Finding V_{OUT} :


$$I_D = \frac{k_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS})$$

$$\Rightarrow \frac{k_n}{2} (V_{OUT} - V_{TN})^2 (1 + \lambda_n V_{OUT}) = \frac{V_{DD} - V_{OUT}}{R}$$


$$\Rightarrow \frac{k_n}{2} (V_{OUT} - V_{TN})^2 \approx \frac{V_{DD} - V_{OUT}}{R}$$

The above equation can be solved for V_{OUT}

NFET: Capacitances

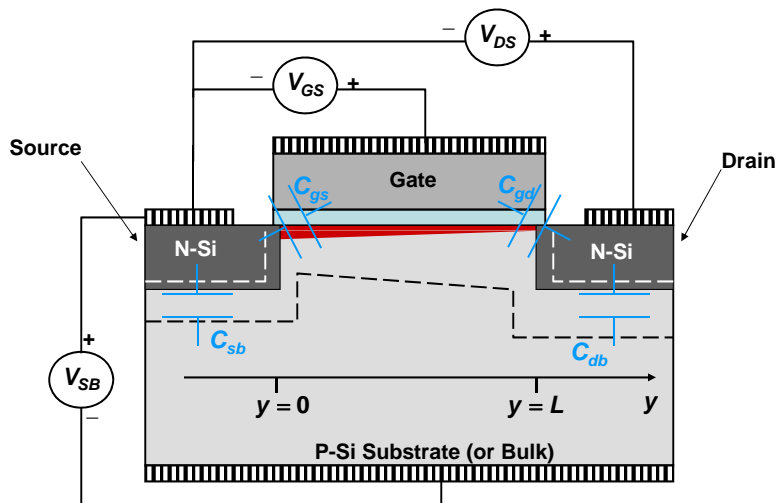

NFET: High Frequency Small Signal Model

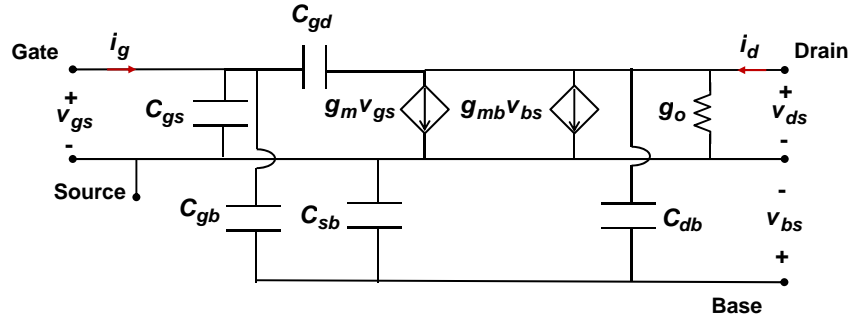

NFET Gate Charge

The gate charge consists of the image charge due to:

- 1) The inversion layer charge
 - 2) The depletion layer charge
- $$Q_G = -(Q_N + Q_B)$$

Inversion layer charge Q_N (units: Coulombs):

$$Q_N = -WC_{ox} \int_0^L (V_{GS} - V_{TN} - V_{CS}(y)) dy = -WC_{ox} \int_0^{V_{DS}} (V_{GS} - V_{TN} - V_{CS}) \frac{dy}{V_{CS}} dV_{CS}$$


Recall that:

$$I_D = W \mu_n C_{ox} (V_{GS} - V_{TN} - V_{CS}(y)) \frac{dV_{CS}(y)}{dy}$$

$$\Rightarrow \frac{dy}{dV_{CS}} = \frac{W \mu_n C_{ox} (V_{GS} - V_{TN} - V_{CS}(y))}{I_D}$$

$$Q_N = -\frac{\mu_n}{I_D} (WC_{ox})^2 \int_0^{V_{DS}} (V_{GS} - V_{TN} - V_{CS})^2 dV_{CS}$$
 
$$= \frac{\mu_n}{3I_D} (WC_{ox})^2 \left[(V_{GS} - V_{TN} - V_{DS})^3 - (V_{GS} - V_{TN})^3 \right]$$



NFET Gate Charge

Inversion layer charge Q_N :

$$Q_N = \frac{\mu_n}{3I_D} (WC_{ox})^2 \left[(V_{GS} - V_{TN} - V_{DS})^3 - (V_{GS} - V_{TN})^3 \right]$$

In saturation ($V_{DS} > V_{GS} - V_{TN}$) but the inversion charge remains fixed at the value when $V_{DS} = V_{GS} - V_{TN}$ because of pinch-off:

$$Q_N = -\frac{2}{3} WLC_{ox} (V_{GS} - V_{TN})$$

Channel depletion layer charge Q_B (units: Coulombs):

$$\begin{aligned} Q_B &= -W \int_0^L \sqrt{2 \epsilon_s q N_a (-2\phi_p + V_{CB}(y))} dy \\ &= -W \int_0^L \sqrt{2 \epsilon_s q N_a (-2\phi_p + V_{CS}(y) + V_{SB})} dy \\ &\approx -W \int_0^L \sqrt{2 \epsilon_s q N_a (-2\phi_p + V_{SB})} dy \\ &= -WL \sqrt{2 \epsilon_s q N_a (-2\phi_p + V_{SB})} \end{aligned}$$

Independent of y ;
consistent with our
earlier approximation
for current

NFET Capacitances in Saturation: A Simple Model

$$Q_G = -(Q_N + Q_B)$$

$$C_{gs} = \left. \frac{\partial Q_G}{\partial V_{GS}} \right|_{V_{DS}, V_{SB}} = \frac{2}{3} WLC_{ox}$$

$$C_{gd} = \left. \frac{\partial Q_G}{\partial V_{GD}} \right|_{V_{GS}, V_{SB}} = - \left. \frac{\partial Q_G}{\partial V_{DS}} \right|_{V_{GS}, V_{SB}} = 0$$



$$C_{gb} = - \left. \frac{\partial Q_B}{\partial V_{GB}} \right|_{V_{SB}, V_{DS}} = - \left. \frac{\partial Q_B}{\partial V_{GS}} \right|_{V_{SB}, V_{DS}} = 0$$

$$C_{sb} = C_{j-sb} - \left. \frac{\partial Q_B}{\partial V_{SB}} \right|_{V_{GS}, V_{DS}} = C_{j-sb} + \left. \frac{\partial Q_N}{\partial V_{SB}} \right|_{V_{GS}, V_{DS}} = C_{j-sb} + \frac{2}{3} WLC_{ox} \frac{\gamma_n}{2\sqrt{-2\phi_p + V_{SB}}}$$


↑
Source-bulk PN junction capacitance

$$C_{db} = C_{j-db} + \left. \frac{\partial Q_N}{\partial V_{DB}} \right|_{V_{DS}, V_{GD}} = C_{j-db}$$

↑
Drain-bulk PN junction capacitance

  

 Including Parasitic and Overlap Capacitances




In Saturation:

$$C_{gs} = \left. \frac{\partial Q_G}{\partial V_{GS}} \right|_{V_{DS}, V_{SB}} = \frac{2}{3} WLC_{ox} + WC_{ov} + WC_p \neq \frac{2}{3} WLC_{ox}$$

$$C_{gd} = \left. \frac{\partial Q_G}{\partial V_{GD}} \right|_{V_{GS}, V_{SB}} = WC_{ov} + WC_p \neq 0$$

PFET Voltage Amplifier and Inverter

 


We need to find the relation between the output and the input voltage

$I_D < 0$ and actual current is flowing out of the drain

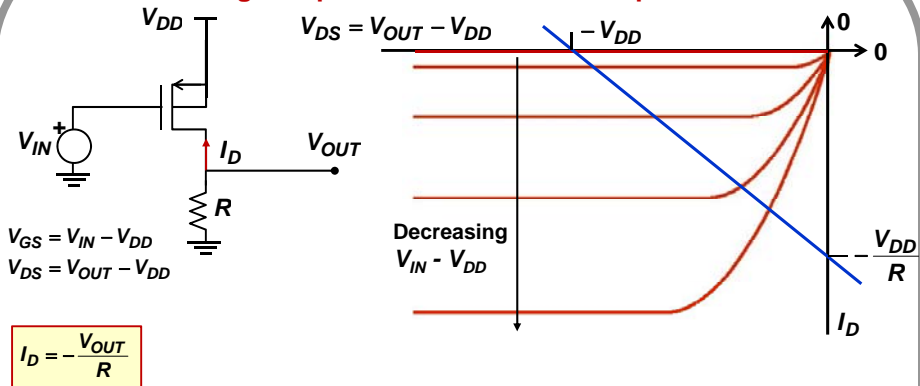- 1) $V_{GS} = V_{IN} - V_{DD} > V_{TP}$
The FET is in cut-off regime and $I_D = 0$ and consequently $V_{OUT} = 0$
- 2) $V_{GS} = V_{IN} - V_{DD} < V_{TP}$
The FET is turned on and $I_D \neq 0$ and consequently $V_{OUT} = -I_D R$


PFET Voltage Amplifier and Inverter: A Graphical Solution



$$I_D = \begin{cases} 0 & \text{For } V_{IN} - V_{DD} > V_{TP} \\ -k_p \left[V_{IN} - V_{DD} - V_{TP} - \frac{V_{OUT} - V_{DD}}{2} \right] (V_{OUT} - V_{DD}) & \text{For } 0 \geq V_{OUT} - V_{DD} \geq V_{IN} - V_{DD} - V_{TP} \\ -\frac{k_p}{2} (V_{IN} - V_{DD} - V_{TP})^2 & \text{For } 0 \geq V_{IN} - V_{DD} - V_{TP} \geq V_{OUT} - V_{DD} \end{cases}$$

$k_p = \frac{W}{L} \mu_p C_{ox}$

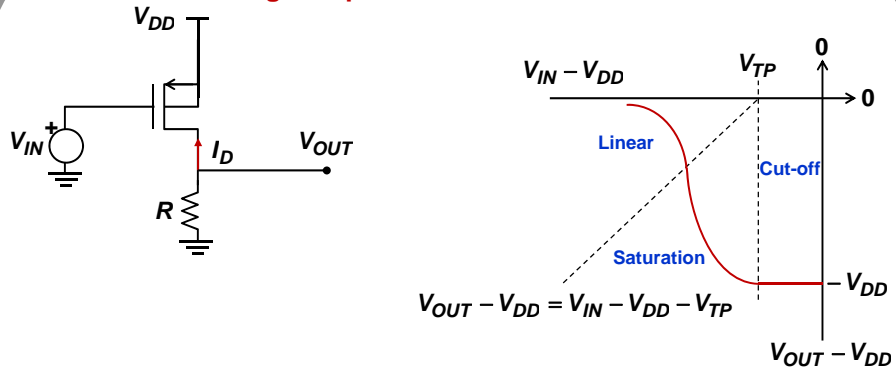PFET Voltage Amplifier and Inverter: Transfer Curve




A high input voltage produces a low output voltage

A low input voltage produces a high output voltage

The device can therefore be used as a logical inverter!

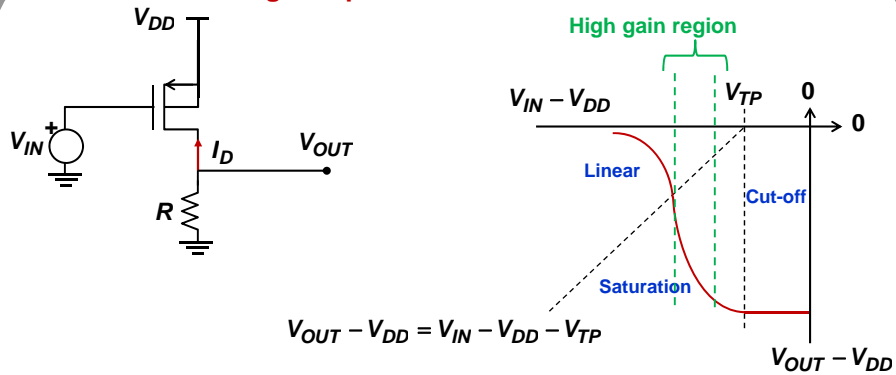PFET Voltage Amplifier and Inverter: Transfer Curve




In the high gain region, the slope $\left| \frac{dV_{OUT}}{dV_{IN}} \right|$ can be larger than unity!


This means a small change in the input voltage will produce a large change in the output voltage

The circuit can therefore be used as a voltage amplifier!

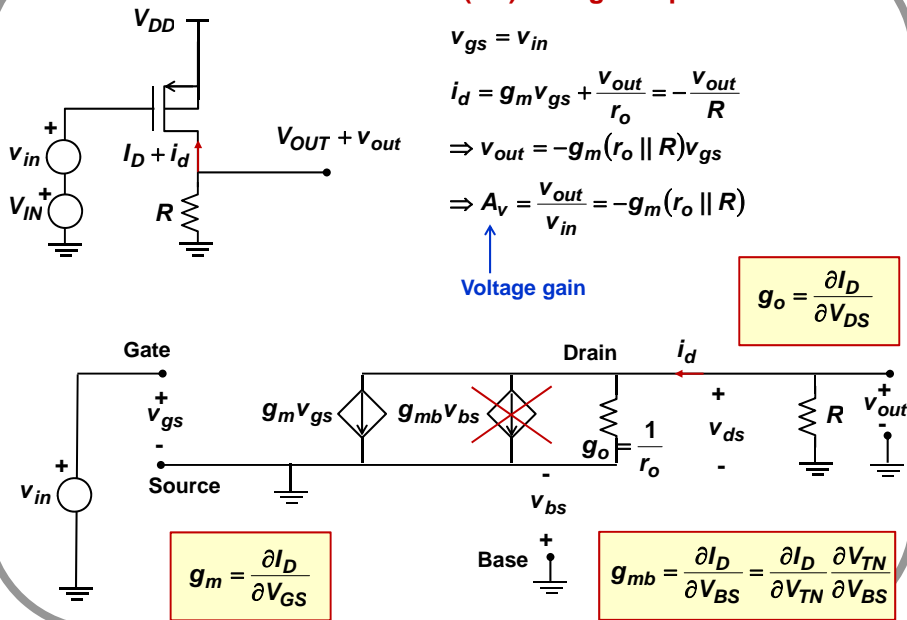PFET Common Source (CS) Voltage Amplifier



The Standard CMOS Process

 

The NFETs and the PFETs can be realized on the same P-substrate by making a N-well inside the substrate for the PFETs

The Double-Well CMOS Process

