

Lecture 13


Biasing and Loading Single Stage FET Amplifiers

The Building Blocks of Analog Circuits - III

In this lecture you will learn:

- Current and voltage biasing of circuits
- Current sources and sinks in CS, CG, and CD amplifiers


The Common Source Amplifier

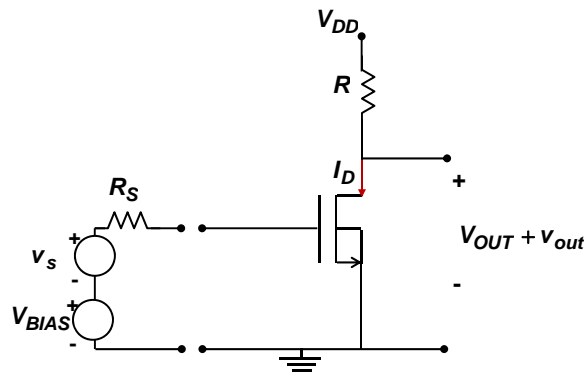

Open circuit voltage gain:

$$A_v = \frac{v_{out}}{v_{in}} = -\frac{i_d R}{v_{in}} = -g_m(r_o \parallel R)$$

The Common Source Amplifier: Problems

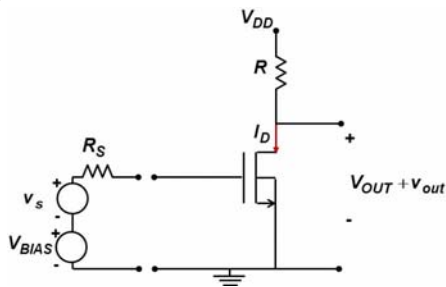

Open circuit voltage gain:

$$A_v = \frac{V_{out}}{V_{in}} = -g_m(r_o \parallel R)$$

In saturation:

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \sqrt{2k_n I_D (1 + \lambda_n V_{DS})}$$



To achieve large gain one needs:

- 1) A large DC current bias I_D in order to get a large g_m
- 2) A large value of the resistor R

Both the above requirements cannot be met easily simultaneously:

- Not easy to realize large resistors in micro-chips
- A large resistor R will limit the maximum value of the DC current bias I_D (because the potential drop $I_D R$ can become large enough to put the FET in the linear region where g_m and the gain will be small)

The Digital Logic Inverter: Problems

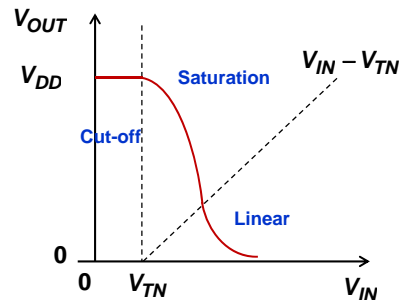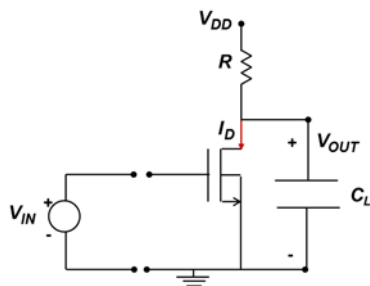


To achieve fast switching one needs:

- 1) A small resistor (because then the RC_L charging time will be smaller when the output switches from "0" to "1")

But

- A small resistor will require a very large current (to achieve a large potential drop across it) when the input is "1", and the NFET is turned on, and the output need to be low or "0" – and this means more power dissipation
- When the input is "1", and the NFET is turned on, there is constant static power dissipation

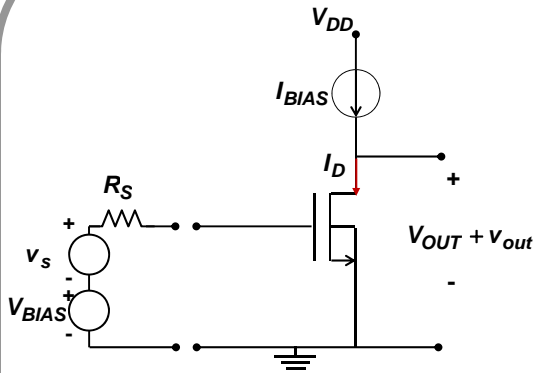The Common Source Amplifier with a Current Source



What is needed is an ideal current source in the drain that can supply a large DC current and at the same time has a large small signal resistance


The incremental (or differential or small signal) resistance looking into an ideal current source is infinite

$$A_v = \frac{v_{out}}{v_{in}} = -g_m r_o$$

An ideal current source, of course, does not exist


But one can certainly do much better than using a resistor in the drain

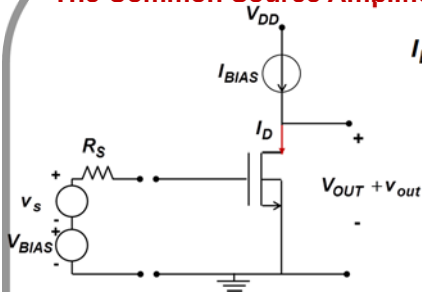The Common Source Amplifier with a Current Source: DC Biasing





$$I_D = I_{BIAS} = \frac{W}{2L} \mu_n C_{ox} (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS})$$

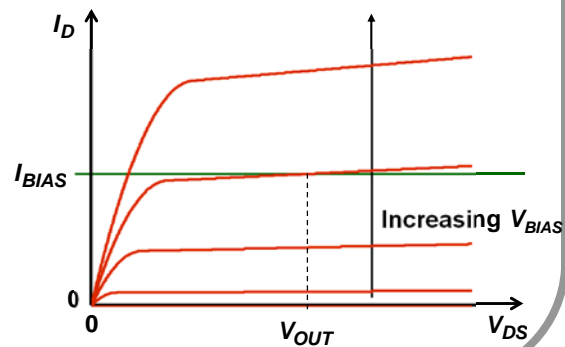The above equation determines $V_{DS} = V_{OUT}$ for a given value of $V_{GS} = V_{BIAS}$



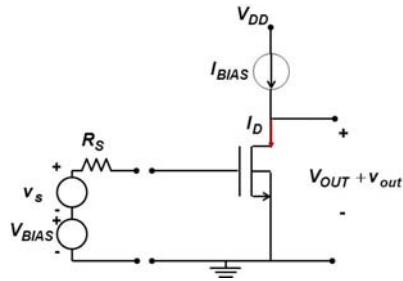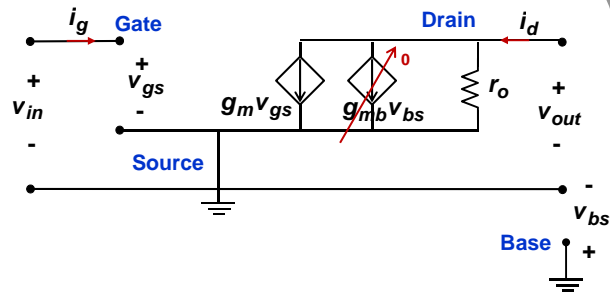The CS Amplifier with a Current Source: Small Signal Analysis




Open circuit voltage gain:

$$A_v = \frac{v_{out}}{v_{in}} = -g_m r_o$$

Output resistance:



$$R_{out} = r_o$$

Large Signal Model of a Current Source

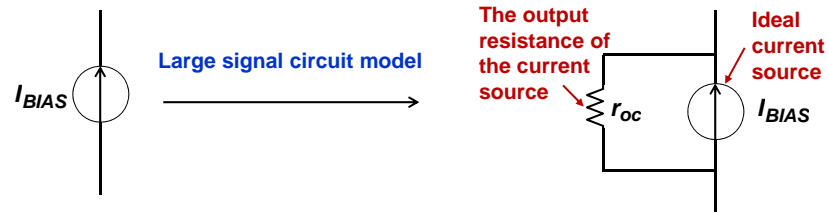


A current source

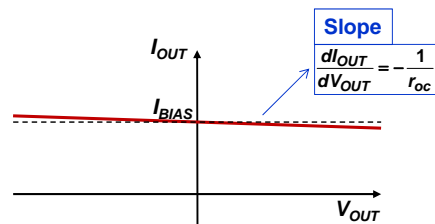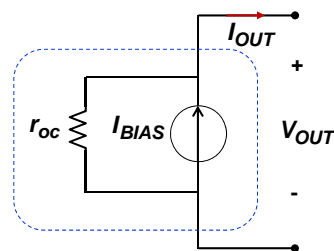- A large signal model of a current source
- r_{oc} is large for a good current source and **infinite** for an **ideal current source**




One can have any voltage at the at the output terminals of a good current source and the current delivered will remain mostly constant

Small Signal Model of a Current Source

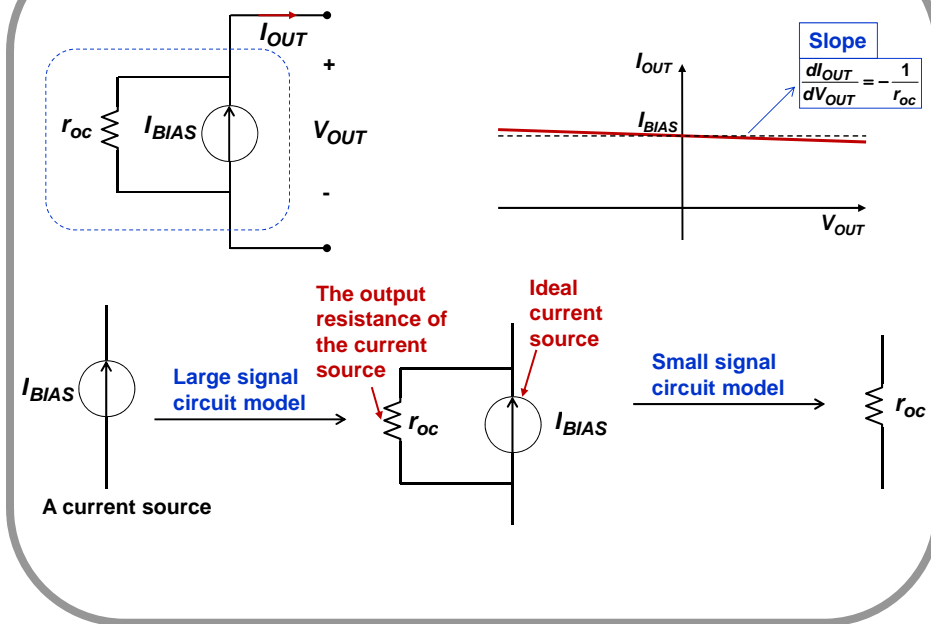


Large Signal Model of a Current Sink

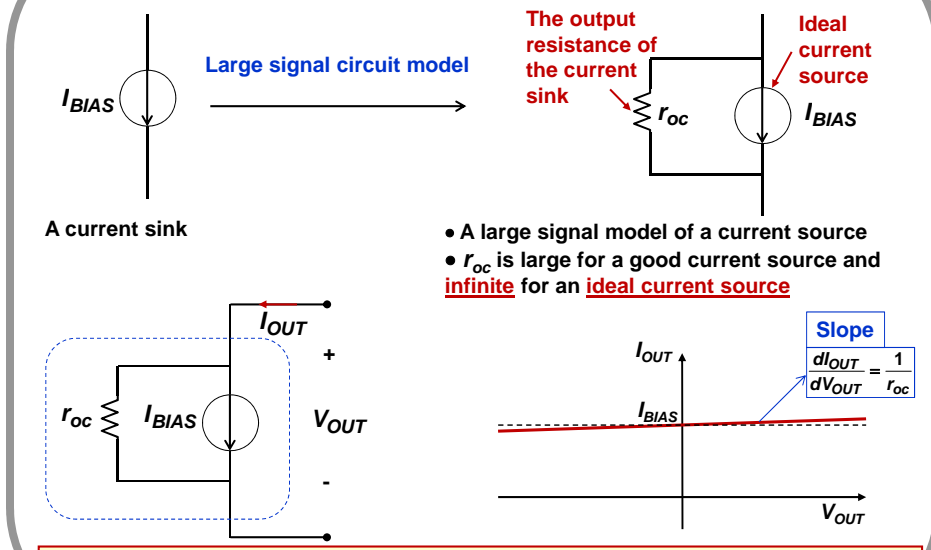


- A large signal model of a current source
- r_{oc} is large for a good current source and infinite for an ideal current source

One can have any voltage at the at the output terminals of a good current sink and the current dinked will remain mostly constant

Small Signal Model of a Current Sink

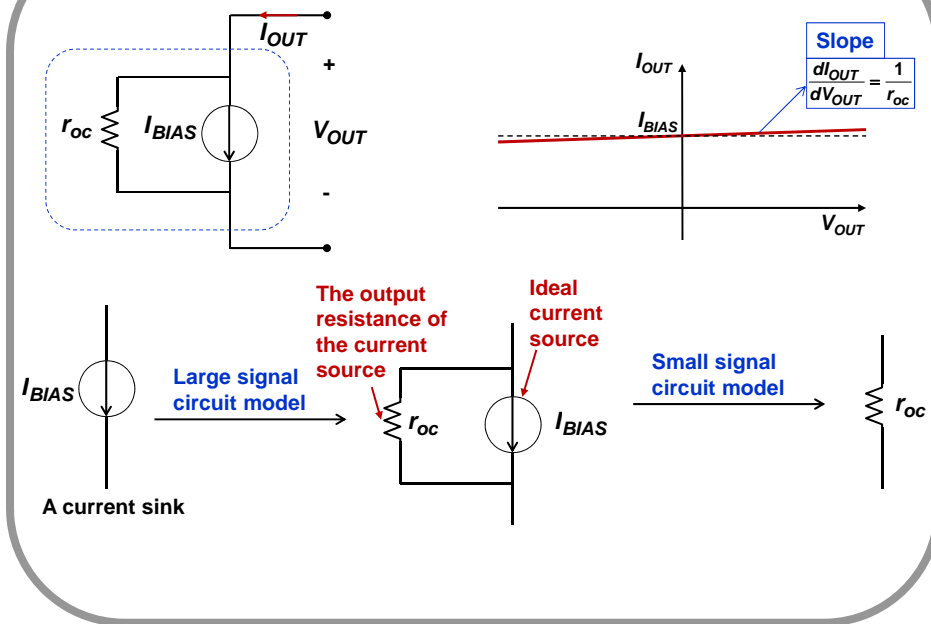


PFET Loaded NFET Common Source Amplifier

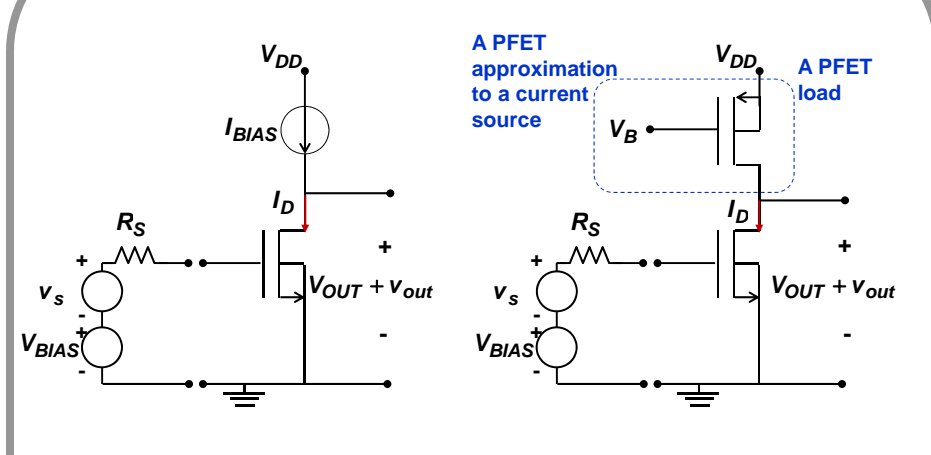


An ideal current source, of course, does not exist
 But one can certainly do much better than using a resistor in the drain
Use a PFET!

Current Sinks and NFET Transistors

Current Sink:

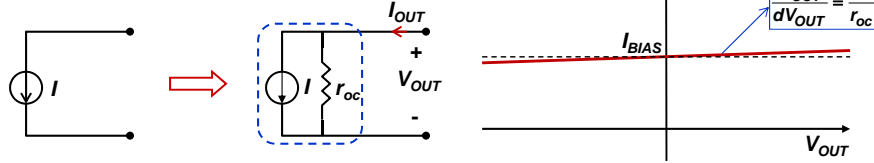


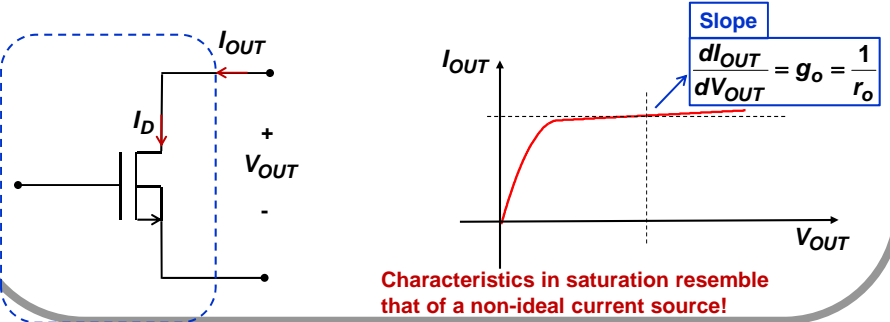One can have any voltage at the at the output terminals of a good current sink and the current sinked will remain mostly constant




Current Sources and PFET Transistors


Current Sources:

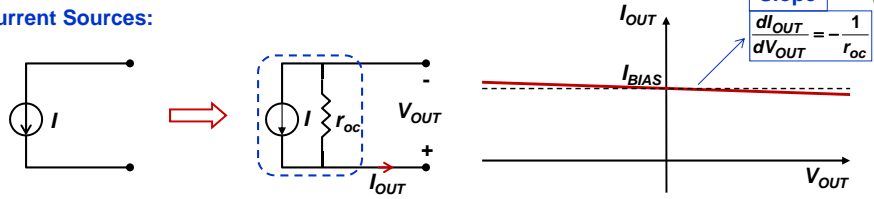

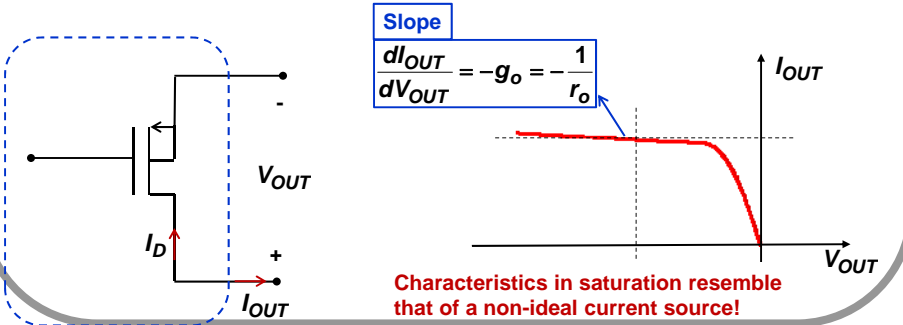One can have any voltage at the at the output terminals of a good current source and the current delivered will remain mostly constant




PFET Loaded NFET: Large Signal Analysis

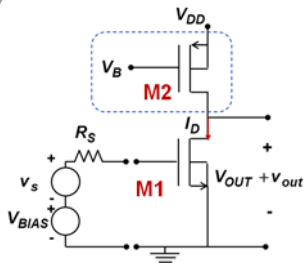

$$V_{DS1} = V_{OUT}$$

$$V_{DS2} = V_{OUT} - V_{DD}$$


$$I_{D1} = I_D = -I_{D2}$$

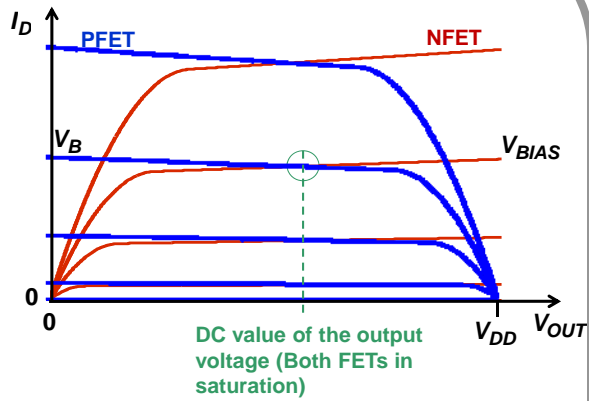

Instead of the resistive load line, we now have the full I_D vs V_{DS} curves of the PFET

The biasing voltages need to be selected carefully, otherwise one of the transistors can go into the linear region!!


PFET Loaded NFET: Large Signal Analysis

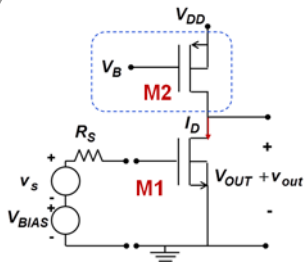

$$V_{DS1} = V_{OUT}$$

$$V_{DS2} = V_{OUT} - V_{DD}$$


$$I_{D1} = I_D = -I_{D2}$$

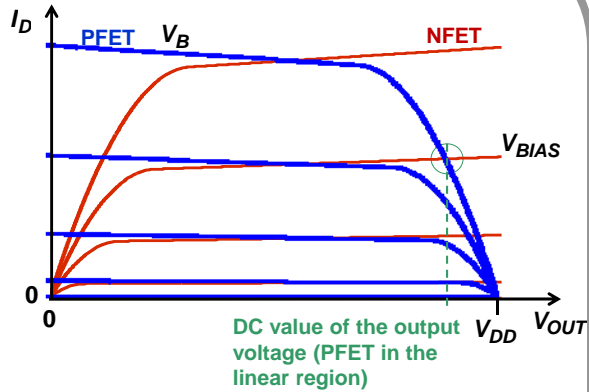

Instead of the resistive load line, we now have the full I_D vs V_{DS} curves of the PMOS

The biasing voltages need to be selected carefully, otherwise one of the transistors can go into the linear region!!

PFET Loaded NFET: Large Signal Analysis

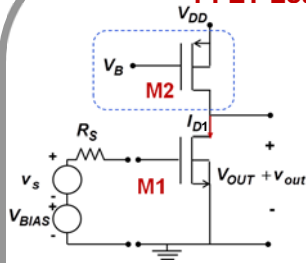

Assuming the biasing is correct, both the FETs are in saturation

Equate the drain current magnitudes of the two FETs

Then the only unknown will be V_{OUT} ; solve for it

Verify that the obtained value of V_{OUT} does indeed result in both the transistors being in saturation

NFET

$$I_{D1} = \frac{k_n}{2} (V_{GS1} - V_{TN})^2 (1 + \lambda_n V_{DS1}) = \frac{k_n}{2} (V_{BIAS} - V_{TN})^2 (1 + \lambda_n V_{OUT})$$

PFET


$$I_{D2} = -\frac{k_p}{2} (V_{GS2} - V_{TP})^2 (1 - \lambda_p V_{DS2}) = -\frac{k_p}{2} (V_B - V_{DD} - V_{TP})^2 (1 - \lambda_p (V_{OUT} - V_{DD}))$$

Equating:

$$I_{D1} = I_D = -I_{D2}$$

$$\Rightarrow \frac{k_n}{2} (V_{BIAS} - V_{TN})^2 (1 + \lambda_n V_{OUT}) = \frac{k_p}{2} (V_B - V_{DD} - V_{TP})^2 (1 + \lambda_p (V_{DD} - V_{OUT}))$$

PFET Loaded NFET: Transfer Curve


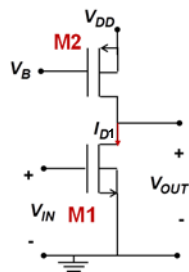


I: $V_{IN} < V_{TN}$
M1 cut-off


II: $V_{IN} > V_{TN}$ & $V_{OUT} > V_{IN} - V_{TN}$ & $V_{OUT} > V_B - V_{TP}$
M1 saturation, M2 Linear

III: $V_{IN} > V_{TN}$ & $V_{OUT} > V_{IN} - V_{TN}$ & $V_{OUT} < V_B - V_{TP}$
M1 saturation, M2 saturation

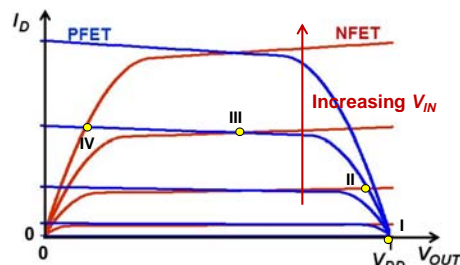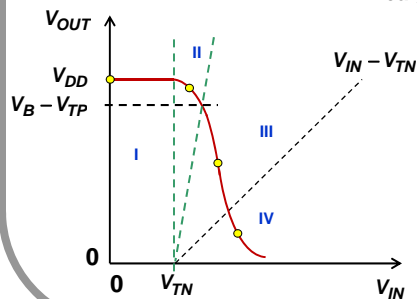
IV: $V_{IN} > V_{TN}$ & $V_{OUT} < V_{IN} - V_{TN}$ & $V_{OUT} < V_B - V_{TP}$
M1 linear, M2 saturation




PFET Loaded NFET: Small Signal Analysis

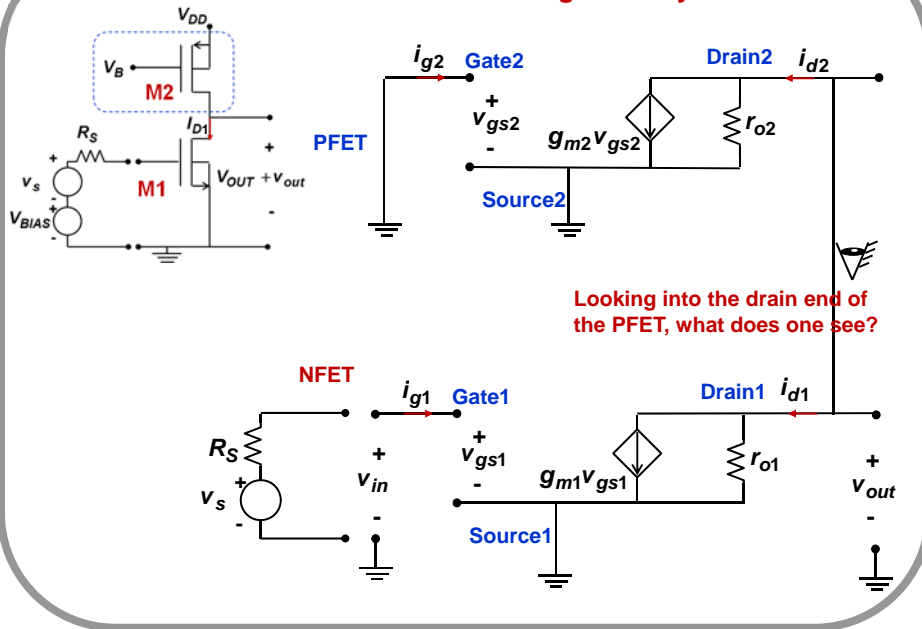

PMOS Loaded NMOS: Small Signal Analysis

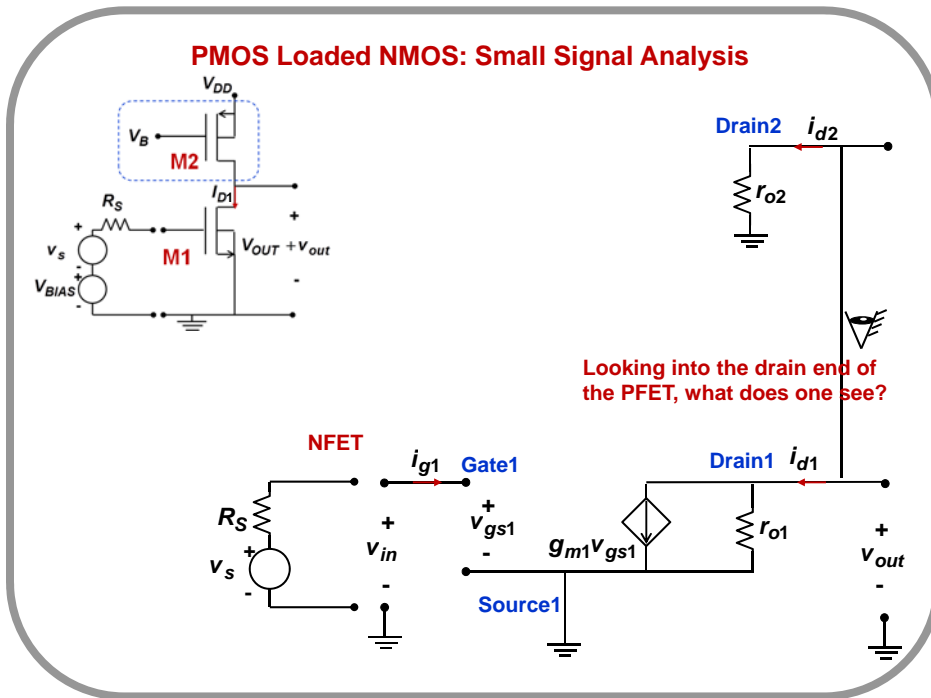

PFET Loaded NFET: Small Signal Analysis

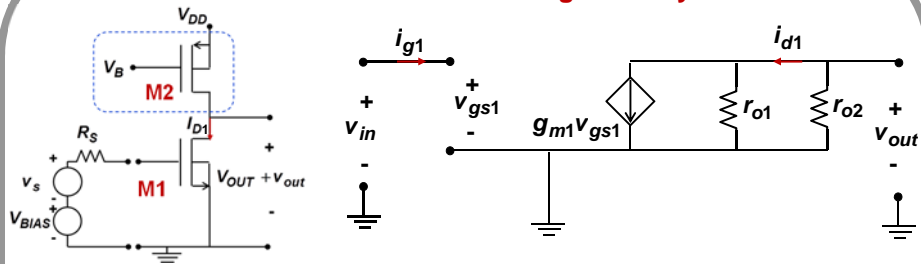


Open circuit voltage gain:

$$A_v = \frac{v_{out}}{v_{in}} = -g_{m1}(r_{o1} \parallel r_{o2})$$

Output resistance:

$$R_{out} = r_{o1} \parallel r_{o2}$$


PFET Loaded NFET: The Cascode PFET Load

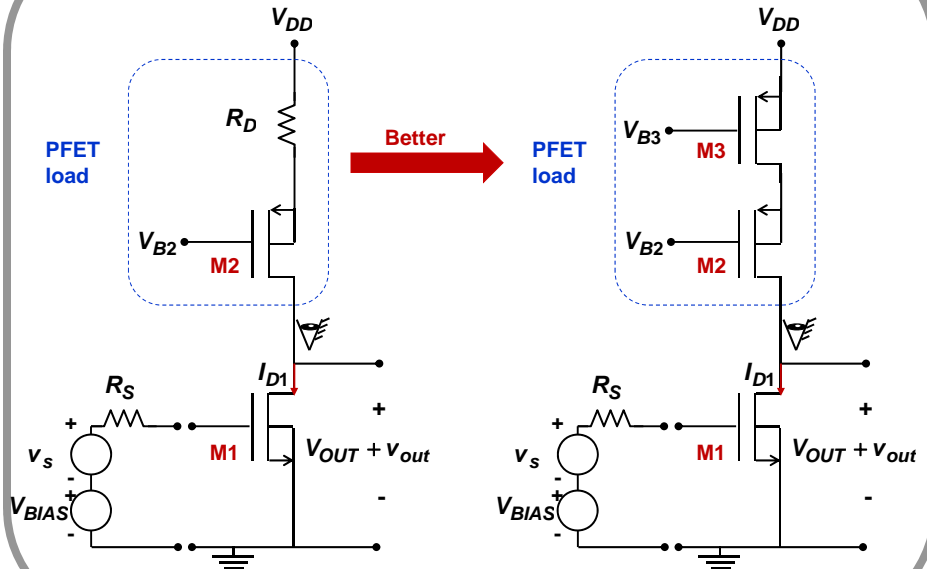


This load has a larger resistance looking into it

This topology is called the "Cascode"


Cascode PFET Load: Small Signal Analysis

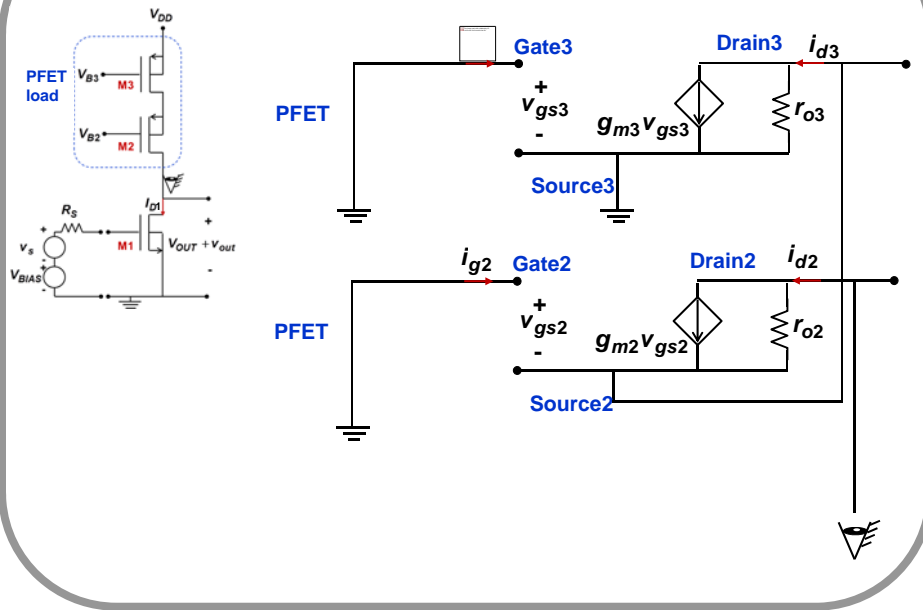

Cascode PFET Load: Small Signal Analysis

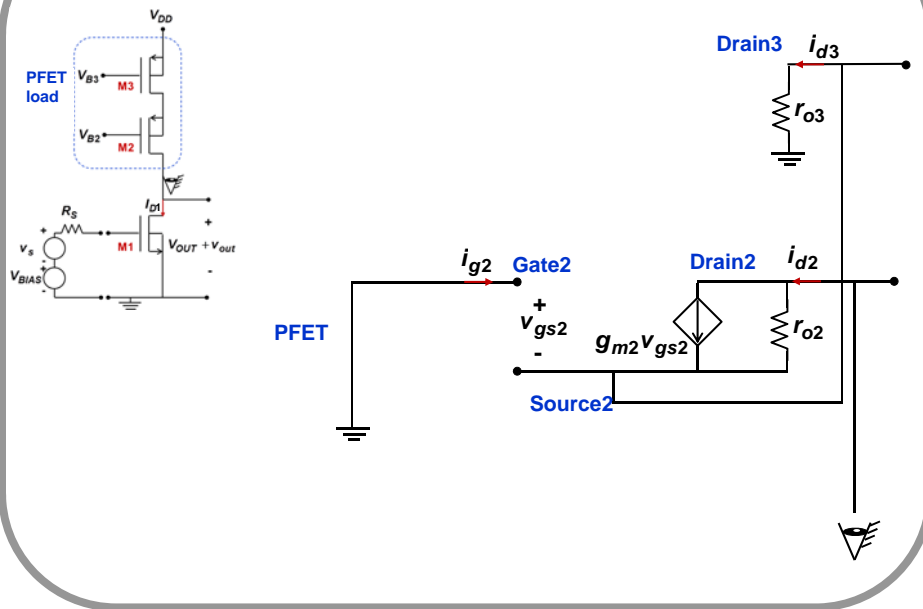

Cascode PFET Load: Small Signal Analysis

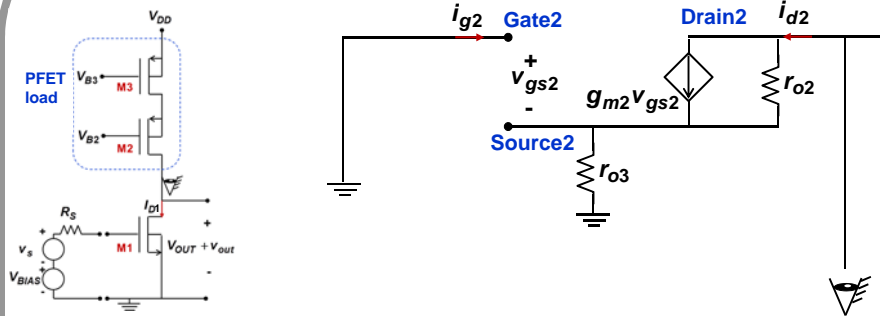


Resistance looking into the current source is:

$$r_{o2} + r_{o3} + g_{m2}r_{o2}r_{o3} = r_{o2} + r_{o3}(1 + g_{m2}r_{o2}) \approx \underline{g_{m2}r_{o2}r_{o3}}$$

Typically a good approximation

Cascode PFET Load: Small Signal Analysis

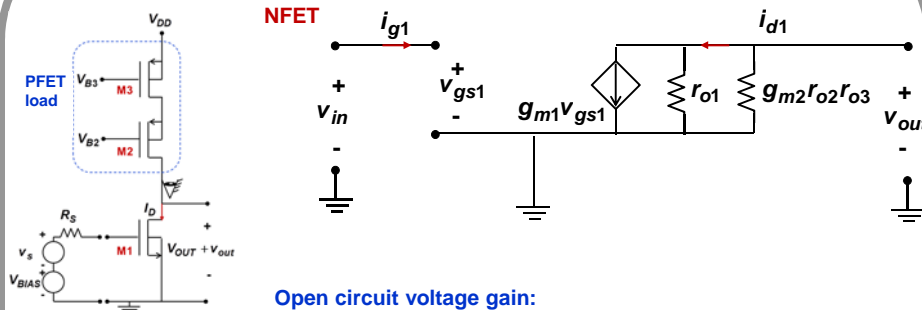

Open circuit voltage gain:

$$A_v = \frac{V_{out}}{V_{in}} = -g_{m1}(r_{o1} \parallel (g_{m2}r_{o2}r_{o3})) \approx \underline{-g_{m1}r_{o1}}$$



Output resistance:

$$R_{out} = r_{o1} \parallel (g_{m2}r_{o2}r_{o3}) \approx \underline{r_{o1}}$$

Typically a good approximation

Typically a good approximation

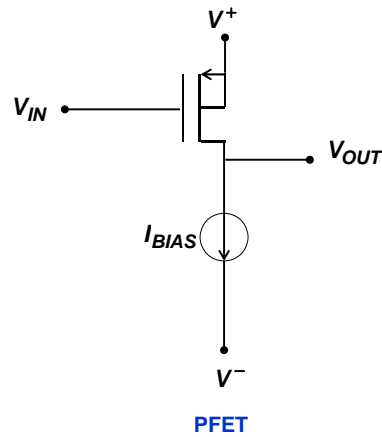
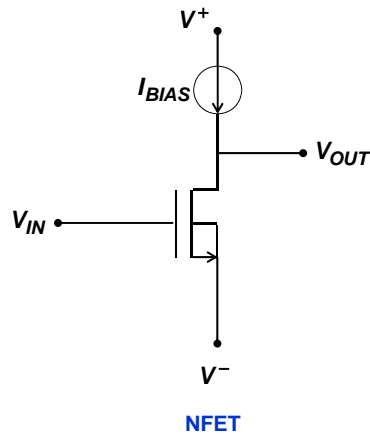
The Common Source Amplifier: General Topology



V^+ is the most positive voltage in the circuit
 V^- is the most negative voltage in the circuit


- Large input resistance
- Large output resistance
- Large voltage gain
- Large current gain
- ⇒ Good transconductance amplifier

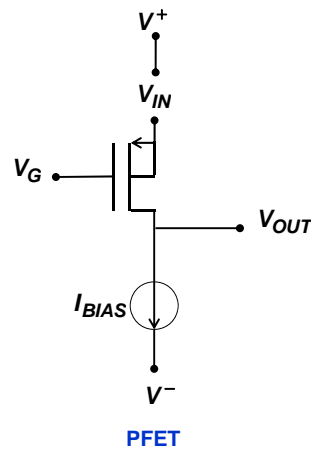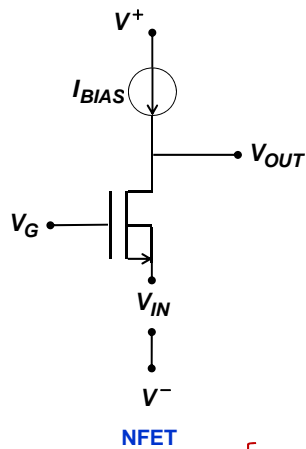The Common Gate Amplifier: General Topology



- Small input resistance
- Large output resistance
- Large voltage gain
- Small (unity) current gain
- ⇒ Good current buffer
- ⇒ Good transimpedance amplifier

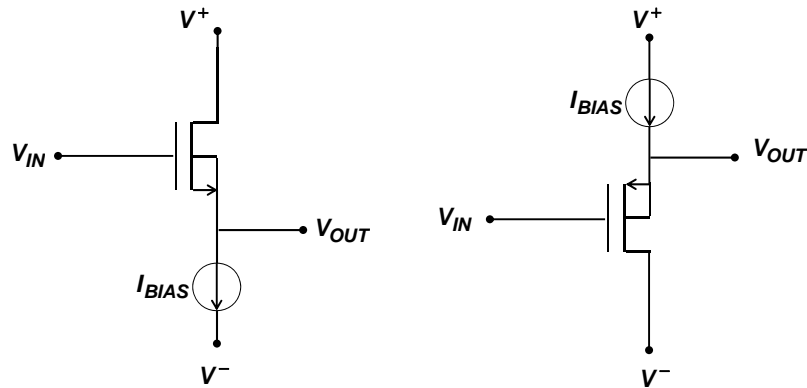The Common Drain Amplifier: General Topology



NFET

PFET

- Large input resistance
- Small output resistance
- Small (less than unity) voltage gain
- Large current gain
- ⇒ Good voltage buffer

Chip-Based Current Sources and Voltage Sources

We have realized a decent load but

How does one generate voltage levels on a chip for biasing??

Current and voltage biasing of circuits require transistor based current and voltage sources on a chip!

What are the good figures of merit of chip-based voltage and current sources?

