

Lecture 15

Multistage FET Amplifiers


In this lecture you will learn:

- Multistage FET Amplifiers
- The Cascade Design
- The Cascode Design


The Need for Multistage Amplifiers

Most modern amplifiers have multiple stage in order to:

 
- 1) Increase the amplifier gain (voltage gain or current gain or transimpedance gain or transconductance gain)
- 2) Transform the input resistance to match the source
- 3) Transform the output resistance to match the load



 A Cascade of Two CS Stages for a Voltage Amplifier




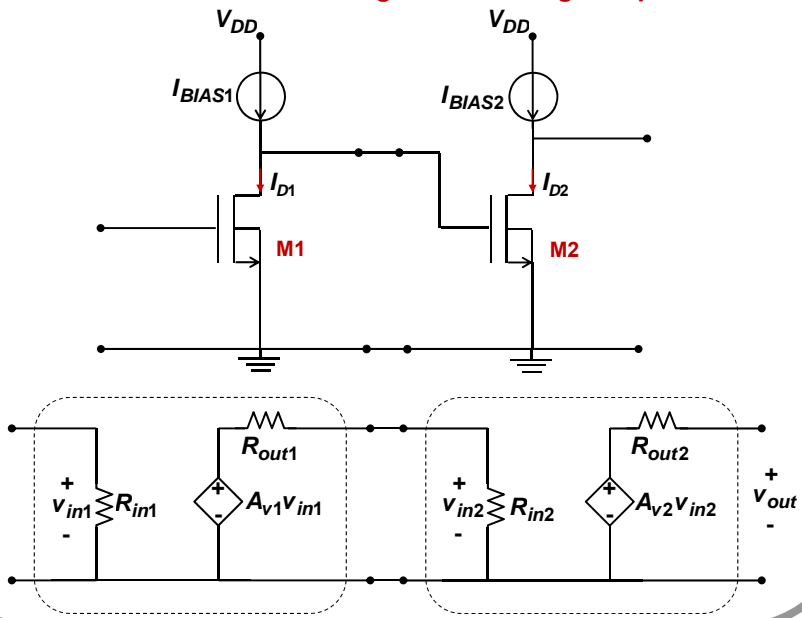A Cascade of Two CS Stages for a Voltage Amplifier



A Cascade of Two CS Stages: Finding Input Resistances

1)

 

1) First find R_{in2} (input resistance of the last stage):

Make sure R_L is in place!!



$$R_{in2} = \infty$$

2) Then find R_{in1} (input resistance of the second last stage):

Make sure R_{in2} is in place!!


$$R_{in1} = \infty$$

2)

  

A Cascade of Two CS Stages: Finding Output Resistances

1)

 

1) First find R_{out1} (output resistance of the first stage):

Make sure R_S is in place!!



$$R_{out1} = (r_{o1} \parallel r_{oc1})$$

2) Then find R_{out2} (output resistance of the second stage):

Make sure R_{out1} is in place!!


$$R_{out2} = (r_{o2} \parallel r_{oc2})$$

2)

  

A Cascade of Two CS Stages: Finding Voltage Gains

1)

 

Open circuit voltage gains of CS stages do not depend on how the stages are connected (i.e. on source or load resistances)


Stage 1 Parameters:

$$R_{in1} = \infty$$

$$R_{out1} = (r_{o1} \parallel r_{oc1})$$

$$A_{v1} = -g_{m1}(r_{o1} \parallel r_{oc1})$$

2)

 


Stage 2 Parameters:

$$R_{in2} = \infty$$


$$R_{out2} = (r_{o2} \parallel r_{oc2})$$

$$A_{v2} = -g_{m2}(r_{o2} \parallel r_{oc2})$$

A Cascade of Two Amplifiers

 

 The two stages can be combined into a single stage:



Input resistance:

$$R_{in} = R_{in1}$$


Output resistance:

$$R_{out} = R_{out2}$$


Open circuit voltage gain:

$$A_v = ?$$

A Cascade of Two Amplifiers

 

 The two stages can be combined into a single stage:




Open circuit voltage gain:

$$\begin{aligned}
 v_{out} &= A_{v2}v_{in2} = A_{v2}A_{v1}v_{in1} \frac{R_{in2}}{R_{out1} + R_{in2}} \\
 &= A_{v2}A_{v1}v_{in} \frac{R_{in2}}{R_{out1} + R_{in2}} \\
 \Rightarrow A_v &= \frac{v_{out}}{v_{in}} = A_{v2}A_{v1} \frac{R_{in2}}{R_{out1} + R_{in2}}
 \end{aligned}$$

Inter-stage voltage divider

 A Cascade of Two Amplifiers with a Source Resistor




Voltage gain:

$$\begin{aligned}
 v_{out} &= A_{v2}v_{in2} \frac{R_L}{R_{out2} + R_L} = A_{v2}A_{v1}v_{in1} \frac{R_{in2}}{R_{out1} + R_{in2}} \frac{R_L}{R_{out2} + R_L} \\
 &= A_{v2}A_{v1}v_{in1} \frac{R_{in2}}{R_{out1} + R_{in2}} \frac{R_L}{R_{out2} + R_L} \\
 &= A_{v2}A_{v1}v_s \frac{R_{in1}}{R_s + R_{in1}} \frac{R_{in2}}{R_{out1} + R_{in2}} \frac{R_L}{R_{out2} + R_L} \quad \left[\text{For the CS FET stages: } R_{in1} = R_{in2} = \infty \right] \\
 \Rightarrow \frac{v_{out}}{v_s} &= A_{v2}A_{v1} \frac{R_{in1}}{R_s + R_{in1}} \frac{R_{in2}}{R_{out1} + R_{in2}} \frac{R_L}{R_{out2} + R_L}
 \end{aligned}$$

Input voltage divider Inter-stage voltage divider Output voltage divider

 A Cascade of Two Amplifiers with a Source Resistor



Voltage gain:

$$\begin{aligned}
 v_{out} &= A_v v_{in} \frac{R_L}{R_{out} + R_L} \\
 &= A_v v_s \frac{R_{in}}{R_s + R_{in}} \frac{R_L}{R_{out} + R_L} \\
 \Rightarrow \frac{v_{out}}{v_s} &= A_v \frac{R_{in}}{R_s + R_{in}} \frac{R_L}{R_{out} + R_L}
 \end{aligned}$$

Input voltage divider


Output voltage divider

It is easier to use the single-stage model

The expression is the same as the one on the previous slide

A Cascade of Two CS Stages for a Voltage Amplifier

Putting it all together:

 

Input resistance:

$$R_{in} = \infty$$

Output resistance:


$$R_{out} = r_{o2} \parallel r_{oc2}$$

Open circuit voltage gain:

$$\begin{aligned}
 A_v &= \frac{v_{out}}{v_{in}} = A_{v1} A_{v2} \\
 &= [-g_{m1}(r_{o1} \parallel r_{oc1})][-g_{m2}(r_{o2} \parallel r_{oc2})]
 \end{aligned}$$

Not really a good voltage amplifier – output resistance is too large – but a decent transconductance amplifier

 A Cascade of Three FET Stages: 2 CS and 1 CD



Input resistance:

$$R_{in} = \infty$$

Output resistance:

$$\frac{1}{R_{out}} \approx \frac{1}{r_{oc3}} + (g_{m3} + g_{mb3}) \approx (g_{m3} + g_{mb3})$$


Small

Open circuit voltage gain:

$$A_v = A_{v1} A_{v2} A_{v3} \approx [-g_{m1}(r_{o1} \parallel r_{oc1})][-g_{m2}(r_{o2} \parallel r_{oc2})][\sim 1]$$

Now it is a better voltage amplifier!

 A Cascade of Three FET Stages: Direct Coupling and DC Biasing




In a direct-coupled scheme, as above, the DC bias of one stage affects the DC bias of other stages

Need to ensure appropriate DC bias of every stage such that:

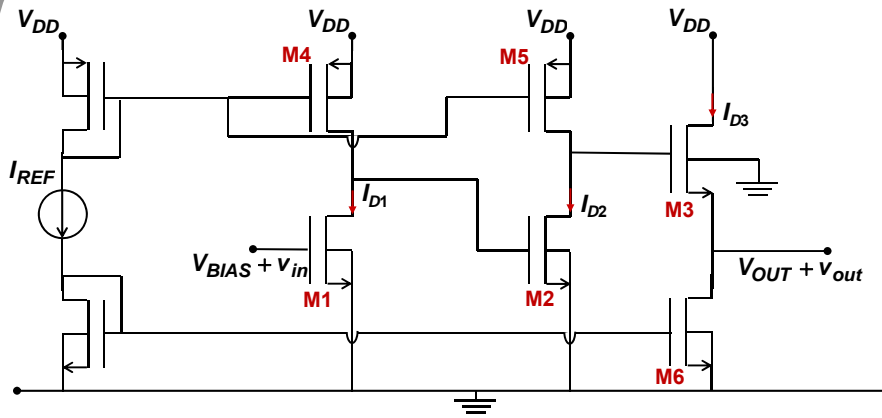
- i) The FETs are operating in saturation
- ii) The desired voltage swing does not cause problems (e.g. cause some FET to go out of saturation)

A Cascade of Three FET Stages: A Better DC Biasing



The sizes (W/L ratios) of **M4**, **M5**, and **M6** can be adjusted to get the desired bias currents for the three amplifier stages

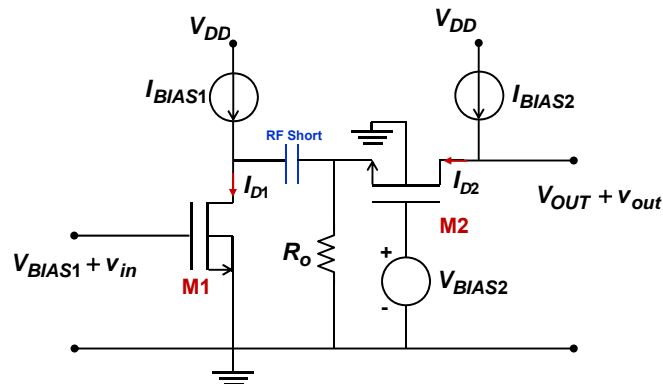A Cascade of CS and CG: A Capacitively-Coupled Cascode




The FET cascode has a large input resistance, a very large output resistance, and a large gain

But it is much better than a CS-CS cascade in terms of the frequency performance, as we will see later in the course

The above topology can be simplified.....

 
A Cascade of CS and CG: A Direct-Coupled Cascode



One current source can bias both the stages in a direct-coupling topology....!



This is the preferred way for on-chip designs

A Cascade of CS and CG: The Cascode

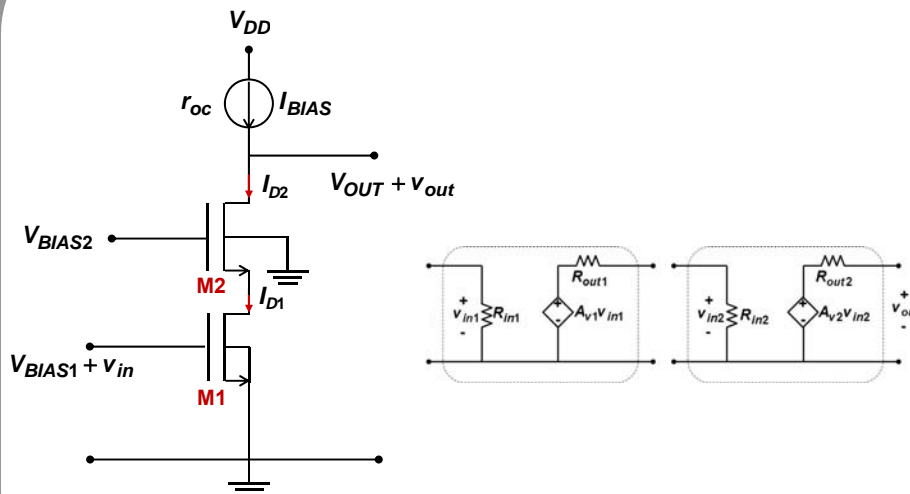

A different way to draw the same circuit

  The FET Cascode: Input and Output Resistances of Each Stage



Input resistances:

$$R_{in2} \approx \frac{1}{g_{m2} + g_{mb2}} \left(1 + \frac{r_{oc}}{r_{o2}} \right)$$

Assuming $R_L = \infty$

$$R_{in1} = \infty$$

$$\Rightarrow R_{in} = R_{in1} = \infty$$

Output resistances:



$$R_{out1} = r_{o1}$$

$$R_{out2} = r_{oc} \parallel [r_{o2} + R_{out1} + r_{o2}(g_{m2} + g_{mb2})R_{out1}]$$

$$\approx r_{oc} \parallel [(g_{m2} + g_{mb2})r_{o1}r_{o2}]$$

$$\Rightarrow R_{out} = R_{out2} \approx r_{oc} \parallel [(g_{m2} + g_{mb2})r_{o1}r_{o2}]$$

  The FET Cascode: Voltage Gains of Each Stage



Voltage Gains:

$$A_{v1} = -g_{m1}r_{o1}$$

$$A_{v2} = (g_{m2} + g_{mb2})(r_{o2} \parallel r_{oc})$$


$$\Rightarrow A_v = \frac{v_{out}}{v_{in}} = A_{v2}A_{v1} \frac{R_{in2}}{R_{out1} + R_{in2}} = (-g_{m1}r_{o1}) \left((g_{m2} + g_{mb2}) \frac{r_{o2}r_{oc}}{r_{o2} + r_{oc}} \right) \frac{1}{(g_{m2} + g_{mb2})r_{o1} \frac{r_{o2}}{r_{o2} + r_{oc}} + 1}$$

If $r_{oc} \gg r_{o2}, r_{o1}$:

$$\Rightarrow A_v \approx [-g_{m1}r_{o1}] [(g_{m2} + g_{mb2})r_{o2}]$$

→ Very large

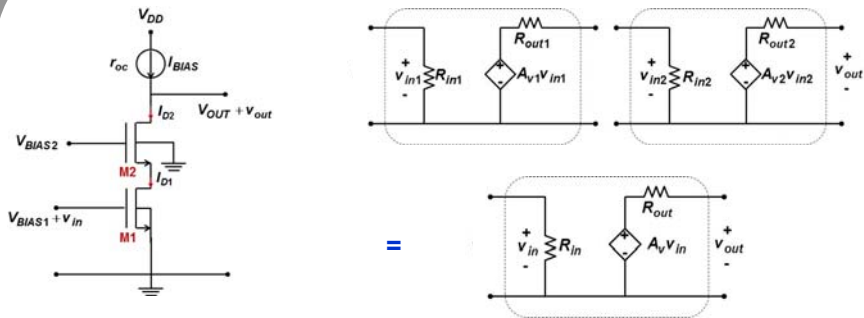The FET Cascode: Voltage Gains of Each Stage



Voltage Gains:

$$A_{v1} = -g_{m1}r_{o1} \quad A_{v2} = (g_{m2} + g_{mb2})(r_{o2} \parallel r_{oc})$$


$$\Rightarrow A_v = \frac{v_{out}}{v_{in}} = A_{v2}A_{v1} \frac{R_{in2}}{R_{out1} + R_{in2}} = (-g_{m1}r_{o1}) \left((g_{m2} + g_{mb2}) \frac{r_{o2}r_{oc}}{r_{o2} + r_{oc}} \right) \frac{1}{(g_{m2} + g_{mb2})r_{o1} \frac{r_{o2}}{r_{o2} + r_{oc}} + 1}$$

If $r_{oc} \sim r_{o2}, r_{o1}$:

$$\Rightarrow A_v \approx (-g_{m1}r_{o1}) \left((g_{m2} + g_{mb2}) \frac{r_{o2}r_{oc}}{r_{o2} + r_{oc}} \right) \frac{1}{(g_{m2} + g_{mb2})r_{o1} \frac{r_{o2}}{r_{o2} + r_{oc}}}$$

$$\Rightarrow A_v \approx -g_{m1}r_{oc} \quad \longrightarrow \quad \text{Can still be large}$$

The FET Cascode: Transconductance Gain

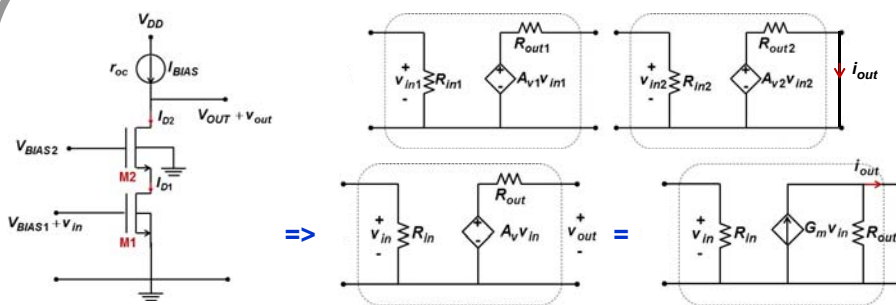


Transconductance Gain (with output shorted):

$$G_m = \frac{i_{out}}{v_{in}} = \frac{A_v}{R_{out}} \approx -g_{m1}$$

Biasing the FET Cascode Amplifier

Choose voltage biasing such that:

$$I_{D1} = I_{D2} = I_{BIAS}$$

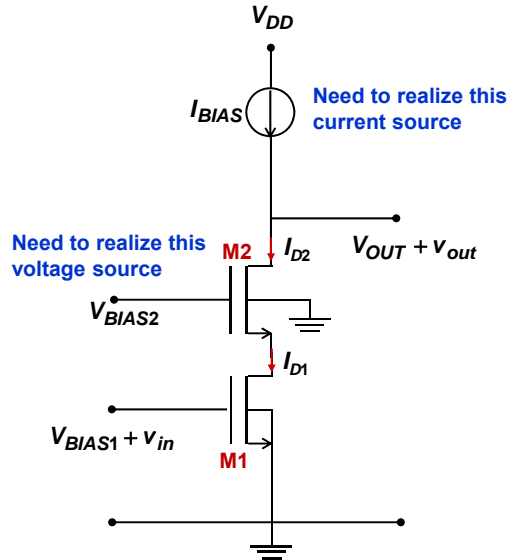


Biasing the FET Cascode Amplifier

Choose voltage biasing such that:

$$I_{D1} = I_{D2} = -I_{D3}$$

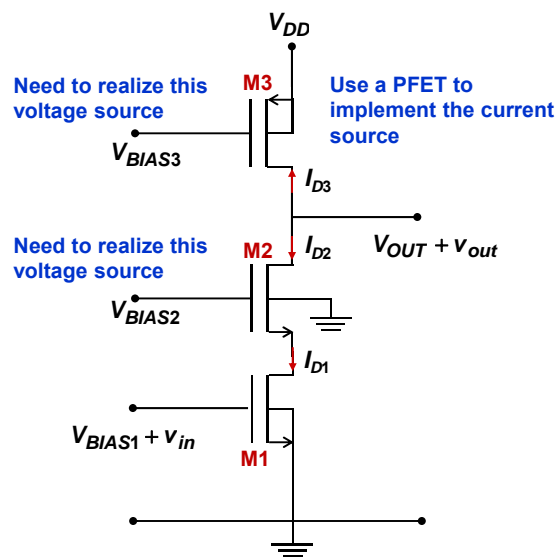Problem: To be accurate with voltage biasing, one needs to know the characteristics (i.e. k_n , k_p , etc) of the FETs accurately, and this information is usually not available to the circuit designer


Solution: Use circuit biasing schemes that are not too sensitive to the circuit designer's detailed knowledge of the FETs!



Biasing the FET Cascode Amplifier

Choose voltage biasing such that:
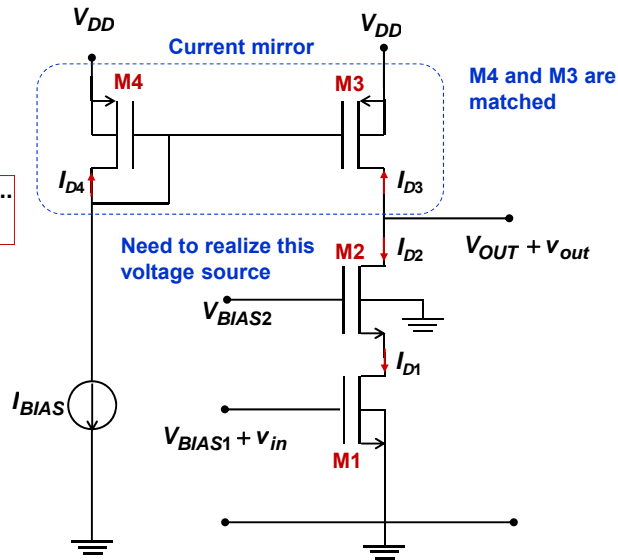
$$I_{D1} = I_{D2} = -I_{D3} = \dots \\ = -I_{D4} = I_{BIAS}$$




Biasing the FET Cascode Amplifier


Choose voltage biasing such that:

$$I_{D1} = I_{D2} = -I_{D3} = \dots \\ = -I_{D4} = I_{D5} = \dots \\ = I_{BIAS}$$

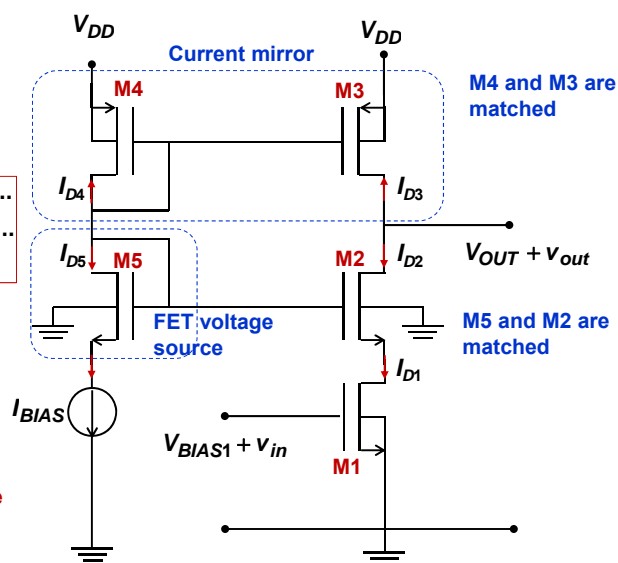What if we have only a single stable current source available on the chip..?



Biassing the FET Cascode Amplifier

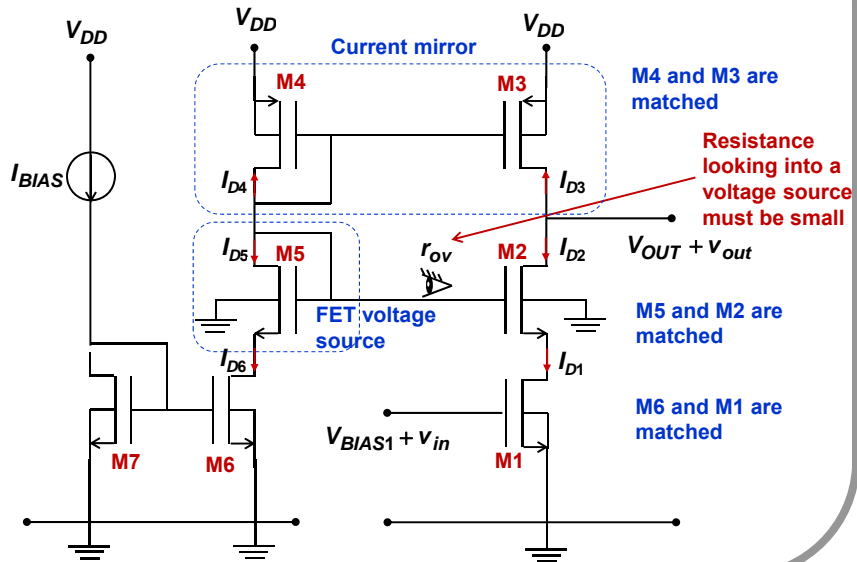

Biassing the FET Cascode Amplifier

