


Lecture 17

Differential Amplifiers – II Advanced Concepts


In this lecture you will learn:

- Differential Amplifiers
- Use of Current Mirrors in Differential Amplifiers
- Small Signal and Large Signal Models with Current Mirrors

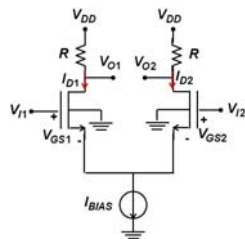Differential Amplifier: Double-Ended Output



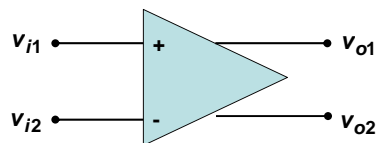The FET differential amplifiers considered in the previous handout had a double-ended output



$$v_{o1} = \frac{A_{vd}}{2}(v_{i1} - v_{i2}) + A_{vc}\left(\frac{v_{i1} + v_{i2}}{2}\right)$$

$$= A_{vd} \frac{v_{id}}{2} + A_{vc} v_{ic}$$

$$v_{o2} = -\frac{A_{vd}}{2}(v_{i1} - v_{i2}) + A_{vc}\left(\frac{v_{i1} + v_{i2}}{2}\right)$$

$$= -A_{vd} \frac{v_{id}}{2} + A_{vc} v_{ic}$$

Difference-Mode Output:


$$v_{od} = v_{o1} - v_{o2} = A_{vd} v_{id}$$

Common-Mode Output:

$$v_{oc} = \frac{v_{o1} + v_{o2}}{2} = A_{vc} v_{ic}$$

Differential Amplifier: Double-Ended Output

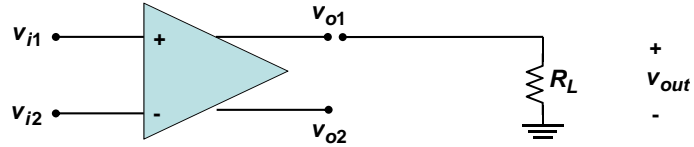
Suppose one tries to connect a load to one of the outputs:



$$v_{out} = v_{o1} = A_{vd} \frac{v_{id}}{2} + A_{vc} v_{ic} \approx A_{vd} \frac{v_{id}}{2} \longrightarrow \text{We have lost half of the voltage}$$


We can do better.....

Try another scheme:

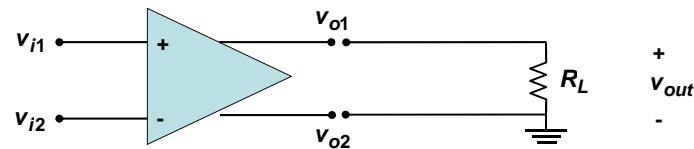

$$v_{out} = v_{od} = v_{o1} - v_{o2} = A_{vd} v_{id} \longrightarrow \text{We have recovered the full signal but this scheme is not always practical}$$

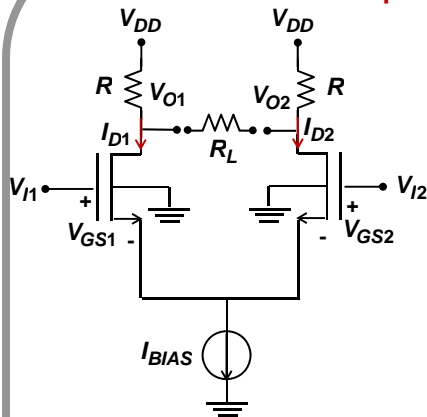
Differential Amplifier: Single-Ended Output




This is an awkward way to connect the load at the output

Most of the time what one would really like to have is a single-ended output (without losing the factor of 2):
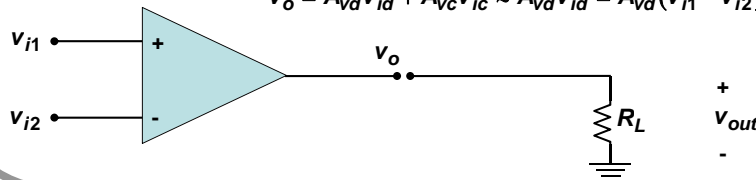
$$v_o = A_{vd} v_{id} + A_{vc} v_{ic} \approx A_{vd} v_{id} = A_{vd} (v_{i1} - v_{i2}) = v_{out}$$



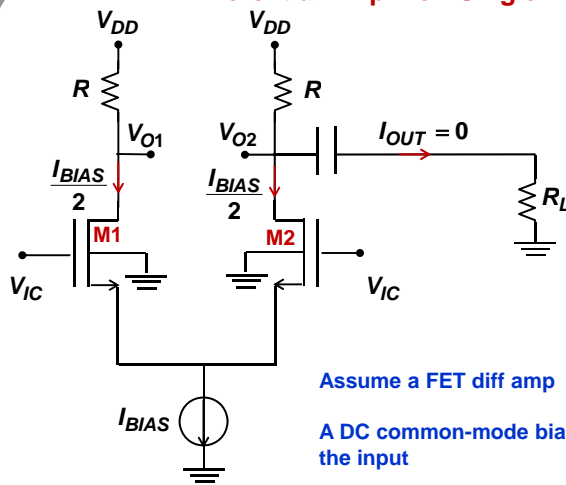FET Differential Amplifier: Single-Ended Operation




Assume a FET diff amp

A DC common-mode bias V_{IC} is applied at the input

Assume very large r_{o1} , r_{o2} , and R (compared to R_L) for simplicity

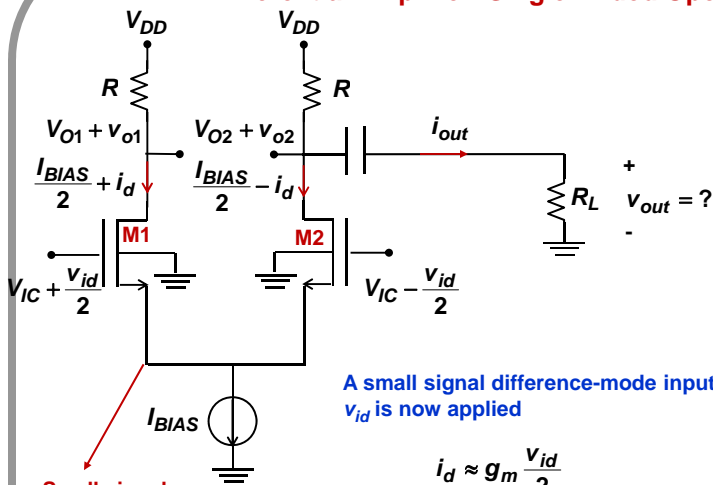FET Differential Amplifier: Single-Ended Operation




A small signal difference-mode input signal v_{id} is now applied

Small signal ground


$$i_d \approx g_m \frac{v_{id}}{2}$$

$$v_{o1} = -i_d R \approx -g_m \frac{v_{id}}{2} R$$

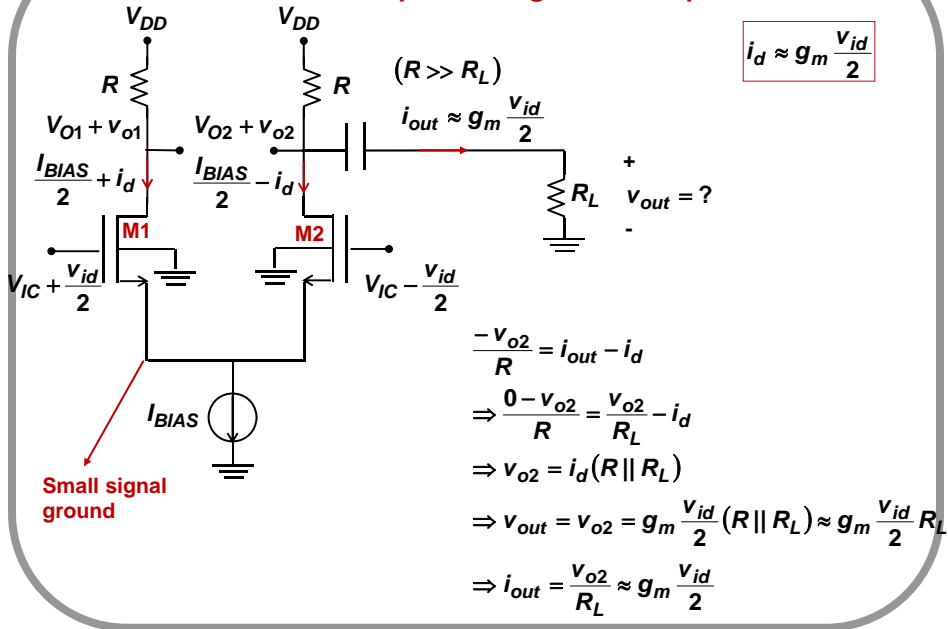
FET Differential Amplifier: Single-Ended Operation



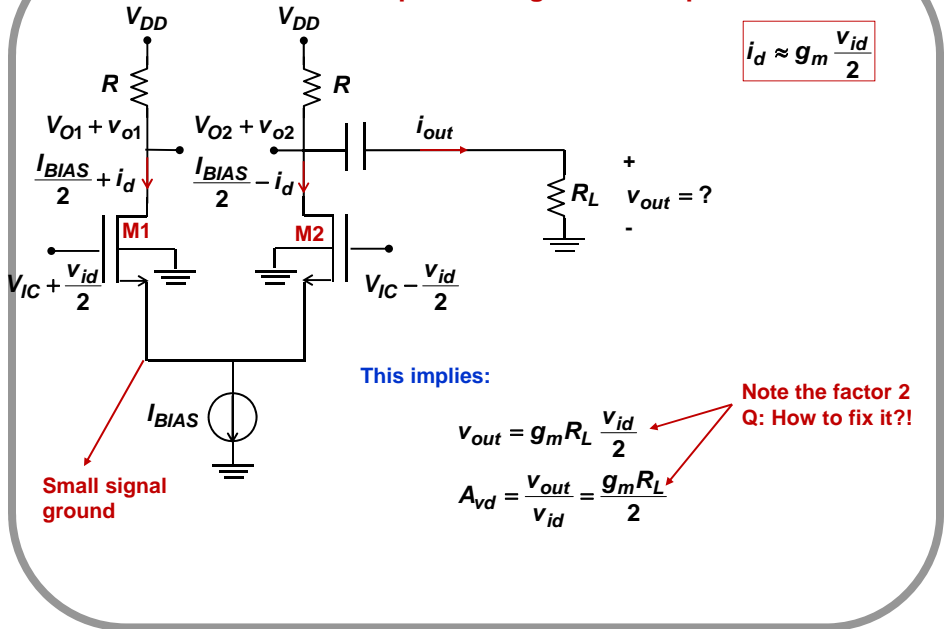FET Differential Amplifier: Single-Ended Operation



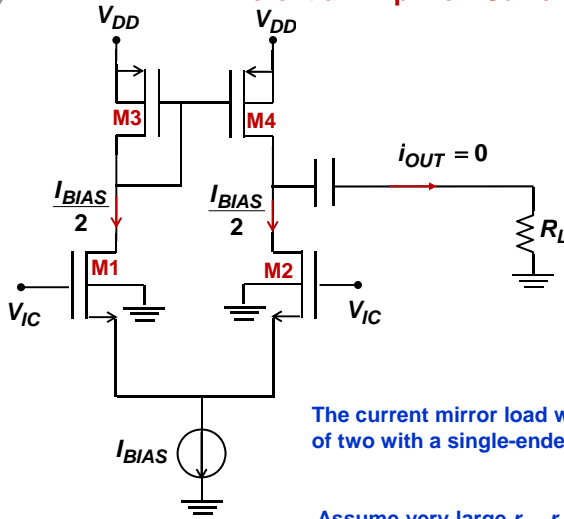
FET Differential Amplifier: Current Mirror Load



The current mirror load will let us recover the factor of two with a single-ended output!

Assume very large r_{o1} , r_{o2} , r_{o3} and r_{o4} (compared to R_L)

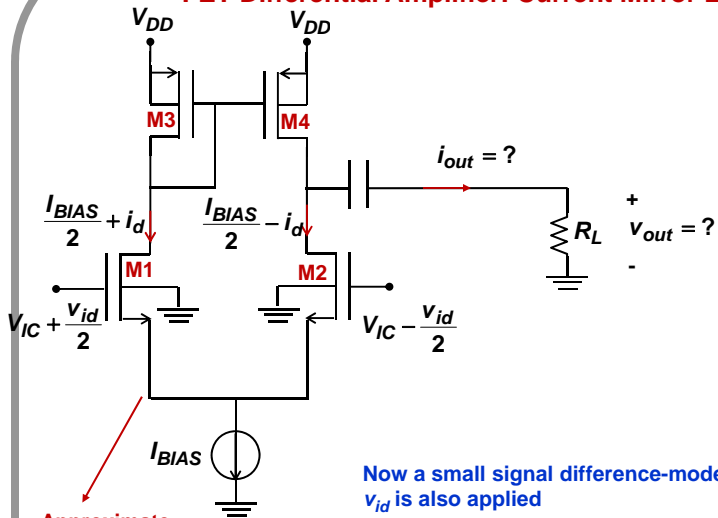FET Differential Amplifier: Current Mirror Load




$$i_d \approx g_{mn} \frac{v_{id}}{2}$$

Approximate small signal ground

Now a small signal difference-mode input signal v_{id} is also applied

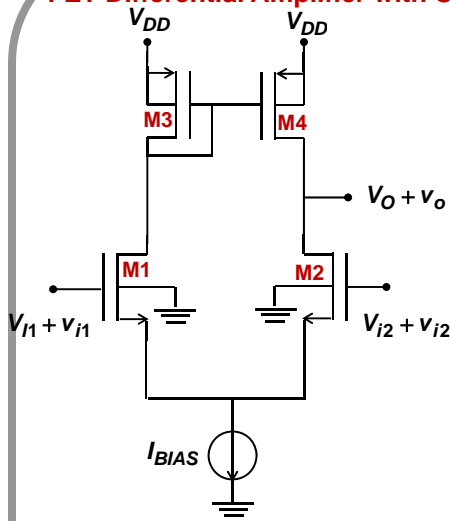FET Differential Amplifier with Current Mirror: Small Signal Analysis




Need to make and analyze a small circuit model and calculate:


$$A_{vd} = \frac{v_o}{v_{id}} \quad \text{Difference-Mode Gain}$$

$$A_{vc} = \frac{v_o}{v_{ic}} \quad \text{Common-Mode Gain}$$

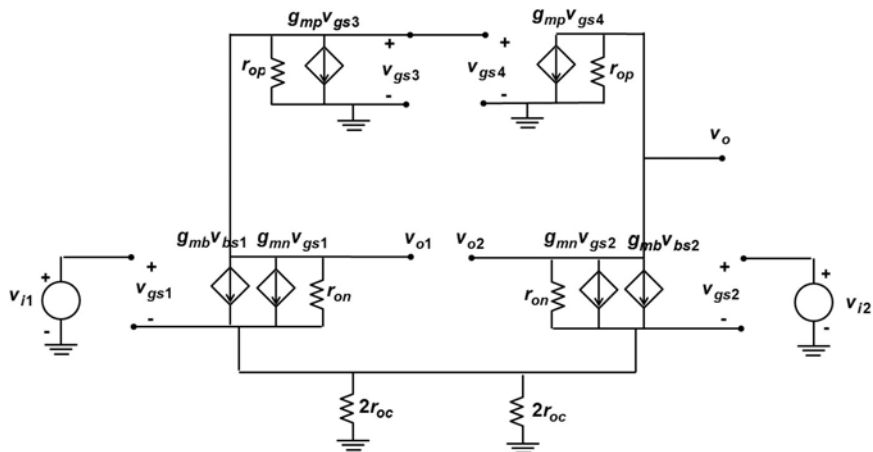FET Differential Amplifier with Current Mirror: Small Signal Analysis



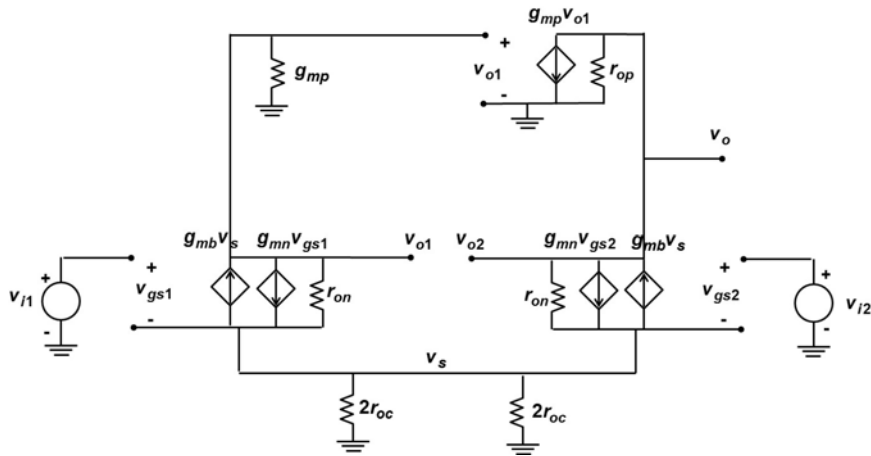
FET Differential Amplifier with Current Mirror: Small Signal Analysis



Small signal circuit model

Note the lack of symmetry!!

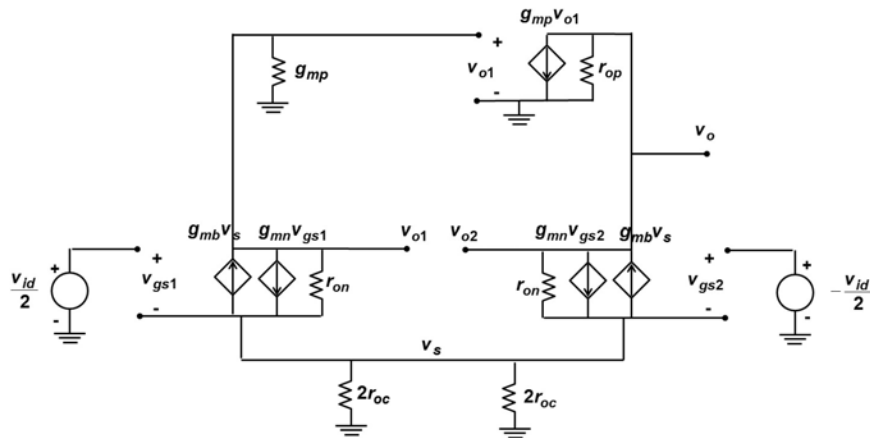Small Signal Analysis: Difference-Mode Input




There are three unknown internal voltage variables: v_{o1} v_{o2} v_s

We therefore need three equations


Try KCL at three different nodes.....

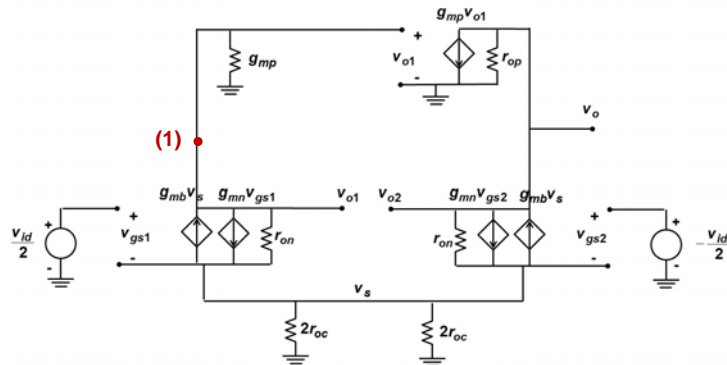Small Signal Analysis: Difference-Mode Input




$$\begin{aligned}
 (1) \quad & g_{mn} \left(\frac{v_{id}}{2} - v_s \right) + g_{on} (v_{o1} - v_s) - g_{mb} v_s + g_{mp} v_{o1} = 0 \\
 \Rightarrow & g_{mn} \left(\frac{v_{id}}{2} - v_s \right) - (g_{on} + g_{mb}) v_s + \overset{\text{small}}{g_{on} + g_{mp}} v_{o1} = 0 \\
 \Rightarrow & -(g_{on} + g_{mb}) v_s + g_{mp} v_{o1} \approx -g_{mn} \left(\frac{v_{id}}{2} - v_s \right)
 \end{aligned}$$

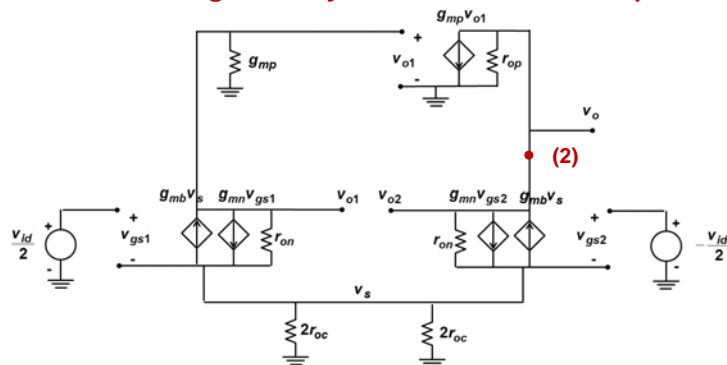Small Signal Analysis: Difference-Mode Input



$$\begin{aligned}
 (2) \quad & g_{mn} \left(-\frac{v_{id}}{2} - v_s \right) + g_{on} (v_{o2} - v_s) - g_{mb} v_s + g_{mp} v_{o1} + g_{op} v_{o2} = 0 \\
 \Rightarrow & g_{mn} \left(-\frac{v_{id}}{2} - v_s \right) + (g_{on} + g_{op}) v_{o2} - (g_{on} + g_{mb}) v_s + g_{mp} v_{o1} = 0 \\
 \Rightarrow & g_{mn} \left(-\frac{v_{id}}{2} - v_s \right) + (g_{on} + g_{op}) v_{o2} - g_{mn} \left(\frac{v_{id}}{2} - v_s \right) \approx 0 \\
 \Rightarrow & v_o = v_{o2} = \frac{g_{mn}}{g_{on} + g_{op}} v_{id} = g_{mn} (r_{on} \parallel r_{op}) v_{id} \quad \left\{ A_{vd} = \frac{v_o}{v_{id}} \approx g_{mn} (r_{on} \parallel r_{op}) \right.
 \end{aligned}$$

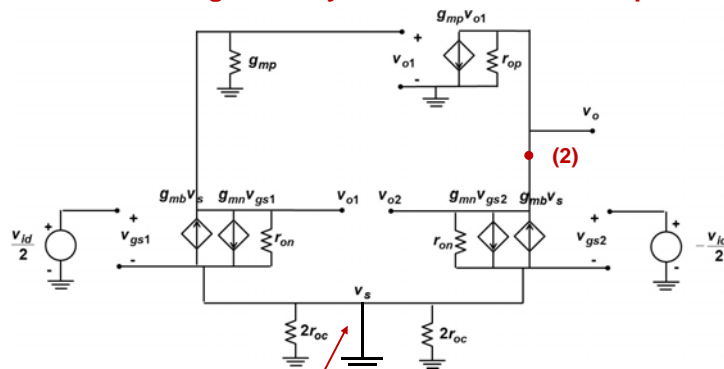Small Signal Analysis: Difference-Mode Input




One can also get the correct results by assuming a-priori that in the difference-mode the voltage v_s is approximately zero (i.e. the node is a small signal ground)

If v_s is assumed to be approximately zero then:

$$v_{o1} \approx -\frac{g_{mn}}{g_{mp}} \frac{v_{id}}{2} \rightarrow v_{o2} \approx \frac{-g_{mp} v_{o1} + g_{mn} \frac{v_{id}}{2}}{(g_{on} + g_{op})} = \frac{g_{mn} v_{id}}{(g_{on} + g_{op})}$$

$$= g_{mn} (r_{on} \parallel r_{op}) v_{id} = v_o$$

Small Signal Analysis: Common-Mode Input

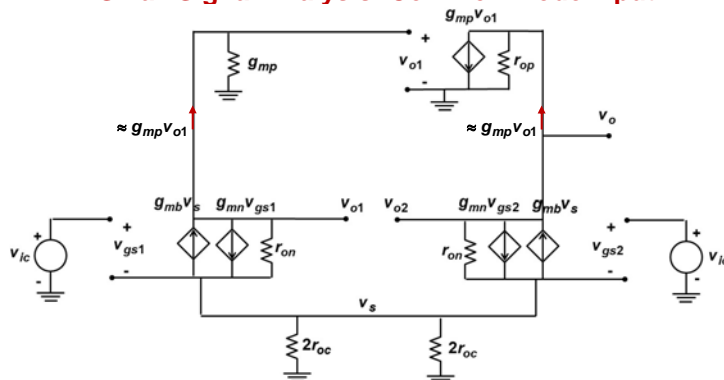


One good way to think about the amplifier in common-mode operation:

If the output resistance of **M4** is assumed to be very large, then the current mirror, as the name suggests will ensure that the drain currents of **M1** and **M2** are identical (both equal to $-g_{mp} v_{o1}$) – as you can see above as well.


Since the input voltages, v_{ic} , on the two sides are also the same, the circuit (at least the bottom portion) has complete left-right symmetry in common-mode operation

Small Signal Analysis: Common-Mode Input

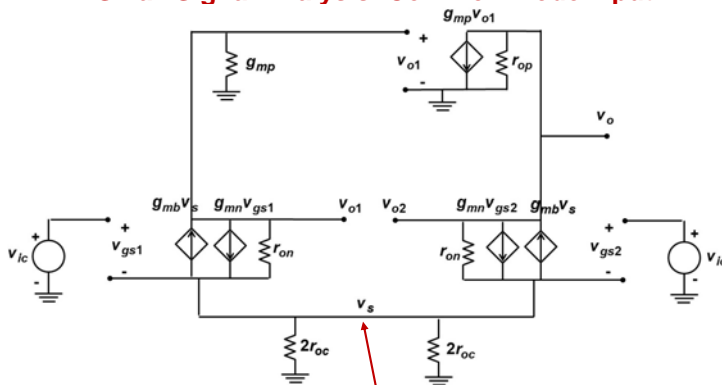

So one can assume that in the common-mode, even with the current mirror, no current flows in the bottom most horizontal wire (i.e. it is a small signal open)


Small Signal Analysis: Common-Mode Input

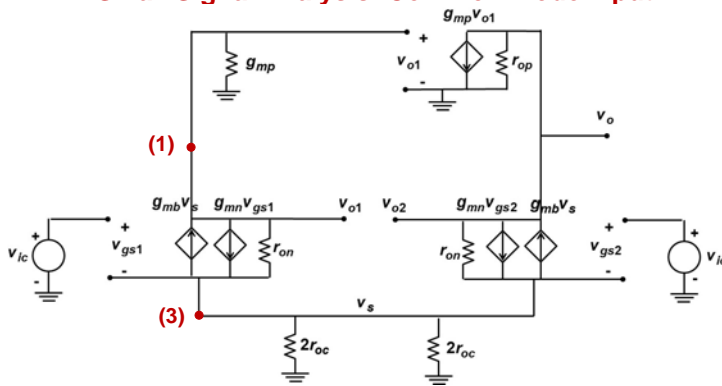

Doing KCL at (1) and (3) gives:

$$v_{o1} \approx - \frac{g_{mn} r_{on}}{r_{on} + \frac{1}{g_{mp}} + 2r_{oc} + (g_{mn} + g_{mb})r_{on}(2r_{oc})} v_{ic}$$

Small Signal Analysis: Common-Mode Input

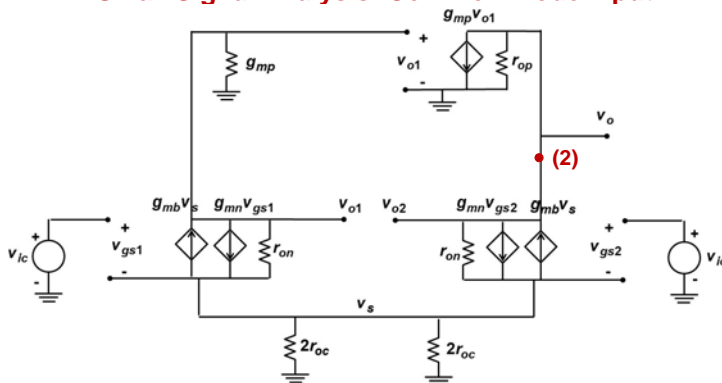


Using the left-right symmetry gives:

$$v_o = v_{o2} \approx v_{o1}$$

$$A_{vc} = \frac{v_o}{v_{ic}} \approx - \frac{\frac{g_{mn} r_{on}}{g_{mp}}}{r_{on} + \frac{1}{g_{mp}} + 2r_{oc} + (g_{mn} + g_{mb})r_{on}(2r_{oc})}$$


Small Signal Analysis: Output Resistance

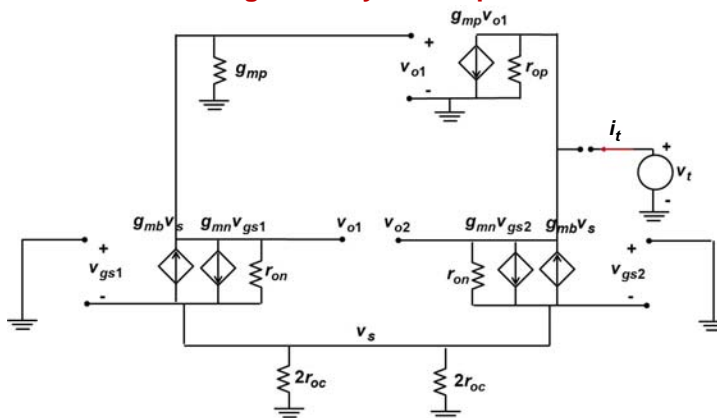

$$R_{out} \approx r_{on} \parallel r_{op}$$

Left for homework

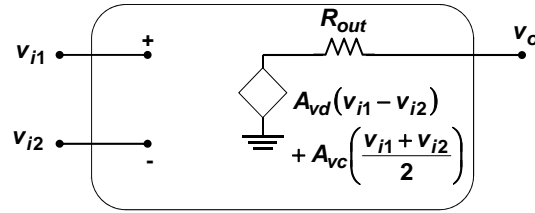Two-Port Model of a FET Differential Amplifier with Current Mirror




$$A_{vd} \approx g_{mn}(r_{on} \parallel r_{op})$$

$$A_{vc} = \frac{v_o}{v_{ic}} \approx - \frac{\frac{g_{mn} r_{on}}{g_{mp}}}{r_{on} + \frac{1}{g_{mp}} + 2r_{oc} + (g_{mn} + g_{mb})r_{on}(2r_{oc})}$$

$$\approx - \frac{\frac{g_{mn}}{g_{mp}}}{1 + \frac{2r_{oc}}{r_{on}} + (g_{mn} + g_{mb})(2r_{oc})}$$

$$R_{out} \approx r_{on} \parallel r_{op}$$

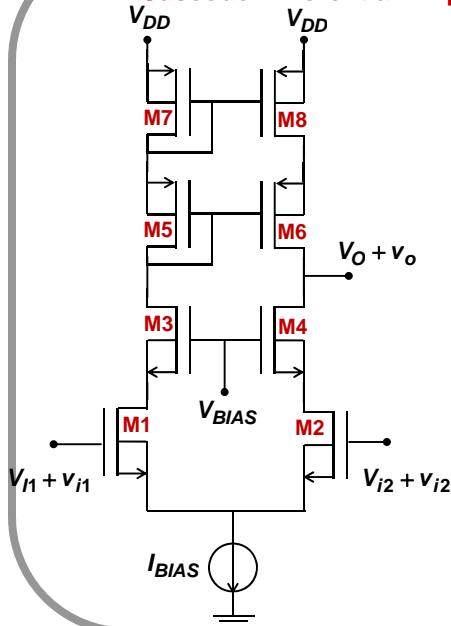FET Cascode Differential Amplifier with Cascode Current Mirror



$$R_{out} \approx (g_{mn}r_{on}r_{on}) \parallel (g_{mp}r_{op}r_{op})$$

$$A_{vd} \approx g_{mn}R_{out}$$

$$A_{vd} \approx g_{mn}[(g_{mn}r_{on}r_{on}) \parallel (g_{mp}r_{op}r_{op})]$$