

## Lecture 18

### Bipolar Junction Transistors (BJTs)

In this lecture you will learn:

- The operation of bipolar junction transistors
- Forward and reverse active operations, saturation, cutoff
- Ebers-Moll model
- Small signal models

### Bipolar Transistors



First Bipolar Transistor (AT&T Bell Labs)




First Bipolar Transistor (AT&T Bell Labs)




William Shockley, John Bardeen, Walter Brattain  
(Nobel Prize for the Transistor, AT&T Bell Labs)


### NPN Bipolar Junction Transistor

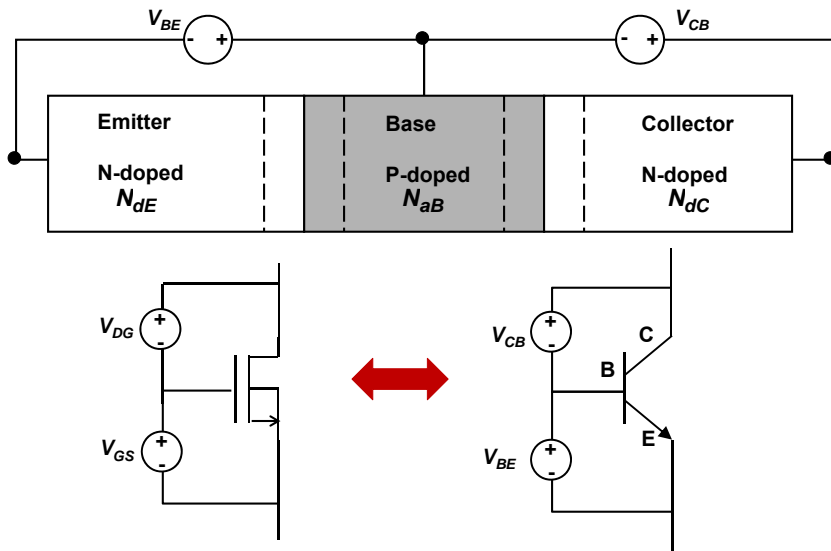

### PNP Bipolar Junction Transistor

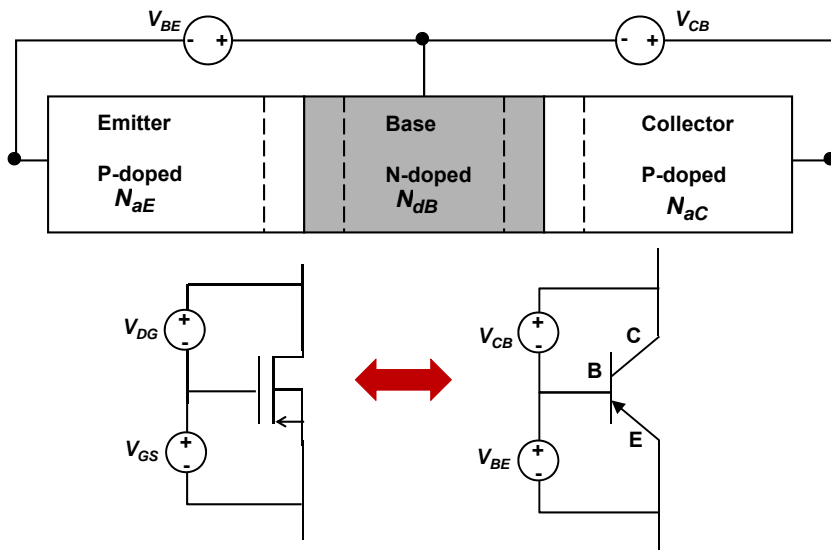

### NPN BJT: Basic Operation

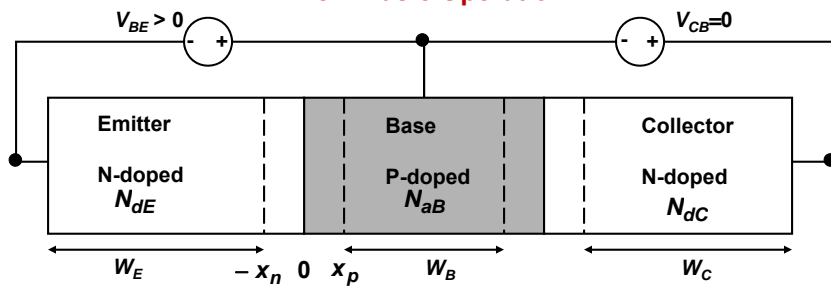

Suppose:

The base-emitter junction is **forward biased**


$$V_{BE} > 0$$

The base-collector junction is **zero biased**

$$V_{CB} = 0$$

This biasing scheme will put the device in the “**forward active**” operation (to be discussed fully later)


### NPN BJT: Basic Operation

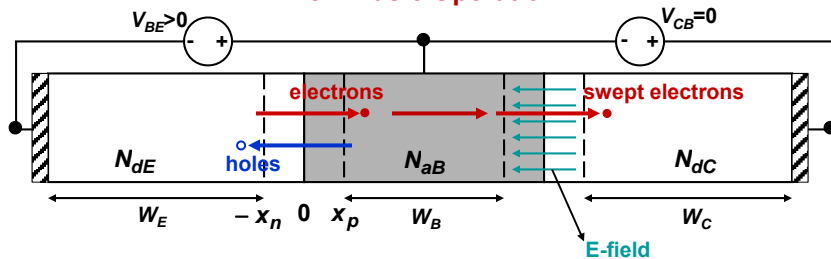

Consider the action in the base first ( $V_{BE} > 0$  and  $V_{CB} = 0$ )

- The electrons diffuse from the emitter, cross the depletion region, and enter the base
- In the base, the electrons are the minority carriers
- In the base, the electrons diffuse towards the collector
- As soon as the electrons reach the base-collector depletion region they are immediately swept away into the collector by the strong electric fields in the depletion region

### NPN BJT: Electron-Hole Populations

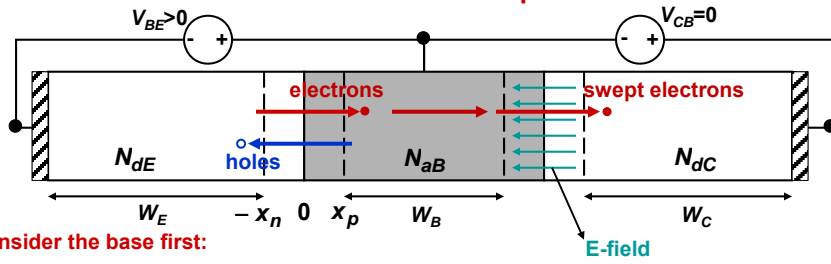

Consider the base first:


In the base, the electron population can be written as:

$$n(x) = n_{po} + n'(x) \quad \left. \begin{array}{l} \text{Equilibrium electron density} \\ \text{Excess electron density} \end{array} \right\} n_{po} = \frac{n_i^2}{N_{aB}}$$

In the base, the excess electron population satisfies the differential equation:

$$\frac{\partial^2 n'(x)}{\partial x^2} - \frac{n'(x)}{L_n^2} = 0 \quad \left. \begin{array}{l} \text{Boundary conditions} \end{array} \right\} \begin{array}{l} n'(x_p) = \frac{n_i^2}{N_{aB}} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) \\ n'(x_p + W_B) = \frac{n_i^2}{N_{aB}} \left( e^{\frac{qV_{BC}}{KT}} - 1 \right) = 0 \end{array}$$

### NPN BJT: Electron-Hole Populations

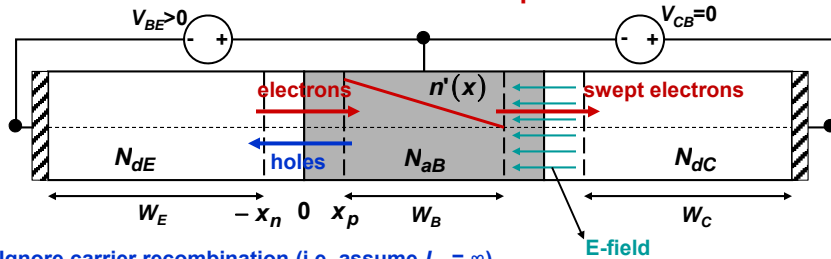


• Ignore carrier recombination (i.e. assume  $L_n = \infty$ )

$$\frac{\partial^2 n'(x)}{\partial x^2} = 0 \quad \left. \begin{array}{l} \text{Boundary conditions} \end{array} \right\} \begin{array}{l} n'(x_p) = \frac{n_i^2}{N_{aB}} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) \\ n'(x_p + W_B) = \frac{n_i^2}{N_{aB}} \left( e^{\frac{qV_{BC}}{KT}} - 1 \right) = 0 \end{array}$$

Solution is:

$$n'(x) = n'(x_n) \left( 1 - \frac{x - x_p}{W_B} \right) = \frac{n_i^2}{N_{aB}} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) \left( 1 - \frac{x - x_p}{W_B} \right)$$

### NPN BJT: Electron-Hole Populations

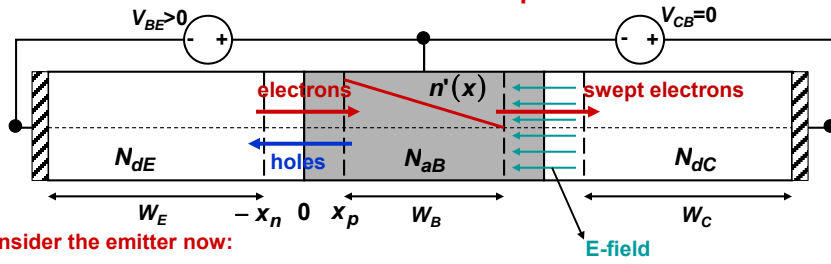

Consider the emitter now:


In the emitter, the hole population can be written as:

$$p(x) = p_{no} + p'(x) \quad \left. \begin{array}{l} \text{Equilibrium hole density} \\ \text{Excess hole density} \end{array} \right\} p_{no} = \frac{n_i^2}{N_{dE}}$$

In the emitter, the excess hole population satisfies the differential equation:

$$\frac{\partial^2 p'(x)}{\partial x^2} - \frac{p'(x)}{L_p^2} = 0 \quad \left. \begin{array}{l} \text{Boundary conditions} \\ p'(-x_n) = \frac{n_i^2}{N_{dE}} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) \\ p'(-x_n - W_E) = 0 \end{array} \right\}$$

### NPN BJT: Electron-Hole Populations

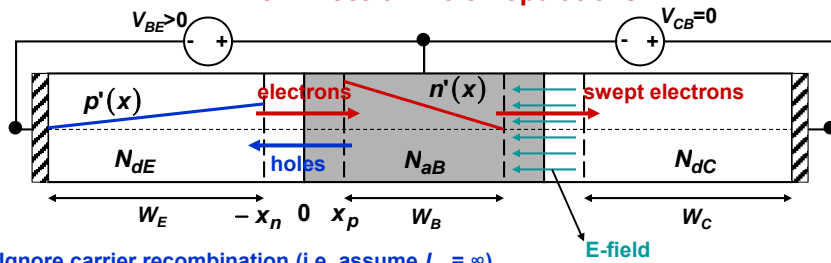


• Ignore carrier recombination (i.e. assume  $L_p = \infty$ )

$$\frac{\partial^2 p'(x)}{\partial x^2} = 0 \quad \left. \begin{array}{l} \text{Boundary conditions} \\ p'(-x_n) = \frac{n_i^2}{N_{dE}} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) \\ p'(-x_n - W_E) = 0 \end{array} \right\}$$

Solution is:

$$p'(x) = p'(-x_n) \left( 1 + \frac{x+x_n}{W_E} \right) = \frac{n_i^2}{N_{dE}} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) \left( 1 + \frac{x+x_n}{W_E} \right)$$
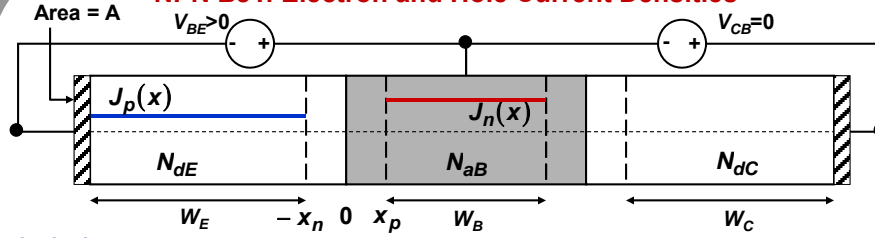
### NPN BJT: Electron and Hole Current Densities



**In the base:**

- The electron current is:


$$J_n(x) \approx q D_n \frac{\partial n(x)}{\partial x} = q n_i^2 \frac{D_n}{N_{aB} W_B} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

**In the emitter:**

- The hole current is:

$$J_p(x) \approx -q D_p \frac{\partial p(x)}{\partial x} = q n_i^2 \frac{D_p}{N_{dE} W_E} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

### NPN BJT: Terminal Currents

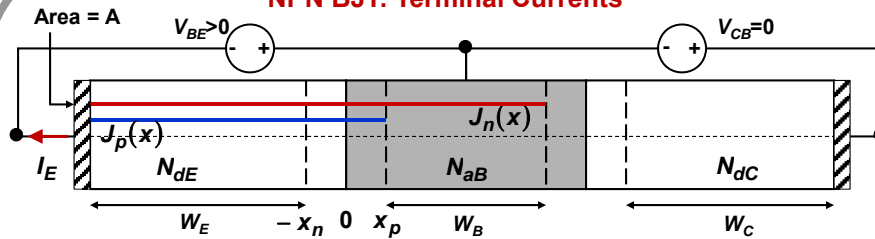


**Emitter current:**

- The current flowing out of the emitter is the sum of the total electron and total hole currents in the emitter:

$$I_E = q n_i^2 A \left( \frac{D_p}{N_{dE} W_E} + \frac{D_n}{N_{aB} W_B} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

### NPN BJT: Terminal Currents

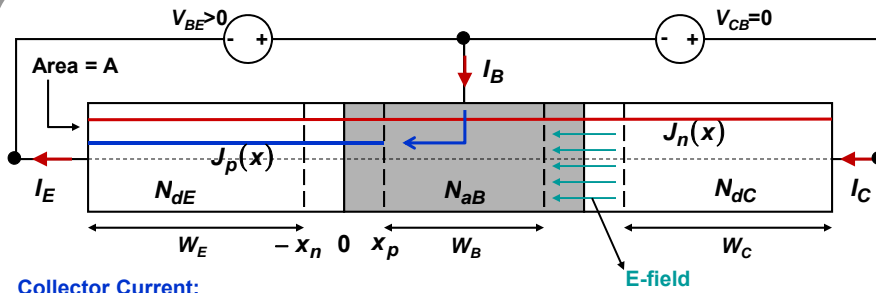

#### Collector Current:

- The current going into the collector is due to the electrons that got swept from the Base through the Base-Collector depletion region by the electric fields:


$$I_C = qn_i^2 A \left( \frac{D_n}{N_{aB}W_B} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

#### Base Current:

- The current going into the Base is due to the holes that got injected from the base into the emitter:

$$I_B = qn_i^2 A \left( \frac{D_p}{N_{dE}W_E} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

### NPN BJT: Terminal Currents

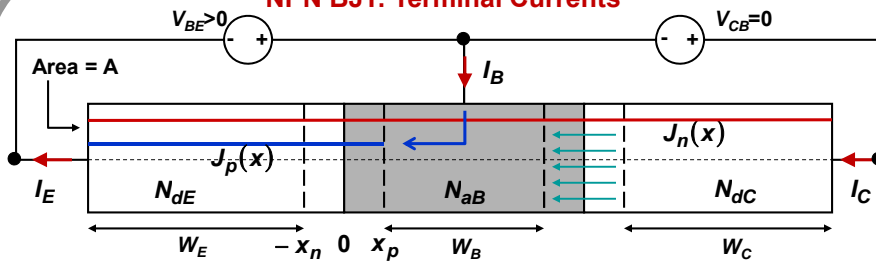


$$I_E = qn_i^2 A \left( \frac{D_p}{N_{dE}W_E} + \frac{D_n}{N_{aB}W_B} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

$$I_C = qn_i^2 A \left( \frac{D_n}{N_{aB}W_B} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

$$I_B = qn_i^2 A \left( \frac{D_p}{N_{dE}W_E} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

$$I_E = I_B + I_C$$

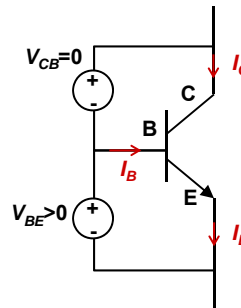

### NPN BJT: Circuit Level Parameters

**Current gain  $\beta_F$ :**

Current gain of the BJT in the forward active operation is defined as the ratio of the collector and base currents:

$$\beta_F = \frac{I_C}{I_B} = \frac{D_n}{N_{aB}W_B} \frac{N_{dE}W_E}{D_p} \Rightarrow I_C = \beta_F I_B$$

Typical values of  $\beta_F$  are between 20-200 and:

$$N_{dE} \gg N_{aB} > N_{dC}$$


**$\alpha_F$ :**

In the forward active operation  $\alpha_F$  is defined as the ratio of the collector and emitter currents:

$$\alpha_F = \frac{I_C}{I_E} = \frac{\frac{D_n}{N_{aB}W_B}}{\frac{D_p}{N_{dE}W_E} + \frac{D_n}{N_{aB}W_B}} \Rightarrow I_C = \alpha_F I_E$$

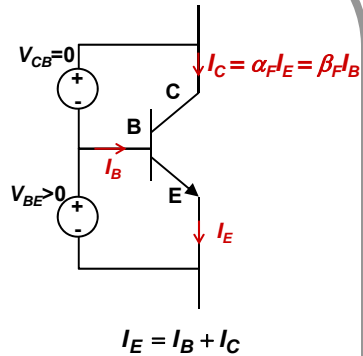
**Transistor relation:**

$\alpha_F$  and  $\beta_F$  are related: 
$$\beta_F = \frac{\alpha_F}{1 - \alpha_F}$$


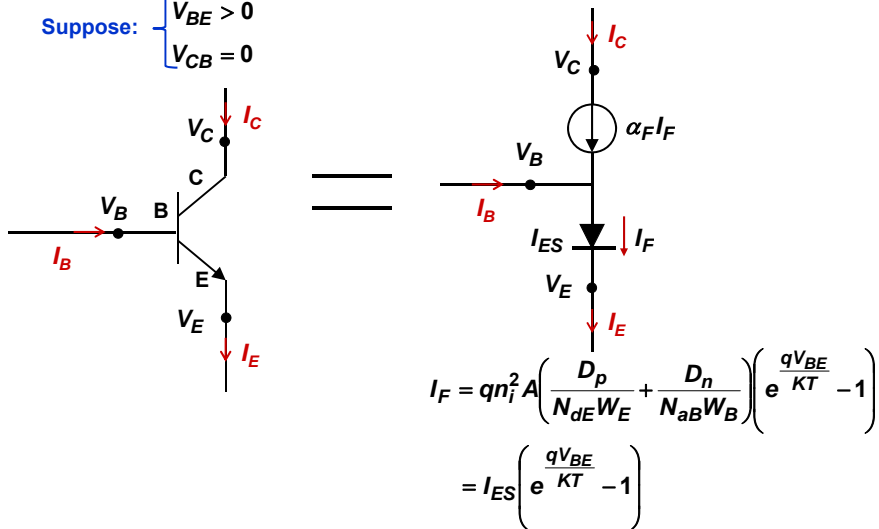
### NPN BJT: Ebers-Moll Model for Forward Active Operation


Suppose:  $\begin{cases} V_{BE} > 0 \\ V_{CB} = 0 \end{cases}$



The circuit level simplified model with an **ideal diode** and a **current-controlled current source** models the NPN transistor in the forward active operation


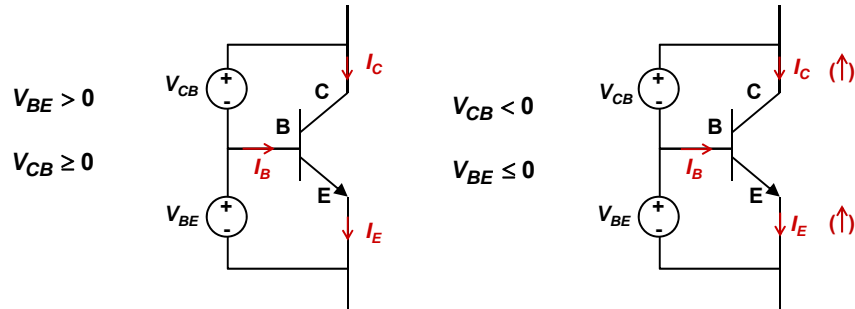
### NPN BJT: Forward and Reverse Active Operations



Forward active operation

$$\beta_F = \frac{I_C}{I_B}$$

$$\alpha_F = \frac{I_C}{I_E}$$

$$\beta_F = \frac{\alpha_F}{1 - \alpha_F}$$

Reverse active operation

$$\beta_R = -\frac{I_E}{I_B} = \frac{D_n}{N_{aB}W_B} \frac{N_{dC}W_C}{D_p}$$


$$\alpha_R = \frac{I_E}{I_C}$$

$$\beta_R = \frac{\alpha_R}{1 - \alpha_R}$$

In a well designed transistor:  $\beta_F \gg \beta_R$
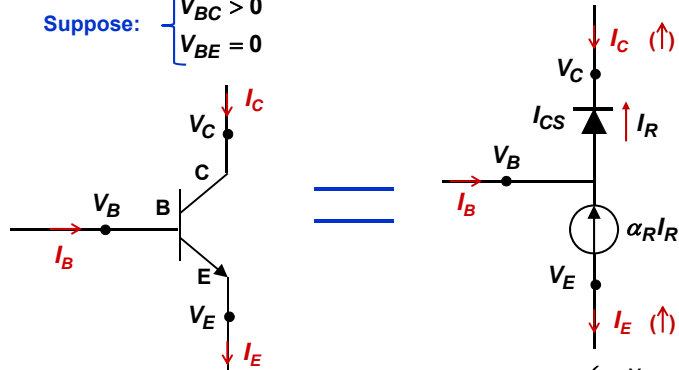
### NPN BJT: Ebers-Moll Model for Reverse Active Operation

Suppose:  $\begin{cases} V_{BC} > 0 \\ V_{BE} = 0 \end{cases}$




$$I_R = qn_i^2 A \left( \frac{D_p}{N_{dC}W_C} + \frac{D_n}{N_{aB}W_B} \right) \left( e^{\frac{qV_{BC}}{KT}} - 1 \right) = I_{CS} \left( e^{\frac{qV_{BC}}{KT}} - 1 \right)$$

The circuit level simplified model with an ideal diode and a current-controlled current source models the NPN transistor in the reverse active operation

### NPN BJT: Ebers-Moll Model and Terminal Currents

Terminal currents:

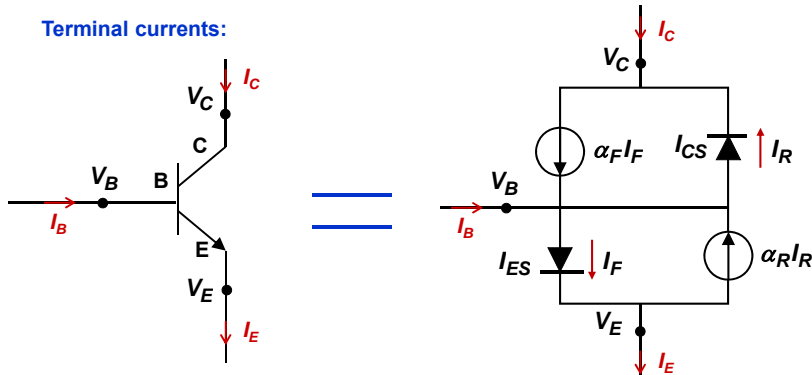

$$I_R = I_{CS} \left( e^{\frac{qV_{BC}}{KT}} - 1 \right)$$

$$I_F = I_{ES} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$


And

$$I_B = (1 - \alpha_F) I_F + (1 - \alpha_R) I_R$$

$$I_C = \alpha_F I_F - I_R$$

$$I_E = I_F - \alpha_R I_R$$

### NPN BJT: Regimes of Operation - I

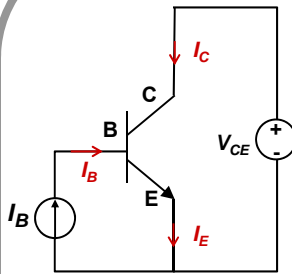

In forward active operation:



$$I_B > 0 \quad V_{BE} > 0 \quad V_{CB} \geq 0$$

Since:  $V_{CE} = V_{CB} + V_{BE}$

$\Rightarrow$  In forward active operation:  $V_{CE} \geq V_{BE}$

$$I_C = qn_i^2 A \left( \frac{D_n}{N_{aB} W_B} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) = \beta_F I_B$$

$\Rightarrow$  Independent of  $V_{CE}$

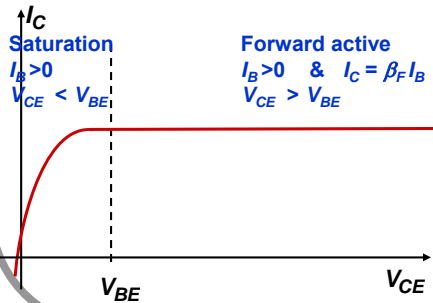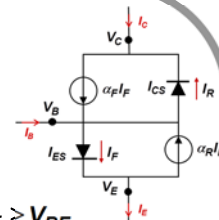

**Forward active:**

Base-emitter junction forward biased  
Base-collector junction reversed biased

$$I_B > 0 \quad V_{BE} > 0 \quad V_{CB} \geq 0$$


**Saturation:**

Base-emitter junction forward biased  
Base-collector junction forward biased

$$I_B > 0 \quad V_{BE} > 0 \quad V_{CB} < 0$$


### Carrier Densities in Different Regimes of Operation

Forward active:

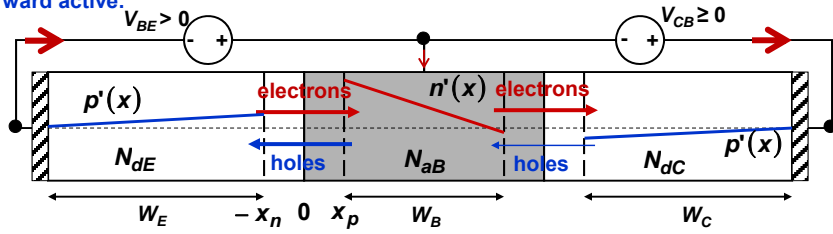



$$N_{dE} \gg N_{aB} > N_{dC}$$

Saturation:

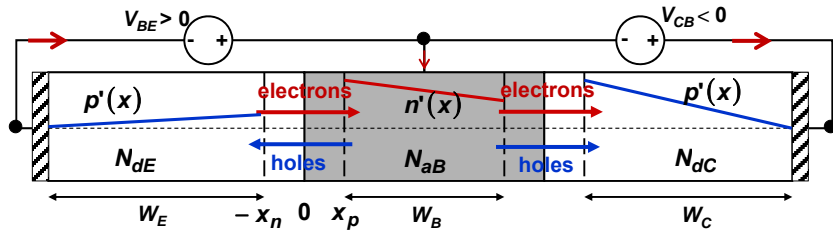

The forward biased base-collector junction reduces the collector current!

### NPN-BJT: Regimes of Operation - II

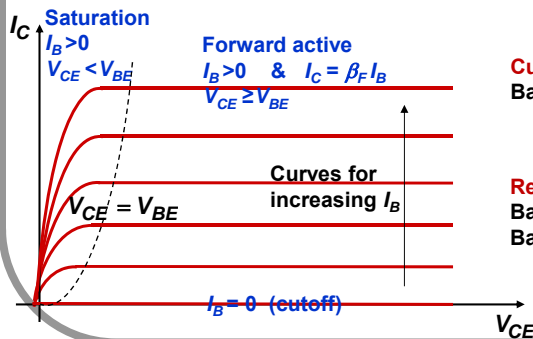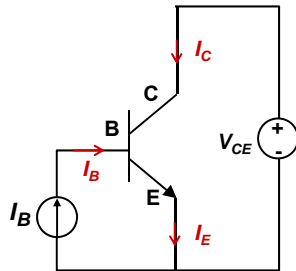

**Forward active:**

Base-emitter junction forward biased  
Base-collector junction reverse biased

$$I_B > 0 \quad V_{BE} > 0 \quad V_{CB} \geq 0$$

**Saturation:**

Base-emitter junction forward biased  
Base-collector junction forward biased

$$I_B > 0 \quad V_{BE} > 0 \quad V_{CB} < 0$$

**Cutoff:**

Base current zero


$$I_B = 0$$

**Reverse active:**


Base-emitter junction reverse biased  
Base-collector junction forward biased

$$I_B > 0 \quad V_{BE} \leq 0 \quad V_{CB} < 0$$
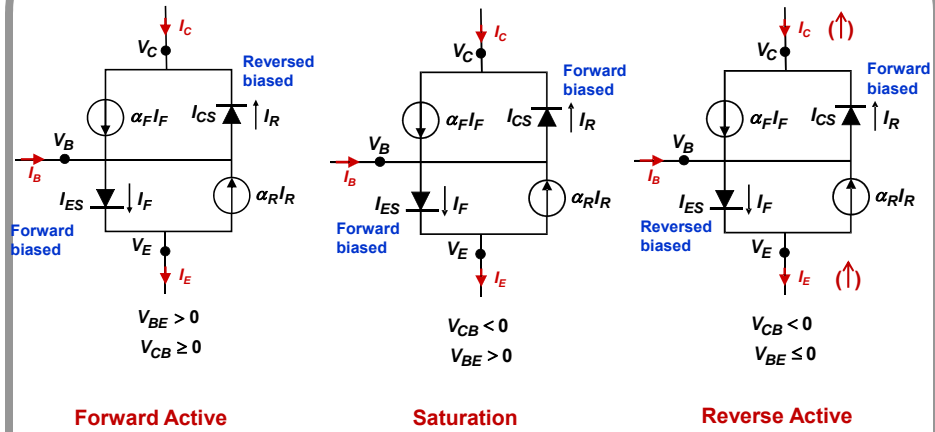
## NPN BJT: Different Regimes of Operation



## NPN BJT: A Simple Amplifier Circuit

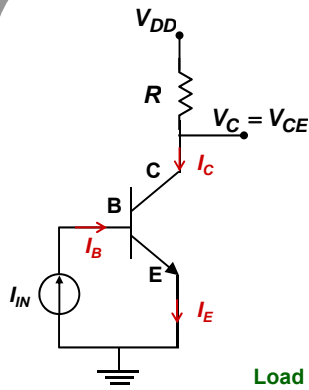


Current gain (in forward active regime):

$$\frac{I_{OUT}}{I_{IN}} = \frac{I_C}{I_B} = \beta_F$$

Load line equation:


$$V_{CE} = V_{DD} - I_C R$$
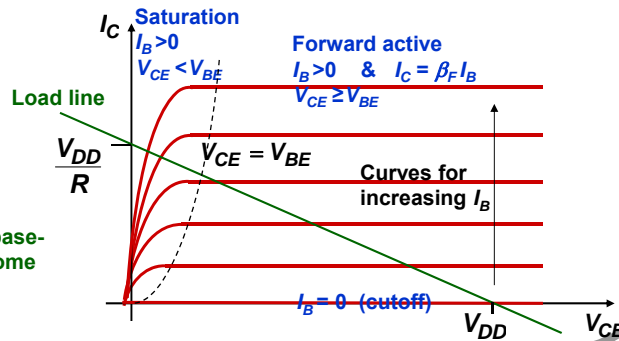
$$\Rightarrow I_C = \frac{V_{DD} - V_{CE}}{R}$$



**Lesson:** Don't let the base-collector junction become forward biased


## NPN BJT

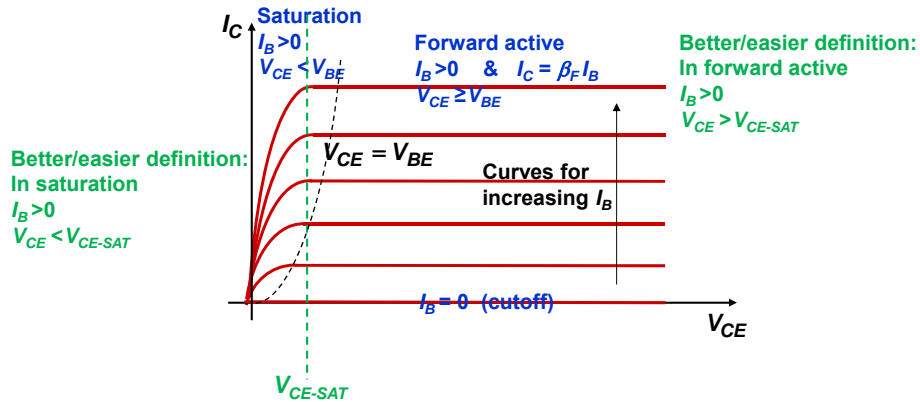

### NPN BJT: Voltage Biasing of a Simple Amplifier Circuit

$V_{BE-ON} \sim 0.6 \text{ V}$   
 $V_{CE-SAT} \sim 0.2 \text{ V}$

Acting as a current source

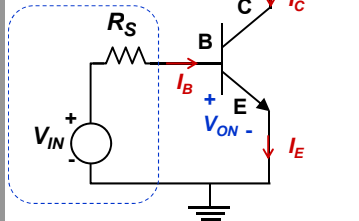

Approximate analysis of transistor DC biasing:

If:  $V_{IN} < V_{BE-ON} \Rightarrow I_B \approx 0 \Rightarrow$  **Transistor in cut-off**

If:  $V_{IN} \geq V_{BE-ON} \Rightarrow$

$$V_{IN} = I_B R_S + V_{BE-ON}$$

$$I_B = \frac{V_{IN} - V_{BE-ON}}{R_S}$$

Assume forward active operation ( $V_{CE} > V_{CE-SAT}$ ):

$$I_C = \beta_F I_B$$


$$V_{OUT} = V_{DD} - I_C R = V_{DD} - \beta_F \left( \frac{V_{IN} - V_{BE-ON}}{R_S} \right) R$$

Final Step - confirm if the assumption of forward active operation was valid:

$$V_{CE} \geq V_{CE-SAT}$$


$$\Rightarrow V_{CE} = V_{OUT} = V_{DD} - I_C R = V_{DD} - \beta_F \left( \frac{V_{IN} - V_{BE-ON}}{R_S} \right) R \geq V_{CE-SAT}$$
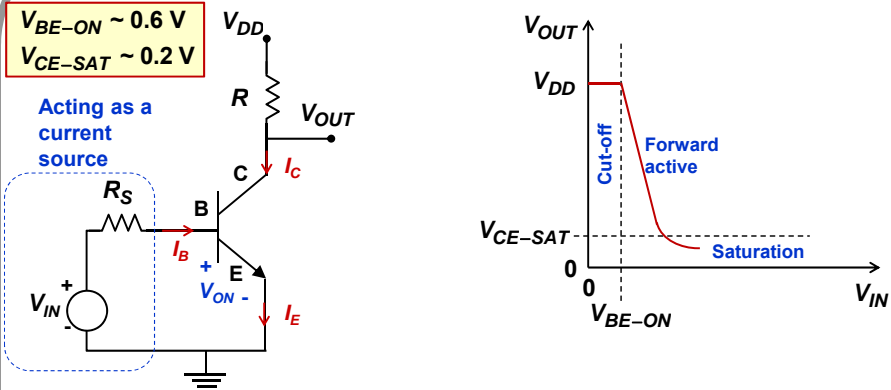
### NPN BJT Amplifier Circuit: Transfer Curve



- If:  $V_{IN} < V_{BE-ON} \Rightarrow I_B \approx 0 \Rightarrow V_{OUT} = V_{DD}$  { Transistor in cut-off
- If:  $V_{IN} \geq V_{BE-ON} \Rightarrow I_B = \frac{V_{IN} - V_{BE-ON}}{R_S}$  { Transistor in forward active
- $V_{OUT} = V_{DD} - I_C R = V_{DD} - \beta_F \frac{R}{R_S} (V_{IN} - V_{BE-ON})$
- If:  $I_B > 0$  &  $V_{CE} = V_{OUT} \leq V_{CE-SAT} \Rightarrow$  { Transistor in saturation

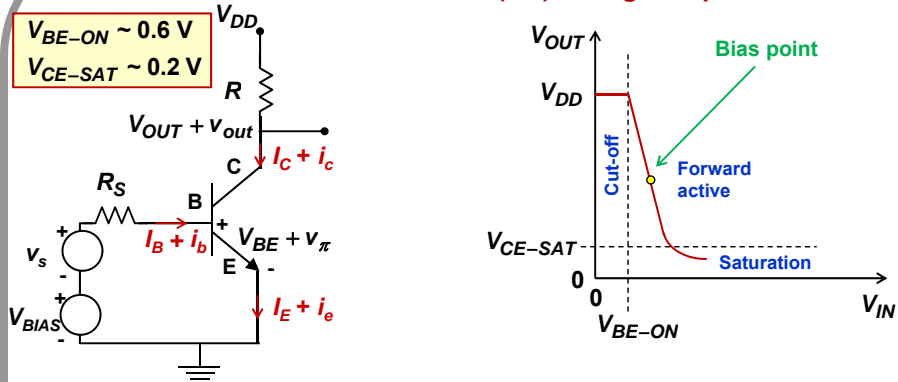
### NPN BJT Common Emitter (CE) Voltage Amplifier



We need better techniques to calculate the voltage gain of such amplifier circuits

We need small signal models of the BJTs!

### NPN BJT: Small Signal Circuit Model

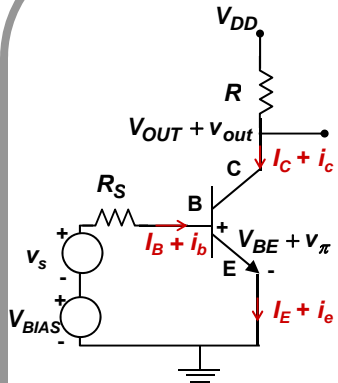

Base current:

$$I_B = qn_i^2 A \left( \frac{D_p}{N_{dE} W_E} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

$$= I_{BS} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

$$\Rightarrow I_B + i_b = I_{BS} \left( e^{\frac{q(V_{BE} + v_\pi)}{KT}} - 1 \right)$$

$$\Rightarrow i_b = \frac{\partial I_B}{\partial V_{BE}} v_\pi = \frac{q(I_B + I_{BS})}{KT} v_\pi \approx \frac{qI_B}{KT} v_\pi = g_\pi v_\pi$$

$$\Rightarrow g_\pi = \frac{qI_B}{KT}$$



Collector current:

$$I_C + i_c = \beta_F (I_B + i_b)$$

$$\Rightarrow i_c = \beta_F i_b = \beta_F g_\pi v_\pi = g_m v_\pi$$

$$g_m = \beta_F g_\pi = \beta_F \frac{qI_B}{KT} = \frac{qI_C}{KT} \quad \leftarrow \text{Increases linearly with the collector current}$$



### NPN BJT: Small Signal Circuit Model

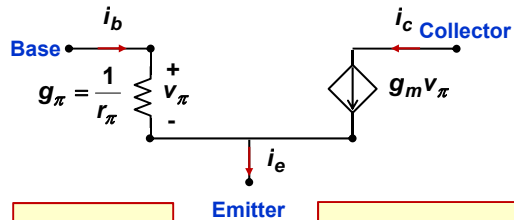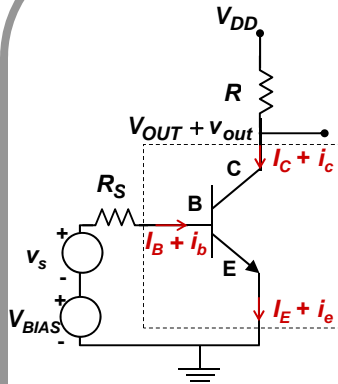

$$g_\pi = \frac{qI_B}{KT}$$

$$g_m = \beta_F g_\pi = \frac{qI_C}{KT}$$
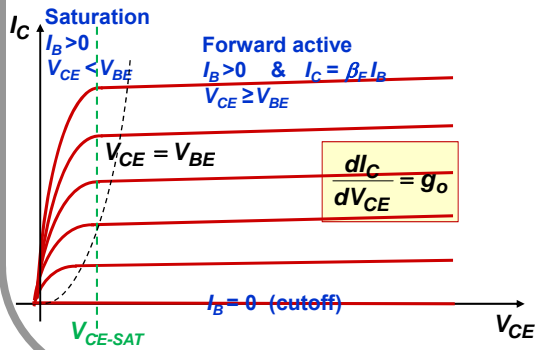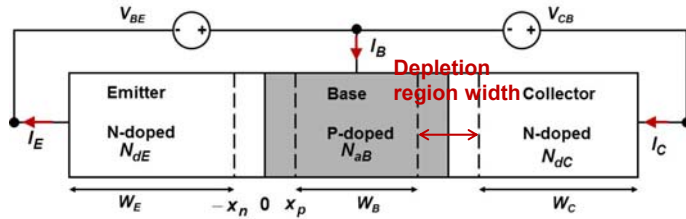
### NPN BJT: Forward Active Current vs $V_{CE}$




As  $V_{CE}$  becomes more positive, the base-collector junction becomes more reverse biased, and the thickness of the depletion increases thereby reducing the thickness  $W_B$  of the base

Consequently, the collector current increases

The output conductance  $g_o$  is not zero!
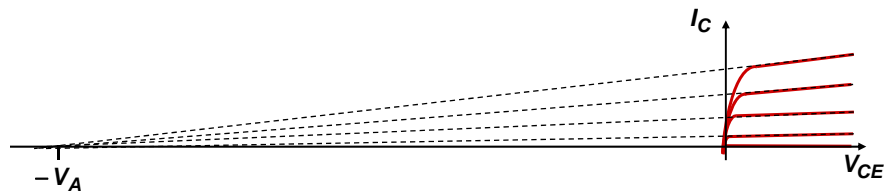
### NPN BJT: Output Conductance and the Early Voltage




The slope of the  $I_C$  vs  $V_{CE}$  curves are modeled using the early voltage  $V_A$ :

$$\frac{dI_C}{dV_{CE}} = g_o = \frac{I_C}{V_A} = \lambda_n I_C$$

The early voltage is usually in the 50-200 V range




### NPN BJT: Output Conductance

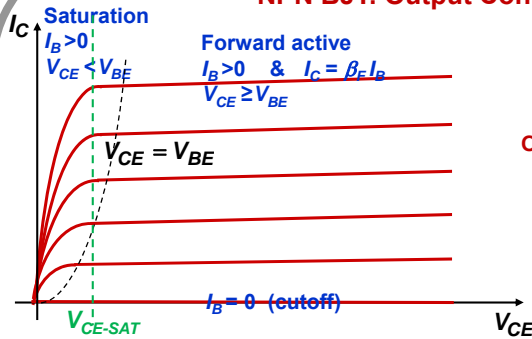


Output conductance:
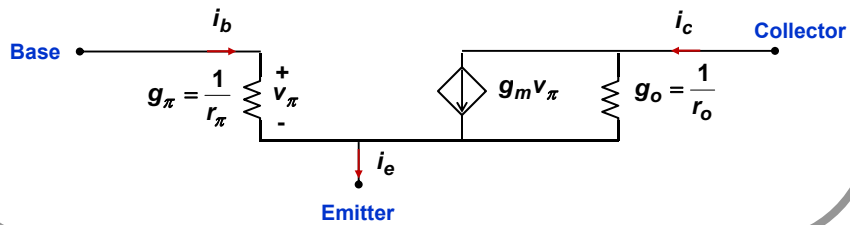
$$g_o = \frac{1}{r_o} = \frac{\partial I_C}{\partial V_{CE}}$$


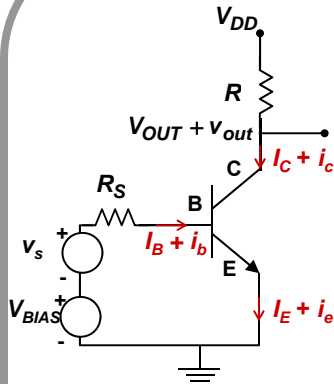
### NPN BJT Common Emitter (CE) Voltage Amplifier



$$v_{\pi} = v_s \frac{r_{\pi}}{r_{\pi} + R_s}$$

$$i_c = g_m v_{\pi} + \frac{v_{out}}{r_o}$$


$$v_{out} = -i_c R$$

$$\Rightarrow v_{out} = -g_m (r_o \parallel R) v_{\pi}$$


$$\Rightarrow v_{out} = -g_m (r_o \parallel R) \frac{r_{\pi}}{r_{\pi} + R_s} v_s$$

Voltage gain:
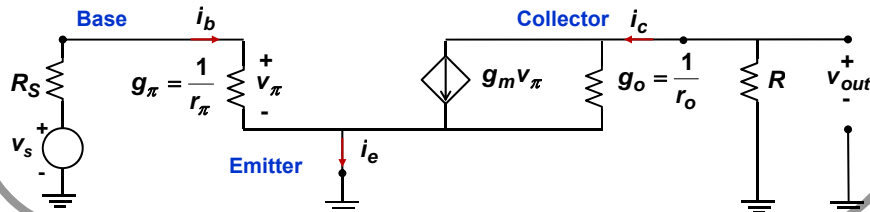
$$A_v = \frac{v_{out}}{v_s} = -g_m (r_o \parallel R) \frac{r_{\pi}}{r_{\pi} + R_s}$$


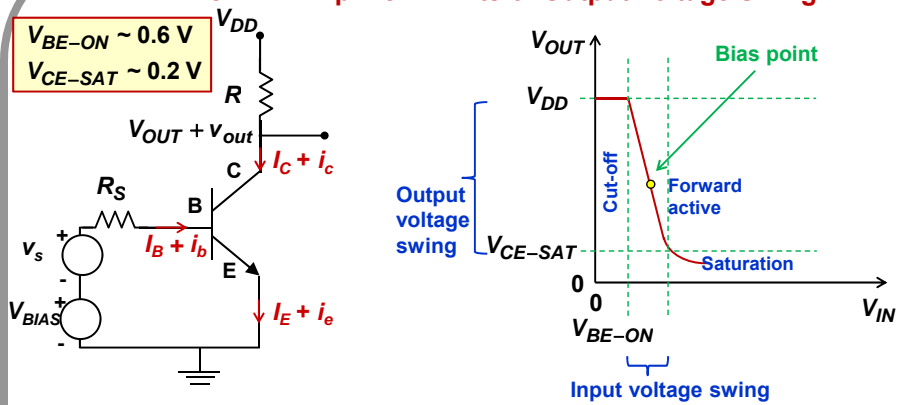
### NPN BJT CE Amplifier: Limits of Output Voltage Swing



### A Silicon NPN BJT

