

## Lecture 19


### High Frequency Analysis of FET Circuits

---

In this lecture you will learn:

- High Frequency Analysis of FET Circuits
- Miller Effect and the Miller Capacitance
- The Transition Frequency and the Ultimate Performance limits of FET Devices

### Phasor Analysis: Complex Impedances

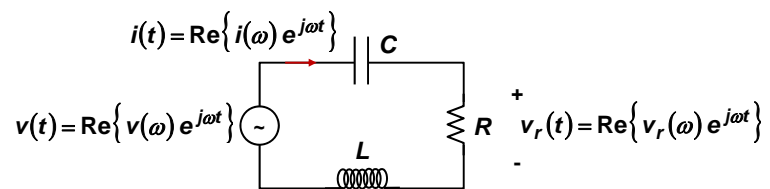


Capacitive Impedance/Admittance:

$$Z(\omega) = \frac{1}{Y(\omega)} = \frac{1}{j\omega C}$$

Inductance Impedance/Admittance:

$$Z(\omega) = \frac{1}{Y(\omega)} = j\omega L$$
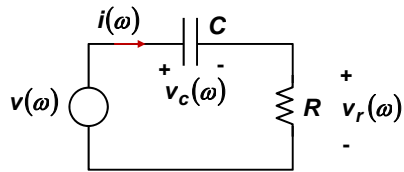
### Phasor Analysis: Calculations with Impedances




One can compute the voltage phasors using the impedances:

$$v_c(\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} v(\omega) = \frac{1}{1 + j\omega RC} v(\omega)$$

$$v_r(\omega) = \frac{R}{R + \frac{1}{j\omega C}} v(\omega) = \frac{j\omega RC}{1 + j\omega RC} v(\omega)$$
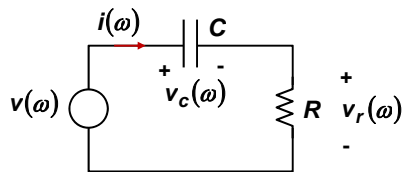
### Phasor Analysis: Calculations with Impedances




One can compute the voltage phasors using the impedances:


$$v_c(\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} v(\omega) = \frac{1}{1 + j\omega RC} v(\omega)$$

$$v_r(\omega) = \frac{R}{R + \frac{1}{j\omega C}} v(\omega) = \frac{j\omega RC}{1 + j\omega RC} v(\omega)$$


### Phasor Analysis: Bode Plots

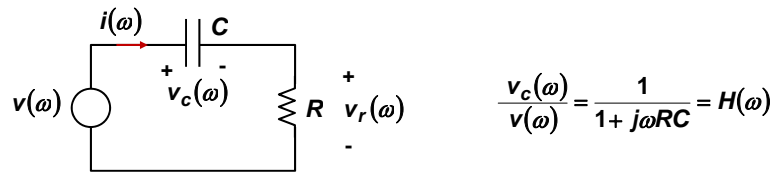

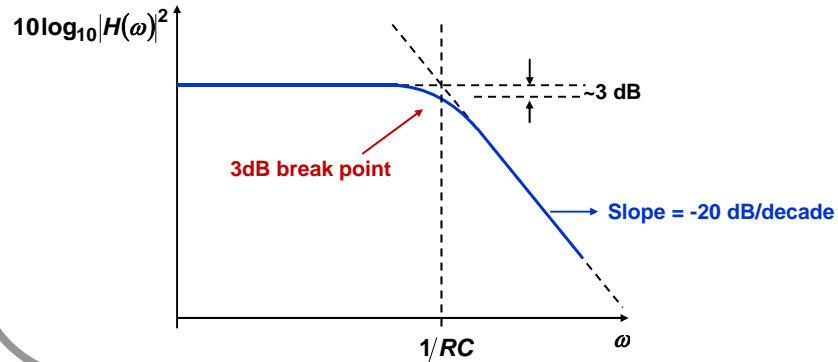
A transfer function with a pole at frequency  $1/RC$




### Phasor Analysis: Bode Plots

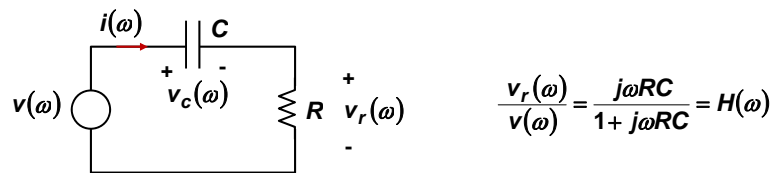

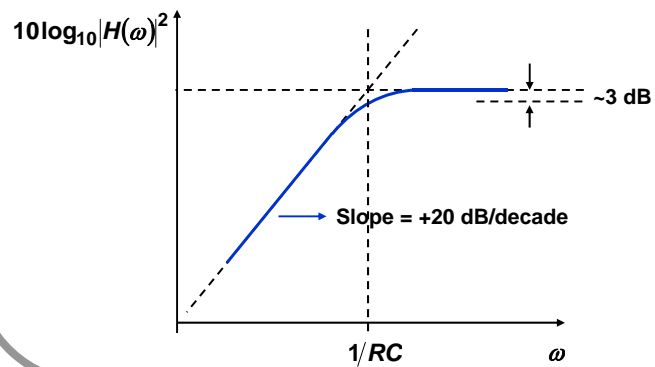
A transfer function with a zero at zero frequency and a pole at frequency  $1/RC$



### NFET: Capacitances

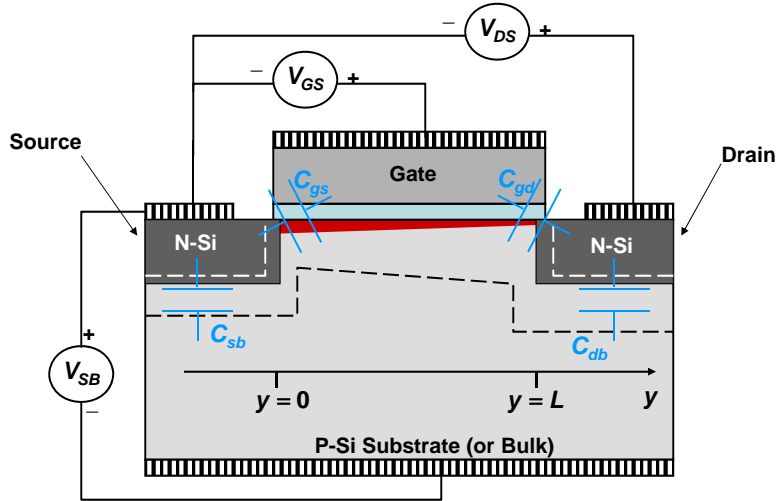

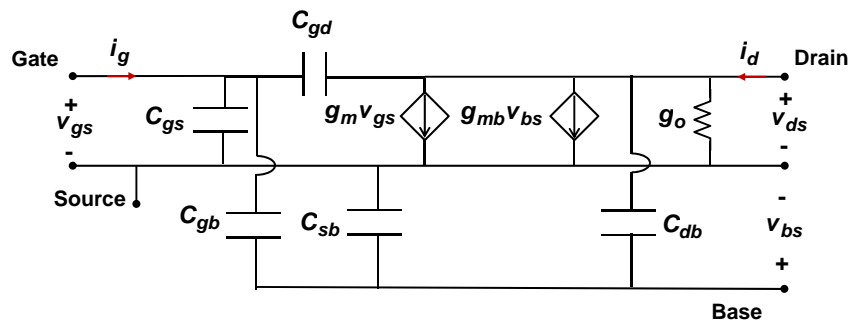
### NFET: High Frequency Small Signal Model




### Capacitances

**In Saturation:**


$$C_{gs} = \left. \frac{\partial Q_G}{\partial V_{GS}} \right|_{V_{GD}, V_{GB}} = \frac{2}{3} WLC_{ox} + WC_{ov} + WC_p \neq \frac{2}{3} WLC_{ox}$$
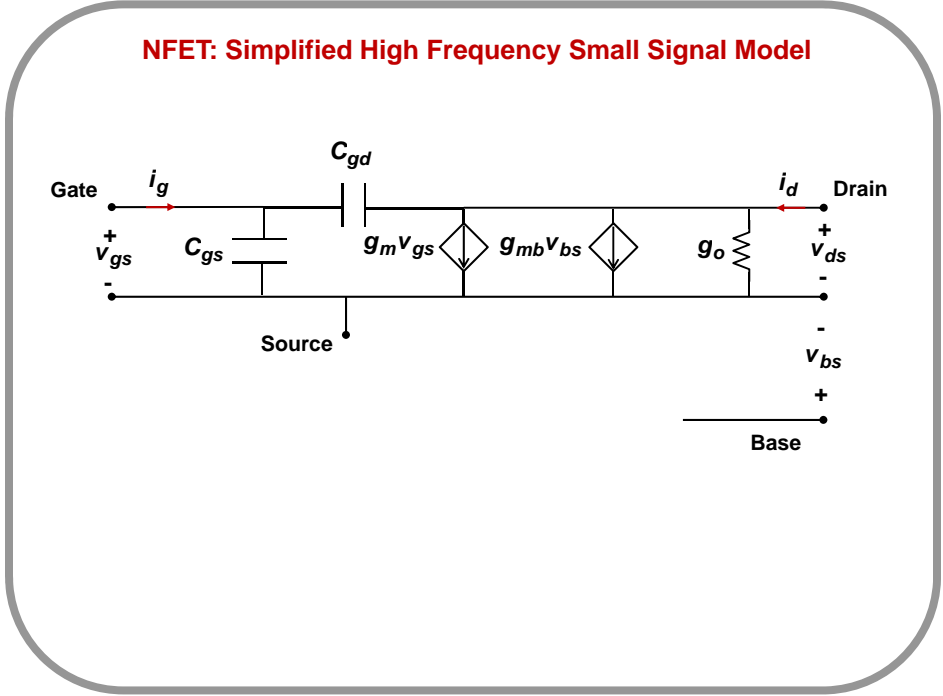
$$C_{gd} = \left. \frac{\partial Q_G}{\partial V_{GD}} \right|_{V_{GS}, V_{GB}} = WC_{ov} + WC_p \neq 0$$


### The Common Source Amplifier

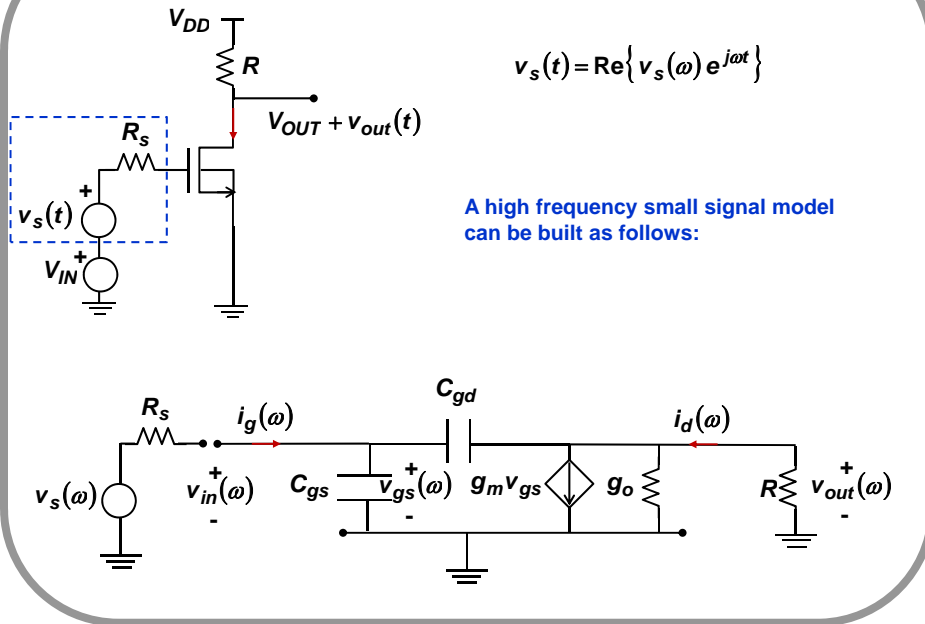
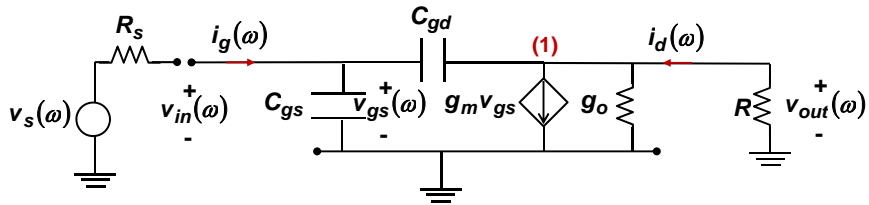
### The Common Source Amplifier: Open Circuit Voltage Gain



Need to find:

$$A_v(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} \quad \text{and} \quad H(\omega) = \frac{v_{out}(\omega)}{v_s(\omega)}$$

KCL at (1) gives:

$$i_d(\omega) = g_o v_{out}(\omega) + g_m v_{in}(\omega) + [v_{out}(\omega) - v_{in}(\omega)]j\omega C_{gd}$$

Also:


$$v_{out}(\omega) = -i_d(\omega)R$$

The above two give:


$$A_v(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = -\frac{g_m R - j\omega R C_{gd}}{1 + g_o R + j\omega R C_{gd}}$$
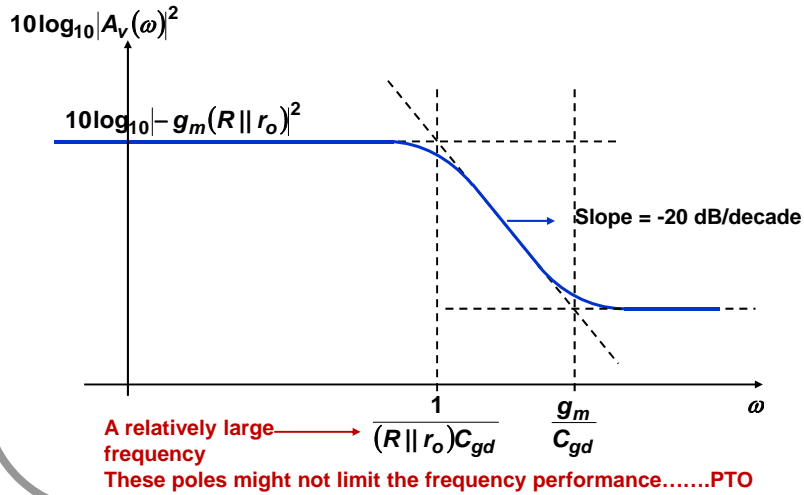
### The Common Source Amplifier: Open Circuit Voltage Gain

$$A_v(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = -\frac{g_m R - j\omega R C_{gd}}{1 + g_o R + j\omega R C_{gd}} = -g_m (R \parallel r_o) \frac{1 - j\omega \frac{C_{gd}}{g_m}}{1 + j\omega C_{gd} (R \parallel r_o)}$$


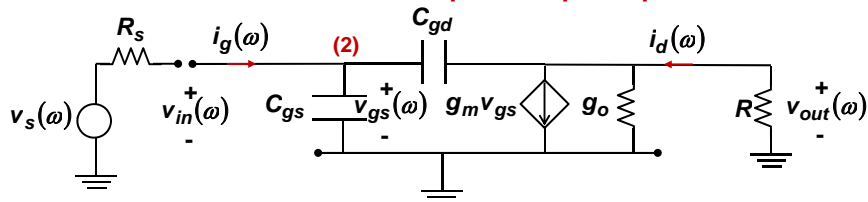
### The Common Source Amplifier: Input Impedance



KCL at (2) gives:

$$i_g(\omega) = \frac{v_s(\omega) - v_{in}(\omega)}{R_s} \quad \left\{ \frac{v_{out}(\omega)}{v_{in}(\omega)} = A_v(\omega) \right.$$

$$= j\omega C_{gs} v_{in}(\omega) + j\omega C_{gd} [v_{in}(\omega) - v_{out}(\omega)]$$


$$= (j\omega C_{gs} + j\omega C_{gd} [1 - A_v(\omega)]) v_{in}(\omega)$$

$$\frac{v_{in}(\omega)}{i_g(\omega)} = Z_{in}(\omega) = \frac{1}{j\omega C_{gs} + j\omega C_{gd} [1 - A_v(\omega)]}$$

The input impedance is:

$$Z_{in}(\omega) \approx \frac{1}{j\omega [C_{gs} + C_{gd} (1 - A_v(\omega))]}$$
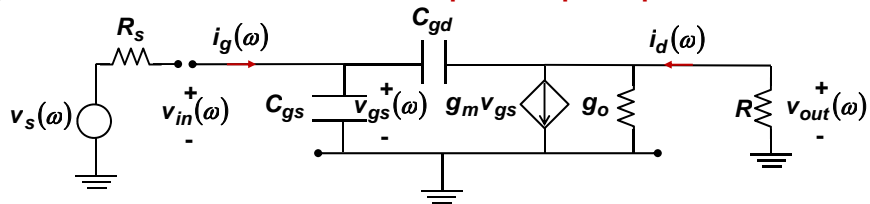
### The Common Source Amplifier: Input Impedance




Looking in from the input terminal the capacitance  $C_{gd}$  seems to be magnified by a factor proportional to the open circuit voltage gain of the amplifier!!

$$\frac{v_{in}(\omega)}{v_s(\omega)} \approx \frac{Z_{in}(\omega)}{R_s + Z_{in}(\omega)} = \frac{1}{1 + j\omega [C_{gs} + C_{gd}(1 - A_v(\omega))]R_s}$$

Looking in from the input terminal the capacitance  $C_{gd}$  seems to be magnified by a factor proportional to the open circuit voltage gain of the amplifier!!
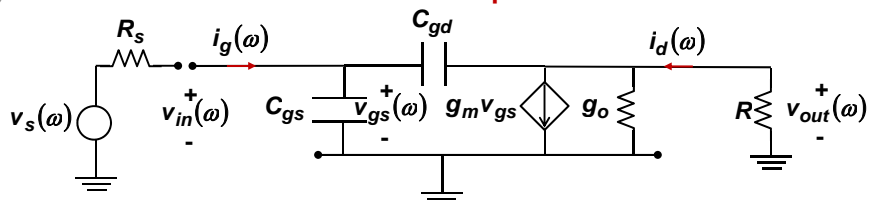
### The Common Source Amplifier: Total Gain



Finally:

$$H(\omega) = \frac{v_{out}(\omega)}{v_s(\omega)} = \frac{v_{out}(\omega)}{v_{in}(\omega)} \frac{v_{in}(\omega)}{v_s(\omega)} = A_v(\omega) \frac{Z_{in}(\omega)}{R_s + Z_{in}(\omega)} = \frac{A_v(\omega)}{1 + j\omega [C_{gs} + C_{gd}(1 - A_v(\omega))]R_s}$$

Where:

$$A_v(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = -g_m (R \parallel r_o) \left[ \frac{1 - j\omega C_{gd}}{1 + j\omega C_{gd} (R \parallel r_o)} \right]$$



### The Common Source Amplifier: Poles and Zeros of the Total Gain

$$H(\omega) = \frac{A_v(\omega)}{1 + j\omega[C_{gs} + C_{gd}(1 - A_v(\omega))]R_s} = \frac{H(0)(1 - j\omega\tau_3)}{(1 + j\omega\tau_1)(1 + j\omega\tau_2)}$$

A little tedious algebra can show that the transfer function above has two poles and a zero

$$H(0) \approx -g_m(R \parallel r_o) \quad \frac{1}{\tau_3} = \frac{g_m}{C_{gd}}$$

1) Assuming  $g_m R_s \gg 1$ , these poles are:

$$\frac{1}{\tau_1} \approx \frac{g_m}{C_{gs}} + \frac{1}{C_{gd}(R \parallel r_o)} \quad \frac{1}{\tau_2} \approx \frac{1}{[C_{gs} + C_{gd}(g_m(R \parallel r_o))] R_s}$$

This pole will likely determine the smallest frequency at which the total gain rolls over

2) Assuming  $g_m R_s \ll 1$ , these poles are:

$$\frac{1}{\tau_1} \approx \frac{1}{R_s C_{gs}} \quad \frac{1}{\tau_2} \approx \frac{1}{C_{gd}(R \parallel r_o)}$$

This pole will likely determine the smallest frequency at which the total gain rolls over

### The Common Source Amplifier: The Miller Approximation

If the poles and zeros in  $A_v(\omega)$  are at a higher frequency than the poles and zeros associated with the transfer function  $v_{in}(\omega)/v_s(\omega)$  (which would be the case if  $g_m R_s \gg 1$ ) then one may approximate the open circuit gain  $A_v(\omega)$  by its low frequency value:

$$A_v(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = -\frac{g_m R - j\omega R C_{gd}}{1 + g_o R + j\omega R C_{gd}} \approx -g_m(R \parallel r_o) \quad \left[ \begin{array}{l} \text{Miller} \\ \text{approximation} \end{array} \right]$$

And then:


$$H(\omega) = \frac{v_{out}(\omega)}{v_s(\omega)} = \frac{v_{out}(\omega)}{v_{in}(\omega)} \frac{v_{in}(\omega)}{v_s(\omega)} = A_v(\omega) \frac{Z_{in}(\omega)}{R_s + Z_{in}(\omega)} \approx \frac{-g_m(R \parallel r_o)}{1 + j\omega[C_{gs} + C_{gd}(1 + g_m(R \parallel r_o))] R_s}$$

Looking in from the input terminal the capacitance  $C_{gd}$  seems to be magnified by a factor proportional to the low frequency open circuit voltage gain of the amplifier!!

And now the single pole is at:


$$\frac{1}{\tau} \approx \frac{1}{[C_{gs} + C_{gd}(1 + g_m(R \parallel r_o))] R_s}$$
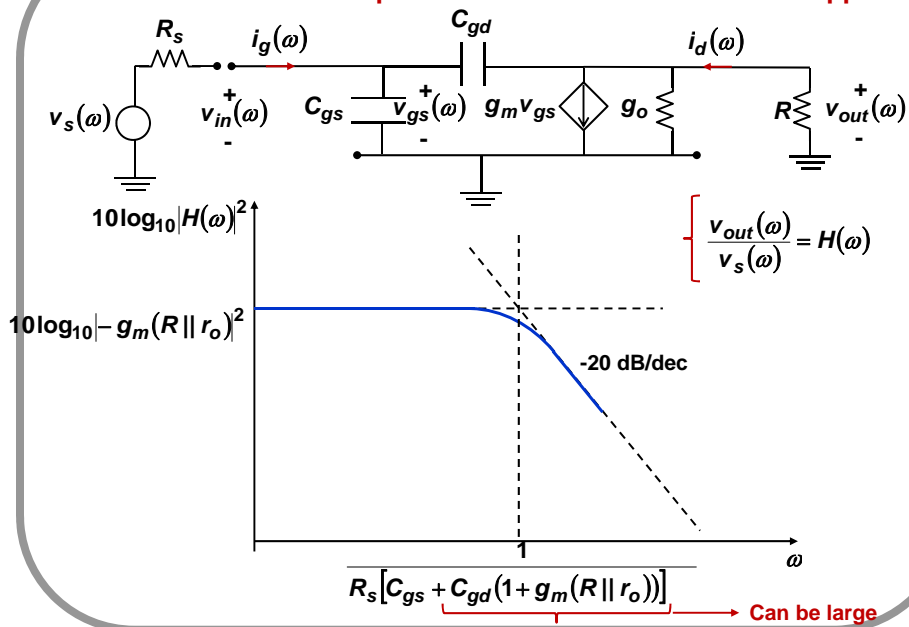
### The Common Source Amplifier: Total Gain Under the Miller Approx


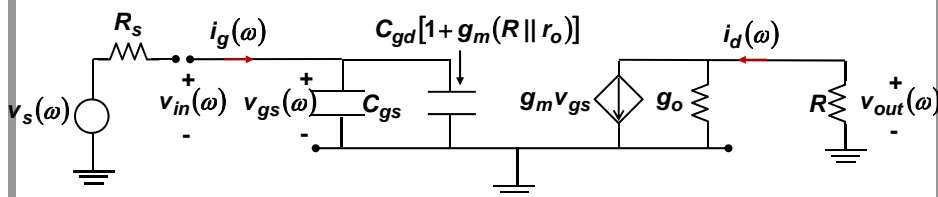
### The Common Source Amplifier: Input Impedance

This approximate equivalent circuit will also work at not too high frequencies.....




Looking in from the input terminal the capacitance  $C_{gd}$  seems to be magnified by a factor proportional to the low frequency open circuit voltage gain of the amplifier!!

$$Z_{in}(\omega) \approx \frac{1}{j\omega [C_{gs} + C_{gd}(1 + g_m(R \parallel r_o))]}$$

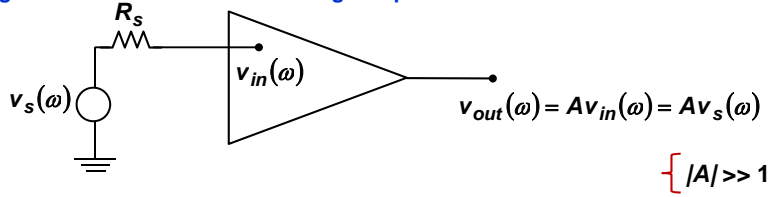
### The Miller Effect and the Miller Capacitance

John A. Miller (1920)

Lets generalize a bit: Consider a voltage amplifier:



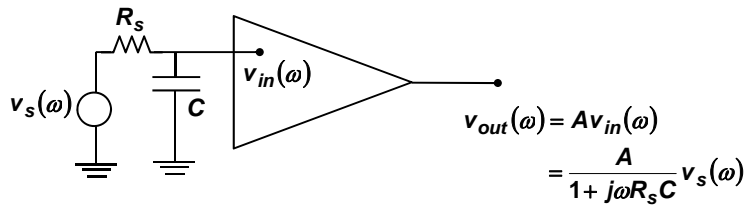
Consider now a capacitor sitting at the input of an amplifier:



Input voltage to the amplifier decreases and so does the output voltage of the amplifier at high frequencies (but not too bad.....)
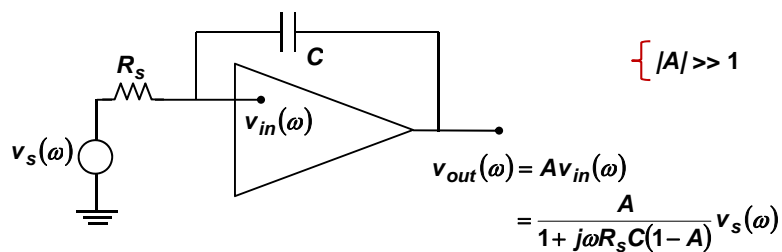
### The Miller Effect and the Miller Capacitance


Consider now a capacitor straddling the input and the output of an amplifier:



Input voltage to the amplifier decreases and so does the output voltage of the amplifier at high frequencies  
But the effective capacitance seen from the input side now is bigger (compared to the case on the previous slide) by a factor proportional to the gain of the amplifier

The amplifier input voltage, and the output voltage, will now begin to drop-off at a much lower frequency!!  
This is the Miller effect and the capacitance positioned this way is called the Miller capacitance
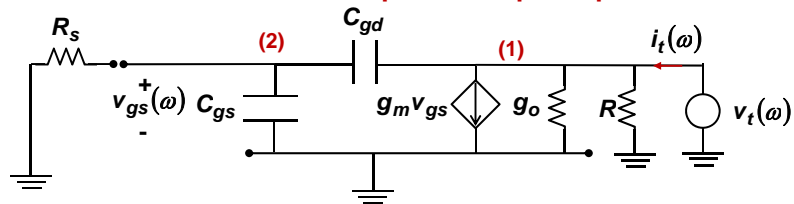
### The Common Source Amplifier: Output Impedance



Need to find:

$$Z_{out}(\omega)$$


KCL at (2) gives:

$$[v_t(\omega) - v_{gs}(\omega)]j\omega C_{gd} = j\omega C_{gs}v_{gs} + \frac{v_{gs}}{R_s}$$

This gives:

$$v_{gs}(\omega) = \frac{j\omega C_{gd}R_s}{j\omega(C_{gs} + C_{gd})R_s + 1} v_t(\omega)$$
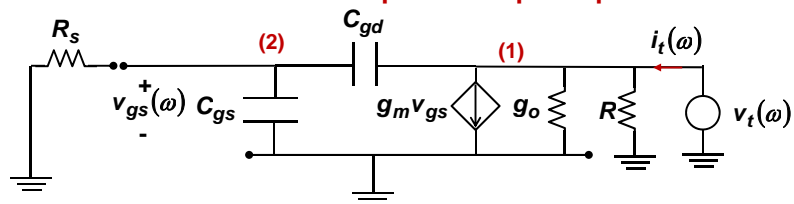
### The Common Source Amplifier: Output Impedance



$$v_{gs}(\omega) = \frac{j\omega C_{gd}R_s}{j\omega(C_{gs} + C_{gd})R_s + 1} v_t(\omega)$$


KCL at (1) gives:

$$i_t(\omega) = \frac{v_t(\omega)}{R \parallel r_o} + g_m v_{gs}(\omega) + [v_t(\omega) - v_{gs}(\omega)]j\omega C_{gd}$$

$$\Rightarrow \frac{1}{Z_{out}(\omega)} = \frac{1}{R \parallel r_o} + \frac{(g_m + j\omega C_{gs})j\omega C_{gd}R_s}{j\omega(C_{gs} + C_{gd})R_s + 1}$$

↑  
Not a bad approximation  
even at moderately high  
frequencies
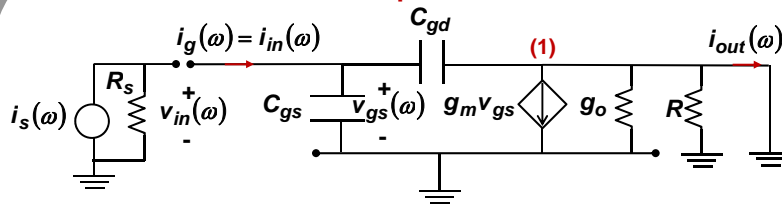
### The Common Source Amplifier: Short Circuit Current Gain



Need to find:

$$\frac{i_{out}(\omega)}{i_{in}(\omega)} \quad \left[ \quad Z_{in}(\omega) \approx \frac{1}{j\omega[C_{gs} + C_{gd}]} \right]$$

Start from KCL at (1):

$$(0 - v_{in}(\omega))j\omega C_{gd} + g_m v_{in}(\omega) + i_{out}(\omega) = 0$$

$$\Rightarrow \frac{i_{out}(\omega)}{v_{in}(\omega)} = -(g_m - j\omega C_{gd})$$

$$\Rightarrow \frac{i_{out}(\omega)}{i_{in}(\omega)} = \frac{i_{out}(\omega)}{v_{in}(\omega)} \frac{v_{in}(\omega)}{i_{in}(\omega)} = -(g_m - j\omega C_{gd}) Z_{in}(\omega) \approx -g_m Z_{in}(\omega)$$


$$= -\frac{g_m}{j\omega(C_{gs} + C_{gd})}$$

### Short Circuit Current Gain and the Transition Frequency ( $f_T$ or $\omega_T$ )

For most transistors, the short circuit current gain falls off with frequency with a -20 dB/dec slope (at high enough frequencies)


The frequency at which the short circuit current gain equals unity is called the transition frequency ( $f_T$  or  $\omega_T$ )

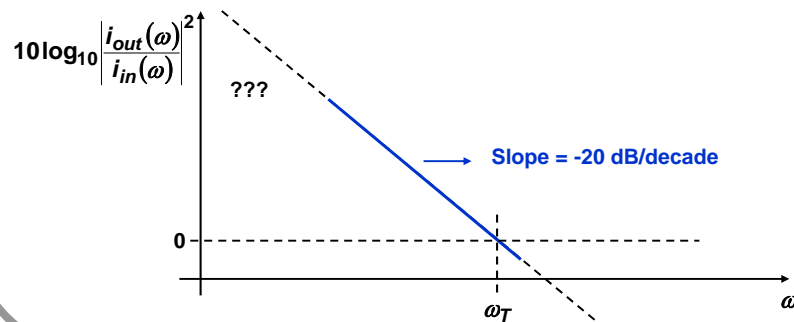The transition frequency expresses the maximum useful frequency of operation of the transistor


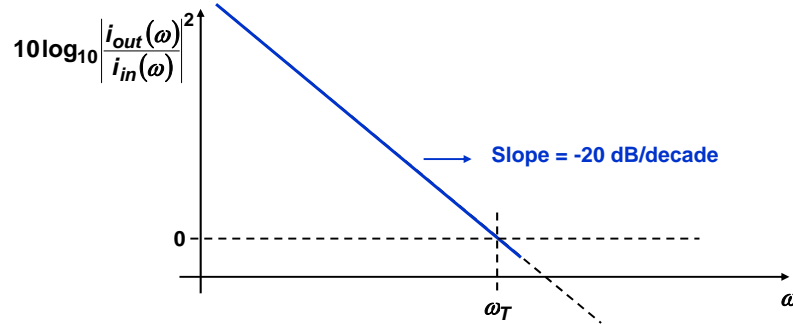
### The Common Source Amplifier: The Transition Frequency

$$\frac{i_{out}(\omega)}{i_{in}(\omega)} = -\frac{g_m}{j\omega(C_{gs} + C_{gd})}$$



The transition frequency is:

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}} \approx \frac{g_m}{C_{gs}}$$

### The Common Source Amplifier: The Transition Frequency

The FET transition frequency is:


$$\omega_T \approx \frac{g_m}{C_{gs}}$$

This is the highest frequency at which the transistor is still useful

Q: What is its physical significance?

$$g_m = \frac{W}{L} \mu_n C_{ox} (V_{GS} - V_{TN})$$

$$C_{gs} = \frac{2}{3} W L C_{ox}$$

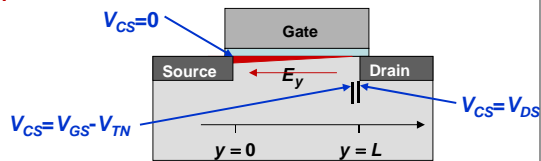

Therefore the transition frequency is:

$$\omega_T = \frac{g_m}{C_{gs}} = \frac{3}{2} \mu_n \frac{(V_{GS} - V_{TN})}{L^2}$$

$$\omega_T \propto \mu_n \frac{(V_{GS} - V_{TN})}{L^2} = \frac{\mu_n (V_{GS} - V_{TN})}{L} = \frac{\mu_n |E_y|}{L} = \frac{v_n}{L} = \frac{1}{\tau_t}$$

Electron transit time through the FET

Therefore, the electron transit time sets the maximum frequency of operation of the FET!!