

## Lecture 22


### Circuit Design Techniques and Applications – II

#### Wireless Communications


In this lecture you will learn:

- Circuits for wireless communications
- Signal multipliers and mixers
- Single-balanced and double-balanced mixers
- Sample and hold circuits
- Analog to digital converters
- Digital to analog converters

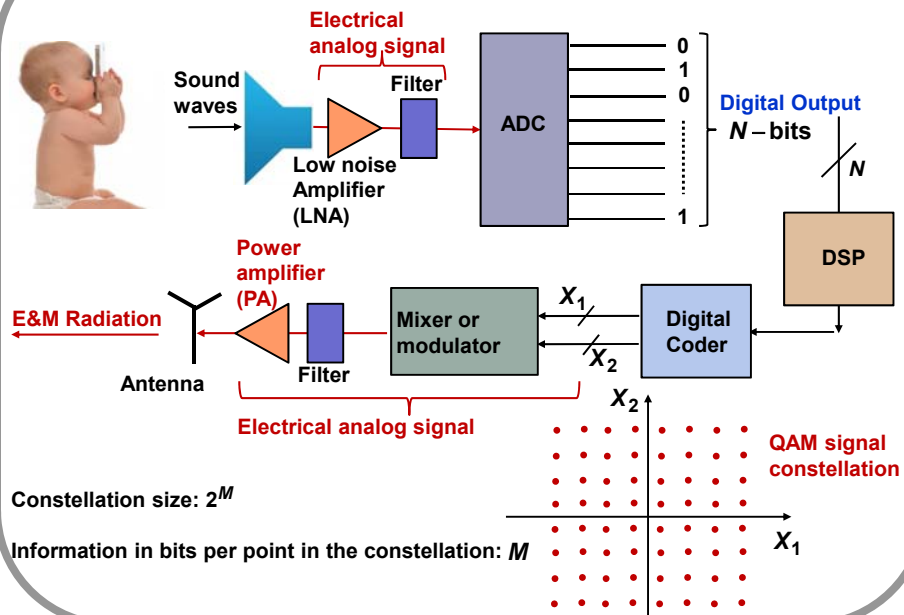
#### Signal Transmission in Wireless Communications



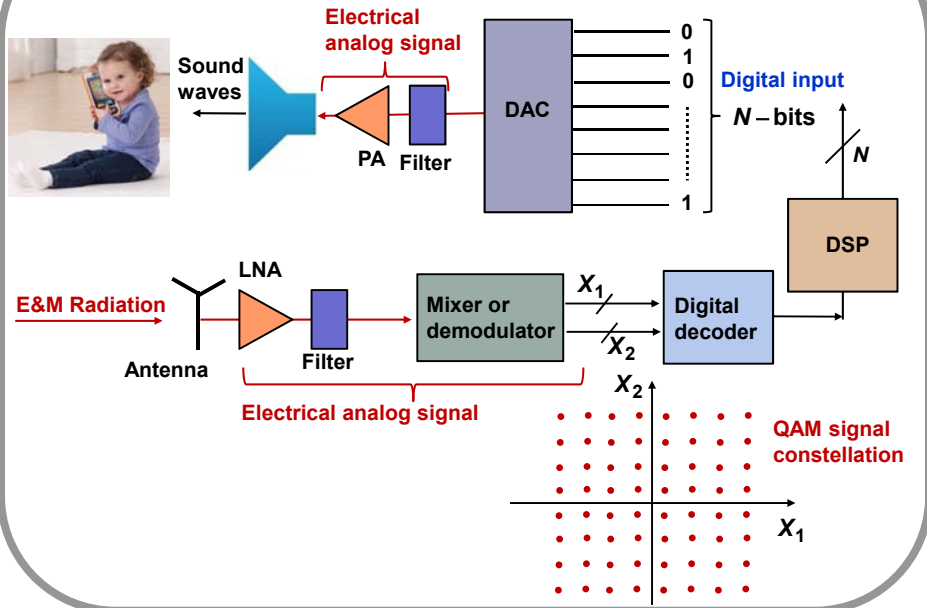
## Signal Reception in Wireless Communications




## RF Mixer or Modulator/Demodulator

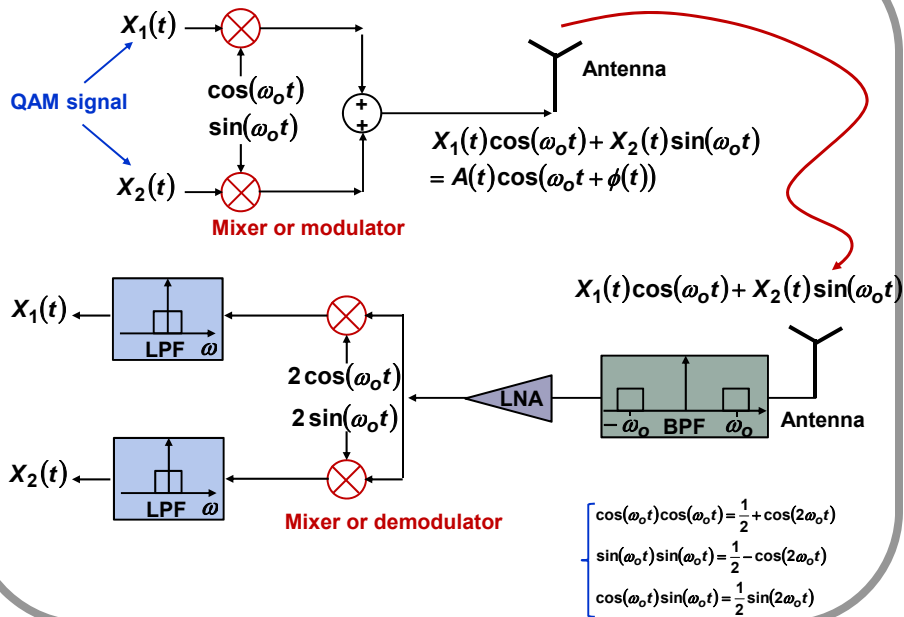
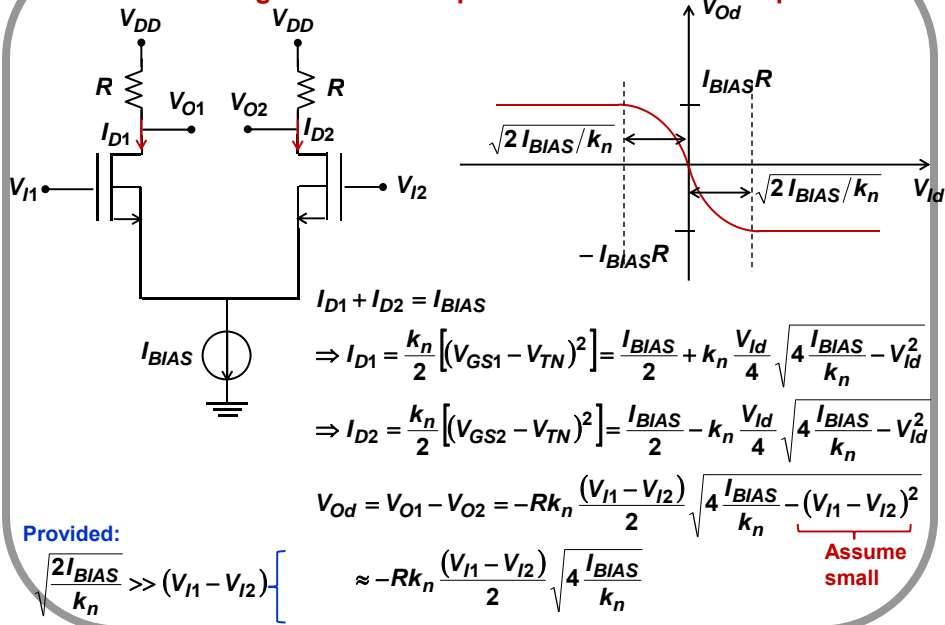
### FET Signal Mixer/Multiplier: Review of a Diff Amp



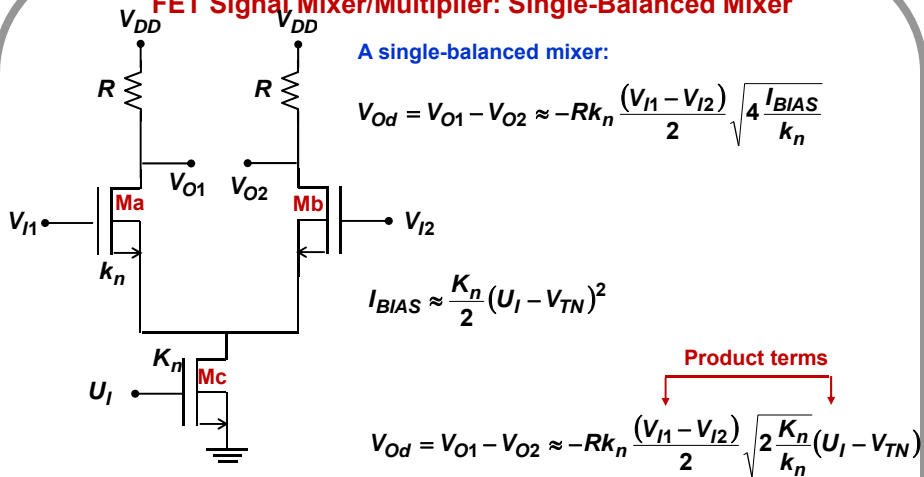
### FET Signal Mixer/Multiplier: Single-Balanced Mixer



But still not quite what one would want.....

- i) The input voltage  $U_1$  is not differential.....
- ii) The two input voltages being multiplied don't appear symmetrically in the final answer
- iii) There is an additional term proportional only to  $V_{I1} - V_{I2}$  in the output
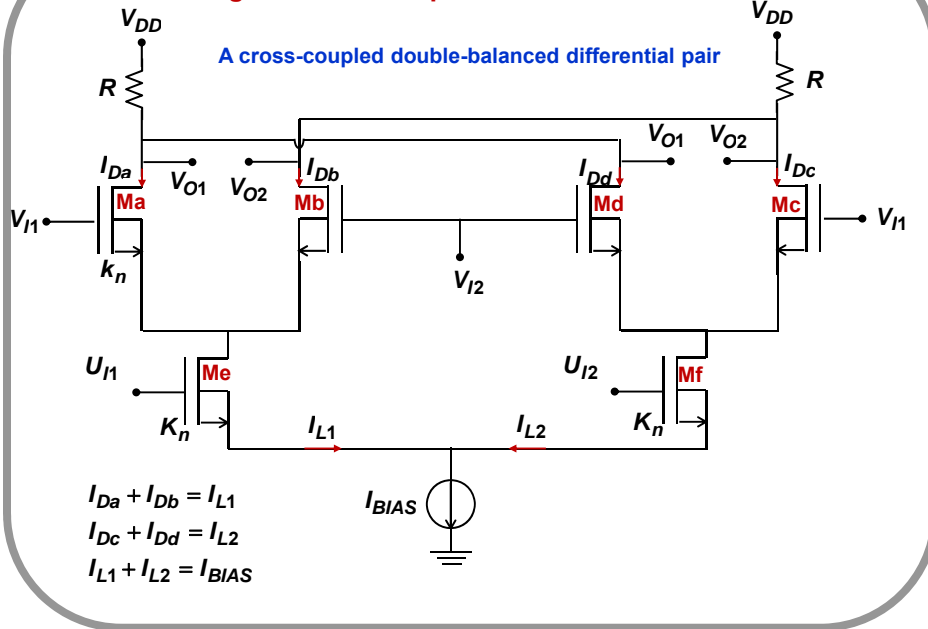
### FET Signal Mixer/Multiplier: A Double-Balanced Mixer



### FET Signal Mixer/Multiplier: A Double-Balanced Mixer

A cross-coupled double-balanced differential pair

$I_{Da} + I_{Db} = I_{L1}$   
 $I_{Dc} + I_{Dd} = I_{L2}$   
 $I_{L1} + I_{L2} = I_{BIAS}$


$I_{Da} = \frac{k_n}{2} [(V_{GSa} - V_{TN})^2] \approx \frac{I_{L1}}{2} + k_n \frac{V_{Id}}{4} \sqrt{4 \frac{I_{L1}}{k_n}}$   
 $I_{Db} = \frac{k_n}{2} [(V_{GSb} - V_{TN})^2] \approx \frac{I_{L1}}{2} - k_n \frac{V_{Id}}{4} \sqrt{4 \frac{I_{L1}}{k_n}}$   
 $I_{Dc} = \frac{k_n}{2} [(V_{GSc} - V_{TN})^2] \approx \frac{I_{L2}}{2} + k_n \frac{V_{Id}}{4} \sqrt{4 \frac{I_{L2}}{k_n}}$   
 $I_{Dd} = \frac{k_n}{2} [(V_{GSd} - V_{TN})^2] \approx \frac{I_{L2}}{2} - k_n \frac{V_{Id}}{4} \sqrt{4 \frac{I_{L2}}{k_n}}$

$V_{Od} = V_{O1} - V_{O2} = -(I_{Da} + I_{Dd})R + (I_{Dc} + I_{Db})R$   
 $\approx -Rk_n \frac{(V_{I1} - V_{I2})}{2} \left( \sqrt{4 \frac{I_{L1}}{k_n}} - \sqrt{4 \frac{I_{L2}}{k_n}} \right)$   
 $= -Rk_n \frac{(V_{I1} - V_{I2})}{2} \sqrt{2 \frac{K_n}{k_n}} (U_{I1} - U_{I2})$   
 $= -R \sqrt{\frac{k_n K_n}{2}} (V_{I1} - V_{I2}) (U_{I1} - U_{I2})$

$V_{Id} = V_{I1} - V_{I2}$   
 $U_{Id} = U_{I1} - U_{I2}$   
 $V_{Od} \propto (V_{I1} - V_{I2})(U_{I1} - U_{I2}) = V_{Id} U_{Id}$


Exactly what one would want! → Product terms
 
### Analog-to-Digital Converters(ADCs) and Digital-to-Analog Converters (DACs)





Resolution:  $\frac{V_{MAX} - V_{MIN}}{2^N - 1}$

Dynamic Range:  $20 \log_{10} \left( \frac{|V_{MAX}|}{|V_{MIN}|} \right)$

 


### Analog-to-Digital Converters (ADCs)

  

Analog value, corresponding to a digital value, is:


$$V_{MIN} + \frac{(V_{MAX} - V_{MIN})}{(2^N - 1)} [2^{N-1} B_{N-1} + 2^{N-2} B_{N-2} + \dots + 2^2 B_2 + 2^1 B_1 + B_0]$$
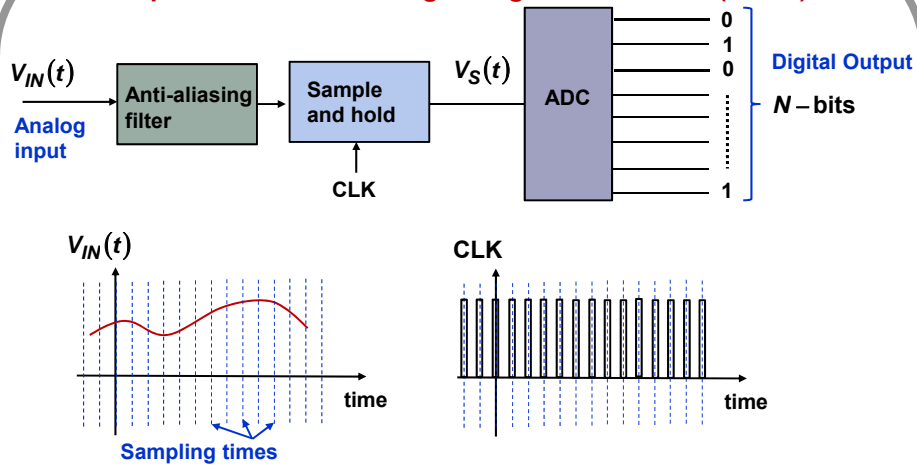
### Sample and Hold in Analog-to-Digital Converters (ADCs)




Sample the input waveform periodically and hold the sampled value in place till the next sampling event

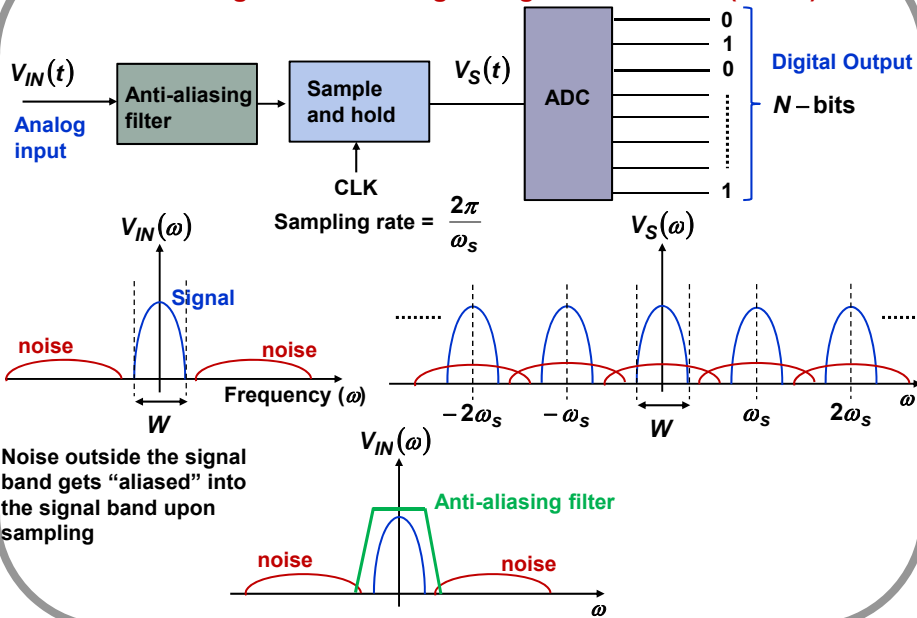
### Anti-Aliasing Filter in Analog-to-Digital Converters (ADCs)


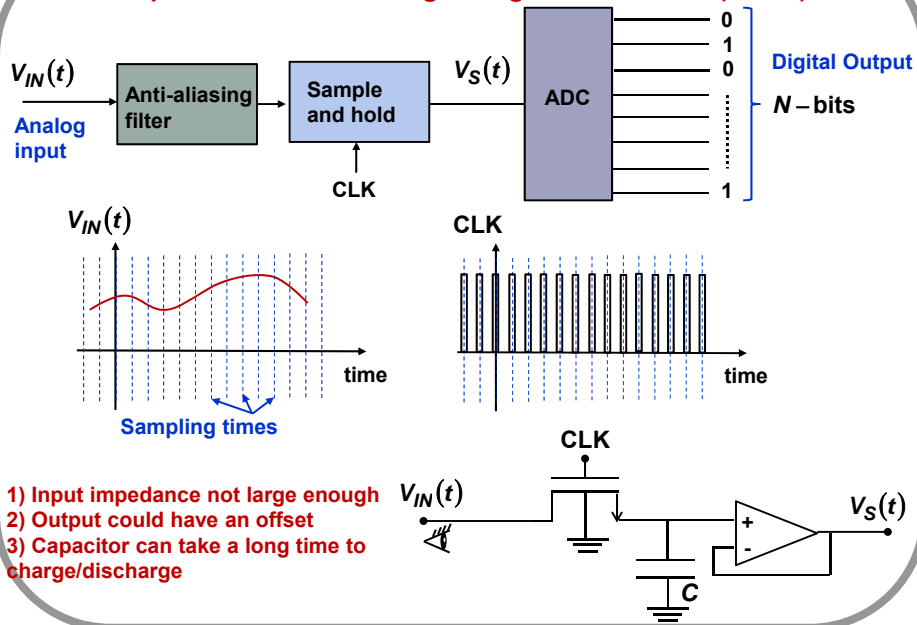
### Sample and Hold in Analog-to-Digital Converters (ADCs)



### A Better Sample and Hold Circuit

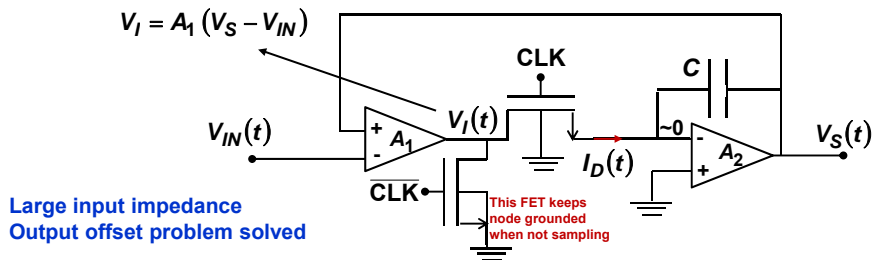

Suppose when the CLK is HIGH the current through the FET is (assuming linear region):

$$I_D = k_n \left( V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} \approx k_n (V_{CLK} - V_{TN}) V_I = \frac{V_I}{R_n}$$

Then:

$$C \frac{d(0 - V_S)}{dt} = I_D = \frac{V_I}{R_n} = \frac{A_1(V_S - V_{IN})}{R_n}$$


$$\Rightarrow \frac{dV_S}{dt} + \frac{A_1}{R_n C} V_S = \frac{A_1}{R_n C} V_{IN}$$

$$\Rightarrow V_S(t) = V_S(0)e^{-\frac{A_1}{R_n C} t} + V_{IN} \left( 1 - e^{-\frac{A_1}{R_n C} t} \right)$$

$V_S$  is pulled to  $V_{IN}$  and  $V_I$  is pulled to  $\sim 0$  V within a very short time after CLK goes HIGH


### Flash Analog-to-Digital Converters (ADCs)

3-bit Flash ADC

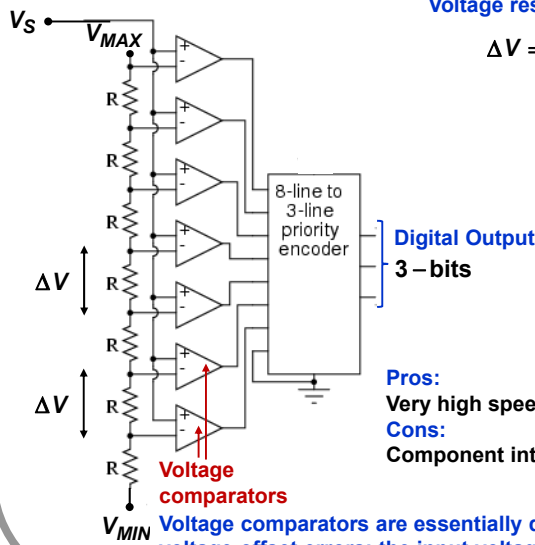

Voltage resolution:

 
$$\Delta V = \frac{V_{MAX} - V_{MIN}}{2^N - 1}$$



- Pros:**  
Very high speed architecture
- Cons:**  
Component intensive (requires  $2^N - 1$  comparators)

Voltage comparators are essentially diff amps that have very low voltage offset errors; the input voltage offset error needs to be much less than the resolution of the ADC
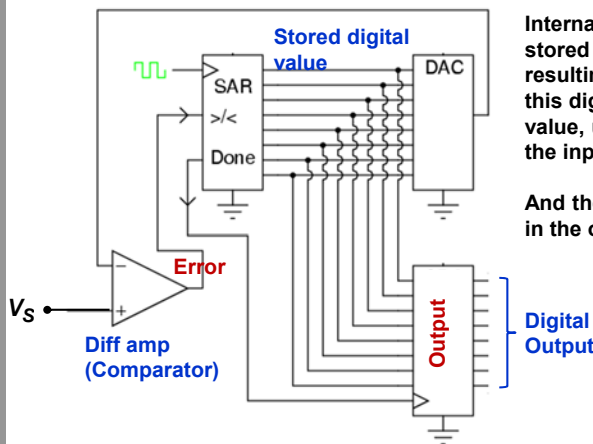
### Successive Approximation Register (SAR) Analog-to-Digital Converters (ADCs)




Internal register keeps updating the stored digital value, compares the resulting analog value obtained from this digital value to the input analog value, until the stored value matches the input value

And then the stored value is placed in the output register


 
## Successive Approximation Register (SAR) Analog-to-Digital Converters (ADCs)



Consider a 4-bit SAR-ADC with a 0-3 V input range

0000  $\Rightarrow$  0 Volts      1111  $\Rightarrow$  3 Volts

Resolution = 0.2 Volt

Suppose the input is 1.70 Volts

**Start**

SAR = 1000  $\rightarrow$  DAC = 1.60 V  $\rightarrow$  Error = +1  $\rightarrow$  Stored value is smaller

SAR = 1111  $\rightarrow$  DAC = 3.00 V  $\rightarrow$  Error = -1  $\rightarrow$  Stored value is larger

SAR = 1100  $\rightarrow$  DAC = 2.40 V  $\rightarrow$  Error = +1  $\rightarrow$  Stored value is larger

SAR = 1010  $\rightarrow$  DAC = 2.00 V  $\rightarrow$  Error = +1  $\rightarrow$  Stored value is larger

SAR = 1001  $\rightarrow$  DAC = 1.80 V  $\rightarrow$  Error = +1  $\rightarrow$  Stored value is larger




**Produce output**

**Pros:** Scalable to high resolutions    **Cons:** Slower than flash

## Pipelined Analog-to-Digital Converters (ADCs)


**Main Idea:** Use features of the flash architecture but scale to higher resolutions

  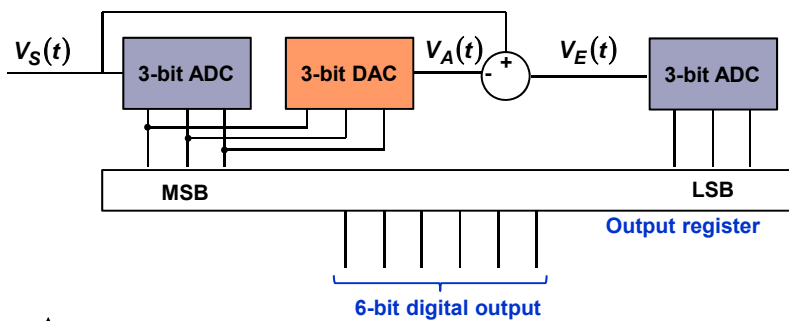**Example:** Build a 6-bit pipelined ADC from two 3-bit Flash ADCs



## Pipelined Analog-to-Digital Converters (ADCs)

Can easily generalize:

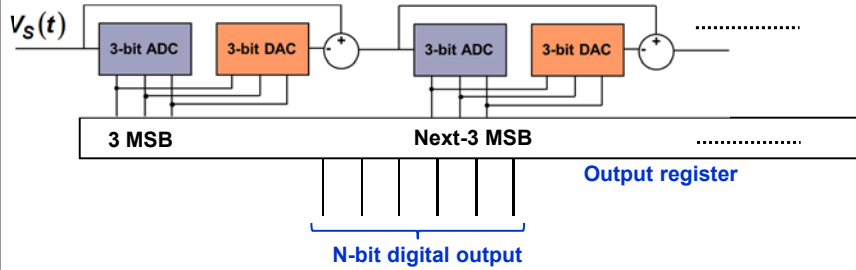


**Pros:**  
 Scalable to high resolutions  
 Fast


**Cons:**  
 Large power dissipation

## Analog-to-Digital Converters (ADCs): State of the Art


Walt Kester, Analog devices (2005)

 

William Klein, Texas Instruments (2007)

 
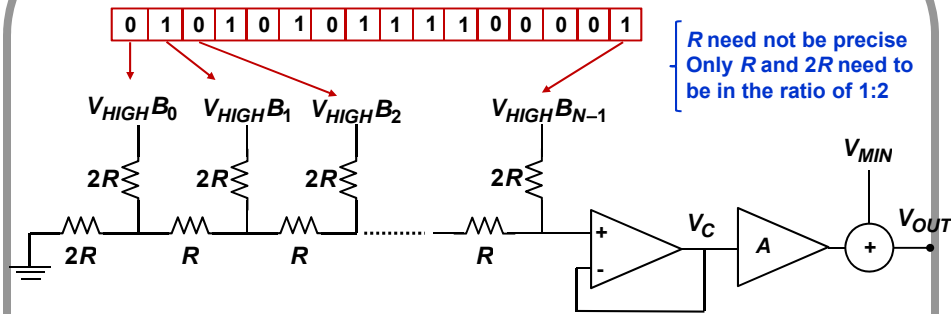
### R/2R Ladder Digital-to-Analog Converters (DACs)



$R$  need not be precise  
Only  $R$  and  $2R$  need to  
be in the ratio of 1:2

$$V_C = V_{HIGH} \left\{ \frac{B_{N-1}}{2} + \frac{B_{N-2}}{4} + \frac{B_{N-3}}{8} + \dots + \frac{B_2}{2^{N-2}} + \frac{B_1}{2^{N-1}} + \frac{B_0}{2^N} \right\}$$


If:

$$A = \frac{(V_{MAX} - V_{MIN})}{2^N - 1} \frac{2^N}{V_{HIGH}}$$


Then the output will be the desired analog output:

$$V_{OUT} = V_{MIN} + \frac{(V_{MAX} - V_{MIN})}{(2^N - 1)} [2^{N-1} B_{N-1} + 2^{N-2} B_{N-2} + \dots + 2^2 B_2 + 2^1 B_1 + B_0]$$
 
### Thermometer Code Digital-to-Analog Converters (DACs)



Dec	B2	B1	B0	D6	D5	D4	D3	D2	D1	D0
0	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1
2	0	1	0	0	0	0	0	0	1	1
3	0	1	1	0	0	0	0	1	1	1
4	1	0	0	0	0	0	1	1	1	1
5	1	0	1	0	0	1	1	1	1	1
6	1	1	0	0	1	1	1	1	1	1
7	1	1	1	1	1	1	1	1	1	1

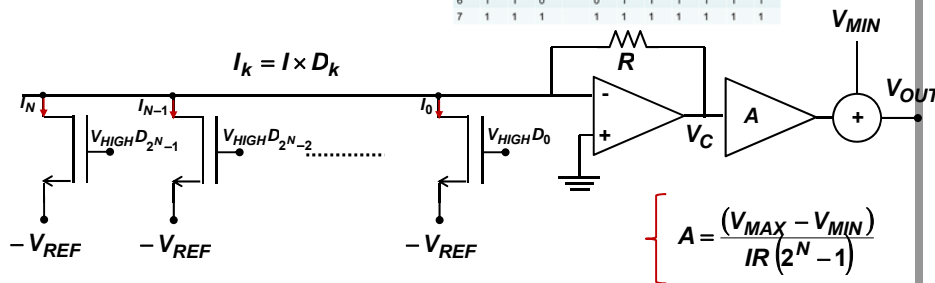

$$A = \frac{(V_{MAX} - V_{MIN})}{IR(2^N - 1)}$$

$$V_C = IR(D_{2^N-1} + D_{2^N-2} + \dots + D_1 + D_0)$$

$$V_C = IR[2^{N-1} B_{N-1} + 2^{N-2} B_{N-2} + \dots + 2^2 B_2 + 2^1 B_1 + B_0]$$

$$V_{OUT} = V_{MIN} + \frac{(V_{MAX} - V_{MIN})}{(2^N - 1)} [2^{N-1} B_{N-1} + 2^{N-2} B_{N-2} + \dots + 2^2 B_2 + 2^1 B_1 + B_0]$$

### Wireless Communications

