




Lecture 23

CMOS Logic Gates and Digital VLSI – I

In this lecture you will learn:


- The CMOS Inverter
- Charge and Discharge Dynamics
- Power Dissipation
- Digital Levels and Noise

A NFET Inverter

  
 


A	X
0	1
1	0

The Load Capacitance


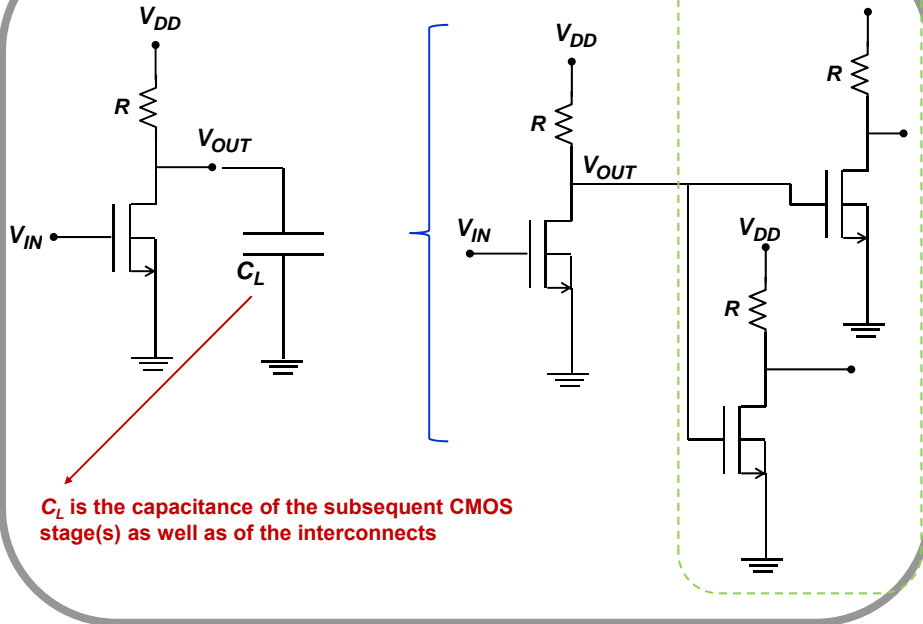


 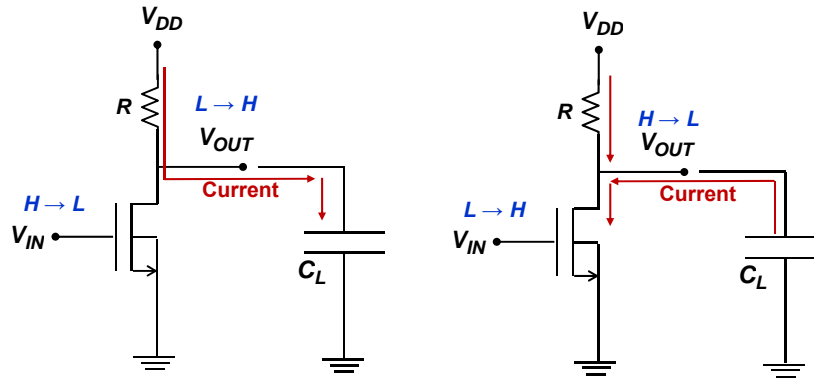A NFET Inverter: Charging and Discharging Dynamics



A	X
0	1
1	0

Digital Signal Levels and Noise

  

One must have:


$$V_{OL} + \text{noise} < V_{IL}$$

$$V_{OH} - \text{noise} > V_{IH}$$

Noise margins:


$$V_{IL} - V_{OL}$$

$$V_{OH} - V_{IH}$$

 


Noise and device variations sets the minimum V_{DD} one can use

A NFET Inverter: Noise Margins

 

 
Problem:

The input/output characteristics are not symmetric




Noise margins are good but not excellent

A NFET Inverter: Charging Dynamics

 

 Problem:


When the output is LOW, charging of the output to HIGH is slow because charging current is not uniform



$$I_{OUT} = \frac{V_{DD} - V_{OUT}}{R} = C_L \frac{dV_{OUT}}{dt}$$

$$\Rightarrow V_{OUT}(t) = V_{DD} \left[1 - e^{-\frac{t}{RC_L}} \right]$$

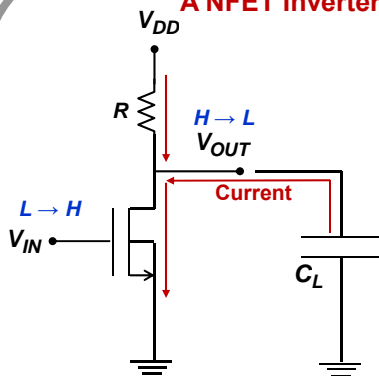
A NFET Inverter: Static Power Dissipation




 
Problem:

When the input is HIGH, and the output is LOW, current keeps flowing through the FET and the resistor forever!!

This is an example of static power dissipation – extremely bad!





A CMOS Inverter: Noise Margins

  


If V_{TN} and $V_{DD} + V_{TP}$ are close to each other, the transition region can be made narrow and sharp
 →The noise margins can be very wide!!

 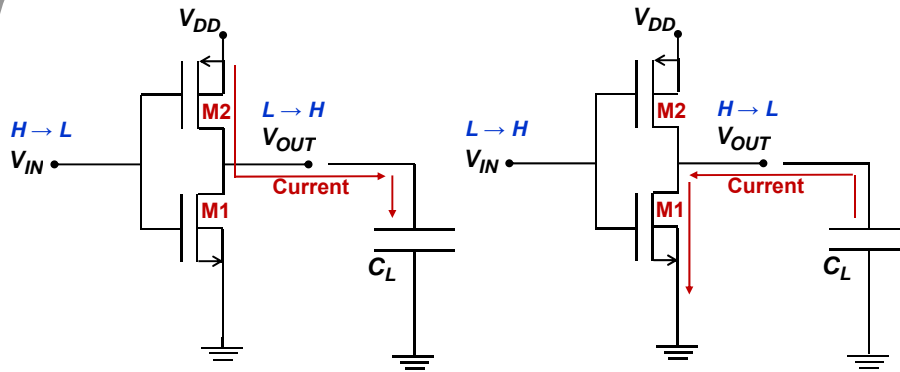A CMOS Inverter: Charging and Discharging Dynamics



A	X
0	1
1	0

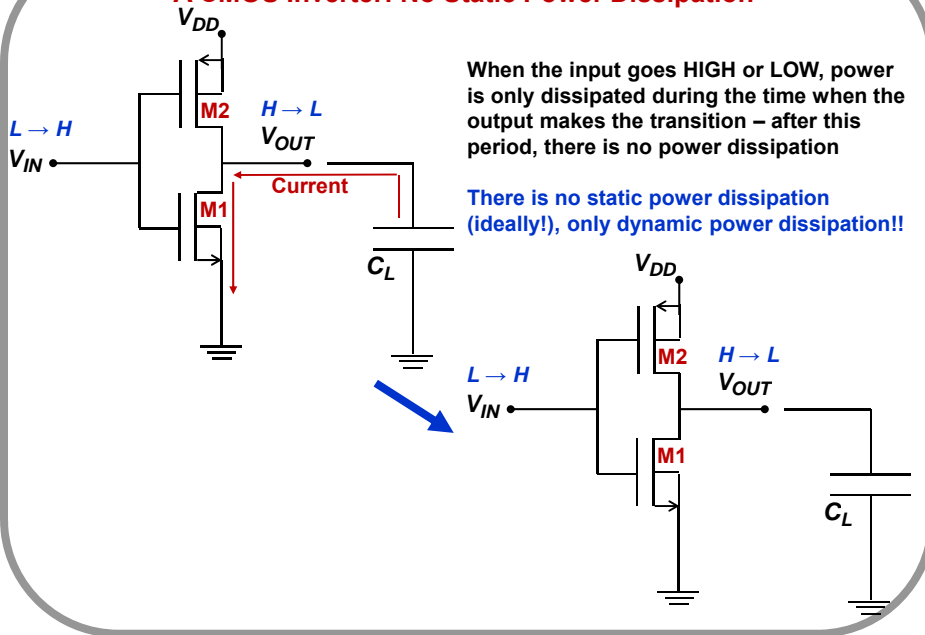
A CMOS Inverter: No Static Power Dissipation



When the input goes HIGH or LOW, power is only dissipated during the time when the output makes the transition – after this period, there is no power dissipation

There is no static power dissipation (ideally!), only dynamic power dissipation!!

A CMOS Inverter: Charging Dynamics

 

When the output is LOW, initial charging of the output to HIGH is done with a uniform current supplied by the PFET in saturation:


$$\begin{aligned}
 I_{OUT} &= C_L \frac{dV_{OUT}}{dt} \\
 \Rightarrow \frac{k_p}{2} (V_{IN}^L - V_{DD} - V_{TP})^2 &= C_L \frac{dV_{OUT}}{dt} \\
 \Rightarrow \frac{k_p}{2} (V_{DD} + V_{TP})^2 &= C_L \frac{dV_{OUT}}{dt} \\
 \Rightarrow V_{OUT}(t) &= \frac{k_p}{2C_L} (V_{DD} + V_{TP})^2 t
 \end{aligned}$$

Condition for the PFET to be in saturation:

$$\begin{cases}
 V_{DS} < V_{GS} - V_{TP} \\
 \Rightarrow V_{OUT} - V_{DD} < V_{IN} - V_{DD} - V_{TP} \\
 \Rightarrow V_{OUT} < V_{IN} - V_{TP} \approx -V_{TP}
 \end{cases}$$

When V_{OUT} becomes larger than $-V_{TP}$ then the PFET goes into the linear region....

A CMOS Inverter: Charging Dynamics

 

For times $0 < t < t_1$ when the PFET (M2) is in saturation:

$$V_{OUT}(t) = \frac{k_p}{2C_L} (V_{DD} + V_{TP})^2 t$$

$$\Rightarrow t_1 = -V_{TP} \frac{2C_L}{k_p (V_{DD} + V_{TP})^2} = \frac{-2V_{TP}}{(V_{DD} + V_{TP})} \tau \quad \left\{ \tau = \frac{C_L}{k_p (V_{DD} + V_{TP})} \right.$$


A CMOS Inverter: Charging Dynamics

When V_{OUT} becomes larger than $-V_{TP}$ then the PFET goes into the **linear** region, and from then onwards:

$$I_{OUT} = C_L \frac{dV_{OUT}}{dt}$$

$$\Rightarrow k_p \left(V_{IN} - V_{DD} - V_{TP} - \frac{(V_{OUT} - V_{DD})}{2} \right) (V_{OUT} - V_{DD}) = C_L \frac{dV_{OUT}}{dt}$$
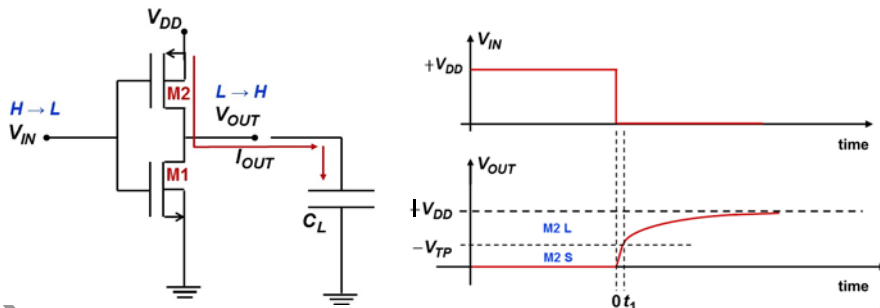
$$\Rightarrow -k_p \left(V_{DD} + V_{TP} + \frac{(V_{OUT} - V_{DD})}{2} \right) (V_{OUT} - V_{DD}) = C_L \frac{dV_{OUT}}{dt}$$




One can obtain faster charging compared to a resistor in place of a PFET!

A CMOS Inverter: Charging Dynamics

$$-k_p \left(V_{DD} + V_{TP} + \frac{(V_{OUT} - V_{DD})}{2} \right) (V_{OUT} - V_{DD}) = C_L \frac{dV_{OUT}}{dt}$$


$$\Rightarrow \int_{V_{OUT}}^{V_{OUT}} \frac{dV_{OUT}}{-V_{TP} \left(V_{DD} + V_{TP} + \frac{(V_{OUT} - V_{DD})}{2} \right) (V_{OUT} - V_{DD})} = -\frac{k_p}{C_L} \int_{t_1}^t dt = -\frac{k_p}{C_L} t$$
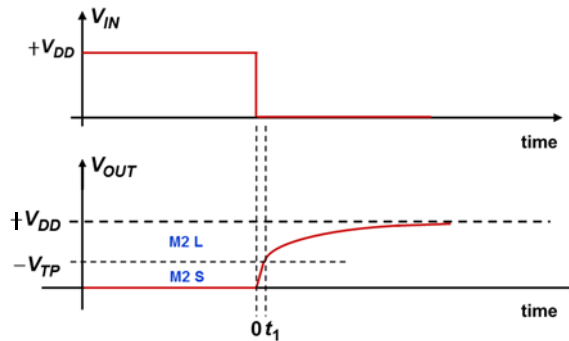
$$\Rightarrow V_{OUT}(t > t_1) = \frac{V_{DD} \left(1 - e^{-(t-t_1)/\tau} \right) - 2V_{TP} e^{-(t-t_1)/\tau}}{1 + e^{-(t-t_1)/\tau}} \quad \left\{ \tau = \frac{C_L}{k_p (V_{DD} + V_{TP})} \right.$$




Rise Times and Fall Times

 
Rise Time: The time it takes the output to increase from 10% to 90% of the HIGH value



 
Fall Time: The time it takes the output to decrease from 90% to 10% of the HIGH value



A CMOS Inverter: Charging Dynamics

 

 One can obtain faster charging compared to a resistor




$$t_r \approx \frac{2C_L}{k_p(V_{DD} + V_{TP})} \left\{ \frac{-V_{TP}}{V_{DD} + V_{TP}} - \frac{1}{2} \ln \left[\frac{0.1V_{DD}}{2(V_{DD} + V_{TP}) - 0.1V_{DD}} \right] \right\}$$

$$\propto \frac{L^2}{\mu_h V_{DD}} \sim \tau_t \quad \left\{ \text{if } C_L \propto C_{gs} \right.$$


FET transit time

In reality, the load capacitance is not just due to the next FET gate - it also includes the interconnect capacitances

A CMOS Inverter: Discharging Dynamics

 

 One can obtain faster charging compared to a resistor




$$t_f \approx \frac{2C_L}{k_n(V_{DD} - V_{TN})} \left\{ \frac{V_{TN}}{V_{DD} - V_{TN}} - \frac{1}{2} \ln \left[\frac{0.1V_{DD}}{2(V_{DD} - V_{TN}) - 0.1V_{DD}} \right] \right\}$$

$$\propto \frac{L^2}{\mu_n V_{DD}} \sim \tau_t \quad \left\{ \text{if } C_L \propto C_{gs} \right.$$


FET transit time

In reality, the load capacitance is not just due to the next FET gate - it also includes the interconnect capacitances

 
A CMOS Inverter: Charging and Discharging Dynamics



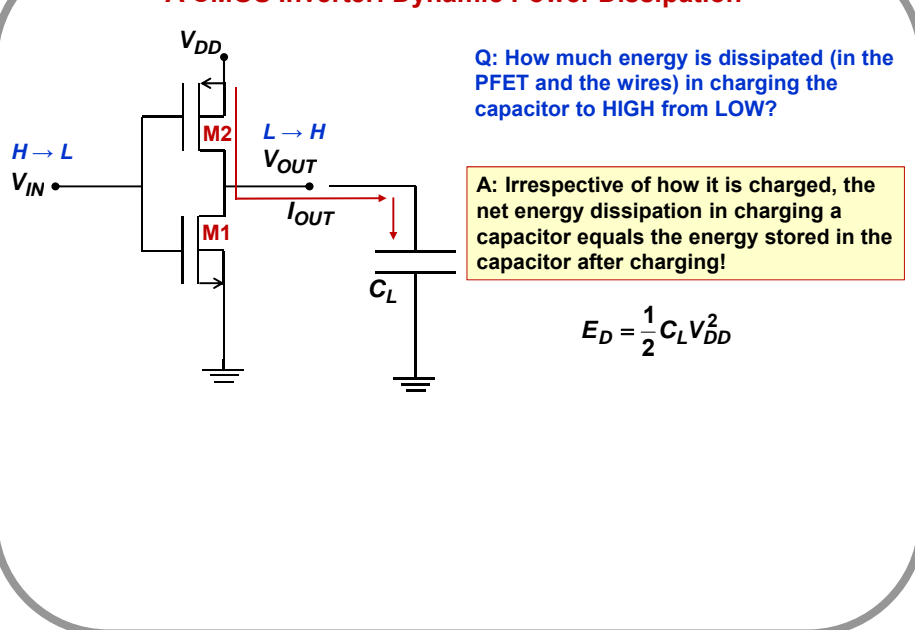A CMOS Inverter: Dynamic Power Dissipation



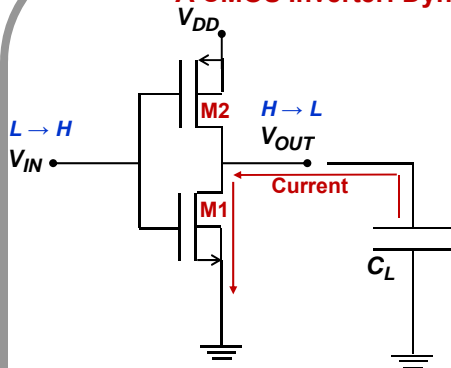A CMOS Inverter: Dynamic Power Dissipation



Q: How much energy is dissipated (in the NFET and the wires) in discharging the capacitor from HIGH to LOW?


A: Irrespective of how it is discharged, the net energy dissipation in discharging a capacitor equals the energy stored in the capacitor before discharging!

$$E_D = \frac{1}{2} C_L V_{DD}^2$$

Total energy dissipation in one charge and discharge cycle:

$$E_D = C_L V_{DD}^2$$

Dynamic Power Dissipation in CMOS Chips

 

Total energy dissipation in one charge and discharge cycle per FET:

$$E_D = C_{gs} V_{DD}^2 \quad \text{--- Ignoring interconnect capacitance}$$

Total energy dissipation in one charge and discharge cycle if N_{FET} FETs in the chip are active:

$$E_D = N_{FET} C_{gs} V_{DD}^2$$

Total power dissipation (energy dissipation per second) if N_{FET} FETs are active:

$$P_D = N_{FET} f_{CLK} C_{gs} V_{DD}^2$$

Number of cycles per second $\sim f_{CLK}$

Dynamic Power Dissipation in CMOS Chips

E8500 45 nm Chipset



Clock speed = 3.16 GHz
 Gate length: 45 nm = .045 μm
 Number of FETs in the chip = 410 X 10⁶
 Power supply voltage ~ 2 V

$$P_D = N_{FET} f_{CLK} C_{gs} V_{DD}^2$$

Fraction of active FETs at any instant on the average (~0.4%)

$$N_{FET} = .004 \times 410e6 = 1.64e6$$

$$f_{CLK} = 3.1e9$$

$$t_{ox} = 10 \text{ \AA} \quad (\text{equivalent low-}\kappa \text{ thickness})$$

$$W = 2 \text{ } \mu\text{m}$$

$$L = .045 \text{ } \mu\text{m}$$

$$C_{gs} = \frac{2 \epsilon_{ox}}{3 t_{ox}} WL = 2 \text{ femto-F}$$

$$V_{DD} = 2 \text{ V}$$

Our power dissipation estimate:

$$P_D = N_{FET} f_{CLK} C_{gs} V_{DD}^2$$


$$= 42 \text{ Watts!!}$$

Actual published number:

$$P_T = 65 \text{ Watts!!}$$

$$= P_D + P_S$$

Power Dissipation in CMOS Chips

 

Power Dissipation in CMOS Chips

