

Problem 8.1

$$\begin{aligned} \text{a) } I_{REF} = I_{D1} = I_{D2} &\Rightarrow I_{REF} = \frac{k_n}{2} (V_1 - V_2 - V_{TN})^2 [1 + \lambda_n (V_1 - V_2)] \\ &= \frac{k_n}{2} (V_2 - V_{TN})^2 (1 + \lambda_n V_2) \end{aligned}$$


$$\Rightarrow V_1 = 2V_2, \quad V_2 = 1.4351V, \quad V_1 = 2.8703V$$

$$\begin{aligned} \text{b) } I_{D3} = I_{D4} &\Rightarrow \frac{k_n}{2} (V_1 - V_3 - V_{TN})^2 (1 + \lambda_n (V_{out} - V_3)) \\ &= \frac{k_n}{2} (V_2 - V_{TN})^2 (1 + \lambda_n V_3) \end{aligned}$$

$$\Rightarrow V_{out} = \frac{1}{\lambda_n} \left[\frac{(V_2 - V_{TN})^2 (1 + \lambda_n V_3)}{(V_1 - V_3 - V_{TN})^2} - 1 \right] + V_3$$

$$\text{c) } M_3: V_1 - V_{TN} < V_{out} \quad M_4: V_2 - V_{TN} < V_3$$

$$\Rightarrow V_{out} > 2.3703V$$

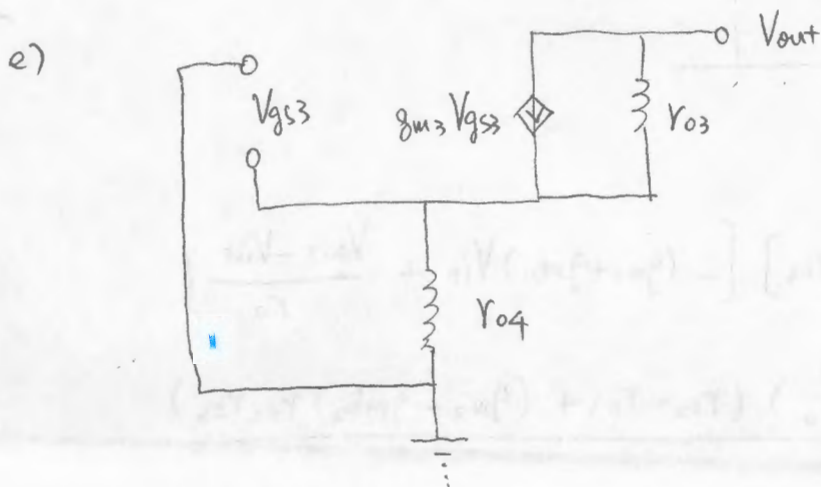


$$\text{f) } r_{oc} = r_{o3} + r_{o4} + g_{m3} r_{o3} r_{o4}$$


$$\text{g) } g_o = \lambda_n I_D \Rightarrow r_{o3} = r_{o4} = 10000 \Omega$$

$$g_{m3} = \sqrt{2k_n I_D (1 + \lambda_n V_{DS})} = 0.002 \text{ S}$$


$$r_{oc} = 2.3387 \times 10^5 \Omega$$

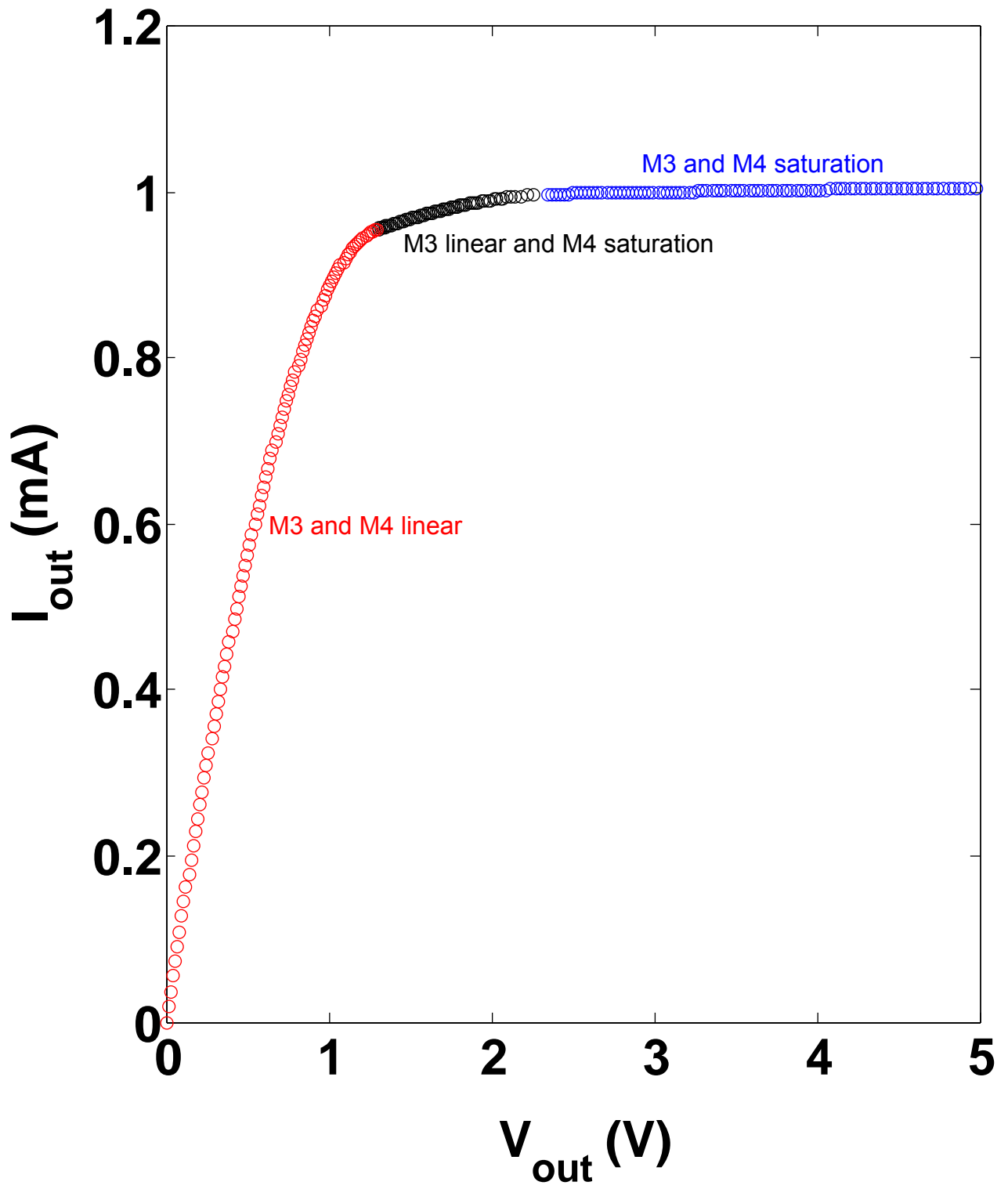

Problem 8.2

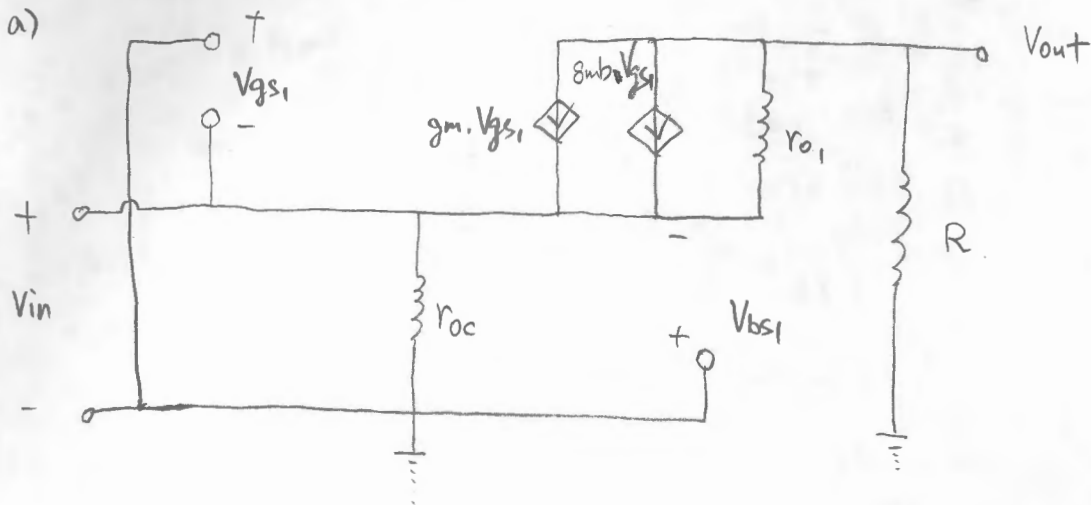

The circuit for R:

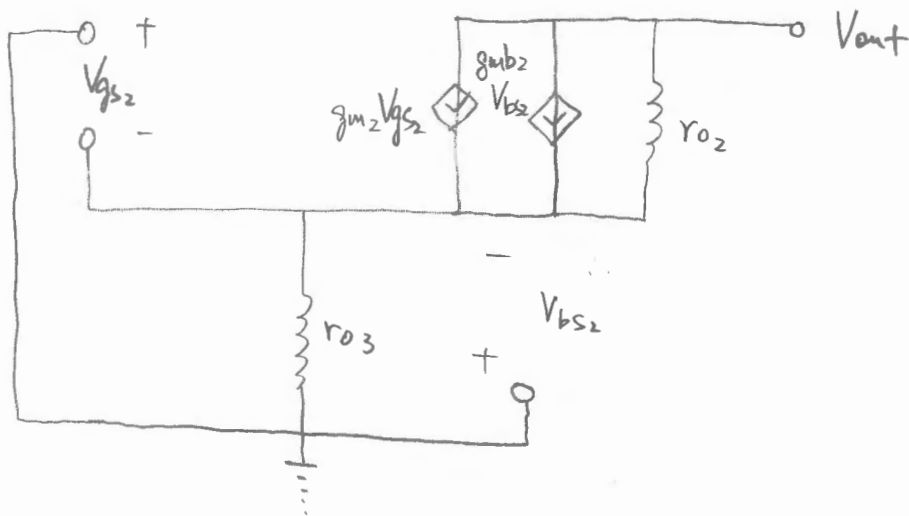


$$R = r_{o2} + r_{o3} + (g_{m2} + g_{mb2}) r_{o2} r_{o3}$$

$$V_{out} = -i_d R = -R \left[-(g_{m1} + g_{mb1}) V_{in} + \frac{V_{out} - V_{in}}{r_{o1}} \right]$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = \frac{(g_{m1} + g_{mb1} + \frac{1}{r_{o1}}) R}{1 + \frac{R}{r_{o1}}}$$

b)

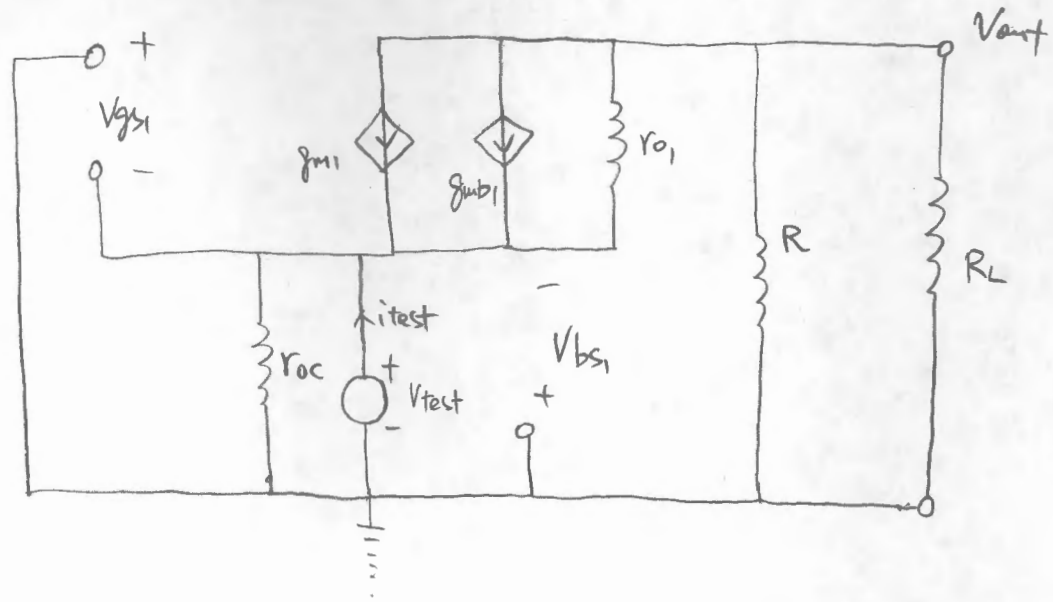


$$i_{test} = (g_{m1} + g_{mb1}) V_{test} - \frac{V_{out} - V_{test}}{r_{o1}} + \frac{V_{test}}{r_{oc}}$$

$$= (g_{m1} + g_{mb1} + \frac{1}{r_{oc}}) V_{test} - \frac{1}{r_{o1}} \left[\frac{(g_{m1} + g_{mb1} + \frac{1}{r_{o1}}) (R // R_L)}{1 + \frac{R // R_L}{r_{o1}}} - 1 \right] V_{test}$$

$$\Rightarrow R_{in} = \frac{i_{test}}{v_{test}} = \frac{(g_{m1} + g_{mb1}) r_{o1} + \frac{r_{o1} + R // R_L}{r_{oc}} + 1}{r_{o1} + R // R_L}$$

c)

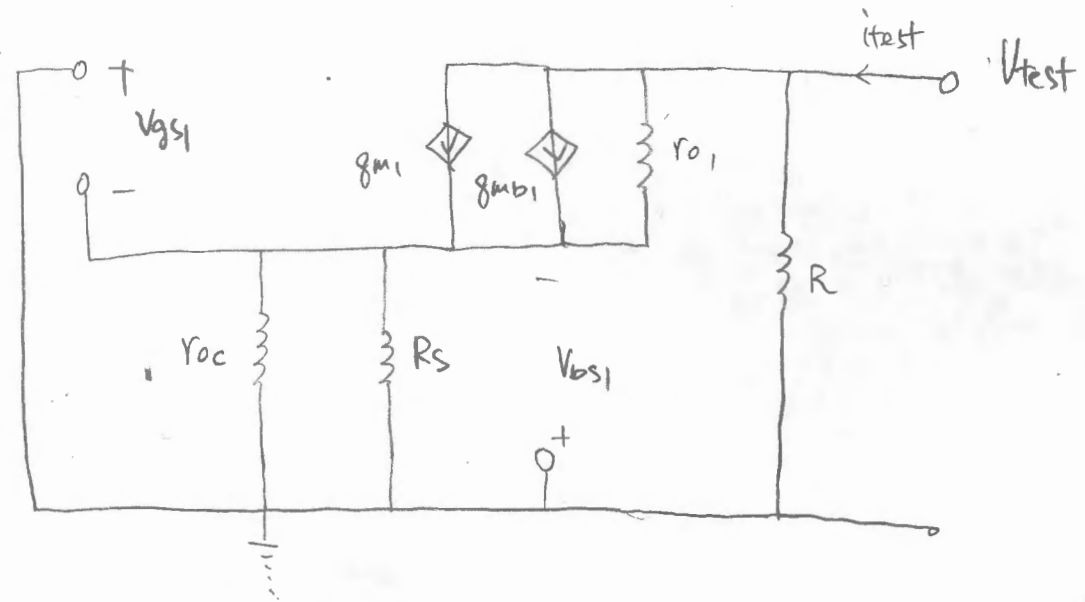

$$i_{test} = i_d + \frac{V_{test}}{R} = \frac{V_{test}}{R} + \frac{V_{test}}{r_{o1}} \left/ \left[1 + \frac{r_{oc} // R_s}{r_{o1}} + (g_{m1} + g_{mb1}) (r_{oc} // R_s) \right] \right.$$

$$\Rightarrow R_{out}^{-1} = \frac{i_{test}}{v_{test}} = \frac{1}{R} + \frac{1}{\left[r_{o1} + r_{oc} // R_s + (g_{m1} + g_{mb1}) r_{o1} (r_{oc} // R_s) \right]}$$

8.3)

a) The transconductance of the cascode amplifier is approximately the transconductance of M_1 . To make

$$g_{m1} = \sqrt{2k_n I_D} \approx 1 \text{ mS} \Rightarrow W_1 = 200 \mu\text{m}$$

b) $M_1: R_{out} \approx r_{o1} = (\lambda_n I_D)^{-1} = 200 \text{ k}\Omega$

$M_2: R_{out} \approx r_{o1}$

$M_3: R_{out} \approx r_{o8}$

$M_8: R_{out} \approx r_{o8} = (\lambda_p I_D)^{-1} = 500 \text{ k}\Omega$

c) $R_{out} \approx g_{m2} r_{o1} r_{o2} = 20 \text{ M}\Omega \Rightarrow g_{m2} = 0.5 \text{ mS}$

d) $g_{m2} = \sqrt{2k_n I_D} = 0.5 \text{ mS} \Rightarrow W_2 = 50 \mu\text{m}$

e) $R_{out} = g_{m3} r_{o3} r_{o8} = 100 \text{ M}\Omega \Rightarrow g_{m3} = 0.4 \text{ mS}$

f) $g_{m3} = \sqrt{2k_p I_D} = 0.4 \text{ mS} \Rightarrow W_3 = 64 \mu\text{m}$

g) $W_4 = W_3 = 64 \mu\text{m}$, $W_5 = W_2 = 50 \mu\text{m}$, $W_6 = W_8 = W_3 = 64 \mu\text{m}$

i) $V_1: -I_{D1} = -\frac{W_1}{2L} \mu_p C_{ox} (V_1 - V_{DD} - V_{TP})^2 \Rightarrow V_1 = 3.5 \text{ V}$

$V_2: -I_{D1} = -\frac{W_4}{2L} \mu_p C_{ox} (V_2 - V_1 - V_{TP})^2 \Rightarrow V_2 = 2 \text{ V}$

$V_3 = V_2 = 2 \text{ V}$

j) $V_4 = V_1 = 3.5 \text{ V}$.

For V_6 :

$$I_{D1} = \frac{W_5}{2L} \mu_n C_{ox} (V_3 - V_6 - V_{TN})^2 \Rightarrow V_6 = 0.6V$$

For V_7 :

$$I_{D1} = \frac{W_6}{2L} \mu_n C_{ox} (V_7 - V_{TN})^2 \Rightarrow V_7 = 1.2V$$

h)
$$I_{D1} = \frac{W_7}{2L} \mu_n C_{ox} (V_7 - V_{TN})^2 \Rightarrow W_7 = W_6 = W_1 = 200 \mu m$$

k)
$$V_{BIAS} = V_7 = 1.2V$$

l)
$$R = \frac{V_{DD} - V_7}{I_{REF}} = 38000 \Omega$$