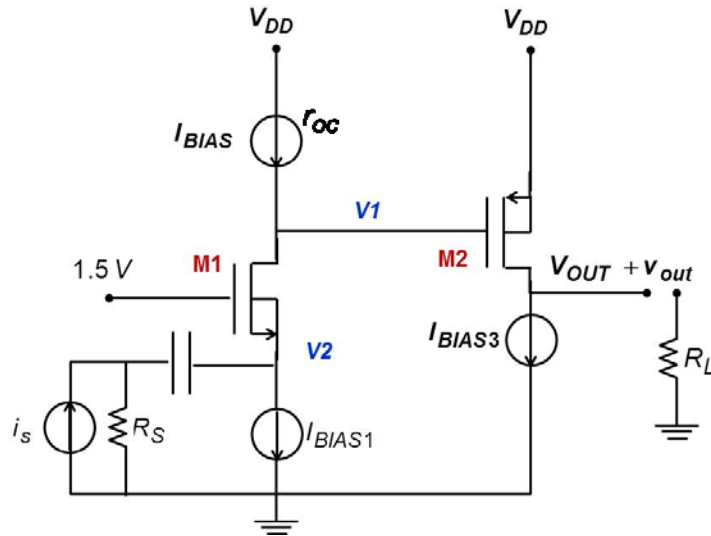


**Problem 9.1: (Designing a cascade transresistance amplifier)**



a) This is a common gate stage followed by a common source stage.

b) One can ignore  $\lambda_n$  in the calculation of the FET width:

$$\frac{k_n}{2} (V_{GS1} - V_{TN})^2 = \frac{W_1}{2L} \mu_n C_{ox} (1.5 - 0.5 - 0.7)^2 = 200 \mu A$$

$$\Rightarrow W_1 \approx 356 \mu m$$

c) One can again ignore  $\lambda_p$  in the calculation of the FET width:

$$\frac{k_p}{2} (V_{GS2} - V_{TP})^2 = \frac{W_2}{2L} \mu_p C_{ox} (3.0 - 5.0 + 1.0)^2 = 500 \mu A$$

$$\Rightarrow W_2 \approx 160 \mu m$$

d)  $R_{in}$  would just be the input resistance of the NFET common gate stage (from the lecture handouts) that is connected to an infinite  $R_L$  but where the resistance  $R$  on the drain side is  $r_{oc}$ :

$$\Rightarrow R_{in} = \frac{r_{on} + r_{oc}}{g_{mn} r_{on} + 1} \approx \frac{1}{g_{mn}} \left( 1 + \frac{r_{oc}}{r_{on}} \right)$$

e)  $R_{out}$  would just be the output resistance of the PFET common source stage (from the lecture handouts) that has an infinite resistance  $R$  on the drain side (because of the ideal current source  $I_{BIAS3}$ ):

$$\Rightarrow R_{out} = r_{op}$$

f) The problem can be solved in two steps; first we find  $v_1/i_s$  and then we find  $v_{out}/v_1$ . Since there the input resistance of stage 2 (i.e. the PFET common source stage) is infinite, there will be no inter-stage voltage division and one can write,

$$R_m = \left( \frac{v_1}{i_s} \right) \left( \frac{v_{out}}{v_1} \right)$$

In the small signal model, the current  $i_s$  must entirely flow through the resistance  $r_{oc}$  (there is no other place for it to go) so:

$$v_1 = i_s r_{oc}$$


For the second common source stage,

$$\frac{v_{out}}{v_1} = -g_{mp} r_{op}$$

Therefore,

$$R_m = \left( \frac{v_1}{i_s} \right) \left( \frac{v_{out}}{v_1} \right) = -g_{mp} r_{op} r_{oc}$$

g)

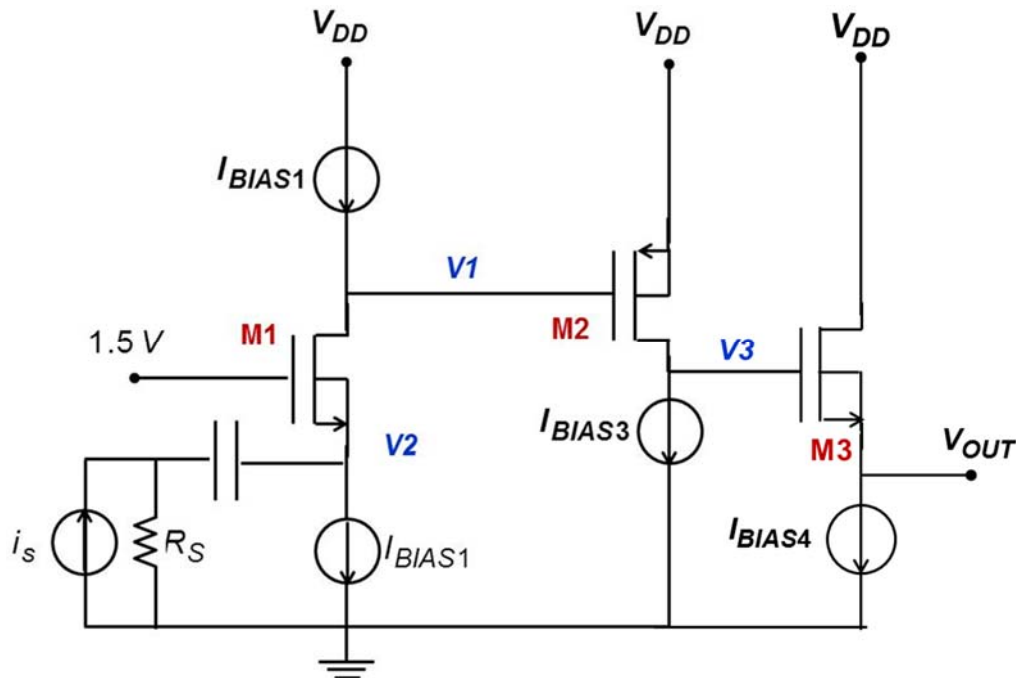

Assuming the current source  $I_{BIAS4}$  is ideal, the output resistance of the amplifier will be the output resistance of the common drain stage (with  $R = 0$ ) and equals:

$$\Rightarrow \frac{1}{R_{out}} = \frac{1}{r_{oc4}} + \frac{g_{mn} r_{on} + 1}{r_{on}} \approx g_{mn}$$

I choose  $R_{out} = 1k\Omega$  then  $g_{mn} = 1mS$ . I choose  $I_{BIAS4}$  to equal  $200 \mu A$ . Other values will work too. Since,

$$g_{mn} \approx \sqrt{2k_n I_D}$$


$$\Rightarrow \frac{W_3}{L} = 50$$

$$\Rightarrow W_3 \approx 200 \mu m$$

I choose,  $V_{OUT} = 1.8 V$ ,



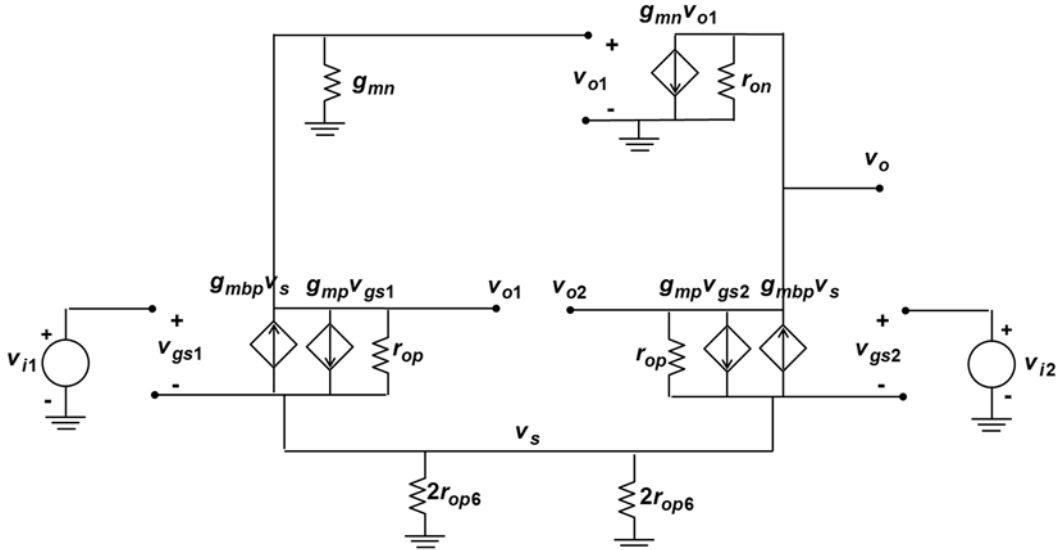
$$A_{vc} = \frac{v_o}{v_{ic}} \approx - \frac{\frac{g_{mp}}{g_{mn}} r_{op}}{r_{op} + \frac{1}{g_{mn}} + 2r_{op6} + (g_{mp} + g_{mbp})r_{op}(2r_{op6})} \approx - \frac{1}{g_{mn}(2r_{op6})}$$



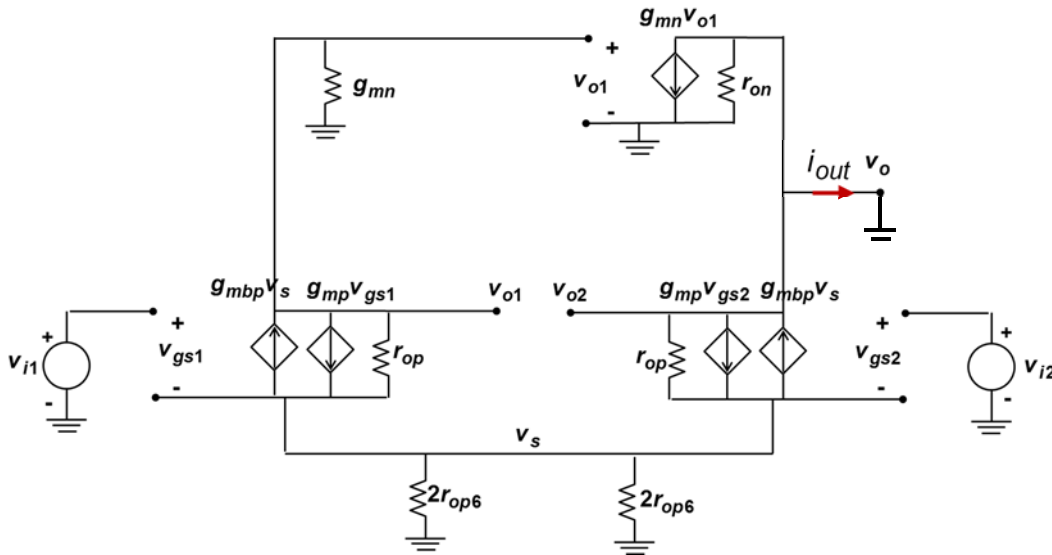e) Easiest way to find the output resistance is to short the output and measure the short circuit output current in the differential mode. We already know the open circuit voltage in the differential mode,

$$v_o \approx g_{mp}(r_{on} \parallel r_{op})v_{id}$$

So if we find the short circuit output current as well, and take the ratio of the open circuit voltage and the short circuit output current we will get the output resistance. Consider the following circuit,



Assuming,

$$v_{i1} = -v_{i2} = v_{id}/2$$

And  $v_s \approx 0$ , we get,  $v_{o1} \approx -\frac{g_{mp}}{g_{mn}} \frac{v_{id}}{2}$ . Doing KCL at the output node we get,

$$\begin{aligned}
g_{mn}v_{o1} + i_{out} + g_{mp}v_{gs2} &= 0 \\
\Rightarrow -g_{mp}\frac{v_{id}}{2} + i_{out} - g_{mp}\frac{v_{id}}{2} &= 0 \\
\Rightarrow i_{out} &= g_{mp}v_{id}
\end{aligned}$$

Finally,

$$R_{out} = \frac{g_{mp}(r_{op} \parallel r_{on})v_{id}}{g_{mp}v_{id}} = (r_{op} \parallel r_{on})$$

If you don't assume that  $v_s \approx 0$ , which is a better and more sensible approach given that the symmetry is not there at all, the same answer for the short circuit current can still be obtained. Doing KCL at the drain end of M1 gives,

$$\begin{aligned}
-v_{o1}g_{mn} &\approx g_{mp}\left(\frac{v_{id}}{2} - v_s\right) - g_{mbp}v_s + g_{op}(v_{o1} - v_s) \\
\Rightarrow v_{o1} &\approx -\frac{g_{mp}}{g_{mn}}\left(\frac{v_{id}}{2} - v_s\right) + \frac{(g_{mbp} + g_{op})}{g_{mn}}v_s
\end{aligned}$$

Again doing KCL at the output node we get,

$$\begin{aligned}
[g_{mn}v_{o1}] + i_{out} + \left[ g_{mp}\left(-\frac{v_{id}}{2} - v_s\right) - g_{mbp}v_s - g_{op}v_s \right] &= 0 \\
\Rightarrow -g_{mp}\frac{v_{id}}{2} + i_{out} - g_{mp}\frac{v_{id}}{2} &= 0 \\
\Rightarrow i_{out} &= g_{mp}v_{id}
\end{aligned}$$

Note that all factors containing  $v_s$  cancel out.

f) It is easiest to calculate the work done by the voltage sources. This equals  $4 I_{BIAS} V_{DD}$ , which is 5 mW.