

ECE 4880 RF Systems Fall 2015
Final Exam

Name: _____

Net ID: _____


Load reflection coefficient Γ_L at the load as: $\Gamma_L = \frac{V_-}{V_+} = \frac{Z_L/Z_o - 1}{Z_L/Z_o + 1}$

$$\begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix} = \frac{1}{S_{21}} \begin{bmatrix} 1 & -S_{22} \\ S_{11} & S_{12}S_{21} - S_{11}S_{22} \end{bmatrix} \quad \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \frac{1}{T_{11}} \begin{bmatrix} T_{21} & T_{11}T_{22} - T_{12}T_{21} \\ 1 & -T_{12} \end{bmatrix}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \frac{Y_0}{(1+S_{11})(1+S_{22}) - S_{12}S_{21}} \begin{bmatrix} (1-S_{11})(1+S_{22}) + S_{12}S_{21} & -2S_{12} \\ -2S_{21} & (1+S_{11})(1-S_{22}) + S_{12}S_{21} \end{bmatrix}$$

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \frac{1}{A + BY_0 + C/Y_0 + D} \begin{bmatrix} A + BY_0 - C/Y_0 - D & 2(AD - BC) \\ 2 & -A + BY_0 - C/Y_0 + D \end{bmatrix} \quad \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{1}{Y_{21}} \begin{bmatrix} -Y_{22} & -1 \\ Y_{12}Y_{21} - Y_{11}Y_{22} & -Y_{11} \end{bmatrix}$$

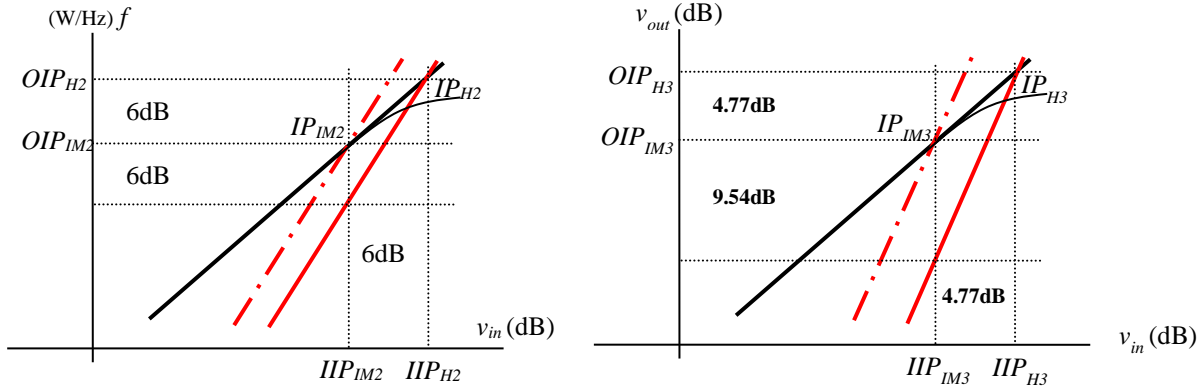Thermal noise at room temperature: $-174\text{dBm} + 10\log_{10}(\text{BW}/1\text{Hz})$



$I_{1dBcomp} = IIP_{IM3} - 9.64\text{dB}$ when only IM3 is dominant.

Nonlinear Taylor coefficients: $A_{IIP_{IM2}} = \left| \frac{a_1}{a_2} \right|$; $A_{IIP_{IM3}}^2 = \frac{4}{3} \left| \frac{a_1}{a_3} \right|^2$

$$\frac{1}{OIP_{IM3,cas}} = \frac{1}{g_2 \cdot OIP_{IM3,1}} + \frac{1}{OIP_{IM3,2}} \quad (\text{IM3 adding coherently})$$


$$\frac{1}{OIP_{IM3,cas}^2} = \frac{1}{(g_2 \cdot OIP_{IM3,1})^2} + \frac{1}{OIP_{IM3,2}^2} \quad (\text{IM3 adding randomly})$$

The noise factor of the cascade: $f_{cas} = f_1 + \sum_{k=2}^N \frac{f_k - 1}{\prod_{i=1}^{k-1} g_i}$

The Leeson empirical approximation for the LO phase noise: $L(\Delta\omega) = \frac{2FkT}{P_{sig}} \cdot \left[1 + \left(\frac{\omega_0}{2Q\Delta\omega} \right)^2 \right] \cdot \left(1 + \frac{\Delta\omega_{1/f^3}}{|\Delta\omega|} \right)$

Part I. Multiple Choices (MC) and Fill-ins. There can be more than one correct choices in each MC question. Wrong choices can deduct the points, but you will not get a negative mark. Please write your MC answers clearly to the left blank space to minimize grading errors. **4 pts** each.

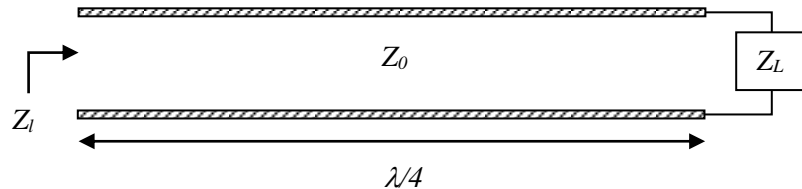
1. **(Quarter wavelength impedance transform)** For a transmission line at quarter wavelength $\lambda/4$ of a given frequency ω with characteristic impedance of Z_0 , the load (complex number) is Z_L and the impedance looking into the transmission line can be represented by Z_i . Z_0 , Z_L and Z_i are all in unit of Ω .



- (a) $Z_L = Z_i$.
- (b) $Z_L = 1/Z_i$.
- (c) $Z_L \cdot Z_i = Z_0^2$.
- (d) If Z_L is inductive (positive imaginary part), then Z_i will be capacitive.
- (e) If Z_L is open circuited, then Z_i will contain a nonzero imaginary part.
- (f) If Z_L is short circuited, then $Z_i = Z_0$.

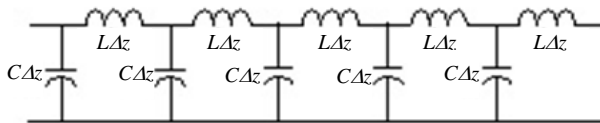2. **(Discrete transmission lines)** For the discrete-element transmission line shown below, if we match the unit elements $L\Delta z$ and $C\Delta z$ to the distributed line characteristic impedance: $Z_0 = \sqrt{\frac{L}{C}}$ and define


$v = \frac{1}{\sqrt{LC}}$. For an AC signal with $f_0 \ll f_{bragg}$,



$$f_{bragg} = \frac{1}{\pi\sqrt{L\Delta z C\Delta z}} = \frac{1}{\pi\sqrt{LC}\Delta z} = \frac{v}{\pi\Delta z}$$

- (a) The wavelength λ_0 corresponding to v/f_0 needs to be much larger than Δz for voltage waveform propagation.
- (b) When we excite a step signal at the left end at $t = 0$, this signal can appear at the right end instantaneously as there is no loss by resistance.
- (c) We cannot use the Smith Chart to calculate the impedance transformation from load to source as v may not be the speed of light.
- (d) For a broadband AC response, the discrete transmission line will behave like a band-pass filter around f_{bragg} .
- (e) For a broadband AC response, the discrete transmission line will behave like a low-pass filter with the corner frequency around f_{bragg} .

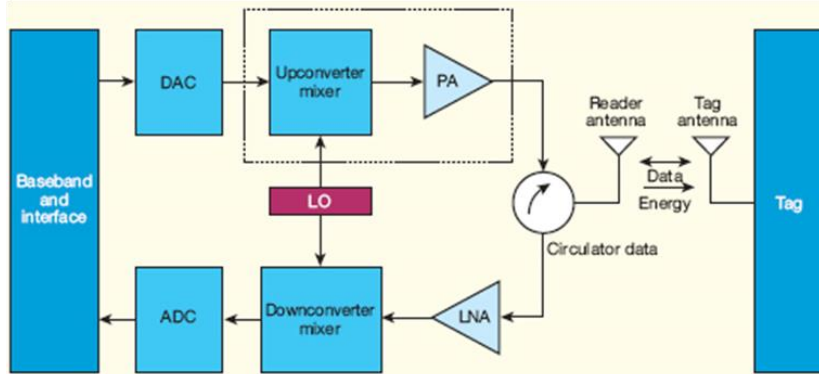3. **(Circulator in a RFID reader)** For the RFID transceiver below, the circulator has 1dB pass loss and -60dB isolation. The transmission loss from reader to tag at the given distance is -45dB . The power amplifier (PA) will emit 30dBm . The low-noise amplifier (LNA) has $I_{1\text{dBcomp}}$ at -10dBm . $f_{LO} = 1\text{GHz}$.



Block diagrams for RFID. Questions 3 – 8 all used the same parameters and conditions.

- (a) The tag will receive about -30dBm power.
 (b) The LNA will receive about -62dBm power from tags.
 (c) The self jamming will be at the level of -30dBm power.
 (d) The LNA will have a signal-to-interference ratio of 15dB .
 (e) The LNA will have a signal-to-interference ratio of -5dB .
 (f) We expect significant signal distortion at the receiver path.
4. **(PA noise and coherent receiver)** The PA above has a gain of 20dB , noise figure of 8dB , $IIP_{IM2} = 25\text{dBm}$, and $IIP_{IM3} = 15\text{dBm}$. The PA output needs an SNR of 20dB for its commands to be correctly decoded by the tag.
- (a) The SNR at the PA input needs to be around 12dB .
 (b) The noise power at the PA input needs to be smaller than -18dBm .
 (c) For thermal noise at -174dBm/Hz , the bandwidth needs to be smaller than 10MHz to satisfy the transmitter SNR requirements.
 (d) The noise figure of the downconverter mixer is not critical as long as LNA has reasonable gain.
 (e) As LO is shared between the transmitter and the receiver, the phase noise of LO will not distort the baseband information.
 (f) As LO is shared between the transmitter and the receiver, the LNA nonlinearity will not cause any DC drift in the direct conversion.

5. **(PA nonlinear parameters)** Use the same PA in question 4 for questions 5 and 6. Fill in the following PA nonlinear parameters, which are independent of the input level. Give both numerical values AND units. Assume nonlinearity is caused by gain saturation and $Z_0 = 50\Omega$.

OIP_{H2}	OIP_{H3}	a_2	a_3

6. **(PA nonlinear responses)** What would be the correct nonlinear output responses in dBm when the PA output is at 30dBm?

p_{IM2}	p_{H2}	p_{IM3}	p_{H3}

7. **(Phase noise in LO)** You make noise power density measurements for the above LO around 1GHz and obtain the following table.

Δf	10Hz	100Hz	1kHz	10kHz	100kHz	1MHz
Noise power density (dBm/Hz)	-73	-104	-124	-145	-165	-164

- Only thermal noise is dominant over the entire range of measured Δf .
- The corner $1/f^3$ frequency is significantly lower than the LO half bandwidth $f_0/2Q$.
- The surface-oriented Flicker noise dominates over thermal noise at $\Delta f = 10\text{kHz}$.
- We can extrapolate the noise power density at 1Hz to be around -63dBm/Hz .
- We need to consider the DC drift issue for the RFID transceiver.



8. **(Nonlinearity and noise interplay)** The received signal after the downconverter mixer contains many spurious frequency elements (spurs) that make the A/D has high bit error rate. To reduce the number and magnitude of the spurious frequency components,
- Decrease IIP_{IM3} of the PA.
 - Use a larger LO magnitude to boost the signal level to PA.
 - Reduce the LO phase noise by adding a good-quality bandpass filter.
 - Increase the noise figure of the receiver mixer.
 - Increase the IIP_{H2} of the LNA.
 - Add a bandpass filter between the tag antenna and the tag.
9. **(Use of RF parameter matrices)** For the S, T, Y, Z and ABCD matrices in the RF module representation, which choice(s) below are correct? Unilateral means output will not affect input.
- The matrix representation is for linear, small-signal calculation as a function of frequency.
 - All S and T parameters are dimensionless.
 - ABCD parameters are dimensionless.
 - For unilateral amplifiers, S_{12} and Y_{12} are 0.
 - For unilateral amplifiers, the S and T matrices are not defined in the reverse signal direction.
 - For unilateral amplifiers, the determinant of the ABCD matrix is 0.
 - For unilateral amplifiers, the determinant of the S matrix is always 0.
10. **(Cascade of RF modules)** Two RF amplifiers are cascaded to obtain a larger gain. Amp1 has $g_1 = 10\text{dB}$; $NF_1 = 2\text{dB}$; $OIP_{IM3} = 25\text{dBm}$. Amp2 has $g_2 = 20\text{dB}$; $NF_2 = 10\text{dB}$; $OIP_{IM3} = 15\text{dBm}$. Assume the worst case of IM3 combination in the cascade.

Cascade	g_{cas} (dB)	NF_{cas} (dB)	$OIP_{IM3,cas}$ (dBm)
Amp1 → Amp2			
Amp2 → Amp1			

Part II. Analysis questions. Please box your final answers clearly. For brief explanation, use 1 – 2 sentences only.

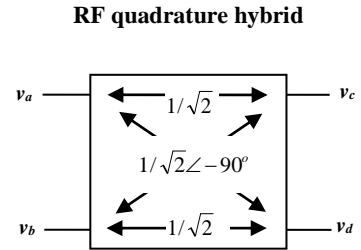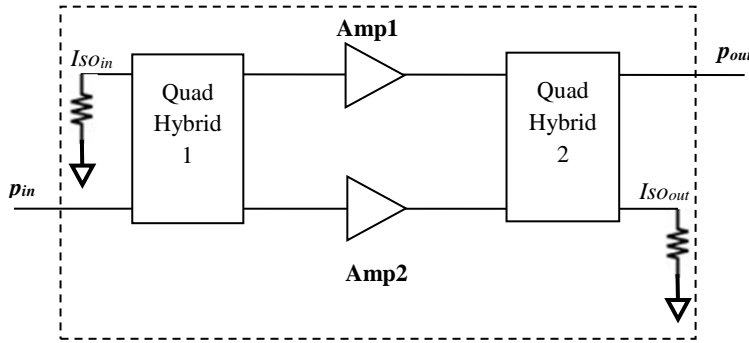11. **(Quadrature hybrid amplifier)** For the quadrature hybrid amplifier below with $Z_0 = 50\Omega$, the individual amplifiers can be described by:

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}_{amp1} = \begin{bmatrix} 0.1 & 0 \\ 10 & 0.1 \end{bmatrix}$$



a) What are the input and output impedance of Amp1 in Ω ? (2 pts)

b) First assume that Amp1 and Amp2 are identical in every aspect. What are the S parameters for the block in the dash-line box? Remember that S parameters are complex numbers. (4 pts)


c) The cross capacitance in Amp1 and Amp2 has caused small leakage to have nonzero $S_{12} = -40\text{dB}$. p_{out} is connected to an antenna and leaks in a signal of -20dBm . Will this signal pollute p_{in} ? If so, what is the leakage signal power in dBm at p_{in} ? (4 pts)

- d) Now ignore the small effect of S_{12} . If you measure the S parameters for Amp2 and find that they are slightly different as below. Estimate the S parameters for the block in the dash-line box now? Assume the quadrature hybrid is still ideal. **(4 pts)** For $p_{in} = 0\text{dBm}$, estimate the power dissipated in Iso_{in} and Iso_{out} . **(4 pts)**

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}_{amp2} = \begin{bmatrix} 0.1 & 0 \\ 8 & 0.15 \end{bmatrix}$$

- e) If both Amp1 and Amp2 have $IIP_{H2} = 31\text{dBm}$ (but their S parameters are slightly different like in part (d)), for $p_{in} = 0\text{dBm}$, estimate the 2nd harmonic H2 power at p_{out} . Assume that H2 will make the total output voltage at Amp1 and Amp2 smaller (i.e., a_2 is negative). **(4 pts)** Compare your answer of the H2 power if $p_{in} = 0\text{dBm}$ is just fed into Amp1. **(4 pts)**

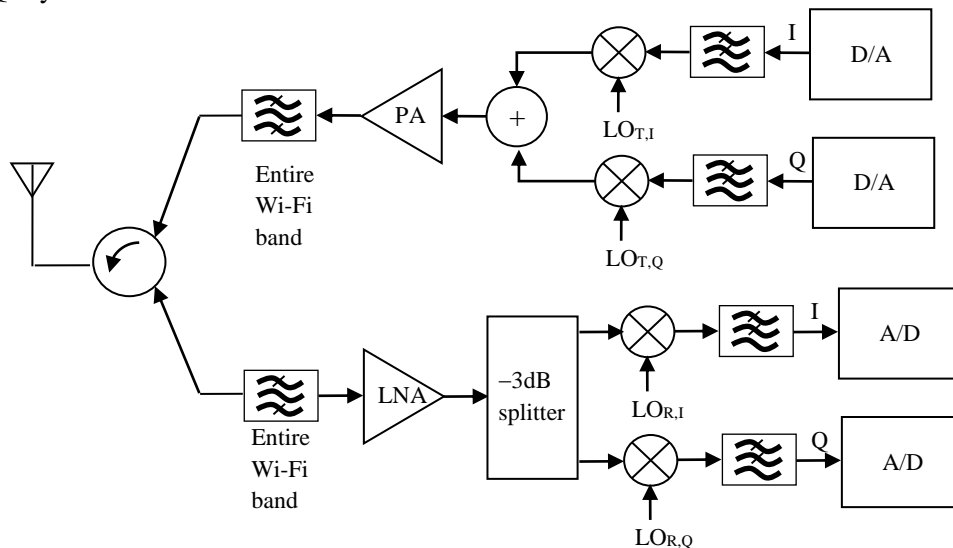12. **(Direct-conversion Q-ary transceivers)** A direct-conversion Wi-Fi transceiver with 4-bit per symbol Q-ary modulation is shown below.



a) The receiver signal power P_R can be modeled by $P_R = P_T K \left(\frac{d_0}{d} \right)^\gamma$, where P_T is the transmitted power, K and d_0 are empirical constants, and the parameter γ represents the multi-path effect. $\gamma = 2$ for line-of-sight channels, and the typical three-hop indoor path has $\gamma = 6$. By using $P_T = 30\text{dBm}$ for both your router and mobile unit, you measure P_R for the line-of-sight and typical indoor three-hop situations. Fill in the table below. **(4 pts)**

Distance between unit to router	0.3m	1m	3m	10m	30m
Receiver signal power at line of sight (dBm)		-20dBm			
Receiver signal power for three-hop indoor (dBm)		-30dBm			

b) For the baseband channel bandwidth of 20MHz and 36Mb/s bit rate, how would you set the low-pass filter corner frequency interfacing with the data converter? What should be the A/D data converter sampling frequency? Briefly explain. **(4 pts)**

c) As the data converter has relatively high frequency, we choose 10 bits for A/D. With no additional variable-gain amplifier, we can only use the LO signal strength to tune the gain in the receiver path. Assume the mixer gain is proportional to the LO voltage magnitude. To accommodate the dynamic range in P_R for the indoor three-hop situation, what is the LO voltage tuning ratio? (4 pts)

d) During the full duplex mode in frequency division, the transmitter and the receiver on the mobile unit are on different channels, which are set up during the initial polling stage. A nearby transmitter of another mobile unit, which can have up to 0dBm leaking to LNA, can however cause received signal desensitization through the LNA nonlinearity. The gain of the LNA is 15dB. Assume the main nonlinearity of LNA is 3rd order. At $P_T = 30\text{dBm}$, estimate the required $\text{IIP}_{\text{IM}3}$ of the LNA. (6 pts) The desensitization amplitude can be estimated by:

$$\text{Amplitude}(f_a) = a_1 A + \frac{a_3}{4} (3A^3 + 6AB^2) \cong A \left(a_1 + \frac{3a_3}{2} B^2 \right). \quad \text{Use } Z_0 = 50\Omega. \quad \text{The signal } A \text{ represents the intended channel which is desensitized by } B.$$

e) For the DC drift concerns, which of the following choice(s) will increase the DC drift at the receiver A/D converter? (4 pts)

- (a) Increasing the LO_R leakage to the antenna.
- (b) Increasing the LO_T leakage to antenna.
- (c) Increasing the noise figure of the LO_T mixer.
- (d) Decreasing $\text{IIP}_{\text{IM}3}$ of the PA.
- (e) Decreasing $\text{IIP}_{\text{IM}2}$ of the LNA.
- (f) $\text{LO}_{R,I}$ and $\text{LO}_{R,Q}$ are not exactly differed by 90° .

