

ECE 2300
Digital Logic & Computer Organization
Fall 2016

Boolean Algebra



Cornell University

Lecture 2: 1

Boolean Algebra

- **Mathematical tool for analyzing and simplifying logic circuits**
- **Boolean algebra (George Boole, 1854)**
 - Two-valued algebraic system
 - Used to formulate true or false postulations
- **Switching algebra (Claude Shannon, 1938)**
 - Adopted Boolean algebra for digital circuits
 - Terms “Boolean algebra” and “switching algebra” are used interchangeably

Boolean Equations

- Describe digital functions
- **variable = expression**
- Variables are either 1 or 0
 - True or False
 - On or Off
 - Set or Reset (or Not Set)
 - Asserted or Deasserted
- Basic operators are AND, OR, and NOT

Operator Precedence

- What does $W \cdot X' + Y \cdot Z$ mean?
- Operator precedence rules
 1. NOT
 2. AND
 3. OR

Definitions


- Literal: variable or its complement
- Product term: AND of literals
 - $X' \cdot Y$
- Sum term: OR of literals
 - $X + Y + Z'$

Sum-of-products

- OR of product terms

$$- X \cdot Y \cdot Z + Y' \cdot Z'$$


- Circuits look something like this

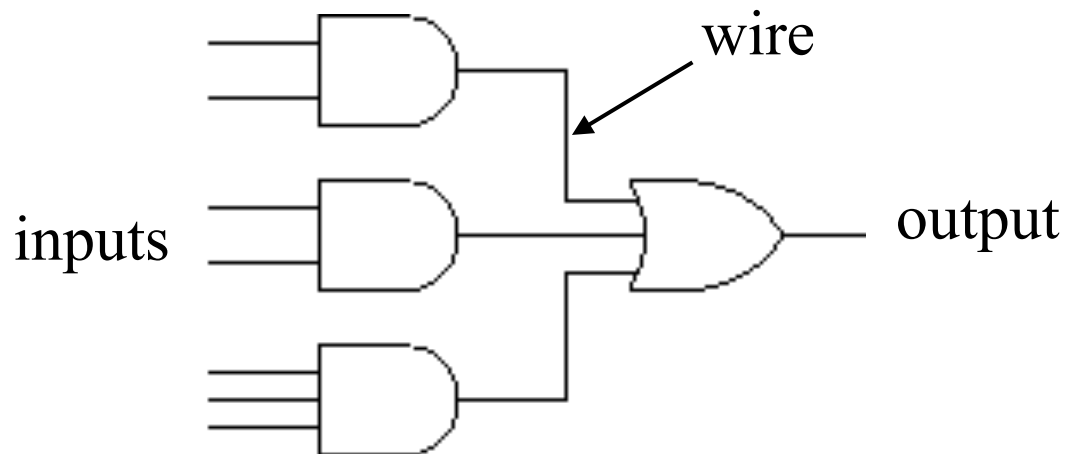

AND-OR

Product-of-sums

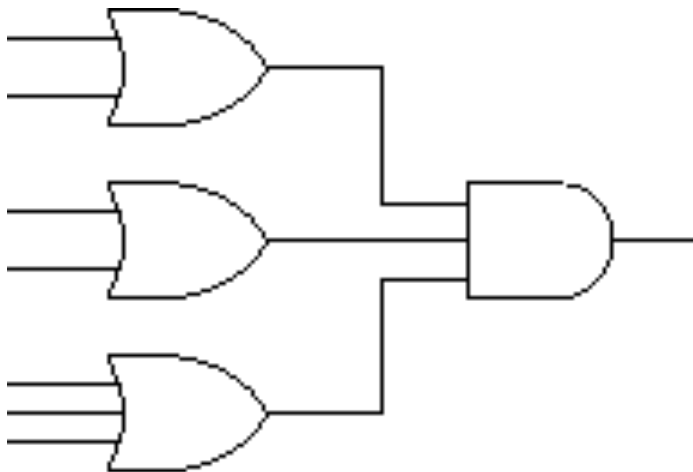- **AND of sum terms**
 - $(X+Y'+Z) \cdot (Y+Z') \cdot (X+Z') \cdot (X+Y+Z')$
- **Circuits look something like this**



OR-AND

Digital logic functions can be expressed as SOP or POS

More Definitions

- **Normal term**: Product or sum term in which every variable appears, and exactly once
- **Minterm**: Normal product
 - $X \cdot Y' \cdot Z$
- **Maxterm**: Normal sum
 - $X' + Y + Z'$

Minterms & Maxterms

XYZ	minterm	minterm name	maxterm	maxterm name
000	$X'Y'Z'$	m_0	$X+Y+Z$	M_0
001	$X'Y'Z$	m_1	$X+Y+Z'$	M_1
010	$X'YZ'$	m_2	$X+Y'+Z$	M_2
011	$X'YZ$	m_3	$X+Y'+Z'$	M_3
100	$XY'Z'$	m_4	$X'+Y+Z$	M_4
101	$XY'Z$	m_5	$X'+Y+Z'$	M_5
110	XYZ'	m_6	$X'+Y'+Z$	M_6
111	XYZ	m_7	$X'+Y'+Z'$	M_7

Two Ways to Express a Logic Function

- Canonical sum: The sum (OR) of minterms for which $F=1$

$$\begin{aligned} - F &= X' \cdot Y' \cdot Z' + X' \cdot Y \cdot Z + X \cdot Y' \cdot Z' + X \cdot Y \cdot Z \\ &= \Sigma_{X,Y,Z}(0,3,4,7) \end{aligned}$$

- Canonical product: The product (AND) of maxterms for which $F=0$

$$\begin{aligned} - F &= (X+Y+Z') \cdot (X+Y'+Z) \cdot (X'+Y+Z') \cdot (X'+Y'+Z) \\ &= \Pi_{X,Y,Z}(1,2,5,6) \end{aligned}$$

XYZ	F
000	1
001	0
010	0
011	1
100	1
101	0
110	0
111	1

- $F = \Sigma_{X,Y,Z}(0,3,4,7) = \Pi_{X,Y,Z}(1,2,5,6)$

Axioms of Boolean Algebra

- **Definitions that are assumed true**
- **Obey the principle of duality**
 - **Interchange 1 and 0, AND and OR, still correct**
 - **Many axioms come in pairs**

Axioms of Boolean Algebra

- Binary

(A1) $X = 0$ if $X \neq 1$ (A1') $X = 1$ if $X \neq 0$

- Complement

(A2) If $X = 0$, then $X' = 1$ (A2') If $X = 1$, then $X' = 0$

Other complement symbols: $\sim X$, $/X$, \overline{X}

Axioms of Boolean Algebra

- **AND and OR**

$$(A3) \quad 0 \cdot 0 = 0$$

$$(A4) \quad 1 \cdot 1 = 1$$

$$(A5) \quad 0 \cdot 1 = 1 \cdot 0 = 0$$

$$(A3') \quad 1 + 1 = 1$$

$$(A4') \quad 0 + 0 = 0$$

$$(A5') \quad 1 + 0 = 0 + 1 = 1$$

- **A1-A5 completely define Boolean algebra**
 - Everything else derived from these axioms

Single Variable Theorems

- Identity: (T1) $X \cdot 1 = X$ (T1') $X + 0 = X$
- Null Element: (T2) $X \cdot 0 = 0$ (T2') $X + 1 = 1$
- Idempotency: (T3) $X \cdot X = X$ (T3') $X + X = X$
- Involution: (T4) $(X')' = X$
- Complements: (T5) $X \cdot X' = 0$ (T5') $X + X' = 1$
- Can prove by *perfect induction*
 - Show that all possible inputs meet the theorem

Proof by Perfect Induction

$$(T3) \quad X \cdot X = X$$

$$X=0 \rightarrow 0 \cdot 0 = 0$$

$$X=1 \rightarrow 1 \cdot 1 = 1$$

$$(T3') \quad X + X = X$$

$$X=0 \rightarrow 0 + 0 = 0$$

$$X=1 \rightarrow 1 + 1 = 1$$

$$(T5) \quad X \cdot X' = 0$$

$$(T5') \quad X + X' = 1$$

Two and Three Variable Theorems

- **Commutativity**

(T6) $X \cdot Y = Y \cdot X$

(T6') $X + Y = Y + X$

- **Associativity**

(T7) $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$

(T7') $(X + Y) + Z = X + (Y + Z)$

- **Distributivity**

(T8) $X \cdot Y + X \cdot Z = X \cdot (Y + Z)$

(T8') $(X + Y) \cdot (X + Z) = X + (Y \cdot Z)$

AND distributes over OR

OR distributes over AND

Two and Three Variable Theorems

- **Covering**

$$(T9) \quad X \cdot (X+Y) = X$$

$$(T9') \quad X+X \cdot Y = X$$

- **Combining**

$$(T10) \quad X \cdot Y + X \cdot Y' = X$$

$$(T10') \quad (X+Y) \cdot (X+Y') = X$$

- **Consensus**

$$(T11) \quad X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$$

$$(T11') \quad (X+Y) \cdot (X'+Z) \cdot (Y+Z) = (X+Y) \cdot (X'+Z)$$

Duality

- **A_n' is the dual of A_n , T_n' is the dual of T_n**
- **Deriving the dual**
 - **Use parentheses to denote operator precedence**
 - **Swap 0's and 1's, AND's and OR's**

Duality Derivation Examples

- Derive T9' from T9

$$X+X\cdot Y = X \quad (\text{T9})$$

$$X+(X\cdot Y) = X \quad (\text{precedence})$$

$$X\cdot(X+Y) = X \quad (\text{T9'})$$

- Derive T11' from T11

$$X\cdot Y+X'\cdot Z+Y\cdot Z = X\cdot Y+X'\cdot Z \quad (\text{T11})$$

$$(X\cdot Y)+(X'\cdot Z)+(Y\cdot Z) = (X\cdot Y)+(X'\cdot Z) \quad (\text{precedence})$$

$$(X+Y)\cdot(X'+Z)\cdot(Y+Z) = (X+Y)\cdot(X'+Z) \quad (\text{T11'})$$

De Morgan's Theorem

- So important, also known as De Morgan's *Law*

$$(T12) \quad (X1 \cdot X2 \cdot \dots \cdot Xn)' = X1' + X2' + \dots + Xn'$$

$$(T12') \quad (X1 + X2 + \dots + Xn)' = X1' \cdot X2' \cdot \dots \cdot Xn'$$

De Morgan Example


- By DeMorgan's Law

$$(X \cdot Y \cdot Z)' = X' + Y' + Z'$$


- Proof by perfect induction

XYZ	$(X \cdot Y \cdot Z)'$	$X' + Y' + Z'$
000	1	1
001	1	1
010	1	1
011	1	1
100	1	1
101	1	1
110	1	1
111	0	0


NAND Logic Gate

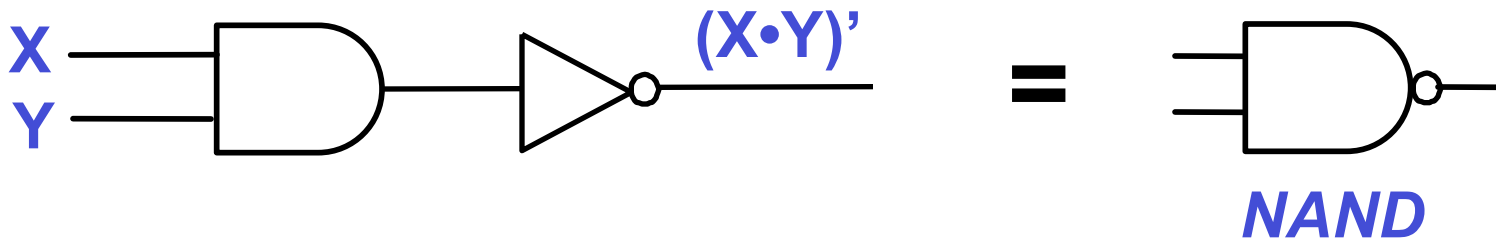

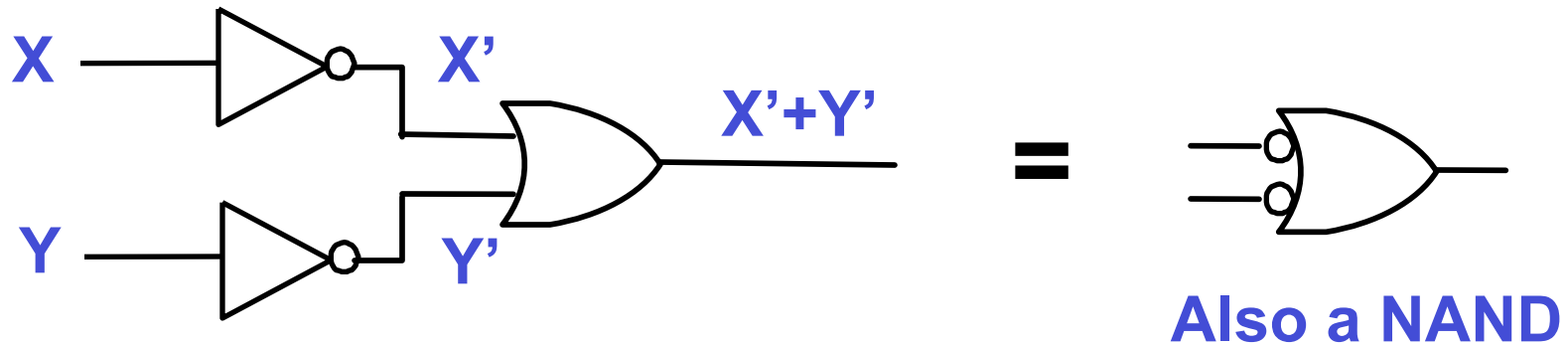
Using De Morgan's Law: $(X \cdot Y)' = X' + Y'$



Sum-of-products Revisited

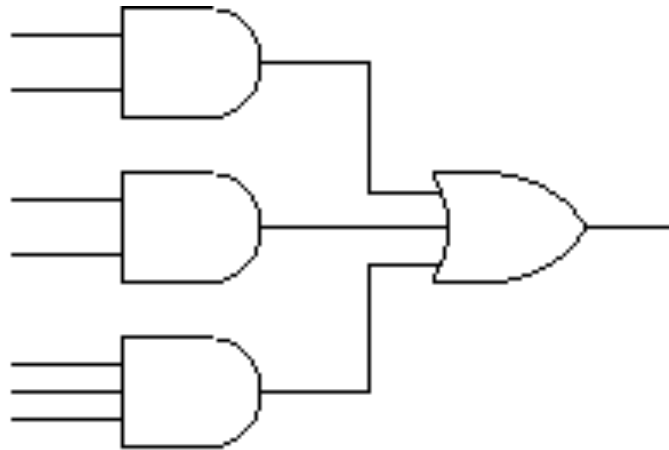


AND-OR

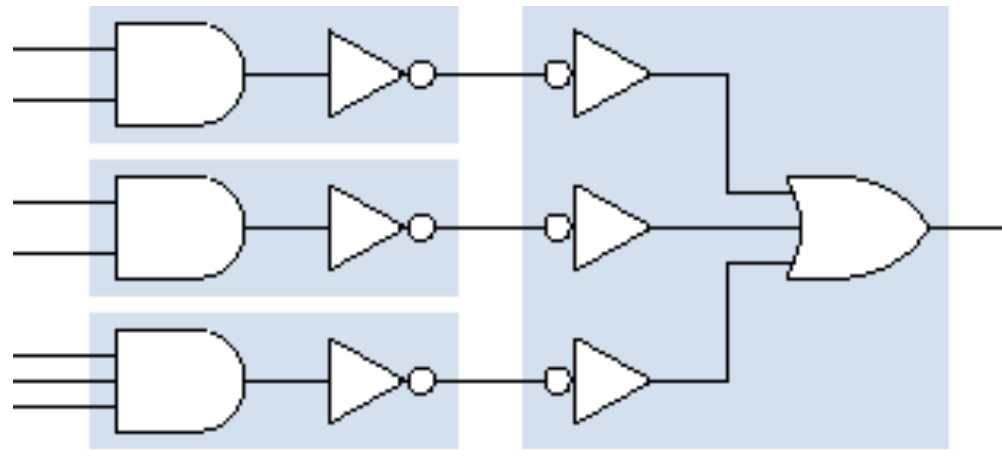


NAND-NAND


NOR Logic Gate

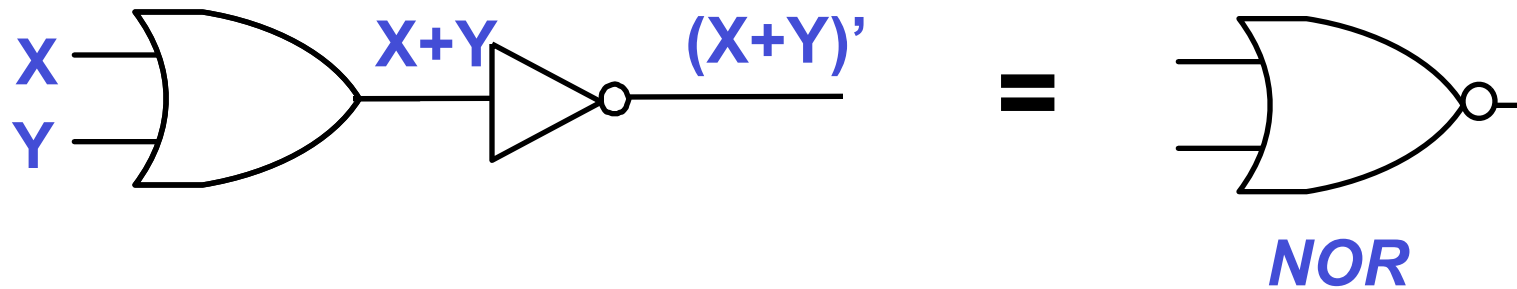


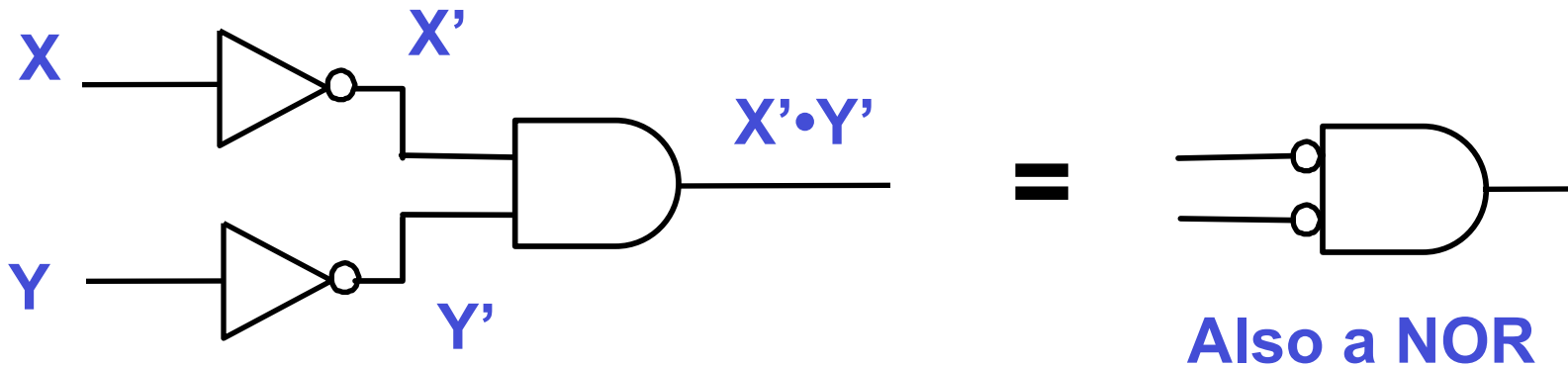
Using De Morgan's Law: $(X+Y)' = X' \cdot Y'$



Product-of-sums Revisited

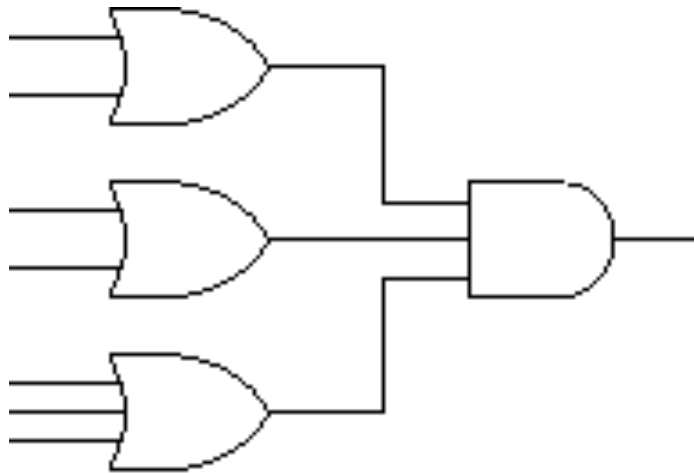

OR-AND

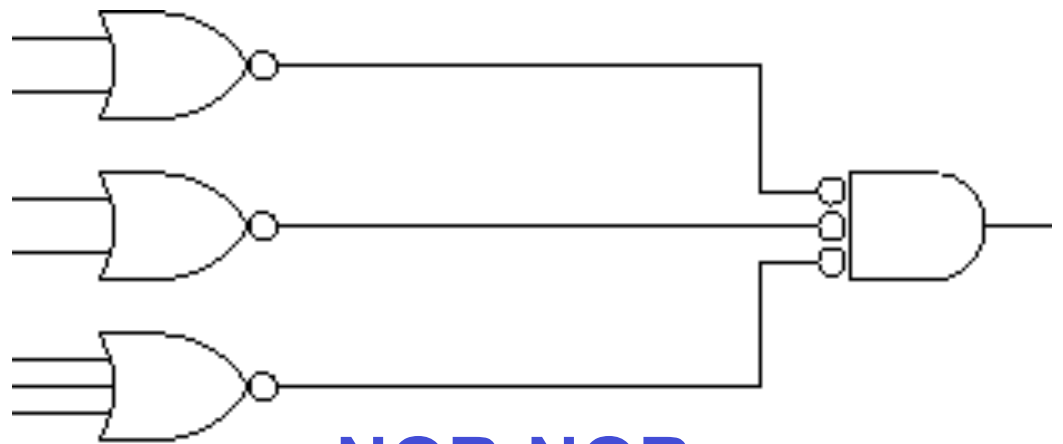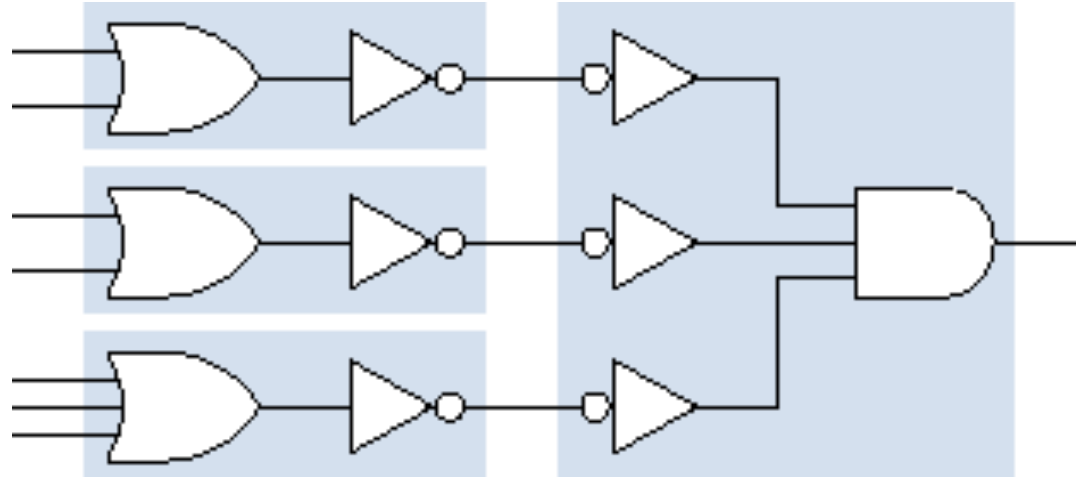

NOR-NOR

Two Ways to Express a Logic Function

- Canonical sum: The sum of minterms for which $F=1$

$$\begin{aligned} - F &= X' \cdot Y' \cdot Z' + X' \cdot Y \cdot Z + X \cdot Y' \cdot Z' + X \cdot Y \cdot Z \\ &= \Sigma_{X,Y,Z}(0,3,4,7) \end{aligned}$$

- Canonical product: The product of maxterms for which $F=0$

$$\begin{aligned} - F &= (X+Y+Z') \cdot (X+Y'+Z) \cdot (X'+Y+Z') \cdot (X'+Y'+Z) \\ &= \Pi_{X,Y,Z}(1,2,5,6) \end{aligned}$$

XYZ	F
000	1
001	0
010	0
011	1
100	1
101	0
110	0
111	1

- $F = \Sigma_{X,Y,Z}(0,3,4,7) = \Pi_{X,Y,Z}(1,2,5,6)$

Algebraic Simplification

- **Apply theorems to canonical sum (product) to reduce (1) the number of terms, and (2) the number of literals in each term**
- **Results in a more compact expression and lower cost digital logic implementation**

Algebraic Simplification Example

- **1-bit binary adder**

- inputs: A, B, Carry-in
- outputs: Sum, Carry-out



- **Truth Table → Canonical sum**

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = A' \cdot B' \cdot Cin + A' \cdot B \cdot Cin' + A \cdot B' \cdot Cin' + A \cdot B \cdot Cin$$

$$Cout = A' \cdot B \cdot Cin + A \cdot B' \cdot Cin + A \cdot B \cdot Cin' + A \cdot B \cdot Cin$$

Idempotency and Combining Theorems

- Idempotency: $X+X = X$
- Combining: $X \cdot Y + X \cdot Y' = X$

Algebraic Simplification Example

$$\begin{aligned} \text{Cout} &= A' \cdot B \cdot \text{Cin} + A \cdot B' \cdot \text{Cin} + A \cdot B \cdot \text{Cin}' + A \cdot B \cdot \text{Cin} \\ &= A' \cdot B \cdot \text{Cin} + A \cdot B' \cdot \text{Cin} + A \cdot B \cdot \text{Cin}' + A \cdot B \cdot \text{Cin} + A \cdot B \cdot \text{Cin} && \text{(idempotency)} \\ &= B \cdot \text{Cin} + A \cdot B' \cdot \text{Cin} + A \cdot B \cdot \text{Cin}' + A \cdot B \cdot \text{Cin} && \text{(combining)} \\ &= B \cdot \text{Cin} + A \cdot B' \cdot \text{Cin} + A \cdot B \cdot \text{Cin}' + A \cdot B \cdot \text{Cin} + A \cdot B \cdot \text{Cin} && \text{(idempotency)} \\ &= B \cdot \text{Cin} + A \cdot \text{Cin} + A \cdot B \cdot \text{Cin}' + A \cdot B \cdot \text{Cin} && \text{(combining)} \\ &= B \cdot \text{Cin} + A \cdot \text{Cin} + A \cdot B && \text{(combining)} \end{aligned}$$

Reduction in Hardware Cost

$$\begin{aligned} \text{Cout} &= A' \cdot B \cdot \text{Cin} + A \cdot B' \cdot \text{Cin} + A \cdot B \cdot \text{Cin}' + A \cdot B \cdot \text{Cin} \\ &= B \cdot \text{Cin} + A \cdot \text{Cin} + A \cdot B \end{aligned}$$

3 inverters

4 three-input ANDs

1 four-input OR



3 two-input ANDs

1 three-input OR

Example: Prime Number Detector

- $F = 1$ if number xyz is prime
- Step 1: Lay out truth table
- Step 2: Derive canonical form
 - $F = \sum_{x,y,z}(1,2,3,5,7) = x'y'z + x'yz' + x'yz + xy'z + xyz$
 - $F = \prod_{x,y,z}(0,4,6) = (x+y+z)(x'+y+z)(x'+y'+z)$
- Step 3: Simplify expression
 - Algebraic simplification
 - Systematic minimization (next time)

xyz	F
000	0
001	1
010	1
011	1
100	0
101	1
110	0
111	1

Algebraic Simplification

- $F = \sum_{x,y,z}(1,2,3,5,7)$


$$= x'y'z + x'yz' + x'yz + xy'z + xyz$$

$$= x'y'z + x'y + xy'z + xyz$$

[combining]

$$= x'y'z + x'y + xz$$

[combining]

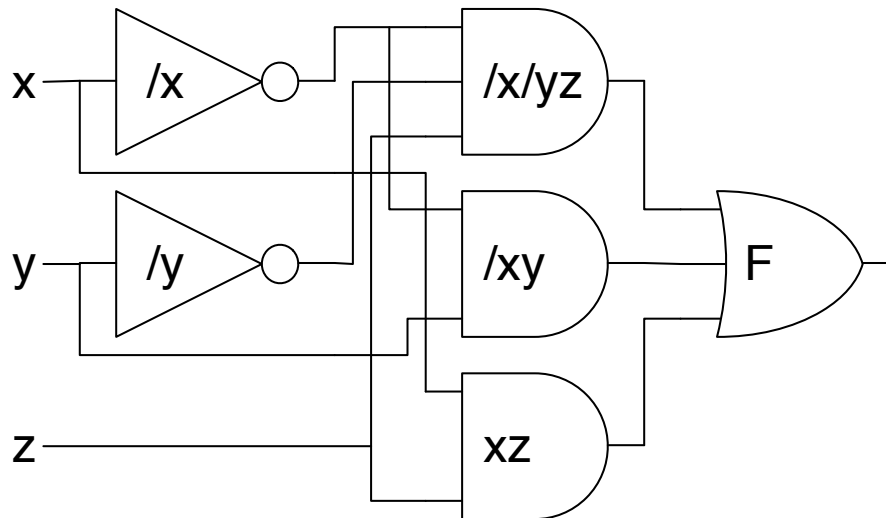

Before Next Class

- H&H 2.4-2.7

Next Time

Combinational Logic Minimization