

# **ECE 2300**

# **Digital Logic & Computer Organization**

## **Fall 2016**

## **CMOS Logic**


## **Combinational Building Blocks**




Cornell University
 
# 5 Variable Karnaugh Maps

$$F = \sum_{VWXYZ} (0, 2, 5, 6, 7, 8, 10, 13, 14, 15, 16, 18, 21, 23, 24, 26, 29, 31)$$



$$V=0$$

 

$$V=1$$

$$F = X' \cdot Z' + X \cdot Z + V' \cdot Y \cdot Z'$$

# 5 Variable *Overlaid* Karnaugh Map

$$F = \Sigma_{VWXYZ}(0,2,5,6,7,8,10,13,14,15,16,18,21,23,24,26,29,31)$$


VWX									
YZ		000	001	011	010	100	101	111	110
	00	1			1	1			1
	01		1	1			1	1	
	11		1	1			1	1	
	10	1	1	1	1	1			1

# 5 Variable *Mirrored* Karnaugh Map


$$F = \Sigma_{VWXYZ}(0,2,5,6,7,8,10,13,14,15,16,18,21,23,24,26,29,31)$$

VWX									
YZ		000	001	011	010	110	111	101	100
00	1			1	1				1
01		1	1			1	1		
11		1	1			1	1		
10	1	1	1	1	1				1

# Sum-of-products

 


**AND-OR**

 


**NAND-NAND**

# Product-of-sums



 


**OR-AND**

 

**NOR-NOR**

# NOT, NAND, and NOR

   

A	Y
0	1
1	0

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

# NOT Gate Input & Output Voltages


A	Y		A	Y		A	Y
0	1	→	L	H	→	0V	5V
1	0		H	L		5V	0V

- When the input voltage is *low* (0), the output should be connected to the voltage supply (1)
- When the input voltage is *high* (1), the output should be connected to ground (0)
- Can build a NOT using two types of switches
  - Type 1: Closed when input = 0, open when input = 1
  - Type 2: Closed when input = 1, open when input = 0



# NOT Using Switches


A	Y
0	1
1	0

 


A	Y
L	H
H	L



A	Y
0V	5V
5V	0V

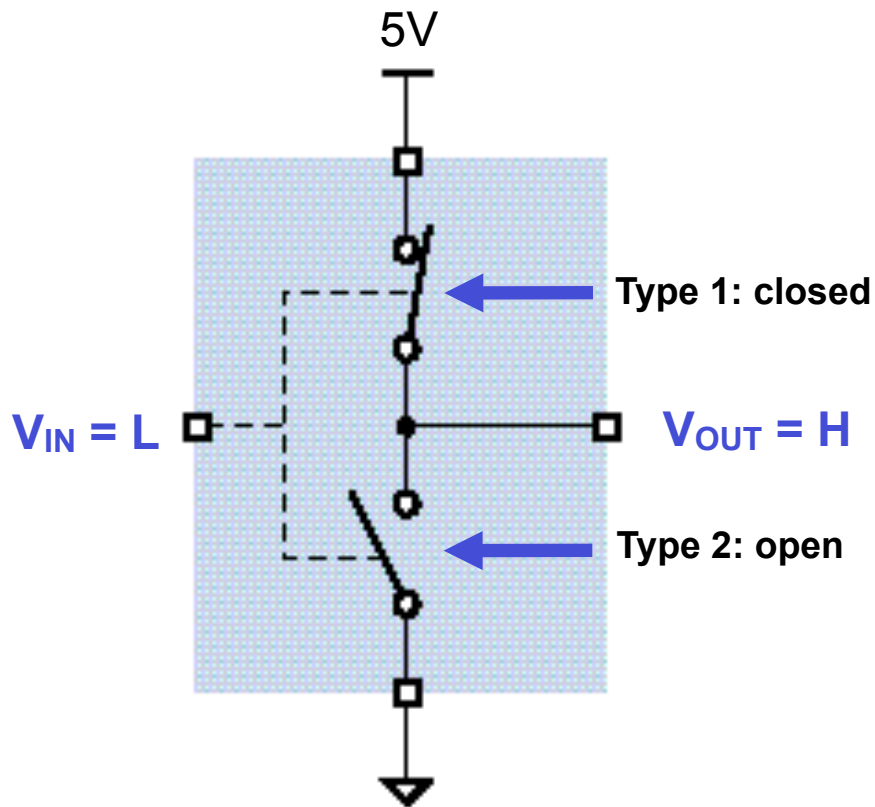


# NAND Using Switches

 


Inputs		Output
A	B	Y
L	L	H

# NAND Using Switches

 

Inputs		Output
A	B	Y
L	L	H
H	L	H


# NAND Using Switches

 

Inputs		Output
A	B	Y
L	L	H
H	L	H
H	H	L
 
# MOS Transistors

- Metal-Oxide Semiconductor Field-Effect Transistors (MOSFETs)





**Voltage-controlled resistance**

- Extreme changes in resistance (0 to  $\infty$ ) make transistors act like switches
  
# MOS Transistors

- Current flows when ON (*conducting*)
- No current flows when OFF (*not conducting*)
- Type 1 and Type 2 switches




○ = LOW closes the switch
 
# MOS Transistors


- **PMOS**

- Closed when input is low
- Open when input is high



- **NMOS**

 - Closed when input is high
- Open when input is low





PMOS and NMOS  
have  
*complementary*  
properties

# CMOS Logic Gates

- **Complementary MOS**
- **Uses both NMOS and PMOS devices such that there is no direct supply-ground path**
  - **Dissipates little power when the inputs don't change**
- **CMOS dominates the digital IC market**
- **Our focus: Static CMOS gates**
  - **Other types as well (pseudo-NMOS, domino, ...)**




# CMOS Inverter

  

$V_{in}$  is high  
T1 is off  
T2 is on  
 $V_{out}$  is low

$V_{in}$  is low  
T1 is on  
T2 is off  
 $V_{out}$  is high


# CMOS NAND Gate

 


A	B	$Q1$	$Q2$	$Q3$	$Q4$	Z
L	L	off	on	off	on	
L	H	off	on	on	off	
H	L	on	off	off	on	
H	H	on	off	on	off	



# 3 Input CMOS NAND Gate

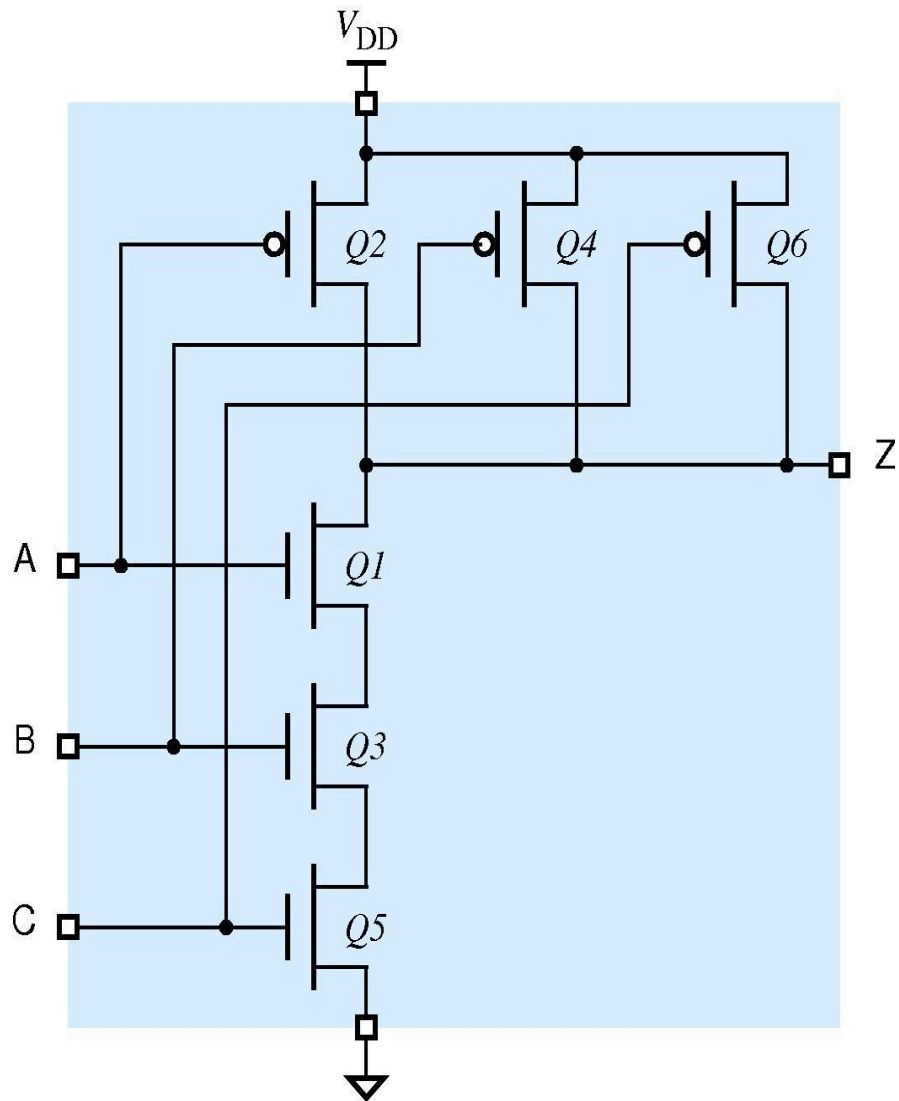


A	B	C	Q1	Q2	Q3	Q4	Q5	Q6	Z
L	L	L	off	on	off	on	off	on	
L	L	H	off	on	off	on	on	off	
L	H	L	off	on	on	off	off	on	
L	H	H	off	on	on	off	on	off	
H	L	L	on	off	off	on	off	on	
H	L	H	on	off	off	on	on	off	
H	H	L	on	off	on	off	off	on	
H	H	H	on	off	on	off	on	off	

 


An  $n$  input gate uses  $2n$  transistors

# CMOS NOR Gate

 

$A$	$B$	$Q1$	$Q2$	$Q3$	$Q4$	$Z$
L	L	off	on	off	on	
L	H	off	on	on	off	
H	L	on	off	off	on	
H	H	on	off	on	off	

 

# Combinational Building Blocks



- **More complex functions built from basic gates**
  - Multiplexers
  - Decoders
  - Exclusive OR (XOR)
  - Comparators
  - Priority encoders
  - Tristate drivers
- **Typically tens to hundreds of transistors**
  - *Medium Scale Integration (MSI)*
- **Building blocks for digital systems**

# Multiplexer (“mux”)

- **Connects one of  $n$  inputs to the output**
  - *select* control inputs pick one of the  $n$  sources
  - $\lceil \log_2 n \rceil$  *select* bits
- **Useful when multiple data sources need to be routed to a single destination**
  - Example: select 1-of- $n$  *registers* as input to the *ALU*

  
# 2-to-1 Mux

- Selects one of two inputs to appear at the output
- $q = s' \cdot d0 + s \cdot d1$



 
# 4-to-1 Mux

- Selects one of four inputs to appear at the output
- $q = s_1' \cdot s_0' \cdot d_0 + s_1' \cdot s_0 \cdot d_1 + s_1 \cdot s_0' \cdot d_2 + s_1 \cdot s_0 \cdot d_3$







# b-bit Mux Organization

 

- **b bits from the selected data input are connected to the data output**
- **Internally organized as b n-to-1 muxes**
  - **Each mux circuit handles 1 bit**
  - **Same *select* input(s) sent to each mux**
 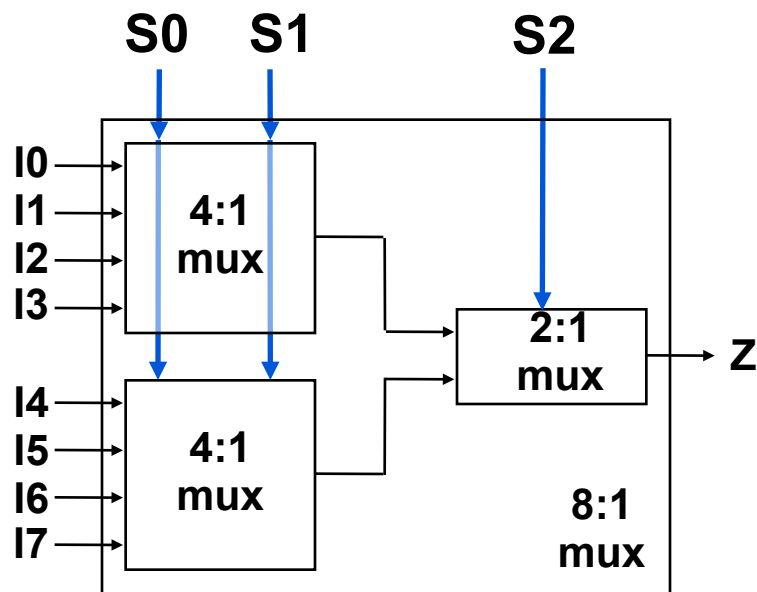
# Cascading Multiplexers



- Large multiplexers can be implemented by cascading smaller ones



# Logic Functions Using Muxes

- Any function of  $n$  variables can be implemented with a  $2^n:1$  multiplexer
  - Input variables connected to *select* inputs
  - Data inputs tied to 0 or 1 according to truth table


A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

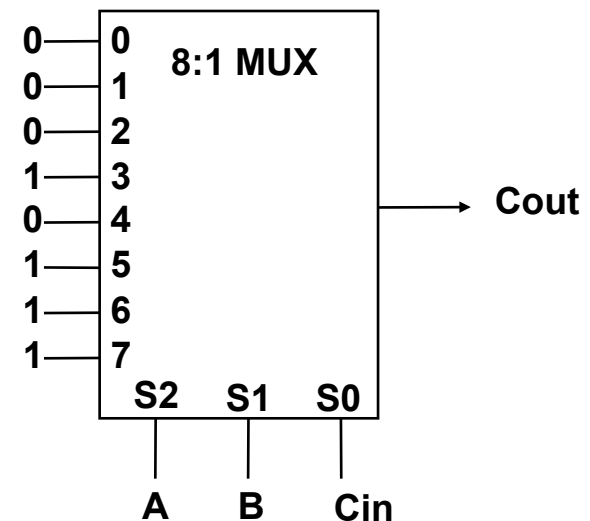 
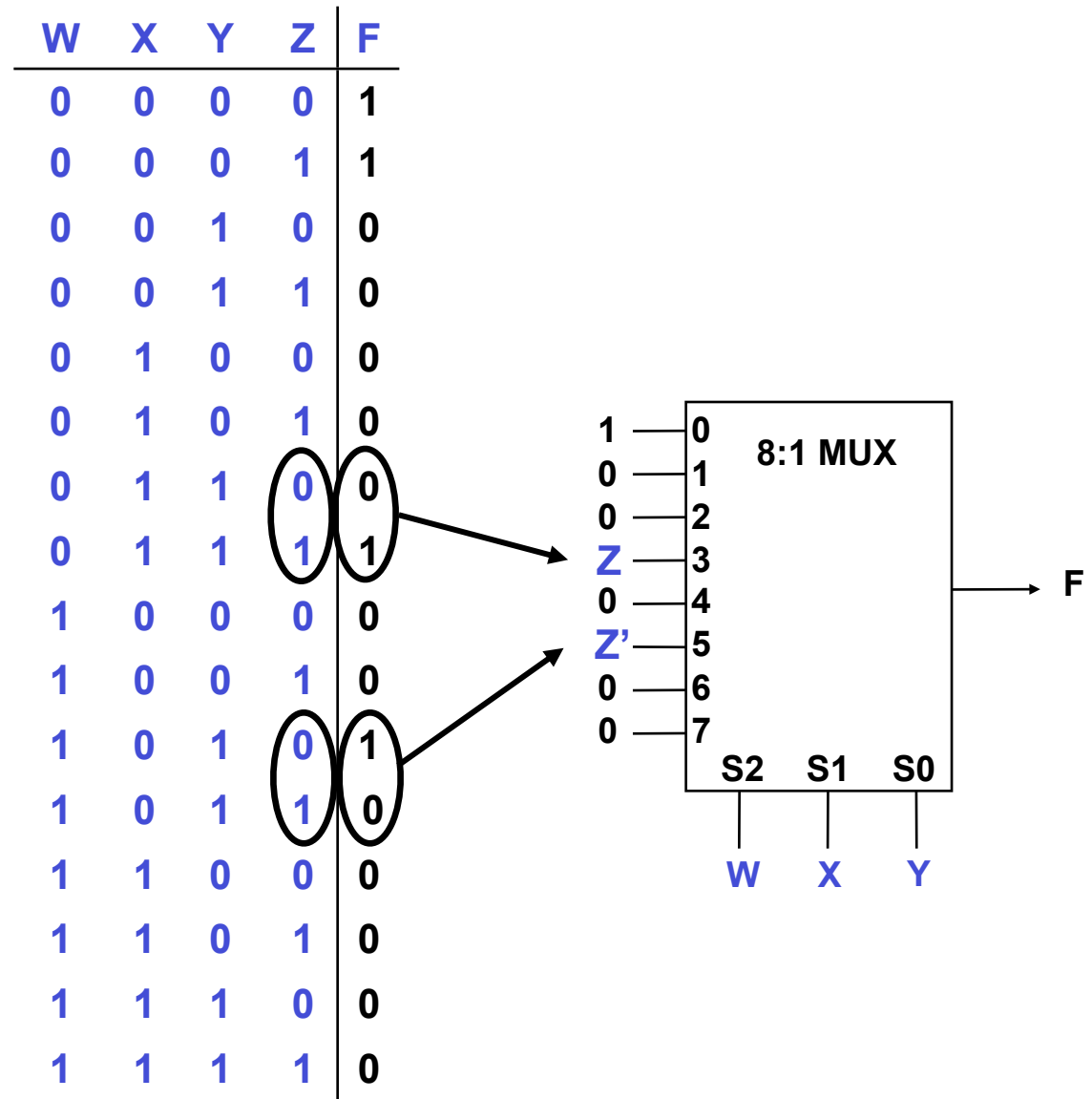
# Getting Away with a Smaller Mux

- Can use  $2^{n-1}:1$  multiplexer and at most one inverter

- Connect  $n-1$  input variables to *select* inputs
- Data inputs tied to 0, 1,  $n^{\text{th}}$  variable, or inverted  $n^{\text{th}}$  variable



# Next Time

**More Combinational Building Blocks**