

ECE 2300
Digital Logic & Computer Organization
Fall 2016

More Combinational Building Blocks



Cornell University

Combinational Building Blocks

- **More complex functions built from basic gates**
 - Multiplexers
 - Decoders
 - Exclusive OR (XOR)
 - Comparators
 - Priority encoders
 - Tristate drivers
- **Typically tens to hundreds of transistors**
 - *Medium Scale Integration (MSI)*
- **Building blocks for digital systems**


Multiplexer (“mux”)

- Connects one of n inputs to the output
- Useful when multiple data sources need to be routed to a single destination
 - Example: select 1-of- n *registers* as input to the *ALU*

Decoder

- **n inputs, 2^n outputs**
- **Each output corresponds to a unique input value**
- **At most one output asserted at a time**

2-to-4 Decoder

 


A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$Y_0 = A_1' \cdot A_0'$$



$$Y_1 = A_1' \cdot A_0$$

$$Y_2 = A_1 \cdot A_0'$$

$$Y_3 = A_1 \cdot A_0$$

 

2-to-4 Decoder with Enable

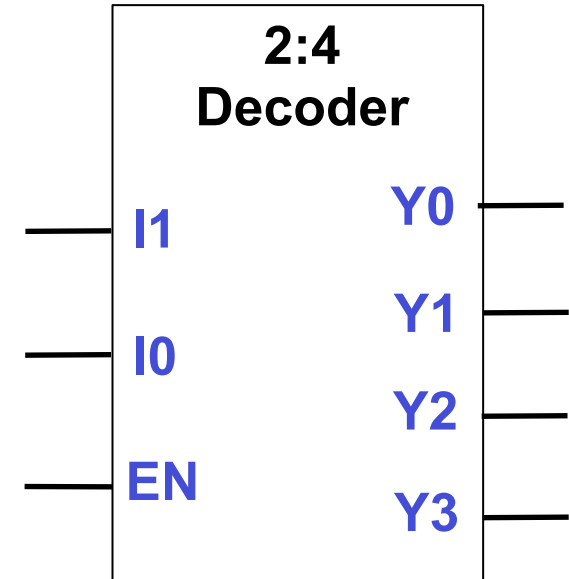 


Example Decoder Applications

- **Microprocessor instruction decoding**
 - Select the appropriate arithmetic operation depending on the decoded instruction type
- **Memories**
 - Select one of n banks of memory chips to read/write
 - Select one of n rows of memory cells within a memory chip to read/write
- **Input/output systems**
 - Select one of n I/O devices to read/write

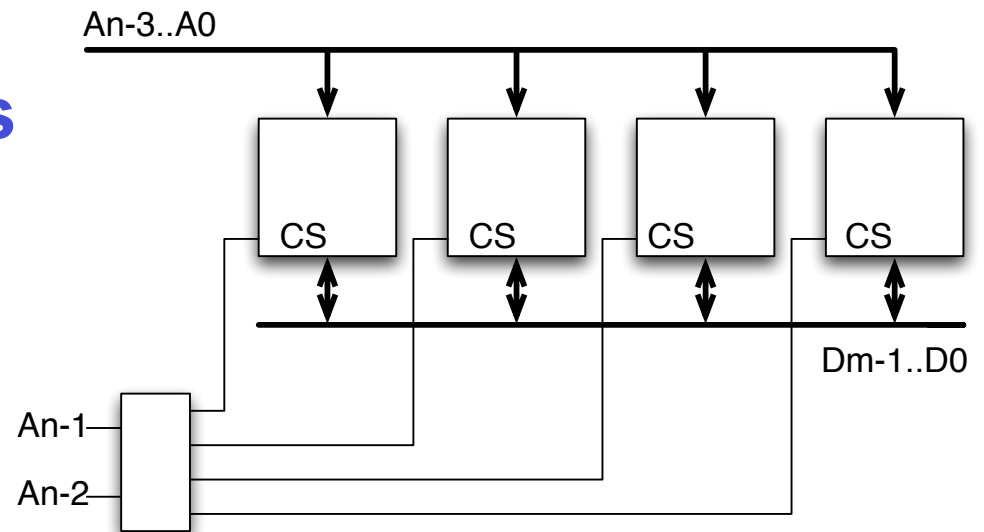
Example: Memory Decoding

- 2^n memory locations spread across 4 chips
 - 2^{n-2} locations per chip
- 2 address bits select the chip
 - Chip Select (CS)
 - Outputs of chips that are not selected are in Hi-Z state (later)
- $n-2$ address bits select row within the chip




Logic Functions Using Decoders

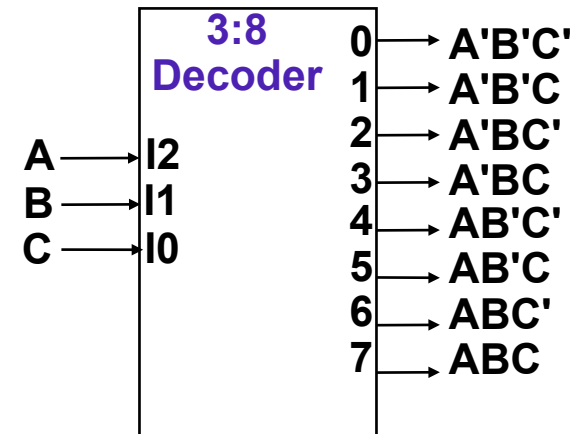- $n:2^n$ decoder can be used to implement any function of n variables
 - Connect variables to inputs
 - Appropriate minterms summed using extra gates to form the function



Logic Functions Using Decoders

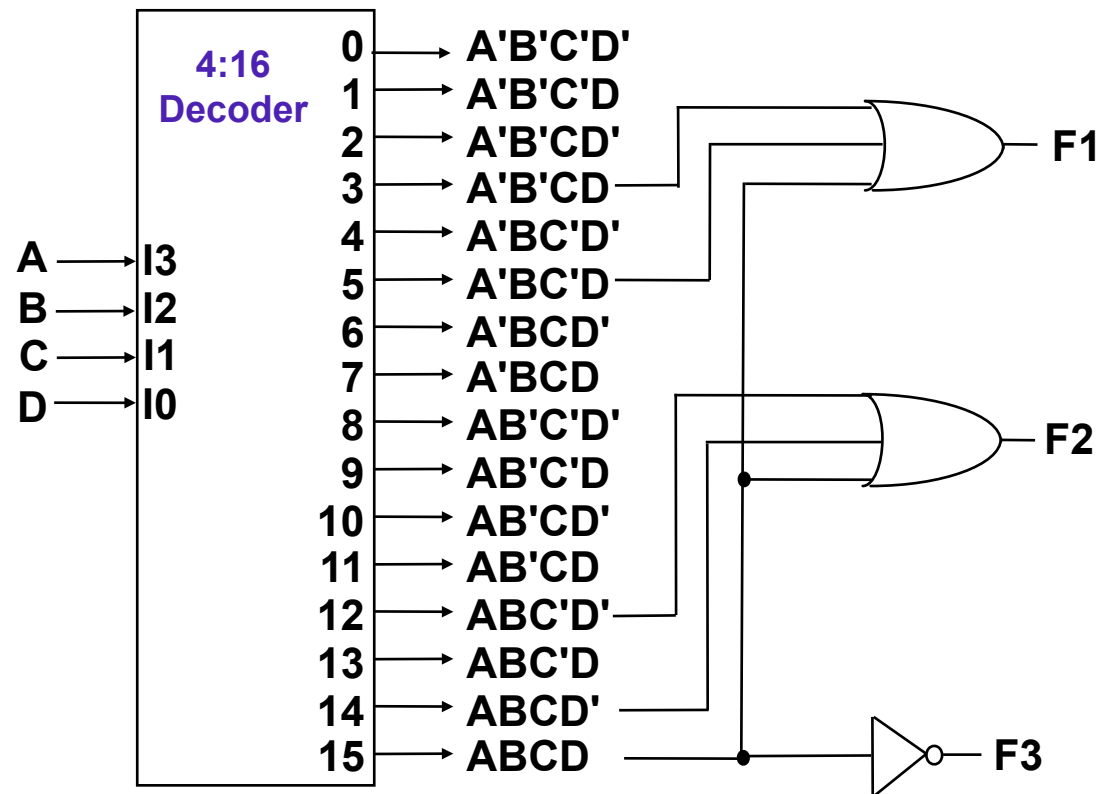- $F1 = A'B'CD + A'BC'D + ABCD$
- $F2 = ABC'D' + ABC$
- $F3 = A'+B'+C'+D'$



XOR Gate


X	Y	$X \oplus Y$	$(X \oplus Y)'$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1




- Same as an OR gate, except when inputs are 1
- Used for comparisons, error checking
- XNOR: complemented version of XOR

XOR Gate Implementations

$$F = X \cdot Y' + X' \cdot Y$$

 

 
$$\begin{aligned} F &= X \cdot Y' + X' \cdot Y \\ &= X \cdot X' + X \cdot Y' + Y \cdot Y' + X' \cdot Y \\ &= X \cdot (X' + Y') + Y \cdot (X' + Y') \\ &= X \cdot (X \cdot Y)' + Y \cdot (X \cdot Y)' \end{aligned}$$




Equality Comparators Using XOR

1-bit comparator


 


4-bit comparator

 

Encoders

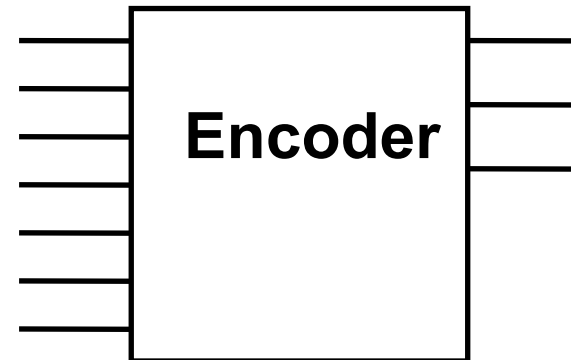 - Opposite of decoders
- 2^n inputs and n outputs




What if multiple inputs
are asserted?

Priority Encoder


- Highest numbered inputs have priority
- Example: 4-to-2 priority encoder

I3	I2	I1	I0	Y1	Y0	None
1	X	X	X	1	1	0
0	1	X	X	1	0	0
0	0	1	X	0	1	0
0	0	0	1	0	0	0
0	0	0	0	0	0	1

 

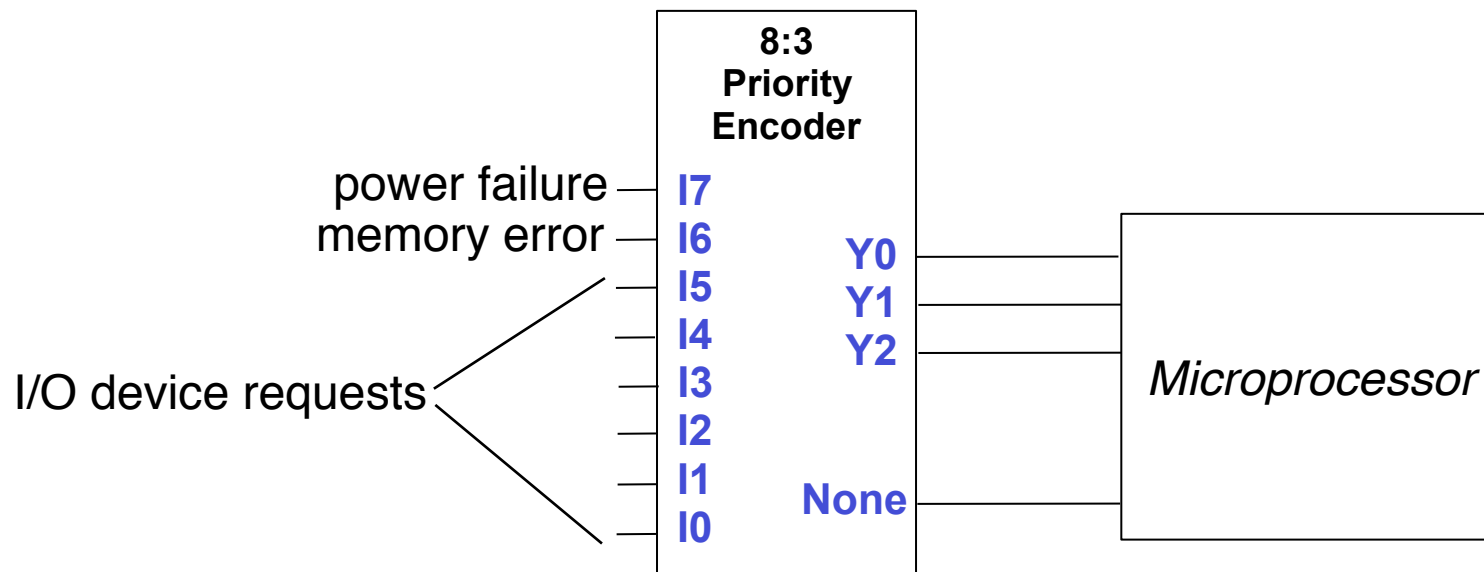
Example: Microprocessor Interrupts

- In order for devices to get service, they *interrupt* the microprocessor
- Most important requests are given priority




Multi-Drop Buses

 - **Multi-drop buses are a low-cost way to communicate data among digital devices**
- **Components of a multi-drop bus**
 - **Set of wires to connect the nodes**
 - **Special circuits for sending and receiving bus data**
 - **Control logic that decides who is allowed to send**



Tri-State Drivers

 
- Along with 0 and 1, there is a third *Hi-Z* output
 - Output “floats” - no connection to supply or ground



EN	A	OUT
0	0	Hi-Z
0	1	Hi-Z
1	0	0
1	1	1





- Used to drive a multi-drop bus
 - Only one node drives the bus, others in Hi-Z state


Tri-State Drivers

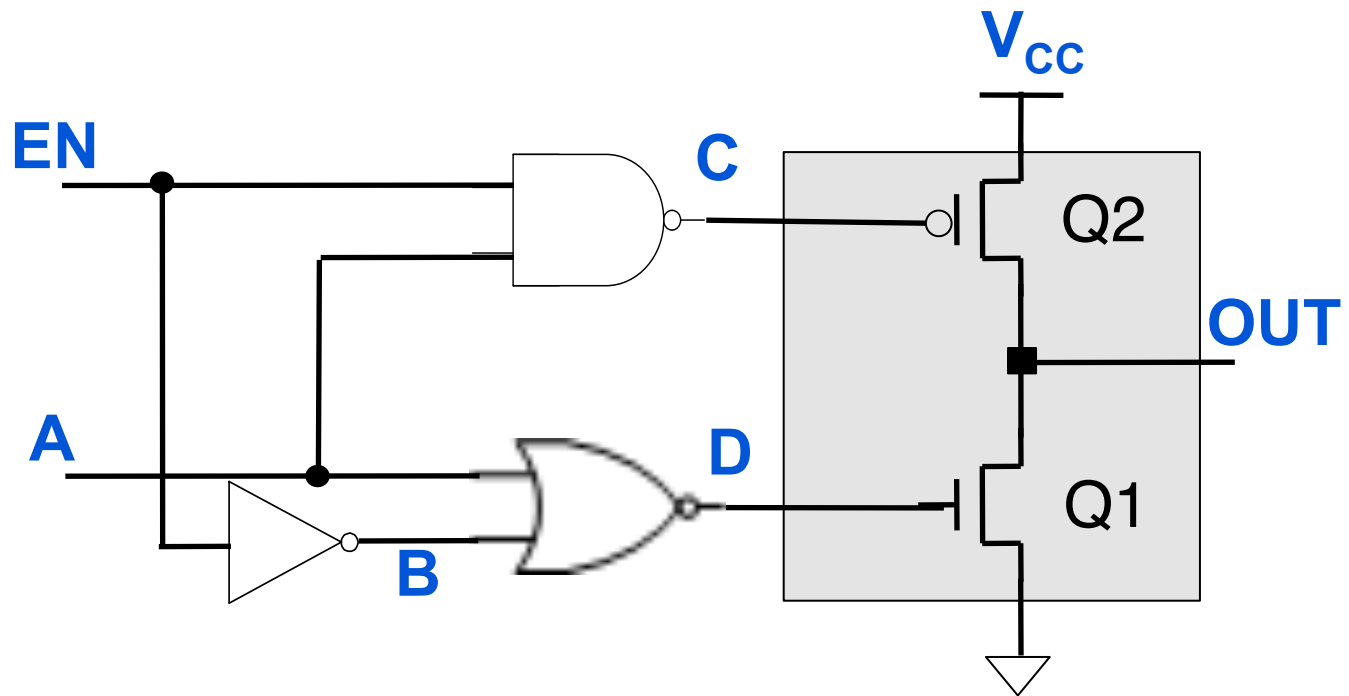

E N	A	B	C	D	Q1	Q2	OUT
L	L	H	H	L	off	off	Hi-Z
L	H	H	H	L	off	off	Hi-Z
H	L	L	H	H	on	off	L
H	H	L	L	L	off	on	H

Variations of Tri-State Drivers

    

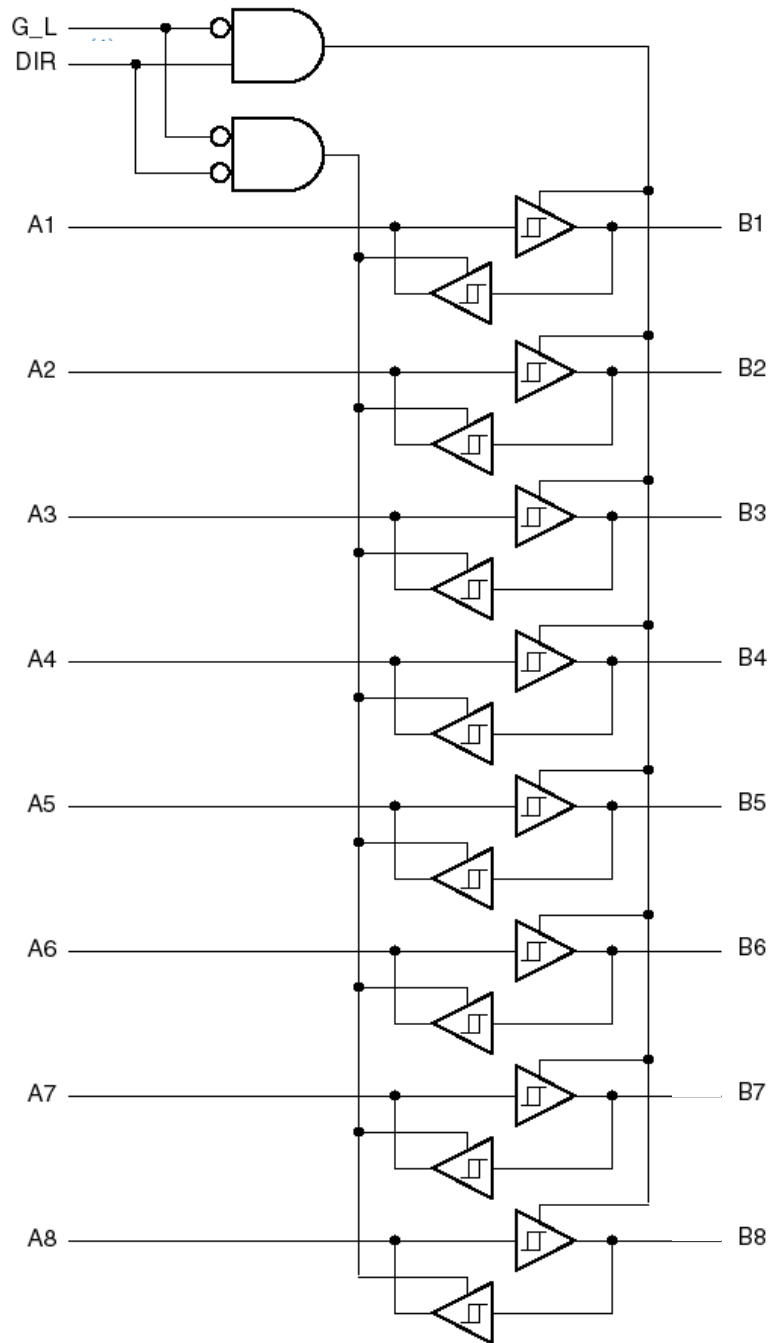

Transceiver

- Data can flow in either direction

G_L	DIR	Action
0	0	$A \leftarrow B$
0	1	$A \rightarrow B$
1	X	A,B Hi-Z

Before Next Class

- H&H 3.1-3.2

Next Time

Sequential Logic: Clocks, Latches, Flip-Flops