

**ECE 2300**  
**Digital Logic & Computer Organization**  
**Fall 2016**

**Sequential Logic:**  
**Clocks**  
**Latches**  
**Flip-Flops**  
**Counters**




Cornell University

# Combinational vs. Sequential Circuits

## Combinational Circuit



## Sequential Circuit

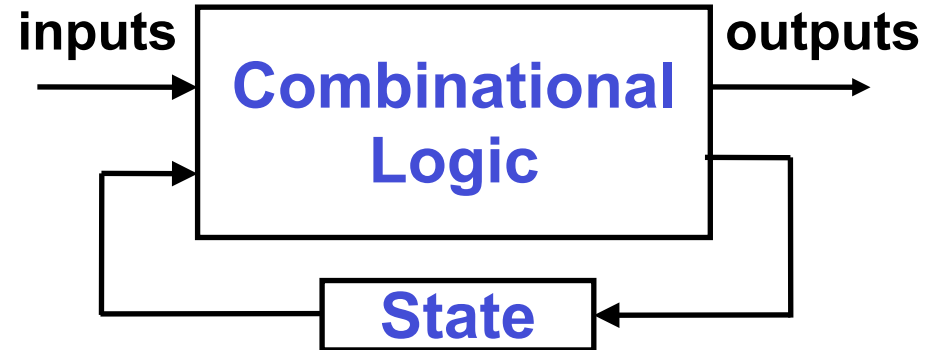

- **Combinational**

- Output depends only on current inputs

- **Sequential**


- Output depends on current inputs plus past history
- Includes memory

# Sequential Circuits



- **Outputs depend on inputs and state variables**
- **The state variables embody the past**
- **Storage elements hold the state variables**
- **A clock periodically advances the circuit**
 
# Bistable Element

- Basic storage element
- Inverters with outputs connected to inputs




# Two Stable States

  

*Need a way to change the output*

# S-R Latch (Set-Reset Latch)

 

$Q_{next}$  is new value of Q when R or S changes

Boolean expression for  $Q_{next}$  in terms of R, S, and Q:


$$\begin{aligned}
 Q_{next} &= (R + QN)' \\
 &= (R + (S + Q))' \\
 &= R' \cdot (S + Q) \\
 &= R' \cdot S + R' \cdot Q
 \end{aligned}$$

S	R	$R' \cdot S$	$R' \cdot Q$	$Q_{next}$
0	0	0	Q	Q
0	1	0	0	0
1	0	1	Q	1
1	1	0	0	0


When  $S=0$  and  $R=0$ , it holds (*latches*) its output value
 
# $\overline{S}$ - $\overline{R}$ Latch

- *S-bar-R-bar* latch
  - Built from NAND gates
  - Inputs are active low rather than active high
  - When both inputs asserted,  $Q = 1$  rather than 0



S	R	Q	QN
0	0	1	1
0	1	1	0
1	0	0	1
1	1	Q	QN

 



# D Latch

- **S-R latch sets or resets the output**
- **D latch captures input data**
- **Operates in two modes**
  - ***Open or transparent*: input flows through to output**
  - ***Closed or opaque*: output does not change**


 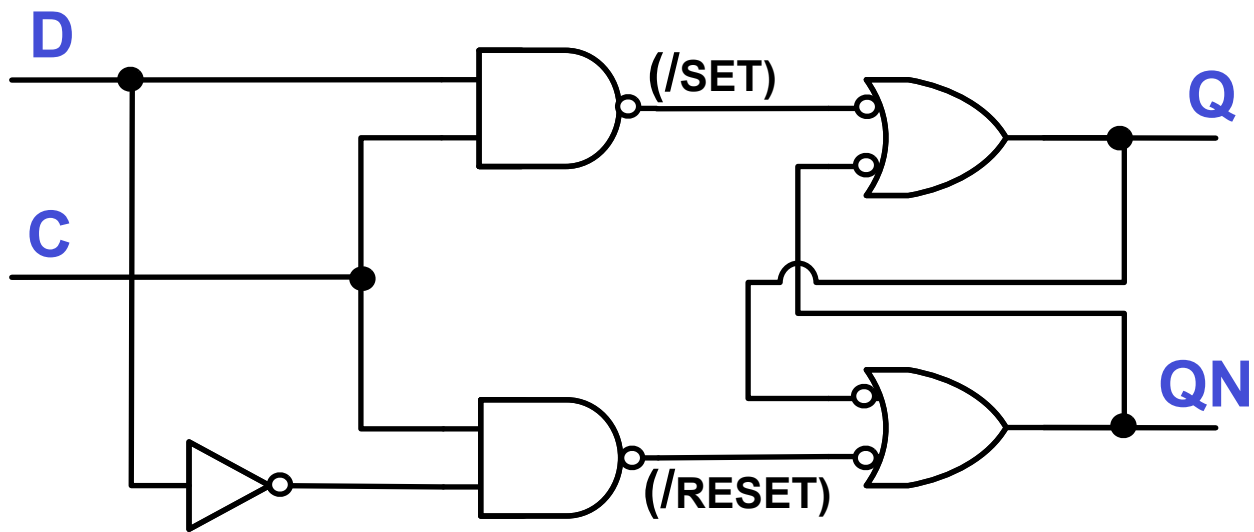
# D Latch

- When C is enabled, Q output follows D input
- When C is disabled, Q output retains last state




C	D	Q	QN
1	0	0	1
1	1	1	0
0	X	Last Q	Last QN

# Clock

- An input to a sequential circuit that changes output and state values at a predetermined rate
- Clock Period: Time between successive transitions in the same direction ( $L \rightarrow H$  or  $H \rightarrow L$ )
  - 1ms, 2ns, 250ps
- Clock Frequency:  $1/\text{period}$ 
  - 1kHz, 500MHz, 4GHz
- Triggering edge: Transition of the clock ( $H \rightarrow L$  or  $L \rightarrow H$ ) that captures input data
- Clock tick: Occurrence of a triggering edge



# Clock Waveform

 


# Flip-Flop

- **Samples input on *triggering edge* of clock**
  - Rising edge → *positive edge-triggered flip-flop*
  - Falling edge → *negative edge-triggered flip-flop*
- **D flip-flop: Two D latches back-to-back**


# D Flip-Flop

  


# D Flip-Flop

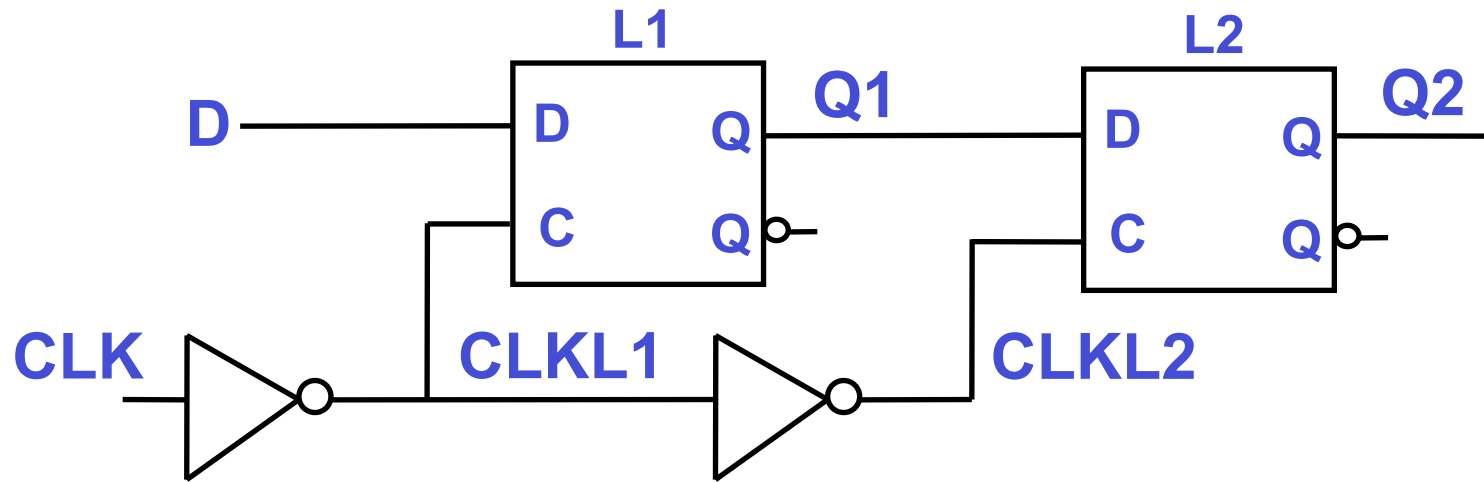

D	CLK	Q	QN
0		0	1
1		1	0
X	0	Last Q	Last QN
X	1	Last Q	Last QN

 

# D Flip-Flop with Enable

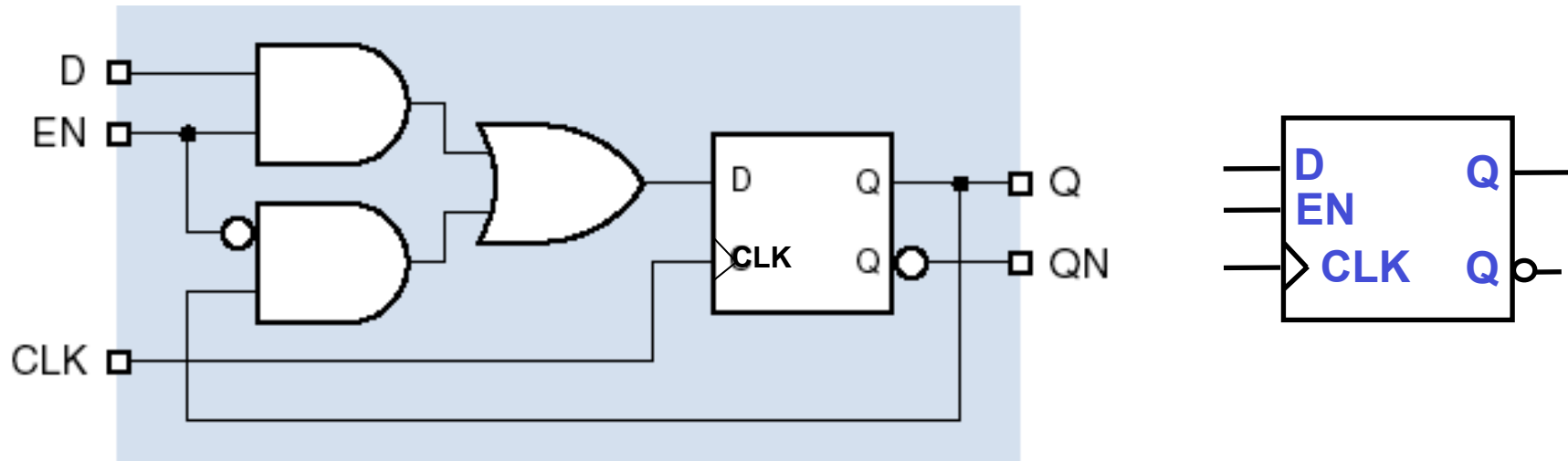


# Preset/Clear Inputs

- **Preset**

- Forces Q to 1

- **Clear**

- Forces Q to 0

 



- **Asynchronous or synchronous**

- **Asynchronous:** Operate independent of the clock
- **Synchronous:** Only take effect on the triggering edge of the clock



# J-K Flip-Flop

- A flip-flop equivalent of an S-R latch

 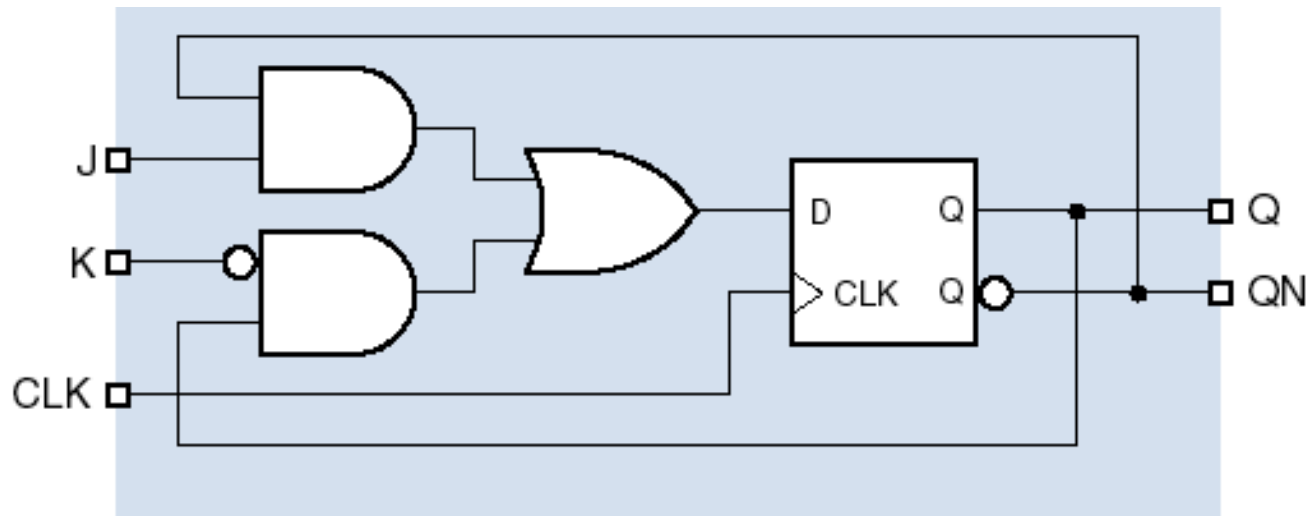


$$Q = J \cdot Q' + K' \cdot Q$$

J	K	CLK	Q	QN
x	x	0	last Q	last QN
x	x	1	last Q	last QN
0	0		last Q	last QN
0	1		0	1
1	0		1	0
1	1		last QN	last Q

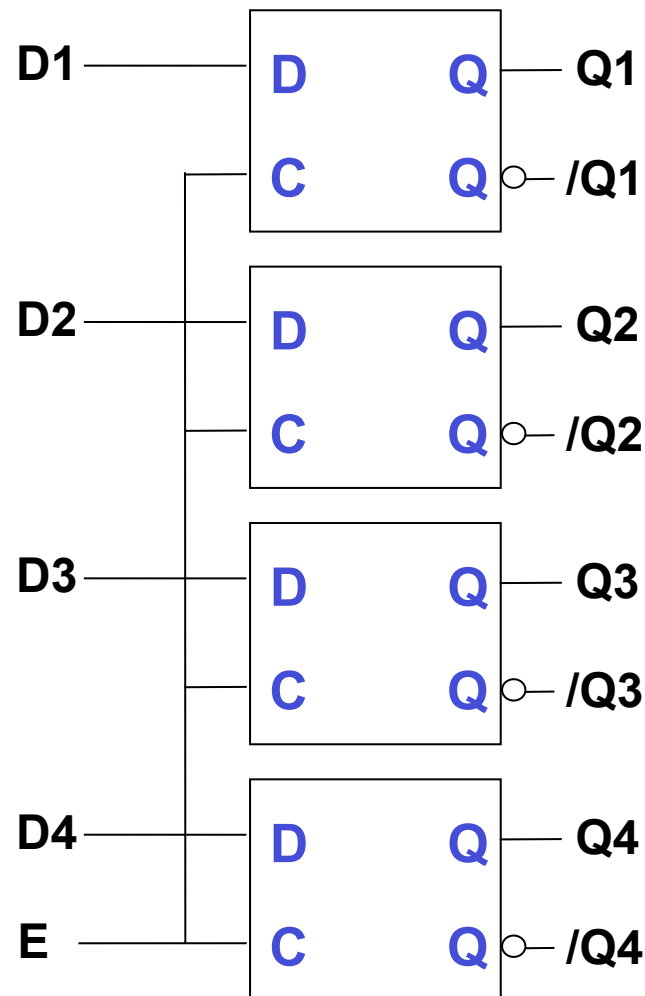
# Multi-bit Latch

- Simultaneously latches multiple bits
- “Latch” may refer to 1 bit latch or multi-bit one



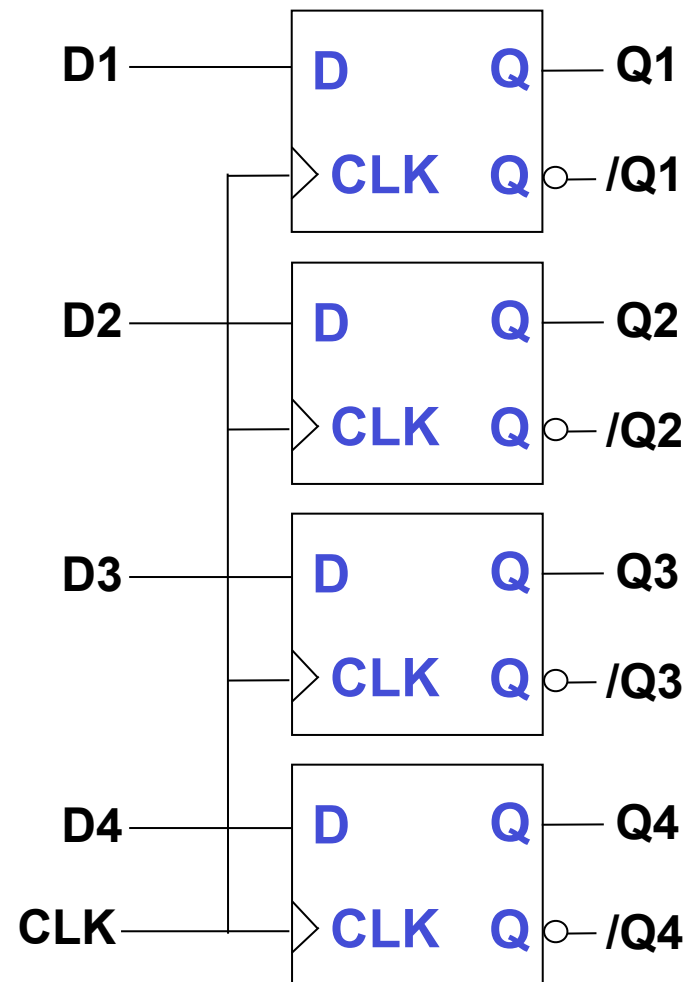
# Register

- Collection of FFs operating off common clock
- A single D flip-flop is a 1-bit register



 
# D Latch

- Output follows input when enable asserted (*open*)
- Input captured when enable deasserted (*closed*)
- Used for building memories


 
# D Flip-Flop

- Output changes only on triggering clock edge
- Used for sequential logic design



# Binary Counter

- Counts in binary in a particular sequence
- Advances at every tick of the clock
- Many types

Up	Down	Free Running	Divide-by-n	n-to-m
0 0 0	1 1 1	0 0 0	0 0 0	n
0 0 1	1 1 0	0 0 1	0 0 1	n+1
0 1 0	1 0 1	0 1 0	0 1 0	n+2
0 1 1	1 0 0	0 1 1	0 1 1	⋮
1 0 0	0 1 1	1 0 0	1 0 0	⋮
1 0 1	0 1 0	1 0 1	⋮	m-1
⋮	⋮	1 1 0	⋮	m
⋮	⋮	1 1 1	n-1	n
⋮	⋮	0 0 0	0 0 0	n+1
		⋮	0 0 1	⋮
		⋮		⋮

# Up Counter Sequence

0 0 0

0 0 1

0 1 0

0 1 1

1 0 0

1 0 1

1 1 0

1 1 1

0 0 0

0 0 1



Toggles every clock tick  
that two right bits = 11

Toggles every clock tick

Toggles every clock tick  
that right bit = 1

# T (*Toggle*) Flip-Flop

- Output toggles each clock tick

  


**Q: 0, 1, 0, 1, 0, 1, 0, ...**



 
# T Flip-Flop with Enable

- Output toggles only if enabled ( $EN = 1$ )
- Output does not change if  $EN = 0$




# Free Running Binary Up Counter

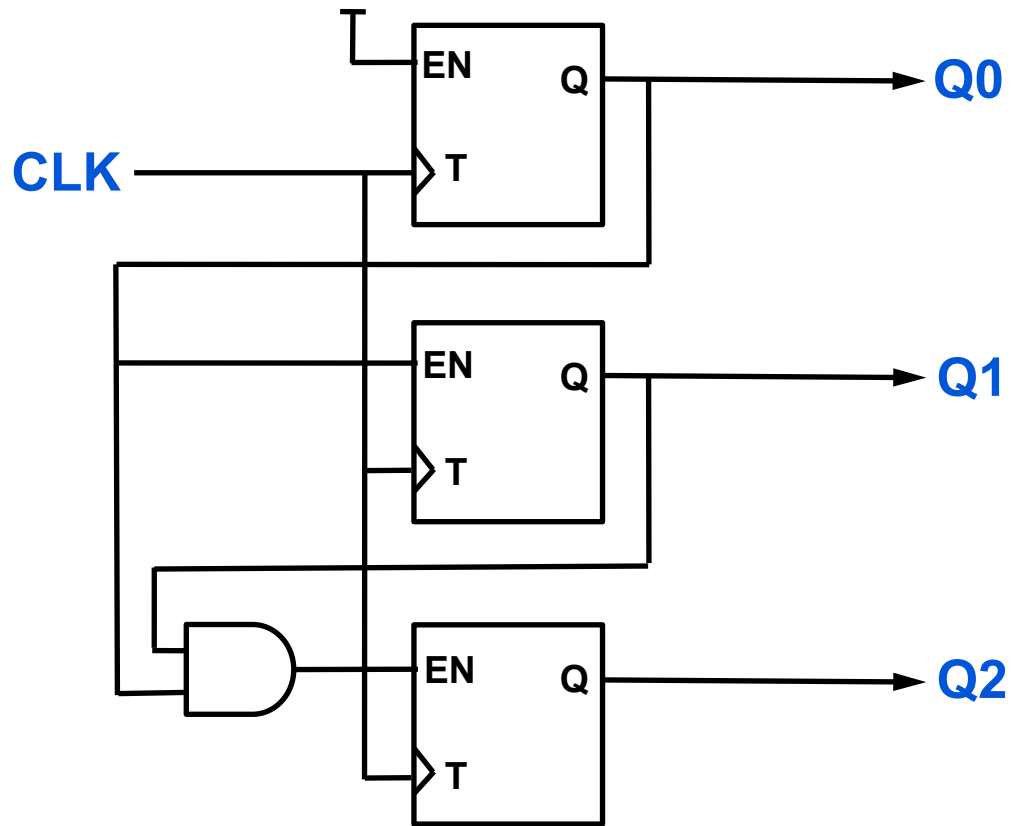

<u>Q<sub>2</sub></u>	<u>Q<sub>1</sub></u>	<u>Q<sub>0</sub></u>
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1
0	0	0
0	0	1

# Binary Up Counter with *Hold*

 


# 4-Bit Binary MSI Counter ('163)

- **Inputs**


- CLK = clock input
- CLR = synchronous clear
- ENT AND ENP = enable counting
- LD = load A,B,C,D (like a register)
- A-D = load inputs

- **Outputs**

 - QA-QD = current number in sequence
- RCO = ripple carry out  
= 1 if QA-QD = 1111, and ENT is 1



# '163 Truth Table

 

Inputs				Current State				Next State			
/CLR	/LD	ENT	ENP	QD	QC	QB	QA	QD*	QC*	QB*	QA*
0	X	X	X	X	X	X	X	0	0	0	0
1	0	X	X	X	X	X	X	D	C	B	A
1	1	0	X	X	X	X	X	QD	QC	QB	QA
1	1	X	0	X	X	X	X	QD	QC	QB	QA
1	1	1	1	0	0	0	0	0	0	0	1
1	1	1	1	0	0	0	1	0	0	1	0
1	1	1	1	0	0	1	0	0	0	1	1
1	1	1	1	0	0	1	1	0	1	0	0
1	1	1	1	0	1	0	0	0	1	0	1
1	1	1	1	0	1	0	1	0	1	1	0
1	1	1	1	0	1	1	0	0	1	1	1
1	1	1	1	0	1	1	1	1	0	0	0
1	1	1	1	1	0	0	0	1	0	0	1
1	1	1	1	1	0	0	1	1	0	1	0
1	1	1	1	1	0	1	0	1	0	1	1
1	1	1	1	1	0	1	1	1	1	0	0
1	1	1	1	1	1	0	0	1	1	0	1
1	1	1	1	1	1	0	1	1	1	1	0
1	1	1	1	1	1	1	0	1	1	1	1
1	1	1	1	1	1	1	1	0	0	0	0

# Before Next Class

- H&H 4.1-4.5 (skip VHDL parts), 5.4

## Next Time

More Counters  
Shift Registers  
Verilog