

ECE 2300

Digital Logic & Computer Organization

Fall 2016

**More Counters
Shift Registers
Verilog**



Cornell University

Lecture 7: 1

Binary Counter

- Counts in binary in a particular sequence
- Advances at every tick of the clock
- Many types

| Up | Down | Free Running | Divide- by-n | n-to-m |
|-------|-------|-----------------|-----------------|--------|
| 0 0 0 | 1 1 1 | 0 0 0 | 0 0 0 | n |
| 0 0 1 | 1 1 0 | 0 0 1 | 0 0 1 | n+1 |
| 0 1 0 | 1 0 1 | 0 1 0 | 0 1 0 | n+2 |
| 0 1 1 | 1 0 0 | 0 1 1 | 0 1 1 | : |
| 1 0 0 | 0 1 1 | 1 0 0 | 1 0 0 | |
| 1 0 1 | 0 1 0 | 1 0 1 | : | m-1 |
| : | : | 1 1 0 | : | m |
| : | : | 1 1 1 | n-1 | n |
| | | 0 0 0 | 0 0 0 | n+1 |
| | | : | 0 0 1 | : |
| | | | : | |


4-Bit Binary MSI Counter ('163)

- **Inputs**


- CLK = clock input
- CLR = synchronous clear
- ENT AND ENP = enable counting
- LD = load A,B,C,D (like a register)
- A-D = load inputs

- **Outputs**

 - QA-QD = current number in sequence
- RCO = ripple carry out
= 1 if QA-QD = 1111, and ENT is 1



'163 Truth Table

 

| Inputs | | | | Current State | | | | Next State | | | |
|--------|-----|-----|-----|---------------|----|----|----|------------|-----|-----|-----|
| /CLR | /LD | ENT | ENP | QD | QC | QB | QA | QD* | QC* | QB* | QA* |
| 0 | X | X | X | X | X | X | X | 0 | 0 | 0 | 0 |
| 1 | 0 | X | X | X | X | X | X | D | C | B | A |
| 1 | 1 | 0 | X | X | X | X | X | QD | QC | QB | QA |
| 1 | 1 | X | 0 | X | X | X | X | QD | QC | QB | QA |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |

Free Running Up Counter

- Always enabled
- Increments every rising clock edge

0 0 0 0

0 0 0 1

0 0 1 0

0 0 1 1

0 1 0 0

0 1 0 1

0 1 1 0


0 1 1 1

1 0 0 0


.

.

.

 

Free Running Counter Timing Diagram

 

Divide-by-11 Counter

- Count sequence

0000

0001

⋮


1001

1010

0000

⋮

 - To divide by 11 (1011), assert clear at 10 (1010)



5-to-15 Counter

- Count sequence

0101

0110

:


1110

1111

0101


:

 - Load 5 (0101) when count reaches 15 (1111)




Cascading Counters

 - Build larger counter from smaller ones
- Next counter enabled when previous = 11...11
- 8-bit cascaded counter




Shift Register

 - Data shifted through a series of D flip-flops
- SERIN appears on SEROUT after n clock ticks
- *Serial-in, serial-out*
- Applications
 - Serial data transmission
 - Computer arithmetic




Serial-In, Parallel-Out Shift Register

 - Data shifted in serially, read out in parallel
- *Serial to parallel conversion*



'194 Shift Register

 

| <i>Function</i> | Inputs | | | Next State | | |
|-----------------|-----------|-----------|------------|------------|------------|------------|
| | <i>S1</i> | <i>S0</i> | <i>QA*</i> | <i>QB*</i> | <i>QC*</i> | <i>QD*</i> |
| Hold | 0 | 0 | QA | QB | QC | QD |
| Shift Right | 0 | 1 | RIN | QA | QB | QC |
| Shift Left | 1 | 0 | QB | QC | QD | LIN |
| Load | 1 | 1 | A | B | C | D |

Ring Counter

- Single 1 shifts through the outputs


| | | | |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| . | . | . | . |

4-bit Ring Counter Using '194

- Load 0001 when RESET asserted
- Then shift left and wrap around

0001
0010
0100
1000
0001


- Wraparound:
Tie QA to LIN

 

Hardware Description Languages (HDLs)

- **Describe hardware behavior**
- **Advantages**
 - Efficiently code large, complex designs
 - Can code at a more abstract level than schematics
 - More understandable than schematics
 - Synthesis tools can automatically generate hardware
- **Typical features**
 - Structure and instantiation
 - Bit-level behavior
 - Concurrency

HDL-based Design Flow

 


- **Back-end differs by target technology**
 - **FPGA, ASIC, full-custom chip**

Verilog

- Developed in the early 1980s by Gateway Design Automation (later bought by Cadence)
- Syntactically similar to C
- Supports modeling, simulation, and synthesis
- We will use a subset of language features
 - Textbook describes additional features that may or may not work with Quartus II


Verilog Program Structure

 - **System is a collection of modules**
 - Module corresponds to a single piece of hardware
- **Declarations**
 - Describe names and types of inputs and outputs
 - Describe local signals, variables, constants, etc.
- **Statements specify what the module does**



Verilog Program Structure

 
```
module V2to4dec(i0,i1,en,y0,y1,y2,y3);
    input i0,i1,en;
    output y0,y1,y2,y3;
    wire noti0,noti1;
    not U1(noti0,i0);
    not U2(noti1,i1);
    and U3(y0,noti0,noti1,en);
    and U4(y1,    i0,noti1,en);
    and U5(y2,noti0,    i1,en);
    and U6(y3,    i0,    i1,en);
endmodule
```



The code is divided into two main sections by blue curly braces:

- Declarations:** This section contains the module header, input and output port declarations, and a wire declaration.
- Statements:** This section contains the logic assignments (U1 through U6) and the endmodule keyword.

Verilog Hierarchy

 

Signal Values

- **Verilog signals can take 4 values**
 - 0 Logical 0, or false
 - 1 Logical 1, or true
 - x Unknown logical value
 - z High impedance (Hi-Z)

Vectors

- **Grouping of 1-bit signals**
 - `reg[7:0] byte1, byte2, byte3;`
 - `wire[0:3] asel;`
 - **Right-most bit is always least significant**
- **Bit selection**
 - `byte1[5:2]`
- **Concatenation**
 - `{byte1,byte2}`
- **Bitwise Boolean operators**
 - `byte1 & byte2`
- **Literals**
 - `8'b11011`

Arithmetic and Shift Operators

- **Arithmetic**
 - + Addition
 - Subtraction
 - * Multiplication
 - / Division
 - % Modulus
- **Shift**
 - << Shift left
 - >> Shift right

Bitwise Boolean Operators

- **Bitwise Boolean Operators**

~ NOT

& AND

| OR

^ Exclusive OR

^~ Exclusive NOR

Variables

- **Store values during program execution, but may not have physical significance**
- **Common types are reg, logic, and integer**
 - **reg: single bit or vector of bits**
 - **logic: introduced as alternative to reg in SystemVerilog**
 - **integer: integer value**
- **Only used in *procedural code***
 - **Cannot be changed from outside the procedure**

Procedural Statements

- Procedural statements are similar to conventional programming language statements
 - Begin-end blocks
 - `begin procedural-statement ... procedural-statement end`
 - If
 - `if (condition) procedural-statement else procedural-statement`
 - Case
 - `case (sel-expr) choice : procedural-statement ... endcase`
 - While
 - `while (logical-expression) procedural-statement`
 - Repeat
 - `Repeat (integer-expression) procedural-statement`

Conditionals

- Logical operators used in conditional expressions

`&&` logical AND

`||` OR

`!` logical NOT

`==` logical equality

`!=` logical inequality

`>` greater than

`>=` greater than or equal

`<` less than

`<=` less than or equal

- Don't confuse with Boolean operators

Nets

- A *net* provides connectivity between elements
- Default net type is a *wire*
 - wire noti0, noti1;
 - Any signal not in the input/output list or net declaration is assumed to be a wire
- Other net types
 - tri, wand, wor, ...
 - Only wire and tri supported by Quartus II

Verilog programming styles


- **Structural**
 - Textual equivalent of drawing a schematic
 - Uses *instance* statements
- **Dataflow**
 - Describes circuit in terms of flow of data and operations on that data
 - Uses *continuous-assignment* statements
 - Called “structural” in textbook
- **Behavioral**
 - High-level algorithmic description
 - Uses *procedural code*

Structural Style

```
module V2to4dec_struct( i0,i1,en,y0,y1,y2,y3 );
    input i0,i1,en;
    output y0,y1,y2,y3;
    wire noti0,noti1;

    not U1(noti0,i0);
    not U2(noti1,i1);
    and U3(y0,noti0,noti1,en);
    and U4(y1,  i0,noti1,en);
    and U5(y2,noti0,  i1,en);
    and U6(y3,  i0,  i1,en);
endmodule
```

Correspondence
with schematic

 

Dataflow Style

```
module V2to4dec_df( i0,i1,en,y0,y1,y2,y3 );
    input i0,i1,en;
    output y0,y1,y2,y3;
    assign y0 = en & ~i0 & ~i1;
    assign y1 = en & i0 & ~i1;
    assign y2 = en & ~i0 & i1;
    assign y3 = en & i0 & i1;
endmodule
```

Correspondence
with Boolean logic

New value is assigned to
the lhs whenever any value
on the rhs changes

Behavioral Style

```
module V2to4dec_beh( i0,i1,en,y0,y1,y2,y3 );
    input i0,i1,en;
    output y0,y1,y2,y3;
    reg y0,y1,y2,y3;

    always @ (en or i0 or i1)
    begin
        y0 = en & ~i0 & ~i1;
        y1 = en & i0 & ~i1;
        y2 = en & ~i0 & i1;
        y3 = en & i0 & i1;
    end
endmodule
```

- **Procedural code**
- **Key element is the *always block***
- **Begin-end block groups sequences of procedural statements**
- **reg needed to change the output values**

Before Next Class

- H&H 3.4, 4.6, 4.9

Next Time

More Verilog
Finite State Machines