

ECE 2300
Digital Logic & Computer Organization
Fall 2016

More Verilog
Finite State Machines



Cornell University


Verilog Programming Styles

- **Structural**
 - Textual equivalent of drawing a schematic
 - Uses *instance* statements
- **Dataflow**
 - Describes circuit in terms of flow of data and operations on that data
 - Uses *continuous-assignment* statements
 - Called “structural” in textbook
- **Behavioral**
 - High-level algorithmic description
 - Uses *procedural code*

Structural Style

```
module V2to4dec_struct( i0,i1,en,y0,y1,y2,y3 );  
  input i0,i1,en;  
  output y0,y1,y2,y3;  
  wire noti0,noti1;  
  
  not U1(noti0,i0);  
  not U2(noti1,i1);  
  and U3(y0,noti0,noti1,en);  
  and U4(y1,  i0,noti1,en);  
  and U5(y2,noti0,  i1,en);  
  and U6(y3,  i0,  i1,en);  
endmodule
```

Correspondence with schematic

 

Dataflow Style

```
module V2to4dec_df( i0,i1,en,y0,y1,y2,y3 );  
  input i0,i1,en;  
  output y0,y1,y2,y3;  
  
  assign y0 = en & ~i0 & ~i1;  
  assign y1 = en & i0 & ~i1;  
  assign y2 = en & ~i0 & i1;  
  assign y3 = en & i0 & i1;  
endmodule
```

**Correspondence
with Boolean logic**

**Only used for
combination logic**

**New value is assigned to
the lhs whenever any value
on the rhs changes**

Behavioral Style

```
module V2to4dec_beh( i0,i1,en,y0,y1,y2,y3 );
```

```
  input i0,i1,en;
```

```
  output reg y0,y1,y2,y3;
```

```
  always @ (en, i0, i1)
```

```
  begin
```

```
    y0 = en & ~i0 & ~i1;
```

```
    y1 = en & i0 & ~i1;
```

```
    y2 = en & ~i0 & i1;
```

```
    y3 = en & i0 & i1;
```

```
  end
```

```
endmodule
```

- **Procedural code**
- **Key element is the *always block***
- **Can be used for both combinational and sequential logic**
- **reg needed for variables on lhs of procedure statements**

Always Blocks


- *Always* block starts execution when the value of any signal in the *sensitivity list* changes
- Execution continues until there are no more changes in sensitivity list
- *Always* blocks execute concurrently with other *always* blocks, instance statements, and continuous assignment statements in a module

Sequential Logic Using Always Blocks


- Sequential logic can only be modeled using always blocks

```
reg q1, q2;
```
 
```
always @( clk, d )  
begin  
  if ( clk )  
    q1 <= d;  
end
```


 
```
always @( posedge clk )  
begin  
  q2 <= d;  
end
```



Blocking and Nonblocking Assignments

- **Blocking statement**

- $A = B \& C;$
- Assignment is immediate

- **Nonblocking statement**

- $A <= B \& C;$
- Assignment is delayed until end of *always* block

```
always
begin
  A = B & C;
  D = ~A;
end
```

$A = B \& C$
 $D = \sim(B \& C)$

```
always
begin
  A <= B & C;
  D <= ~A;
end
```

$A = B \& C$ $D = \sim A$

General Guidelines

- **Use blocking (=) assignments in *always* blocks intended as combinational logic**
- **Use nonblocking (<=) assignments in *always* blocks intended as sequential logic**
- **Do not mix blocking and nonblocking assignments in the same *always* block**
- **Do not make assignments to the same variable in two different *always* blocks**

Inferred Latches In Comb Logic


- Each variable within an *always* block should get assigned a value under all possible conditions
 - Otherwise, the compiler assumes that the last value should be used, and will create a latch

```
reg dout;
always @(din, c)
begin
  /* dout not always assigned
     a value; latch inferred */
  if (c == 1'b1)
    dout = din;
end
```

```
reg dout;
always @(din, c)
begin
  /* dout assigned a value in both
     conditions, latch not inferred */
  if (c == 1'b1)
    dout = din;
  else
    dout = ~din;
end
```

Verilog Code for '163 Counter


```
module counter (CLK, CLR_L, LD_L, ENP, ENT, D, Q, RC0);  
  input CLK, CLR_L, LD_L, ENP, ENT;  
  input [3:0] D;  
  output reg [3:0] Q;  
  output reg RC0;  
  
  always @ (posedge CLK)  
    if (CLR_L ==0)                Q <= 4'b0;  
    else if (LD_L == 0)           Q <= D;  
    else if ((ENT ==1) && (ENP ==1)) Q <= Q+1;  
    else                           Q <= Q;  
  
  always @ (Q, ENT)  
    if ((ENT == 1) && (Q == 4'd15)) RC0 = 1;  
    else                             RC0 = 0;  
endmodule
```

 

Sequential Logic

- **Many logic functions require information about the past in addition to the current inputs**
 - **Vending machine controller**
 - **Traffic light system**
 - **Microprocessor control unit**
- **Such *sequential logic circuits* are implemented using combinational logic and storage**
- **One important sequential logic circuit is a *Finite State Machine (FSM)***


Finite State Machine

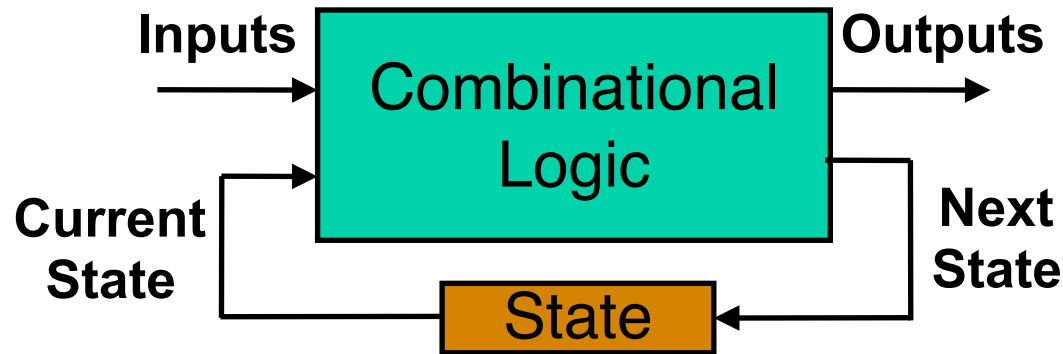

- The state embodies the condition of the system at this particular time
- The combinational logic determines the output and next state values
- The output values may depend only on the current state value, or on the current state and input values

Elements of a FSM

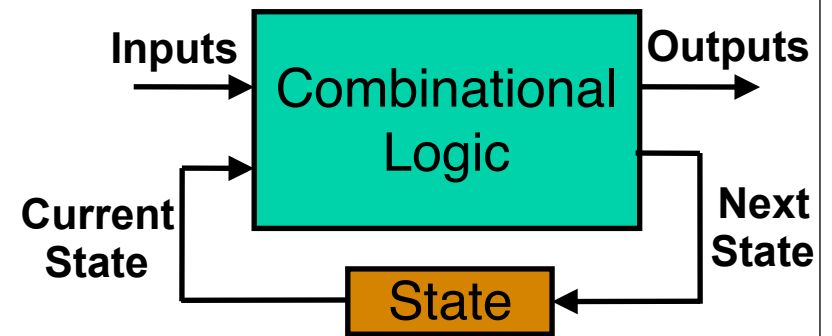
1. A finite number of states
2. A finite number of inputs
3. A finite number of outputs
4. A specification of all state transitions
5. A specification of the output values



Described by a state diagram


- Inputs and current state trigger state transitions
- Output changes triggered by changes in
 - Current state, or
 - Current state + inputs

FSM: General Form

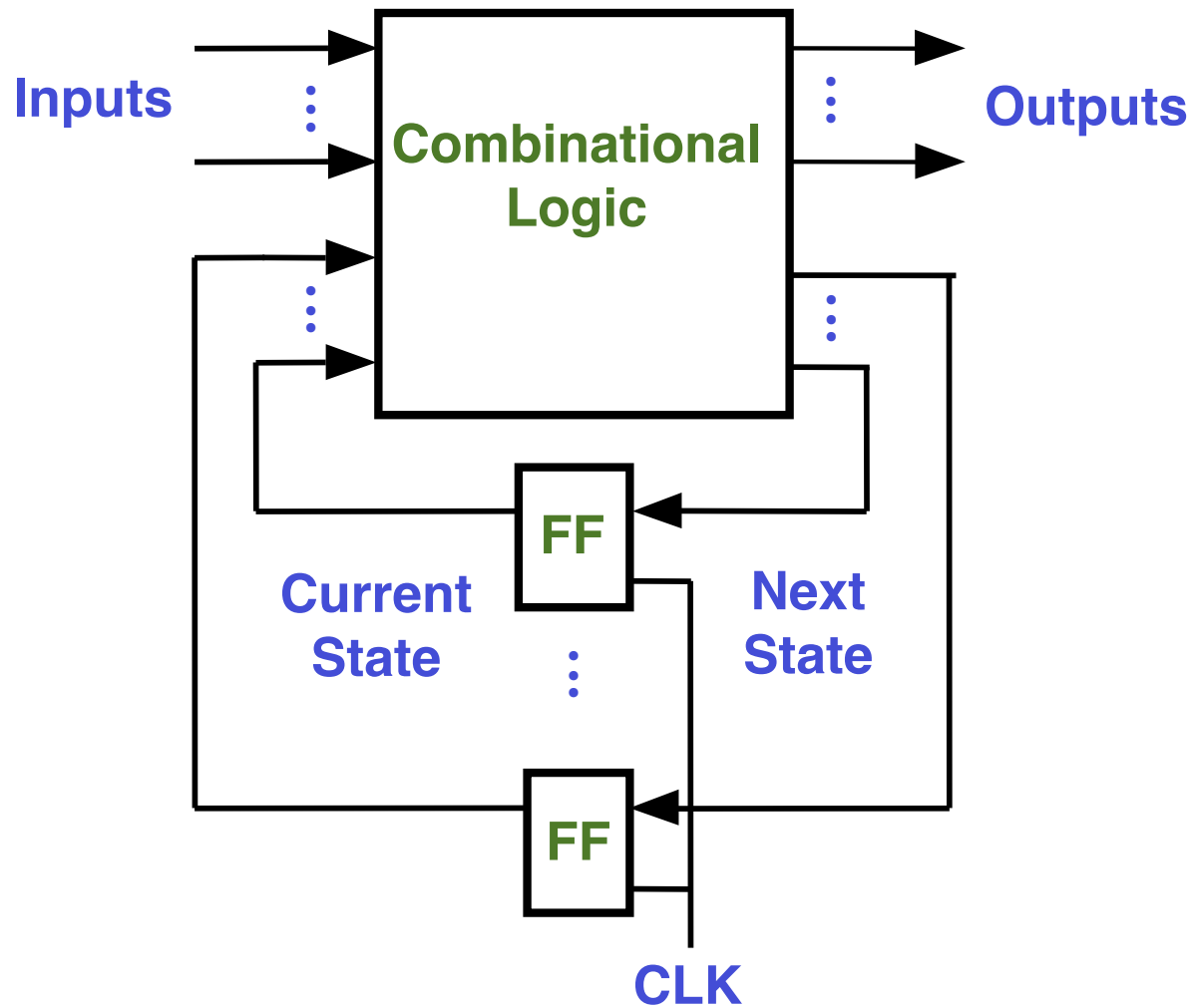


Moore Machine

Outputs depend on current state value

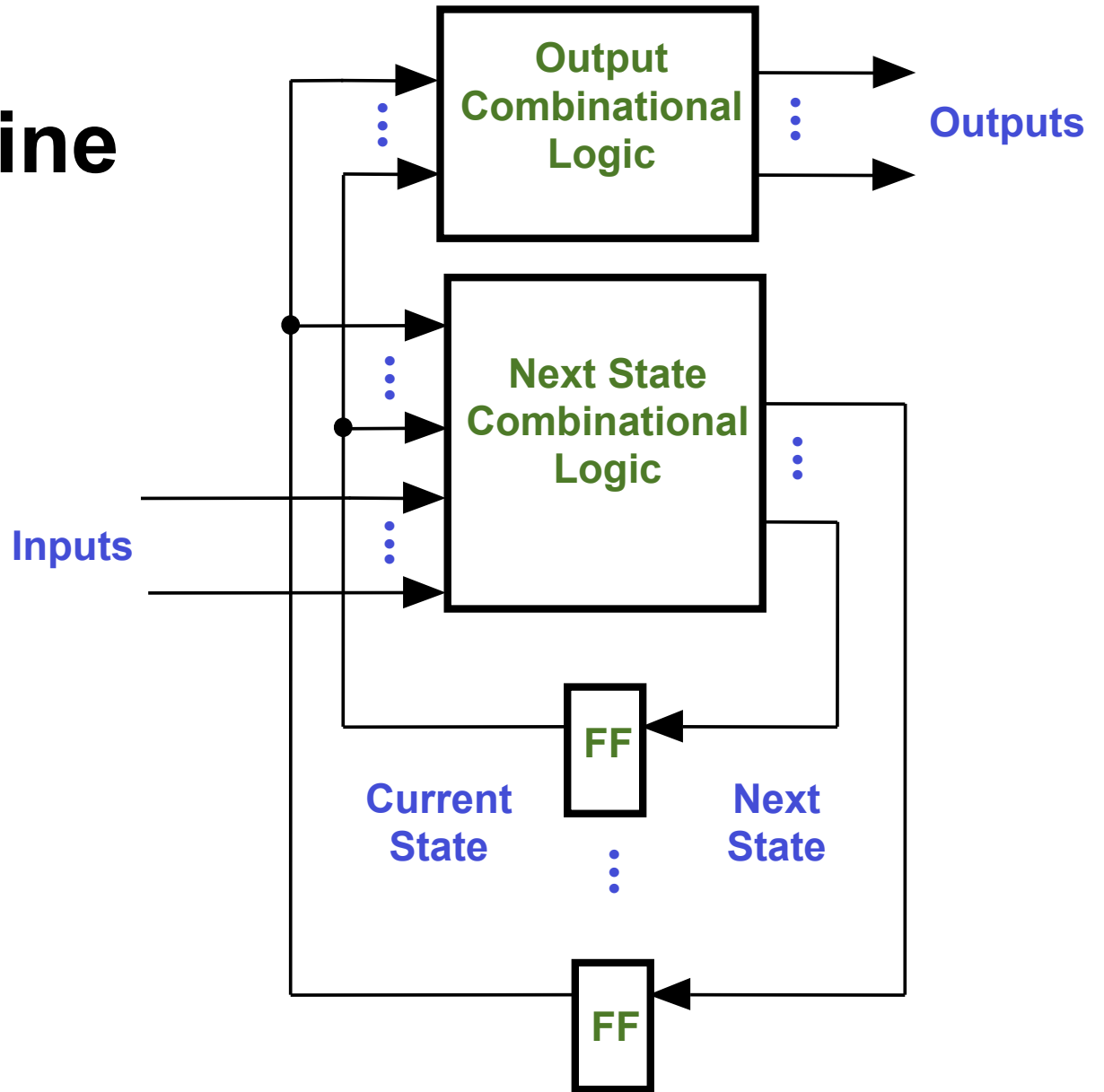

Mealy Machine

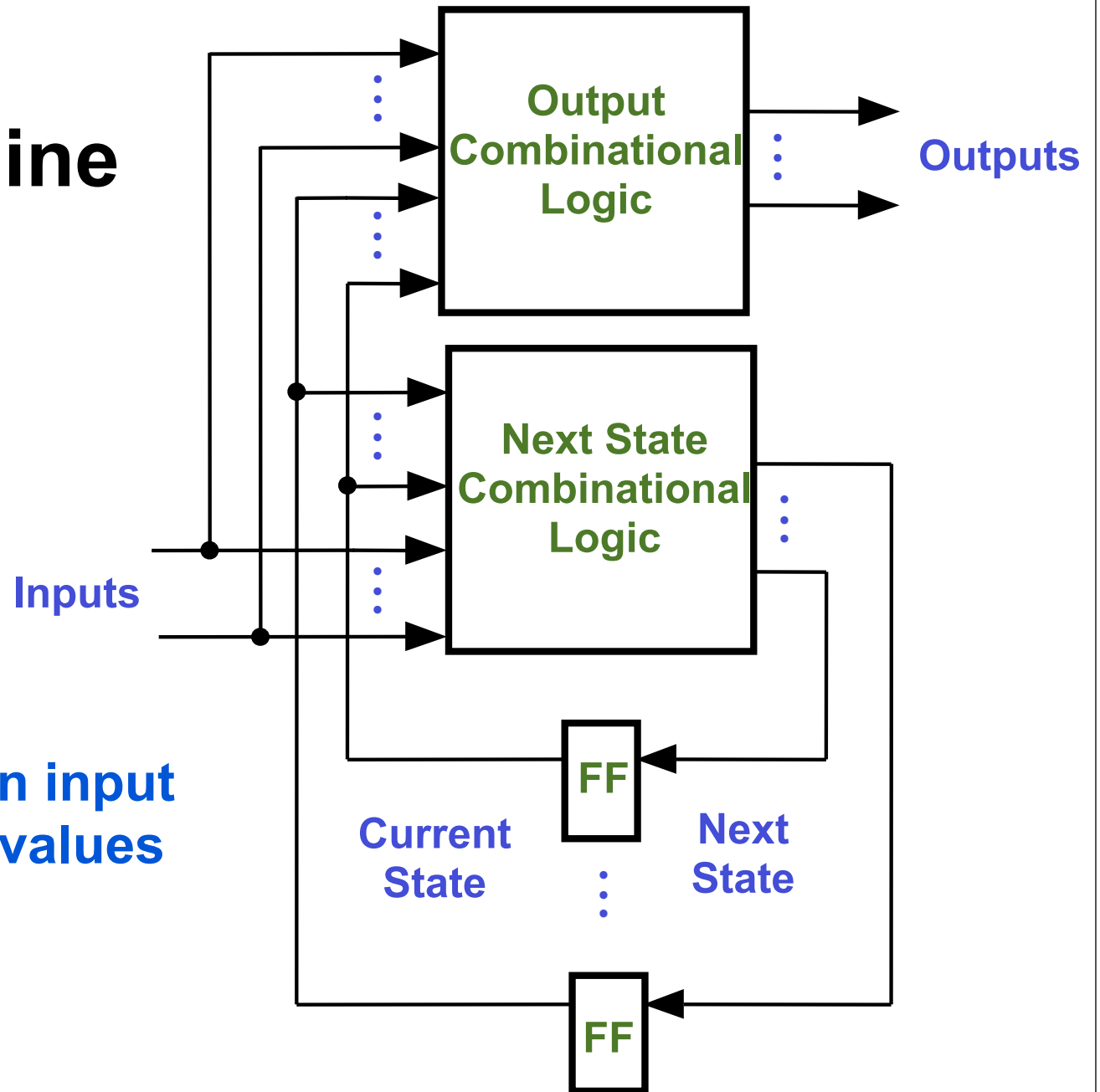

Outputs depend on input and current state values

FSM Design Procedure


- (1) Understand the problem statement and determine inputs and outputs**
- (2) Identify states and create a *state diagram***
- (3) Determine the number of required D FFs**
- (4) Implement combinational logic for outputs and next state**
- (5) Simulate the circuit to test its operation**

State Diagram

- **Visual specification of a FSM**
- **Bubble for every state**
- **Arcs showing state transitions**
- **Input values shown on the arcs**
- **Output values shown within the bubbles (Moore) or on the arcs (Mealy)**
- **Clock input not shown (always present)**

Moore State Diagram


Moore FSM

 

- 1 input, 1 output, 3 states
- Bubble for each state
- State transitions (arcs) for each input value
- Input values on the arcs
- Output values within the bubbles
- Starts at S0 when Reset asserted

Mealy State Diagram

Mealy FSM

 

- 1 input, 1 output, 2 states
- Bubble for each state
- State transitions (arcs) for each input value
- Input values on the arcs (first number)
- Output values on the arcs (second number)
- Starts at S0 when Reset asserted

Example FSM: Pattern Detector

- Monitors the input, and outputs a 1 whenever a specified input pattern is detected
- Example: Output a 1 whenever 111 is detected on the input for 3 consecutive clock cycles
 - Overlapping patterns also detected (1111...)
- Input *In*
- Output *Out*
- *Reset* causes FSM to start in initial state
- *Clock* input not shown (always present)

111 Pattern Detector: Moore State Diagram

111 Pattern Detector: Mealy State Diagram

Example FSM: Pushbutton Lock

- Two pushbutton inputs, X1 and X2
- One output, UL (“Unlock”)
- $UL = 1$ when X1 is pushed, followed by X2 being pushed twice (X1, X2, X2)
- Represent X1 and X2 as two bit input
 - 00: neither button pushed
 - 01: X2 pushed
 - 10: X1 pushed
 - 11: both pushed simultaneously

Pushbutton Lock: Moore State Diagram

Pushbutton Lock: Mealy State Diagram

Next Time

More Finite State Machines