

ECE 2300
Digital Logic & Computer Organization
Fall 2016


More Finite State Machines



Cornell University


Lecture 9: 1

FSM: General Form

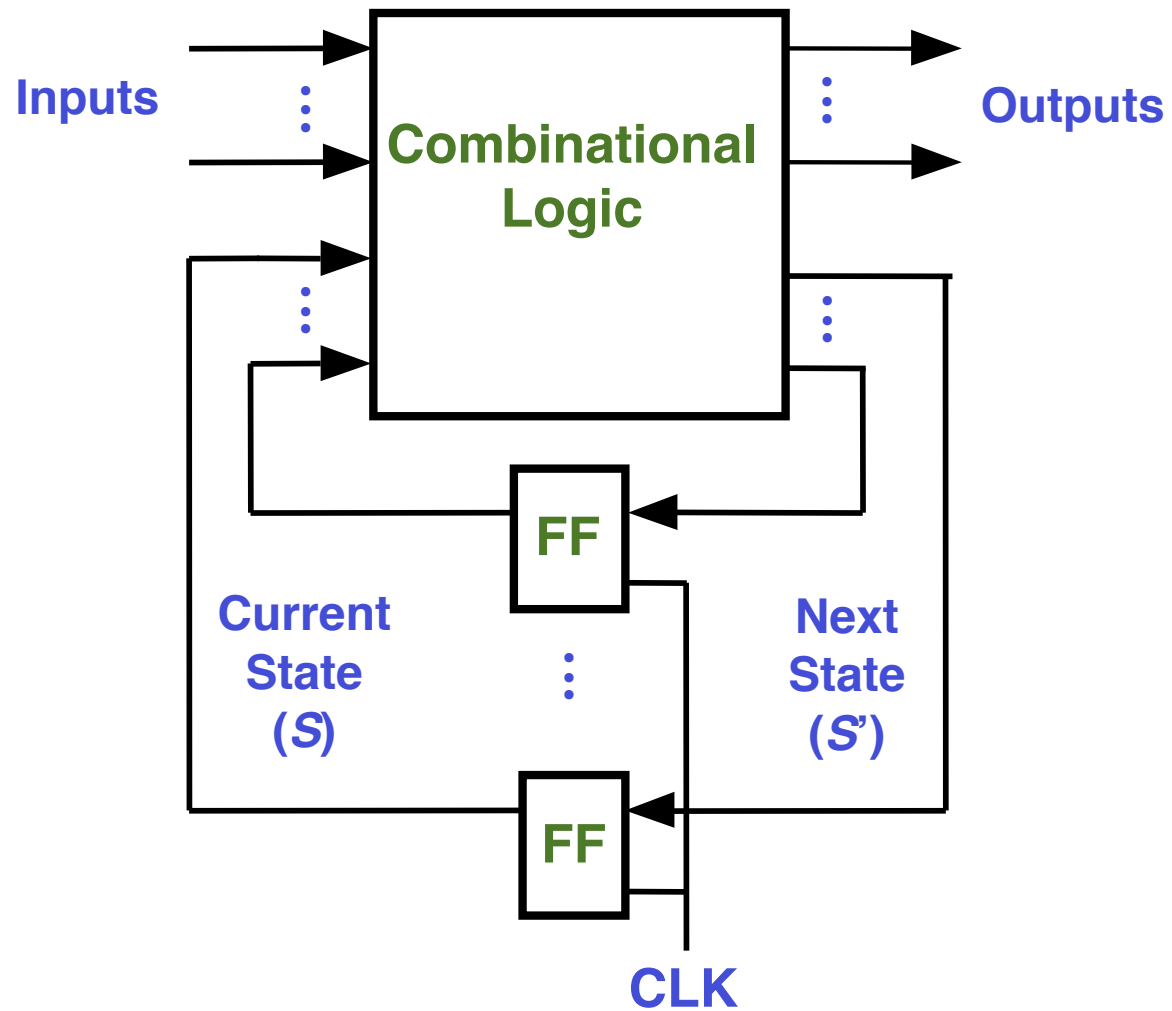


Moore Machine

Outputs depend on current state value

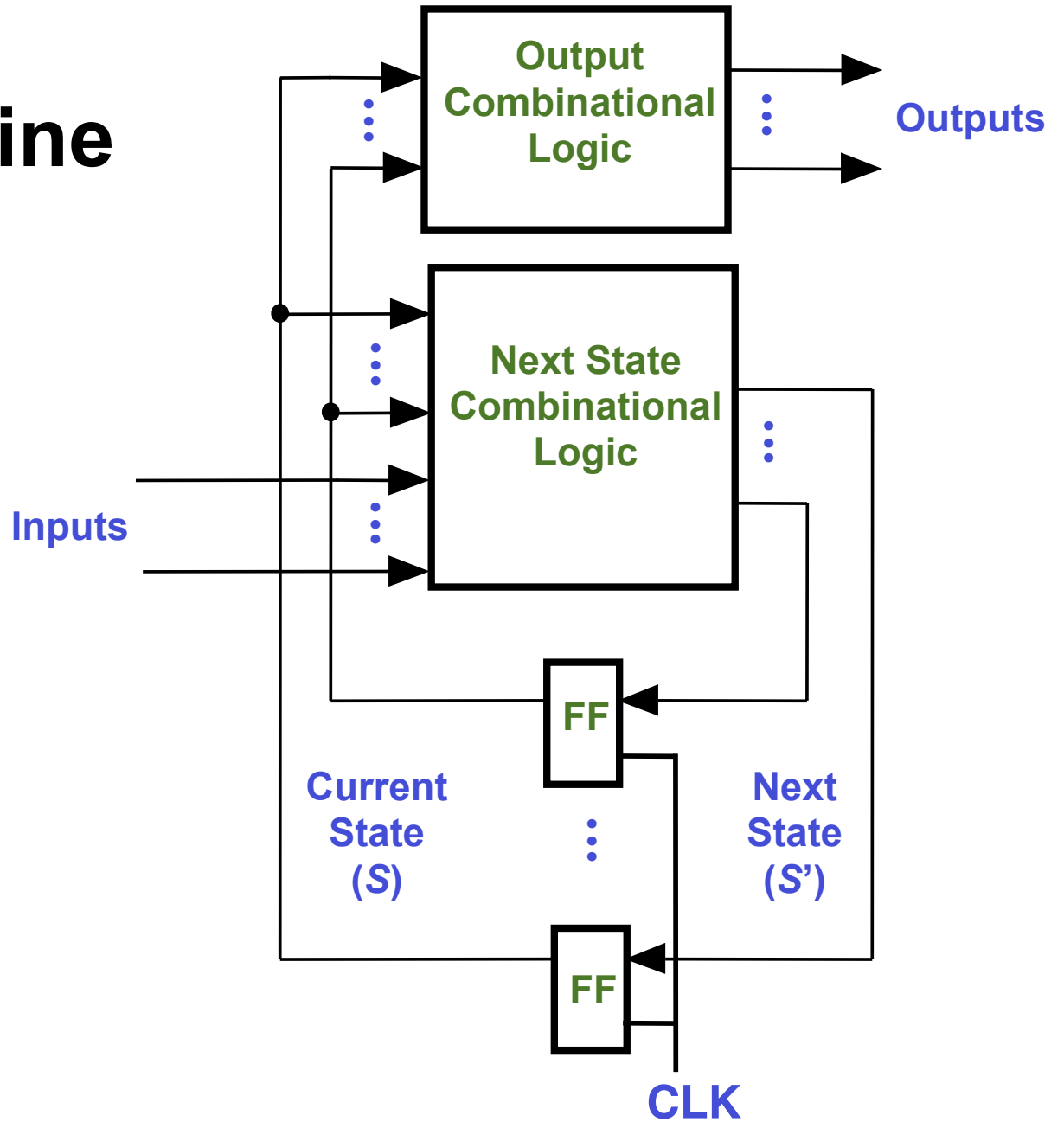

Mealy Machine

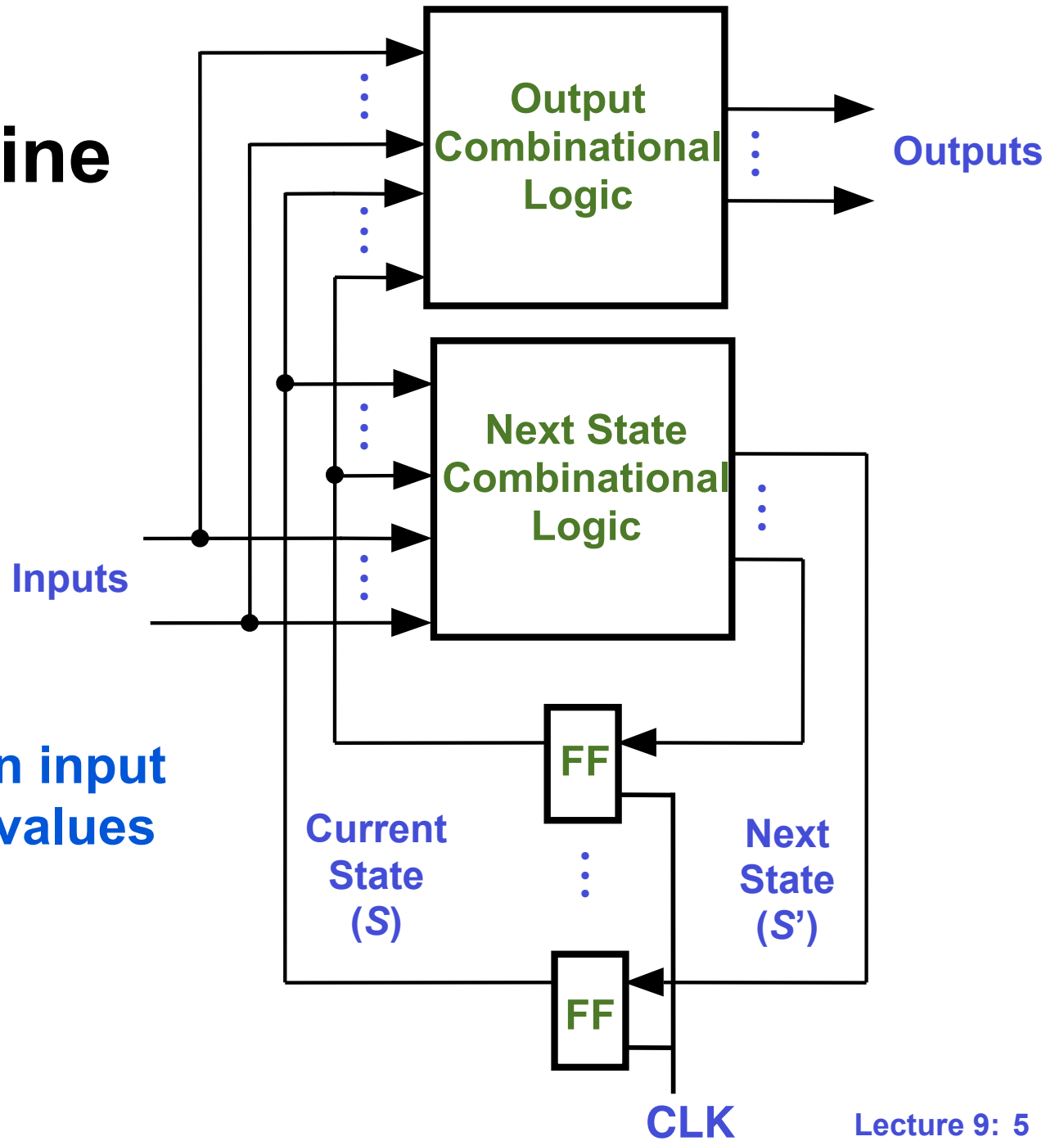Outputs depend on input and current state values



Example FSM: Pattern Detector

- Monitors the input, and outputs a 1 whenever a specified input pattern is detected
- Example: Output a 1 whenever 111 is detected on the input for 3 consecutive clock cycles
 - Overlapping patterns also detected (1111...)
- Input *In*
- Output *Out*
- *Reset* causes FSM to start in initial state
- *Clock* input not shown (always present)

111 Pattern Detector Timing


FSM Design Procedure

- (1) Understand the problem statement and determine inputs and outputs**
- (2) Identify states and create a *state diagram***
- (3) Determine the number of required D FFs**
- (4) Implement combinational logic for outputs and next state**
- (5) Simulate the circuit to test its operation**

Transition/Output Table


- Shows the next state (S') and output values for each combination of current state (S) and inputs
- Used to derive the minimized *state transition* (S') and *output* Boolean equations
- Version 1: uses descriptive state names
- Version 2: uses state binary encodings
- Text shows different type of T/O table

Moore Transition/Output Table 1

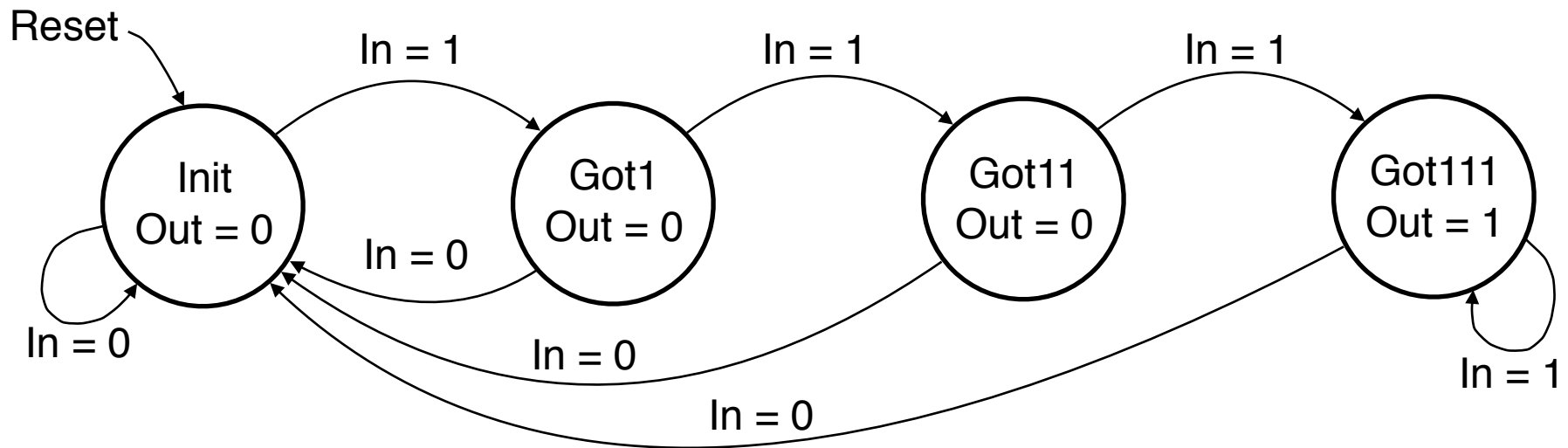

Current State (S)	Next State (S')		Out
	In = 0	In = 1	
Init	Init	Got1	0
Got1	Init	Got11	0
Got11	Init	Got111	0
Got111	Init	Got111	1

Moore Transition/Output Table 2

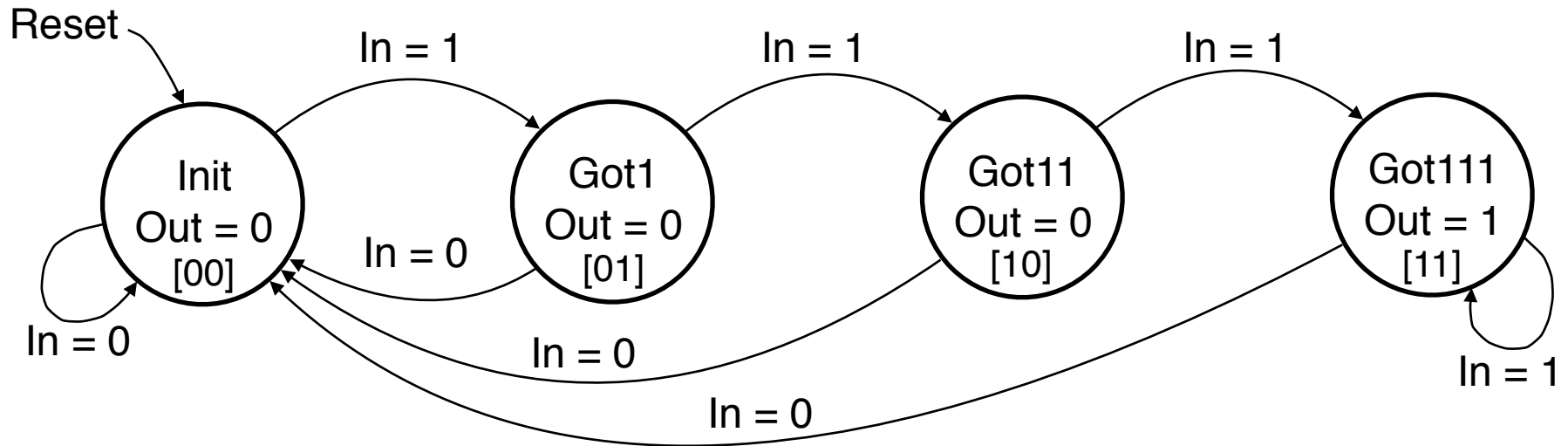


$S_1 S_0$	$S_1' S_0'$		Out
	In = 0	In = 1	
0 0	0 0	0 1	0
0 1	0 0	1 0	0
1 0	0 0	1 1	0
1 1	0 0	1 1	1

Minimized Equations for S' and Out


$S_1 S_0$	$S_1' S_0'$		Out
	In = 0	In = 1	
0 0	0 0	0 1	0
0 1	0 0	1 0	0
1 0	0 0	1 1	0
1 1	0 0	1 1	1

Mealy Transition/Output Table 1

 

Current State (S)	Next State (S'), Out	
	In = 0	In = 1
Init	Init, 0	Got1, 0
Got1	Init, 0	Got11, 0
Got11	Init, 0	Got11, 1

Mealy Transition/Output Table 2

 

$S_1 S_0$	$S_1' S_0', Out$	
	In = 0	In = 1
0 0	0 0, 0	0 1, 0
0 1	0 0, 0	1 0, 0
1 0	0 0, 0	1 0, 1


Minimized Equations for S' and Out

$S_1 S_0$	$S_1' S_0', Out$	
	$In = 0$	$In = 1$
0 0	0 0, 0	0 1, 0
0 1	0 0, 0	1 0, 0
1 0	0 0, 0	1 0, 1

FSMs in Verilog

```
<module statement>  
<input and output declarations>  
  
<reg declarations>  
  
<parameter or typedef statement>  
  
<always block for next state>  
  
<always block for output>  
  
<always block for state D FFs>  
  
endmodule
```

Moore FSM in Verilog

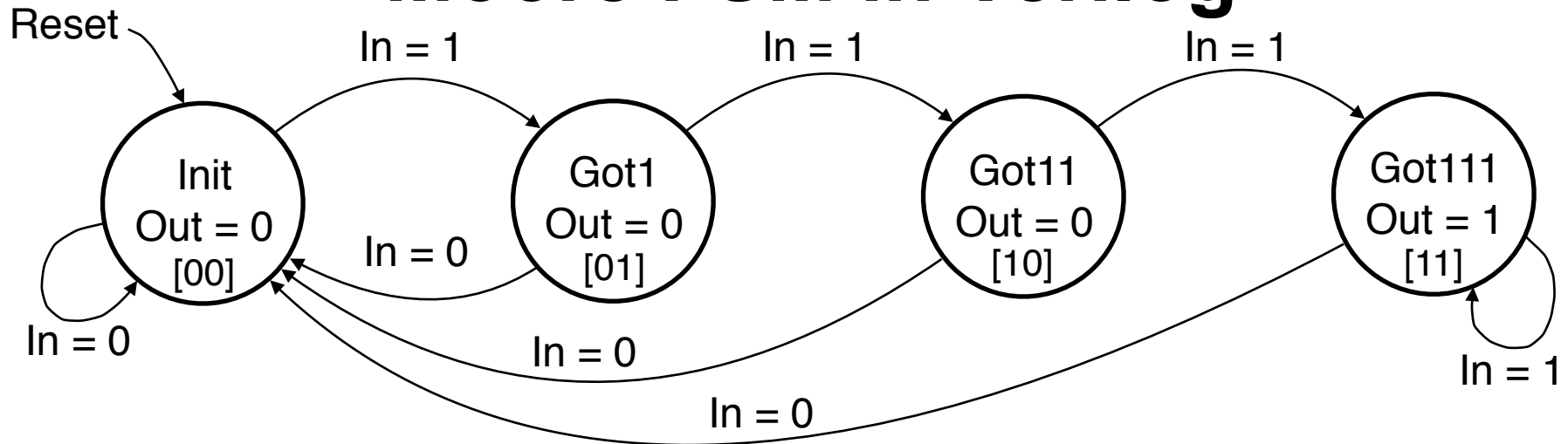


```
module PatDectMoore (Clk, In, Reset, Out);  
input Clk, In, Reset;  
output Out;
```

```
reg Out;  
reg [1:0] Scurr, Snext;
```

```
parameter [1:0] Init = 2'b00,  
               Got1 = 2'b01,  
               Got11 = 2'b10,  
               Got111 = 2'b11;
```


Moore FSM in Verilog

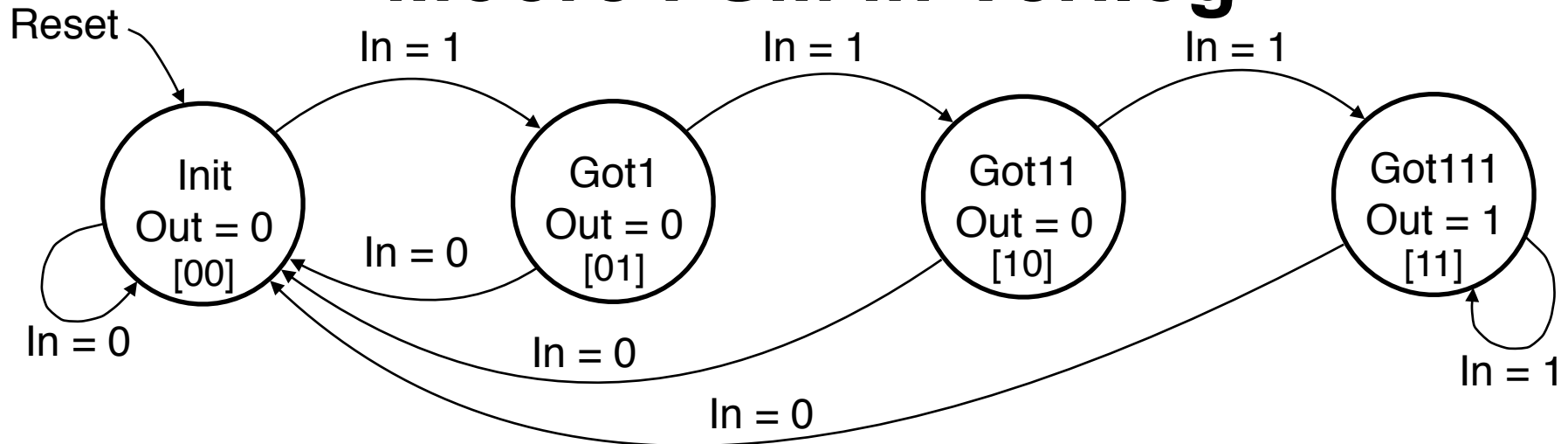

always @ (In, Scurr)

begin

case (Scurr)

Init: if (In == 1) Snext = Got1; else Snext = Init;

Got1: if (In == 1) Snext = Got11; else Snext = Init;

Got11: if (In == 1) Snext = Got111; else Snext = Init;

Got111: if (In == 1) Snext = Got111; else Snext = Init;


default: Snext = Init;

endcase

end

**next state
comb logic**

Moore FSM in Verilog

 

```
always @ (Scurr)
```

```
if (Scurr == Got111) Out = 1; else Out = 0;
```

output comb logic


```
always @ (posedge Clk, posedge Reset)
```

```
if (Reset == 1) Scurr <= Init; else Scurr <= Snext;
```

clock + async reset
state D FFs

```
endmodule
```

Mealy FSM in Verilog

 


```
module PatDectMealy (Clk, In, Reset, Out);  
input Clk, In, Reset;  
output Out;
```

```
reg Out;  
reg [1:0] Scurr, Snext;
```

```
parameter [1:0] Init = 2'b00,  
                Got1 = 2'b01,  
                Got11 = 2'b10;
```

Mealy FSM in Verilog

 

```
always @ (In, Scurr)
```

```
begin
```

```
  case (Scurr)
```

```
    Init: if (In == 1) Snext = Got1; else Snext = Init;
```

```
    Got1: if (In == 1) Snext = Got11; else Snext = Init;
```

```
    Got11: if (In == 1) Snext = Got11; else Snext = Init;
```


```
    default: Snext = Init;
```

```
  endcase
```

```
end
```

**next state
comb logic**

Mealy FSM in Verilog

 

```
always @ (Scurr, In)
```

```
if ((Scurr == Got11) && (In == 1)) Out = 1; else Out = 0;
```

output comb logic

```
always @ (posedge Clk, posedge Reset)
```

```
if (Reset == 1) Scurr <= Init; else Scurr <= Snext;
```


clock + async reset
state D FFs

```
endmodule
```

Example FSM: Pushbutton Lock

- Two pushbutton inputs, X1 and X2
- One output, UL (“Unlock”)
- UL = 1 when X1 is pushed, followed by X2 being pushed twice (X1, X2, X2)
- Represent X1 and X2 as two bit input
 - 00: neither button pushed
 - 01: X2 pushed
 - 10: X1 pushed
 - 11: both pushed simultaneously

Pushbutton Lock: Moore State Diagram

 

Transition/Output Tables

Minimized Equations for S' and UL

Next State *always* Block

Output *always* Block

State FFs *always* Block

Next Time

Factoring FSMs
Analyzing FSMs