

ECE 2300
Digital Logic & Computer Organization
Fall 2016

Hazards, Timing, Clocking




Cornell University

Lecture 11: 1

Propagation Delay

 
- Time for change in input to change the output
- Typically specified between 50% points





- Circuits have *minimum* and *maximum* propagation delays
 - Minimum sometimes called the *contamination delay* and maximum the *propagation delay*

Timing Diagram

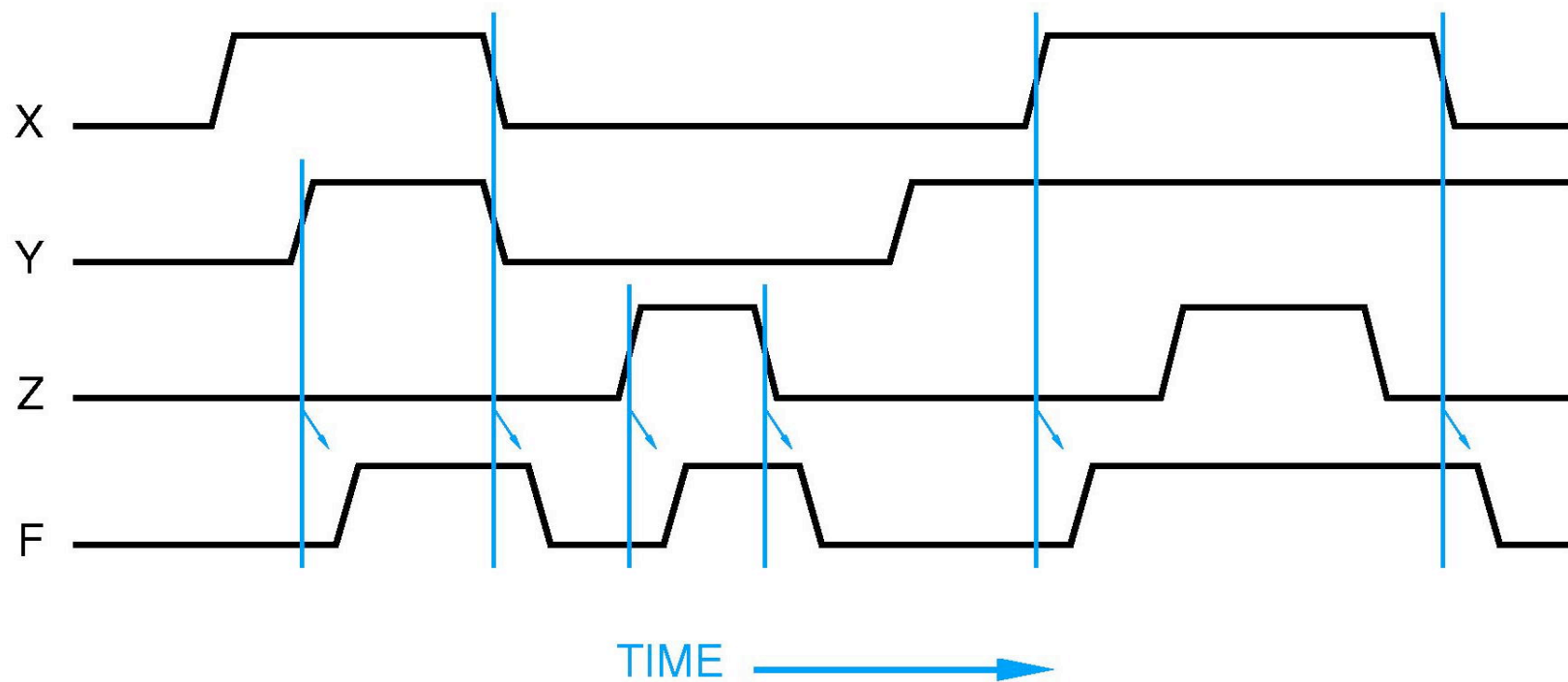- Shows how outputs respond to changes in inputs over time



Timing Diagram

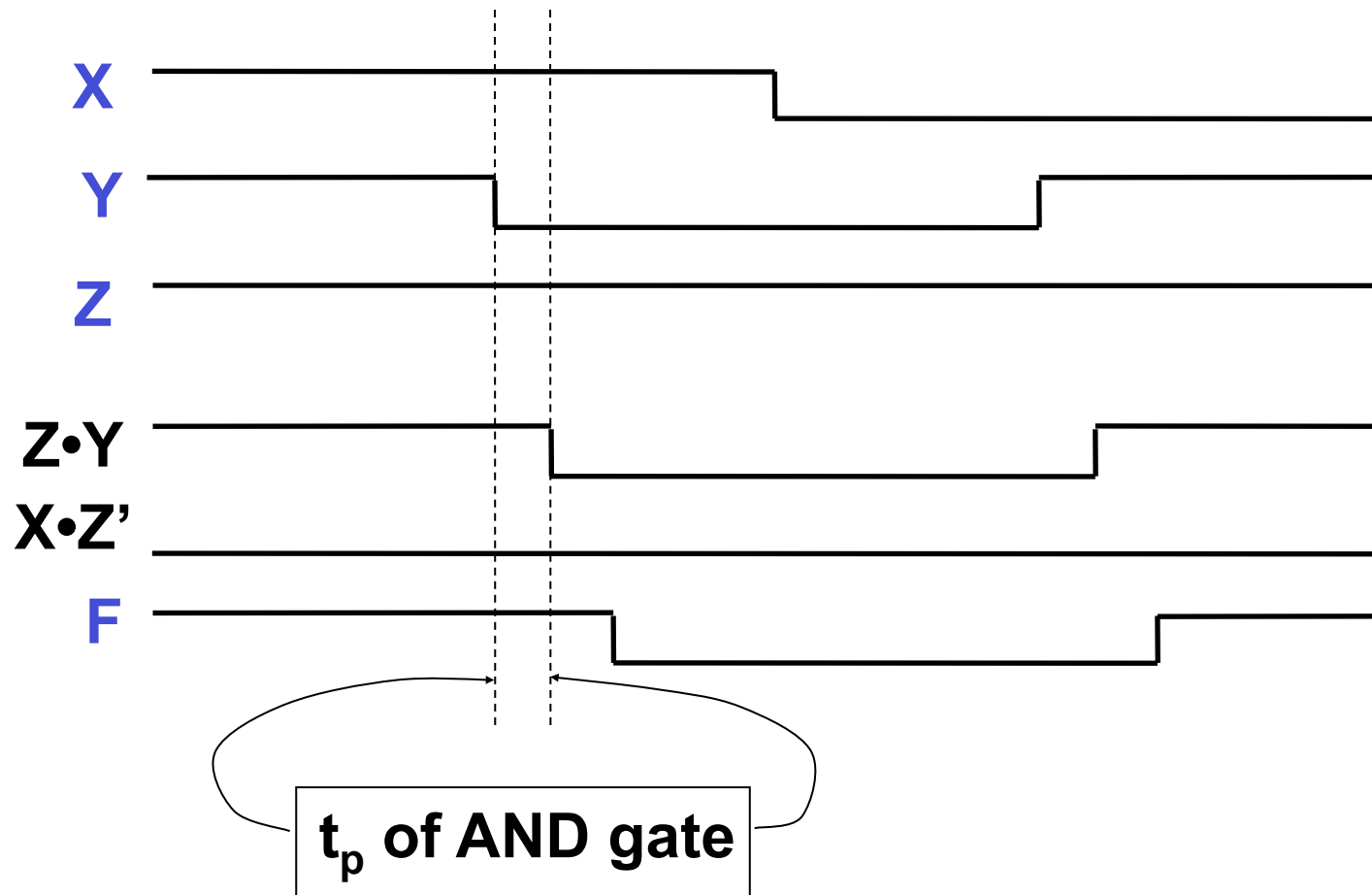 


Hazard (*Glitch*)

- Unplanned momentary switching of an output
- Occurs when different paths through circuit have different propagation delays

Types of Hazards


- **Static 1-hazard**

 - Input change causes output to go from 1 to 0 to 1 (should have stayed 1)





- **Static 0-hazard**

 - Input change causes output to go from 0 to 1 to 0 (should have stayed 0)




- **Dynamic hazards**

  - Input change causes a change from 0 to 1 to 0 to 1 or from 1 to 0 to 1 to 0 (there should be just one change)




Static 1 Hazards

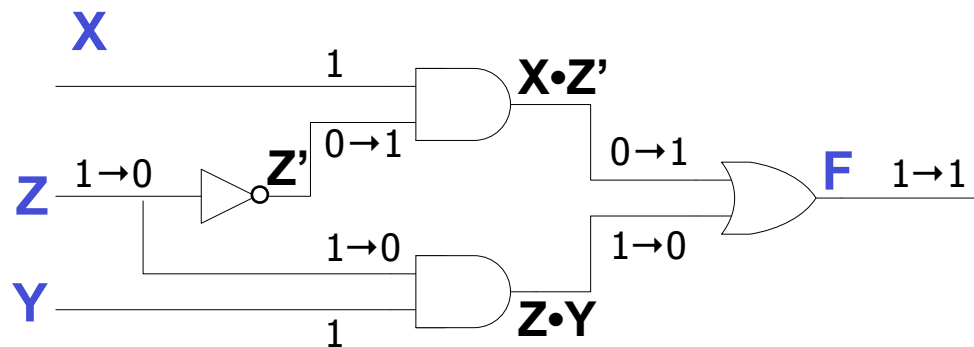- Glitches due to unequal signal propagation delays through the circuit
- Output signal should stay at 1, but shows a transient 0 value



Assume X and Y are 1
Z changes from 1 to 0

Timing Diagram Showing Glitch

 

glitch

Eliminating Static 1 Hazards

- Identify prime implicants that are not overlapping in Karnaugh map
- Include consensus terms to cover transitions between product terms

Hazard Detection and Elimination



$$F = X \cdot Z' + Y \cdot Z$$

$$F = X \cdot Z' + Y \cdot Z + X \cdot Y$$

Z \ XY	00	01	11	10
0	0	0	1	1
1	0	1	1	0


Adding a consensus term

Glitch-free Design Timing Diagram

  

Do Glitches Matter?


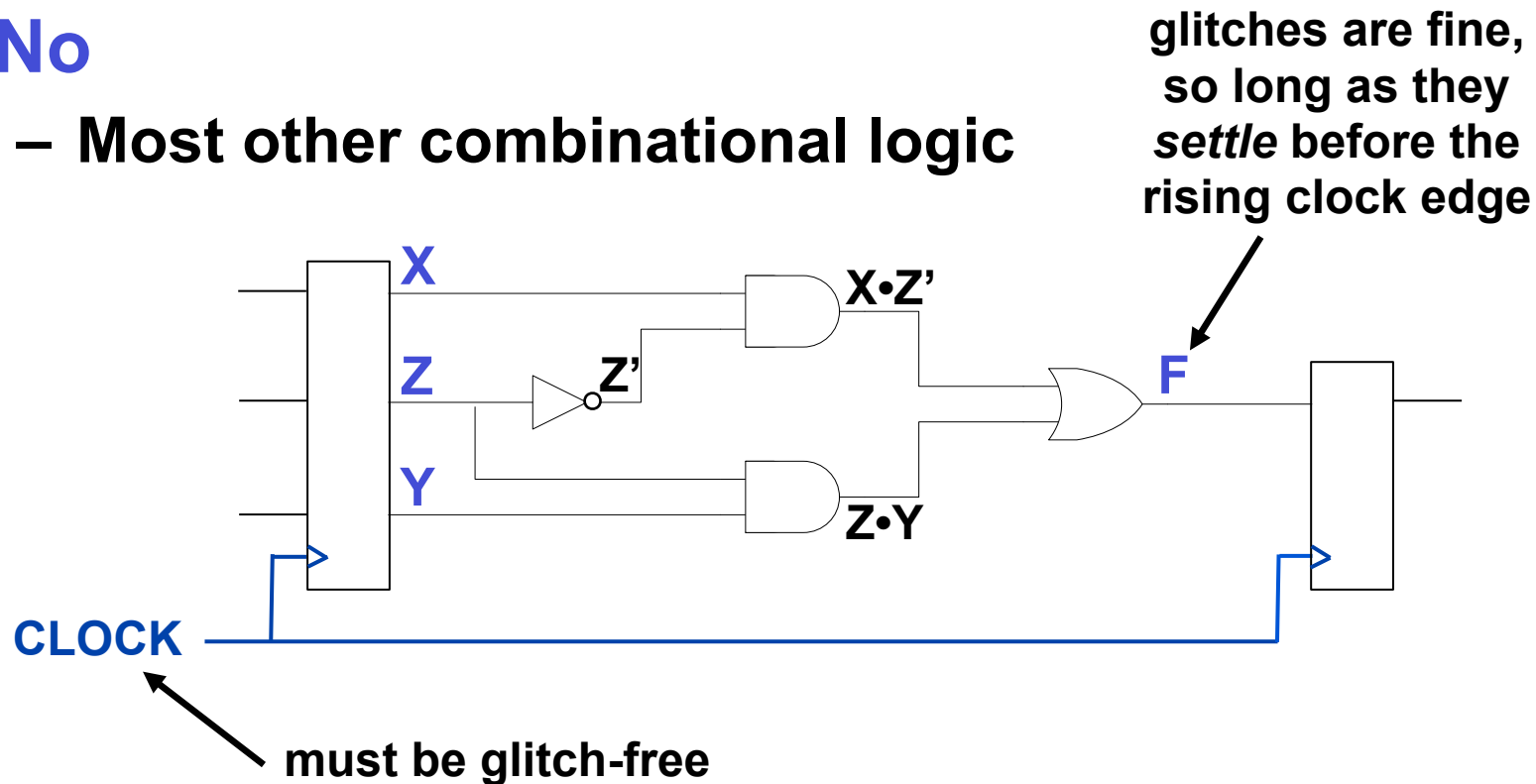
- **Yes**
 - FF clocks and latch enables (and asynch resets!)
- **No**
 - Most other combinational logic





Sequential Circuit Timing

- FFs and latches must meet specified *setup time* and *hold time* requirements
- The *worst case setup time (longest timing path)* determines the maximum clock frequency
- *Timing analysis* involves calculating the time delays between all FF pairs within the circuit
 - To determine the maximum operating frequency
 - To ensure that hold time requirements are met



Sequential Circuit Timing

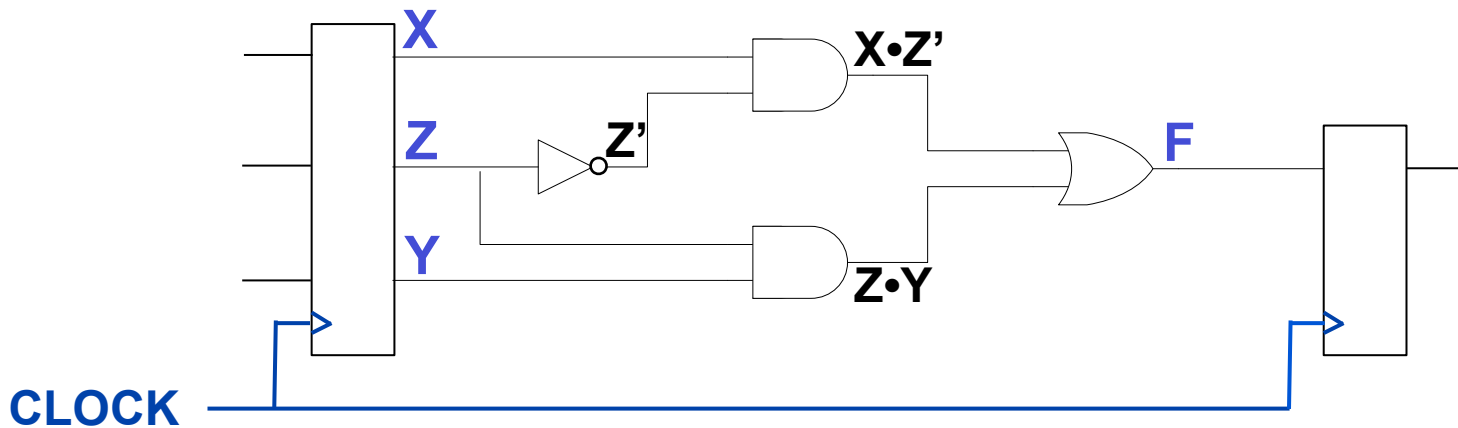 



Glitch on F: No Problem

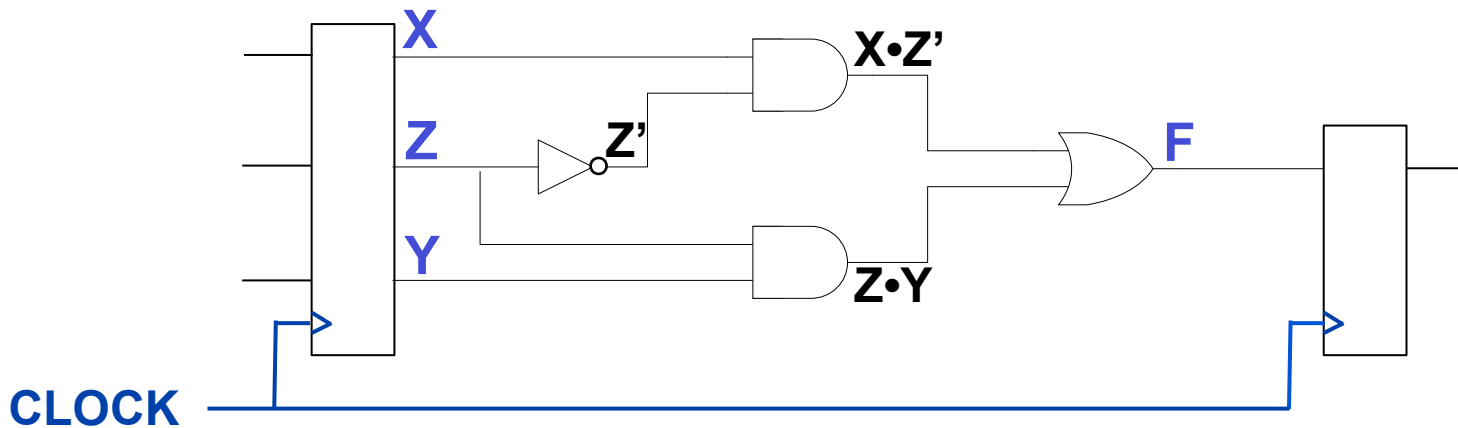 

But What About This Situation?

  


Setup and Hold Time

  


Setup Time

 
- FF input must be stable t_{setup} before the triggering FF clock transition



Setup Time Determines Clock Frequency

 
 
$$t_{\text{clk}} \geq t_{\text{ffpd}(\text{max})} + t_{\text{comb}(\text{max})} + t_{\text{setup}}$$





Setup Time Determines Clock Frequency

- $t_{\text{clk}} \geq t_{\text{ffpd(max)}} + t_{\text{comb(max)}} + t_{\text{setup}}$
- Every circuit path between every pair of FFs must satisfy the above equation to run the circuit at a frequency of $1/t_{\text{clk}}$
- The *worst case* situation is assumed
 - Longest delay through the circuit
 - Worst case temperature and voltage
 - Worst case manufacturing variations



Clock Skew May Make Matters Worse

 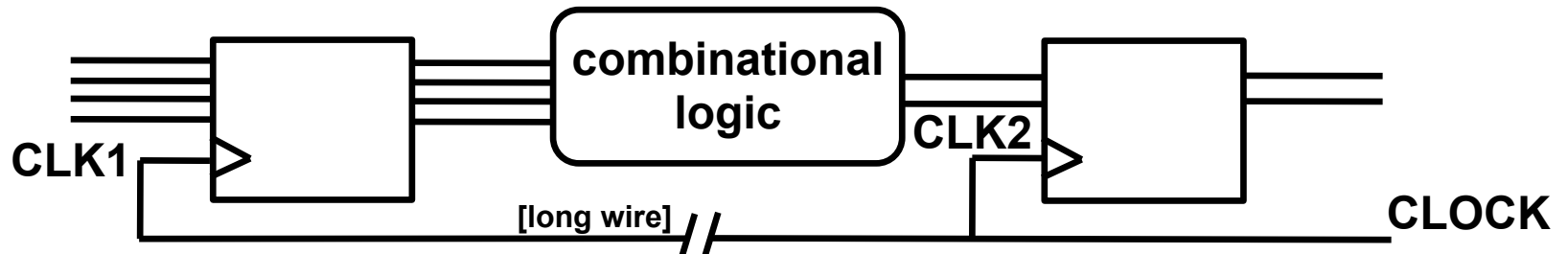- Clock may not reach all flip-flops simultaneously





- We assume the worst case clock skew situation when calculating setup and hold time

Setup Time Without Clock Skew

 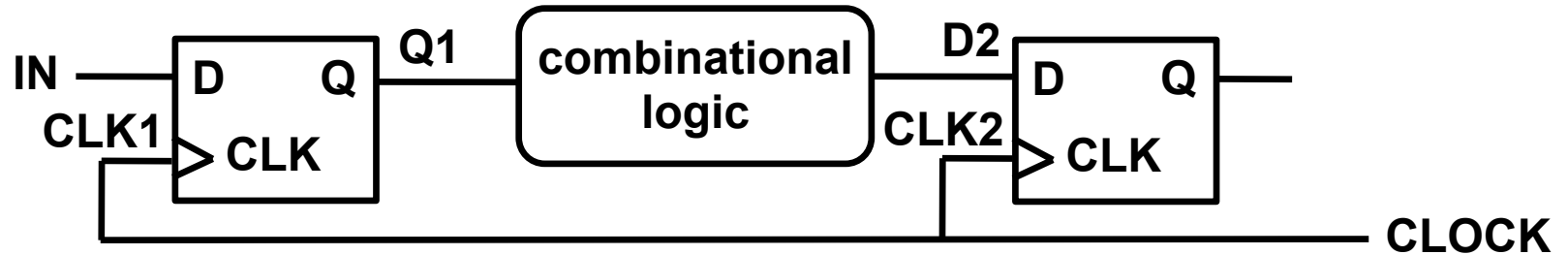



$$t_{clk} \geq t_{ffpd(max)} + t_{comb(max)} + t_{setup}$$

Setup Time With Worst Case Clock Skew

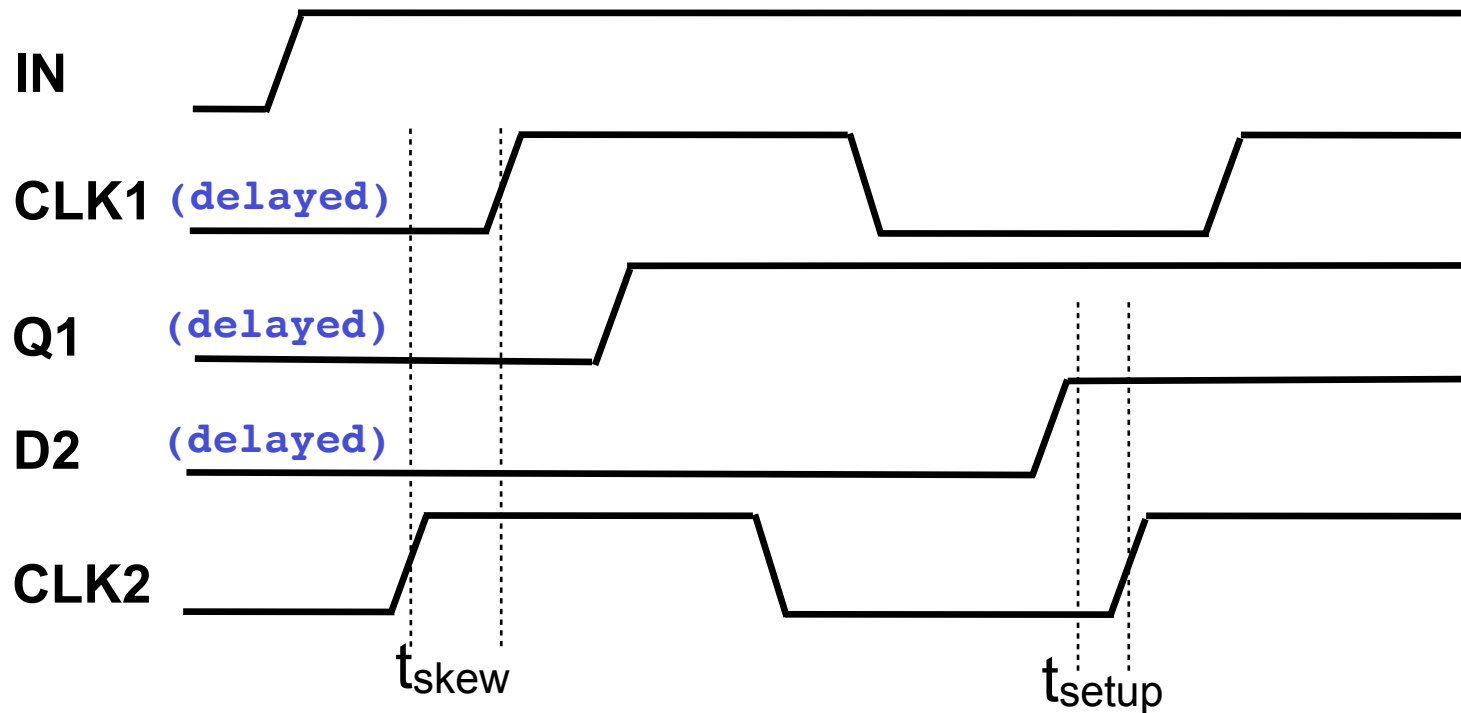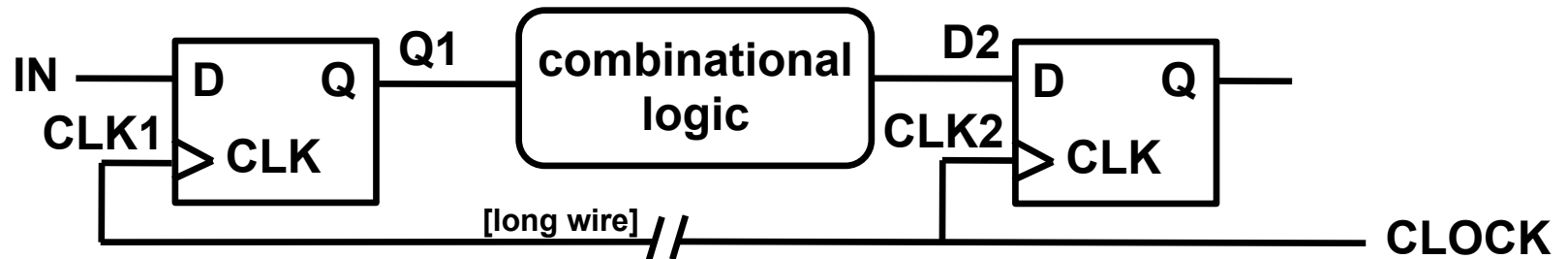


$$t_{clk} \geq t_{ffpd(max)} + t_{comb(max)} + t_{setup} + t_{skew(max)} \quad \text{Lecture 11: 24}$$

What About This Situation?

 
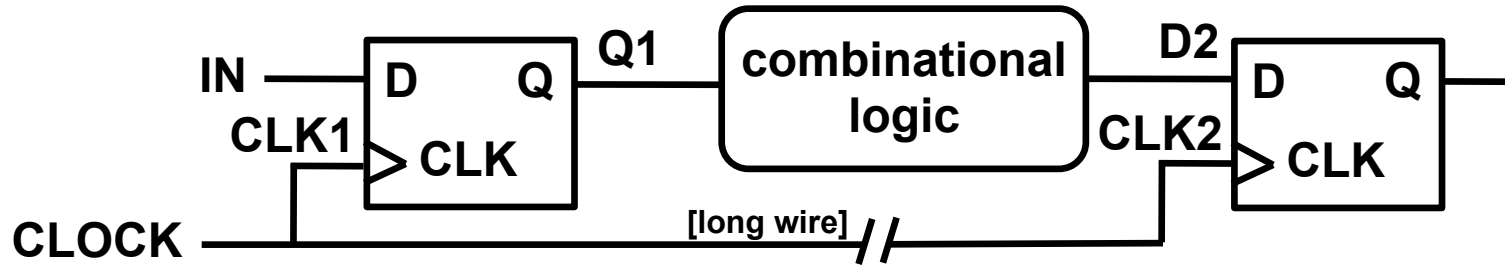


Hold Time

 - FF input must stay stable t_{hold} after the triggering FF clock transition





Hold Time With Clock Skew

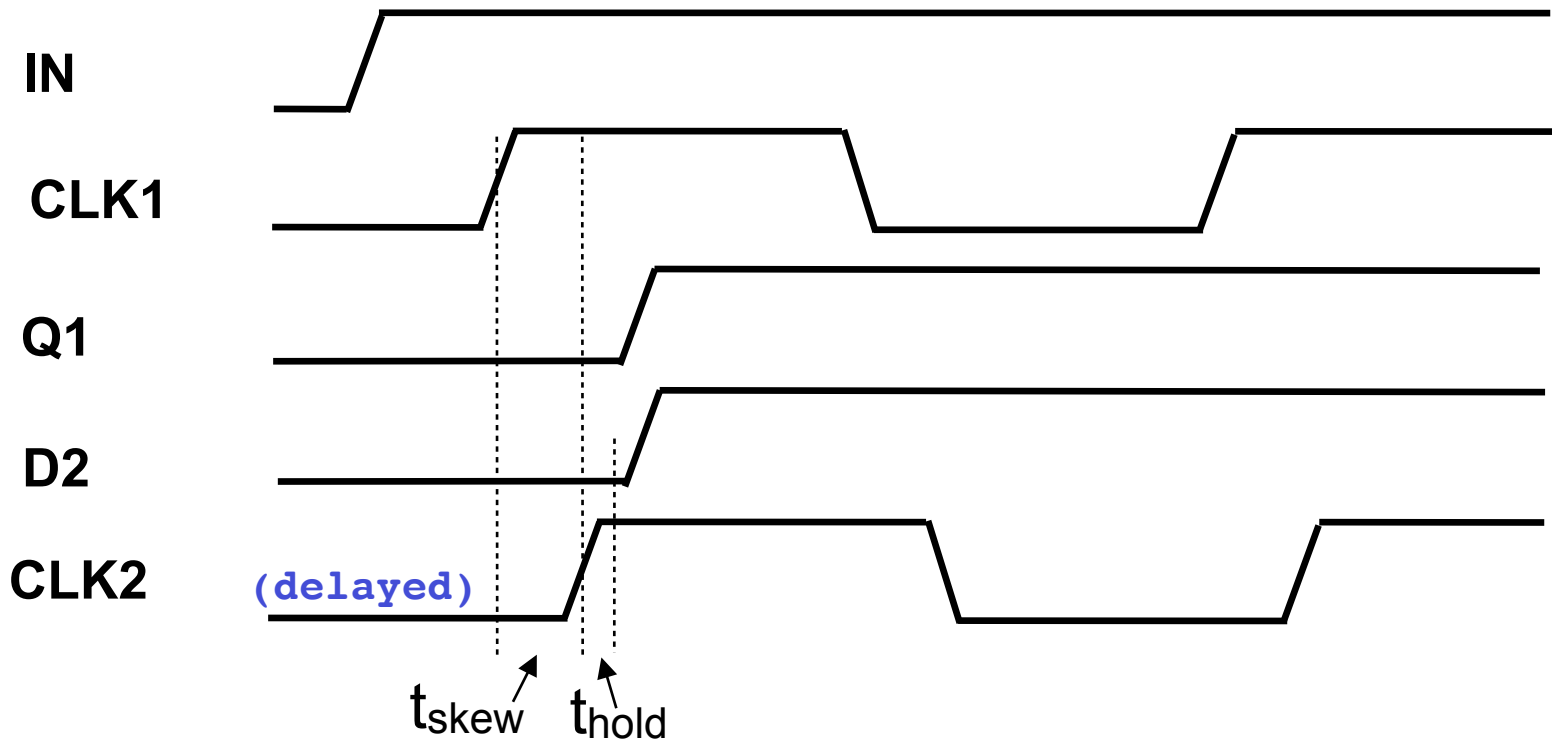
 


$$t_{\text{ffpd}(\text{min})} + t_{\text{comb}(\text{min})} - t_{\text{hold}} - t_{\text{skew}(\text{max})} \geq 0$$


Could Even Clock the Wrong Data!

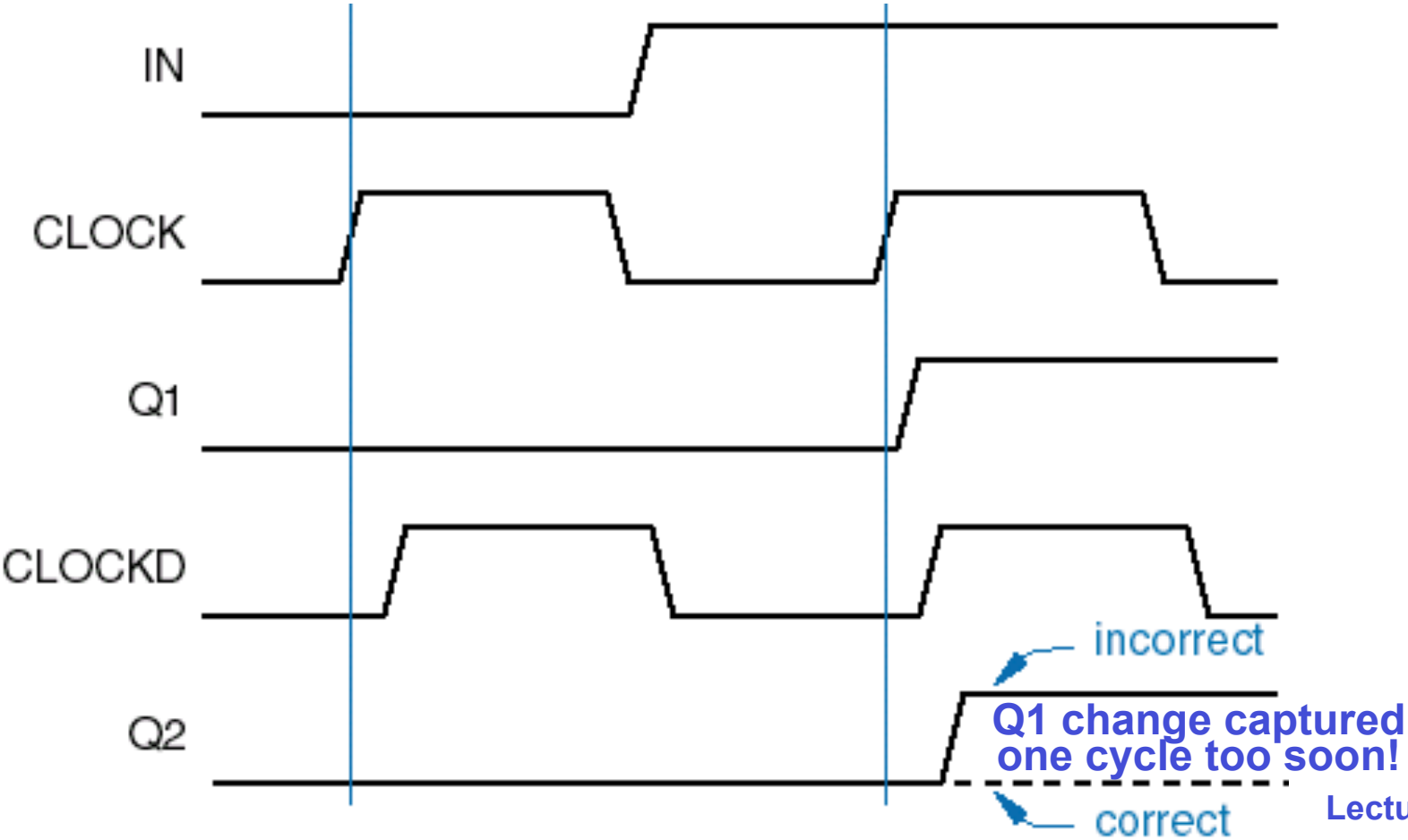 


Setup and Hold Time Calculations

  


Setup and Hold Time Calculations

 

Setup and Hold Time Calculations

 


Clock Distribution

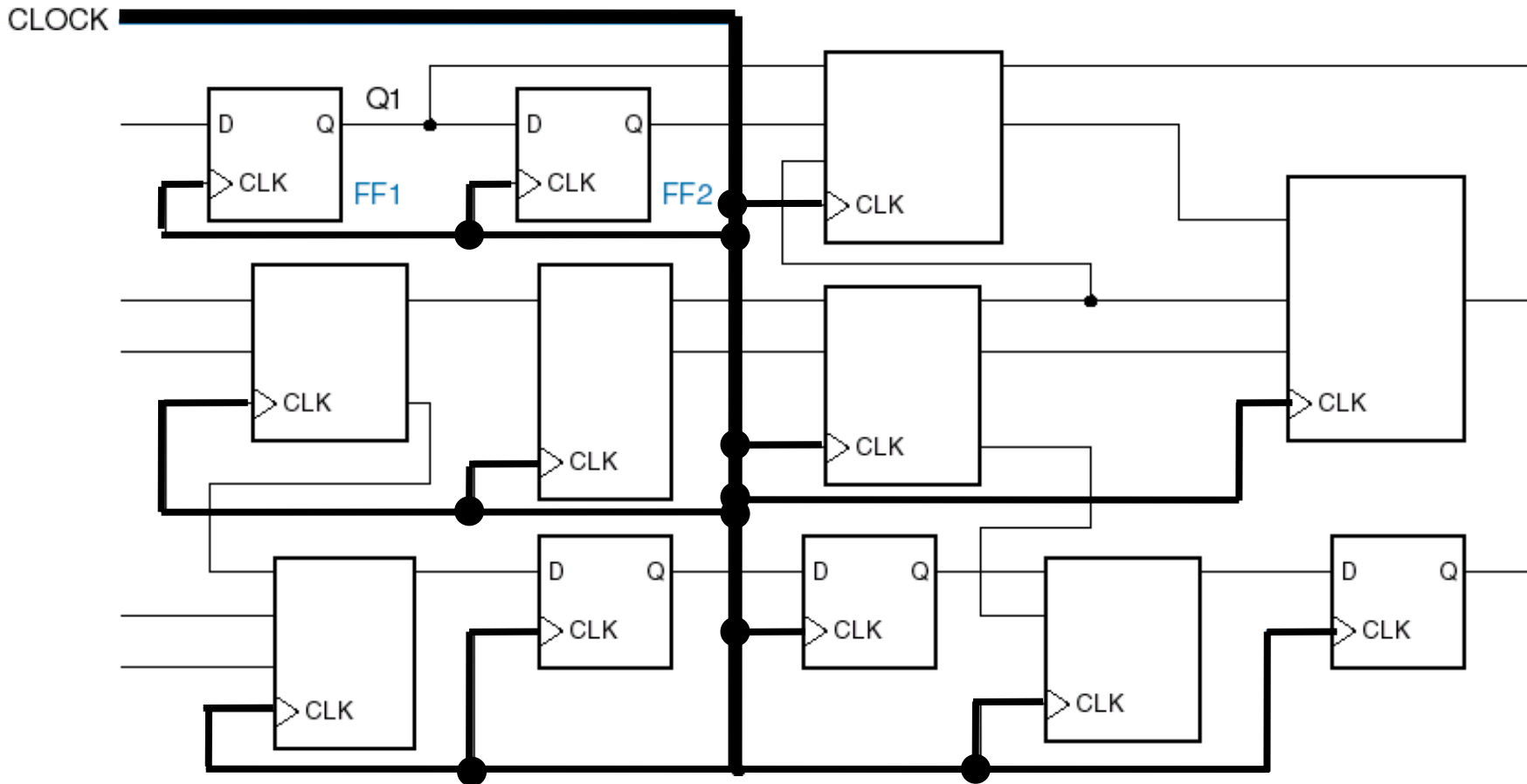


- Tree-like structure (often an “H-tree”)
- Dedicated metal layers (avoid noise, routing contention)
- Wide metal lines (low $R \rightarrow$ low RC time constant)
- Clock buffers for large clock trees

Binary Up Counter Revisited

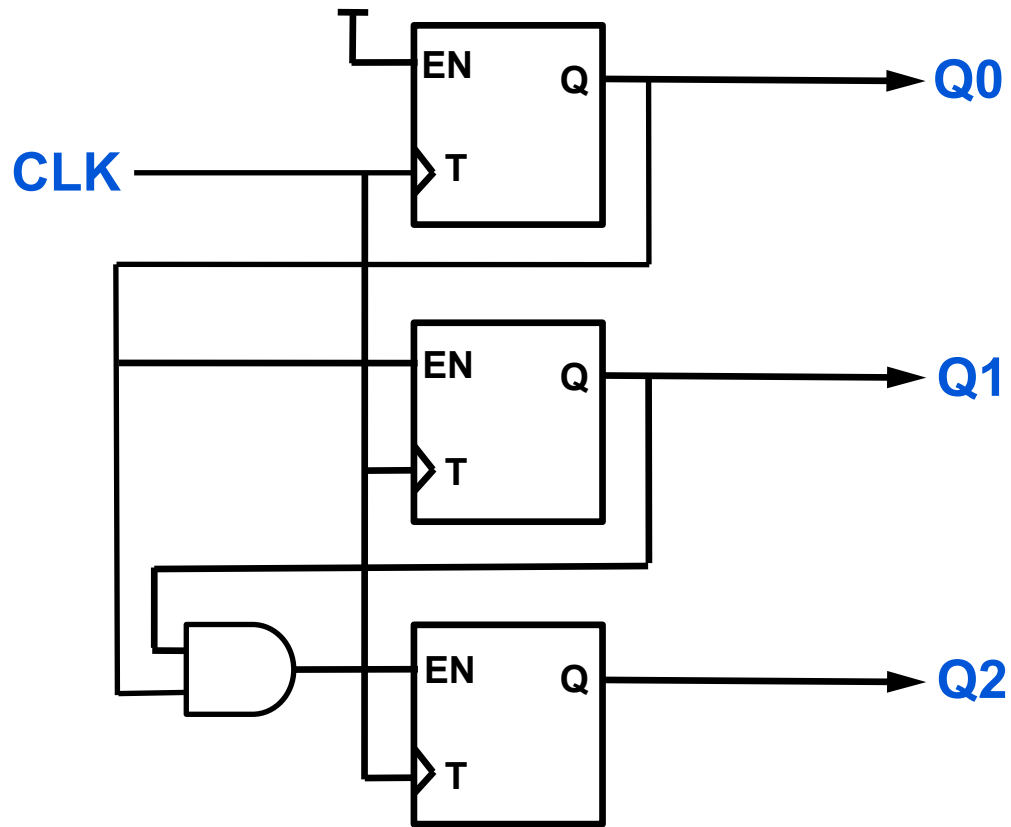

<u>Q₂</u>	<u>Q₁</u>	<u>Q₀</u>
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1
0	0	0
0	0	1

Binary Up Counter Revisited

 

**Avoid the temptation to
mess with the clock input!**

Before Next Class

- H&H 1.4, 5.1-5.2.6

Next Time

Metastability
Binary Arithmetic