

ECE 2300
Digital Logic & Computer Organization
Fall 2016

More ALU
Multiplication
Memories



Cornell University

Arithmetic Logic Unit (ALU)

- **Combinational logic circuit that combines a variety of operations into a single unit**
- **Typical operations may include**
 - **Addition and subtraction**
 - **Logical (OR, AND)**
 - **Shift and rotate**
 - **Comparisons**
- **Computing core of a processor**

Example 8-bit Arithmetic Logic Unit

- **Operations**

- Addition and Subtraction
- Bitwise AND and OR
- Shift Left and Shift Right


- **Inputs**

- A, B, Carry In (CI)
- Shift In (SI)
- Code indicating operation to be performed (OP)

- **Outputs**


- Y, Carry Out (CO)
- Shift Out (SO)
- Flags regarding the result of the operation

ALU Block Diagram

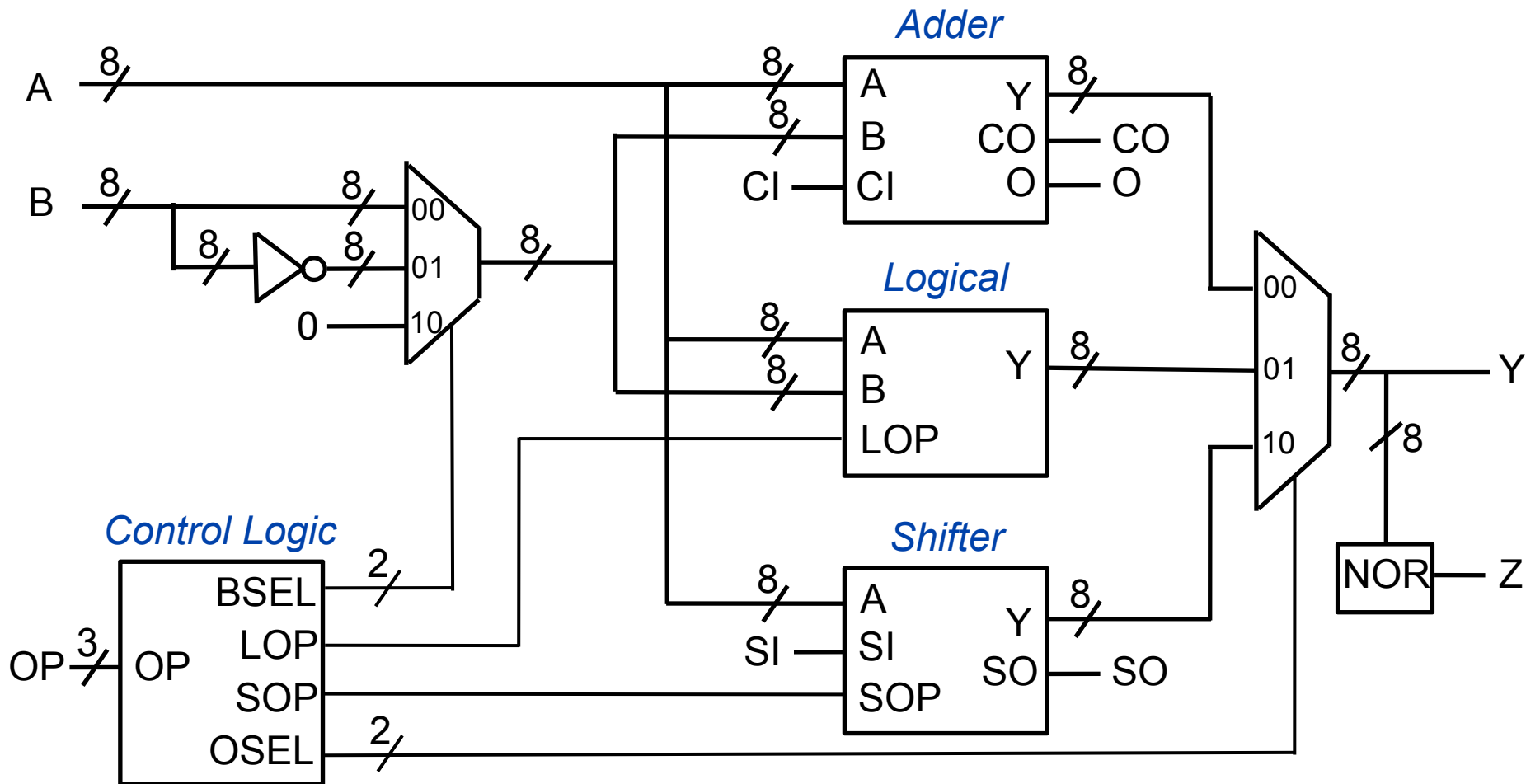


ALU Operations

NAME	OP	BSEL	CI	LOP	SOP	OSEL	Operation
ADD	000	00	0	-	-	00	$Y = A + B + CI$
SUB	001	01	1	-	-	00	$Y = A + B' + CI$
AND	011	00	-	0	-	01	$Y = A \text{ AND } B$
OR	100	00	-	1	-	01	$Y = A \text{ OR } B$
SHL	101	-	-	-	0	10	$Y = A[6..0], SI$
SHR	110	-	-	-	1	10	$Y = SI, A[7..1]$
PASS	111	10	0	-	-	00	$Y = A + B + CI$

 

Comparison Operations

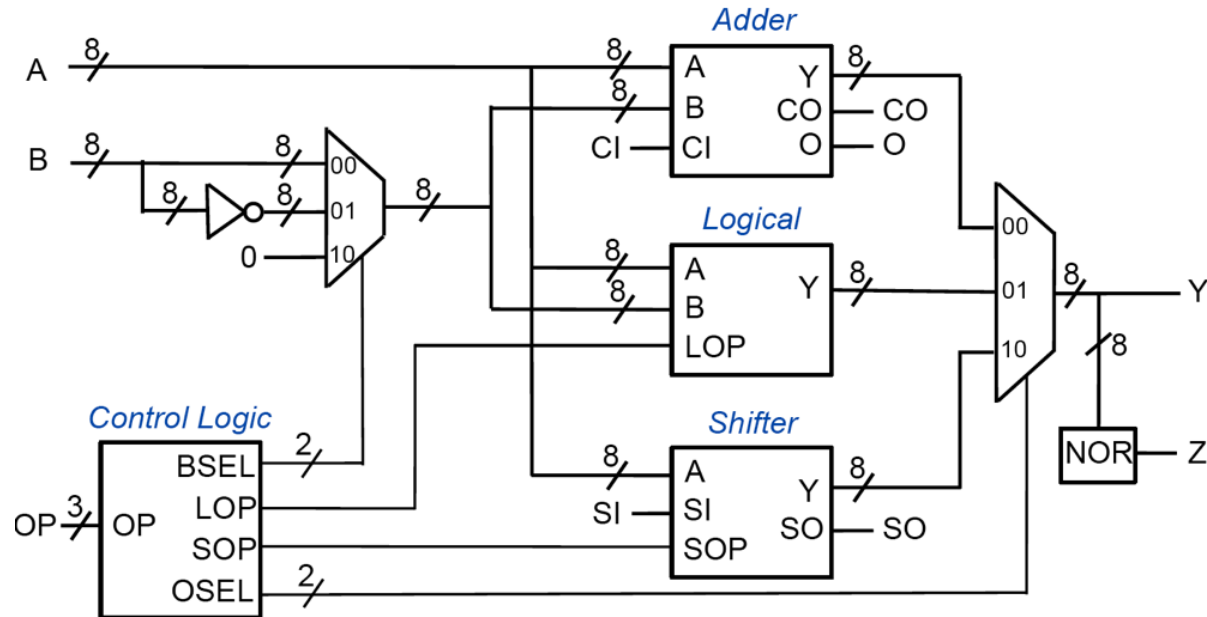- To compare A and B, perform $A - B$
 - If the result is 0, then $A = B$
 - Z flag set to 1 whenever ALU result is 0
 - Can check for $A \geq B$ and $A < B$ by observing the MSB of the result (Y) of $A - B$



Multiplication

- Form each partial product by multiplying a single digit of the multiplier by the multiplicand
- Add shifted partial products to get result

Decimal

$$\begin{array}{r} 230 \\ \times 42 \\ \hline 460 \\ + 920 \\ \hline 9660 \end{array}$$

$$230 \times 42 = 9660$$

Binary


multiplicand	0101
multiplier	x 0111
	<hr/>
partial products	0101
	0101
	0101
	+ 0000
	<hr/>
result	0100011

$$5 \times 7 = 35$$

Memories in Digital Systems

- **Memory is used in virtually all digital designs**
- **Microprocessors have lots of memory**
 - **Caches**
 - **Register files**
 - **Buffers, queues, etc**
 - **Arrays for logic functions**
- **Most microprocessor memory is SRAM**
 - **Very fast**
- **Main memory uses DRAM**
 - **Denser, lower cost/bit, less power**

Our Microprocessor Needs Memory

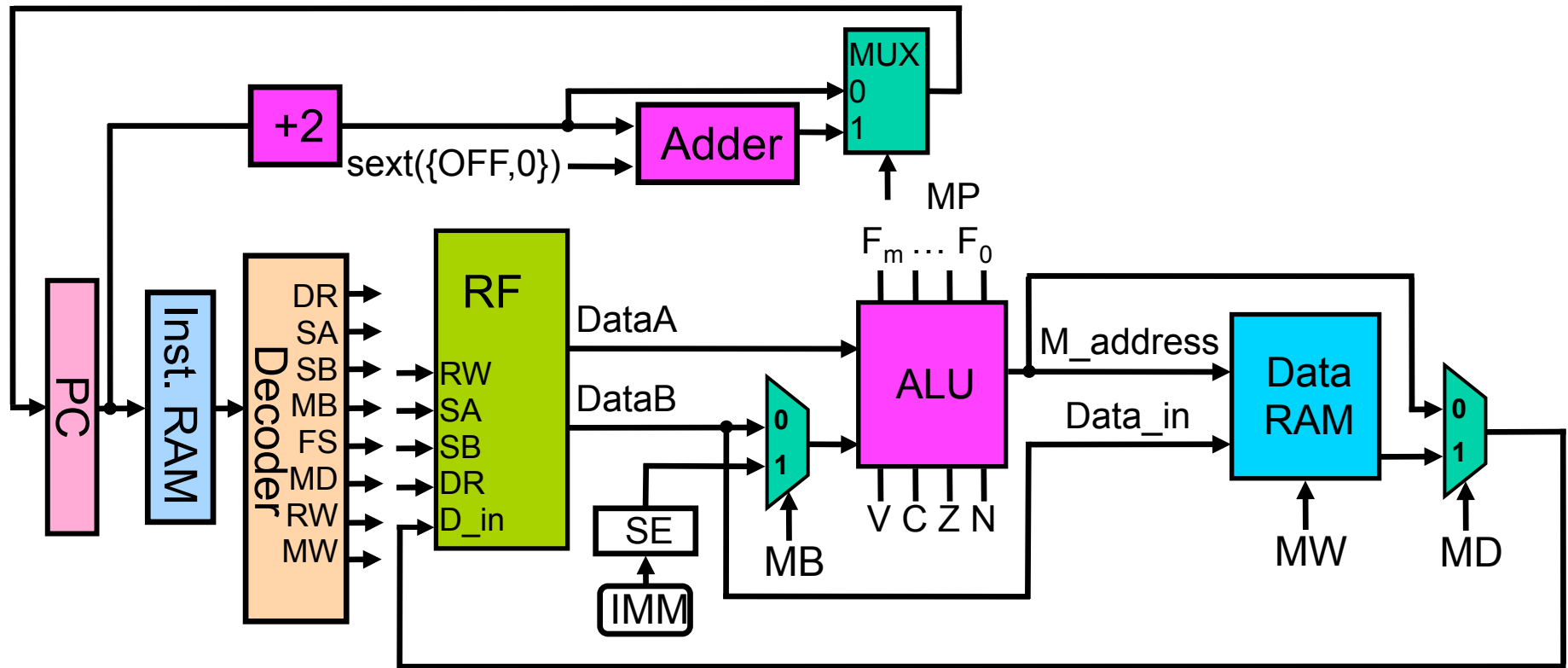


Types of Memories

- **Random Access Memory (RAM)**
 - Read and write any location at similar speeds
 - Volatile: loses contents when powered off
 - SRAM, DRAM
- **Read-Only Memory (ROM)**
 - Truly read-only
 - Written in the factory, and never written after installation
 - Mostly read and rarely written
 - Much faster to read than write
 - Non-volatile
 - ROM, PROM, EPROM, EEPROM, Flash memory

General Memory Organization

 - Two dimensional array of *bit cells*
- Each bit cell stores 1 bit
- *Address* selects a row of *data* (multiple bit cells)




Address	Data		
11	0	1	0
10	1	0	0
01	1	1	0
00	0	1	1

A diagram illustrating the bit cell organization. The table above shows a 4x3 grid of bits. To the right of the table, a vertical double-headed arrow labeled "depth" spans the height of the table. Below the table, a horizontal double-headed arrow labeled "width" spans the width of the table.


General Memory Organization

- More detail

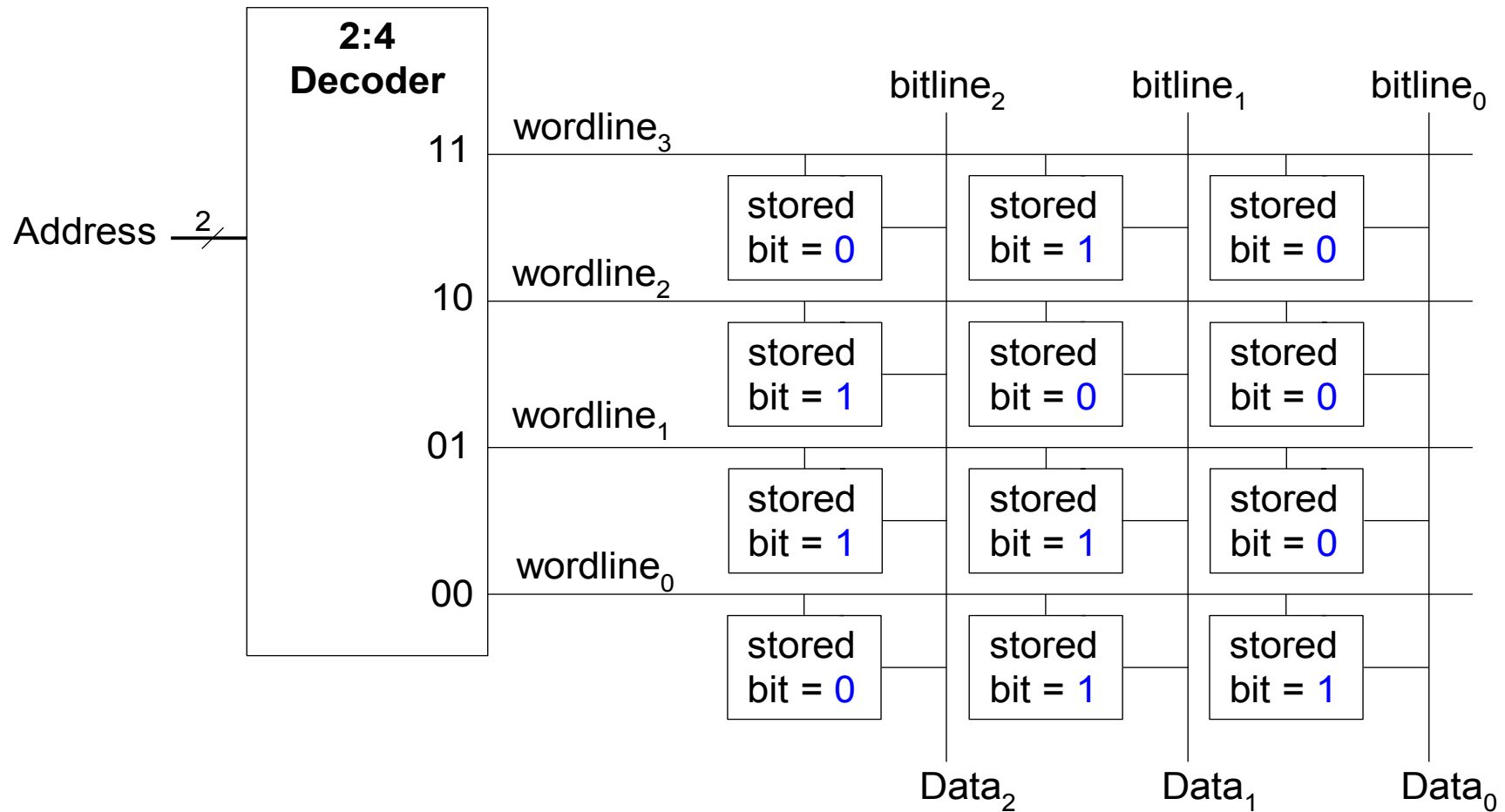


Static RAM (SRAM)

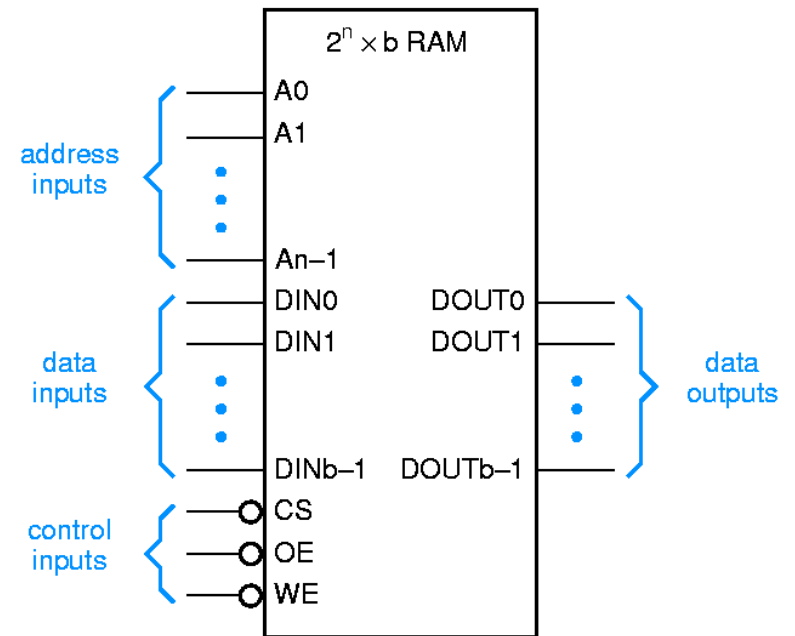- **Address**: points to the location to read or write
- **Data inputs**: data to be written into memory
- **Data outputs**: data read from memory
- **Write Enable (WE)**: tells whether to read or write
- **Chip Select (CS)**: selects the chip for reading/writing
- **Output Enable (OE)**: controls the data output tristate drivers




SRAM Internal Structure

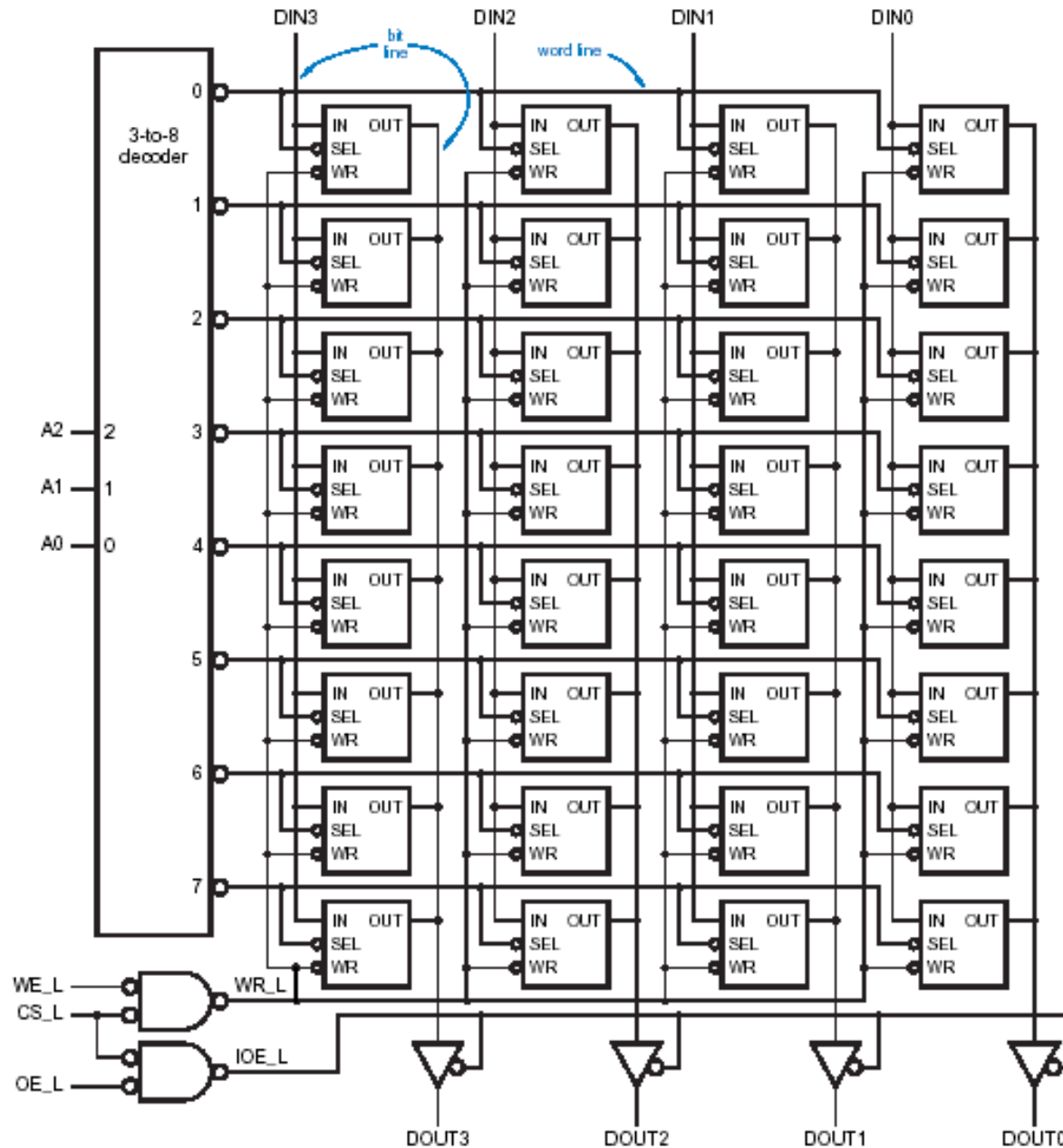


SRAM Cell

 **SEL_L asserted to
access output (read)**




**SEL_L and WR_L
asserted to enable latch (write)**

≡

 

SRAM Read Timing

 

t_{AA} Access time from address


t_{ACS} Access time from chip select

t_{OE} Output enable time

t_{OZ} Output disable time

t_{OH} Output hold time

SRAM Write Timing

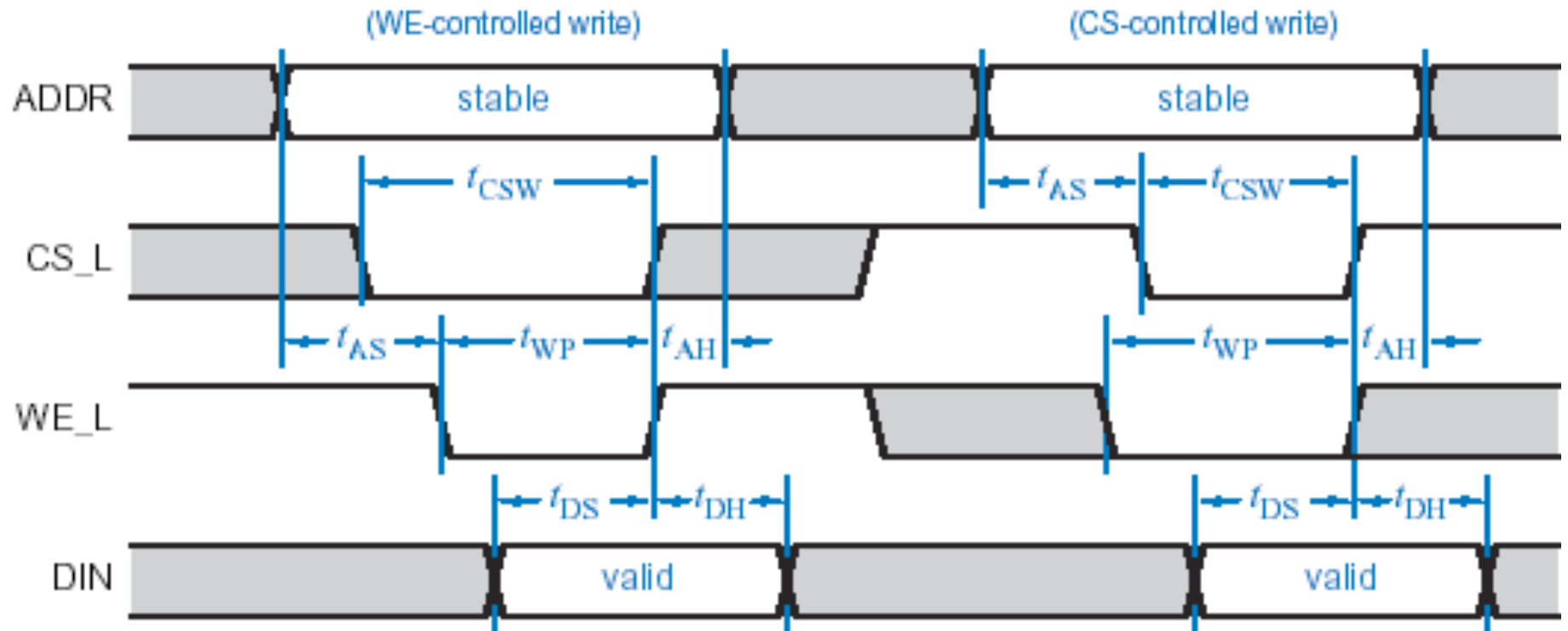

t_{AS} Address setup time before latest of CS_L & WE_L

t_{AH} Address hold time after CS_L & WE_L


t_{CSW} Chip select setup before WE_L

t_{WP} Write pulse width

t_{DS} Data setup time before WE_L

t_{DH} Data hold time after WE_L deasserted

Bi-directional Data Pins

 


- Reduces the number of data pins by half
- Disable output buffer whenever WE_L asserted

Dynamic RAM (DRAM)

- **SRAM advantages and disadvantages**
 - Very fast (+)
 - High power (-)
 - Relatively high area/bit (-)
- **DRAM**
 - Single transistor storage cell
 - Higher density → lower cost/bit
 - Lower power/bit


DRAM Bit Structure

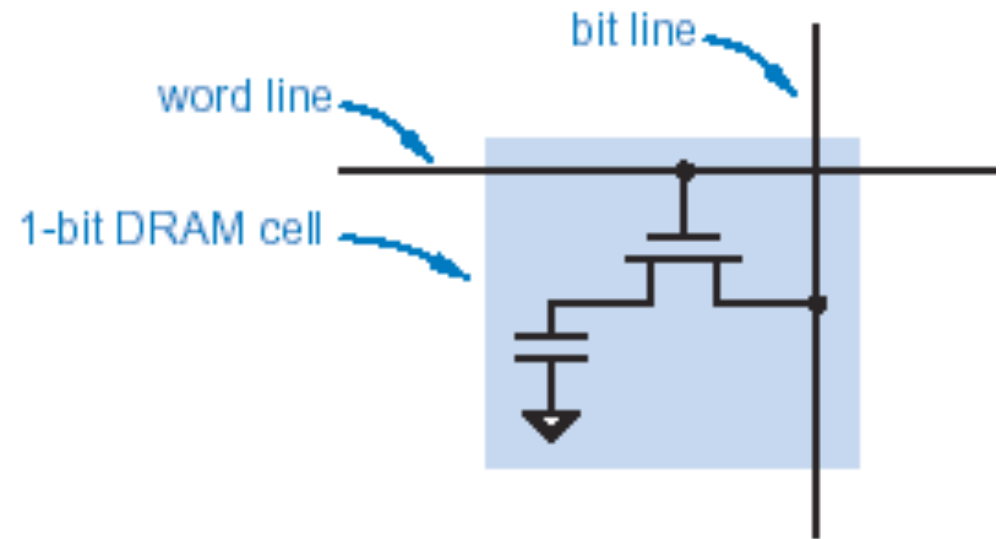- Capacitor accessed through a transistor
- Capacitor is charged through the bit line to store a 1
- Capacitor is discharged through the bit line to store a 0




DRAM Read

 - Bit line *precharged* halfway between 0 and 1
- Word line is asserted
- Capacitor voltage pulls the bit line slightly higher or lower
- *Sense amplifier* detects this small change (1 or 0)




DRAM Organization (64K x 1)

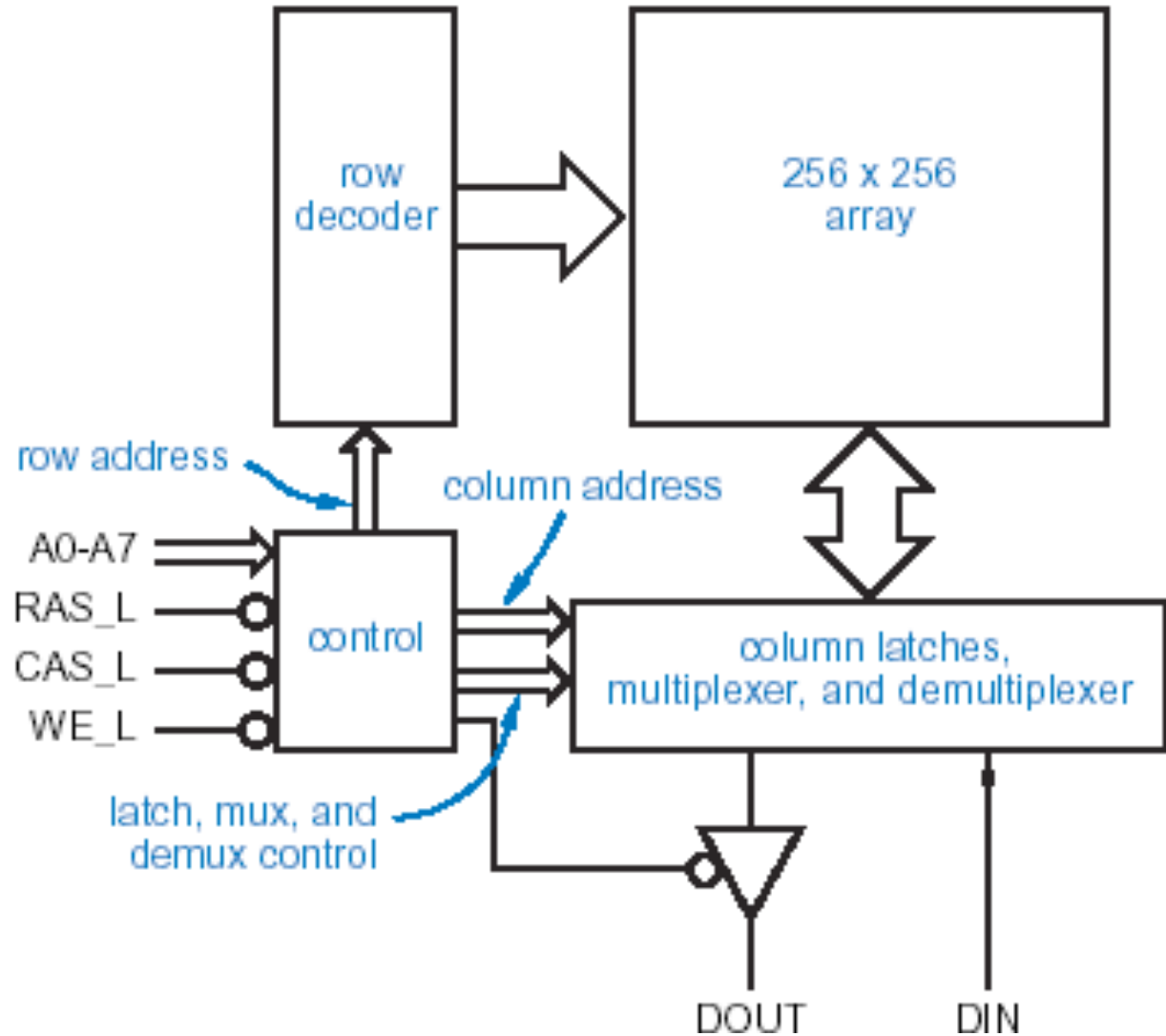
- **Multiplexed address inputs**
- **Row-address strobe (RAS)**
 - Selects row of array
- **Column-address strobe (CAS)**
 - Selects subset of the row



DRAM Read Cycle

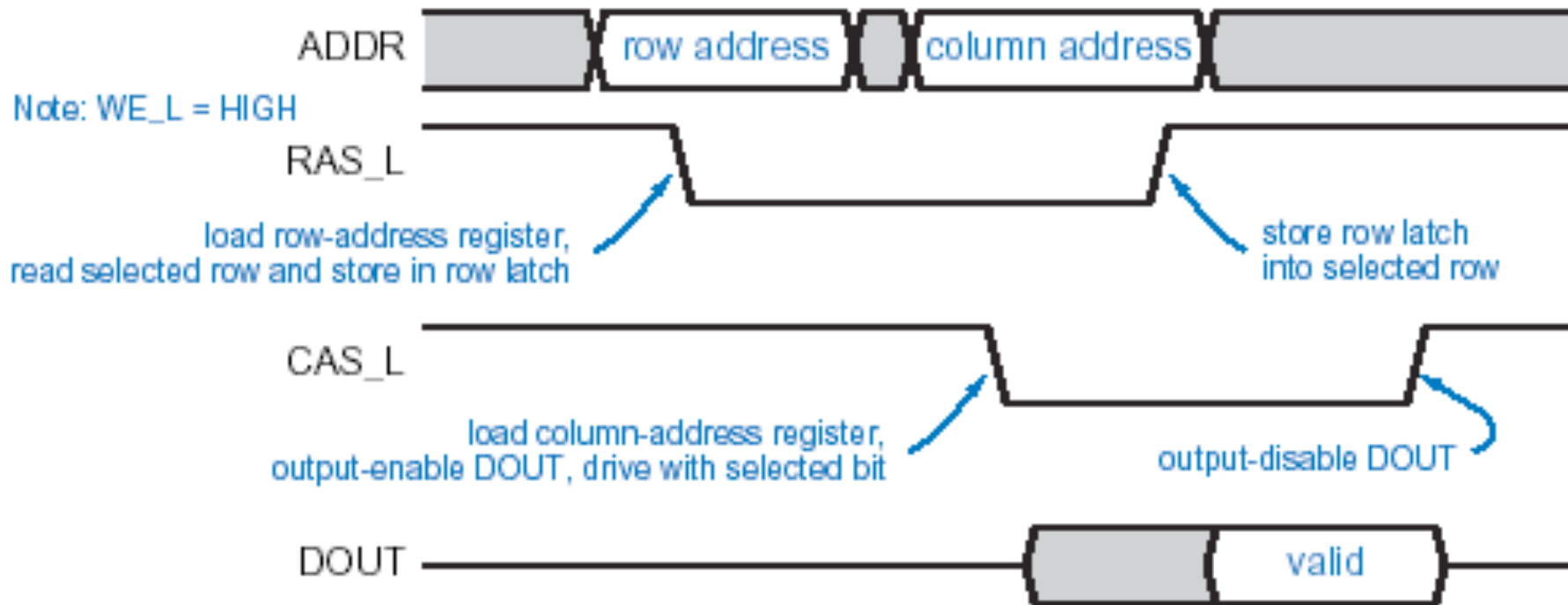


DRAM Write Cycle

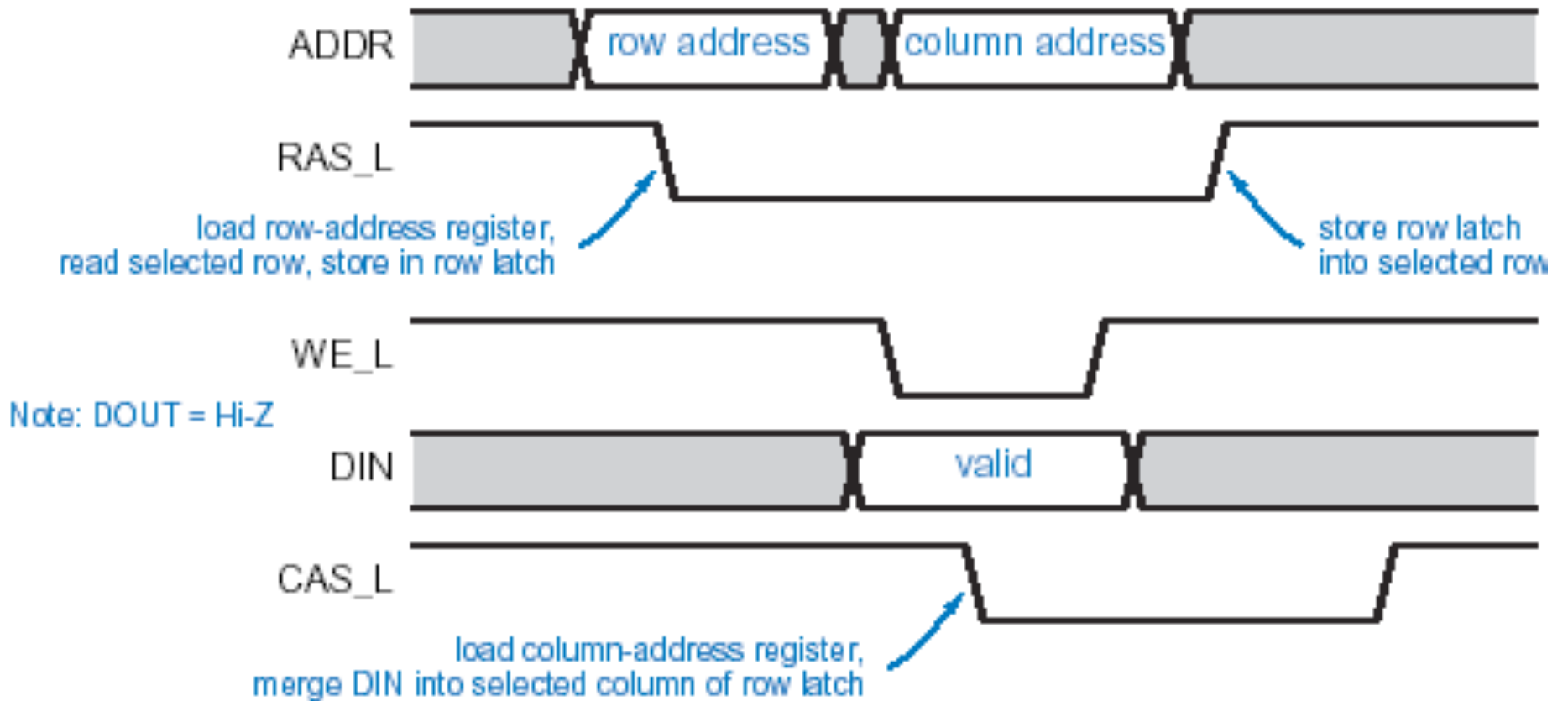


DRAM Refresh

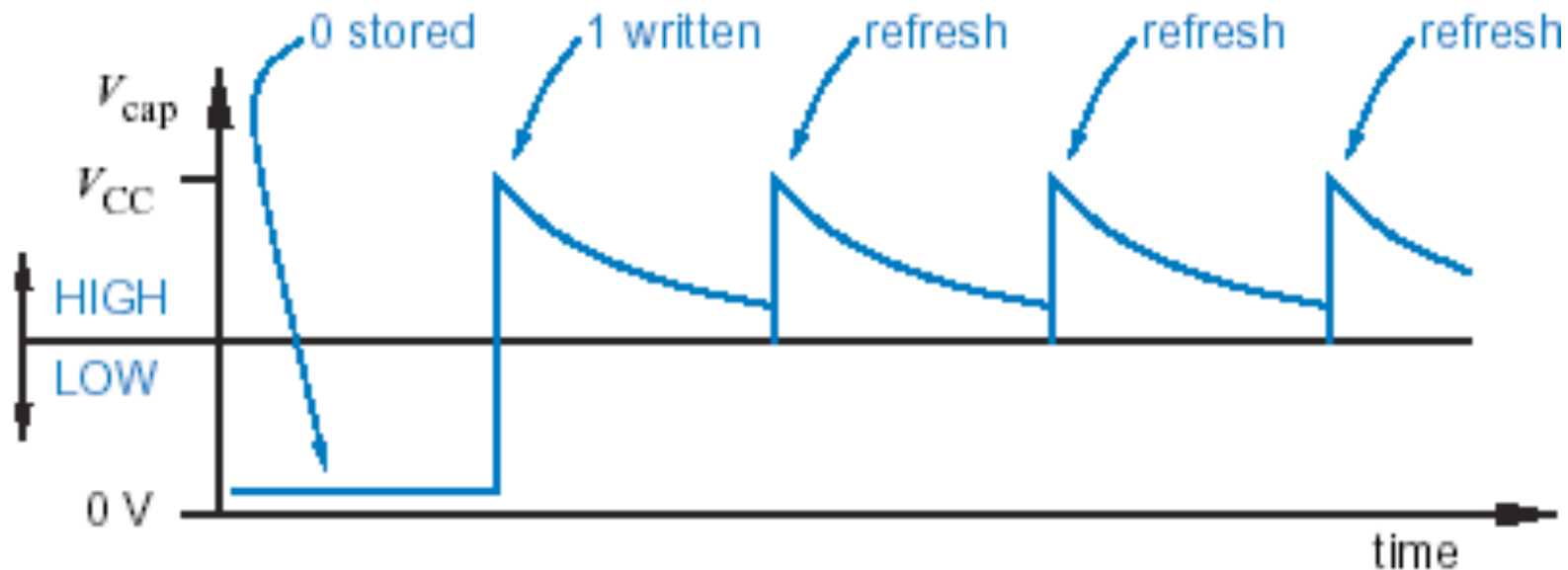- Capacitors discharge over time
- *Refresh* cycles recharge each memory bit
- Each row periodically accessed using RAS, which restores the charge



DRAM Refresh

 

- Refresh an entire row at a time
- Old DRAMs → Each bit must be refreshed every 4 ms
 - 256 refresh operations for entire 64Kx1 DRAM
 - Initiate a refresh cycle every 15.6 microseconds
- New DRAMS → Each bit must be refreshed every 64 ms, but have 4096 rows
 - Still must initiate a refresh every 15.6 microseconds

Synchronous DRAM (SDRAM)

- D FFs on input and output signals
- Can “pipeline” multiple read and write operations
- Multiple banks that can be accessed concurrently
- DDR: data transferred on both rising and falling clock edges

Before Next Class

- **H&H 7.1-7.3.1**

Next Time

More Memories
Single Cycle Microprocessor