


ECE 2300
Digital Logic & Computer Organization
Fall 2016

More Single Cycle Microprocessor



Cornell University

The Basic Processing Cycle

 

- Read data from two registers
- Perform an operation
- Place the result into a register
- All three steps performed in 1 clock cycle

Register File

- **Collection of 2^k n-bit loadable registers**

- **Control inputs**

SA – Source address A

SB – Source address B

DR – Destination address

**LD – Load destination register
with D_in**


- **Data inputs**

D_in – Input data


- **Data outputs**

DataA – Output data A

DataB – Output data B

 


Register File

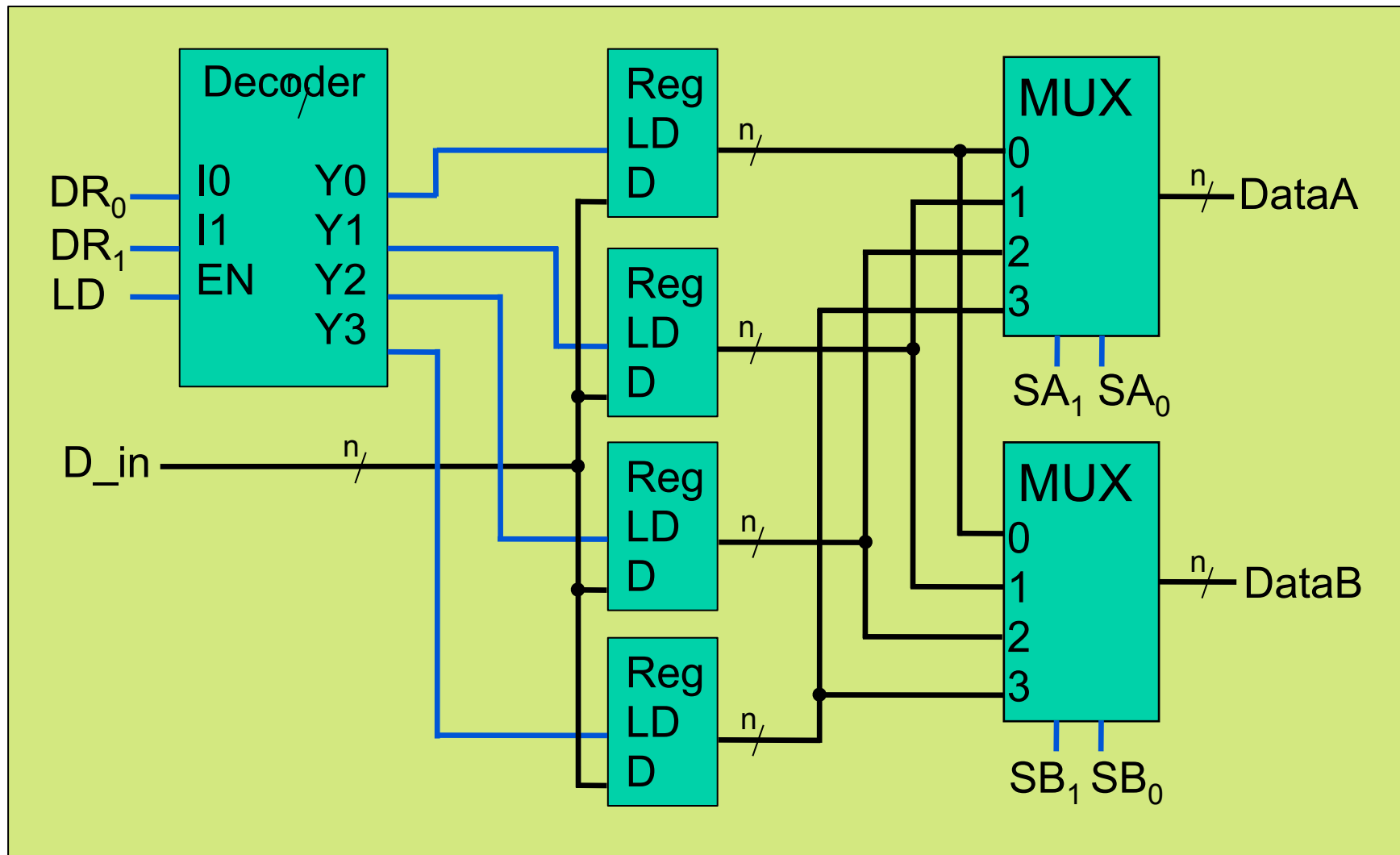

Example with 4 registers. Typically have 32 or more.


Instruction Execution

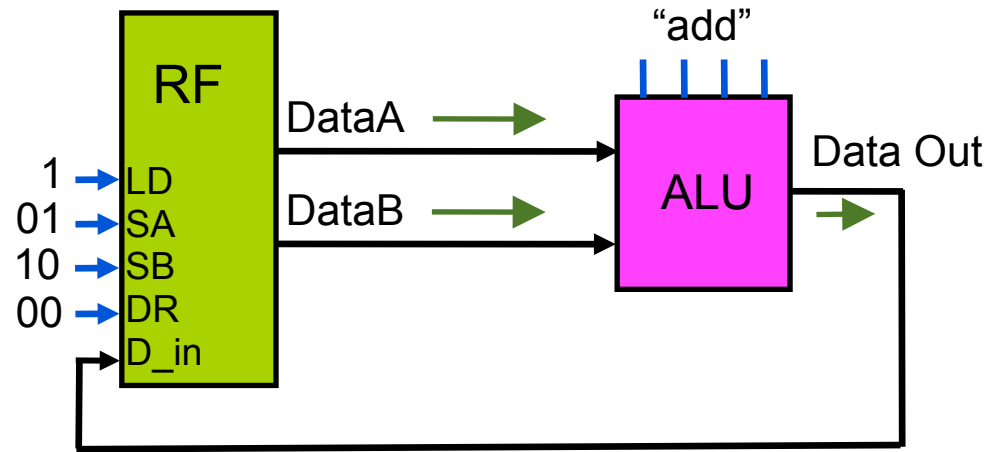


ADD R0, R1, R2

operation destination register source registers


Instruction Execution

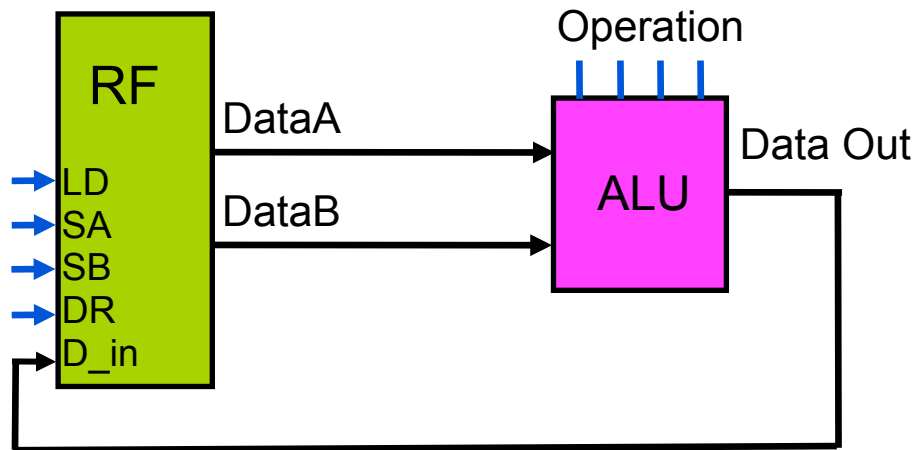


ADD R0, R1, R2

 


Instruction Execution

 


ADD R0, R1, R2
SUB R3, R2, R1

 


Instruction Execution

 

ADD R0, R1, R2
SUB R3, R0, R3

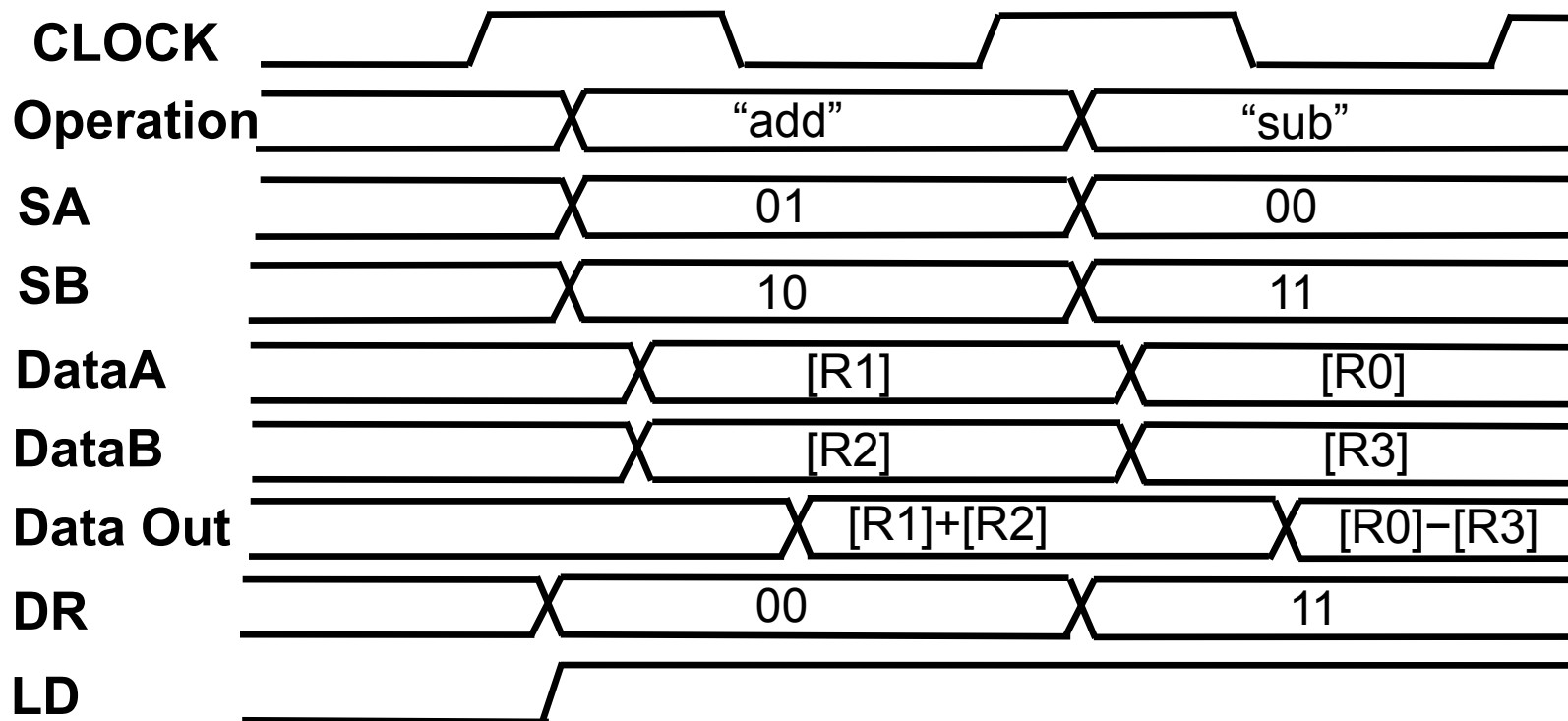

Operations With Constants

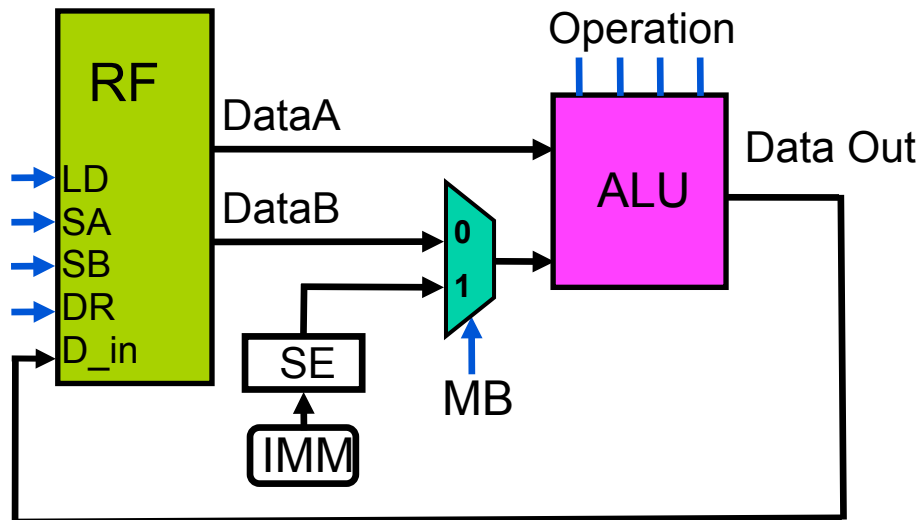


ADDI R1, R1, 1

- Constants are called *immediate values*
- Sign extend (SE) IMM to the width of DataA to perform correct two's complement operation
 - Why? May not have enough bits in instruction (later)
 - Assume IMM is 4 bits and DataA is 8 bits wide

0101 → 00000101


1110 → 11111110

Reading and Writing Memory

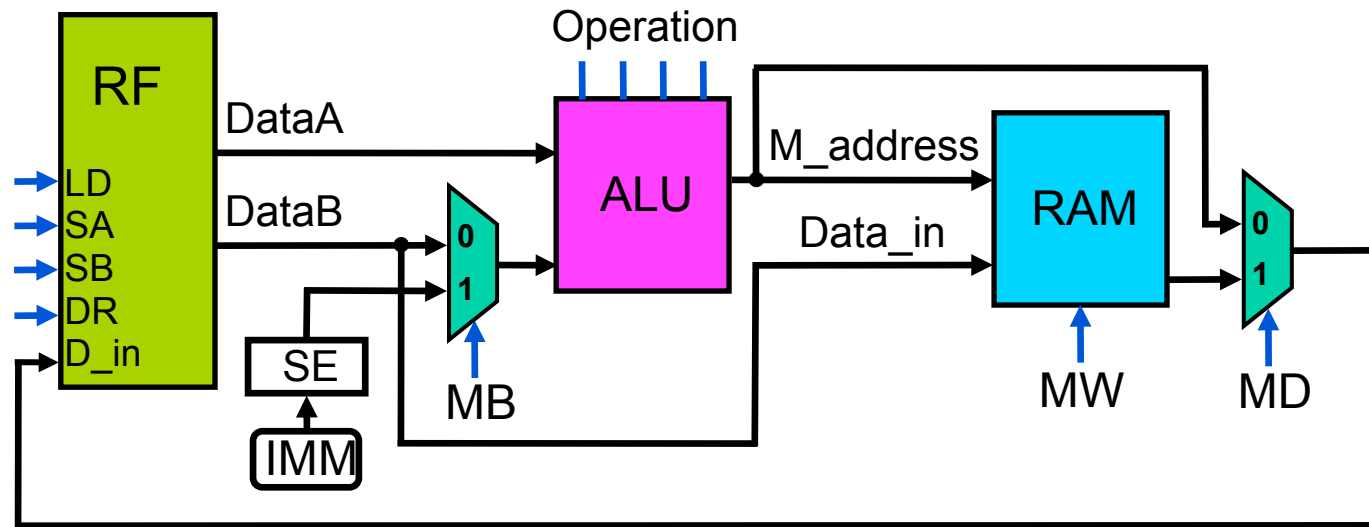

- **Most data is held in memory (RAM)**
- **Must be moved into a register in order to operate on it**
- **Data is also moved out of registers into memory**
 - To make room for other data
 - To move it to permanent storage (e.g., disk)

Reading Memory (“Load”)

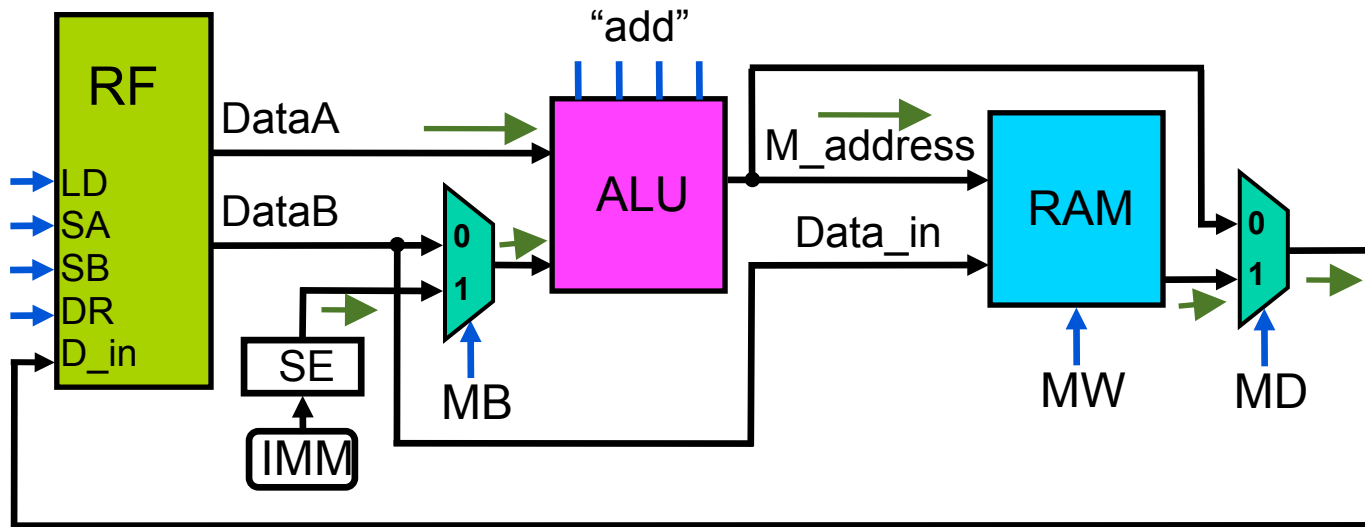


LOAD R3, 4(R1)

Step 1: Form the memory address by adding the value in R1 with the immediate (*offset*) 4

Step 2: Read the data at that address in RAM and place it in R3

Writing Memory (“Store”)

 

STORE R2, 0(R0)


Step 1: Form the memory address by adding the value in R0 with the immediate 0

Step 2: Write the value in R2 into the RAM at that address


Control Unit

- Controls flow of data and operations on data
- Series of *control words* control the datapath to perform a sequence of operations
- The sequence of operations performed by the CU is affected by the *ALU Condition Codes*
 - Z: Zero
 - N: Negative
 - V: Overflow
 - C: Carry out


Datapath + Control Unit

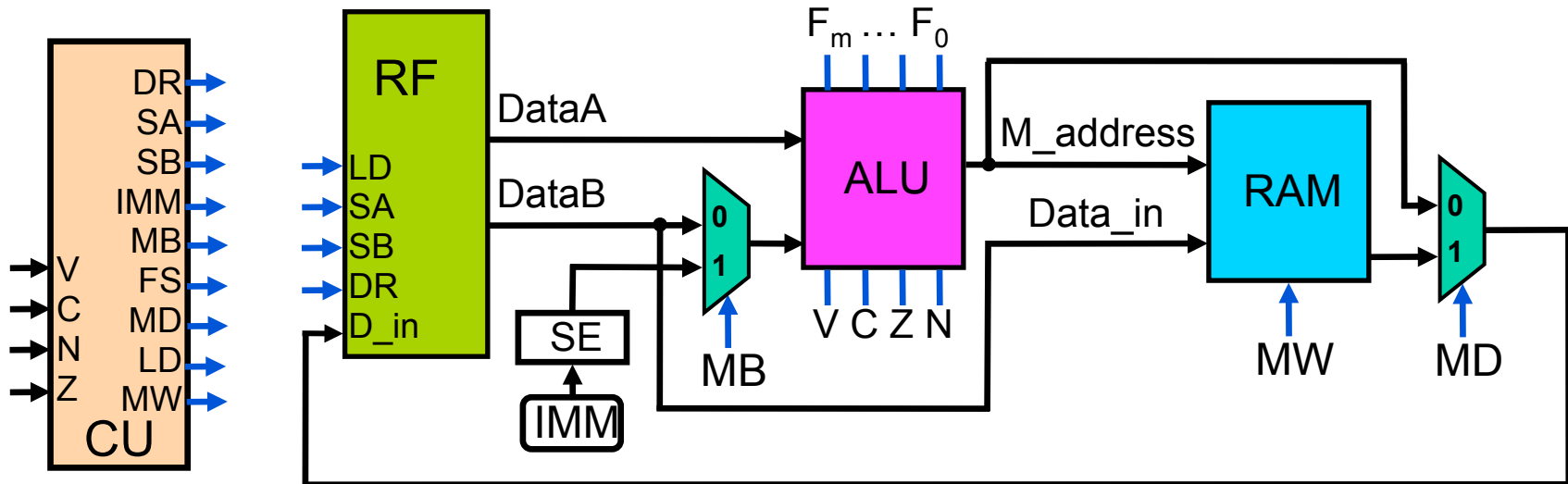

Control Word →

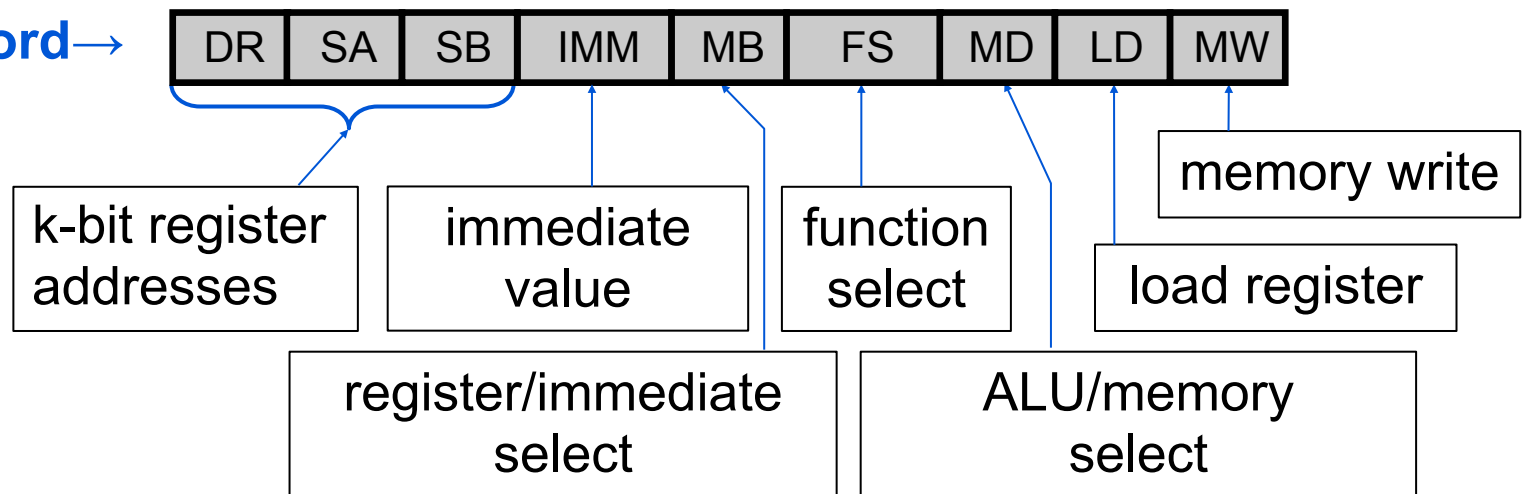

Sequence of Operations

 

$R2 \leq R0 + R1$

$R1 \leq M[R2]$

$M[R2] \leq R0$

$R3 \leq R0 + 3$

DR	SA	SB	IMM	MB	FS	MD	LD	MW
010	000	001	x	0	ADD	0	1	0
001	010	xxx	0	1	ADD	1	1	0
xxx	010	000	0	1	ADD	x	0	1
011	000	xxx	3	1	ADD	0	1	0

Shift and Add Multiplication

- Multiply $A_2A_1A_0$ by $B_2B_1B_0$

$$\begin{array}{r}
 A_2A_1A_0 \\
 B_2B_1B_0 \\
 \hline
 (A_2A_1A_0) \times B_0 \\
 (A_2A_1A_0) \times B_1 \\
 (A_2A_1A_0) \times B_2 \\
 \hline
 P_4P_3P_2P_1P_0
 \end{array}$$

```

R1 <= M[0]           // load A
R2 <= M[1]           // load B
R3 <= 0               // initialize P = 0
    
```

```

(*) R4 <= R2 & 1      // R4 = lsb(B)
if (R4) R3 <= R3+R1  // if lsb(B)=1, add
R1 <= SLL(R1)        // shift A left
R2 <= SRL(R2)        // shift B right
if (R2) goto (*)     // if B!=0, loop
    
```

```

M[2] <= R3           // store P
    
```

- Load R1 with A from M[0]
- Load R2 with B from M[1]
- Initialize R3 (P) to 0
- If lsb of B = 1, P = P + A
- Shift A left one bit (0 into LSB)
- Shift B right one bit (0 into MSB)
- Repeat until B = 0
- Store R3 to M[2]

Shift and Add Multiplication

R1 \leftarrow M[0]

R2 \leftarrow M[1]

R3 \leftarrow 0

R4 \leftarrow R2 & 1

R3 \leftarrow R3 + R1

R1 \leftarrow SLL(R1)

R2 \leftarrow SRL(R2)

M[2] \leftarrow R3

R0 \leftarrow R0 - R0

R1 \leftarrow M[R0]

R2 \leftarrow M[R0+1]

R3 \leftarrow R3 - R3

R4 \leftarrow R2 & 1

R3 \leftarrow R3 + R1

R1 \leftarrow SLL(R1)

R2 \leftarrow SRL(R2)

M[R0+2] \leftarrow R3

S1

S2

S3

S4


S5

S6

S7

S8

S9

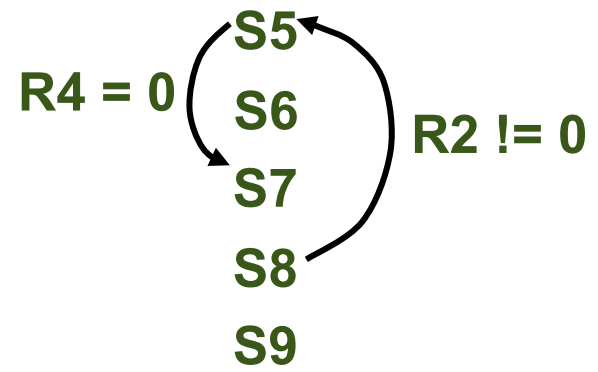


- **Can implement with a 9 state FSM**

- Inputs are the values of R4 and R2
- Outputs are the control words that carry out the above operations

Shift and Add Multiplication

- S1** $R0 \leftarrow R0 - R0$
- S2** $R1 \leftarrow M[R0]$
- S3** $R2 \leftarrow M[R0+1]$
- S4** $R3 \leftarrow R3 - R3$
- S5** $R4 \leftarrow R2 \& 1$
- S6** $R3 \leftarrow R3 + R1$
- S7** $R1 \leftarrow SLL(R1)$
- S8** $R2 \leftarrow SRL(R2)$
- S9** $M[R0+2] \leftarrow R3$

DR	SA	SB	IMM	MB	FS	MD	LD	MW
000	000	000	x	0	SUB	0	1	0
001	000	xxx	0	1	ADD	1	1	0
010	000	xxx	1	1	ADD	1	1	0
011	011	011	x	0	SUB	0	1	0
100	010	xxx	1	1	AND	0	1	0
011	011	001	x	0	ADD	0	1	0
001	001	xxx	x	x	SLL	0	1	0
010	010	xxx	x	x	SRL	0	1	0
xxx	000	011	2	1	ADD	x	0	1

 


Programmable Control Unit

- **Datapath (RF, ALU, RAM, muxes) is flexible**
- **However, Multiplier Control Unit is “hardwired”**
 - **New operation requires new state machine**
- **Programmable Control Unit**
 - **Control words still stored in ROM**
 - **State machine replaced by a *Program Counter* plus *branch operations***
 - **Flexible: Can run multiple sequences of control words (*programs*) stored in ROM**

Program Counter (PC)

- **Special register that points to the location (address) in ROM of the next control word**
- **Updated every clock cycle**
- **Sequential execution**
 - **Control words read from sequential ROM locations**
 - **PC is increased by 1 after each control word read**
- **Branch operations**
 - **Special control flow operations**
 - ***Condition code* determines whether to branch or not**
 - **If so, next ROM address is $PC + \textit{branch offset}$**

PC-Based Control Unit

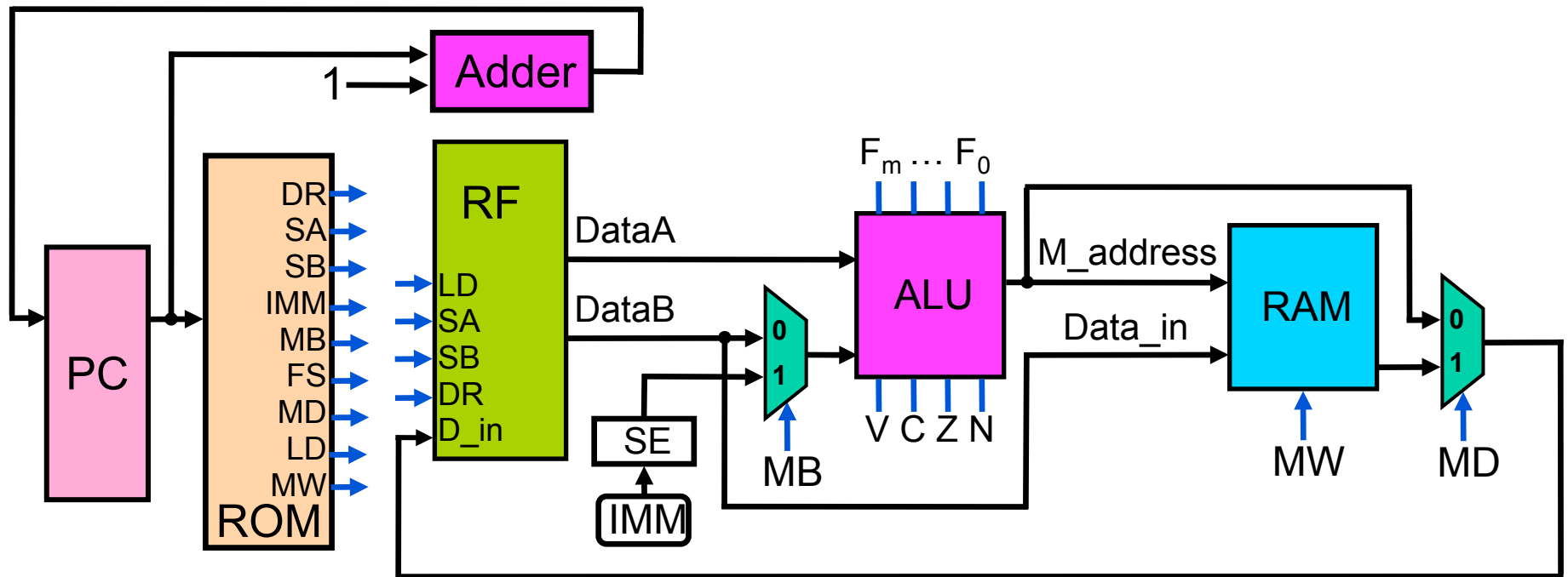

$R2 \leftarrow R0 + R1$

$R1 \leftarrow M[R2]$

$M[R2] \leftarrow R0$

$R3 \leftarrow R0 + 3$

a:

a+1:

a+2:


a+3:

DR	SA	SB	IMM	MB	FS	MD	LD	MW
010	000	001	x	0	ADD	0	1	0
001	010	xxx	0	1	ADD	1	1	0
xxx	010	000	0	1	ADD	x	0	1
011	000	xxx	3	1	ADD	0	1	0


Branch Operations

- Used to jump to a different part of the program
- Consists of a *condition* and an *offset*
- **Condition**
 - Checks to see whether the result of the last instruction met a specified criteria, such as
 - Zero (Z = 1)
 - Negative (N = 1)
- **Offset**
 - How far ahead, or back, to jump within the program if the condition is met


Branch Operations

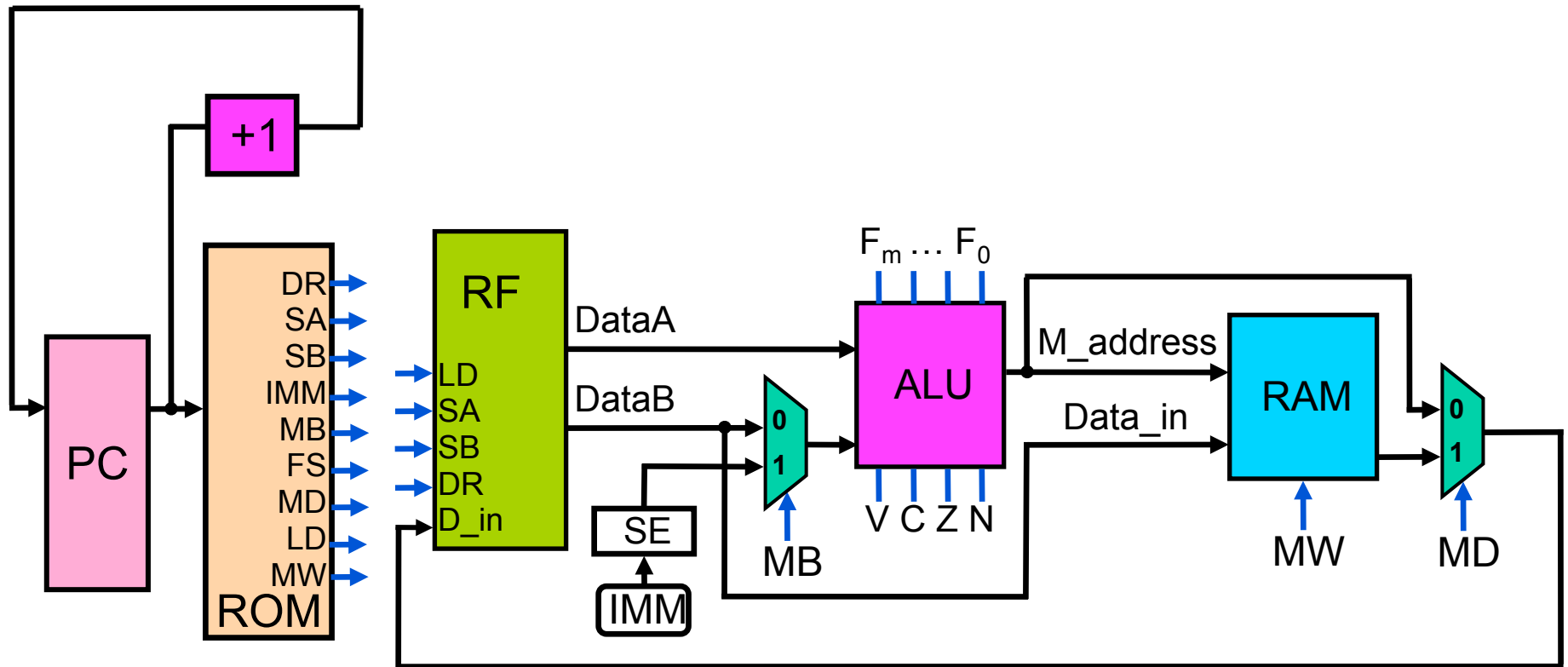


BS	MP	Branch Type
000	0	Branch Never
001	1	Branch Always
010	Z	Branch if Zero
011	Z'	Branch if Not Zero
100	N	Branch if < Zero
101	N'	Branch if >= Zero
110	C	Branch if Carry Out
111	V	Branch if Overflow

 


Branch Operations

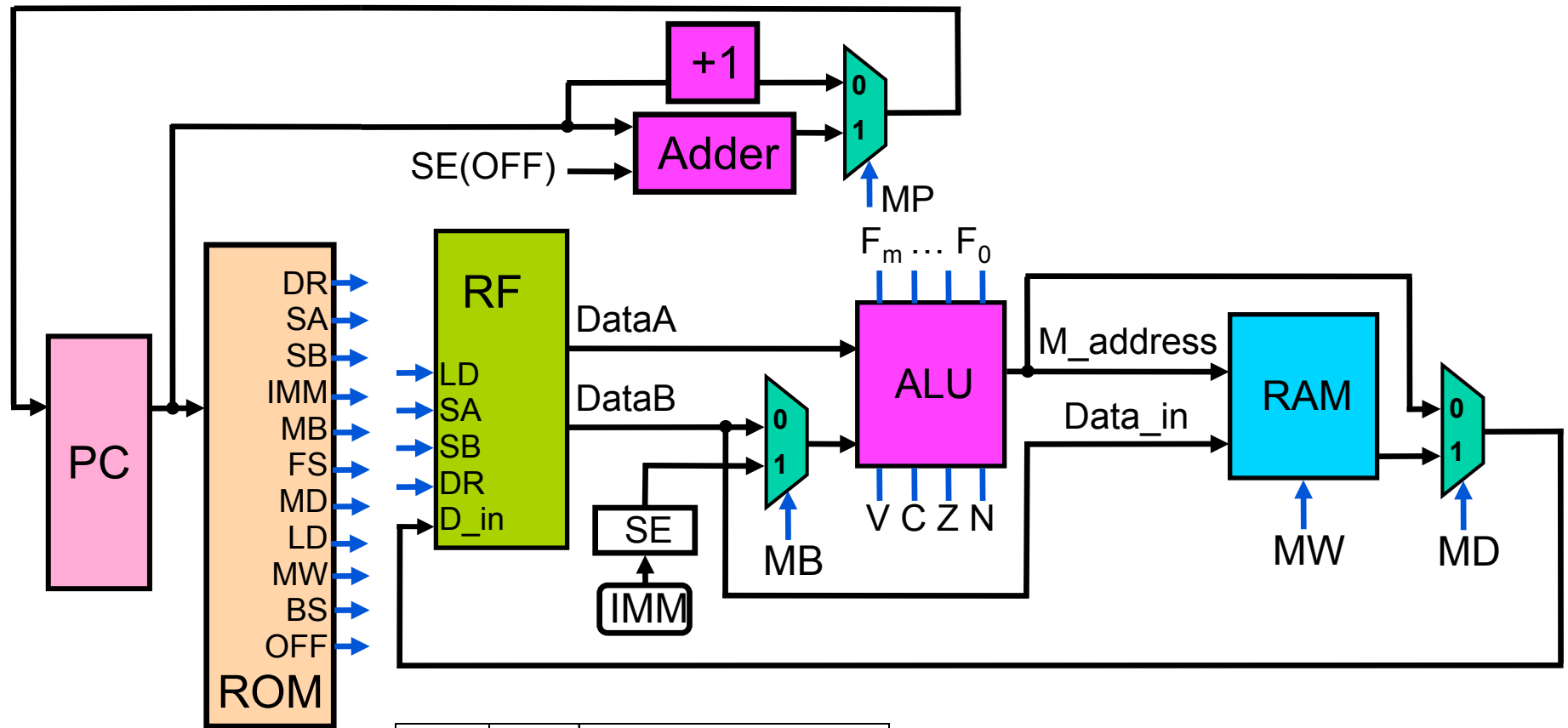

BS	MP	Branch Type
000	0	Branch Never
001	1	Branch Always
010	Z	Branch if Zero
011	Z'	Branch if Not Zero
100	N	Branch if < Zero
101	N'	Branch if >= Zero
110	C	Branch if Carry Out
111	V	Branch if Overflow

 


Branch Operations

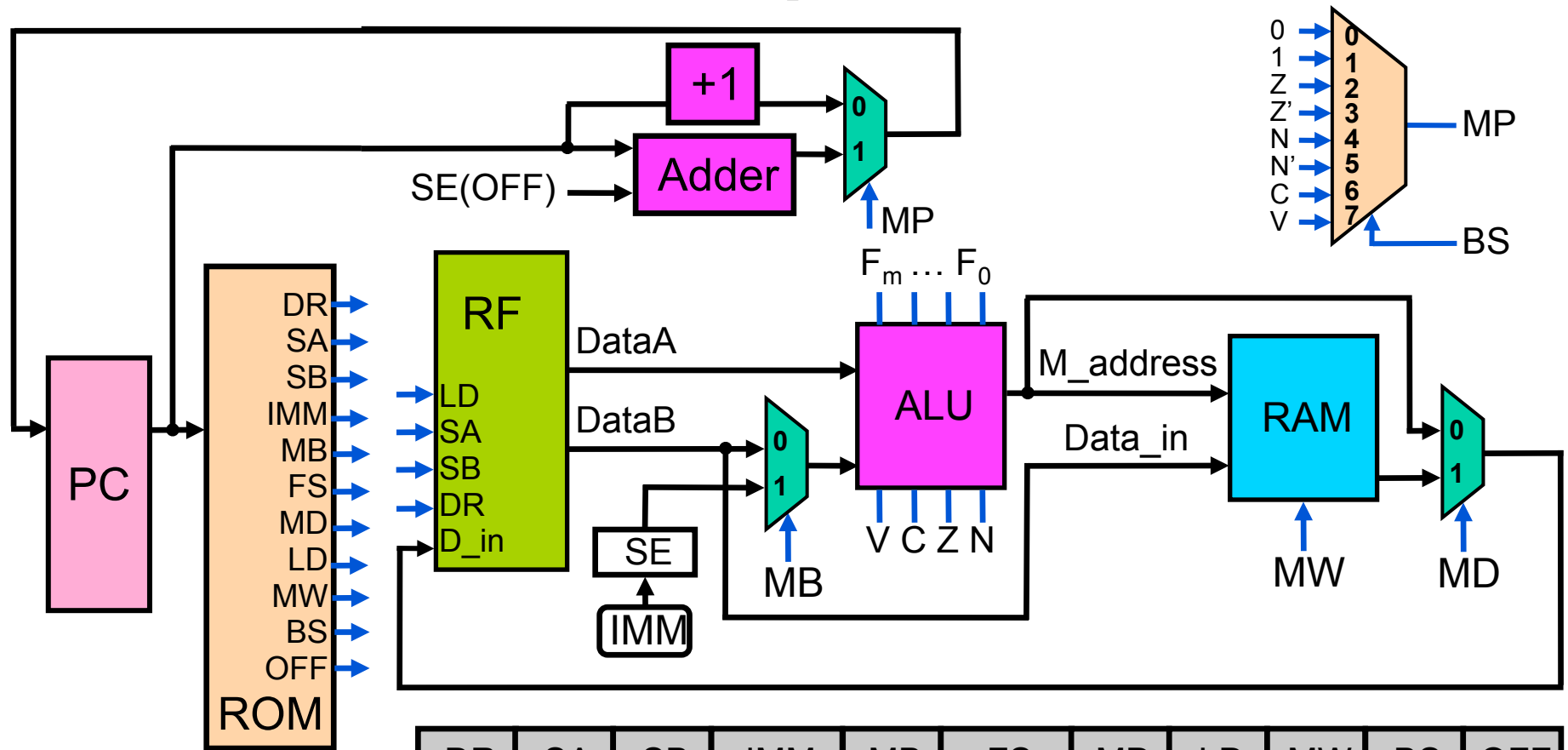

R4 <= R2 & 1
if (R4=0) goto 7
R3 <= R3 + R1
R1 <= SLL(R1)

	DR	SA	SB	IMM	MB	FS	MD	LD	MW	BS	OFF
4:	100	010	x	1	1	AND	0	1	0	000	x
5:	x	100	x	0	1	SUB	x	0	0	010	2
6:	011	011	001	x	0	ADD	0	1	0	000	x
7:	001	001	x	x	x	SLL	0	1	0	000	x

Branch Operations

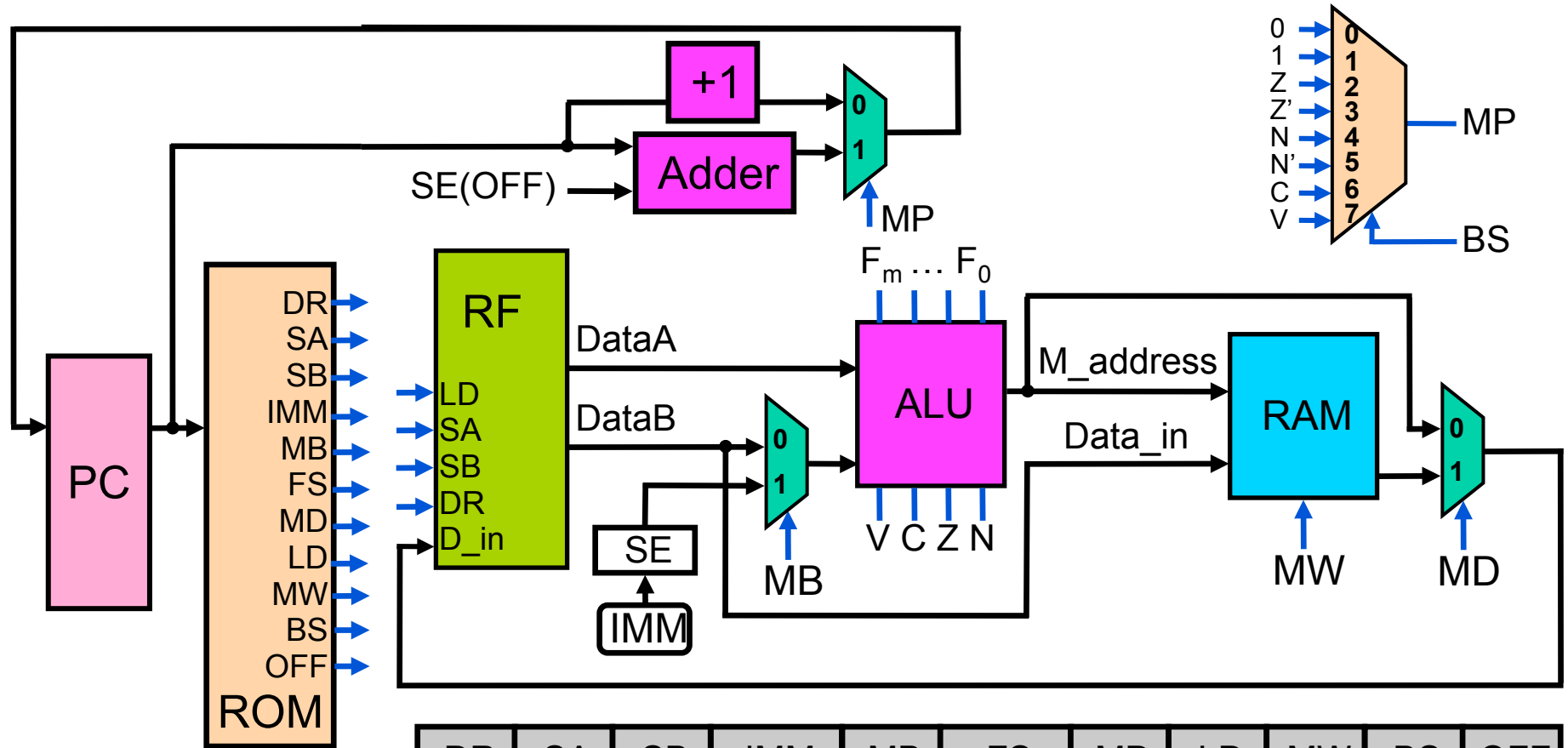

R2 <= SRL(R2)
if (R2≠0) goto 4
M[R0+2] <= R3

	DR	SA	SB	IMM	MB	FS	MD	LD	MW	BS	OFF
8:	010	010	x	x	x	SRL	0	1	0	000	x
9:	x	010	x	0	1	SUB	x	0	0	011	-5
10:	x	000	011	2	1	ADD	x	0	1	000	x

Programmable Multiplication ROM

- 0: $R0 \leq R0 - R0$
- 1: $R1 \leq M[R0]$
- 2: $R2 \leq M[R0+1]$
- 3: $R3 \leq R3 - R3$
- 4: $R4 \leq R2 \& 1$
- 5: if (R4=0) goto 7
- 6: $R3 \leq R3 + R1$
- 7: $R1 \leq SLL(R1)$
- 8: $R2 \leq SRL(R2)$
- 9: if (R2≠0) goto 4
- 10: $M[R0+2] \leq R3$

DR	SA	SB	IMM	MB	FS	MD	LD	MW	BS	OFF
000	000	000	x	0	SUB	0	1	0	000	x
001	000	x	0	1	ADD	1	1	0	000	x
010	000	x	1	1	ADD	1	1	0	000	x
011	011	011	x	0	SUB	0	1	0	000	x
100	010	x	1	1	AND	0	1	0	000	x
x	100	x	0	1	SUB	x	0	0	010	2
011	011	001	x	0	ADD	0	1	0	000	x
001	001	x	x	x	SLL	0	1	0	000	x
010	010	x	x	x	SRL	0	1	0	000	x
x	010	x	0	1	SUB	x	0	0	011	-5
x	000	011	2	1	ADD	x	0	1	000	x

Before Next Class

- H&H 7.5

Next Time

More Single Cycle Microprocessor

Pipelined Microprocessor