

Helpful readings for this homework: Nilsson and Riedel, Chapter 5, Chapter 6, and Chapter 7.

Grading Criteria


Show all work, as each problem will be graded using the grading criteria given below:

- 100% of maximum score if approach is correct and answer is also correct
- 80% of maximum score if approach is correct, but answer is incorrect due to algebraic or other math error
- 60% of maximum score if approach is mostly correct, but there is some conceptual error
- 40% of maximum score if problem has been seriously attempted, but approach is incorrect and/or there are major conceptual errors.
- 20% of maximum score if problem has been attempted, but is illegible.
- 0% of maximum score if there is no attempt to solve the problem.

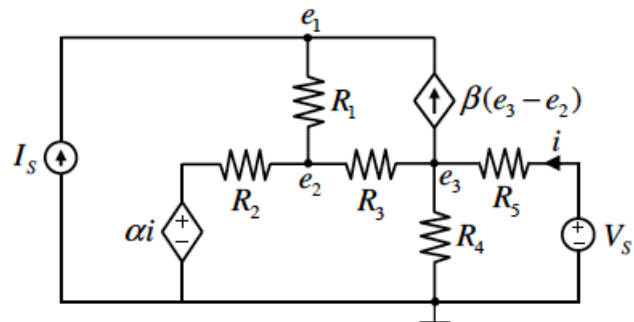Problem 3.1: ($8\frac{1}{3}$ points)

Use the node method to develop a set of simultaneous equations for the network shown on the right, which can be solved to determine the unknown node voltages. Express the set of equations in the form:


$$\mathbf{G} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \mathbf{S}$$



where \mathbf{G} is a 3x3 matrix of conductance terms and \mathbf{S} is a 3x1 vector of terms involving independent sources and constant parameters α and β . *You do not have to solve the set of equations for the node voltages.*

Problem 3.2: ($8\frac{1}{3}$ points)

For the network shown below, determine the Thevenin equivalent circuit as seen from the port defined by the terminal pair bb' . In this circuit β is a constant parameter.

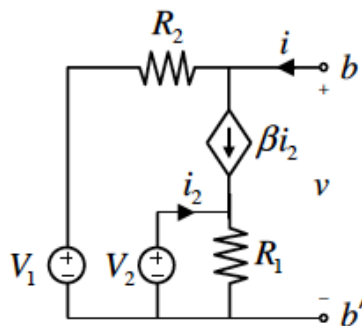


Problem 3.3: (8 $\frac{1}{3}$ points)

This problem studies the MOSFET amplifier known as the “Source Follower” (also called “Common Drain”), as shown below.

Recall from lecture that the MOSFET’s gate current $i_G = 0$, and in the saturation region (i.e., when $0 \leq v_{GS} - V_T \leq v_{DS}$), its drain current $i_D = 0.5K(v_{GS} - V_T)^2$. In this particular design, $V_S = 9\text{ V}$, $R = 1\text{ k}\Omega$, $K = 1\text{ mA/V}^2$, and $V_T = 1\text{ V}$.

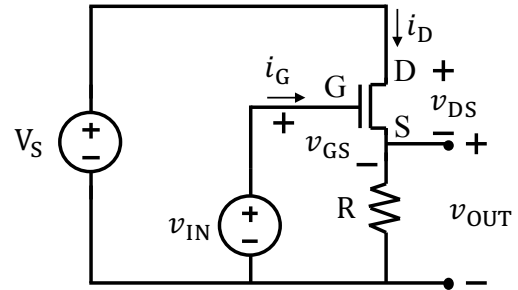- Assuming that the MOSFET operates in its saturation region, determine v_{OUT} as a function of v_{IN} . (Hint: This has two solutions, only one of which is physically possible.)
- Determine the range of v_{IN} over which the MOSFET operates in its saturation region.




For part (c), assume that $v_{IN}(t) = V_{IN} + v_{in}(t)$ and $v_{OUT}(t) = V_{OUT} + v_{out}(t)$, where V_{IN} is a constant input voltage within the range determined in part (b), V_{OUT} is the constant output voltage in response to V_{IN} , and $v_{in}(t)$ and $v_{out}(t)$ are very small amplitude time varying voltages.

- Given that $V_{IN} = 8.5\text{ V}$, draw the small-signal (linear) equivalent circuit model for the given MOSFET amplifier, and determine its small-signal gain $v_{out}(t)/v_{in}(t)$.

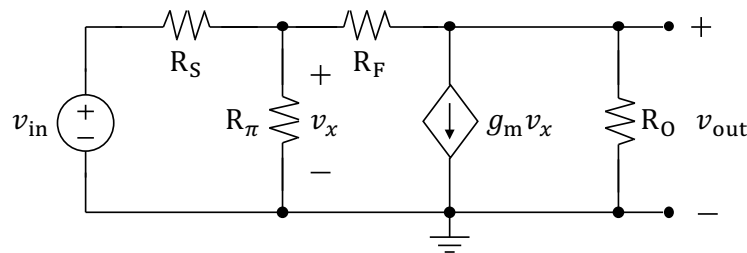Problem 3.4: (8 $\frac{1}{3}$ points)


The circuit shown below is a small-signal model for a transistor-based amplifier. Assume $R_S = 50\ \Omega$, $R_\pi = 200\ \Omega$, $R_F = 1\text{ k}\Omega$, $R_O = 200\ \Omega$, and the transconductance $g_m = 0.5\text{ S}$.



- Find v_{out} as a function of v_{in} .
- Determine and draw the Thevenin equivalent for this circuit when looking into its output port.
- Determine the value of the load resistance which when connected across its output port would extract maximum power from this circuit. Also determine the maximum extracted power $P_{out(max)}$ as a function of v_{in} .
- Determine the value of the Thevenin resistance R_{in} seen by the input voltage source v_{in} (also called input resistance). Also determine the power delivered to the circuit by the input source P_{in} as a function of v_{in} .
- Determine the maximum power gain of this amplifier ($P_{out(max)}/P_{in}$).


Problem 3.5: [Problem 5.5 from Nilsson and Riedel] ($8\frac{1}{3}$ points)

Find i_O in the circuit shown below if the op-amp is ideal.

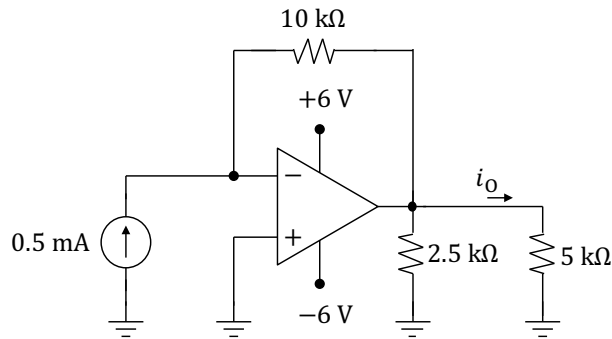

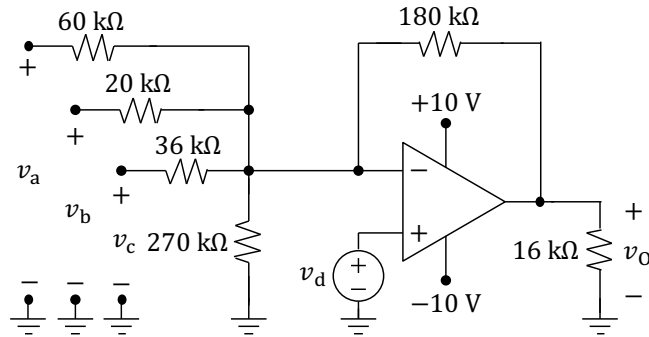Problem 3.6: [Problem 5.14 from Nilsson and Riedel] ($8\frac{1}{3}$ points)

The op-amp in the circuit shown below is ideal.




- Find v_o if $v_a = 3$ V, $v_b = 9$ V, $v_c = 5$ V, and $v_d = 6$ V.
- Assume v_a , v_b , and v_d retain their values as given in part (a). Specify the range of v_c such that the op-amp operates within its linear region.

Problem 3.7: [Problem 5.40 from Nilsson and Riedel] ($8\frac{1}{3}$ points)


Assume that the ideal op-amp in the circuit below is operating in its linear region.

- Calculate the power delivered to the 16 kΩ resistor.
- Repeat part (a) with the op-amp removed from the circuit, that is, with the 16 kΩ resistor connected in series with the voltage source and the 48 kΩ resistor.
- Find the ratio of the power found in part (a) to that found in part (b).
- Does the insertion of the op-amp between the source and the load serve a useful purpose? Explain.

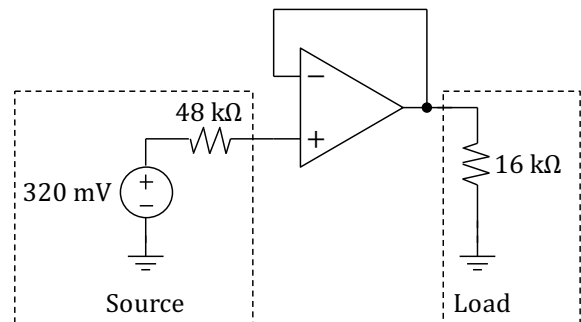

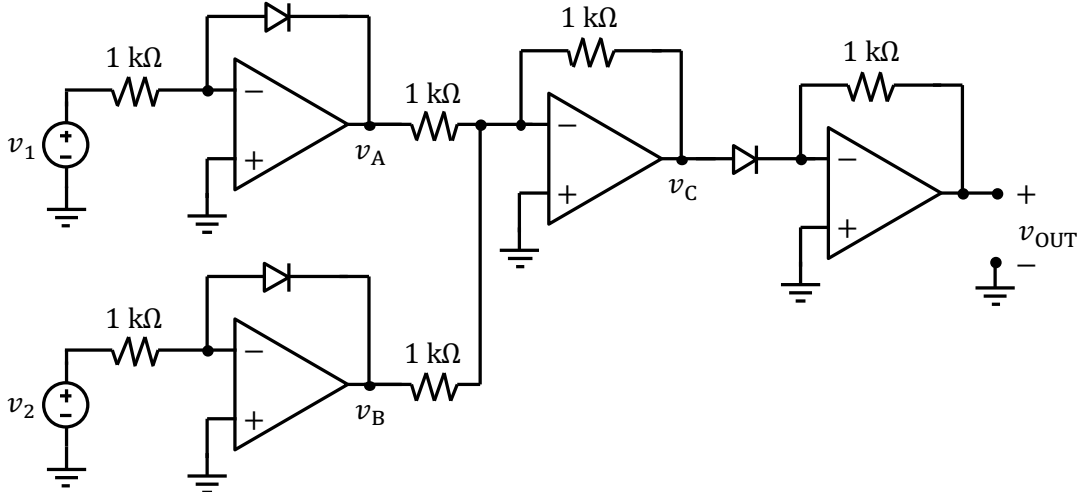Problem 3.8: ($8\frac{1}{3}$ points)

Consider the op-amp circuit shown below in which the diodes have the following i - v relationship:
 $i_D = I_0 e^{(v_D/V_T)}$.




Assume that $v_1 > 0$ and $v_2 > 0$, and remember that: $\ln(x) + \ln(y) = \ln(xy)$.

- Determine v_A and v_B in terms of v_1 and v_2 .
- Determine v_C in terms of v_1 and v_2 .
- Determine v_{OUT} in terms of v_1 and v_2 . What function does this circuit implement?

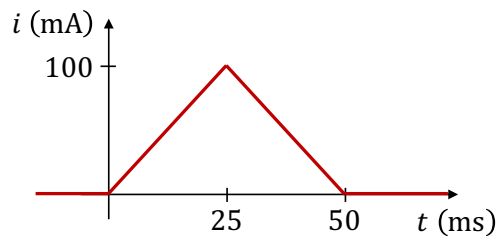Problem 3.9: [Problem 6.2 from Nilsson and Riedel] ($8\frac{1}{3}$ points)


The triangular current pulse shown below is applied to a 500 mH inductor.



- Write the expressions that describe $i(t)$ in the four time intervals: (i) $t < 0$, (ii) $0 \leq t \leq 25$ ms, (iii) $25 \text{ ms} \leq t \leq 50$ ms, and (iv) $t > 50$ ms.
- Derive the expressions for the inductor voltage, power, and energy. Use the passive sign convention.

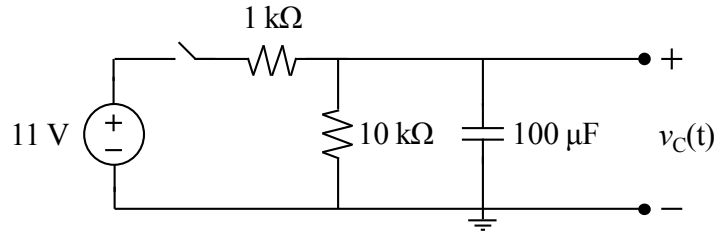Problem 3.10: ($8\frac{1}{3}$ points)


In the circuit shown below, the switch has been left at the open (i.e., off) position for a long time. The switch is closed (i.e., turned on) at time $t = 0$ and then opened (i.e., turned off) again at $t = 1$ second.



- Find the capacitor voltage $v_C(t)$ for $0 \leq t \leq 1$ second.
- Find the capacitor voltage $v_C(t)$ for $t \geq 1$ second.
- Plot the capacitor voltage $v_C(t)$ for $0 \leq t \leq 6$ seconds.

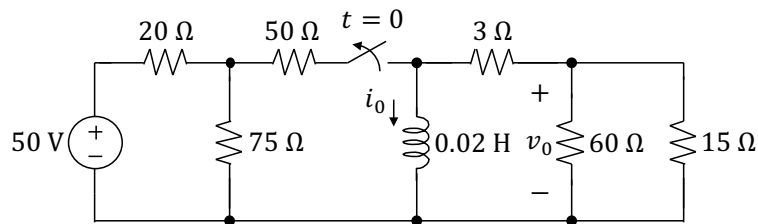Problem 3.11: [Problem 7.2 from Nilsson and Riedel] ($8\frac{1}{3}$ points)


The switch in the circuit shown below has been closed for a long time. At $t = 0$ the switch is opened.



- Write the expression for $i_0(t)$ for $t \geq 0$.
- Write the expression for $v_0(t)$ for $t \geq 0^+$.

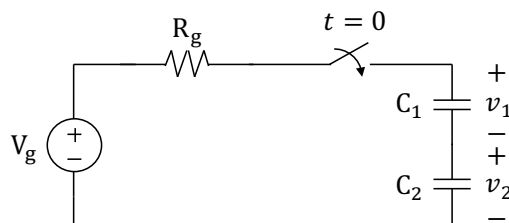Problem 3.12: [Problem 7.66 from Nilsson and Riedel] ($8\frac{1}{3}$ points)

There is no energy stored in the capacitors C_1 and C_2 at the time the switch is closed in the circuit shown below.



- Derive the expressions for $v_1(t)$ and $v_2(t)$ for $t \geq 0$.
- Use the expressions derived in part (a) to find $v_1(\infty)$ and $v_2(\infty)$.