

Helpful readings for this homework: Nilsson and Riedel, Chapter 15, Chapter 12, Chapter 13 and Chapter 9.


Grading Criteria

Show all work, as each problem will be graded using the grading criteria given below:

- 100% of maximum score if approach is correct and answer is also correct
- 80% of maximum score if approach is correct, but answer is incorrect due to algebraic or other math error
- 60% of maximum score if approach is mostly correct, but there is some conceptual error
- 40% of maximum score if problem has been seriously attempted, but approach is incorrect and/or there are major conceptual errors.
- 20% of maximum score if problem has been attempted, but is illegible.
- 0% of maximum score if there is no attempt to solve the problem.

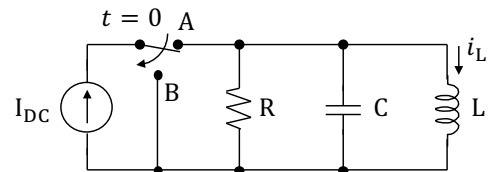Problem 6.1: [Problem 12.28 from Nilsson and Riedel] ($8\frac{1}{3}$ points)

The switch in the circuit shown to the right has been in position A for a long time. At time $t = 0$, the switch moves instantaneously to position B.



- Derive the differential equation that governs the behavior of the inductor current $i_L(t)$ for $t \geq 0^+$.
- Determine the value of the inductor current at $t = 0^-$, i.e., $i_L(0^-)$, and the value of the time derivative of the inductor current at $t = 0^-$, i.e., $i_L'(0^-)$.
- Using s -domain analysis (i.e., Laplace Transforms), show that:

$$I_L(s) = \frac{I_{DC} \left(s + \frac{1}{RC} \right)}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

Problem 6.2: [Problem 12.40(a) from Nilsson and Riedel] ($8\frac{1}{3}$ points)

Determine the time-domain function $f(t)$ associated with the following s -domain function:

$$F(s) = \frac{6(s + 10)}{(s + 5)(s + 8)}$$

Hint: Use partial fraction expansion and a table of Laplace Transform pairs.


Problem 6.3: [Problem 12.41(b) from Nilsson and Riedel] ($8\frac{1}{3}$ points)

Determine the time-domain function $f(t)$ associated with the following s -domain function:

$$F(s) = \frac{-s^2 + 52s + 445}{s(s^2 + 10s + 89)}$$


Problem 6.4: ($8\frac{1}{3}$ points)

In the network to the right, the voltage source delivers an impulse of area Q_0R volt-seconds at time $t = 0$. Using s -domain analysis, determine an expression for the capacitor voltage $v_C(t)$ for $t > 0$.

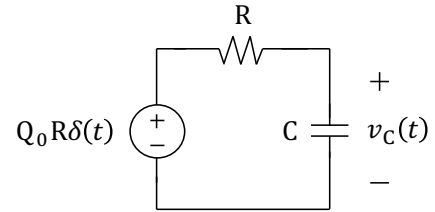

Problem 6.5: ($8\frac{1}{3}$ points)


In the circuit to the right, the current source delivers an impulse of area Q_0 coulombs at time $t = 0$, and the voltage source delivers an impulse of area Λ_0 volt-seconds at time $t = 0$. Using superposition in the s -domain, determine an expression for the capacitor voltage $v_C(t)$ for $t > 0$.

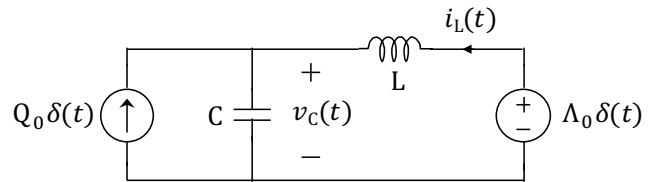

Problem 6.6: [Problem 13.7 from Nilsson and Riedel] ($8\frac{1}{3}$ points)

Consider the circuit shown on the right.


- Determine the impedance $Z_{ab}(s)$ seen looking into the terminals a,b of the circuit.
- Determine the values of the poles and zeros of $Z_{ab}(s)$.

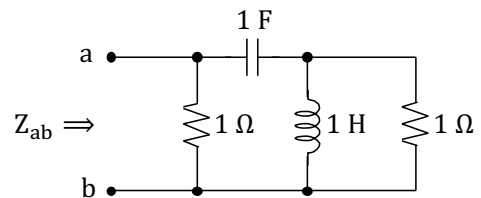

Problem 6.7: [Problem 13.17 from Nilsson and Riedel] ($8\frac{1}{3}$ points)

Consider the circuit shown on the right.


- Using s -domain analysis, determine the expression for $V_O(s)$.
- Use the s -domain expression derived in (a) to predict the initial- and final-values of $v_O(t)$.
- Determine the time-domain expression for $v_O(t)$.

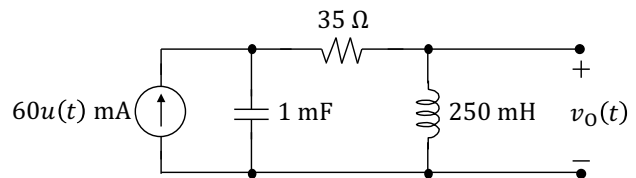

Problem 6.8: [Problem 13.54 from Nilsson and Riedel] ($8\frac{1}{3}$ points)


The op-amp in the circuit to the right is ideal.

- Determine an expression for the transfer function $H(s) = V_O(s)/V_I(s)$ in terms of R_1 , R_2 , C_1 , C_2 and s .
- Determine the numerical values of the poles and zeros of $H(s)$.
- Sketch the magnitude Bode plot of this circuit's transfer function $H(j\omega)$, and identify whether it is a low-pass, band-pass, or high-pass filter.

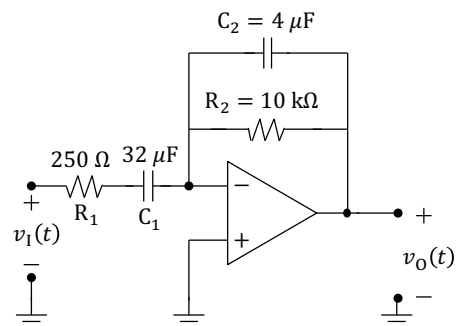

Problem 6.9: ($8\frac{1}{3}$ points)


For the circuit shown on the right, determine an expression for the impedance $Z_{ab}(s)$ seen looking into its terminals a,b in terms of R_s , R_p , L , C and s .

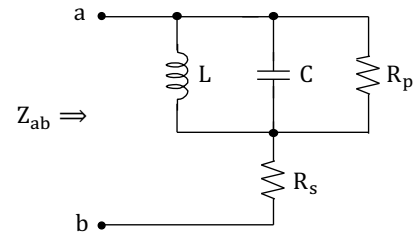

Problem 6.10: [Problem 13.52 from Nilsson and Riedel] ($8\frac{1}{3}$ points)

Consider the circuit shown to the right.


- (a) Determine an expression for its transfer function $H(s) = V_O(s)/V_I(s)$ in terms of R , C and s .
- (b) Determine the numerical values of the poles and zeros of $H(s)$, and show these on the complex s -plane.
- (c) Sketch the magnitude and phase Bode plot of this circuit's transfer function $H(j\omega)$.

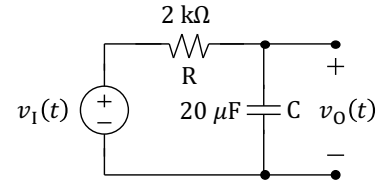

Problem 6.11: ($8\frac{1}{3}$ points)

Consider the circuit shown to the right.

- (a) Determine an expression for its transfer function $H(s) = V_O(s)/V_I(s)$ in terms of R , L , C and s .
- (b) Determine the numerical values of the poles and zeros of $H(s)$, and show these on the complex s -plane.
- (c) Sketch the magnitude and phase Bode plot of this circuit's transfer function $H(j\omega)$.

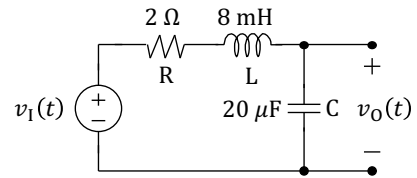

Problem 6.12: [Problem 9.6 from Nilsson and Riedel] ($8\frac{1}{3}$ points)

The root-mean-square (rms) value of the sinusoidal voltage supplied to the convenience outlet of a home in Scotland is 240 V. What is the maximum value of the voltage at the outlet?