

Prelab Problem 5.1: Input and output sinusoids

Figure 1 shows the input and output sinusoidal voltage waveforms for a two-port linear network. Since the network is linear both sinusoids have the same frequency.

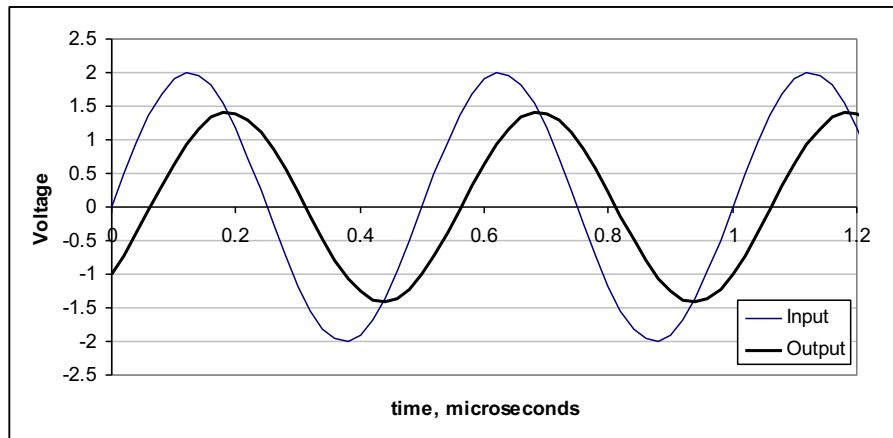


Fig. 1. Input and output sinusoidal waveforms for a two-port linear network.

From these two overlaid sinusoidal voltage waveforms, estimate:

- The frequency of the sinusoidal waveforms in Hz and in radians per second.
- The ratio of the amplitude of the output waveform to the amplitude of the input waveform.
- The phase of the output waveform relative to the phase of the input waveform. (Note that time delay corresponds to negative phase.)
- Express the input and output voltage waveforms as phasors (i.e., as $Ae^{j\phi}$, where A is the amplitude and ϕ is the phase; note you can arbitrarily choose the phase of the input voltage waveform as zero).
- Express the transformation \hat{H} from input to output voltage as a phasor, i.e., determine $\hat{H} \equiv \hat{V}_{\text{out}}/\hat{V}_{\text{in}}$, where \hat{V}_{out} is the output voltage phasor and \hat{V}_{in} is the input voltage phasor. Also convert \hat{H} into a complex number in Cartesian coordinates $\hat{H} = a + jb$, i.e., determine a and b . (Hint: You can use Euler's Formula: $e^{j\phi} = \cos \phi + j \sin \phi$).

Prelab Problem 5.2: Impedance and voltage-division characteristics of RLC networks

In lab 5, you will be analyzing the impedance and voltage-division characteristics of several two-port “black box” networks to reverse engineer them. To gain insights helpful for lab 5, here you will perform similar analysis on the four different two-port networks shown in Fig. 2. In Fig. 2, network A is purely resistive, network B has a capacitor in addition to two resistors, network C has an inductor in addition to two resistors, and network D has an inductor, a capacitor and a resistor.

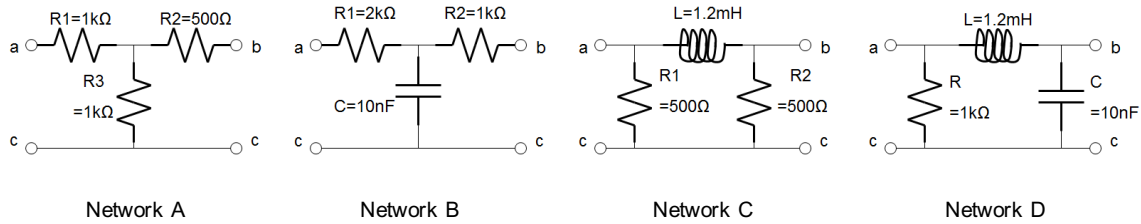


Fig. 2. Four example two-port linear networks.

For each network of Fig. 2, do the following:

- (a) Determine the impedance across each pair of terminals, i.e., determine Z_{ac} , Z_{bc} and Z_{ab} ? (Note that in general for an RLC network, impedance is a complex number and is a function of the applied sinusoid's frequency $\omega = 2\pi f$). Also compute the values of these three impedances at $f = 0$ Hz.

The two-port networks of Fig. 2 are driven by a sinusoidal voltage source $v_1(t) = 1 \text{ V} \cdot \cos(\omega t)$ ($\hat{V}_1 = 1e^{j0}$) applied to port 1 (across terminals a and c), as shown in Fig. 3(a). For each network of Fig. 2, use voltage divider analysis to do the following:

- (b) Determine the magnitude $|\hat{V}_2|$ and phase ϕ_2 of the voltage \hat{V}_2 at port 2 (across terminals b and c) as a functions of ω . Also compute the values of $|\hat{V}_2|$ and ϕ_2 at $f = 1$ kHz and $f = 100$ kHz. Also find the frequency in the range $1 \text{ kHz} < f < 100 \text{ kHz}$, where $|\hat{V}_2|$ is maximum.

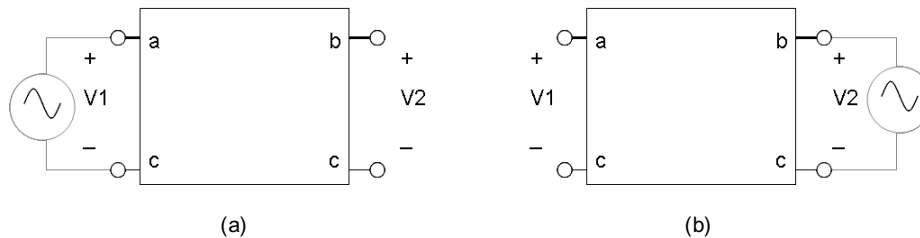


Fig. 3. Two-port network driven by a sinusoidal voltage source applied to: (a) port 1 and (b) port 2.

The two-port networks of Fig. 2 are driven by a sinusoidal voltage source $v_2(t) = 1 \text{ V} \cdot \cos(\omega t)$ ($\hat{V}_2 = 1e^{j0}$) applied to port 2 (across terminals b and c), as shown in Fig. 3(b). For each network of Fig. 2, use voltage divider analysis to do the following:

- (c) Determine the magnitude $|\hat{V}_1|$ and phase ϕ_1 of the voltage \hat{V}_1 at port 1 (across terminals a and c) as a functions of ω . Also compute the values of $|\hat{V}_1|$ and ϕ_1 at $f = 1$ kHz and $f = 100$ kHz. Also find the frequency in the range $1 \text{ kHz} < f < 100 \text{ kHz}$, where $|\hat{V}_1|$ is maximum.
- (d) Based on the zero-frequency impedances and voltage divider results for network B, describe how you would extract the values of R_1 and R_2 in network B.
- (e) Based on the zero-frequency impedances and voltage divider results for network C, describe how you would extract the values of R_1 and R_2 in network C.
- (f) Based on the zero-frequency impedances and voltage divider results for networks D and C, describe how you would distinguish network D from network C, and how you would extract the values of each component in network D.