

# Homework 1


Deliver to Homework Dropbox in PHL 2nd floor, February 9, 2018 no later than 6:00pm

Name: \_\_\_\_\_ NetID: \_\_\_\_\_

**Important:** You may collaborate with other students on this homework assignment, but each student must turn in their own assignment and in their own writing. In addition, **you must specify the names of all your collaborators** and all the resources used to solve the homework assignment. Failing to specify your collaborator(s) or resources **will** result in a 20% penalty. Late homework will receive a 20% penalty for every day late (including submissions made after 6:00pm); homework more than 3 days late will not be accepted.

**Get bonus points!** Follow these instructions to receive **5 bonus points**: Put your name and NetID on the first page. All your answers must be within the blank spaces of this homework. You have to print the homework two-sided and staple it prior to submission in the top-left corner. In the exceptional case you have source code, Cadence schematics, or plots you want to include in your submission, you are allowed to add *one* printed page per plot *after* the associated question; do not forget to clearly label each additional sheet. *Clearly mark all your final answers.*


<b>Question</b>	<b>Maximum Points</b>	<b>Points</b>
1	15	
2	20	
3	30	
4	35	
Follow the rules	+5 bonus	
<b>Total</b>	<b>100 (+5 bonus)</b>	

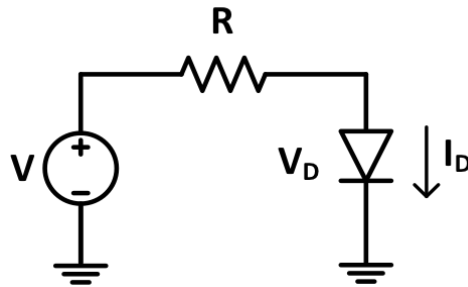**Problem 1 (15pts): “Fun” with a Diode**

1. Find the supply voltage  $V$  that needs to be provided so that the voltage across the diode,  $V_D$ , is equal to 1.6 V. Use  $R = 3\text{k}\Omega$  and  $n = 1.8$ ,  $I_s = 10^{-18}\text{A}$ , and  $\phi_T = 26\text{mV}$ . Use the ideal Shockley diode equation from the lecture notes.

2. Assume  $R = 500\Omega$  and  $V = 9V$ , and the diode parameters above. Compute  $V_D$ . Compute this voltage graphically and/or numerically but without the use of scientific software.

### Problem 2 (20pts): Transistor Chain

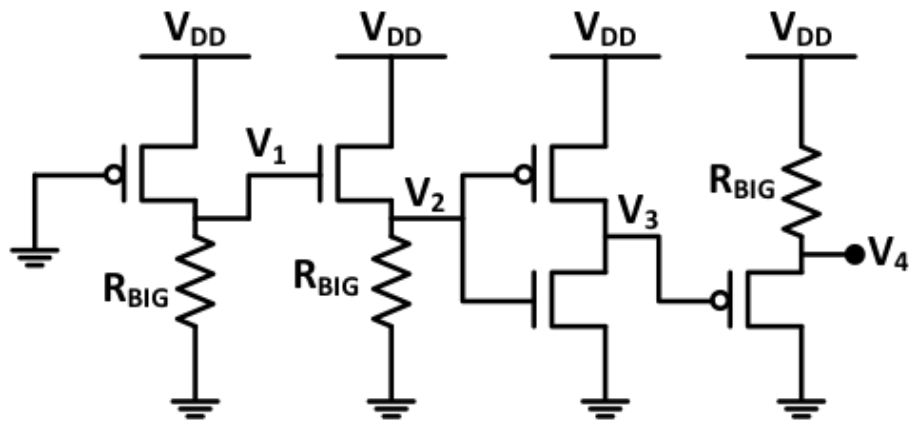


- Find all voltages  $V_1$  to  $V_4$  in the following circuit using the switch models introduced in class. Assume  $R_{ON} < R_{BIG} < R_{OFF}$  and  $V_{DD} > 2|V_{Tp}|$  and  $V_{Tn} < |V_{Tp}|$ .

2. Replace all NMOS with PMOS and vice versa. Find all voltages  $V_1$  to  $V_4$ .

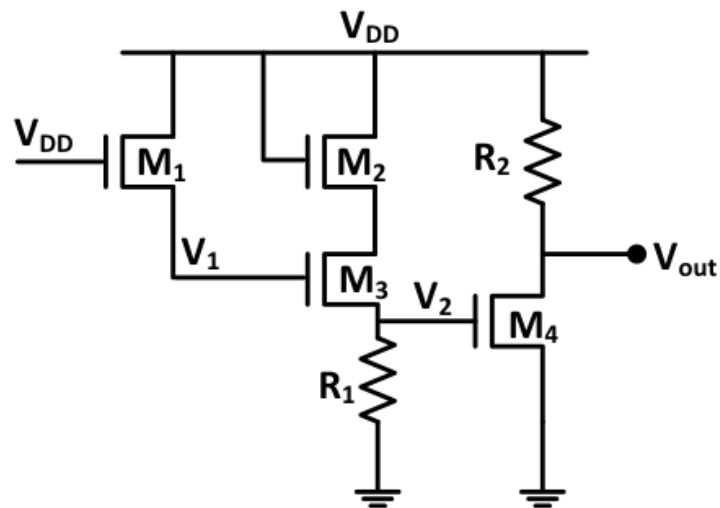**Problem 3 (30pts): Read the Hint**

Determine the voltages  $V_1$ ,  $V_2$ , and  $V_{out}$ . Ignore the body effect and channel-length modulation. Note that transistor  $M_2$  is diode connected and  $M_3$  is biased at the onset of saturation (meaning  $M_3$  operates at the boundary of saturation and the linear regime). Size of  $M_3$  is unknown and the rest of transistors are sized by  $W/L$  provided below. *Hint: assume the switch model for  $M_1$ .*



$$\begin{aligned} V_{DD} &= 1V \\ V_T &= 0.25V \\ \lambda, \gamma &= 0 \end{aligned}$$

$$\begin{aligned} \mu_n C_{ox} &= 50 \mu A/V^2 \\ W/L &= 4m/0.5m \end{aligned}$$

$$\begin{aligned} R_1 &= 30k\Omega \\ R_2 &= 250k\Omega \end{aligned}$$





## Problem 4 (35pts): DIBL a Little in Cadence

Make the schematic in Cadence with the minimum dimensions ( $W = 120\text{nm}$ ,  $L = 100\text{nm}$ ). Turn in three plots total, one plot for each part, i.e., overlay parametric sweeps onto one plot. *Hint: Before solving this problem, finish Part 1 of Lab 1.*

To save the threshold voltage for DC sweeps, create a file using gedit called "saveop.scs". Add the line "save NM0:all" and this will save all the DC operating point information. In your ADE go to Setup→Model Libraries and add saveop.scs.

Id results can be plotted directly. For threshold voltage results, go to Tools→Results Browser, find the "dc" folder and select NM0/Vth.

### 1. Plot Id vs. VDS


Use DC analysis (dc analysis→Design Variable) to set up a sweep of VDS from 0V to 1.2V and plot Id (Outputs→Save All, select device currents). When setting up the Id plot, make sure to select the transistor as an output variable so that Id actually plots. Use a parametric sweep (Tools→Parametric Analysis) with 4 steps for VGS (0V, 0.4V, 0.8V, 1.2V). Press the run button on the parametric sweep screen.

### 2. Plot VT vs. L

Sweep length from 100n to 5 $\mu$  (dc analysis→Component Parameter) and plot threshold voltage. Use a parametric sweep with 4 VDS voltages (0V, 0.4V, 0.8V, 1.2V).
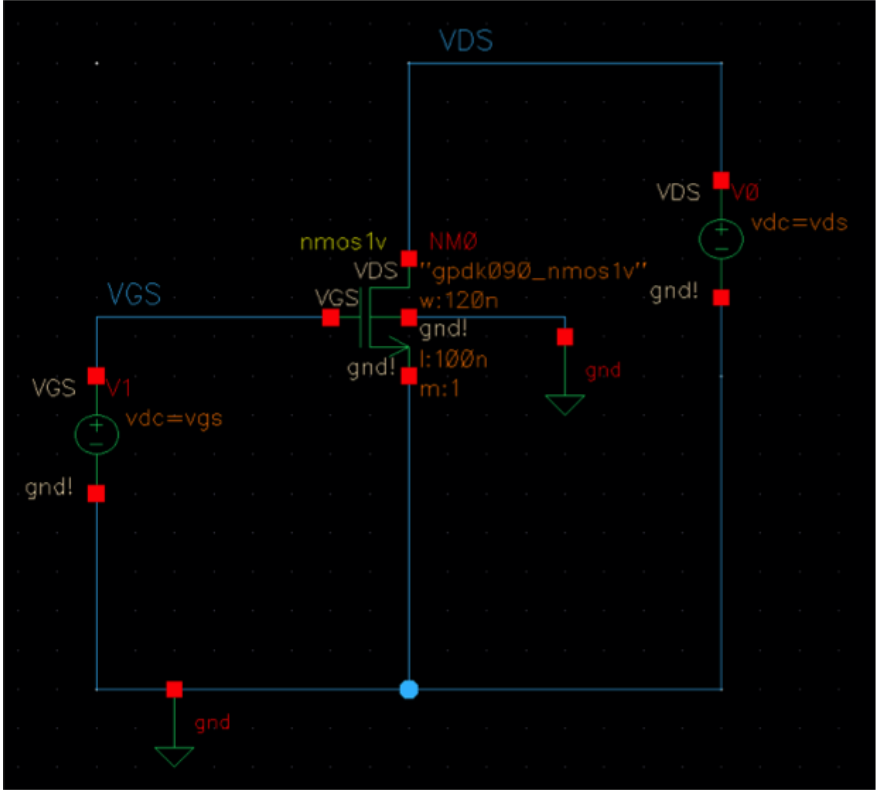
### 3. Plot VT vs. VDS

Sweep VDS from 0V to 1.2V and plot threshold voltage. Use a parametric sweep with 4 steps for VGS (0V, 0.4V, 0.8V, 1.2V).



Last updated: August 20, 2018 by Oscar Castañeda/RG/cs