

ECE4740: Digital VLSI Design



Lecture 6: Inverter sizing

193

Very important concepts


Brief timing recap

194

 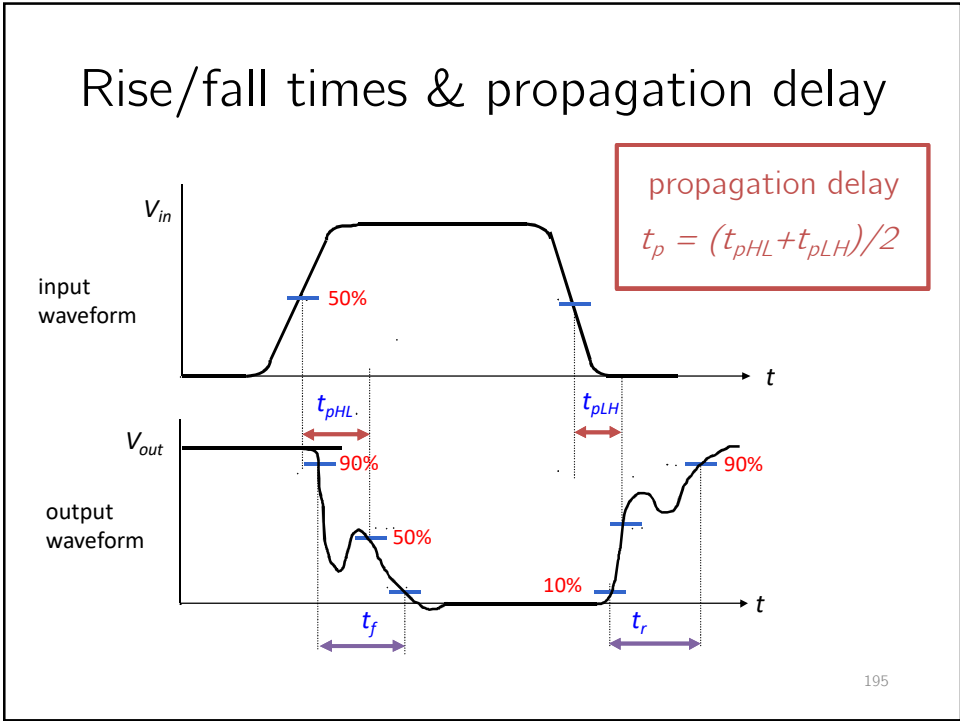

First-order analysis: extract R_{eq}

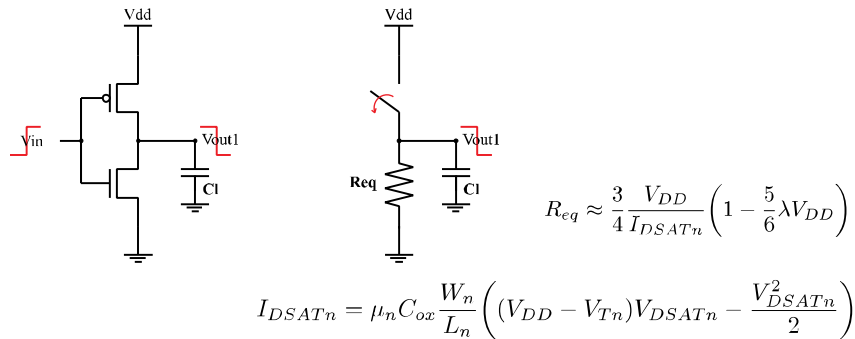- Approximations required as $C_L(v)$ and $i(v)$ are non-linear and voltage v dependent



197

Use RC circuit to model t_{pHL}

- Decay time from 100% to 50% is

$$t_{pHL} = \ln(2) R_{eqn} C_L \approx 0.69 R_{eqn} C_L$$

- Same can be obtained for low-to-high time

$$t_{pLH} = \ln(2) R_{eqp} C_L \approx 0.69 R_{eqp} C_L$$

- Propagation delay:

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} \approx 0.69 C_L \left(\frac{R_{eqn} + R_{eqp}}{2} \right)$$

198

Increase both W_n and W_p !

Inverter sizing

199

Split load capacitance C_L

$$t_p \approx 0.69R_{eq}(C_{int} + C_{ext})$$

intrinsic output capacitances from self-loading etc. (diffusion, Miller)

extrinsic capacitances: fan-out and wiring

- Just rewrite as:

$$t_p \approx \underbrace{0.69R_{eq}C_{int}}_{t_{p0}} \left(1 + \frac{C_{ext}}{C_{int}} \right)$$

"unloaded" propagation delay

effect on propagation delay caused by extrinsic capacitances

assume that NMOS and PMOS are sized such that rise and fall times are equivalent

200

Impact of sizing factor S

$$t_p \approx 0.69R_{eq}C_{int} \left(1 + \frac{C_{ext}}{C_{int}} \right)$$

- Intrinsic capacitances: $C_{int} = SC_{ref}$
- Gate resistance: $R_{eq} = R_{ref}/S$

resistance of a
unit-sized device



capacitance of a
unit-sized device

- Leads to:

$$t_p \approx 0.69R_{ref}C_{ref} \left(1 + \frac{C_{ext}}{SC_{ref}} \right)$$

201

An equivalent view

  


- Propagation delay: $t_p = 0.69R_{eq}(C_{int} + C_{ext})$
- Simplifying: $t_p = 0.69 \frac{R_{ref}}{S} (C_{ref}S + C_{ext})$
 $= 0.69R_{ref}C_{ref} \left(1 + \frac{C_{ext}}{SC_{ref}} \right)$

202

What exactly is “S”?

 - The sizing factor is how much larger you make the widths of NMOS **and** PMOS
 - You usually keep the PMOS:NMOS ratio fixed
 - Gate lengths L usually kept at the minimum



**S=2 corresponds to
2Wp and 2Wn**

203

Impact of sizing S (cont'd)


$$t_p \approx \underbrace{0.69 R_{ref} C_{ref}}_{\text{intrinsic delay of inverter: } t_{p0}} \left(1 + \frac{C_{ext}}{S C_{ref}} \right)$$

intrinsic delay
of inverter: t_{p0}

- Intrinsic delay of gate independent of S
 - no load means no effect on propagation delay
- **Making S large, eliminates effect of load**
 - at the cost of inverter area!
 - **and it will affect the load of the preceding logic!**

204

Example: Sizing impact* on t_p

 

large improvement
already achieved for $S=5$

self loading
(intrinsic capacitance
dominates) \rightarrow not
much gain anymore

Image taken from:
http://bwrcs.eecs.berkeley.edu/Courses/icdesign/ee141_f01/Notes/chapter5.pdf

*for a fixed load!

205


A more relevant case

Sizing a chain of inverters

206

Sizing a chain of inverters

 - For isolated inverter: Increasing S **reduces delay** but also **increases input capacitance**
 - not very useful in practice!
- **More relevant case:** chain of inverters:



207

It's a trade-off

- **Sizing up an inverter reduces delay, but will also increase its input capacitance!**
- Intrinsic capacitance C_{int} proportional to gate capacitance: $C_{int} = \gamma C_g$

$$t_p \approx \underbrace{0.69 R_{eq} C_{int}}_{=t_{p0}} \left(1 + \frac{C_{ext}}{C_{int}} \right)$$

- γ is technology dependent (and about 1)

208

The effective fan-out f


- Delay of an inverter: a function of the ratio between external load and its input cap!

$$t_p \approx t_{p0} \left(1 + \frac{C_{ext}}{\gamma C_g} \right) = t_{p0} (1 + f/\gamma)$$

- Effective fan out: $f = \frac{C_{ext}}{C_g}$
- The goal is to minimize the delay through the entire inverter chain

209

Chain of N inverters

 

- Delay of j^{th} inverter: $t_{p,j} = t_{p0} \left(1 + \frac{C_{g,j+1}}{\gamma C_{g,j}} \right)$
- Total delay is: $t_p = \sum_{j=1}^N t_{p,j}$
- Assume: $C_{g,N+1} = C_L$
- Optimality conditions: $\delta t_p / \delta C_{g,j} = 0$

210

Image adapted from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Optimum size of inverter

$$\frac{\delta}{\delta C_{g,j}} \left(1 + \frac{C_{g,j}}{\gamma C_{g,j-1}} \right) + \left(1 + \frac{C_{g,j+1}}{\gamma C_{g,j}} \right) = 0$$

- Optimum size of each inverter is **geometric mean** of neighbor's sizes!

$$\frac{C_{g,j}}{C_{g,j-1}} = \frac{C_{g,j+1}}{C_{g,j}} \quad C_{g,j} = \sqrt{C_{g,j-1} C_{g,j+1}}$$

211

Implications

$$\frac{C_{g,j}}{C_{g,j-1}} = \frac{C_{g,j+1}}{C_{g,j}} = f_{opt} \quad \longrightarrow \quad C_{g,j+1} = f_{opt} C_{g,j}$$

- Each inverter should be sized up by same factor f_{opt} compared to preceding gate

$$C_L = f_{opt}^N C_{g,1} \quad \text{WHY?}$$

212

Implications (cont'd)

- With $f_{opt} = \sqrt[N]{C_L/C_{g,1}} = \sqrt[N]{F}$

the minimum (total) delay is


$$t_{p,min} = Nt_{p0}(1 + \sqrt[N]{F}/\gamma)$$

- Simply a result of

$$t_p = \sum_{j=1}^N t_{p,j} \quad t_{p,j} = t_{p0}(1 + f_{opt}/\gamma)$$

213

Example: simple chain

 

- $F=C_L/C_1$ has to be evenly distributed across $N=3$ stages: $f_{opt} = \sqrt[3]{8} = 2$

$$t_{p,min} = 3t_{p0}(1 + \sqrt[3]{8}/\gamma)$$

214

Optimal number of stages N_{opt}

$$t_{p,min} = Nt_{p0}(1 + \sqrt[N]{F}/\gamma)$$

- There is a trade-off
 - too many stages: intrinsic delay dominates
 - too few stages: effective fan-out dominates

$$\frac{\delta}{\delta N} N(\gamma + \sqrt[N]{F}) = 0$$

- Has no closed-form solution ☹️
- Solution is about 3.6 for $\gamma = 1$

215


Assume no self loading

- Implies $\gamma = 0$
- Solve $\frac{\delta}{\delta N} \log(N \sqrt[N]{F}) = 0$
- Leads to so-called exponential horn

$$N_{opt} = \log(F) \quad \longrightarrow \quad f_{opt} = e \approx 2.72$$

216

Optimum effective fan-out f_{opt}

 

- Choosing f larger than optimum has little effect on delay and reduces # stages
 - $f=4$ is common practice for $\gamma = 1$
 - too many stages has negative impact on delay

Image taken from: http://bwrcs.eecs.berkeley.edu/Courses/icdesign/ee141_f01/Notes/chapter5.pdf

217

Example: buffer design

	N	f	t_p
	1	64	65
	2	8	18
	3	4	15
	4	2.8	15.3

218

Example: size the buffers

always C_{ext}/C_{int}

C_1 $C_L = 64C_1$

$$\frac{2C_2}{C_1} = \frac{3C_3}{C_2} = \frac{C_L}{C_3} = f_{opt}$$

$$\frac{2\cancel{C_2}}{C_1} \times \frac{3\cancel{C_3}}{\cancel{C_2}} \times \frac{C_L}{\cancel{C_3}} = f_{opt}^3 \quad \rightarrow \quad \frac{6C_L}{C_1} = f_{opt}^3$$

219

Example: size the buffers (cont'd)

C_1 $C_L = 64C_1$

$$\sqrt[3]{\frac{6C_L}{C_1}} = f_{opt} \approx 7.2685$$

buffer 2 is 3.6x larger than buffer 1

$$\frac{2C_2}{C_1} \approx 7.2685 \rightarrow C_2 \approx 3.6342C_1$$

buffer 3 is 8.8x larger than buffer 1

$$\frac{3C_3}{C_2} \approx 7.2685 \rightarrow C_3 \approx 2.4228C_2 \rightarrow C_3 \approx 8.8051C_1$$


220

Examples

Delay minimization

221

Two cases for delay minimization

 

- Known number of gates N , unknown f
 - Find optimal f such that $F=f^N$
- Known f_{opt} , unknown N
 - Find N with f as close as possible to f_{opt}


$$f_{opt} = \sqrt[N]{C_L/C_{g,1}} = \sqrt[N]{F}$$

$$t_p = N t_{p0} (1 + \sqrt[N]{F}/\gamma)$$

Image adapted from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

222

Example: propagation delay t_p

 

$$t_{p1} = t_{p0} \left(1 + \frac{4C_g + C_g}{\gamma C_g} \right) \quad t_{p2} = t_{p0} \left(1 + \frac{16C_g + C_W}{\gamma 4C_g} \right)$$

$$t_{p3} = t_{p0} \left(1 + \frac{C_L}{\gamma 16C_g} \right)$$

223