

ECE4740: Digital VLSI Design

Lecture 9: Wire models

316

Should I even care?

Wire basics

317

Interconnect parasitics

- Wiring in today's circuits will
 - increase the propagation delay
 - have an impact on power consumption
 - cause extra noise/interference (reliability)
 - affect the density of your chip

- Classes of parasitic effects

- Capacitive
 - Resistive
 - Inductive
- less important...


cross talk

IR drop


inductive peaking

318

Example

 

schematic view

 


physical view


Images taken from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris

319

Example (cont'd)

 

"all-inclusive" model

 


capacitance model

Images taken from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris

320

Wire model: simplifications

 - Inductive effects can be ignored if resistance is large enough or transients are slow
- Short wires: resistivity can be ignored
- If separation between wires is large, inter-wire capacitance can be ignored




Images taken from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris

321

Wire models

 - “All-inclusive” models too complicated for manual analysis; we need simpler models:
 - Lumped C
 - Lumped RC
 - Distributed RC
 - Lumped RL
 - Distributed RL
 - Distributed LC
 - Transmission lines
 - Lossy TL




when to use
which model?

Images taken from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris

322

Length distribution

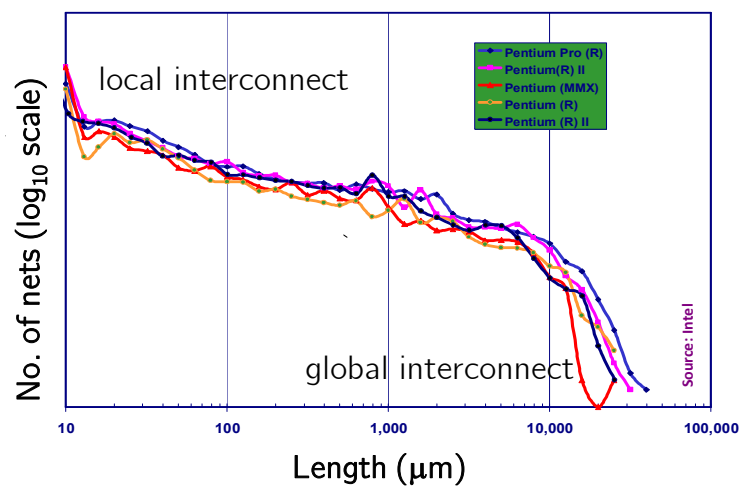



323

The basic model

Wire capacitance

324

Lumped capacitance

  

- Valid if
 - short wires
 - low resistivity
 - low frequency

325

Images taken from: ECE424 – Fall 2014 Introduction to VLSI Design, by Emre Yengel

Parallel plate model

- Width of wire much larger than thickness of insulating material → **area capacitance**

 


Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

326

Permittivity of dielectrics

$$\epsilon_{di} = \epsilon_0 \epsilon_r$$

Labels: relative permittivity (pointing to ϵ_r), free-space permittivity (pointing to ϵ_0)

$$\epsilon_0 \approx 8.854 \cdot 10^{-12} \text{F/m}$$

Material	Relative Permittivity ϵ_r
Free space	1
Aerogels	1.5
Low-K SiO ₂ (porous)	1.5 – 2
Polyimides (organic)	3 – 4
Silicon Dioxide (SiO ₂)	3.9 – 4.5
Glass-epoxy (PC board)	5
Silicon Nitride (Si ₃ N ₄)	7 - 9
Alumina (package, Al ₂ O ₃)	9.5
Silicon	11.7

327

Height of wire does matter


- Previous model is too simplistic
- Current designs:
 - cross section $W \times H$ as large as possible
 - denser wiring led to increase in H/W ratio (>1)
- Parallel plate model not accurate anymore



328

Fringing capacitance

 
- Capacitance between wire sides & substrate



329

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Fringing capacitance (cont'd)

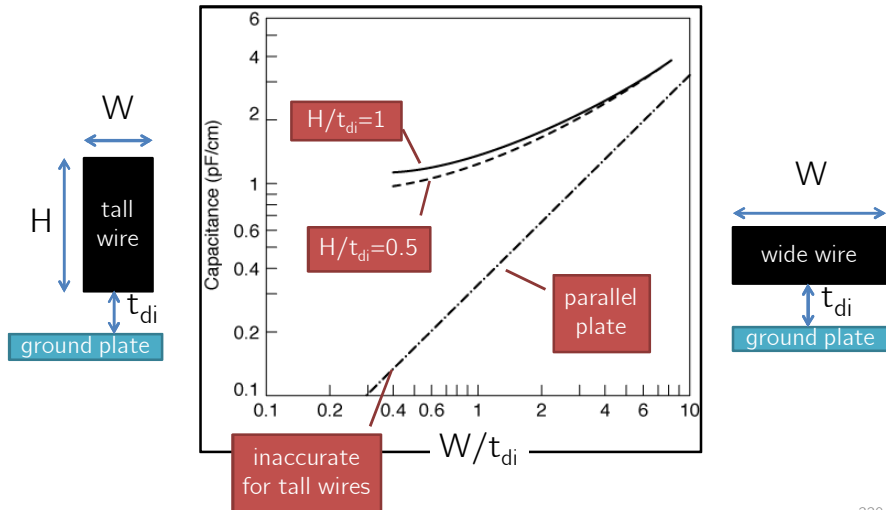

330

Example: Capacitances in 250nm

bottom plate of capacitor

	Field	Active	Poly	Al1	Al2	Al3	Al4
Poly	88						
	54						
Al1	30	41	57				
	40	47	54				
Al2	13	15	17	36			
	25	27	29	45			
Al3	8.9	9.4	10	15	41		
	18	19	20	27	49		
Al4	6.5	6.8	7	8.9	15	35	
	14	15	15	18	27	45	
Al5	5.2	5.4	5.4	6.6	9.1	14	38
	12	12	12	14	19	27	52

Annotations: 'area capacitance aF/ μm^2 ' points to the Poly row, and 'fringe capacitance aF/ μm ' points to the Al1 and Al2 rows.

331

Inter-wire capacitance

- Wires are coupled to GND and to neighboring wires (same or different layer)
- Floating capacitors cause cross-talk

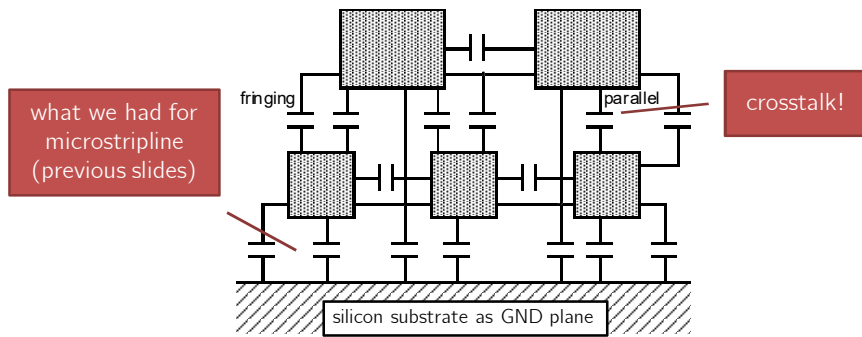


Image taken from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris

332

Inter-wire capacitance

- **Growing problem**
 - multilayer structures
 - decreasing feature sizes

wires are getting closer and closer

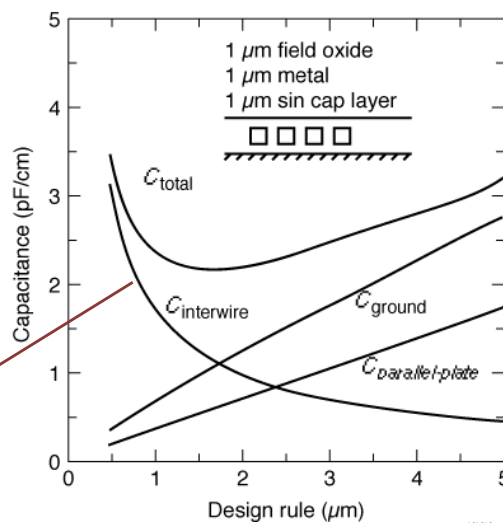


Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

333

Example: Capacitances in 250nm

- Inter-wire capacitances (minimum spacing)

Layer	Poly	Al1	Al2	Al3	Al4	Al5
Capacitance [aF/ μm]	40	95	85	85	85	115

- Use top layers for
 - supply: large caps. are good = tiny “batteries”
 - if used for signals, **separate more than minimum**
 - careful: vias are going to add resistance!

334

Dealing with capacitance

- Use low capacitance (low-k) dielectrics (=insulators) such as polyamide or even air
 - must be robust (thermal and mechanical stress)
 - must be compatible with interconnect
- Copper interconnect allows wires to be thinner without increasing their resistance
- Silicon on insulator (SOI) to reduce junction capacitance

335


Important for not-so-short wires

Wire resistance

336

Basics and definitions

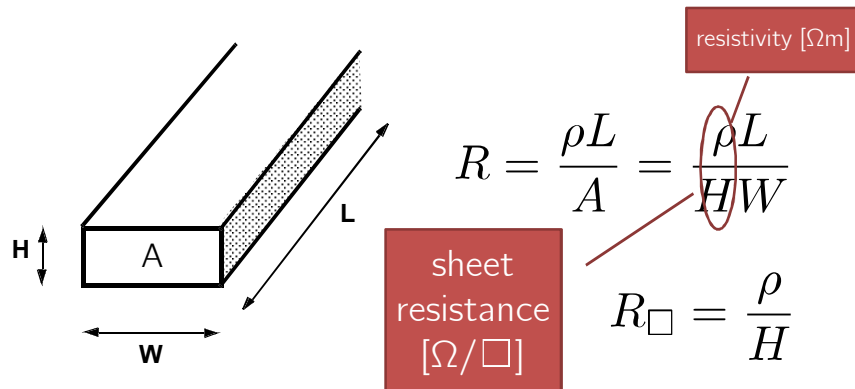- Resistance proportional to length L
- Inversely proportional to cross section A



337

Resistivity of common conductors

- ρ at 20°C

Material	Resistivity (Ωm)	
Silver (Ag)	1.6×10^{-8}	
Copper (Cu)	1.7×10^{-8}	more popular recently (low resistivity)
Gold (Au)	2.2×10^{-8}	
Aluminum (Al)	2.7×10^{-8}	low cost and good in manufacturing
Tungsten (W)	5.5×10^{-8}	

338

Fun fact: AudioQuest K2 Cable

- 2.44m audio speaker cable
- **Silver** connectors and cables
- “Optimized for full range”
- Price: **1 used from \$13,099.00**



471 of 488 people found the following review helpful

★☆☆☆☆ Thanks a lot.

By Daniel A. Garcia on December 30, 2010

My cats chewed on this cable and now they can both speak.

[12 Comments](#)

Was this review helpful to you?

Yes

No

339

Sheet resistance in 250nm

Material	Sheet resistance (Ω/\square)
n- or p-well diffusion	1000-1500
n+, p+ diffusion	50-150
n+, p+ polysilicon	150-200
aluminum (Al)	0.05-0.1

only good for local interconnect

$$R_{\square} = \frac{\rho}{H}$$

340

Dealing with wire resistance


- Selective technology scaling (less scaling of wire thickness)
- Use better interconnect materials
 - Use copper in metal layers and silicides close to silicon (active and poly gate)
- More interconnect layers
 - Reduces average wire length

remember: contacts (vias) add resistance (contact resistance)

341

Skin effect

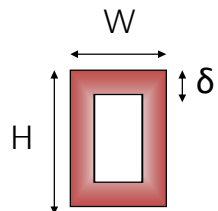- For high frequencies f , currents tend to flow mostly on surface of conductor
- Skin depth δ : depth where current is $e^{-1} \approx 0.368$ times less than nominal



$$\delta = \sqrt{\frac{\rho}{\pi f \mu}}$$

2.6 μm for Al at 1GHz

permeability of free space

342

Skin effect (cont'd)

- Effective area lower \rightarrow **resistance increases!**
- For $f > f_s$, the resistance gets

resistance per unit length

$$r(f) = \frac{\sqrt{\pi f \mu \rho}}{2(H + W)}$$

frequency where skin depth is equal to half the largest dimension of the conductor

$$f_s = \frac{4\rho}{\pi \mu (\max\{W, H\})^2}$$

343

Really?

Wire inductance

344

Should we even care?

- Inductance plays a role in multi GHz range
- Useful relation:

$$l \times c = \epsilon \mu$$

The diagram shows the equation $l \times c = \epsilon \mu$ with four red boxes below it. Lines connect the terms as follows: l connects to 'inductance per unit length', c connects to 'capacitance per unit length', ϵ connects to 'permittivity', and μ connects to 'permeability'.

- The larger the capacitance, the smaller the inductance, and vice versa!
- **Depends on the wire thickness**

345


Useful for back-of-the-envelope calculations

Lumped wire model

346

Lumped wire model revisited

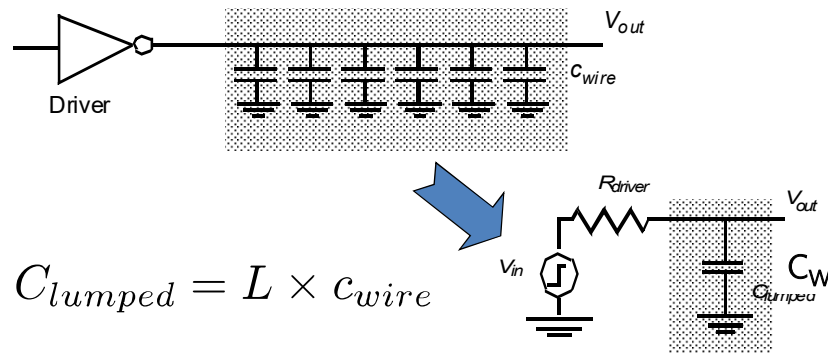- Ignore inductive effects and assume small resistive component




347

Images taken from: ECE424 – Fall 2014 Introduction to VLSI Design, by Emre Yengel

 Example: long wire

- Source resistance: $10\text{k}\Omega$
- All wire: 10cm long, $1\mu\text{m}$ wide: 11pF
- Compute transient response time (50% point reached; V_{in} goes from GND to VDD)



$$t = \ln(2)\tau \approx 0.69\tau$$


what is τ ?

348

Image taken from: ECE424 – Fall 2014 Introduction to VLSI Design, by Emre Yengel

Lumped RC model

 - RC tree
- Properties:
 - Single input s
 - Capacitors between node and ground
 - Network contains no resistive loops



349

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic


(Shared) path resistance (R_{ik}) R_{ij}

- Resistance between source s and node 4: R_{44}

$$R_{44} = R_1 + R_3 + R_4$$

- Shared path resistance R_{ik}
 
$$R_{ik} = \left\{ \sum R_j : j \in \{\text{path}(s \rightarrow i) \cap \text{path}(s \rightarrow k)\} \right\}$$




350

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Elmore delay

- Assume all nodes are discharged to GND
- Step input applied at node s at $t=0$
- Elmore delay at node i is given by

$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$

 

equivalent to first-order time constant!

351


Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Example: Elmore delay

- Elmore delay τ_{Di} for node i ?

$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$

sum over every cap.

 

$$\tau_{Di} = C_1 R_1 + C_2 R_1 + C_3 (R_1 + R_3) + C_4 (R_1 + R_3) + C_i (R_1 + R_3 + R_i)$$

352

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Resistive capacitive wire

- Partition wire of length L in N segments
 - Resistance of segment rL/N (with $R=rL$)
 - Capacitance of segment cL/N (with $C=cL$)
- Use Elmore delay formula

$$\tau_{DN} = \left(\frac{L}{N} \right)^2 (rc + 2rc + \dots + Nrc)$$

$$\tau_{DN} = RC \frac{N+1}{2N} \rightarrow \frac{RC}{2} = \frac{rcL^2}{2}$$

353

Resistive capacitive wire (cont'd)

- Implications of

$$\tau_{DN} = RC \frac{N+1}{2N} \rightarrow \frac{RC}{2} = \frac{rcL^2}{2}$$

- Doubling wire length L quadruples delay
- Lumped RC model overestimates the delay by a factor of 2 (**pessimistic estimate**)

remember: it is only a 1st order approximation

354