 


ECE4740: Digital VLSI Design


Lecture 11: More CMOS logic

410

Example: $x = \overline{a \cdot b + c \cdot d}$



logic graph:


 


a → b → c → d is a consistent Euler path!

411

Example: $x = \overline{a \cdot b + c \cdot d}$

stick diagram for {a,b,c,d}

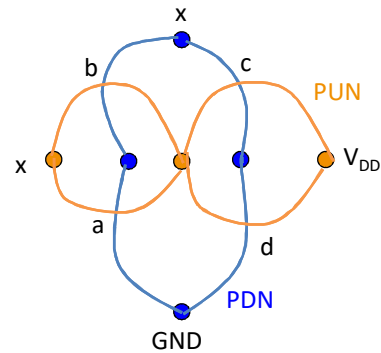 

$a \rightarrow b \rightarrow c \rightarrow d$ is a consistent Euler path

412


Your turn: $x = \overline{a + b \cdot c}$

- Find truth table
- Draw PUN, PDN, and logic gate
- Draw logic graph
- Find consistent Euler paths
- Draw stick diagram

a	b	c	x
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


413

Solution: $x = \overline{a + b \cdot c}$

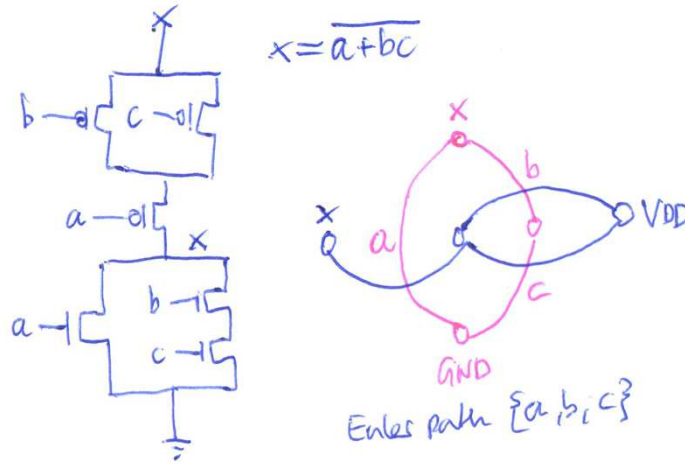

414

Solution: $x = \overline{a + b \cdot c}$

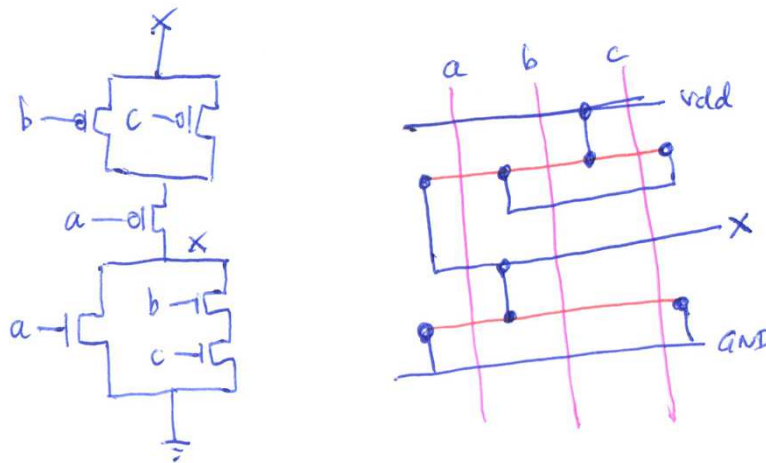

415

Static CMOS gates summary

- Essentially behave like a CMOS inverter
- Full rail-to-rail swing; **high noise margins**
- Logic levels don't depend on device sizes
- Always path to VDD or GND in steady state; **low output impedance**
- Very **high input resistance**; nearly-zero steady-state input current (can drive infinite fan-out)
- (almost) no direct path in steady state between power and ground; **low static power**

416

DC characteristics and propagation delay

Static & dynamic properties

417

DC properties of CMOS gates

- VTC depends on input data applied to gate

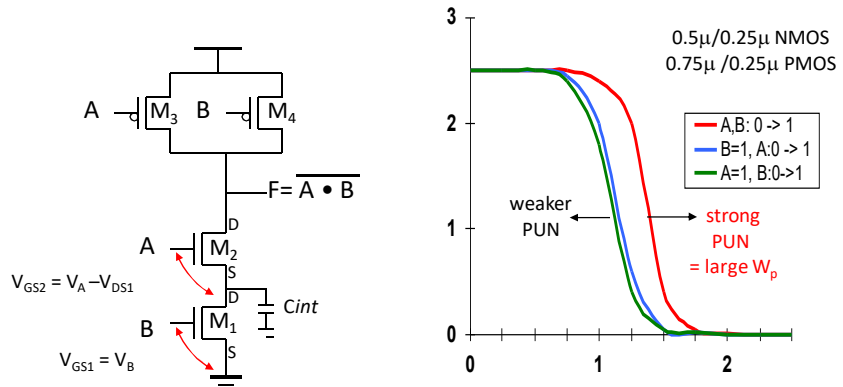



Image taken from: http://bwrcs.eecs.berkeley.edu/Classes/icdesign/ee141_f01/Notes/chapter6.pdf

418

Remember the switching threshold?

$$V_M \approx \frac{rV_{DD}}{1+r}$$

 
$$r = \frac{\nu_{SATp} W_p}{\nu_{SATn} W_n}$$



- For $A=B=0$, both PMOS are simultaneously on
- Parallel PMOS lead to larger effective W_p

419

The other two cases

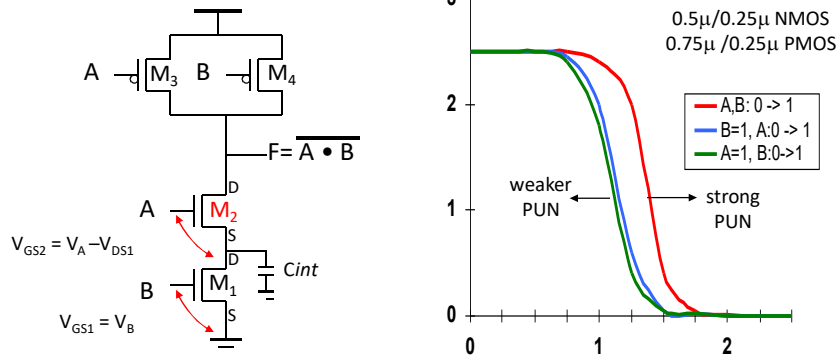


- Threshold of M_2 is higher due to body effect: $V_T = V_{T0} + \gamma(\sqrt{|2\phi_F + V_{SB}|} - \sqrt{|2\phi_F|})$

420


Propagation delay of CMOS logic

- Use RC model for logic gate:

 

421

Input data affects propagation delay

 


2 resistors in parallel

2 resistors in series

- Propagation delay depends on input pattern
- Low-to-high output
 - Both inputs go low
 - $t_{LH} = 0.69 R_{eqp}/2 C_L$
 - One input goes low
 - $t_{LH} = 0.69 R_{eqp} C_L$
- High-to-low output
 - Both inputs go high
 - $t_{HL} = 0.69 2R_{eqn} C_L$

422

Delay dependence on input patterns

 

Input Data Pattern	Delay (psec)
A=B=0→1	67
A=1, B=0→1	64
A= 0→1, B=1	61
A=B=1→0	45
A=1, B=1→0	80
A= 1→0, B=1	81

NMOS = 0.5μm/0.25 μm, PMOS = 0.75μm/0.25 μm, $C_L = 100$ fF

423


Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Similar to that of the CMOS inverter

Static CMOS gate sizing

424


Design goal: reduce max. delay

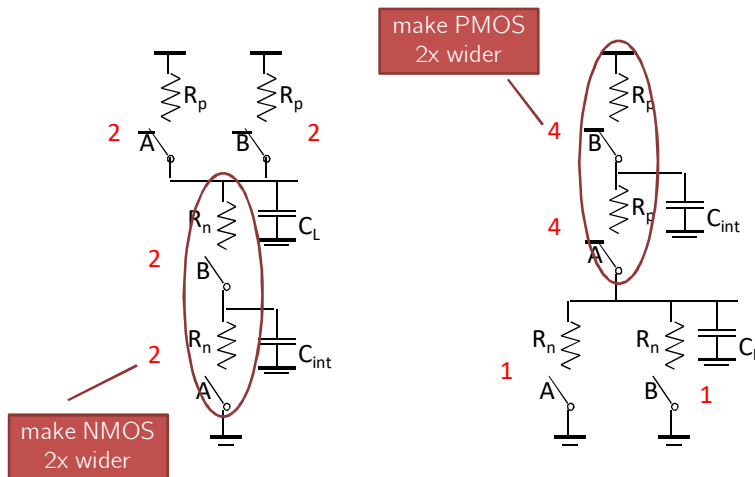

Assume initial NMOS/PMOS width ratio $W_p = 2W_n$

425

Sizing of a (more) complex gate

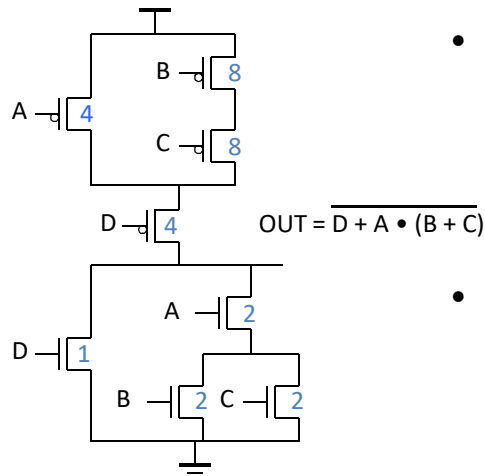


- Assume PMOS/NMOS width ratio of 2:1

- Assume negligible capacitive self loading

426


Multiple solutions possible!

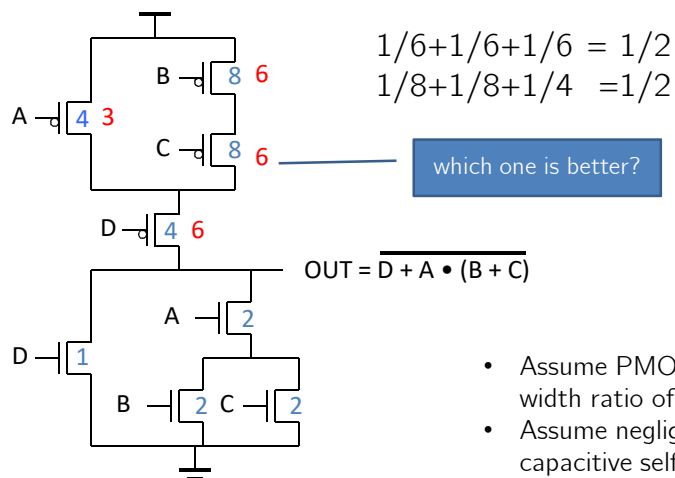

- Assume PMOS/NMOS width ratio of 2
- Assume negligible capacitive self loading

427

 
Size this gate: $x = \overline{a + b \cdot c}$




- Assume PMOS:NMOS ratio 2:1 for symmetric VTC
- Are there multiple sizing solutions?

428

Gates with large fan-ins

 

 - How can we compute t_{pHL} ?
- Use Elmore delay!




$$t_{pHL} = 0.69R_{neq}(C_1 + 2C_2 + 3C_3 + 4C_4)$$

junction capacitances and C_{GS} , C_{GD} (Miller effect)

429

Delay t_p as function of fan-in

 


- Gates with fan-in > 4 should be avoided

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

430

Delay as function of fan-in (cont'd)

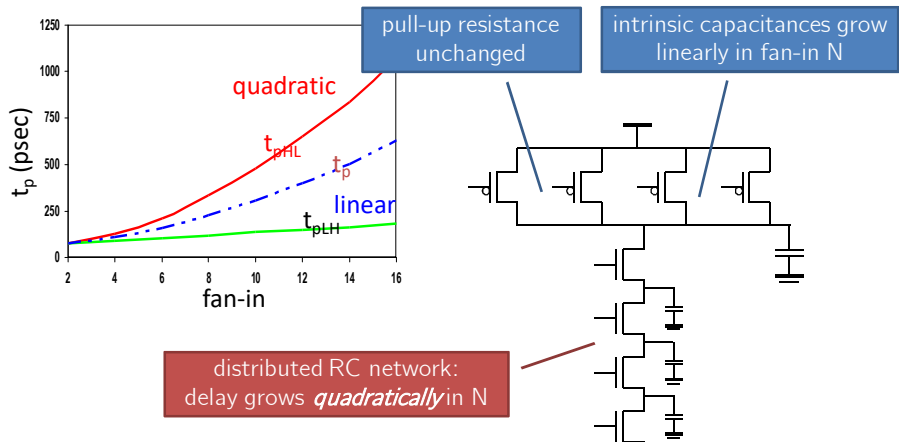

- $t_{pHL} = 0.69R_{neq} (1C_1 + 2C_2 + 3C_3 + 4C_L)$

431

Design techniques


Fast complex gates

432

Method 1: Transistor sizing

- As long as fan-out capacitance dominates
- **Progressive sizing:**

careful with self loading

 

Recall distributed RC line

$$M1 > M2 > M3 > \dots > MN$$

(the FET closest to the output should be the smallest)

Can reduce delay by more than 20%; decreasing gains as technology shrinks

layout difficult for varying sizes!

433

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Method 2: Input re-ordering

- Latest signal should be closest to output


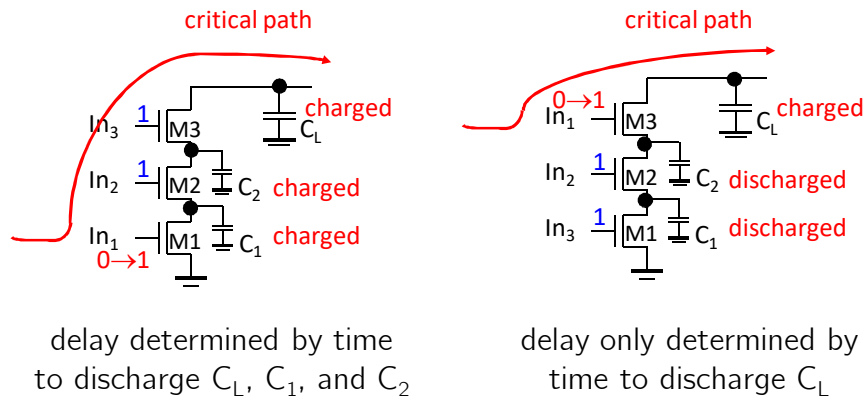


Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

434

Method 3: Use alternative logic

 - $F = A \cdot B \cdot C \cdot D \cdot E \cdot F \cdot G \cdot H$




- Called logic restructuring
- See supplementary material for an example

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

435

Method 4: Isolate fan-in from fan-out

- Buffer insertion

 

Large C_L from fan-out

- Important: optimizing propagation delay of an isolated gate is often misguided

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

436

(Method 5: Reduce voltage swing)

- Linear reduction in propagation delay

$$t_{pHL} \approx 0.69 \frac{3 C_L V_{DD}}{4 I_{DSATn}} \approx 0.69 \frac{3 C_L V_{swing}}{4 I_{DSATn}}$$

- Also reduces power consumption
- But following gate will be **much slower**
 - requires “sense amplifier” to restore signal level (used in memory design or serial interconnects)

437