

# ECE4740: Digital VLSI Design

Lecture 12: CMOS logic sizing

438

Needed for sizing CMOS logic gates

## Logical effort


439

## Sizing logic paths for speed

- Input capacitance of logic path is often constrained
  - E.g., ALU in old Intel microprocessor is 0.5pF
- Logic also has to drive some load
- How do we size logic for maximum speed?
- We have solved this for the inverter chain
- **Can we generalize it for any type of logic?**
  - Determine transistor sizes for complex logic
  - Hand-calculation (=approximation)

440

## Remember? Simple buffer example

 

$$t_p = t_{p0} \sum_{i=1}^N \left( 1 + \frac{C_{i+1}}{\gamma C_i} \right) = t_{p0} \sum_{i=1}^N \left( 1 + \frac{f_i}{\gamma} \right)$$

effective fan-out

- Optimality condition:  $C_i/C_{i-1} = C_{i+1}/C_i$
- Optimum fan-out:  $f_{opt} = \sqrt[N]{C_L/C_{in}}$

Image adapted from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

441

## Can we generalize this approach?

- Yes: Logical effort (**quite complicated!**)
- Need to generalize inverter delay

$$t_p = t_{p0} \left( 1 + \frac{f}{\gamma} \right)$$

unloaded gate can  
have higher delay  
than inverter

complicated gates  
might require more  
effort to drive output

442

## Logical effort

- Generalizes formula for inverter delay

$$t_p = t_{p0} \left( p + g \cdot \frac{f}{\gamma} \right) = t_{p0} (p + g \cdot h)$$

- $t_{p0}$  = **intrinsic delay of inverter**
- $h$  = effective fan out → **electrical effort**
- $p$  = ratio of intrinsic (unloaded prop. delay) of gate and a simple inverter (topology & layout)
- $g$  = **logical effort**

443

## Detailed explanation

- Consider loaded delay of NAND gate:

$$t_{p,\text{NAND}} = 0.69R_{\text{NAND}}(C_{\text{int},\text{NAND}} + C_{\text{ext}})$$

external load capacitance

- Consider unloaded delay of INV gate:

$$t_{p,\text{INV}} = 0.69R_{\text{INV}}C_{\text{int},\text{INV}}$$

- How much higher is propagation delay of NAND gate than INV gate:

$$D = \frac{t_{p,\text{NAND}}}{t_{p,\text{INV}}}$$

444

## Detailed explanation (cont'd)

- Let us evaluate that factor:

$$D = \frac{t_{p,\text{NAND}}}{t_{p,\text{INV}}} = \frac{R_{\text{NAND}}}{R_{\text{INV}}} \left( \frac{C_{\text{int},\text{NAND}}}{C_{\text{int},\text{INV}}} + \frac{C_{\text{ext}}}{C_{\text{int},\text{INV}}} \right)$$

- We assume gate has been sized so that worst-case resistances match, i.e.,  $\frac{R_{\text{NAND}}}{R_{\text{INV}}} = 1$

- Then, we get  $D = \frac{C_{\text{int},\text{NAND}}}{C_{\text{int},\text{INV}}} + \frac{C_{\text{ext}}}{C_{\text{int},\text{INV}}}$

intrinsic delay: how much slower unloaded NAND is than unloaded INV

$$= p$$

445

## Detailed explanation (cont'd)

- Focus on the second term:  $D = p + \frac{C_{\text{ext}}}{C_{\text{int,INV}}}$

- We want to know how much more this is than for standard sized inverter:

$$D = p + \frac{C_{\text{ext}}}{C_{\text{int,INV}}} = p + \frac{C_{\text{g,NAND}}}{C_{\text{g,NAND}}} \frac{C_{\text{ext}}}{C_{\text{int,INV}}}$$

- We used:

$$\gamma C_{\text{g,INV}} = C_{\text{int,INV}}$$

logical effort: how much more work is needed compared to INV to drive external load

$$= p + \frac{C_{\text{g,NAND}}}{C_{\text{int,INV}}} \frac{C_{\text{ext}}}{C_{\text{g,NAND}}}$$

$$= p + \frac{C_{\text{g,NAND}}}{\underbrace{C_{\text{g,INV}}}_{=g}} \frac{C_{\text{ext}}}{\underbrace{\gamma C_{\text{g,NAND}}}_{=h}}$$

fan out

446

## Summary


$$D = \underbrace{\frac{C_{\text{int,NAND}}}{C_{\text{int,INV}}}}_{=p} + \frac{C_{\text{g,NAND}}}{\underbrace{C_{\text{g,INV}}}_{=g}} \frac{C_{\text{ext}}}{\underbrace{\gamma C_{\text{g,NAND}}}_{=h}}$$

- Intrinsic delay:  $p$
- Logical effort:  $g$
- Effective fan out:  $h$  (aka. electrical effort)
- Final delay:  $t_{\text{p,NAND}} = t_{\text{p0}} \cdot D = t_{\text{p,INV}} \cdot D$

447
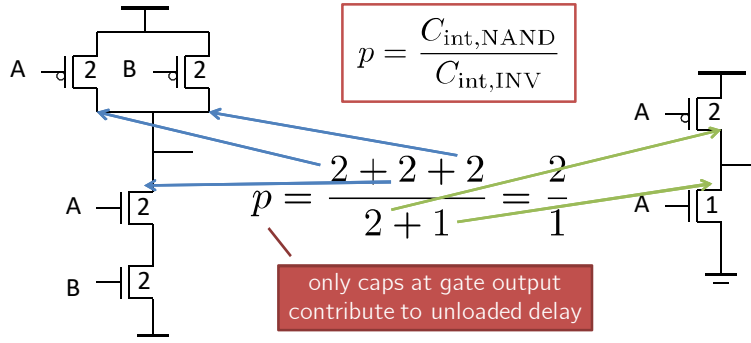
## Intrinsic delay $p \quad t_p = t_{p0} (p) + g \cdot h$

- Consider min-sized symmetrical NAND2
- **Depends on output capacitances\***



**\*always in comparison to standard-sized inverter!**

448

## Intrinsic delay $p \quad t_p = t_{p0} (p) + g \cdot h$

- "How much slower than a CMOS inverter"
- More complex a logic gates  $\rightarrow$  higher the intrinsic delay (compared to INV)

Gate Type	$p$
Inverter	1
n-input NAND	$n$
n-input NOR	$n$
n-way mux	$2n$
XOR, XNOR	$n \cdot 2^{n-1}$

depends on how you build them

Ignoring second order effects such as internal node capacitances

449

## Logical effort $g$ for logic gates


- Inverter has smallest logical effort ( $g=1$ ) and intrinsic delay ( $p=1$ )  

$$t_p = t_{p0} (p + g \cdot h)$$
- **Logical effort is ratio of input capacitance of given gate to inverter capacitance**
  - gate must be sized to deliver same current
  - logical effort refers to only one input
- Logical effort increases with gate complexity
  - function of topology, independent of sizing

450
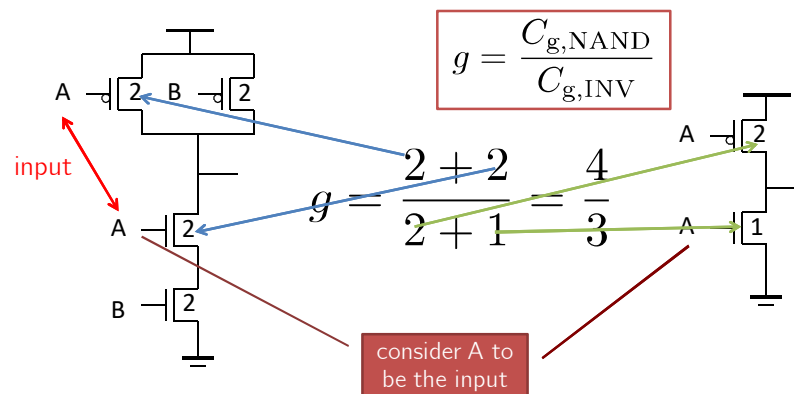
## Logical effort $g$ $t_p = t_{p0} (p + g \cdot h)$

- Consider min-sized symmetrical NAND2
- **Depends on input capacitances**



451

## Logical effort $g$ $t_p = t_{p0} (p + g \cdot h)$

- Logical effort: given a load, complex gates must work harder to produce similar speed

Gate Type	g (for 1 to 4 input gates)			
	1	2	3	n
Inverter	1			
NAND		4/3	5/3	(n+2)/3
NOR		5/3	7/3	(2n+1)/3
mux		2	2	
XOR		4	12	

Always in comparison to inverter!

452

## Logical effort illustrated

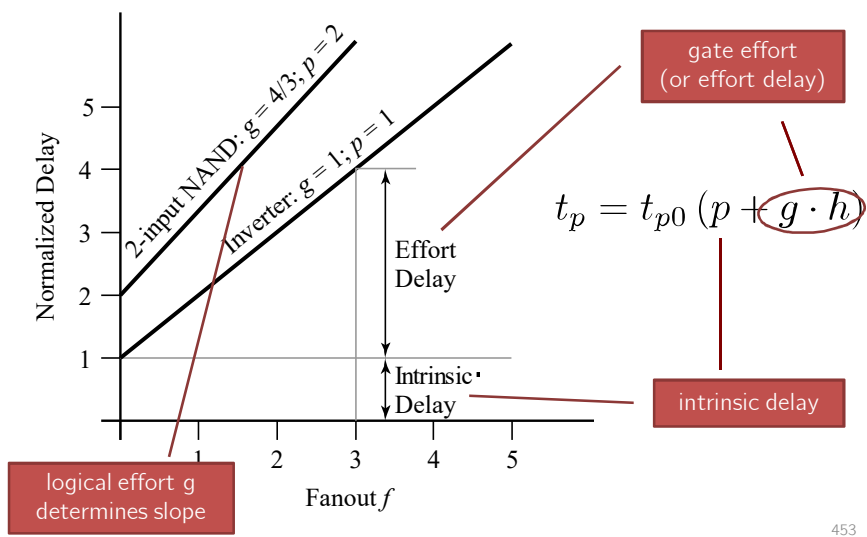


Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

453



More definitions\*  $t_p = t_{p0} (p + g \cdot h)$

- Gate delay:  $d = p + f$ 
  - intrinsic delay
  - gate effort (effort delay or stage effort)
- Gate effort:  $f = g \cdot h$ 
  - logical effort
  - effective fan-out  $C_{out}/C_{in}$
- Logical effort: function of topology, independent of sizing; h is function of load

\*critical assumption  $\gamma=1$

454




More definitions...

## Sizing of multistage networks

456

### Example

 

- Assume we want to
  - compute the propagation delay
  - find the minimum propagation delay
  - manually size the gates to achieve minimum propagation delay

457

## Path delay of complex gate network

- Total path delay:  $t_p = t_{p0} \sum_{j=1}^N (p_j + g_j h_j)$
- Minimum delay through path determines that each stage bears **same gate effort**
  - take partial derivatives to obtain:

$$g_1 h_1 = g_2 h_2 = \dots = g_N h_N = f_{opt}$$

In what follows, we assume  $\gamma=1$

458

## We also need branching effort

- Some drive current is directed on considered path, some is directed off path
- Branching effort

$$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$$

 


Image adapted from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

459

## Total path effort

- Path logical effort:  $G = \prod_{j=1}^N g_j$
- Path effective fan out:  $H = C_L / C_{g1}$
- Path branching effort:  $B = \prod_{j=1}^N b_j$
- **Total path effort:**  $F = G \cdot B \cdot H$
- Gate effort for min. path delay:  $f_{opt} = \sqrt[N]{F}$
- Effective fan-out of each stage:  $h_j = f / (g_j b_j)$

460

## Minimum path delay

- Path intrinsic delay:  $P = \sum_{j=1}^N p_j$
- **Minimum delay through path:**

$$D = t_{p0} \left( P + N \sqrt[N]{F} \right)$$

only depends on types  
of logic gates on  
considered path

461

## How to size CMOS logic gates

- Proceed from start to end; assume that unit-size gate has drive strength of inverter
- Find sizing for first stage:

input capacitance of 2<sup>nd</sup> gate  $g_2 s_2 C_{ref} = \frac{h_1}{b_1} g_1 s_1 C_{ref}$  input capacitance of reference inverter

equal to input capacitance of chain  $C_{g1}$

- General formula:

$$s_i = \frac{g_1 s_1}{g_i} \prod_{j=1}^{i-1} \frac{h_j}{b_j}$$

462

## Summary

Term	Stage expression	Path expression
Logical effort	$g_i$ (depends on logic style, technology, but not on size)	$G = \prod g_i$
Electrical effort	$h_i = C_{out,i}/C_{in,i}$ ( $C_{out,i}$ depends on $W_{i+1}$ , and $C_{in,i}$ depends on $W_i$ )	$H = \prod h_i$
Branch effort	$b_i$	$B = \prod b_i$
Path effort	$f_i = g_i h_i b_i = f$ (equalize stage delay)	$F = \prod f_i$
Intrinsic delay	$p_i$	$P = \sum p_i$
Number of stages	1	N

463


## The delay calculation recipe

- Path logical effort:  $G = \prod_{j=1}^N g_j$
- Path effective fan out:  $H = C_L / C_{g1}$
- Path branching effort:  $B = \prod_{j=1}^N b_j$
- **Total path effort:**  $F = G \cdot B \cdot H$
- Path intrinsic delay:  $P = \sum_{j=1}^N p_j$
- Minimum delay:  $D = t_{p0} \left( P + N \sqrt[N]{H} / \gamma \right)$

sizing not required  
for min. delay!

464


## Example 1: optimize delay

 

- Effective fan-out:  $H=5/1$
- **Path logical effort:**  $G=1 \cdot 5/3 \cdot 5/3 \cdot 1=25/9$
- Path branching effort:  $B=1$  (no branching)
- Total path effort:  $F=GBH=125/9$

465


### Example 1: optimize delay (cont'd)

 

- Total path effort:  $F=GDB=125/9$
- Optimal gate effort:  $f_{opt}=(125/9)^{1/4}=1.93$
- $f_{opt}=g_1*h_1=1*a/1 \rightarrow a=1.93$
- $f_{opt}=g_2*h_2=5/3*b/a \rightarrow b=2.23$

466

### Example 1: optimize delay (cont'd)

 

- $f_{opt}=g_2*h_2=5/3*b/a \rightarrow b=2.23$
- $f_{opt}=g_3*h_3=5/3*c/b \rightarrow c=2.59$
- **Final check:**  $C_L/c=f_{opt}$ ?  $5/2.59=1.93=f_{opt}$
- Now we can size the gates...

467

## Sizing is done iteratively


- Remember the recursive sizing formula:

$$g_{i+1}s_{i+1} = \frac{h_i}{b_i} g_i s_i$$

- s = sizing factor
- g = logical effort
- b = branching effort
- E.g., proceed from beginning to end

468

## Example 1: 3-NAND sizing

 

- PMOS
  - ( $W_p=2$  to match inverter) \*  $h_2 = 2.32$
  - or:  $2 * s_2 = 2.32$
- NMOS
  - ( $W_n=3$  to match inverter) \*  $h_2 = 3.48$
  - or:  $3 * s_2 = 3.48$


$$s_2 = \frac{h_1}{b_1 g_2} g_1 s_1$$

Diagram illustrating the calculation of  $s_2$  for the PMOS transistor in stage 2. The input capacitance of stage 2 is 1.93, which is equal to  $h_1$ . The branching effort  $b_1$  is 1. The logical effort of stage 2 is  $g_2 = 5/3$ . The output capacitance of stage 1 is 1, which is equal to  $g_1 s_1$ . Blue arrows point from these values to the corresponding terms in the equation.

469




### Example 1: NOR sizing

 

- PMOS
  - ( $W_p=4$  to match inverter) \*  $h_3 * h_2 = 5.4$
  - or:  $4 * s_3 = 5.4$
- NMOS
  - ( $W_n=1$  to match inverter) \*  $h_3 * h_2 = 1.34$
  - or:  $1 * s_3 = 1.34$

470

### Example 1: INV sizing

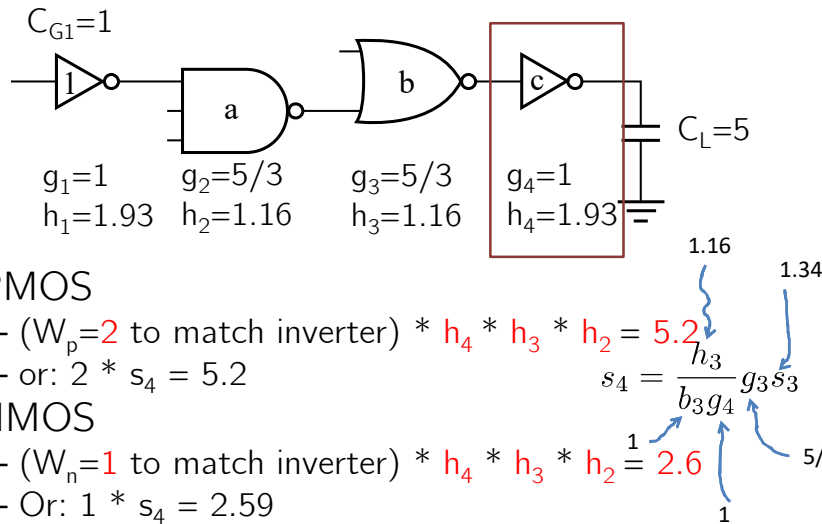

- PMOS
  - ( $W_p=2$  to match inverter) \*  $h_4 * h_3 * h_2 = 5.2$
  - or:  $2 * s_4 = 5.2$
- NMOS
  - ( $W_n=1$  to match inverter) \*  $h_4 * h_3 * h_2 = 2.6$
  - Or:  $1 * s_4 = 2.59$

**DONE!**

471