

ECE4740: Digital VLSI Design

Lecture 15: Dynamic logic


542

Recap

Pseudo NMOS and pass-transistor logic

543

Ratio'ed logic

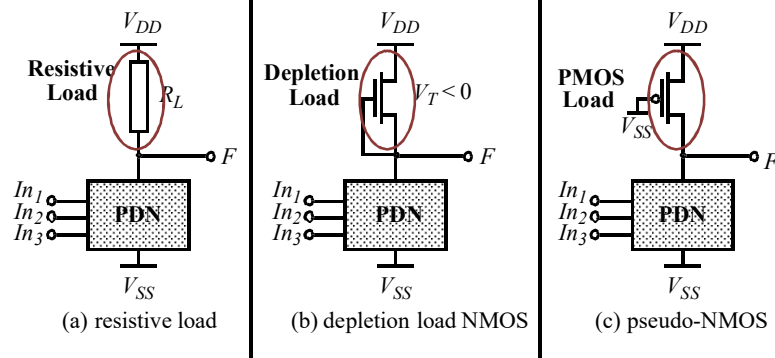


- Goal: Reduce # of transistors over CMOS
- Ratio'ed = functionality depends on ratios!
- Static power \rightarrow When exactly?

544

Image taken from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris

Improving loads is critical

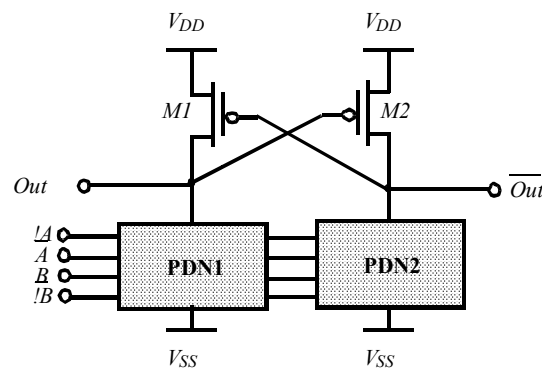


- Differential cascode voltage switch logic (DCVSL)
- No static power consumption but more routing
- Gates keep state \rightarrow why could this be useful?

545

Image taken from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris

Pass transistor logic: AND gate

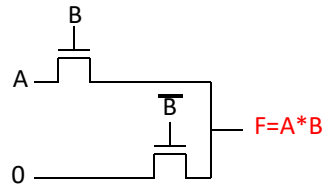


A	B	F=A*B
0	0	0
0	1	0
1	0	0
1	1	1

- Requires 4 logic gates (needs an inverter)
- CMOS logic would require 6 logic gates
- The gate has no rail-to-rail swing
- Non-inverting logic

546

Key issue: static power

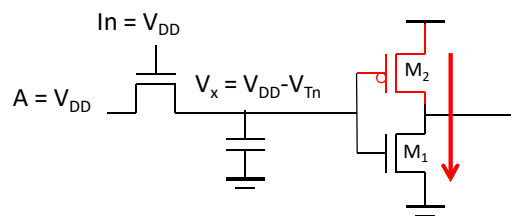

- Pass transistor suffers from body effect
- M_2 may be weakly conducting forming a path from V_{DD} to GND
- Can fix with level-restorer transistor


547

We can go faster

Dynamic logic

548

Do not confuse with sequential logic

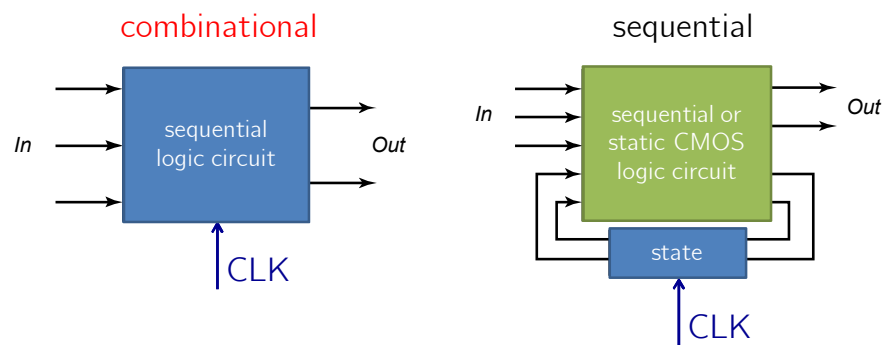

- Sequential logic circuit considers input history
- Dynamic logic may also have a clock input!



549

What is dynamic CMOS?

- **Static** CMOS circuits:
 - Output is (except during switching) connected to GND or V_{DD} via low-resistance path
 - N-input gate requires at least $2N$ transistors
- **Dynamic** circuits:
 - Circuits rely on **temporary storage of signal values** on capacitance of high impedance nodes
 - N-input gate requires (at least) $N+2$ transistors

550


Principle of dynamic gate

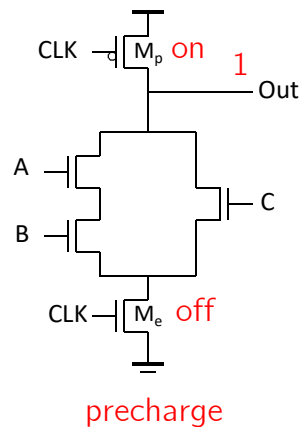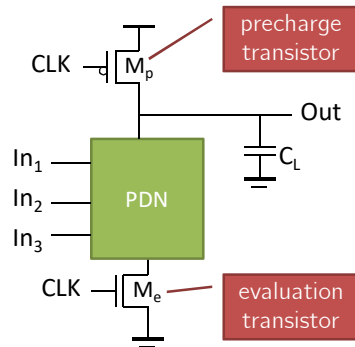


- Two-phase operation:
 - Precharge \rightarrow CLK=0
 - Evaluation \rightarrow CLK=1

551

Principle of dynamic gate (cont'd)

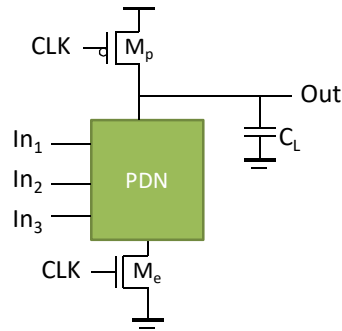

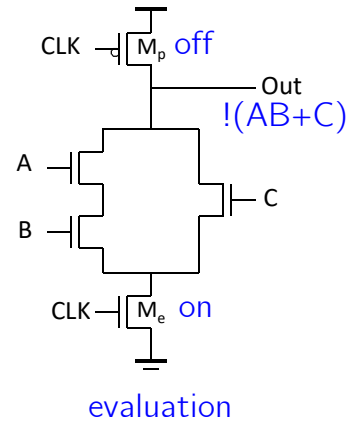- Two-phase operation:
 - Precharge \rightarrow CLK=0
 - Evaluation \rightarrow CLK=1



552


Conditions on output

- Once output of dynamic gate is discharged, it cannot be charged again until next cycle
- Inputs to gate can make at most one transition during evaluation: **no glitches**
- Output can be in high-impedance state during and after evaluation (PDN off)
 - State is temporarily stored on C_L

553

Why not this?

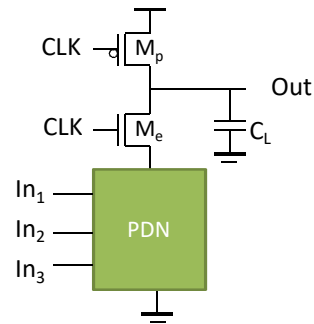- Clock signal needs to have higher voltage to enable evaluation transistor → slower
- Body effect increases V_T even further
- Worse clock feed-through → I will talk about that today



554

Properties of dynamic gates

- Logic function implemented by PDN only
 - # of transistors is $N+2$ (vs. $2N$ for CMOS)
 - Smaller area than static CMOS
- Full swing outputs ($V_{OL}=GND$, $V_{OH}=V_{DD}$)
- Unratio'ed*: **sizing only for performance**
- No cross-over current: all current provided by PDN goes into discharging C_L

*ignoring parasitic effects

555

Properties of dynamic gates (cont'd)

- Faster switching speeds
 - Reduced load capacitance due to lower number of transistors per gate → **lower logical effort**
 - Reduced C_L due to smaller fan-out
- **Power dissipation should be better?**
 - Consumes only dynamic power, no cross-over (or short circuit power)
 - Lower C_L : C_{int} and C_{ext} **FREE LUNCH!?**
 - No glitching


556

What are the disadvantages?

- Power usually **much higher** than CMOS
 - Higher transition probabilities (due to precharge)
 - Extra load on clock signal
 - Clock signal switches every cycle
 - Every gate needs a clock input
- **PDN starts to work as soon as input signals exceed V_{Tn} : $V_M = V_{IH} = V_{IL} = V_{Tn}$**
 - Low noise margin (NM_L)
- **Needs a precharge/evaluate clock**

557

Dynamic behavior

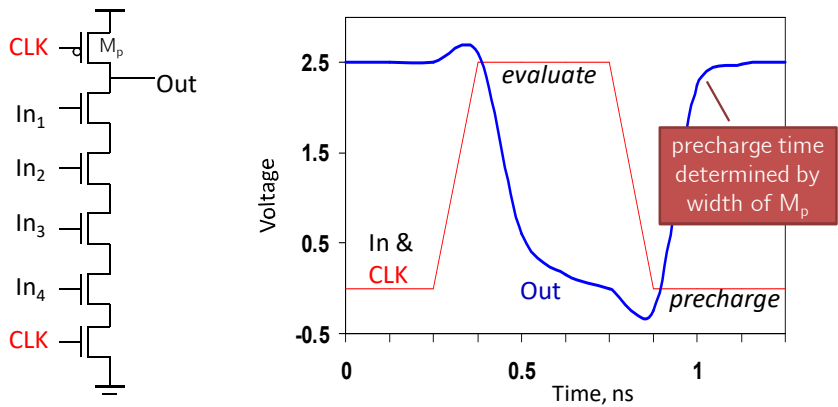


#Trns	V_{OH}	V_{OL}	V_M	NM_H	NM_L	t_{pHL}	t_{pLH}	t_{pre}
6	2.5V	0V	V_{Tn}	$2.5 - V_{Tn}$	V_{Tn}	110ps	0ns	83ps

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic 558


Gate parameters are time dependent

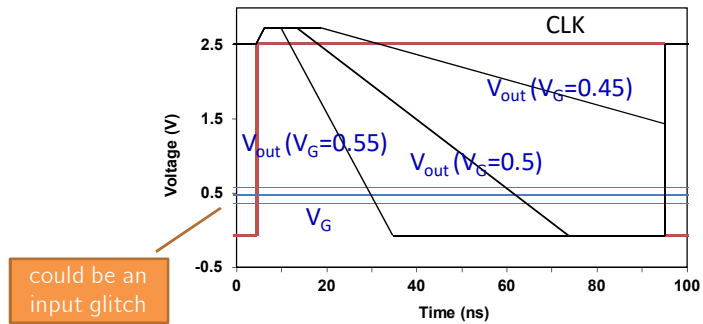- Amount of output voltage drop depends on
 - Input voltage
 - Available evaluation time (short is better)



559

Power consumption

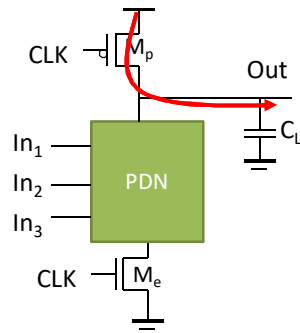

- Power only dissipated when previous Out=0
- Switching activity can be higher than static CMOS
 - Activity does not depend on previous state
 - Activity depends on signal probabilities only


560

Dynamic logic

Issues and solutions

561

Issue 1: charge leakage

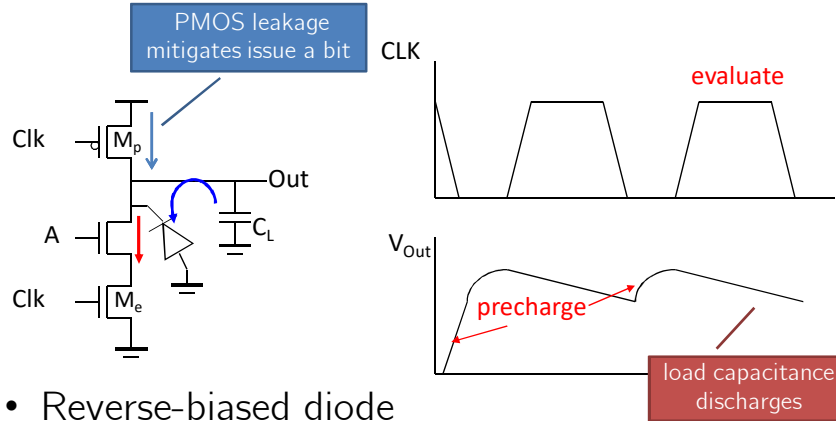


- Reverse-biased diode
- Subthreshold current (dominant)
- Limits **minimum** clock frequency

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

562


Issue 1: charge leakage (cont'd)

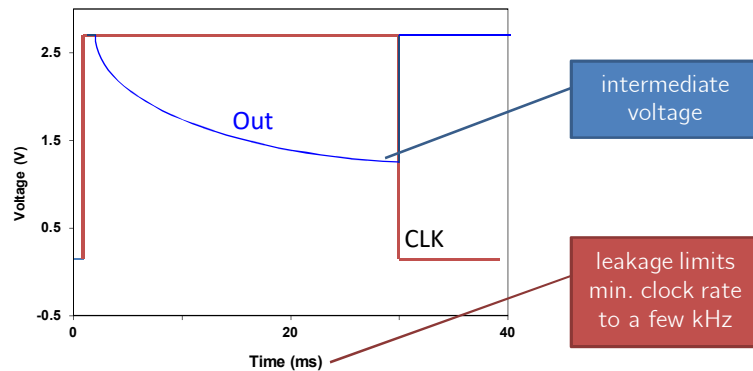- Output settles at voltage determined by resistive divider of PMOS & NMOS



563

Solution to charge leakage

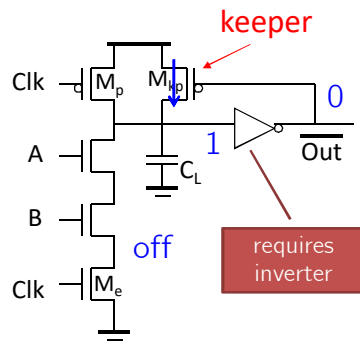


similar idea as for
pass-transistor logic

- During precharge
 - Out = V_{DD} and !Out = GND
- During evaluation
 - PDN off: keeper helps to retain charge
 - PDN on: if M_{kp} is weak, PDN wins → ratio'ed logic!

564

Issue 2: charge sharing

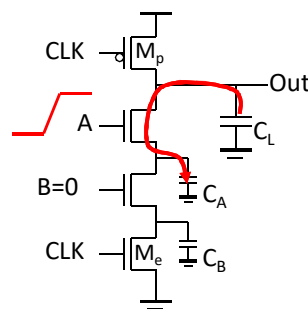


- Charge stored originally on C_L is redistributed (shared) over C_L and C_A
- Leads to static power consumption by downstream gates and possible malfunction
- When $\Delta V_{out} = -V_{DD}(C_A/(C_A+C_L))$ drop in V_{out} is below the threshold of driving gate → malfunction

“capacitive
voltage divider”

565

Charge sharing example: XOR3

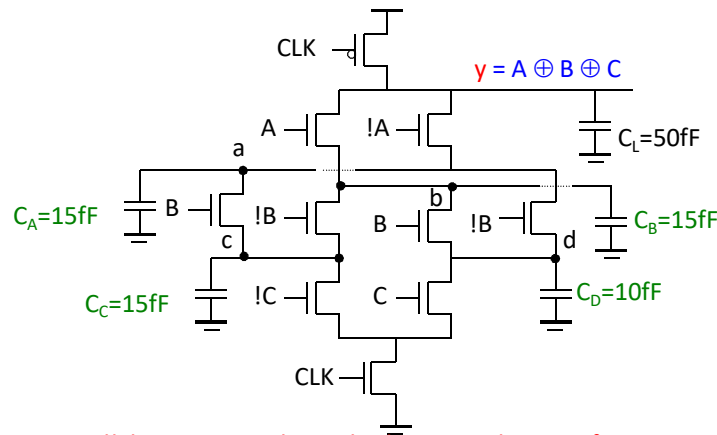- What is worst-case voltage drop on node y ?




Assume all inputs are low during precharge & caps = 0V

566

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Worst-case charge sharing

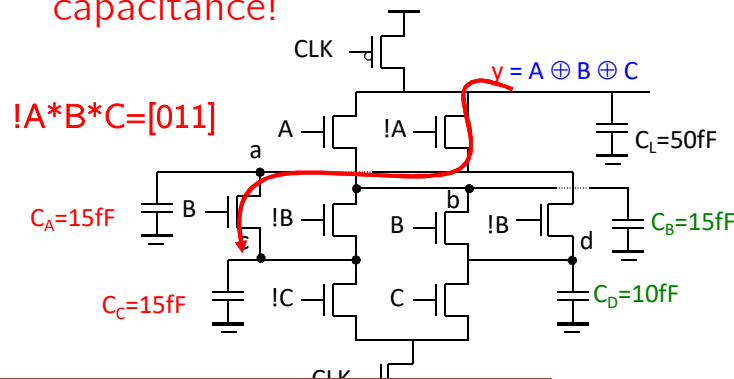- Expose maximum amount of internal capacitance!




$$\Delta V_{out} = -V_{DD}((C_A + C_C) / (C_A + C_C + C_L))$$

567

Worst-case charge sharing (cont'd)


- 2nd solution:

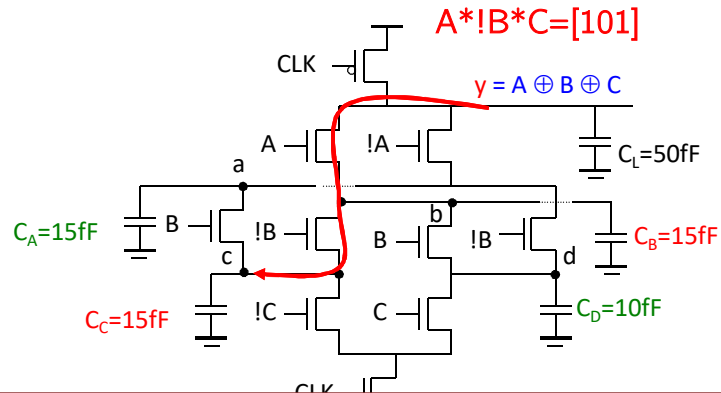

$$\Delta V_{\text{out}} = -V_{\text{DD}}((C_B + C_C)/(C_B + C_C + C_L)) = -V_{\text{DD}}(30/80)$$

568

("Solution" to charge sharing)

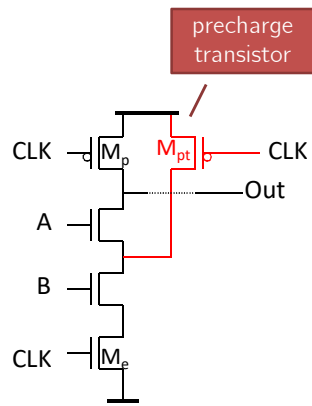


- Precharge all internal (and critical) nodes using PMOS
 - Increases area
 - Increases power (larger capacitance)
 - Reduces speed (larger capacitance)


569

Issue 3: capacitive & backgate coupling

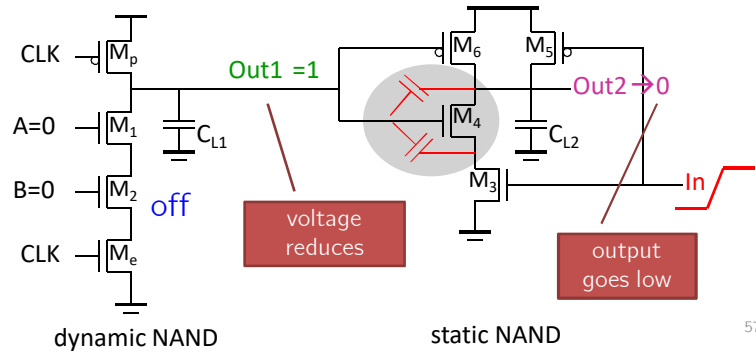- Susceptible to crosstalk
 - High-impedance output node
 - Capacitive coupling from neighboring node
- Backgate coupling:



Backgate coupling effect

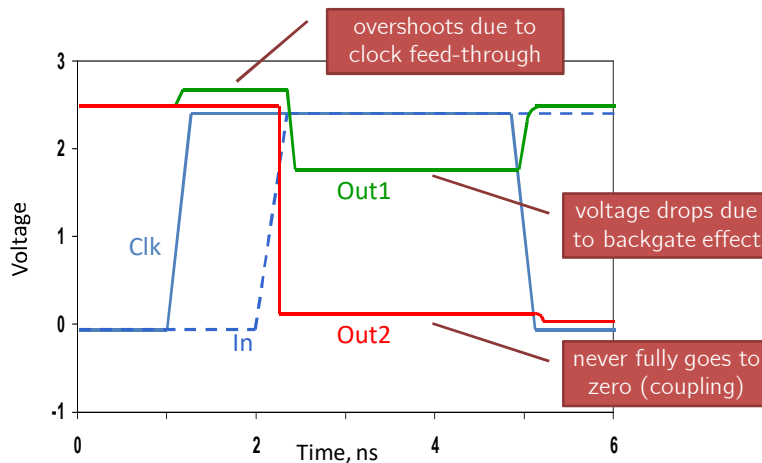


If Out1 drops too much → incorrect behavior → careful with layout!

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Issue 4: Clock feedthrough


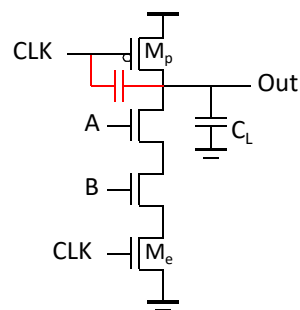
- Capacitive coupling between CLK input of precharge transistor and dynamic node



- Coupling between Out and CLK input of precharge device due to C_{GD}
- Voltage of Out can rise above V_{DD}
- Fast rising (falling edges) of clock couple to Out

572

Remember? dynamic behavior

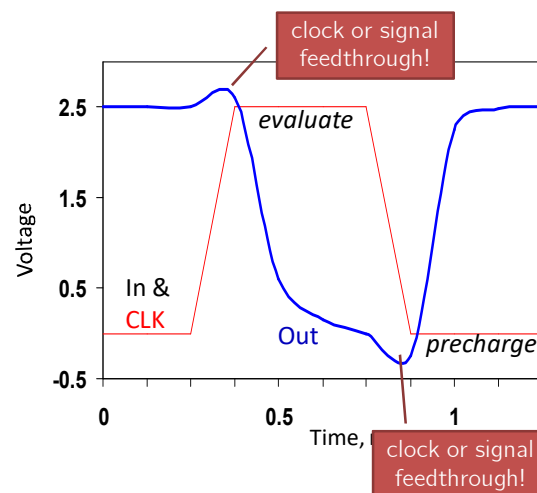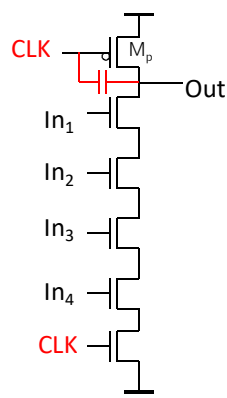

Does not only happen for dynamic circuits

573



It's not that easy

Problem with cascading dynamic gates

574

Cascading causes problems


Two inverters:

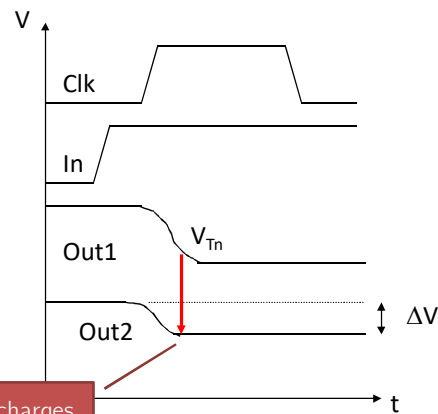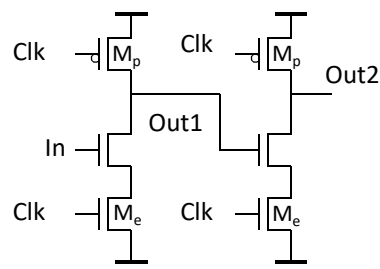

also discharges, because Out1 is initially at VDD

575


Cascading causes problems (cont'd)

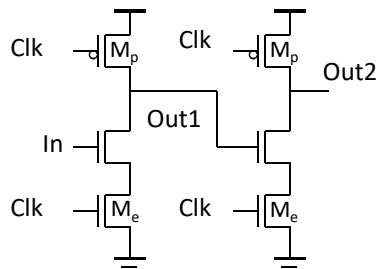

- As nodes are charged to 1, they may cause unwanted discharge
- **Setting all inputs to 0 during precharge would fix the problem**
- Only a **single 0 → 1** transition allowed at inputs during the evaluation period!

576


Cascading causes problems (cont'd)

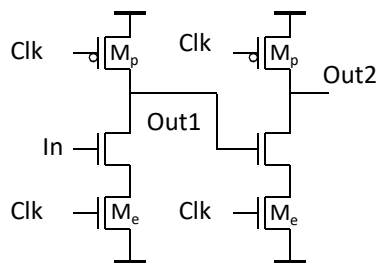

- As nodes are charged to 1, they may cause unwanted discharge
- **Setting all inputs to 0 during precharge would fix the problem**
- Only a **single 0 → 1** transition allowed at inputs during the evaluation period!

577


Solution: domino logic

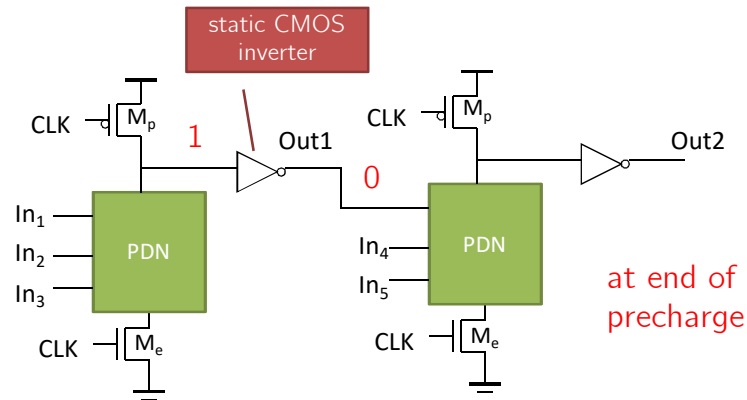

- Inputs to domino gate are set to 0 at end of precharge period

578


Solution: domino logic (cont'd)

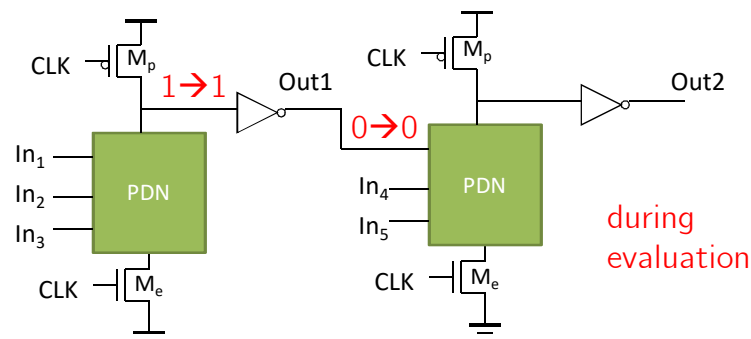

- Inputs to domino gate are set to 0 at end of precharge period

579

Solution: domino logic (cont'd)

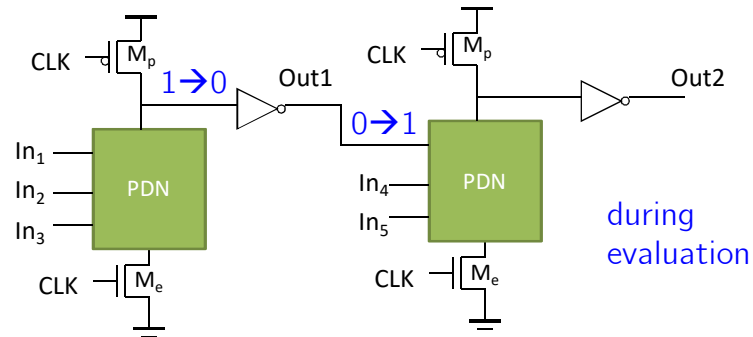

- Only possible transition is $0 \rightarrow 1$, which guarantees signal integrity

580