


ECE4740: Digital VLSI Design

Lecture 26: Architecture transforms

954



Recap

Architecture transforms*

 


*H. Kaeslin, "Digital Integrated Circuit Design," Cambridge Univ. Press, 2008

955

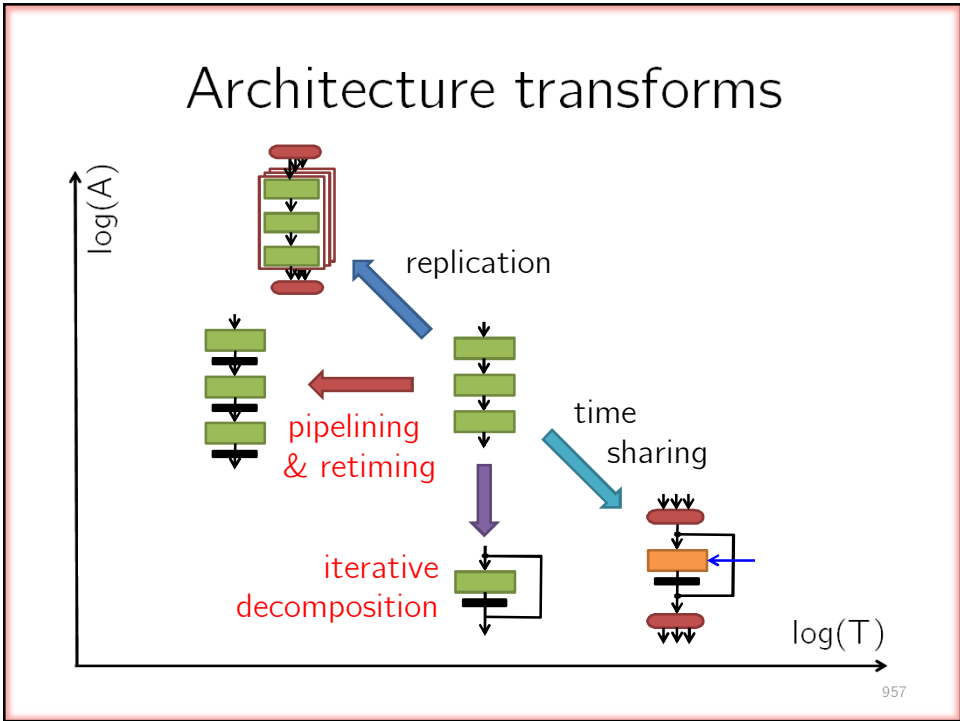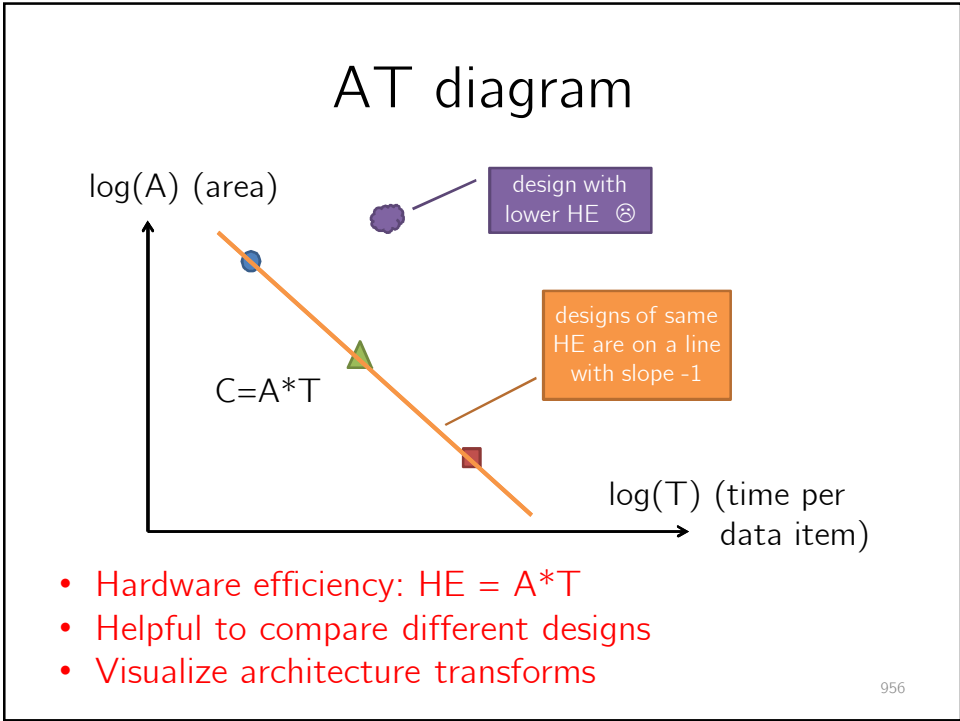

Recall: rotation CORDIC (simplified)

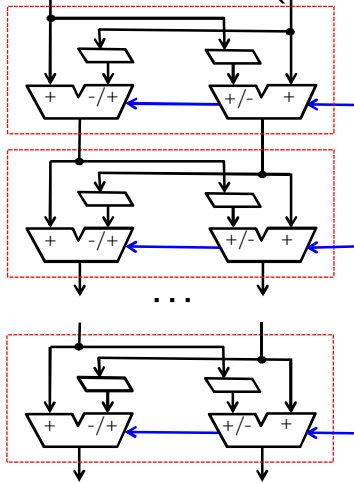


- Isomorphic architecture:
 - Each operation has its own circuit

- $A_{iso} = K * A_{PR}$
- $T_{iso} = K * T_{PR}$

PR = pseudo rotation

958

Fully pipelined architecture

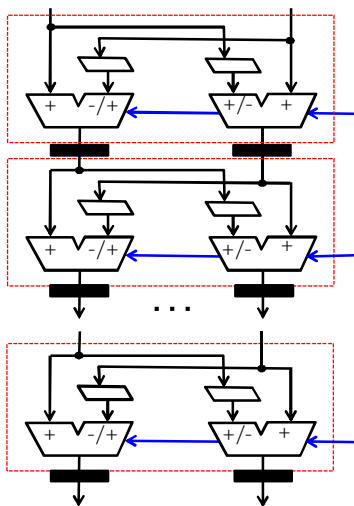


- Pipelined architecture
- $A_p = K * A_{PR} + K * A_{ff}$
- $T_p = T_{PR} + T_{ff}$

includes propagation delay and setup time

- How much is the latency?

959

Fully decomposed architecture

 


- Architecture needs MUX at input and configurable shifter
- $A_u = A_{PR} + A_{ff} + A_{MUX}$
- $T_u = \frac{K}{2} (T_{PR} + T_{ff} + T_{MUX})$

note that shifter must be programmable and hence will be more complex

- How much is the latency?

960

2x decomposed architecture

 

- Partially unrolling the architecture
- $A_{u2} = 2(A_{PR} + A_{ff} + A_{MUX})$
- $T_{u2} = \frac{1}{2} K (T_{PR} + T_{ff} + \frac{1}{2} T_{MUX})$


less impact of the multiplexer

- There is a HE-optimal unroll factor!

*shifters now only support 1/2 of the modes

961


2x replicated architecture

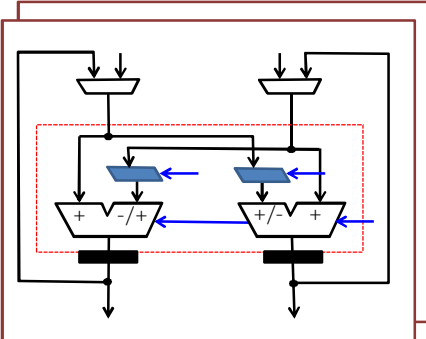

- Replication makes things 2x faster at 2x the area
- $A_{ur} = 2 * (A_{PR} + A_{ff} + A_{MUX})$
- $T_{ur} = K / 2 * (T_{PR} + T_{ff} + T_{MUX})$

962


Example of CORDIC transforms

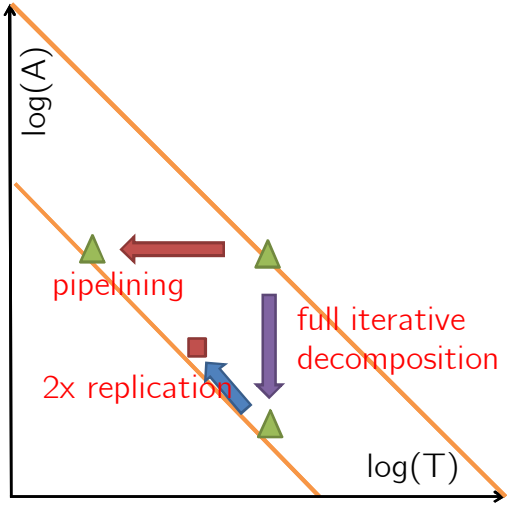

- Optimized designs will have similar HE
- Optimal design depends on the throughput requirements or area constraints

963

Real-world CORDIC trade-off

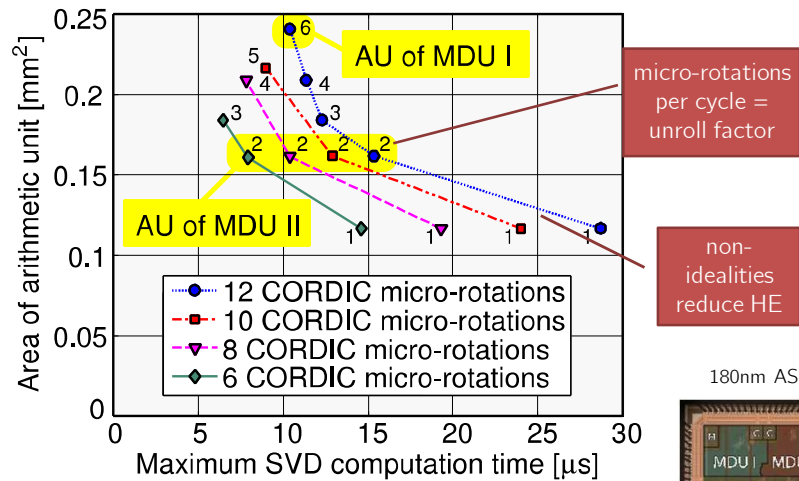


CS, P. Blösch, P. Friedli, and A. Burg, "Matrix Decomposition Architecture for MIMO Systems: Design and Implementation Trade-offs," ASILOMAR, 2007


Architecture transforms summary

- General tool to optimize hardware-efficiency or to meet target specifications:
 - Throughput
 - Area
 - (Power?)
- First-order estimates area and delay can be obtained with hand calculations
 - Non-idealities or secondary effects determine real A and T

Pipelining can reduce area

 


 - Assume tight timing constraint so that fast and large adder and multiplier must be used
- Pipelining relaxes timing and may enable the use of slower but smaller circuits



966


Pipelining can reduce power

 

- Lower area typically leads to lower power
- Pipeline stages stop glitch propagation
 - Lower dynamic power consumption
- Pipelining increases clock frequency
 - Make circuit faster than required and apply voltage-frequency scaling to reduce power
- Overhead of flip-flops may increase power

967

Retiming can increase the area

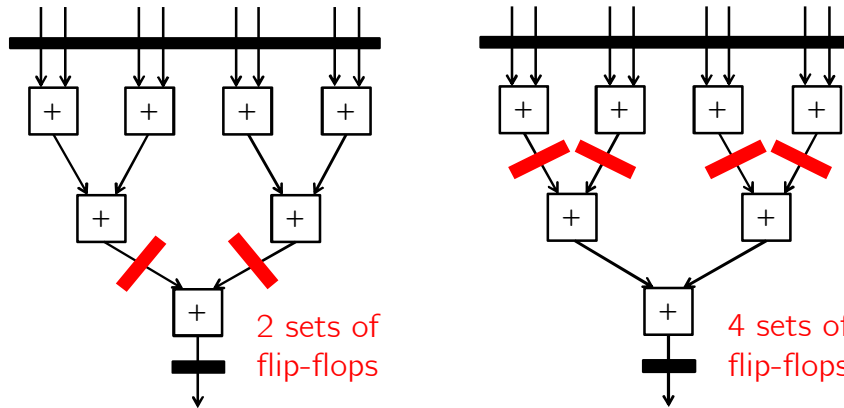

968

Horner's method

Practice architecture transforms

969

Your turn: Horner's method

- Evaluate polynomial:

$$f(x) = a_0 + a_1x + a_2x^2 + a_3x^3 + a_4x^4$$

- Straightforward approach requires 4 additions and **10 multiplications**
- Horner's method:

$$f(x) = a_0 + x(a_1 + x(a_2 + x(a_3 + x(a_4))))$$


requires only 4 multiplications*

*again, algorithmic transforms help the most!

970

Your turn: Horner's method (cont'd)

- Isomorphic VLSI architecture:

 


- Assume $a_{MAC}=10$ and $t_{MAC}=10$ for MAC unit
- Assume $a_{ff}=1$ and $t_{ff}=1$ for flip-flops

- Perform pipelining (add 1 & 3 stages)
- Compute A, T and HE


971

Architectures*

 - 1x pipelined: $A=40+1$, $T=20+1$, $AT=861$



 - 3x pipelined: $A=40+3$, $T=10+1$, $AT=473$




*ignoring registers used to align latency!!!

972

Your turn: Horner's method (cont'd)

- Isomorphic VLSI architecture:

 


- Assume $a_{MAC}=10$ and $t_{MAC}=10$ for MAC unit
- Assume $a_{ff}=1$ and $t_{ff}=1$ for flip-flops

- Perform iterative decomposition (1 & 2 stages per cycle)
- Compute A, T and HE


973

Architectures* (cont'd)

 - Full iterative decomposition: $A=10+1$,
 $T=4(10+1)$, $AT=484$



 - Iteratively decomposed: $A=20+1$,
 $T=2(20+1)$, $AT=882$




*ignoring latency alignment and coefficient registers!

974

Trade-offs for Horner's method

Architecture	Area	Time	A*T
Isomorphic	40	40	1600
1x pipelined	41	21	861
3x pipelined	43	11	473
1x decomposed	11	44	484
2x decomposed	21	42	882
Original formulation*	~100	~80	~8000

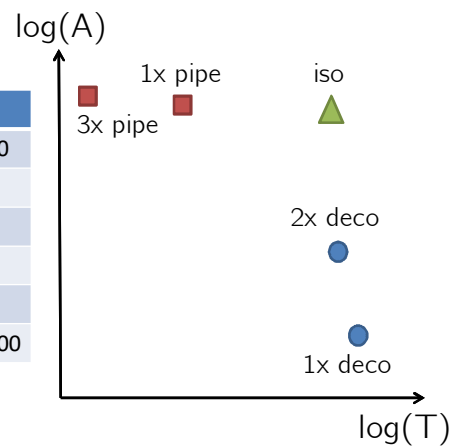

*estimates for original polynomial formulation

975