

ECE4740: Digital VLSI Design

Lecture 27: (A)synchronous circuits

976

Dos and don'ts (or do's and don'ts, or do's and don't's)

Safe (a)synchronous circuits

977

Careful with sequential logic

- Digital VLSI designs often fail because of timing issues and not wrong functionality
- Correct and deterministic operation can only be guaranteed if all signals settled before stored in flip-flop, latch, RAM, etc.
- There are essentially three ways
 - Synchronous clocking
 - Asynchronous clocking
 - (Self-timed clocking)


978

Synchronous clocking

- All storage operations and state transitions occur periodically at precise moments in time determined by a single clock
- Clock domain: Subcircuit where all clock signals maintain fixed frequency and phase relationships
- Clock boundary: the separation between two distinct so-called clock domains

979

Synchronous clocking (cont'd)

 

- Data path and clock/reset strictly separated
- Clock and reset nets may contain buffers


980

Asynchronous clocking

- Some or all of the storage elements are permitted to change their states independently from a global reference
- Such circuits may contain
 - Zero-latency feedback loops, ring oscillators
 - Asynchronous state machines (ASMs)
 - Logic gates on clock and reset nets
 - Unclocked bistables (e.g., SR latch)
 - Etc.

981


Asynchronous clocking (cont'd)

 

- Data path and clock/reset **not** separated
- Logic on clock/reset nets
- Multiple clock sources
- Zero latency feedback loops

982

(Self-timed circuits)

 

- Request and acknowledge signals control dataflow among blocks
- Each block runs as fast as it can



Why is careful clocking important

- Glitches/hazards are unwanted transients
 - Glitch is what you see, hazard is the cause
 - Causes: Reconvergent fan-outs, multiple inputs that change at different time instants, etc.
- **Critical rule: clocks, asynchronous reset, write lines of RAMs etc. must always be glitch free**

984

Potential failures if rule violated

- Unwanted transitions in state machines
- Unwanted reset to initial state
- Erroneous triggering of interrupts in processor
- Storage of bogus data in flip-flop or RAM
- Data loss or duplicates during data transfer
- Deadlocks in asynchronous communication
- Metastable behavior or marginal triggering
- And many more...

985

Rules for safe synchronous designs

- Strictly separate reset, clock, and information signals (data, control, test, etc.)
- Allow all signals to settle before storage
- No unclocked bistables (e.g., SR latch)
- No zero-latency feedback loops
- No logic on clock/reset signals*
- Distribute clock & async. reset by fanout tree
- Never use reset for functionality (gated reset)

*terms and conditions may apply

986

Pros of synchronous clocking

- Glitches do not compromise functionality
- No chance for inconsistent data
- Immunity to noise and interference
- All timing constraints are one-sided; enables to slow down or deactivate computation
- Deterministic behavior
- Enables separation of functional verification from timing analysis
- Automated tool support
- Simplified functional circuit testing and verification

987


But how about enable signals and clock gating?

Never have logic on clock signal!!!

988

Rule: Never use logic on clock signal

 
- Very few exceptions: **only if you know what you are doing!**



989

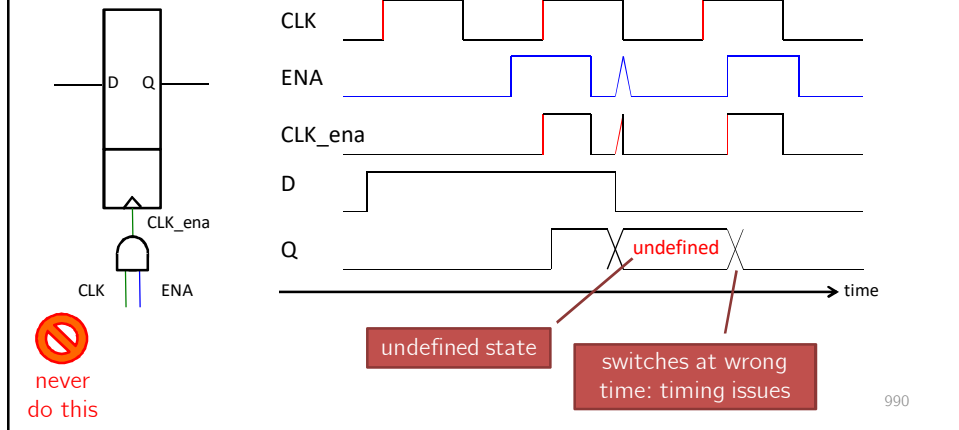
Problems with this approach

- Glitches on ENA (will) cause failures
- Timing issues




Safe flip-flop with ENA

 - Compliant with rules for synchronous design
- No logic on clock signal
- Not efficient from energy perspective: clock still active
 - Solution: safe clock gating



Clock gating

 
- Idea: Switch off clock to disable flip-flop(s)
- Significantly reduces dynamic power consumption of entire subcircuits



- AND gate on clock path disables activity of flip-flop
- Glitches cause failures

992

Clock gating (cont'd)

 


- Ensure that glitches and early ENA release signals do not contaminate CKG signals!
- Modern standard-cell libraries often include robust clock-gate cells

993

Safe clock gate implementation

- Single-edge triggered clock gate:

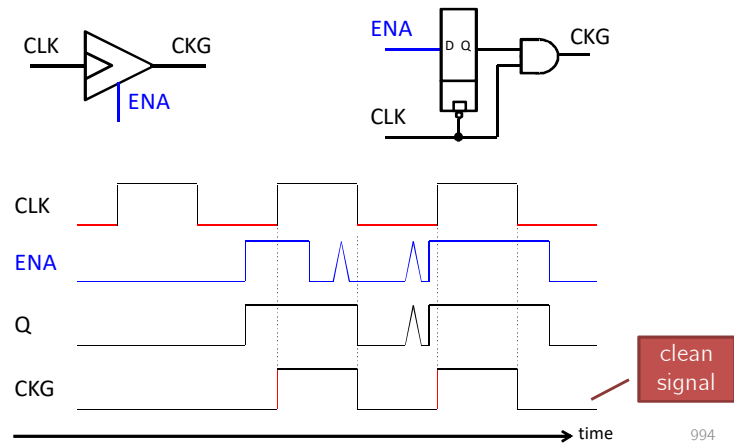

Every sequential circuit needs this!

Reset

995


The reset signal

- Required to force circuit into predefined state (initialization)
- Determines **when** to enter a given state
- Usually applied at beginning of time/operation
- Rarely applied during operation
→ common exception: watchdog



996

Synchronous reset

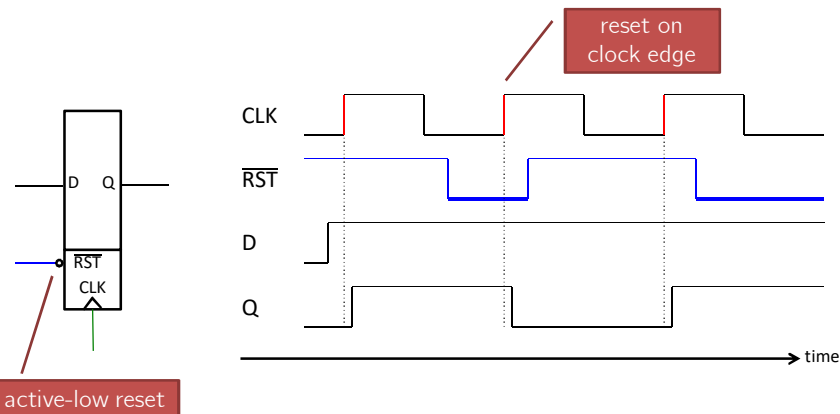

- Resets whenever $\overline{RST}=0$ and at clock edge
- Applied as any other input to flip-flop


997

Why is reset usually active low?

- During power-up, keeping !RST=0 is more safe as voltage high level where gates are operating correctly is not clearly defined
 - Low level (GND) is always clearly defined
- It is easier for external sources (e.g., switches) to safely provide active low signal
 - Active high requires V_{DD} available at at switch
- Also a historical reason from TTL circuits:
 - Could easily produce GND but not VDD
 - Can sink more current than source

998

Synchronous reset (cont'd)

 

- !RST signal behaves as regular input signal
- Versions that set FF to 1 also exist


999

Synchronous reset (cont'd)

- Synchronous reset advantages
 - Circuit completely synchronous
 - (Sometimes smaller flip-flops)
- Synchronous reset disadvantages
 - Reset tree required to ensure all resets occur in same clock cycle
 - May require pulse stretch to ensure that all flip-flops see !RST signal at rising clock edge
 - Requires a clock to be present

1000


Asynchronous reset

 

- Resets state whenever !RST is low
- Clock edges do not matter

1001

Asynchronous reset (cont'd)

 

- NAND gate either sets output to 1 (if !RST low) or inverts A

!RST	A	!(RST*A)
0	0	1
0	1	1
1	0	1
1	1	0

From H. Kaeslin, "Digital Integrated Circuit Design,"
Cambridge Univ. Press, 2008


1002

Asynchronous reset (cont'd)

- **Asynchronous reset advantages**
 - Reset has priority over any other signal
 - Reset happens without clock present
 - Data paths are always clear of reset signals
 - Synthesis tools understand what is going on
- **Asynchronous reset disadvantages**
 - Reset de-assertion (=release) must occur within the same clock cycle for all flip-flops
 - Reset line is sensitive to glitches at any time

1003


Fully asynchronous reset

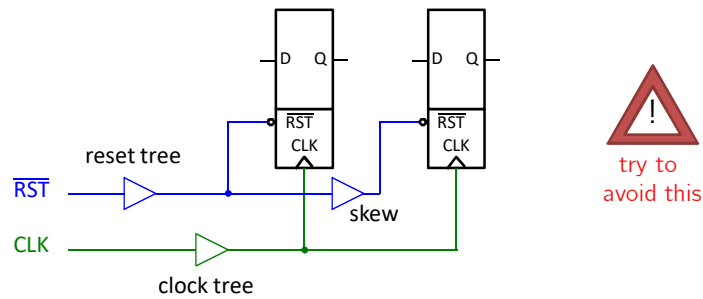

- One must be careful that reset de-assertion (\overline{RST} from 0 to 1) happens in same cycle
- This approach should be avoided

1004


Fully synchronized async. reset

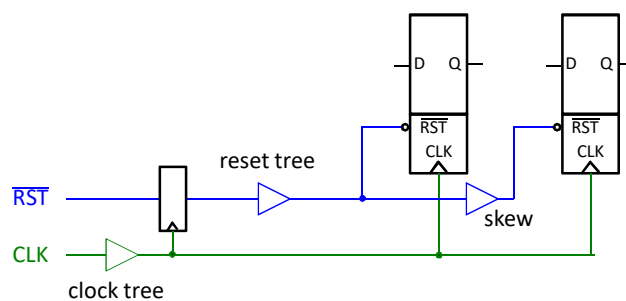

- Reset and de-assertion happens in synchronous way (w.r.t. the clock signal)
- Can use tools to generate reset tree

1005

Async. reset, synch. de-assertion

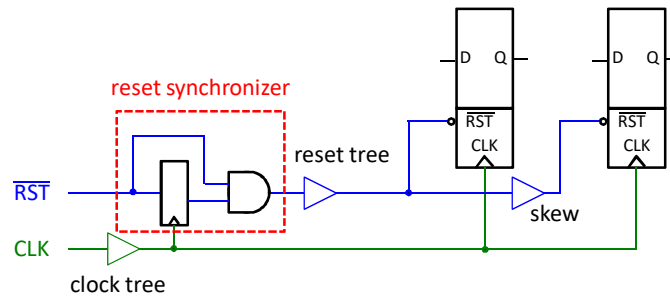


- Reset is applied in fully asynchronous way
- De-assertion in synchronous way
- Can use tools to generate reset tree

1006

Include reset in ALL flip-flops*

- A simple example
- [Reset cycle](#)

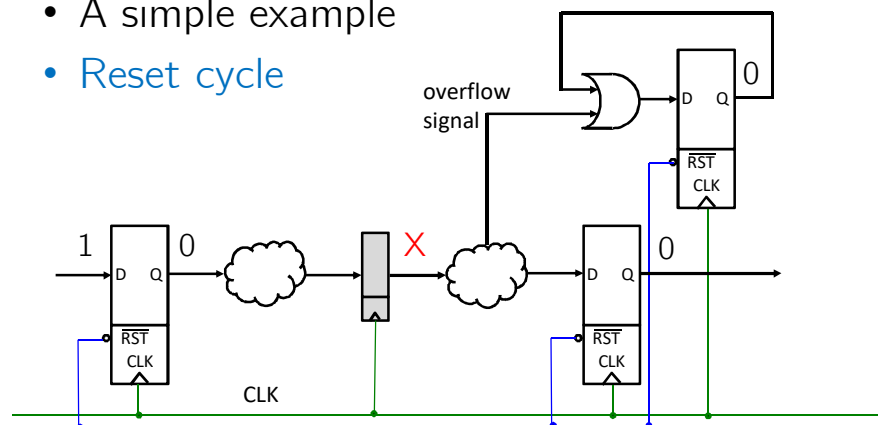


*unless you are a pro; but even then, think thrice (and also think about this slide)

1007

Include reset in ALL flip-flops*

- A simple example
- Cycle 1

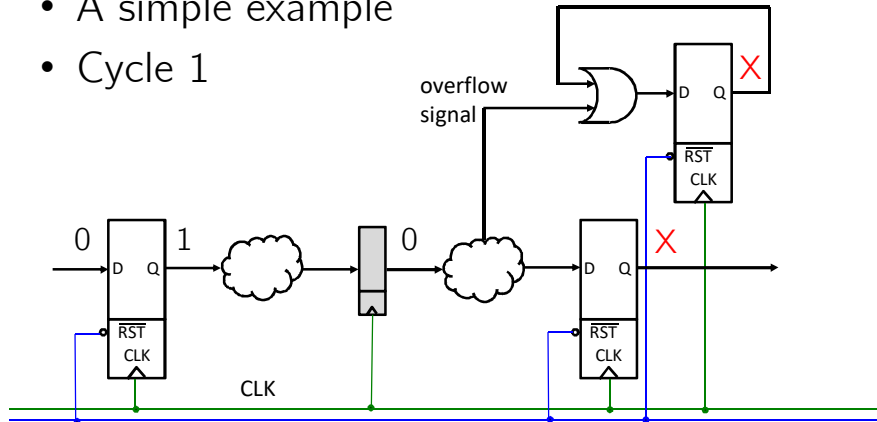


*unless you are a pro; but even then, think thrice (and also think about this slide)

1008

Include reset in ALL flip-flops*

- A simple example
- Cycles 2,3,.....

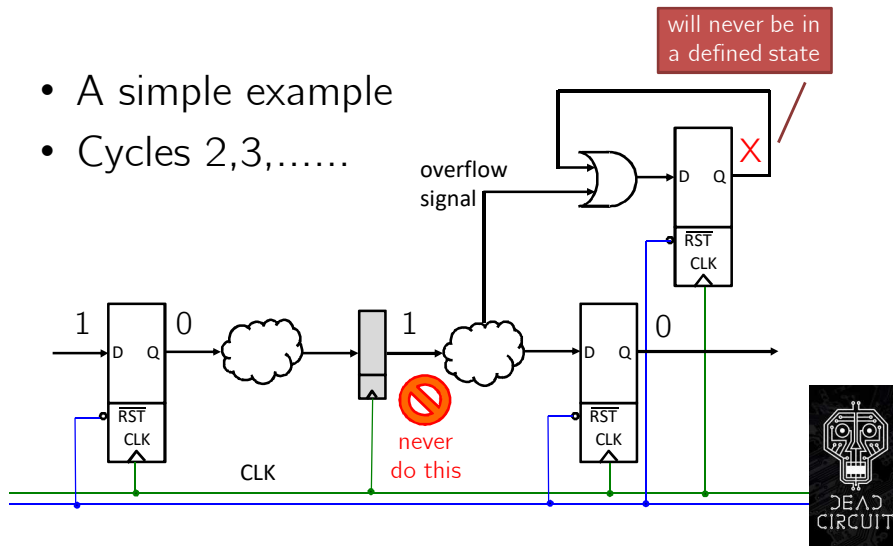

*unless you are a pro; but even then, think thrice (and also think about this slide)

1009

Things to remember

- Glitches must be avoided on reset signal
- No logic on reset signal allowed
- **Never use reset to implement functionality**
- Careful with timing on reset signal
- Distribute reset signal by fanout tree
- **All flip-flops should have a reset input**
 - Simplifies design for test
 - Avoids unknown states that remain forever


1010

Acquisition of asynchronous data

Synchronization

1011


Signals between two clock domains

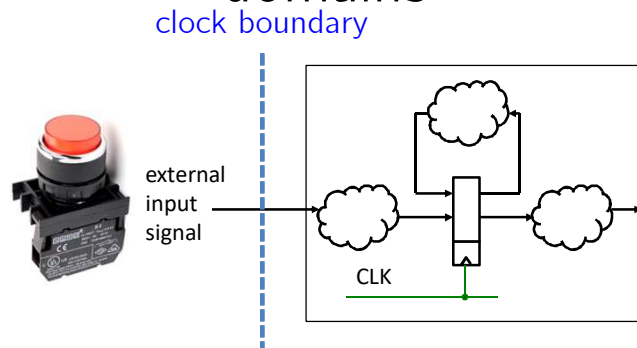

- External input signal is not synchronized to the CLK signal within the RHS circuit
- Can also be signal from another clock domain!

1012



Signal may not be sampled correctly

 

- Signal may violate setup/hold timing
- Signal may remain metastable for long time

1013

Remember metastability?

  

- Once FF goes metastable, can stay infinitely long at metastable point
- **Common model: Probability of staying at C decreases exponentially over time**

1014

Model for metastability


- Probability that metastability remains longer than time t' can be approximated as

$$P(t_{DQ} > t') = \frac{T_0}{T_c} \exp\left(\frac{-t'}{\tau_s}\right)$$

- t_{DQ} , time from input to output
- T_0/T_c describes probability that input changes during setup/hold time (aperture)
- τ_s and T_0 can be obtained from simulations

1015

The “solution”: Synchronizer FF

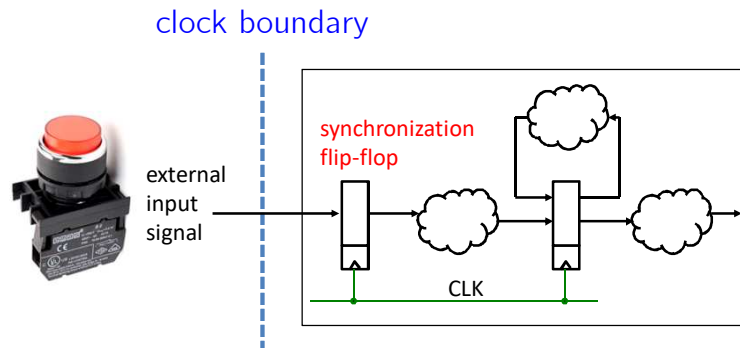

- Synchronization flip-flop reduces likelihood of metastability **but does not solve the problem**

1016

Probability of synchronizer failure

$$P(\text{failure}) = N \frac{T_0}{T_c} \exp\left(\frac{-(T_c - t_{\text{setup}})}{\tau_s}\right)$$

- Models probability of failure per second
 - N average number of asynchronous input changes per second
 - T_c = clock period
 - T_{setup} = setup time

1017

Mean-time between failure (MTBF)

$$MTBF = \frac{1}{P(\text{failure})} = \frac{T_c}{NT_0} \exp\left(\frac{T_c - t_{\text{setup}}}{\tau_s}\right)$$

- MTBF is a design parameter
- Set to 1e19 seconds (lifetime of universe)
- MTBF can be increased by
 - Fewer switching events
 - Longer period, smaller setup time

1018


Example: single synchronizer

$$MTBF = \frac{1}{P(\text{failure})} = \frac{T_c}{NT_0} \exp\left(\frac{T_c - t_{\text{setup}}}{\tau_s}\right)$$

- Example parameters in 0.25um process:
 - $\tau_s = 20$ ps
 - $T_0 = 15$ ps
 - $N = 50$ MHz
 - $T_c = 0.5$ ns (ignore setup time)
- What is the MTBF?

1019


Solution: Multiple synchronizer FFs

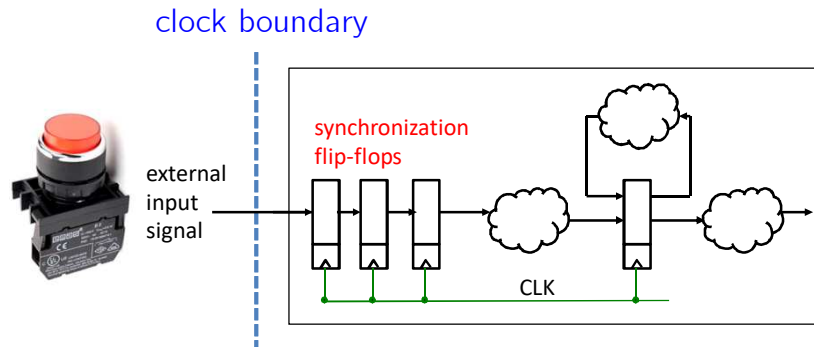

- Cascading multiple synchronization flip-flops reduces probability of failure (increases MTBF)

1020

How about multiple parallel signals?

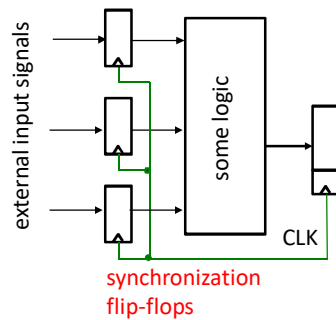

- Problem: “fast bits” and “slow bits” may be sampled in different periods
- Multiple sequential sync. FFs do not help!

1021

