

ECE4740: Digital VLSI Design

Lecture 28: Memories


1024

Contribute significantly to area and power of VLSI circuits

Semiconductor memories

1025


Memory hierarchy in a processor

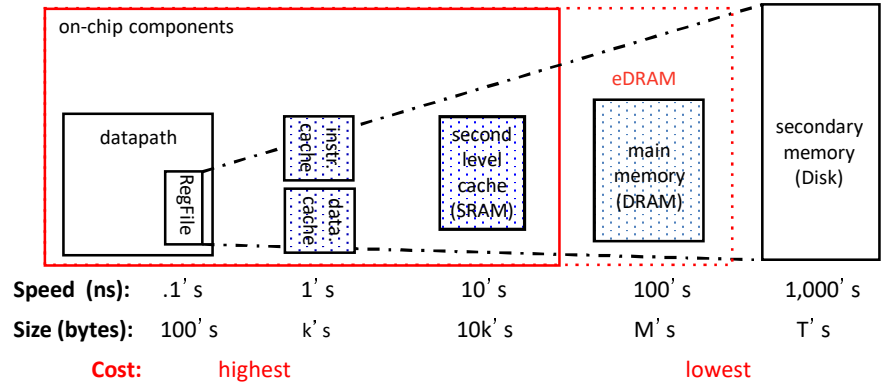

- Exploit locality:
 - large amount of cheap memory
 - sufficient amount of fast, expensive memory

1026

Memories in an ASIC

 

- Critical data stored in flip-flops within datapath
- Small memories, typically build from standard-cell based static cells (latches or flip-flops)
- Larger amounts of data stored in SRAM macrocells
- Off-chip DRAMs store GBs of data

1027

Semiconductor memories

read/write memories		non-volatile		
RWM		NVRWM		ROM
Random Access	Non-Random Access	EPROM	Mask-programmed	
SRAM (cache, register file)	FIFO/LIFO	E ² PROM		
DRAM	Shift register CAM	FLASH	Electrically-programmed (PROM)	

- 50% (growing) of silicon area is memory in most designs
- Often limits throughput or energy efficiency

1028

Also this: write-only memories

signetics FULLY ENCODED, 9046 X N, RANDOM ACCESS WRITE-ONLY-MEMORY **25120**

FINAL SPECIFICATION⁽¹⁰⁾

DESCRIPTION

The Signetics 25000 Series 9046XN Random Access Write-Only-Memory employs both enhancement and depletion mode P-Channel, N-Channel and Neu¹¹ channel MOS devices. Although a static device, a single TTL level clock phase is required to drive the on-board multi-port clock generator. Data refresh is accomplished during CB and LH periods⁽¹¹⁾. Quadri-state outputs (when applicable) allow expansion in many directions, depending on organization.

INPUT PROTECTION


All terminals are provided with slip-on latex protectors for the prevention of Voltage Destruction. (PILL packaged devices do not require protection.)

COOLING



The 25120 is easily cooled by the employment of a six foot fan 1/2"ility is from the package. If the device fails you have exceeded the ragings. In such cases, more air is recommended.

APPLICATIONS

 
- DON'T CARE BUFFER STORES
- LEAST SIGNIFICANT CONTROL MEMORIES
- POST MORTEM MEMORIES (WEAPON SYSTEMS)
- ARTIFICIAL MEMORY SYSTEMS
- NON-INTELLIGENT MICRO CONTROLLERS
- FIRST-IN NEVER-OUT (FINO) ASYNCHRONOUS BUFFERS.
- OVERFLOW REGISTER (BIT BUCKET)




1029

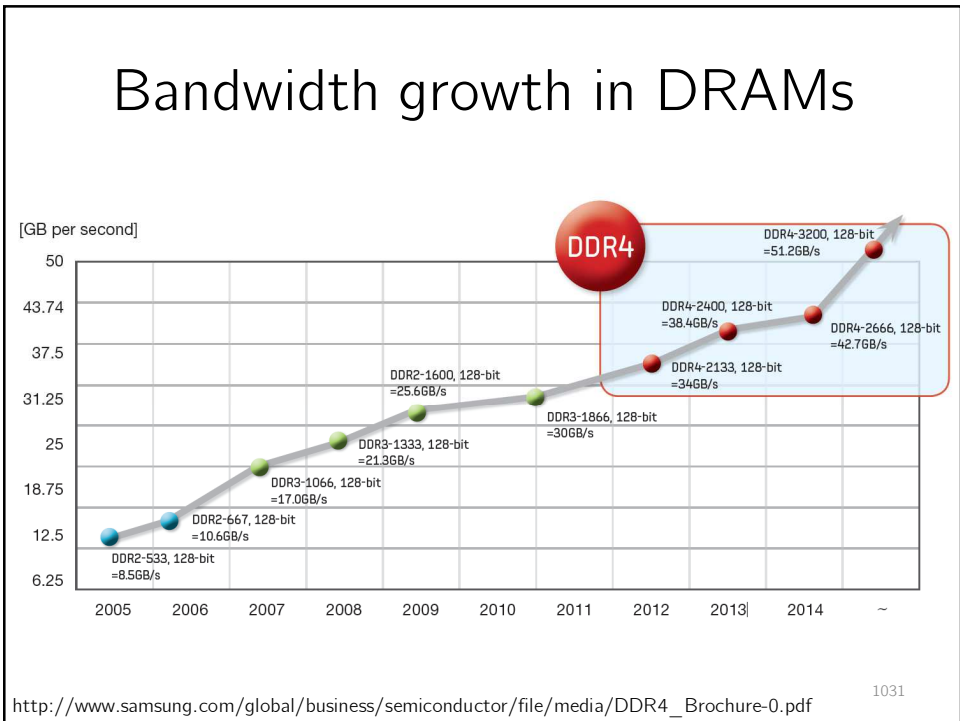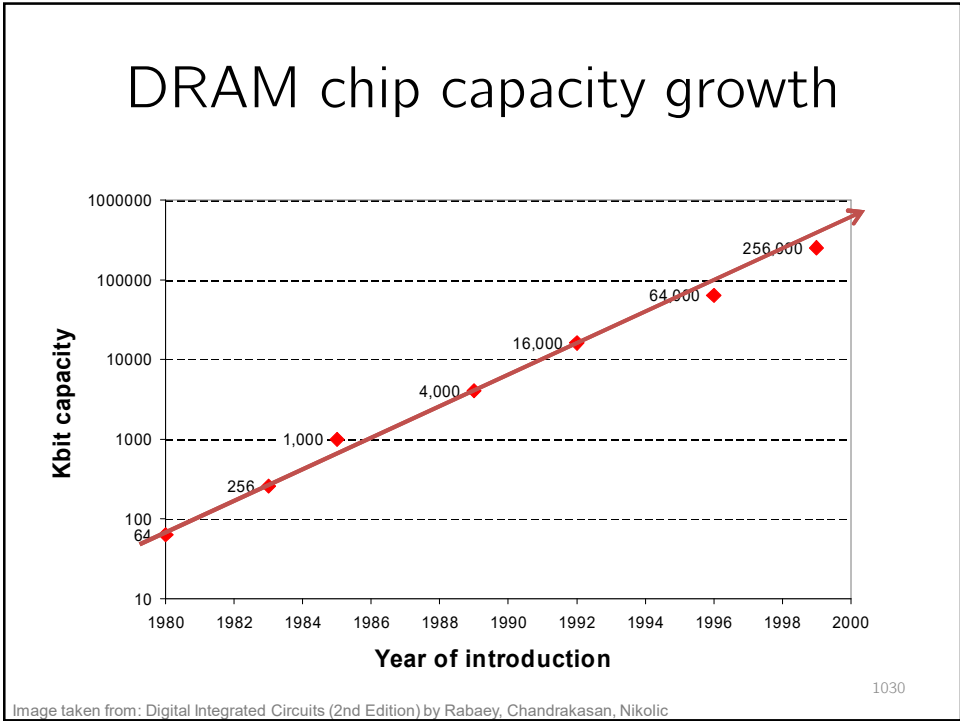


Memory architecture overview

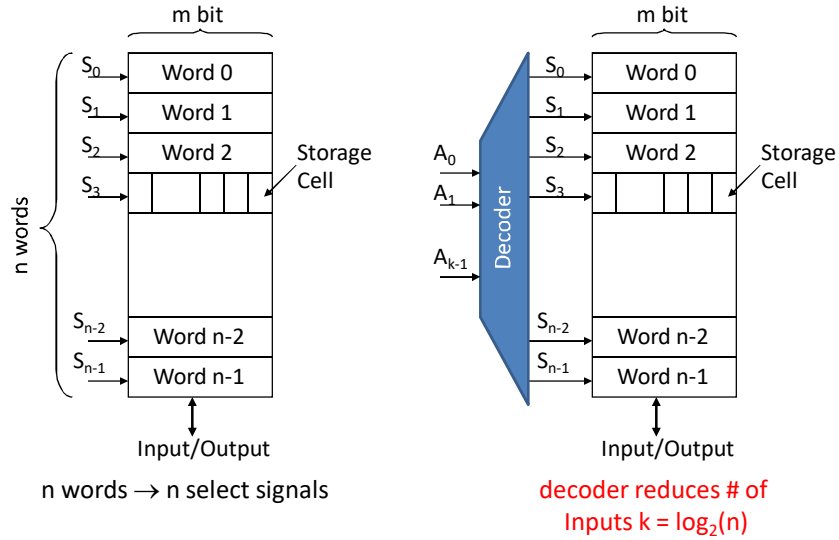

Memory architecture details

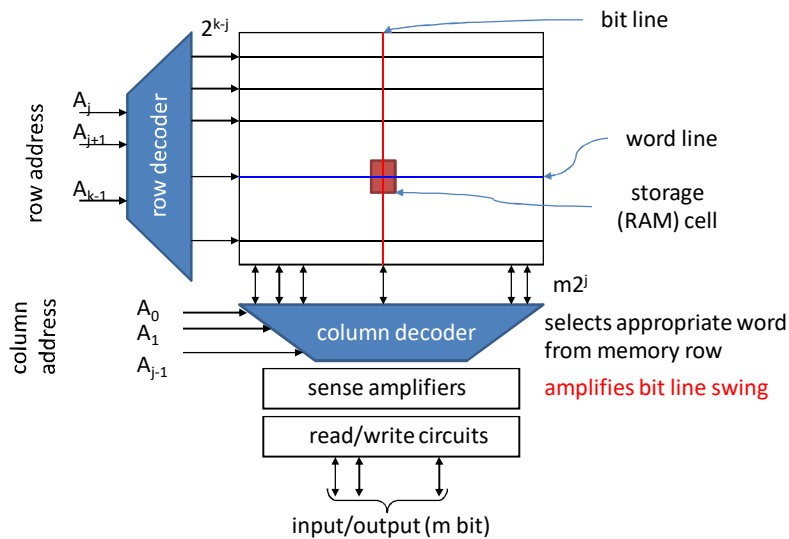

Split large memories in blocks/banks

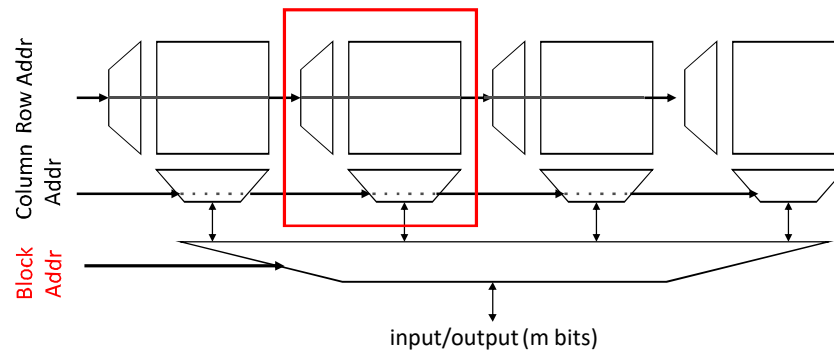

- Shorter word and bit lines → faster
- BlockAddr signal activates only 1 block → power reduction


1034

Useful for large look-up tables (LUTs)


Read-only memories (ROMs)

1035


Read-only memory cells

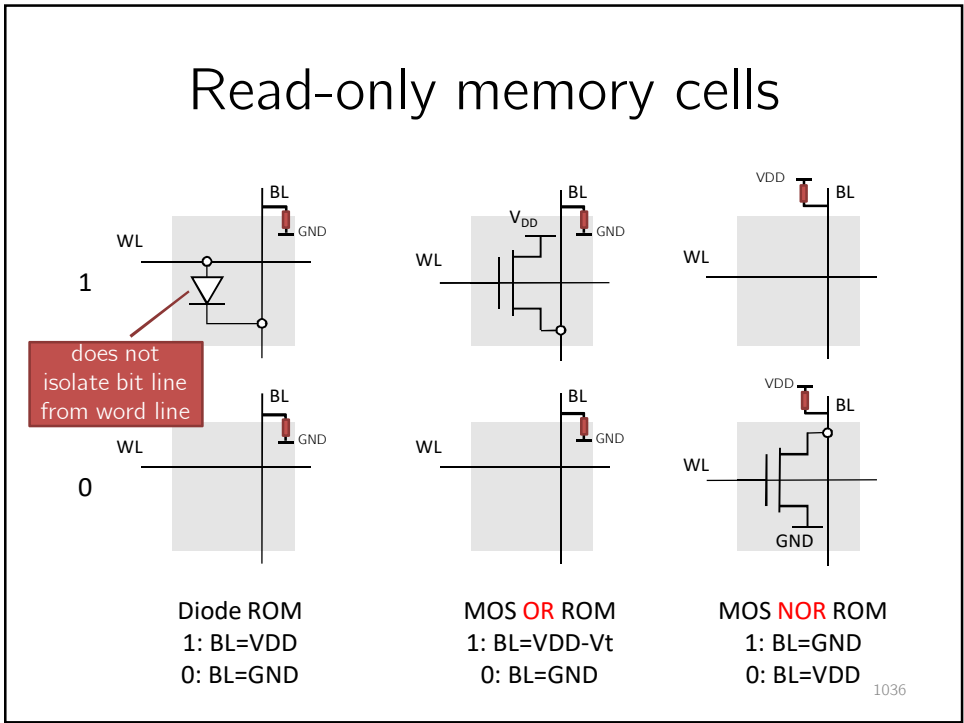

4x4 MOS OR ROM cell array

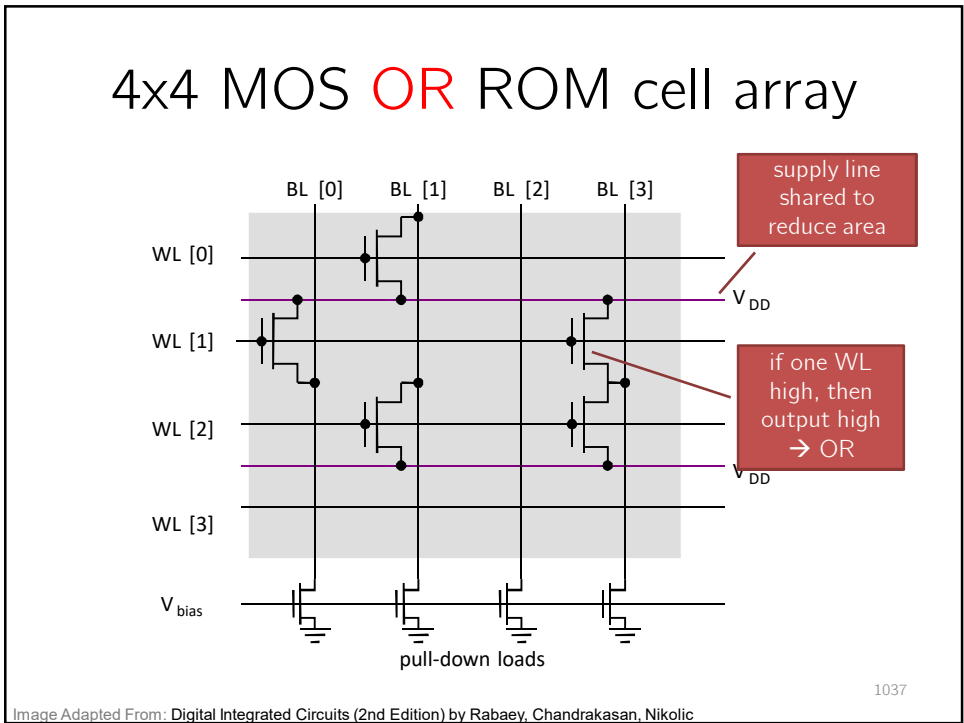


4x4 MOS NOR ROM cell array


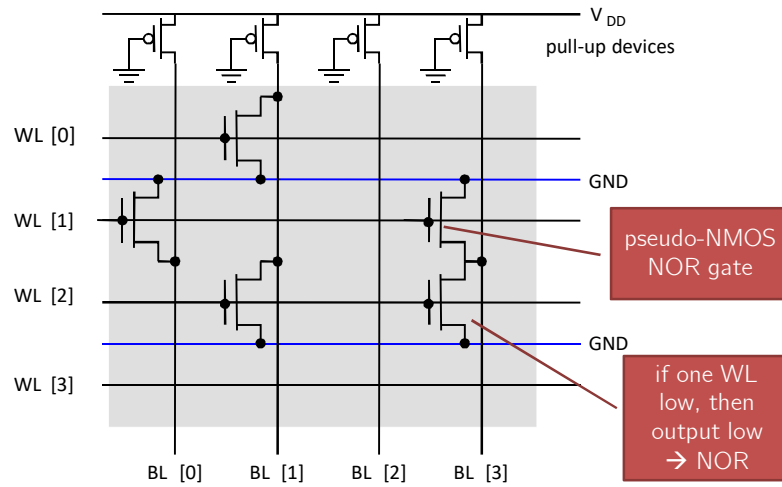


1038

MOS NOR ROM layout

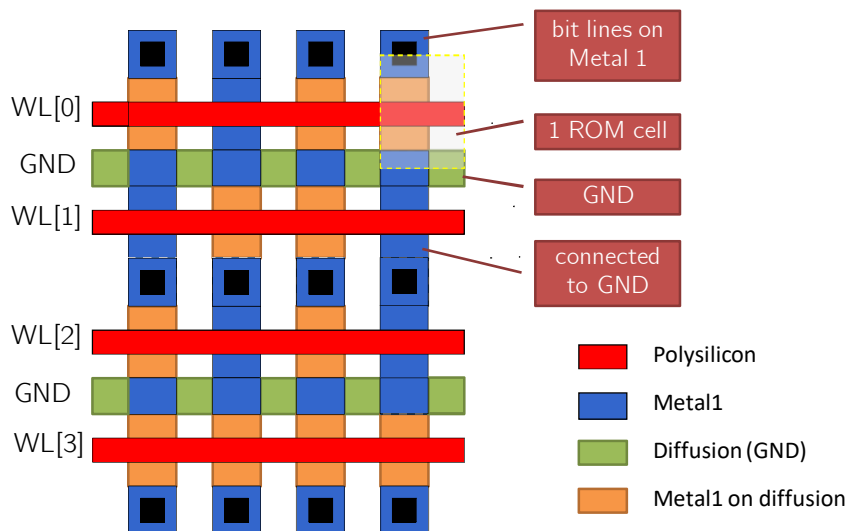

1039

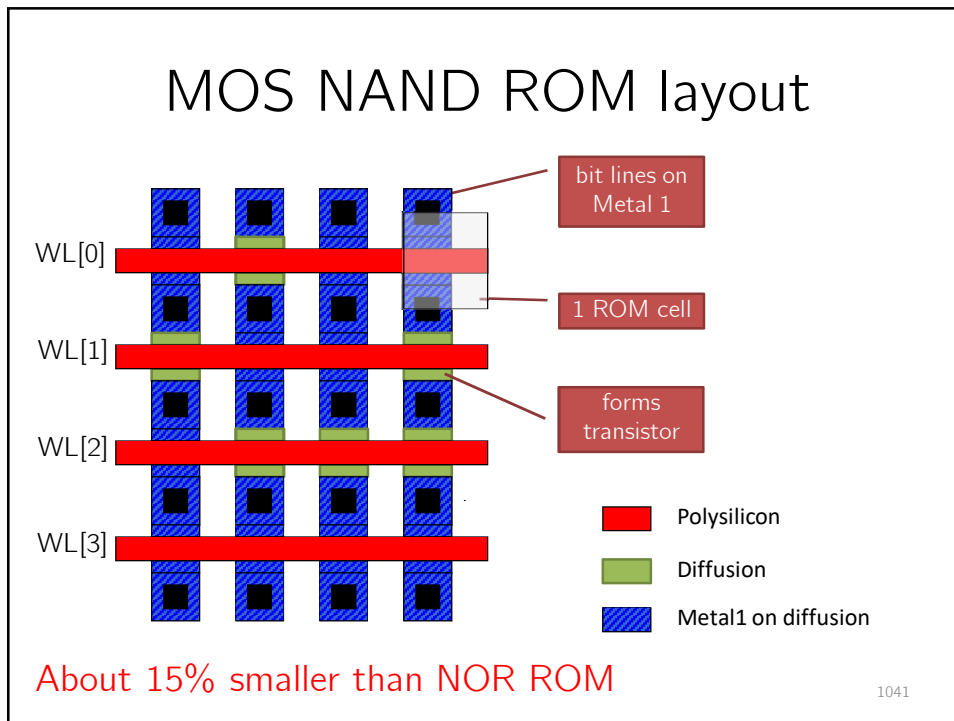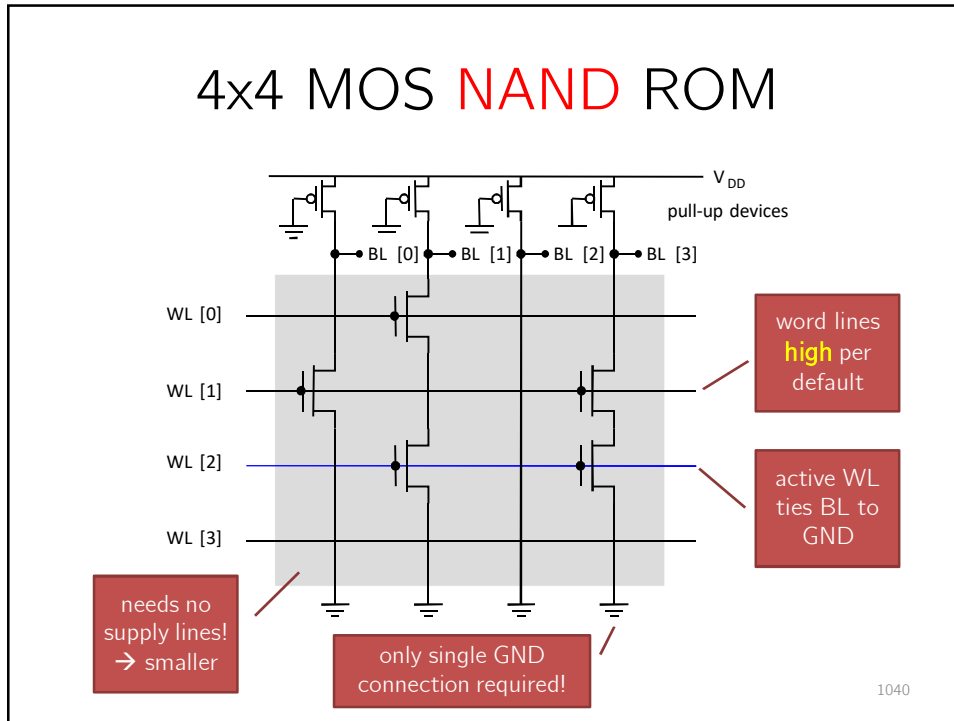


(Model for NOR ROM)

- **Word-line parasitics**

- Wire capacitance and gate capacitance
- **Wire resistance (polysilicon)**

NOR model

 


- **Bit-line parasitics**

- Resistance not dominant (metal)
- Drain and gate-drain capacitance

1042

Precharged MOS **NOR** ROM

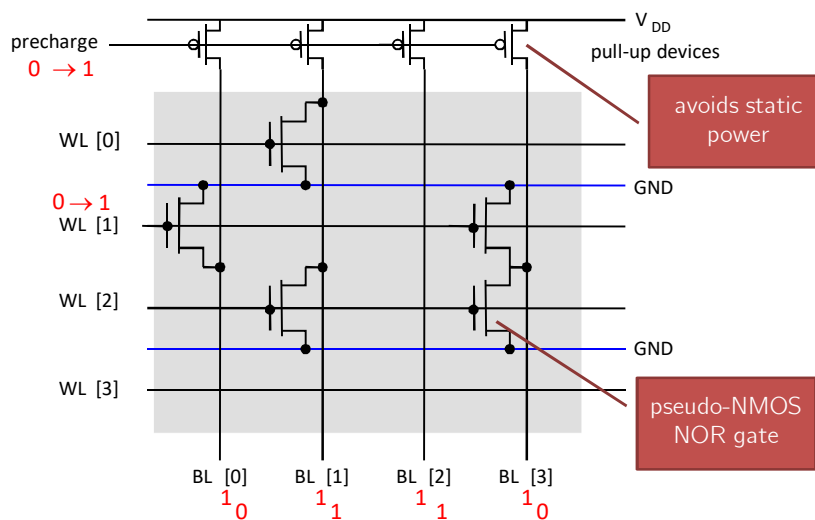

1043

Image adapted from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

(Model for NAND ROM)


- Word-line parasitics

- Wire capacitance and gate capacitance

- Wire resistance (polysilicon)

NAND ROM is smaller but also much slower!!!!

NAND model

 

- Bit-line parasitics

- Resistance of cascaded transistors dominates


- Drain/source and complete gate capacitance

1044

Remember: reducing word-line delay


- Use bypasses!

- Drive word line from both sides

 

- Use metal bypass (better materials)


e.g., use silicides

 

1045

ROMs for look-up tables (LUTs)

 - LUTs used in ASIC designs and some processors
 - Store fixed program (hard-coded software)
 - Fast division and square root units
 - Approximating arbitrary arithmetic functions



- Just set input value to word address and output value is ROM content
- ROM-based approach only useful for large LUTs

1046

RWM is hard to pronounce


Read-write memories (RAMs)

1047

Read-write memories (RAMs)

- Static: SRAM
 - Data is stored as long as supply is applied
 - Large cells (6T) → fewer bits per area
 - Fast (used where speed is important)
 - Differential outputs (BL and !BL)
 - Use sense amps for better performance
 - Compatible with CMOS technology
- Dynamic: DRAM
 - Requires periodic refresh
 - Small cells (1T to 3T) → more bits per area
 - Slower (used for large main memories)
 - Single-ended output (BL only)
 - Need sense amps for correct operation
 - Not typically compatible with regular CMOS technology


Memory timing

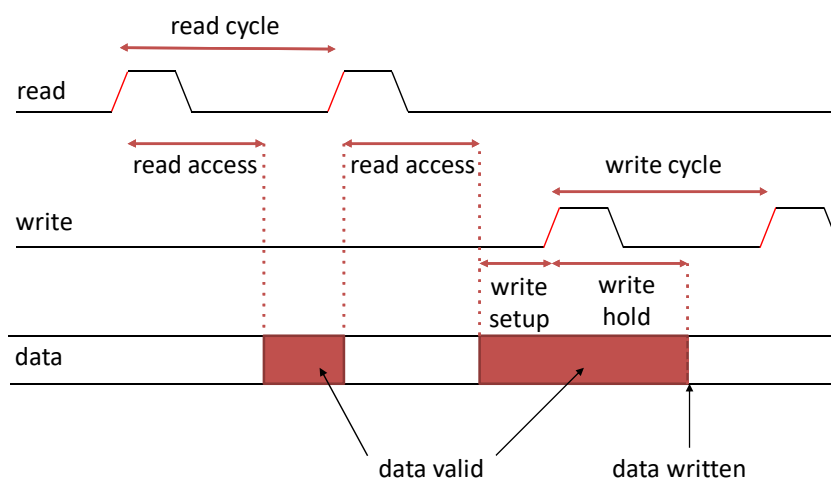

1049

SRAMs are used everywhere!

 
- Turbo-decoder ASIC for LTE
- 65nm CMOS
- 129kb SRAM
- Single-port only
- Runs at 300MHz



S, Benkeser, Belfanti, & Huang, 2011


1050

4x4 static RAM (SRAM)

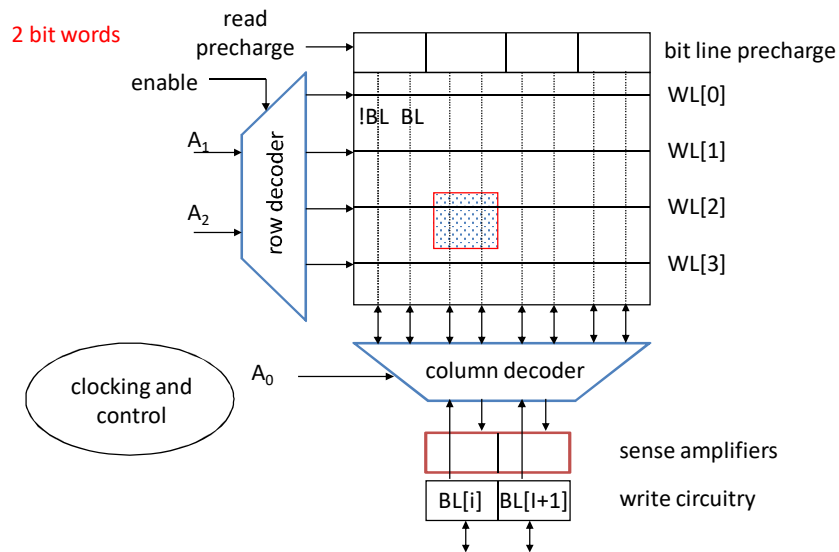

1051


2D memory configuration

 

1052

 Example: large SRAM


- UltraSparc 512KB cache SRAM
- Split into 4 subarrays
 - 4x 128KB subarrays
 - Each subarray consists of 16 8KB banks
 - Also includes control and cache circuitry



1053

Image taken from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris


6T SRAM cell

 

- Cross-coupled inverters → sizing critical

1054


6T SRAM cell: read

 

- Read disturb (read upset):
 - Bit-line capacitance C_{bit} can be in pF range
 - Limit allowed voltage rise on !Q to not change SRAM cell state

1055

(6T SRAM cell: read)

 

- Cell ratio: $CR = (W_1/L_1)/(W_5/L_5)$
- $\Delta V =$ maximum allowed voltage ripple


$$k_{n,M5} \left((V_{DD} - \Delta V - V_{Tn}) V_{DSATn} - \frac{V_{DSATn}^2}{2} \right) = k_{n,M1} \left((V_{DD} - V_{Tn}) \Delta V - \frac{\Delta V^2}{2} \right)$$

M5 = saturation
M1 = linear

$$\Delta V = \frac{V_{DSATn} + CR(V_{DD} - V_{Tn}) - \sqrt{V_{DSATn}^2(1 + CR) + CR^2(V_{DD} - V_{Tn})^2}}{CR}$$

1056

(6T SRAM cell: read)

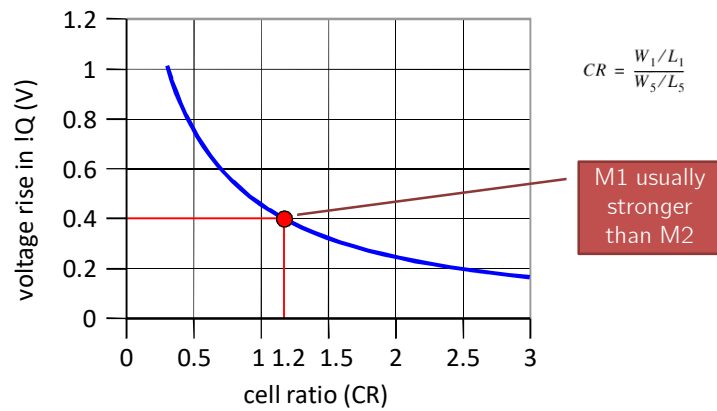


- Common cell ratios are 1.25 to 2

$V_{dd} = 2.5V, V_{Tn} = 0.5V$

1057


6T SRAM cell: write

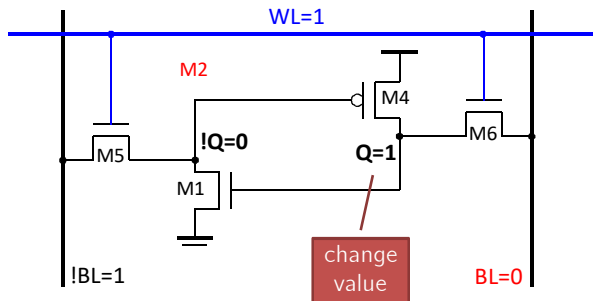

- Q=1 stored in cell, trying to write a 0
- M6 must be more conductive than M4 to pull node Q low enough for M1 & M2

1058

(6T SRAM cell: write)

 

- Pullup ratio: $PR = (W_4/L_4)/(W_6/L_6)$


$$k_{n,M6} \left((V_{DD} - V_{Tn}) V_Q - \frac{V_Q^2}{2} \right) = k_{p,M4} \left((V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)$$

$$V_Q = V_{DD} - V_{Tn} - \sqrt{(V_{DD} - V_{Tn})^2 - 2 \frac{k_p}{k_n} PR \left((V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)}$$

M4 = saturation
M6 = linear

1059

(6T SRAM cell: write)

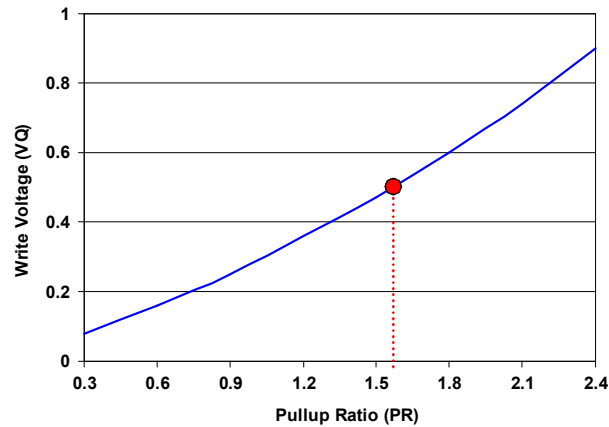

- Node Q must be pulled below V_{Tn}

$V_{dd} = 2.5V, |V_{Tp}| = 0.5V, \mu_p/\mu_n = 0.5$

1060

Cell sizing

- Keep cell size minimized → max. density
- Min-sized pull-down FETs (M1 and M3)
 - Requires min-width and longer-than-min-length PTs (M5 and M6) to ensure proper CR
 - Sizing of PTs increases load on bit lines
- Min-sized PTs can be used
 - Increase width of pull-downs (M1 and M3)
 - Reduces load on word lines but increases size

1061

Cell layout of 6T SRAM

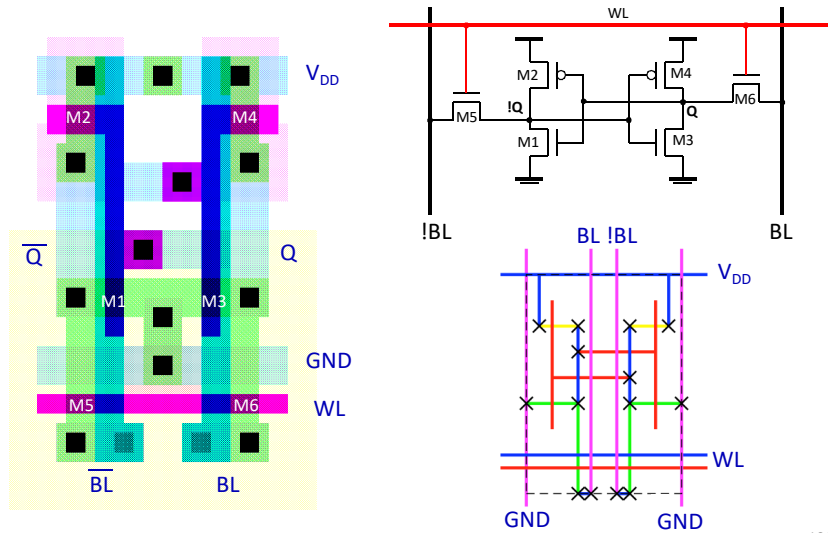



Image taken from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris

1062

Memories with multiple ports

- So far: single-port memories:
 - either read or write
- Dual (or two) port memories:
 - read and write, 2x read, or 2x write

 careful with sizing of PTs and also access contentions




1063

Reducing bit-line delay

- Reduce voltage swing
 - Needs sense amplifier to restore signal
- Isolate memory cells from bit lines after sensing → pulsed word line
- Isolate sense amplifiers from bit lines after sensing → **bit line isolation**

1064

Bit line isolation

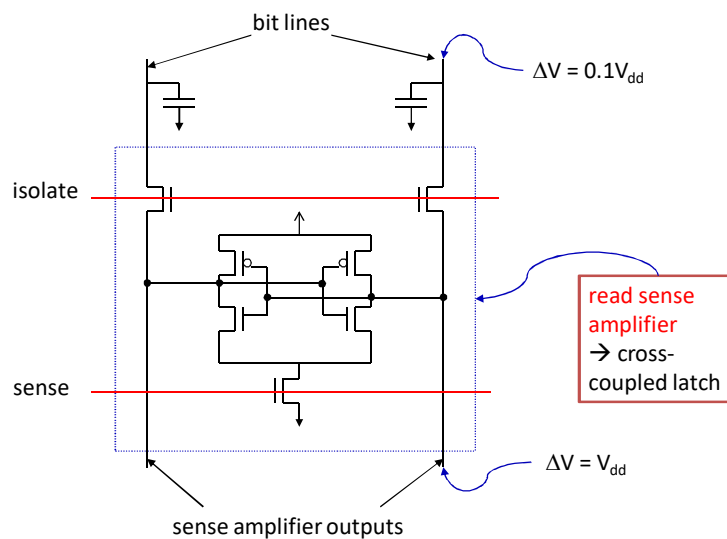

1065

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Higher density than static RW memories (SRAMs)

Dynamic RAM (DRAM)


1066

DRAM properties

- Requires periodic refresh
- Small cells (1T to 3T) → more bits/area
- Slower (used for large main memories)
- Single-ended output (bit-line only)
- Need sense amps for correct operation
- Typically not compatible with regular CMOS technology ☹


1067

4x4 dynamic RAM (DRAM)

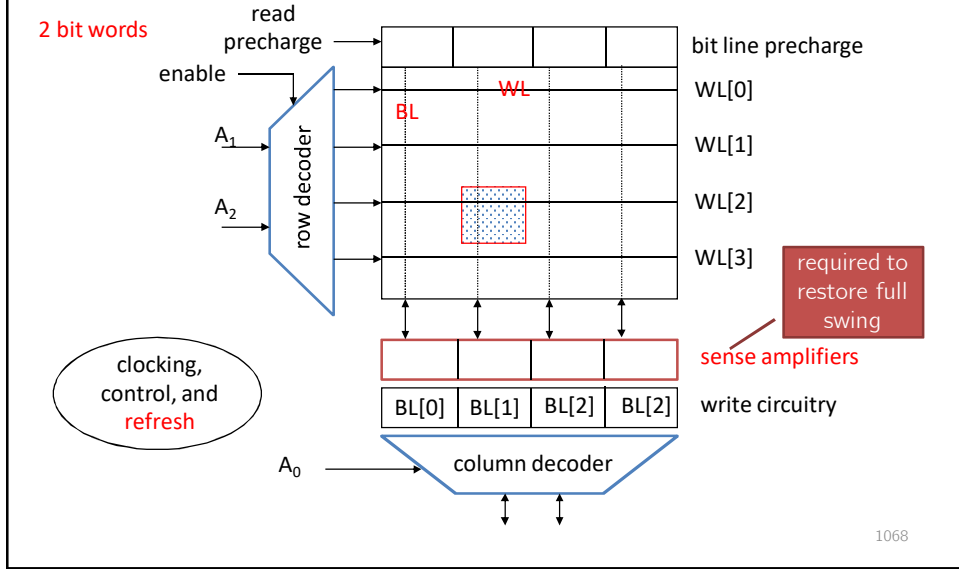

1068

3T DRAM cell

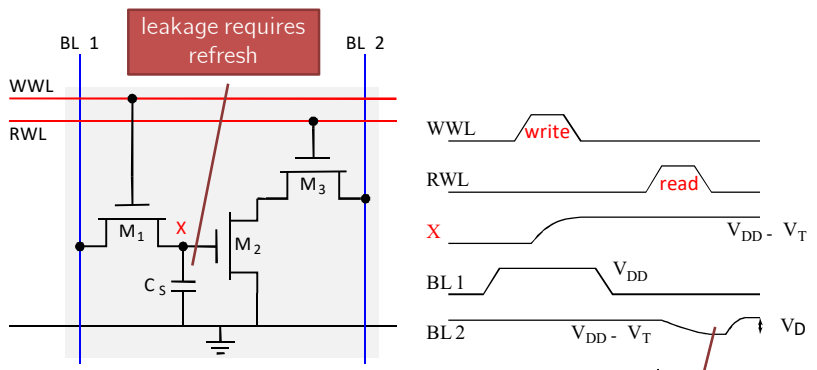


- No constraint on device ratios
- Reads are non-destructive
- Value stored at node X: "1" = $V_{WWL} - V_{Tn}$

reads are inverting!

1069

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Layout of 3T DRAM cell

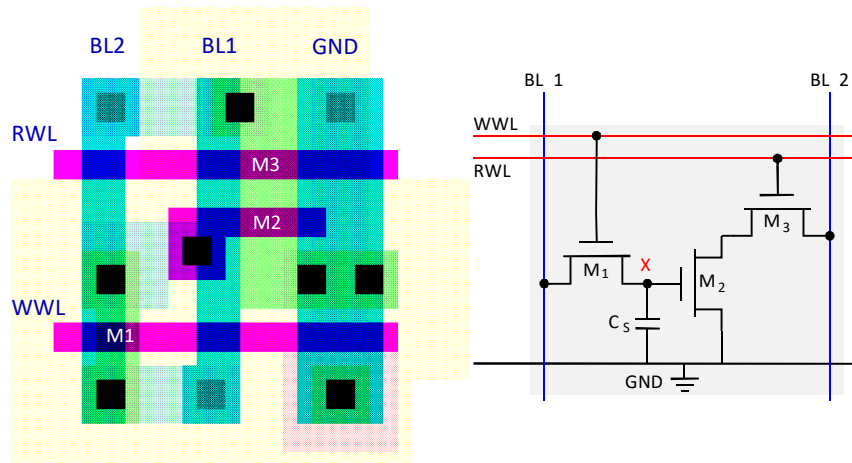


- About 2x smaller than SRAM cell

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

1070

1T DRAM cell

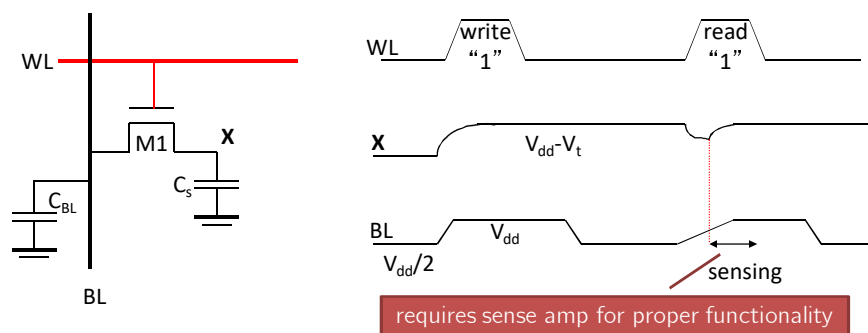


requires sense amp for proper functionality

- Write: C_S is charged (or discharged) by asserting WL and asserting (or lowering) BL
- Read: Charge distribution between C_{BL} and C_S
- Read is destructive → refresh after read

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

1071

Sense amplifier operation

 


- Sense amplifier needed for **functionality**

1072

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

1T DRAM cell properties

 - Output is single-ended (requires special sense amps)
- **Requires extra capacitor to store state**
- Not compatible with conventional CMOS processes



1073

Decoders, sense amps, etc.

Peripheral memory circuits

1074

Row decoders (remember Lab 2)

- M to 2^M decoder consists of 2^M logic gates
- Two main options:
 - NAND decoder

$$WL_0 = A_0 A_1 A_2 A_3 \dots A_6 A_7 A_8 A_9$$

$$WL_{511} = \bar{A}_0 \bar{A}_1 \bar{A}_2 \bar{A}_3 \dots \bar{A}_6 \bar{A}_7 \bar{A}_8 \bar{A}_9$$


- NOR decoder

$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$

$$WL_{511} = \overline{A_0 + \bar{A}_1 + \bar{A}_2 + \bar{A}_3 + \bar{A}_4 + \bar{A}_5 + \bar{A}_6 + \bar{A}_7 + \bar{A}_8 + \bar{A}_9}$$

1075


Hierarchical row decoding

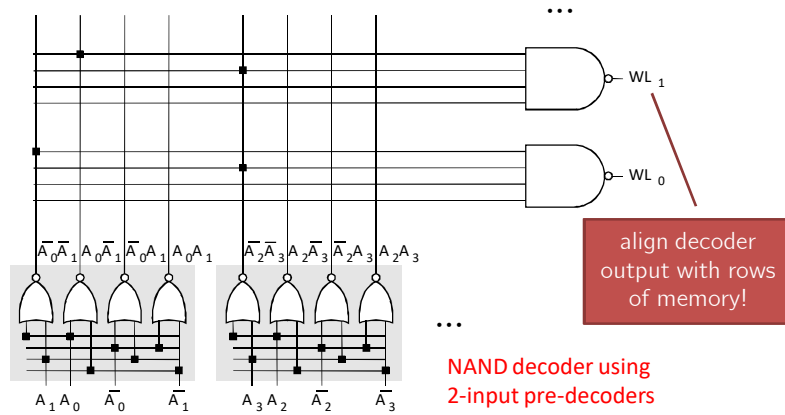

- Multi-stage decoding improves performance

1076

Dynamic NOR row decoder

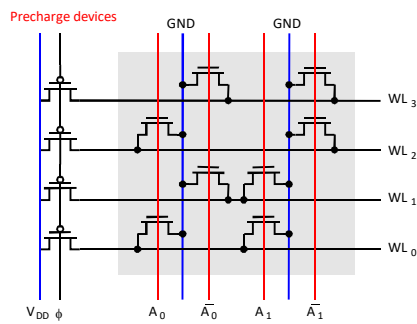


- Precharge all outputs high
- Then, GND inactive outputs
- Active “high” signals

- Signal goes through at most one FET
- Almost constant propagation delay

1077

Dynamic NAND row decoder

 


- Precharge all outputs high
- Then, discharge active output
- Active “low” signals

- All inputs must be low during precharge (prevent VDD and GND short)
- Slower than NOR implementation (3 FETs in series)

1078

PT-based column decoder

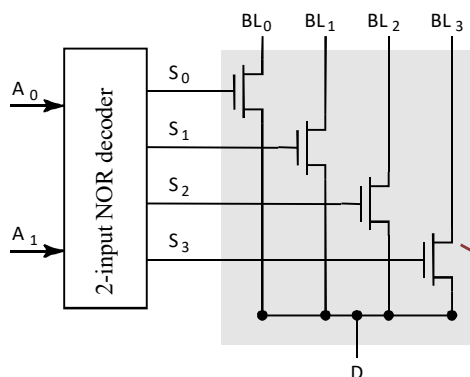


- One transistor per bit line
- $k \cdot 2^k$ transistors in total
- $k=10 \rightarrow 10240T$

SRAMs require 2x the transistors for BL and !BL

- Advantage: speed (only 1 extra T in path)
- Disadvantage: large transistor count

1079

Tree-based column decoder

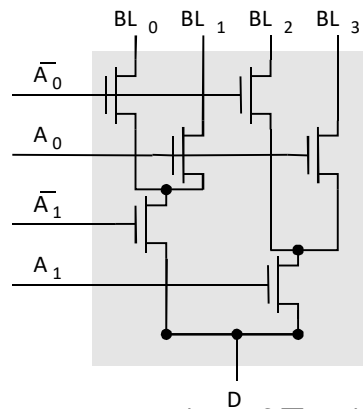


- One transistor per bit line
- $2 \cdot (2^k - 1)$ transistors in total
- $k=10 \rightarrow 2046T$

- Advantage: number of T reduced significantly
- Disadvantage: **delay increases quadratically with stages**
 - prohibitive for large decoders
 - Add buffers, progressive sizing, combination of tree and PTs


1080

Bit-line precharging: SRAM

static pull-up precharge

 

clocked precharge

 


equalization transistor:
equalizes levels
on BL and !BL

- Static: no precharge clock required, but consumes static power (fight against bit-line discharge)
- Clocked: can use large precharge devices and bit line equalization much faster, but large clock load

1081


Sense amplifiers

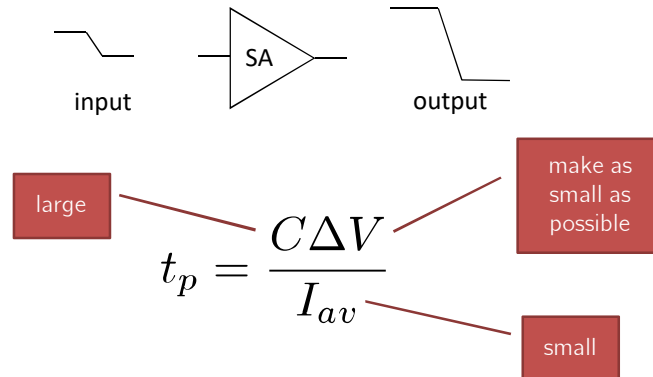- Amplifies small swing on bit lines to full rail-to-rail swing needed at memory output



1082


Differential sense amplifier

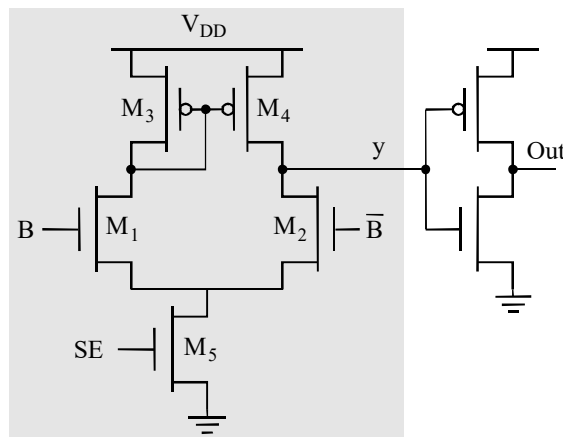


- Directly applicable to SRAMs

1083

Differential sensing (cont'd)

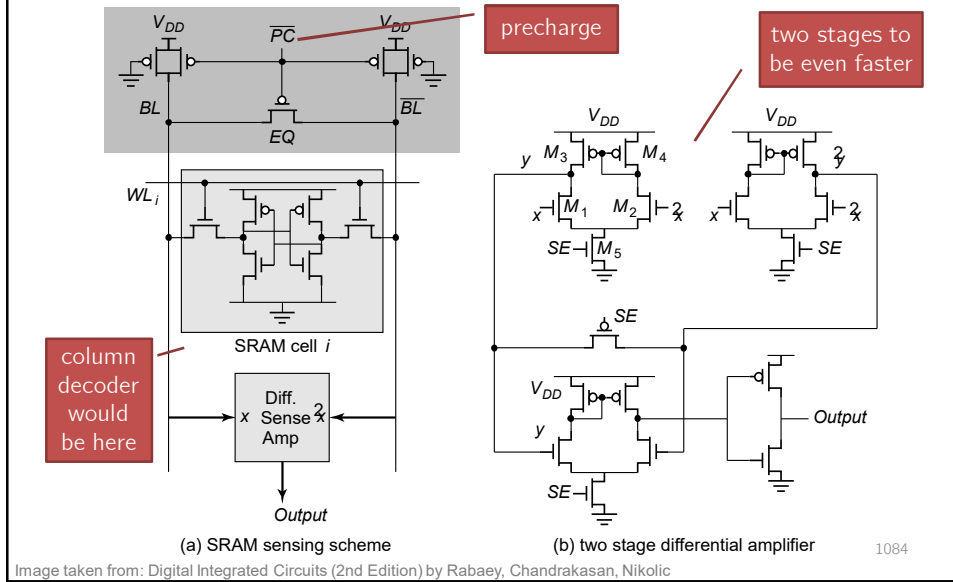


Latch-based sense amp

 

- EQ used to initialize latch in its meta-stable point
- Once adequate voltage established SE=1 enables sense amplifier
- Positive feedback quickly forces output to stable operating point

1085

Read/write circuitry

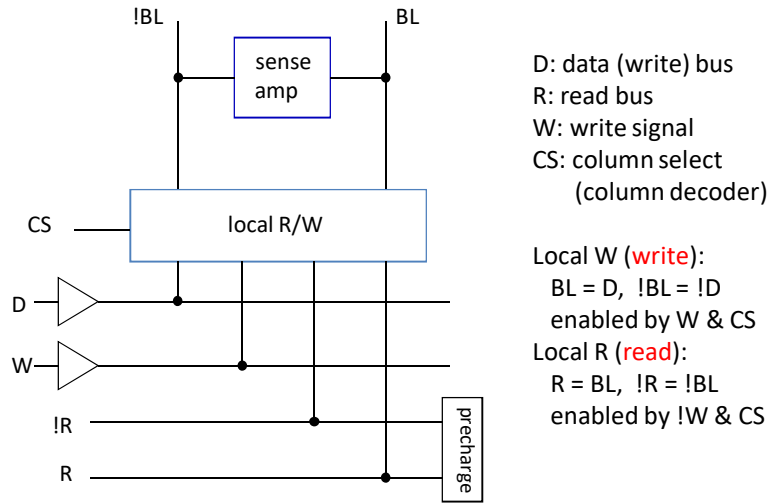

1086

Trade-off noise for density and performance

Reliability and yield

1087

Reliability and yield

- Semiconductor memories trade-off noise margin for bit density and performance
 - Sensitive to noise (crosstalk, supply noise, etc.)
- High-density and large die size causes yield problems:

A = chip area


D = defect density

$$\text{Yield} = 100 \frac{\# \text{ of good chips/wafer}}{\# \text{ of chips/wafer}} \quad Y = \left(\frac{1 - e^{-AD}}{AD} \right)^2$$

- Increase yield using error correction and redundancy

1088

Yield vs. chip area and process

 


- Yield curves at different stages of process maturity [Veendricks92]


1089

Soft errors

 - Ionizing radiation can cause non-recurrent and nonpermanent errors in memories




Redundancy in memory structure

 

- Replace bad row or column with "spare" → set by fuse bank
- Solves problem at manufacturing time, but not soft errors

Redundancy and error correction

- Suitable for preventing soft errors

 

1092

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Example: (7,4,3) Hamming code

- Consider 4-bit number $[B_3, B_5, B_6, B_7]$
- Add 3 parity check bits $[P_1, P_2, P_4]$
- Chose parity bits as follows:

$$\begin{array}{l}
 P_1 \oplus B_3 \oplus B_5 \oplus B_7 = 0 \quad 1 \\
 P_2 \oplus B_3 \oplus B_6 \oplus B_7 = 0 \quad 1 \\
 P_4 \oplus B_5 \oplus B_6 \oplus B_7 = 0 \quad 0
 \end{array}$$

• Error in bit B_3 would cause 1st and 2nd parity check to fail

• Implies that bit 3 is in error → can be corrected (flipped)

$$011 = 3$$

1093