

ECE4740: Digital VLSI Design

Lecture 29: Final lecture

1094

No ones favorite but crucial!

Design for test (DFT)

1095

Testing is important

- Testing is among the most expensive aspects of digital VLSI design:
 - Logic verification accounts for more than 50% of the design effort for most VLSI designs
 - Debug after fabrication incurs extreme costs
- Example: Intel FDIV bug (1994)
 - Logic error found after >1M parts shipped
 - Recall cost \$450M; image loss even worse

1096

Logic verification

- Does the design simulate correctly?
 - Verification engineers develop test-bench
 - Exhaustive tests often not possible
 - Test critical corner cases
- Example: 32-bit adder
 - Exhaustive testing: $>10^{19}$ combinations
 - Test only corner cases: 0,1,2, $2^{31}-1$, -1, -2^{31} etc.

designing
good tests
is difficult


1097

Silicon debugging

- Logic bugs vs. electrical failures
 - Most failures are logic bugs from insufficient simulations, bad testing strategy, etc.
 - Some are electrical failures: crosstalk, leakage, charge sharing, ratio failures, etc.
 - Some fabrication errors: process variation
- Fix the bugs and fabricate corrected chip
- Main goal: *First time right!*

1098

Finding errors late is expensive

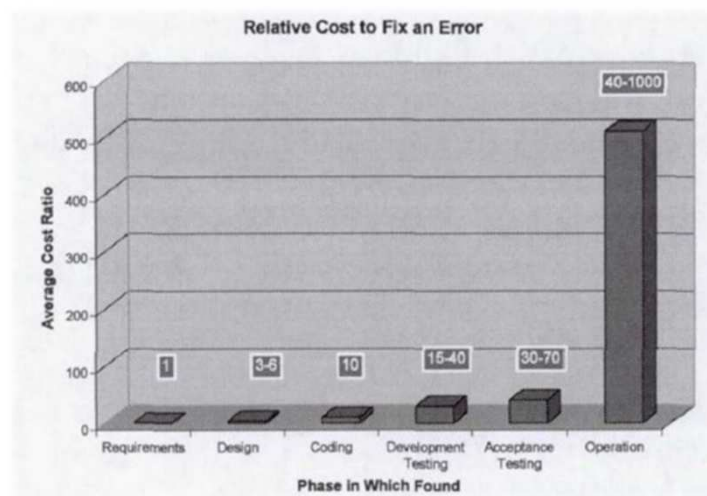


<http://www.power-supply-designer.com/review/>

1099

How to diagnose failures?

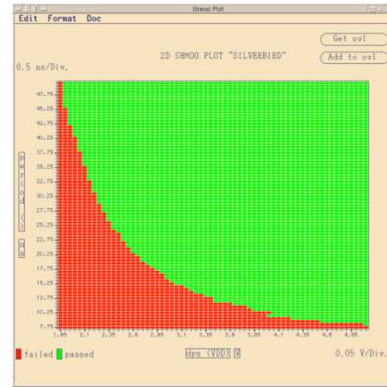- Hard to access chips:
 - Picoprobes on chip
 - Electron beam
 - Built-in self test (BIST)
- “Schmoo plots”
 - Vary voltage/frequency
 - Look for cause of electrical failures



From P. Luethi (<http://www.electronic-engineering.ch/study/silverbird/silverbird.html>)

1100

Manufacturing test

- Yield of any chip is <100%
 - Test chips before delivered to customers
- Manufacturing tests are expensive
 - Minimize test time/chip
 - Maximize # of failures you can detect



1101

Manufacturing failures

 


Image adapted from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris


1102

The "stuck-at" fault model

- Common failures are shorts between two conductors or opens in a conductor
 - Effect of such failures can be very complex
- Use a simpler model:
 - Assume all failures cause nodes to be "stuck-at" 0 or 1, i.e., short to GND or V_{DD}
 - Two types:
 - Stuck-at 1 (SA1)
 - Stuck-at 0 (SA0)

1103

Example stuck-at fault: NAND2

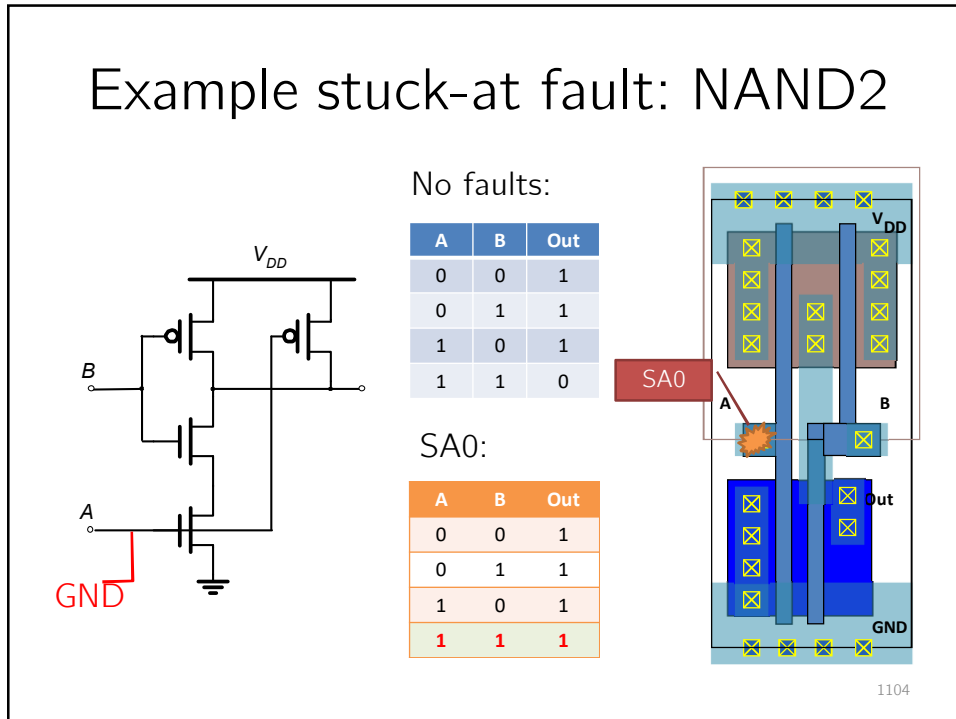

Observability and controllability

- **Observability:** able to observe internal node by observing external output (=pins) of chip
- **Controllability:** able to force internal node to 0 and 1 via inputs (=pins) of chip
- Combinational logic: nodes are rather easy to control and observe
- **Sequential logic: extremely difficult or even impossible to control and observe**


1105

Test pattern generation

- Generate inputs (=stimuli) and expected outputs (=responses) of a given design
- Apply smallest sequence of test vectors to prove that each node is **not stuck**
- **You have to ensure good observability and controllability of internal nodes:**
 - Reduces number of test vectors (lower cost)
 - Increases number of nodes that can be tested

1106

Example: NAND2

 

- **Min. test vector set: {01,11,10}**

A=SA0

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

A=SA1

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

B=SA0

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

B=SA1

| A | B | Out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

1107

Design for test (DFT)



- Idea: Design the chip to increase observability and controllability
- If each register could be observed and controlled, testing reduces to testing combinational logic between registers
- Even better: logic could enter test mode where they test themselves automatically

add test structures already during design

1108

Scan chain

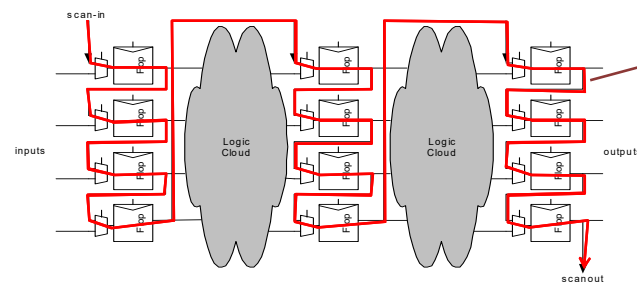 
- Convert each flip-flop to a scan register
 - Cost = one MUX
 - Scan mode: behaves as a shift register



in scan mode, we can set and read the state of each flip-flop

1109

MS ET flip-flop with scan capability

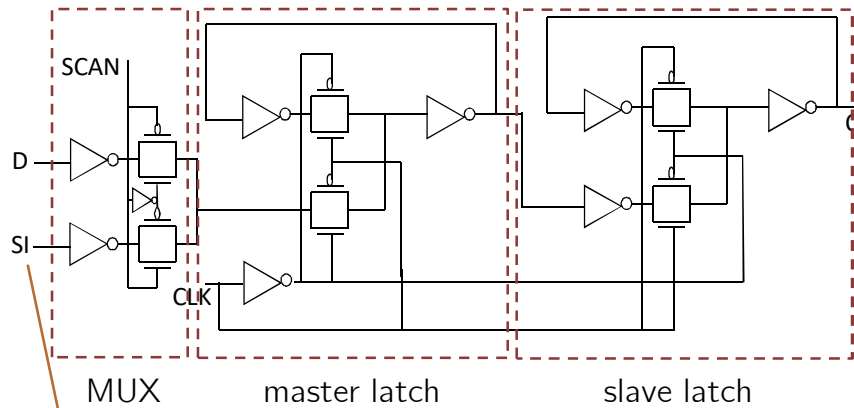


I could easily give one lecture only about scan chains

1110

Be able to reset your circuit

 - You must be able to set your circuit in a predefined state (think reset button!)
- Add reset functionality to each flip-flop



From H. Kaeslin, "Digital Integrated Circuit Design," Cambridge Univ. Press, 2008

1111


Automatic test pattern generation

- ATPG produces good set of vectors for each block of combinational logic
 - Scan chains used to control and observe blocks
- Complete coverage of all nodes requires large number of test vectors → expensive
- Most products have >95% test coverage
- Macrocells (SRAMs, ROMs, etc.) make good test coverage difficult

1112

Block isolation

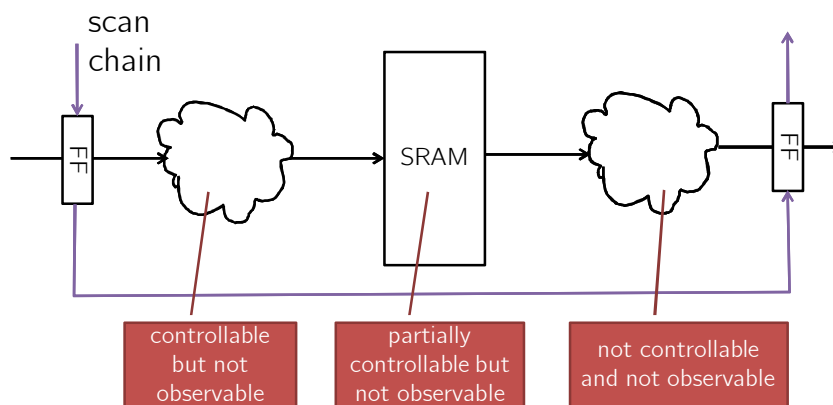
- Memories have usually no scan capabilities



1113

Block isolation (cont'd)

- Isolate macrocells (e.g., SRAMs)

 


- Logic now controllable and observable
- How to test the isolated block (=SRAM)?

1114

Built-in self test (BIST)

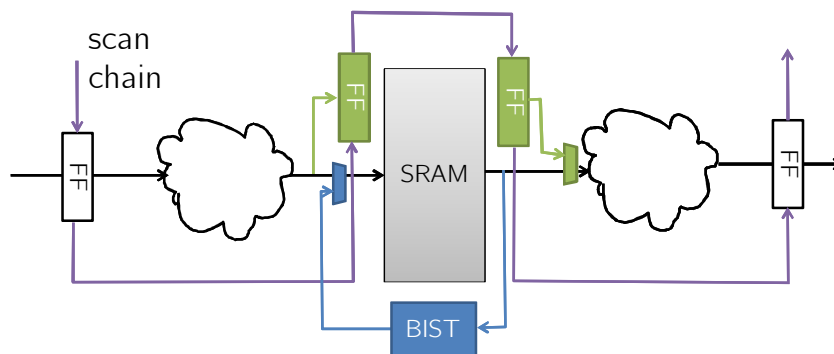- Add circuitry that tests the isolated block



- Usually write and/or read pseudo-random data

1115

Summary on design for test (DFT)

- Think about testing from the beginning
 - Simulate already during the design
 - Plan for test after fabrication
 - Add test structures (scan, BIST, isolation, etc.)
 - Try to get it “first time right”

**“if you don't test it,
it won't work (guaranteed!)”**

1116

Just the basics

Low power design techniques

1117

Sources of power consumption

$$P = \sum_k P_{dyn,k} + P_{dp,k} + P_{stat,k}$$

- Dynamic power consumption
 - Switching: $P_{dyn,k} = V_{DD}^2 f_{clk} \alpha_k C_k$
 - Direct-path: $P_{dp,k} = \frac{\beta \alpha_k}{24} (V_{DD} - 2V_T)^2 t_{ra,k}$
- Static power consumption
 - Leakage: $P_{stat,k} = I_{stat,k} V_{DD}$

1118


Reduce number of gates

- Reduces all 3 sources of power consumption
- Optimization on algorithm level
 - Use (or design new) algorithm that requires smallest number of gates for given throughput
 - Our research area
- Optimization on circuit level
 - Use logic optimization (tools)
 - Minimize circuit area in non-critical paths

1119


Reduce switching activity: Clock gating

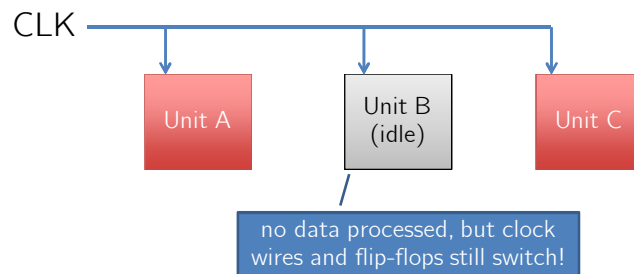- Most popular method for power reduction
- Gate clock signal if part of circuit is idle



1120


Clock gating

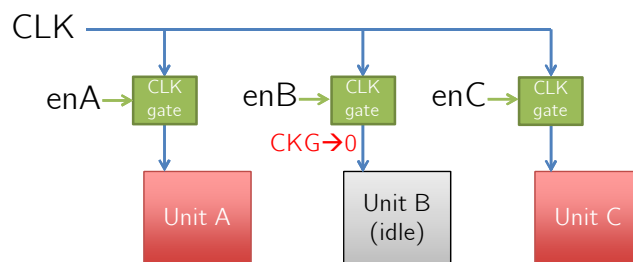

- Clock gates switch off clock signals
 - Be very careful with glitches on clock signal
 - Increases additional delay/skew on CLK signals

1121


Reduce activity: Signal silencing

 

- In practice, only outputs of one unit needed
- Input data is propagating through both units

1122


Signal silencing: method 1

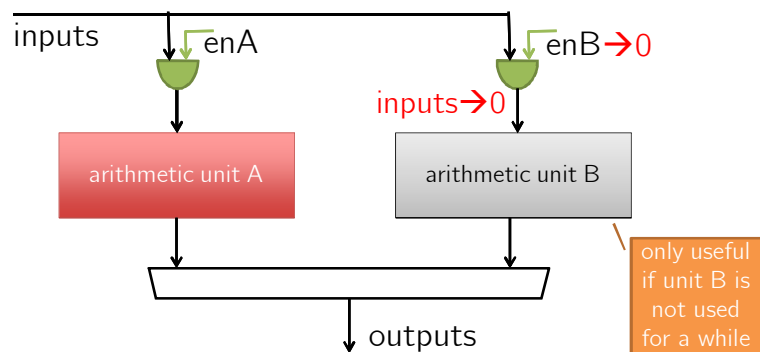

- Similar idea as clock gating, but not a problem as logic is **NOT** on clock path
- Drawback: switching off unit causes activity

1123

Signal silencing: method 2

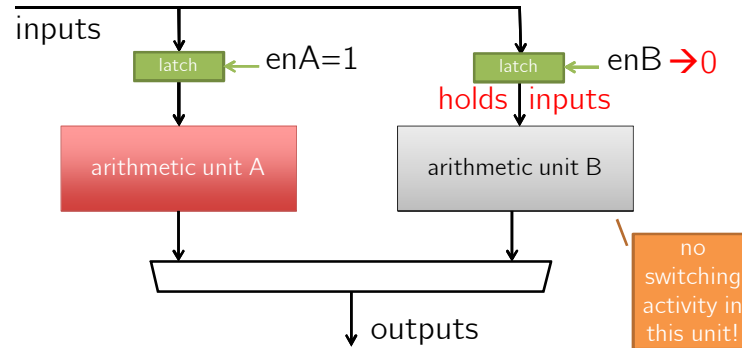


- Switching off unit causes **NO** activity
- Increases critical path and area!

1124

Suppress glitches by pipelining

 - Glitches increase switching activity
- **Glitches depend on logic depth of circuit**
 - More logic gates increases likelihood of uneven arrival times at gate inputs
- Reduce logic depth by pipelining:




- Faster design → **voltage/frequency scaling**

1125

Voltage/frequency scaling

- Decreasing V_{DD} reduces power quadratically but increases gate delays!
- Having a design that is faster than necessary allows one to reduce V_{DD}

→ often substantial power reduction!

 

1126

Dynamic frequency/voltage scaling

- Dynamically adjust clock frequency and supply voltage to processing needs
 - High speed, high V_{DD} if needed → high power
 - Low speed, low V_{DD} → low power
- Used in virtually all modern microprocessors

1127

Reduce direct path currents

- Direct path currents depend on rise and fall times of clock signals in each gate
- Minimize rise and fall times:
 - Reduce clock loads in the design
 - Carefully place buffers in your clock tree




- Good CLK also reduces jitter → faster designs

1128

Reduce leakage currents

 - Reducing V_T exponentially increases sub-threshold leakage currents
- Reducing V_T decreases gate delay
→ faster logic



1129

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic


Reduce leakage currents (cont'd)

- Determine critical path(s) of design
- Leakage reduction:
 - Use low- V_T devices for timing-critical circuits
 - Use high- V_T devices for the rest
- Usually tool-assisted (if cell library contains both types of logic cells)

1130

Adaptive body biasing (ABB)

 
- Vary V_T at run-time by varying V_{SB}
- Negative bias increases V_T of NMOS
- Combine with with dynamic voltage/frequency scaling to lower leakage power



1131

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Suppressing leakage

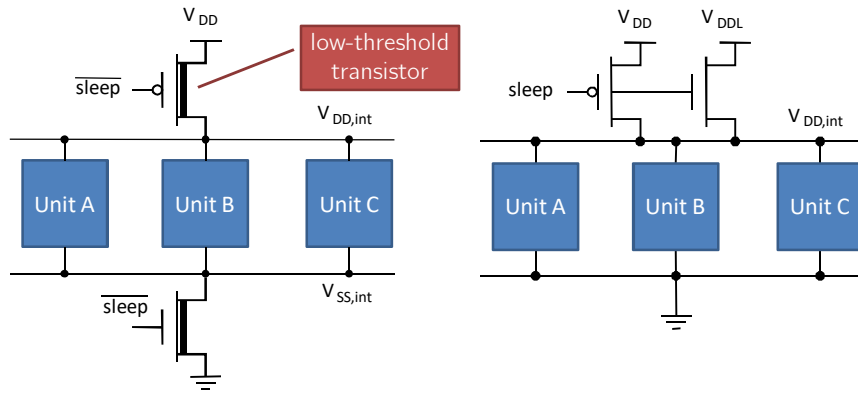


increasing resistance &
reducing supply voltage

reducing supply voltage

1132

Power gating → eliminates leakage

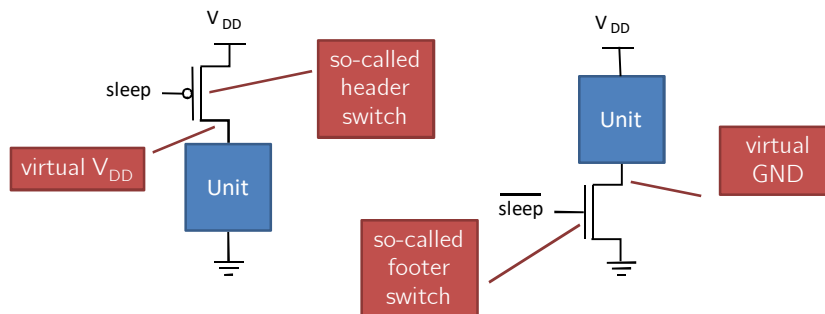
- Completely switch off idle units
- Drawback: Overhead in storing state and resetting functionality → **takes time**



1133

What to do in practice?

- Combine all low-power techniques!

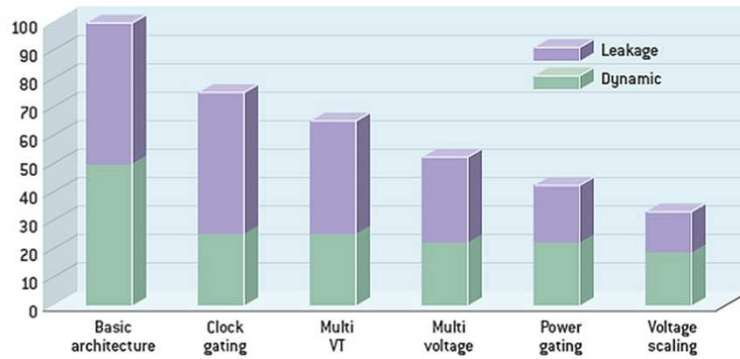

From <http://www.newelectronics.co.uk/electronics-technology/power-optimisation-for-low-power-socs-targeting-mobile-devices/34896/>

1134