

# **ECE/ENGRD 2100**

Introduction to Circuits for ECE

## Lecture 12

Large and Small Signal Analysis of Transistor Circuits


# Announcements

---

- Upcoming due dates:
  - Lab report 2 due by 11:59 pm on Wednesday 27, 2019
- Prelim 1 on Thursday February 21, 2019 from 7:30 – 9 pm in 203 Phillips
  - Email [afridi@cornell.edu](mailto:afridi@cornell.edu) if have conflict
  - Make up exams on same day (Thursday February 21):
    - 10 – 11:30 am in 307 Phillips
    - 2:30 – 4 pm in 228 Phillips
  - Will cover material through Lecture 11
  - Prelim is closed-book and closed-notes
  - One double-sided page formula sheet is allowed
  - Bring a calculator

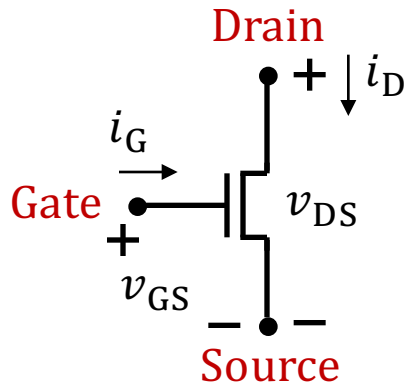
# MOSFET $i$ - $v$ Characteristics

Metal-Oxide-Semiconductor Field-Effect Transistor (MOSFET) – n-channel




$i_G = 0$

*Triode*

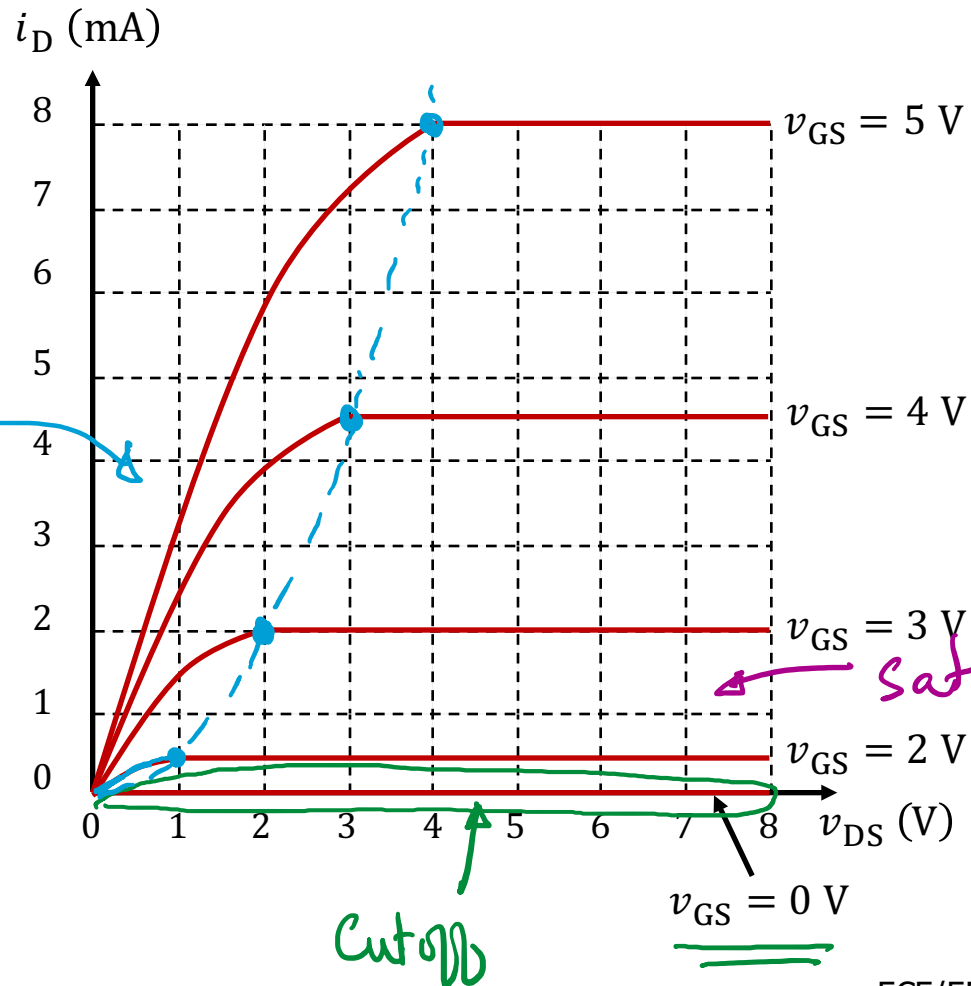

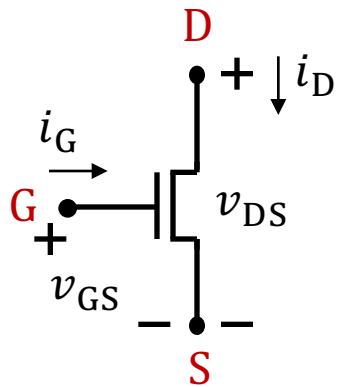
# MOSFET $i$ - $v$ Characteristics (Cont.)



$$i_G = 0$$
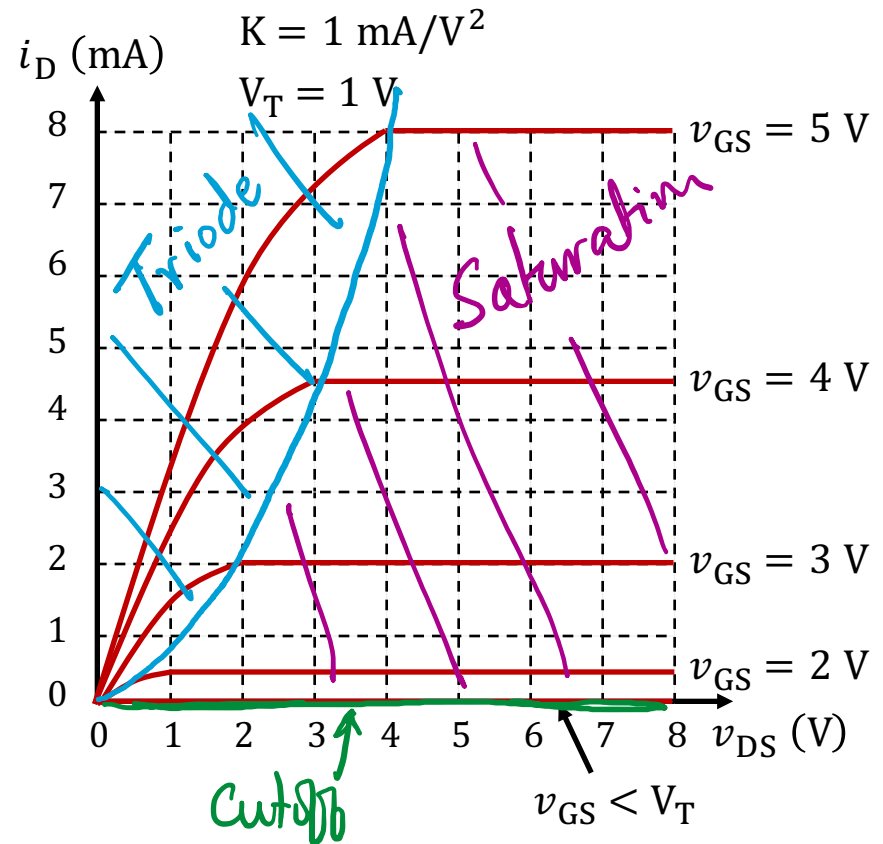
$$i_D = \begin{cases} 0 & \text{if } v_{GS} < V_T \\ K \left[ (v_{GS} - V_T)v_{DS} - \frac{v_{DS}^2}{2} \right] & \text{if } v_{GS} \geq V_T \text{ and } v_{DS} < v_{GS} - V_T \\ \frac{K}{2} (v_{GS} - V_T)^2 & \text{if } v_{GS} \geq V_T \text{ and } v_{DS} \geq v_{GS} - V_T \end{cases}$$






if  $v_{GS} < V_T$  **Cutoff**

if  $v_{GS} \geq V_T$  and  $v_{DS} < v_{GS} - V_T$  **Triode**




if  $v_{GS} \geq V_T$  and  $v_{DS} \geq v_{GS} - V_T$  **Saturation**
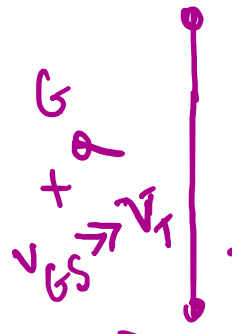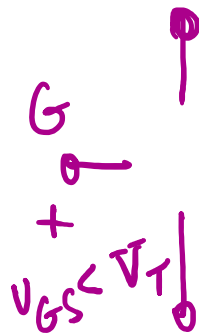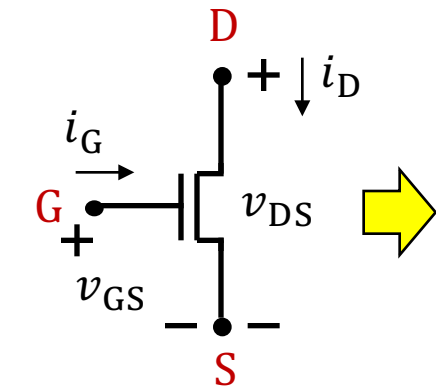
# MOSFET as a Switch

- MOSFET can be used as a switch (e.g., for digital logic) by going between cutoff and triode regions



Cutoff  $\leftrightarrow$  Triode

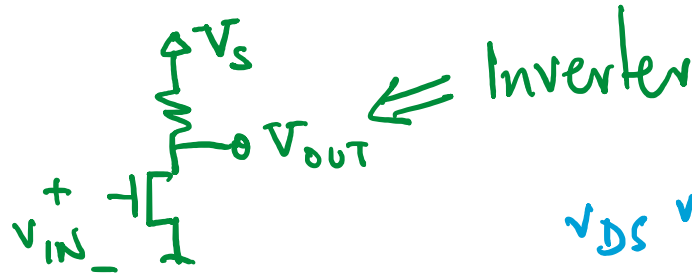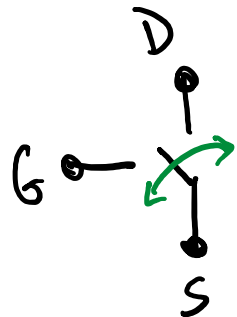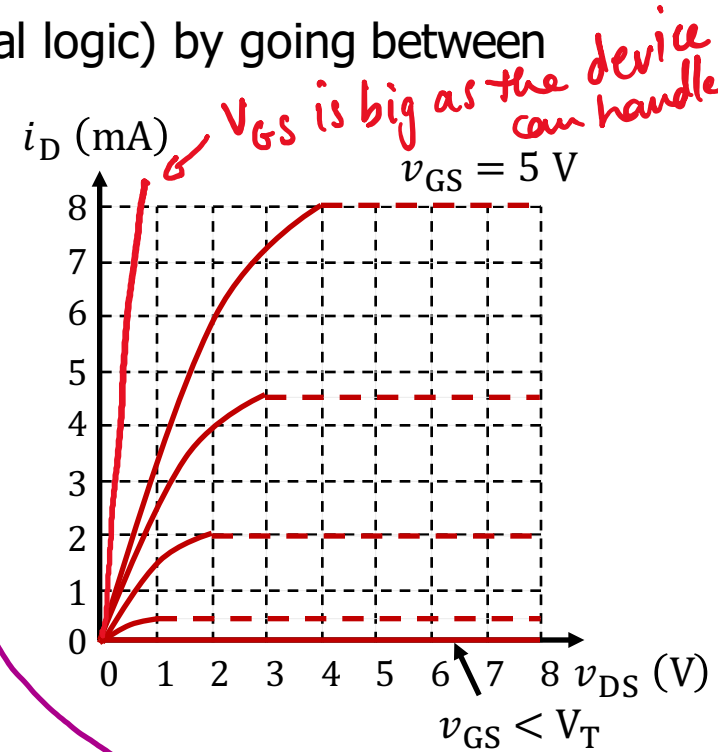

$\Leftarrow$  Inverter

$$i_D = \begin{cases} 0 \\ K \left[ (v_{GS} - V_T)v_{DS} - \frac{v_{DS}^2}{2} \right] \end{cases}$$

Cutoff

Triode




$v_{DS}$  very small

$$\approx K(v_{GS} - V_T)v_{DS}$$

$$R = \frac{1}{K(v_{GS} - V_T)}$$
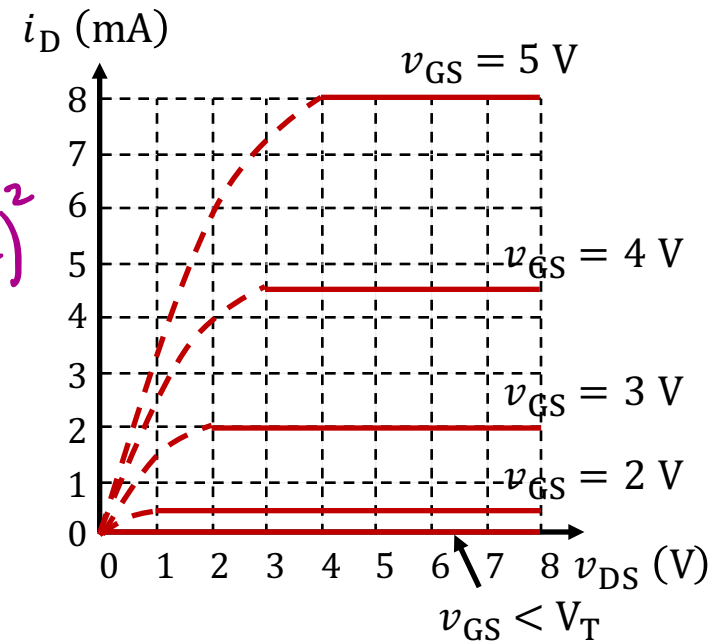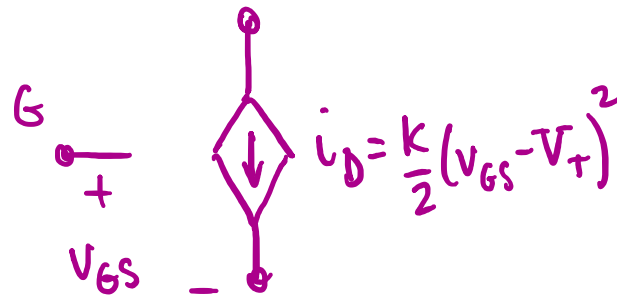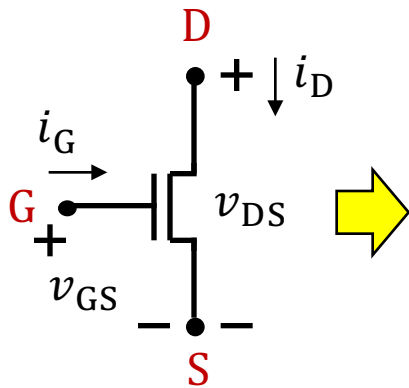
# MOSFET as a Controlled Current Source


- MOSFET can be used as a Voltage Controlled Current Source by operating it in its saturation region



$$i_D = \frac{K}{2}(v_{GS} - V_T)^2 \quad \text{Saturation}$$
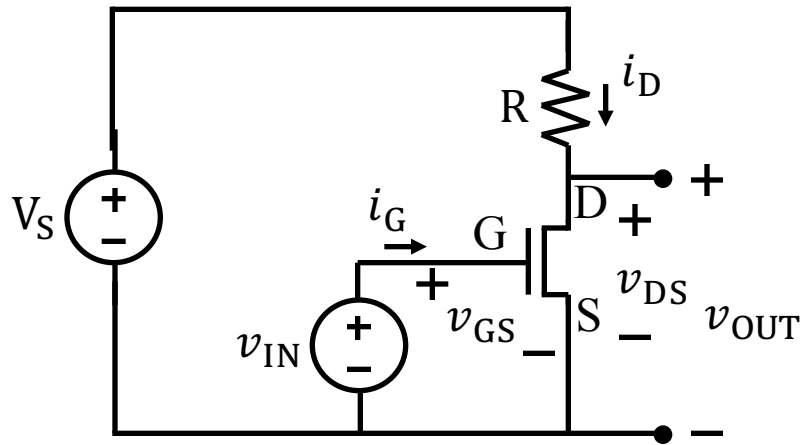
# MOSFET Circuit – Large-Signal Analysis

Given: MOSFET operating in Saturation  $v_{GS} \geq V_T$  and  $v_{DS} \geq v_{GS} - V_T$




$$V_S = 8 \text{ V}$$

$$R = 1 \text{ k}\Omega$$

$$K = 1 \text{ mA/V}^2$$


$$V_T = 1 \text{ V}$$

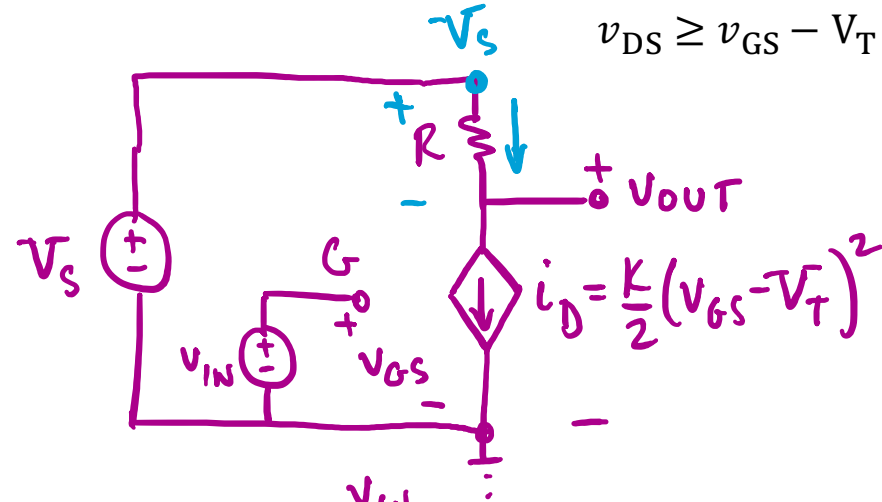

$$v_{OUT} = V_S - R i_D = V_S - \frac{RK}{2} (v_{GS} - V_T)^2$$

$$v_{OUT} = 8 - \frac{1}{2} (v_{IN} - 1)^2$$
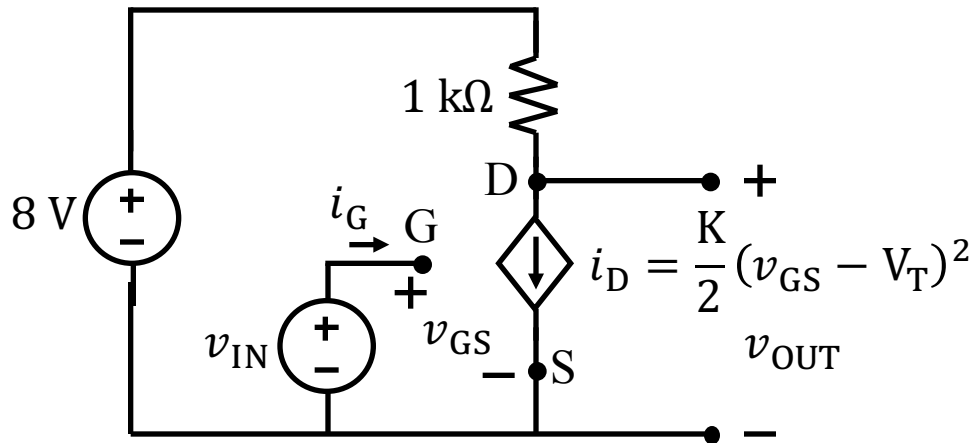
# MOSFET Circuit – Large-Signal Analysis (Cont.)



$$v_{OUT} = 8 - \frac{1}{2}(v_{IN} - 1)^2$$

MOSFET in Saturation

$$K = 1\text{ mA/V}^2$$


$$V_T = 1\text{ V}$$

MOSFET is in Saturation when:

$$v_{GS} \geq V_T \Rightarrow v_{IN} \geq 1$$


$$v_{DS} \geq v_{GS} - V_T \Rightarrow v_{OUT} \geq v_{IN} - 1$$
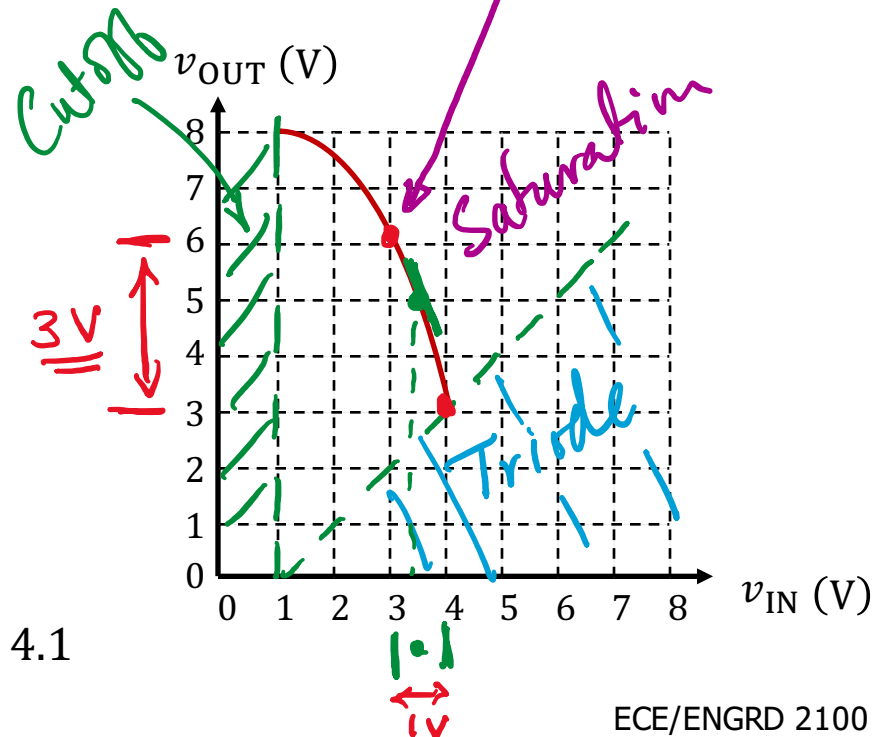
$$\Rightarrow 8 - \frac{1}{2}(v_{IN} - 1)^2 \geq v_{IN} - 1 \Rightarrow v_{IN} \leq 4.1$$





# MOSFET Circuit – Small-Signal Analysis

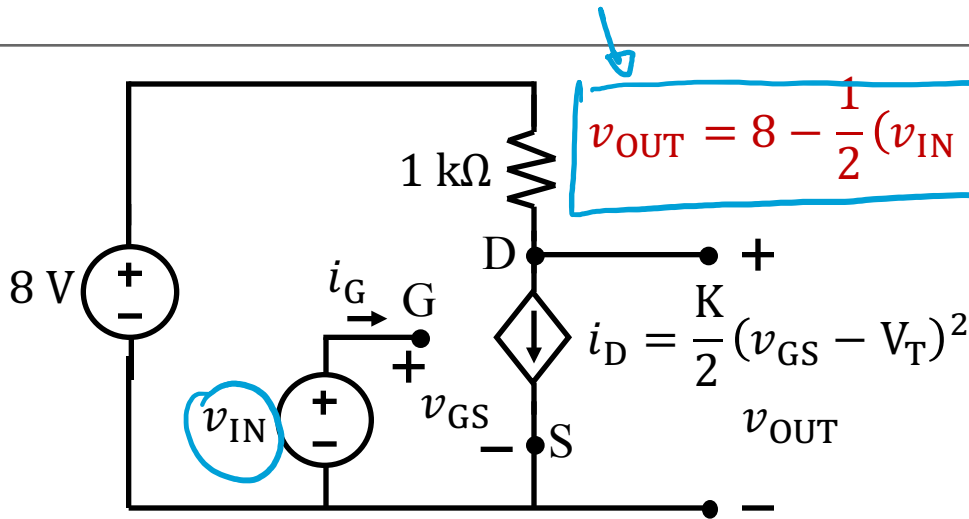

$$v_{OUT} = 8 - \frac{1}{2} (v_{IN} - 1)^2$$

small signal

$$v_{IN} = V_{IN} + v_{in}(t)$$

$$v_{OUT} = V_{OUT} + v_{out}(t)$$

$$v_{OUT} = f(v_{IN})$$

$$V_{OUT} + v_{out} = f(V_{IN} + v_{in})$$

ignore


$$V_{OUT} + v_{out} = f(V_{IN}) + \left. \frac{\partial f}{\partial v_{IN}} \right|_{v_{IN}=V_{IN}} \cdot v_{in} + \dots$$

$$V_{OUT} = f(V_{IN})$$


$$v_{out} = \left. \frac{\partial f}{\partial v_{IN}} \right|_{v_{IN}=V_{IN}} \cdot v_{in}$$

higher order terms
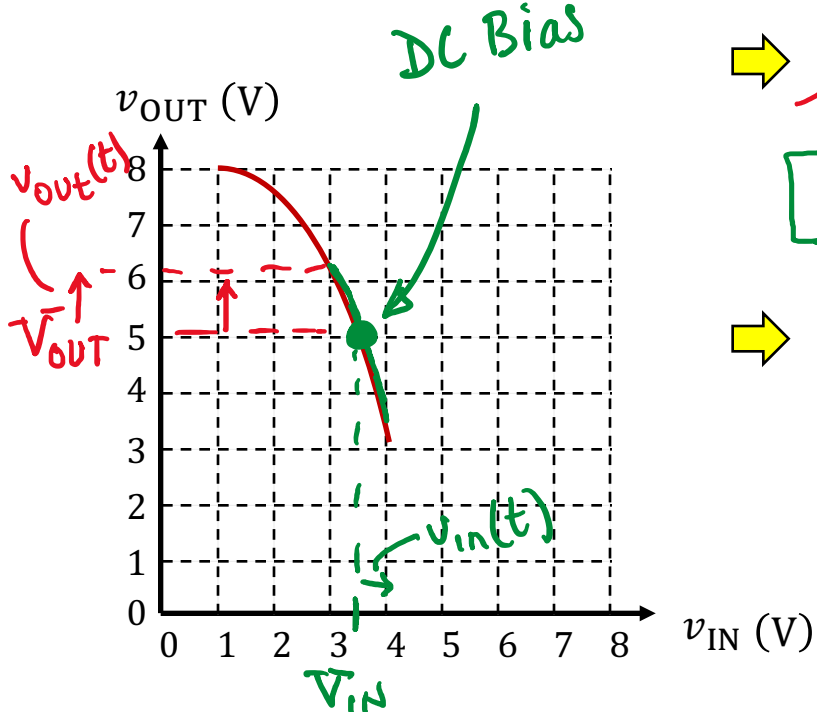
$$v_{out}(t) = -(V_{IN} - 1) \cdot v_{in}(t)$$




# Small-Signal Circuit Method

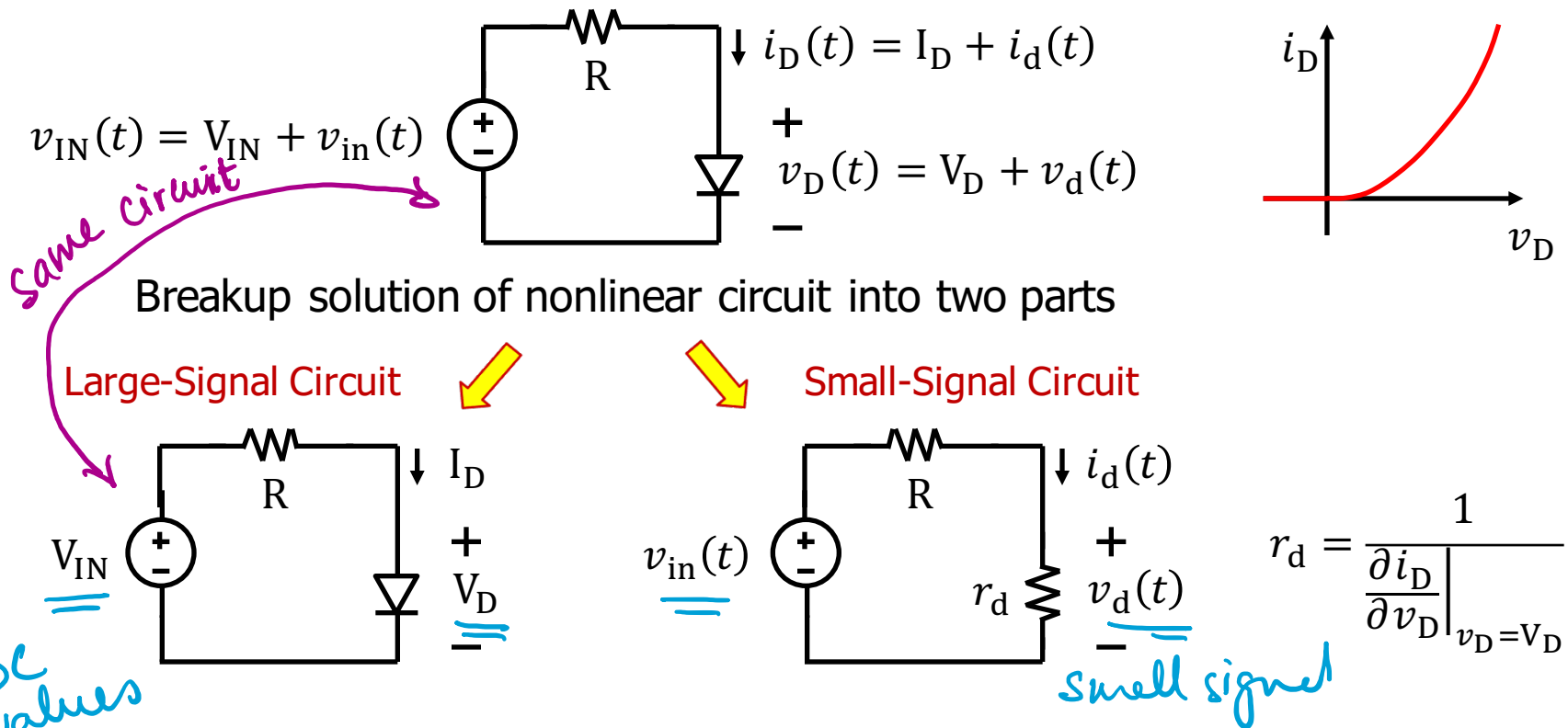

- 1) Find DC Bias Point using Large-Signal Circuit – i.e., using non-linear large-signal constitutive relations for the non-linear elements
- 2) Create Small-Signal Circuit by replacing non-linear elements by their linearized (small-signal) models, with values appropriate for DC Bias Point
- 3) Solve the resulting Small-Signal Circuit – which is linear

# Small-Signal Model of MOSFET in Saturation

Large-Signal Model

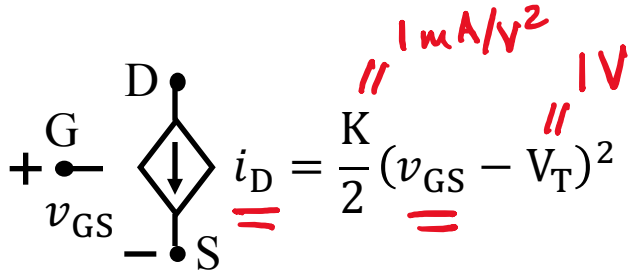

Small-Signal Model

*small signal response*

$$i_d = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GS}} \cdot v_{gs}$$

*small signal input*

*Slope at  $v_{GS}=V_{GS}$*

$$\left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GS}} = \frac{\partial}{\partial v_{GS}} \left( \frac{K}{2} (v_{GS} - V_T)^2 \right) \Big|_{v_{GS}=V_{GS}}$$


$$\left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GS}} = K (V_{GS} - V_T)$$

# Small-Signal Models for Various Circuit Elements

## Large-Signal Model

## Small-Signal Model

### Linear Elements


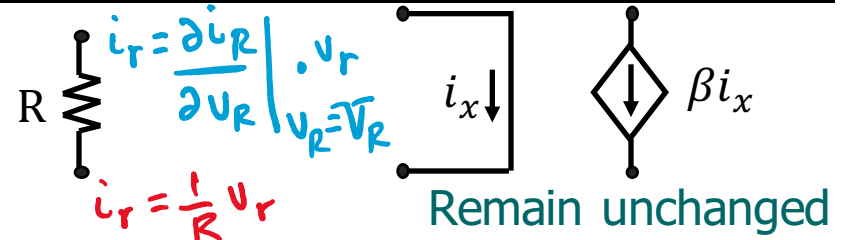


### Constant Voltage/Current Sources




Set to zero

### MOSFET in Saturation

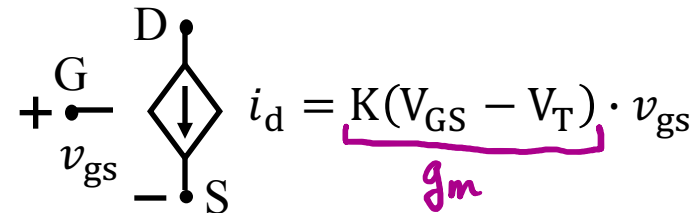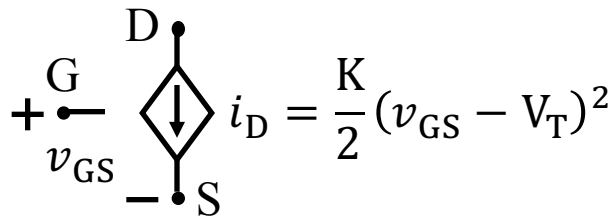


Linear Dependent Source

### Small Signal Sources

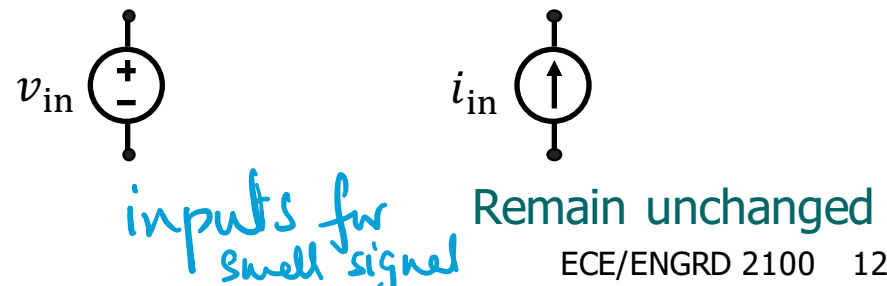

# MOSFET Amplifier – Small-Signal Circuit

Large-Signal Circuit

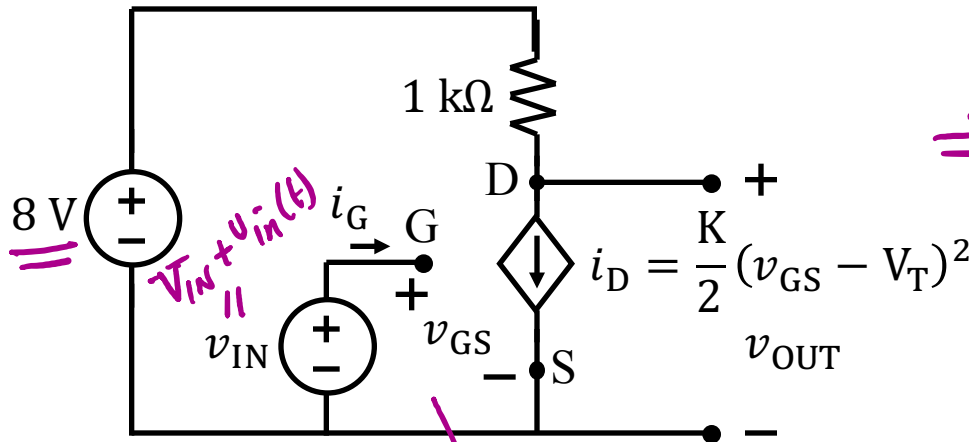


$$K = 1\text{ mA/V}^2$$

$$V_T = 1\text{ V}$$

$$v_{IN} = V_{IN} + v_{in}(t)$$

$$V_{GS} = V_{IN}$$

Small Signal Circuit

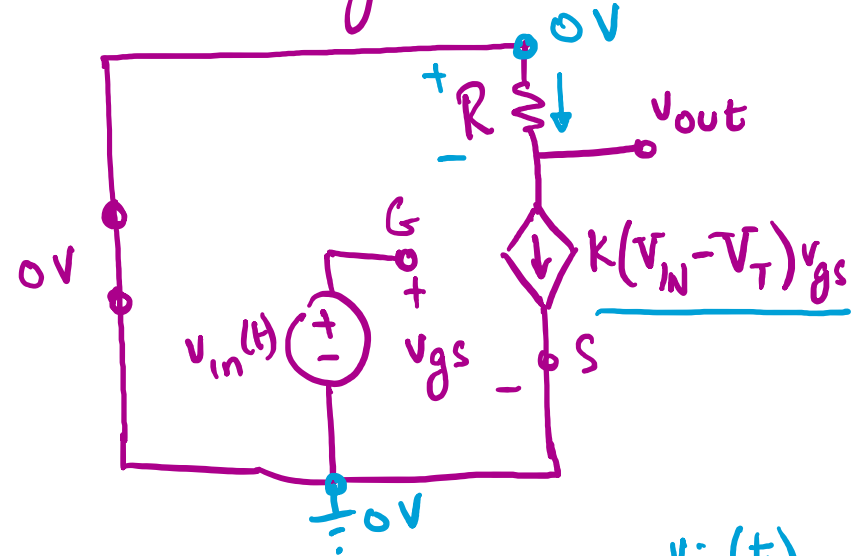


$$v_{out}(t) = 0 - RK(V_{IN} - V_T)v_{gs}'' v_{in}(t)$$

$$v_{out}(t) = -RK(V_{IN} - V_T)v_{in}(t)$$

$$v_{out}(t) = -(V_{IN} - 1)v_{in}(t)$$

# MOSFET Amplifier – Graphical Analysis

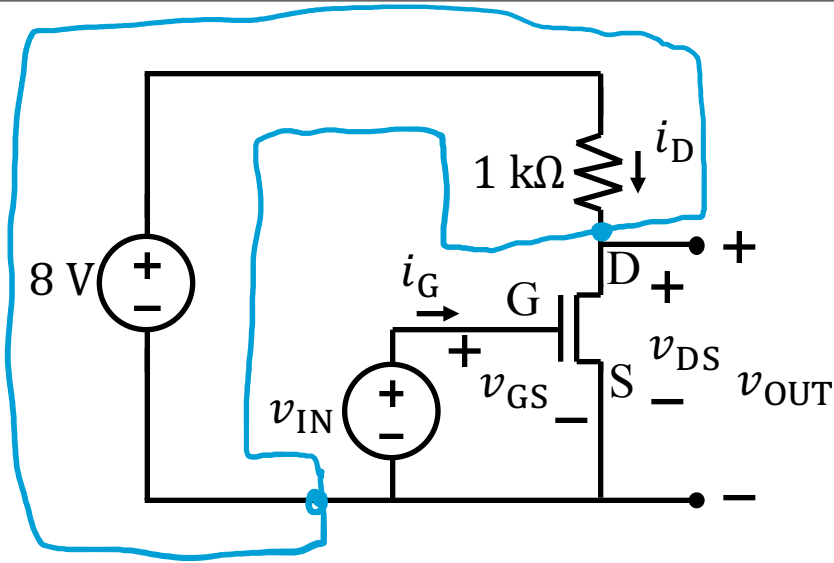

$$v_{OUT} = 8V - (1k)\ i_D$$

