

ECE/ENGRD 2100

Introduction to Circuits for ECE


Lecture 14

Implementing Linear and Non-Linear Functions
Using Op-Amps



Announcements

- Recommended Reading:
 - Textbook Chapter 5
- Upcoming due dates:
 - Lab report 2 due by 11:59 pm on Wednesday 27, 2019

Ideal Op-Amp

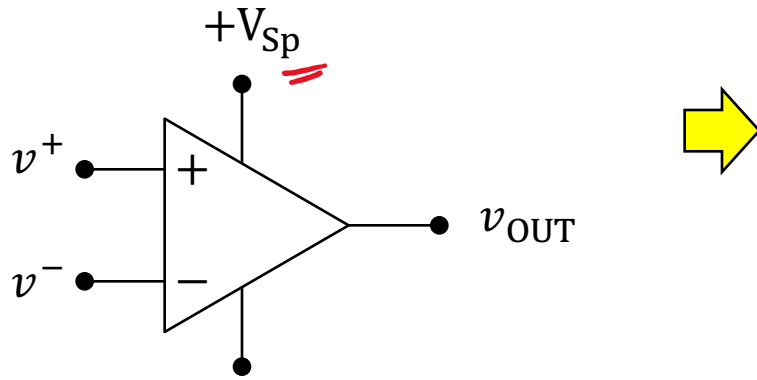

Non-ideal Op Amp

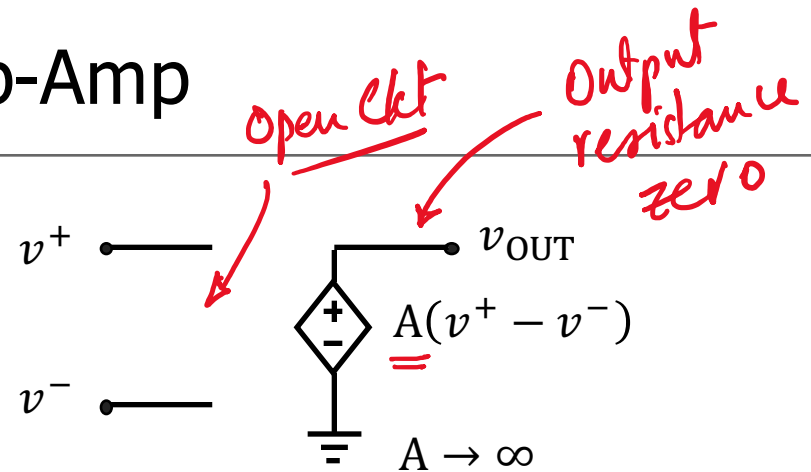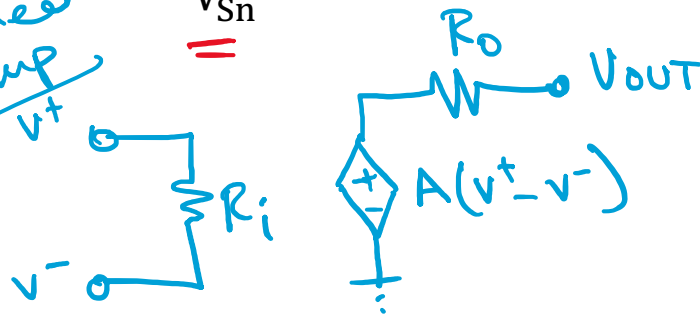


Ideal Op-Amp

- Infinite Gain, i.e., $A \rightarrow \infty$
- Infinite Input Resistance
- Zero Output Resistance
- Output v_{OUT} can take any value

Ideal Op-Amp Under Negative Feedback


- Virtual Short: $v^- \approx v^+$
- Infinite Input Resistance: $i^- = 0$ and $i^+ = 0$

Negative Feedback

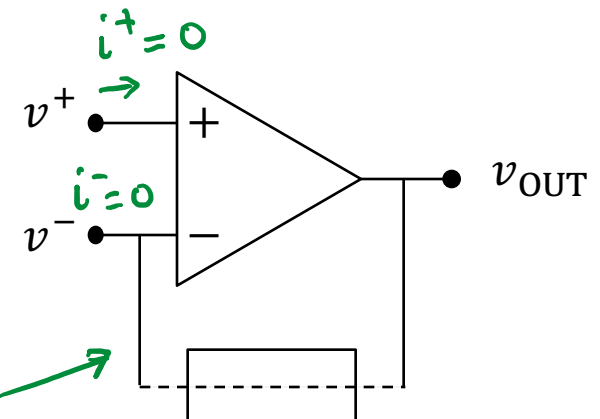


Op-Amp Amplifiers

Non-Inverting Amplifier

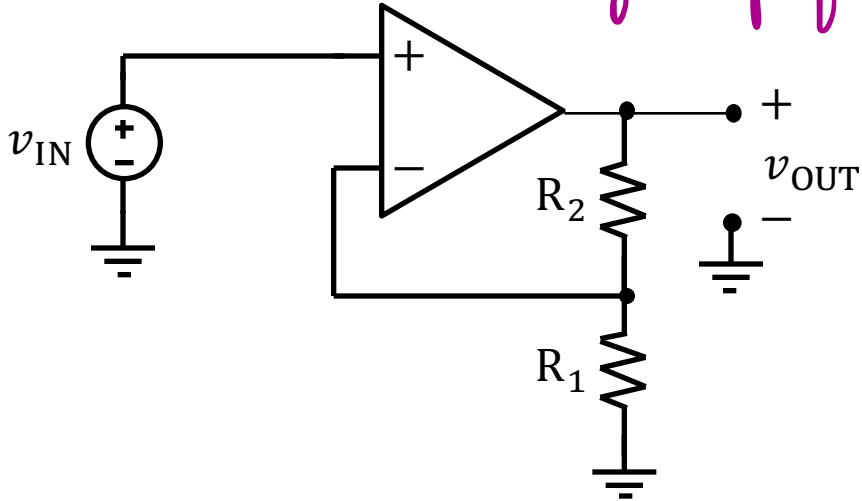


$$v_{OUT} = \left(1 + \frac{R_2}{R_1}\right) v_{IN}$$

Inverting Amplifier

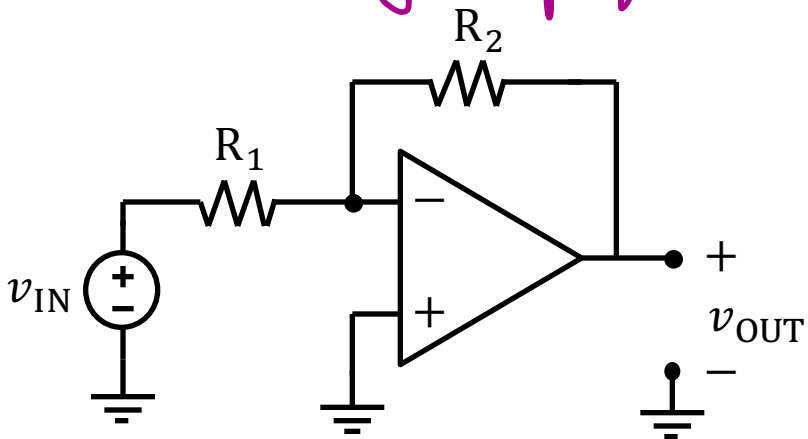

$$v_{OUT} = -\frac{R_2}{R_1} v_{IN}$$

Another Linear Operation with Op-Amp

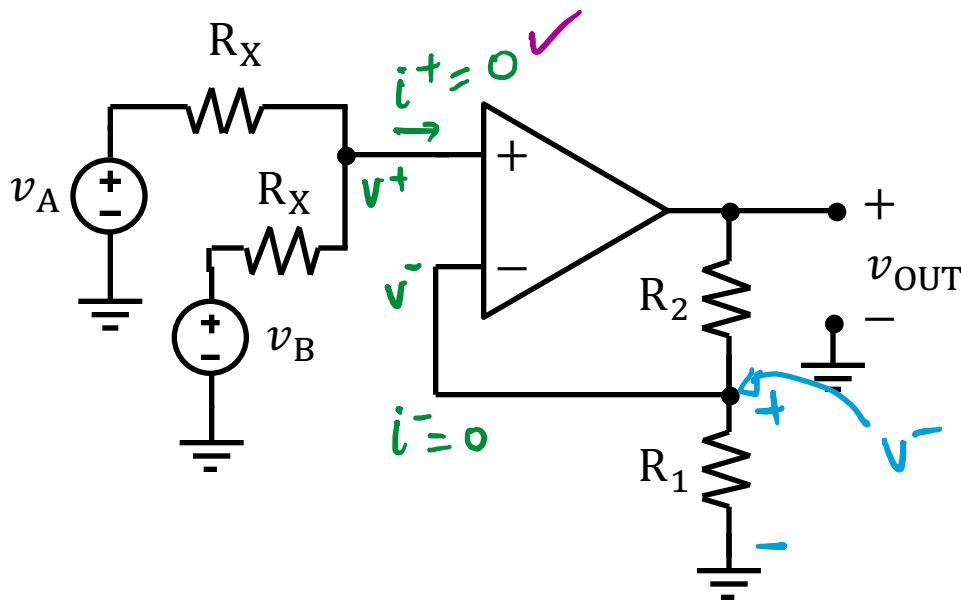

$$v^+ = \frac{R_X}{R_X + R_X} v_A + \frac{R_X}{R_X + R_X} v_B = \frac{v_A}{2} + \frac{v_B}{2}$$

$$v^- = \frac{R_1}{R_1 + R_2} v_{OUT}$$

$$v^+ \approx v^-$$


$$\frac{v_A + v_B}{2} = \frac{R_1}{R_1 + R_2} v_{OUT}$$

$$\Rightarrow v_{OUT} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{v_A + v_B}{2}\right)$$

if Pick $R_1 = R_2 \Rightarrow$ $v_{OUT} = v_A + v_B$ ← Adder

Averaging Ckt

Yet Another Linear Operation with Op-Amp

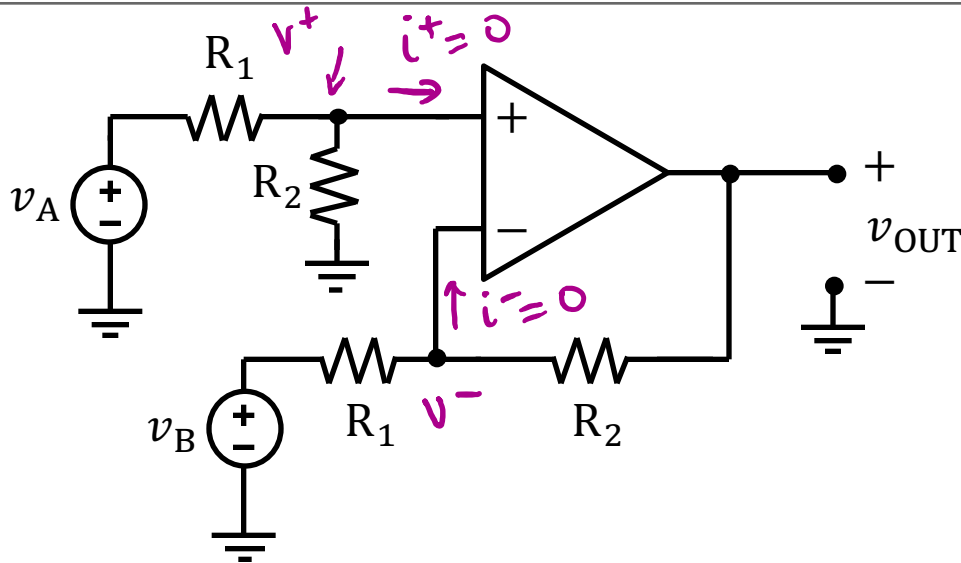

$$v^+ = \frac{R_2}{R_1 + R_2} v_A$$

$$v^- = \frac{R_1}{R_1 + R_2} v_{OUT} + \frac{R_2}{R_1 + R_2} v_B$$

$$v^+ \approx v^- \Rightarrow \frac{R_1}{R_1 + R_2} v_{OUT} + \frac{R_2}{R_1 + R_2} v_B = \frac{R_2}{R_1 + R_2} v_A$$



$$\Rightarrow v_{OUT} = \frac{R_2}{R_1} (v_A - v_B)$$

← Difference Amplifier

If Pick $R_1 = R_2 \Rightarrow v_{OUT} = v_A - v_B$


← Subtraction Ckt

Implementing Non-Linear Functions

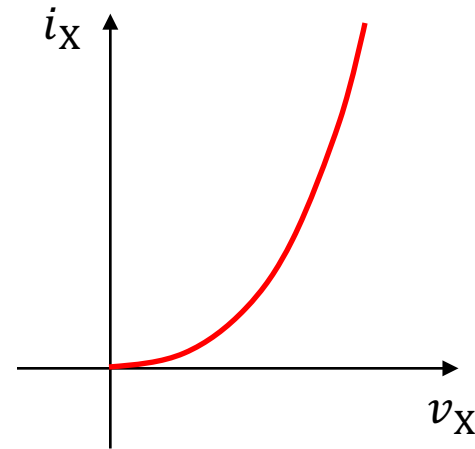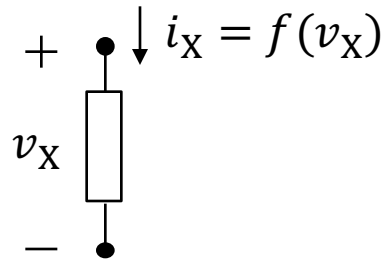

Want to implement: $v_{\text{OUT}} = f(v_{\text{IN}})$

Recall: Inverting Amplifier

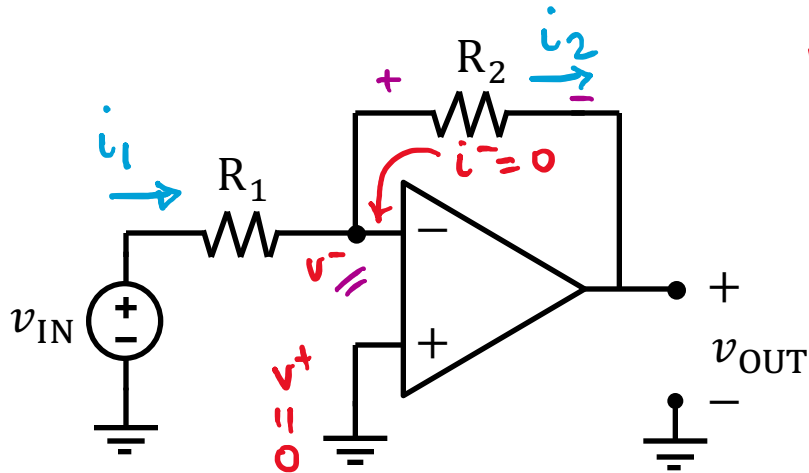

$$v^- \approx v^+ = 0$$

$$v_{OUT} = 0 - R_2 i_2 = -R_2 i_1$$



$$v_{OUT} = -R_2 i_X$$

$$\Rightarrow v_{OUT} = -R_2 \frac{v_{IN}}{R_1}$$

$$i_1 = \frac{v_{IN}}{R_1}$$

$$i_2 \approx i_1$$

Op-Amp with a Non-Linear Device

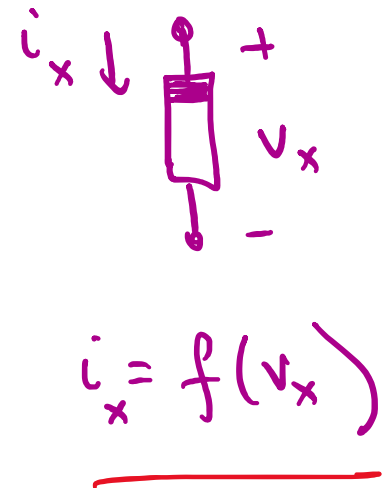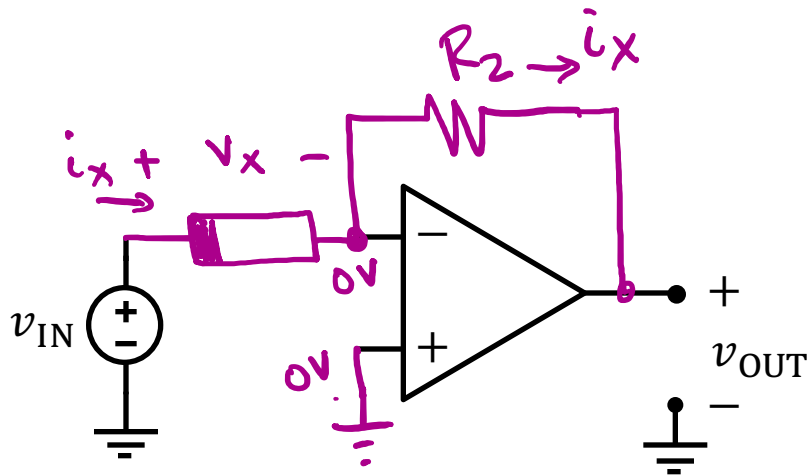

$$i_x = f(v_x)$$



$$\Rightarrow i_x = f(v_{IN})$$

$$v_{OUT} = -R_2 i_x = -R_2 f(v_{IN})$$

$$\text{Pick } R_2 = 1 \Rightarrow v_{OUT} = -f(v_{IN})$$

Cascade an inverting Amp with gain of "-1" to get $v_{OUT} = f(v_{IN})$

Op-Amp with a Non-Linear Device Example

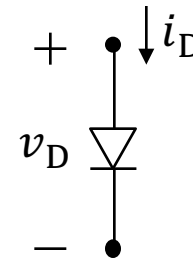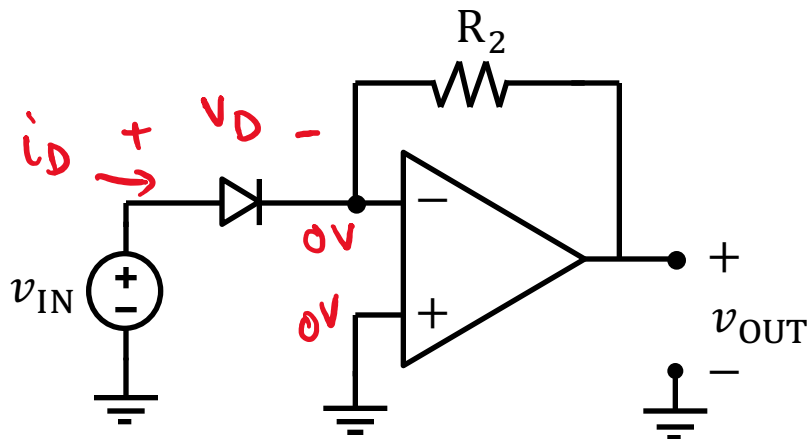

$$i_D = I_S (e^{v_D/V_{TH}} - 1)$$

$$V_{TH} = \frac{kT}{q}$$



$$v_{OUT} = -R_2 i_D = -R_2 I_S (e^{v_D/V_{TH}} - 1) = -R_2 I_S (e^{v_{IN}/V_{TH}} - 1)$$

Pick $R_2 I_S = 1$

$$v_{OUT} = - (e^{v_{IN}/V_{TH}} - 1)$$

$$v_{IN}' \rightarrow \boxed{V_{TH}} \rightarrow v_{IN}' V_{TH}$$

Non-Linear Device in Feedback Loop

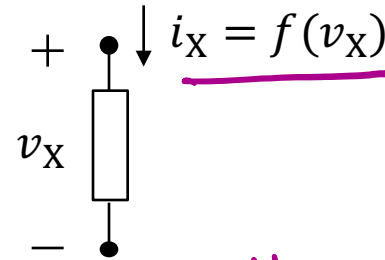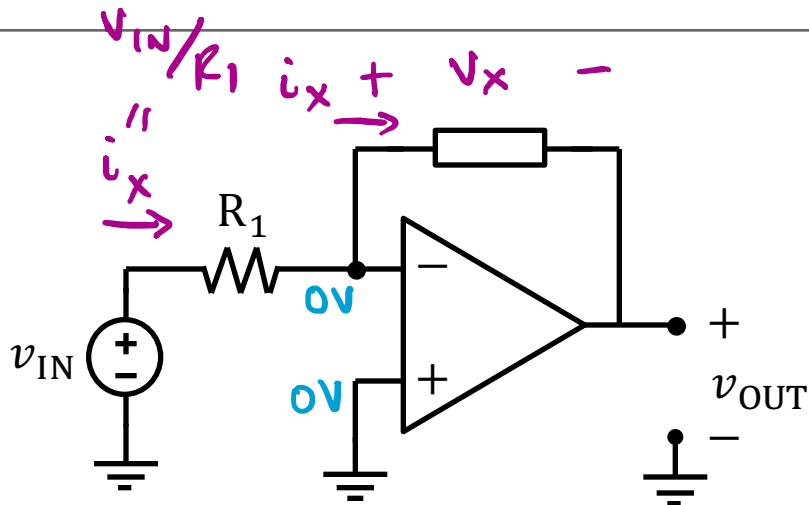


$$v_x = f^{-1}(i_x)$$

$$v_{OUT} = 0 - v_x = -v_x$$

$$v_{OUT} = -f^{-1}(i_x) = -f^{-1}\left(\frac{v_{IN}}{R_1}\right)$$

Logarithmic Amplifier

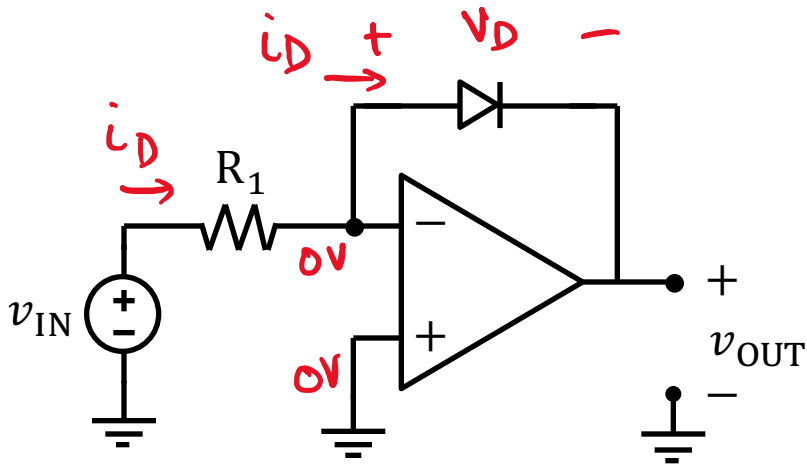

$$i_D = I_S (e^{v_D/V_{TH}} - 1)$$

$$\Downarrow$$
$$\frac{i_D}{I_S} + 1 = e^{v_D/V_{TH}}$$

$$v_D = V_{TH} \ln\left(\frac{i_D}{I_S} + 1\right)$$


$$v_{OUT} = -v_D = -V_{TH} \ln\left(\frac{i_D}{I_S} + 1\right)$$

$$i_D = \frac{v_{IN}}{R_1} \Rightarrow$$

$$v_{OUT} = -V_{TH} \ln\left(\frac{v_{IN}}{R_1 I_S} + 1\right)$$


Pick $R_1 I_S = 1$

Square Root Using an Op-Amp

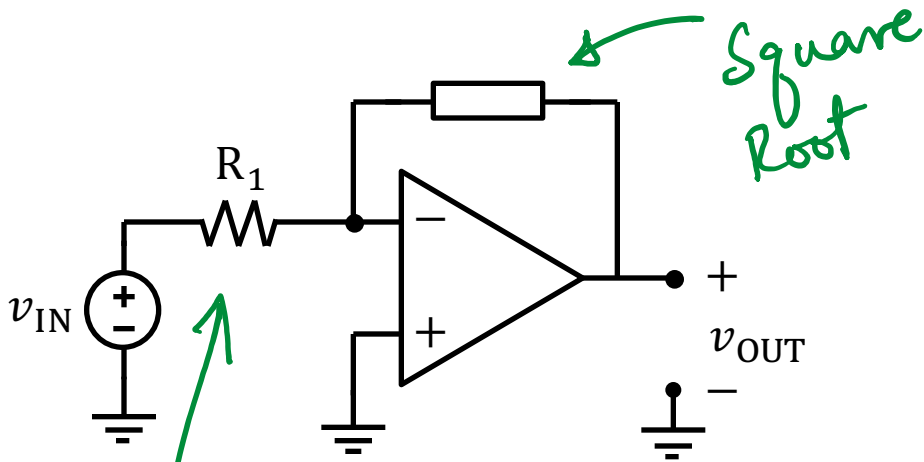

For Square
Put this device
here

$$i_D = \frac{K}{2} (v_{DS} - V_T)^2$$

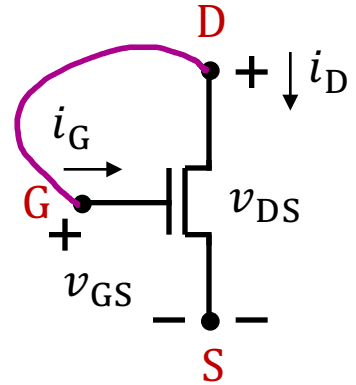

$$i_D = \frac{K}{2} (v_{GS} - V_T)^2$$

Saturation

$$v_{GS} \geq V_T$$

$$v_{DS} \geq v_{GS} - V_T$$

$$v_{GS} \geq v_{GS} - V_T$$

True for $V_T > 0$

$$v_{GS} = v_{DS}$$

$$v_{DS} \geq V_T$$