

ECE/ENGRD 2100

Introduction to Circuits for ECE


Lecture 16

Capacitors and Inductors

Announcements

- Recommended Reading:
 - Textbook Chapter 6
- Upcoming due dates:
 - Prelab 3 due by 12:20 pm on Tuesday March 5, 2019
 - Homework 3 due by 11:59 pm on Friday March 8, 2019
 - Lab report 3 due by 11:59 pm on Friday March 15, 2019
- Lab 3 is next week (starting Tuesday March 5, 2019)

Capacitors

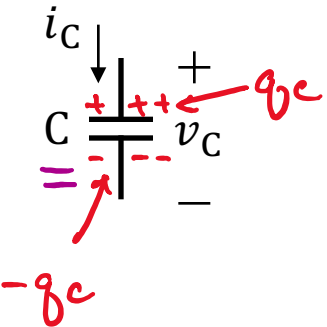

Linear Capacitor

$$i_C = C \frac{dv_C}{dt}$$

i_C is constant



$$q_C = C v_C \Rightarrow \frac{dq_C}{dt} = C \frac{dv_C}{dt}$$

$$C \equiv \frac{dq_C}{dv_C}$$


Capacitance measured in Farads [F]

$$1 \text{ F} \equiv 1 \frac{\text{C}}{\text{V}}$$

Coulomb
↓
Volt

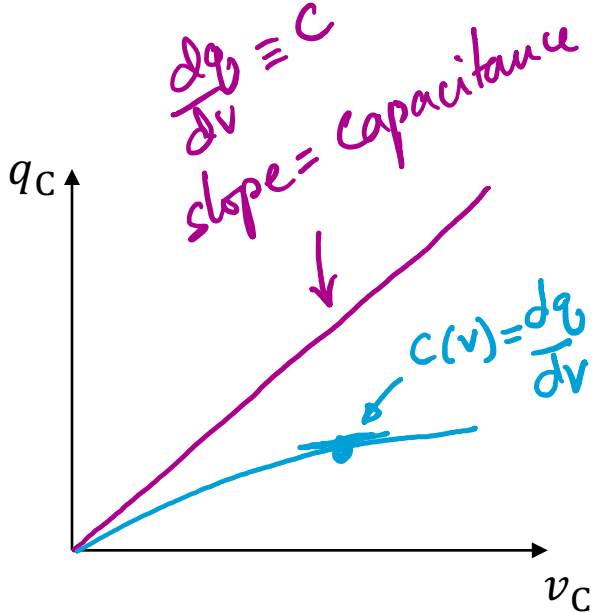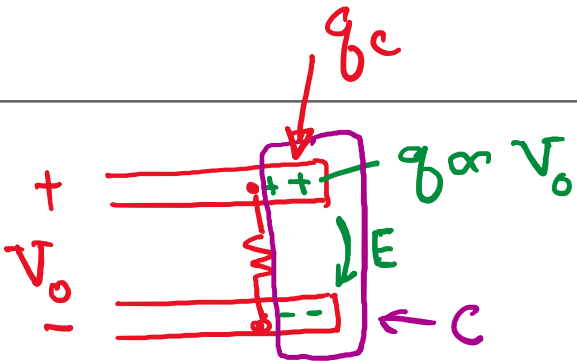

Capacitance of Parallel-Plate Capacitor

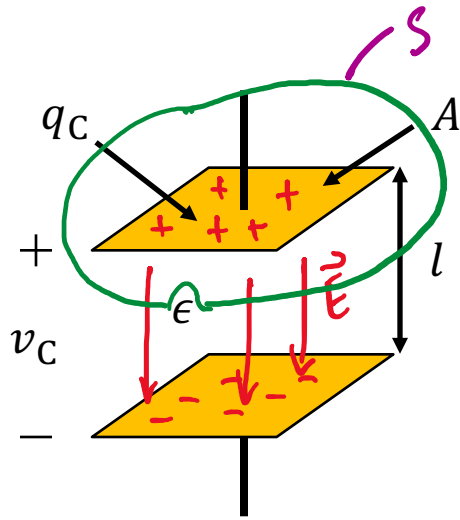

Gauss' Law: $\oiint \vec{D} \cdot d\vec{s} = \iiint \rho dv = q_c$

where: $\vec{D} = \epsilon \vec{E}$

$$\vec{E} = \frac{V_c}{l}$$

$$\oiint_S \epsilon \frac{V_c}{l} d\vec{s} = q_c$$

$$\frac{\epsilon V_c A}{l} = q_c$$


$$C \equiv \frac{dq_c}{dV_c} = \frac{\epsilon A}{l}$$

Energy Stored in a Capacitor

Power \equiv Time Rate of Change of Energy

$$p = \frac{dw}{dt}$$

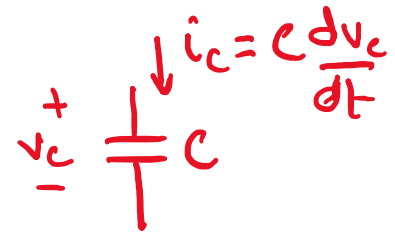
Energy: $w_C(t_1) = \int_{-\infty}^{t_1} p_C dt = \int_{-\infty}^{t_1} v_C i_C dt = \int_{-\infty}^{t_1} v_C C \frac{dv_C}{dt} dt$



$$w_C(t_1) = C \int_0^{V_1} v_C dv_C = \frac{1}{2} C V_C^2$$



$$w_C = \frac{1}{2} C V_C^2$$

Inductors

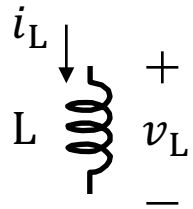

Linear Inductor

$$v_L = L \frac{di_L}{dt}$$

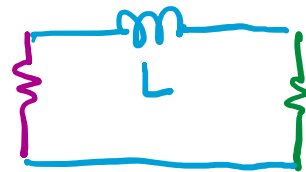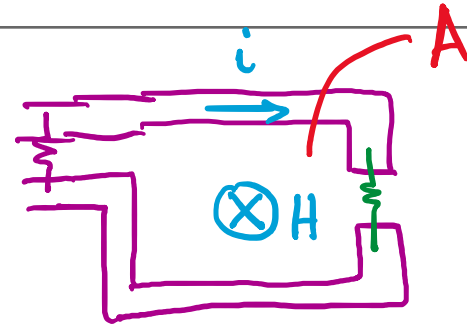

$$\lambda = NA\mu H$$

of turns

Faraday's Law

$$v = \frac{d\lambda}{dt}$$

$$\lambda \propto i \Rightarrow \lambda = Li$$

Flux Linkage


$$L \equiv \frac{d\lambda_L}{di_L}$$

Inductance measured in Henrys [H]



$$1 \text{ H} \equiv 1 \text{ Wb/A}$$

Weber = Volt·sec

Amp

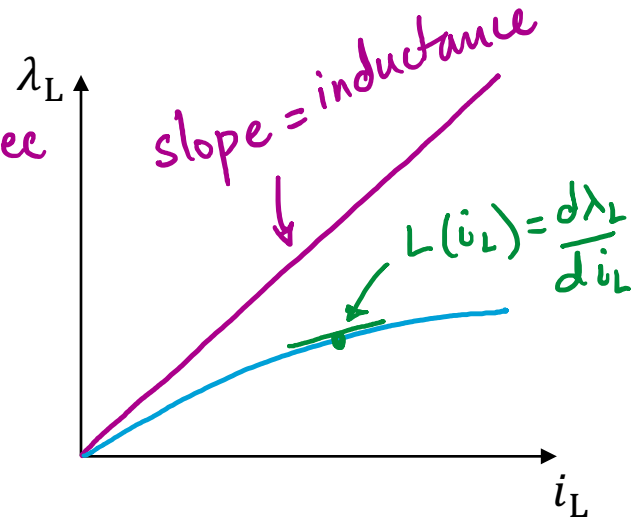

Inductance of Toroidal Inductor

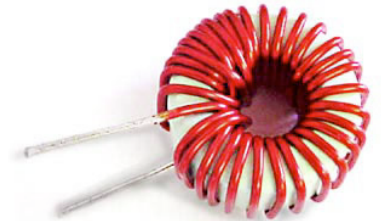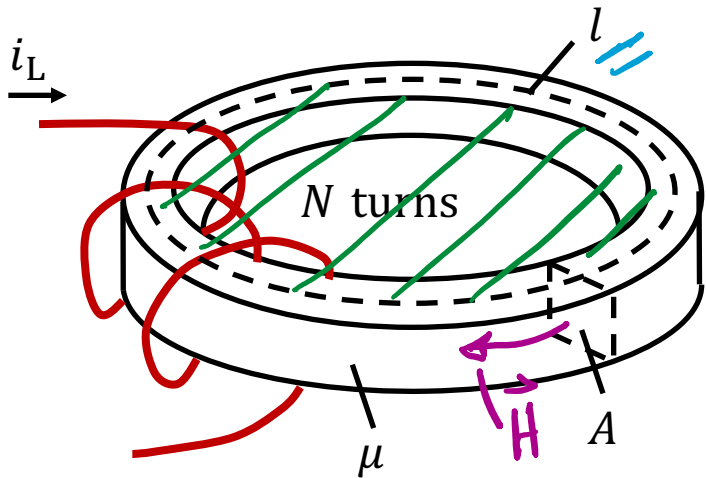

Ampere's Law: $\oint \vec{H} \cdot d\vec{l} = \iint \vec{J} \cdot d\vec{s} + \frac{\partial}{\partial t} \iint \vec{D} \cdot d\vec{s}$

Handwritten annotations: $H \cdot l$ (under the first term), Ni_L (under the second term), and a blue arrow pointing to the third term.

$\Rightarrow H = \frac{Ni_L}{l}$

$$B = \mu H = \frac{\mu N i_L}{l}$$

$$\lambda_L = NBA = \frac{\mu N^2 A i_L}{l}$$

$$L \equiv \frac{d\lambda_L}{di_L} = \frac{\mu A N^2}{l}$$

Compare to: $C = \frac{\epsilon A}{l}$

Energy Stored in an Inductor


Energy: $w_L(t_1) = \int_{-\infty}^{t_1} p_L dt \quad \Rightarrow \quad w_L(t_1) = \int_{-\infty}^{t_1} i_L v_L dt$

$v_L = L \frac{di_L}{dt}$

$$I_1 = i_L(t_1)$$

$$\Rightarrow \boxed{w_L = \frac{1}{2} L I_1^2}$$

Example Capacitor Circuit

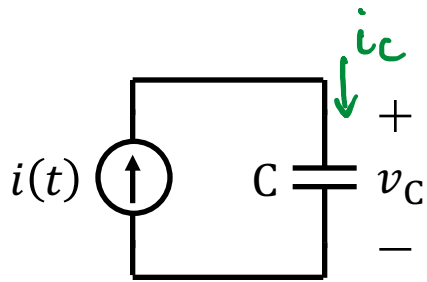



$$i_c = C \frac{dv_C}{dt}$$

$$\frac{dv_C}{dt} = \frac{I_0}{C}$$


$$\frac{dv_C}{dt} = \frac{i_c}{C}$$

$$v_C(t) = \frac{1}{C} \int_{-\infty}^t i_c dt$$

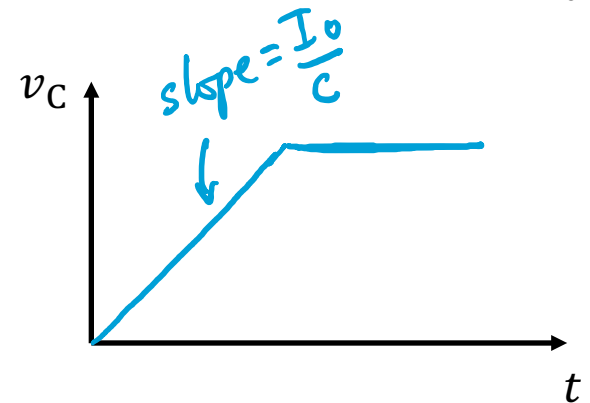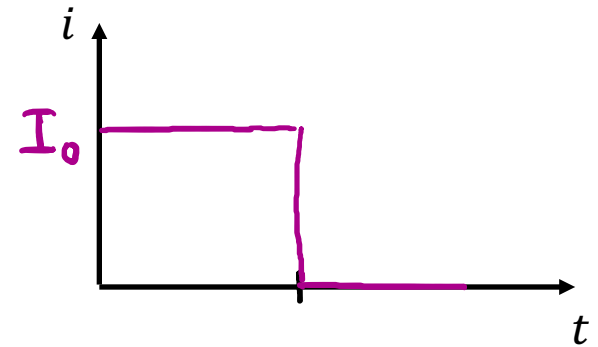
$$v_C(t) = \frac{1}{C} \int_{t_0}^t i_c dt + v_C(t_0)$$





Example Inductor Circuit

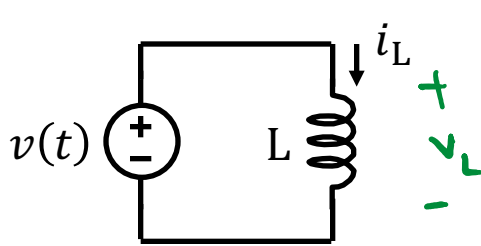

$$v_L = L \frac{di_L}{dt}$$

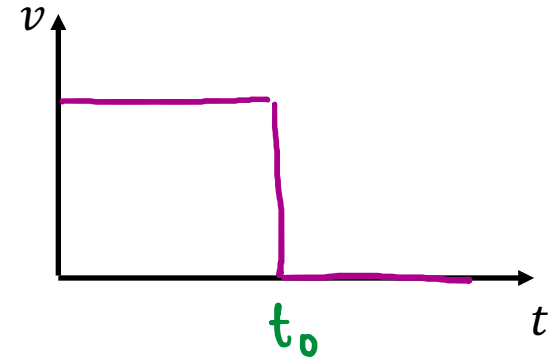

$t > t_0$

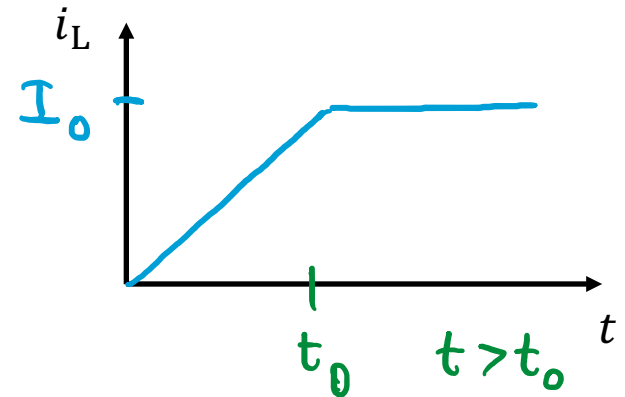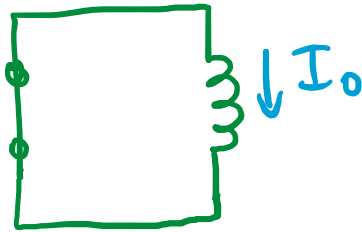


$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L dt$$


$$\Rightarrow i_L(t) = \frac{1}{L} \int_{t_0}^t v_L dt + i_L(t_0)$$

Series and Parallel Combinations of Capacitors

Parallel

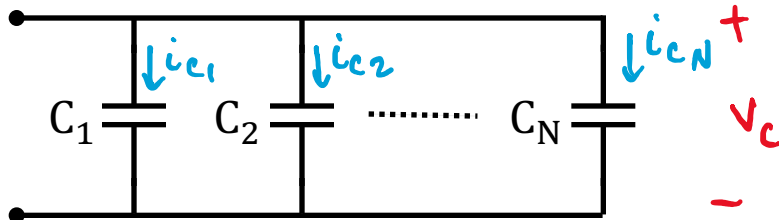
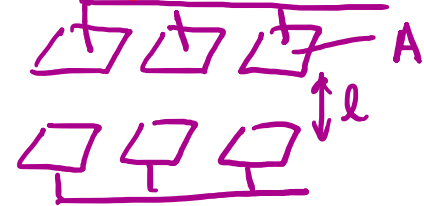
$$i_c = i_{c_1} + i_{c_2} + \dots + i_{c_N} = C_1 \frac{dv_c}{dt} + C_2 \frac{dv_c}{dt} + \dots + C_N \frac{dv_c}{dt}$$




$$C = \frac{\epsilon A}{l}$$

$$C_{eq} = C_1 + C_2 + \dots + C_N$$

$$i_c = \underbrace{(C_1 + C_2 + \dots + C_N)}_{C_{eq}} \frac{dv_c}{dt}$$

Series

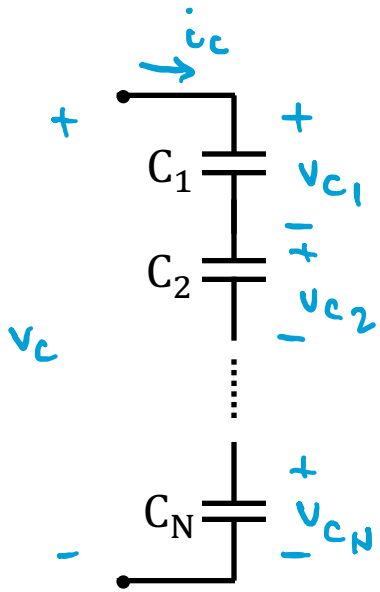

$$v_c = v_{c_1} + v_{c_2} + \dots + v_{c_N}$$


$$v_c = \frac{1}{C_1} \int_{-\infty}^t i_c dt + \frac{1}{C_2} \int_{-\infty}^t i_c dt + \dots + \frac{1}{C_N} \int_{-\infty}^t i_c dt$$

$$v_c = \underbrace{\left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right)}_{\frac{1}{C_{eq}}} \int_{-\infty}^t i_c dt$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$


Series and Parallel Combinations of Inductors

Parallel

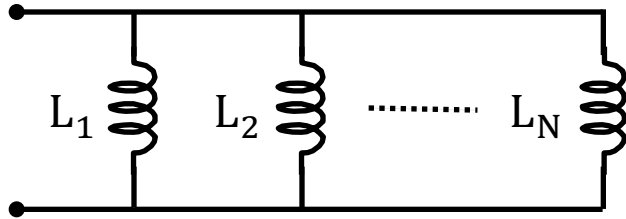

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

Series

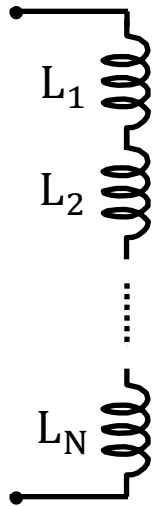


$$L_{eq} = L_1 + L_2 + \dots + L_N$$

Continuity Condition – State Property

Capacitor

$$i_C = C \frac{dv_C}{dt}$$

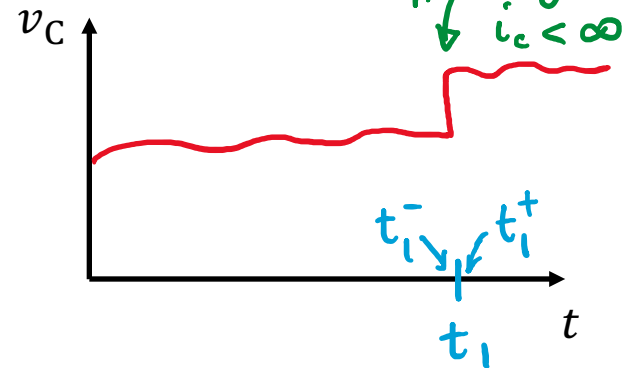
$$v_C(t_1^+) = v_C(t_1^-) \quad \text{if } i_C < \infty$$



Inductor

$$v_L = L \frac{di_L}{dt}$$
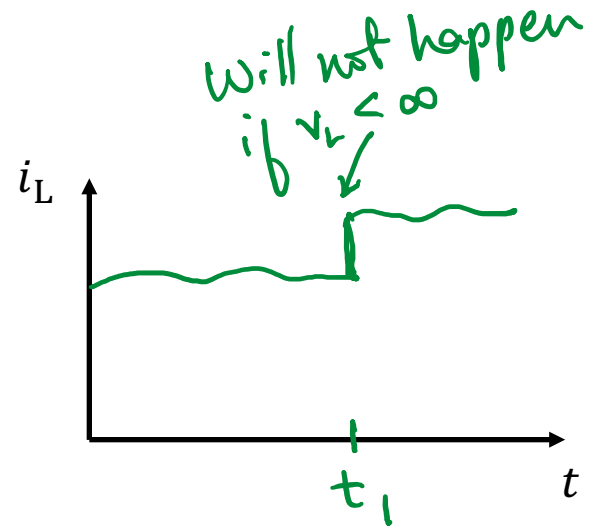
$$i_L(t_1^+) = i_L(t_1^-) \quad \text{if } v_L < \infty$$



State Property of Capacitors and Inductors

Capacitor

$$i_C = C \frac{dv_C}{dt}$$



$$v_C(t_1) = v_C(t_0) + \frac{1}{C} \int_{t_0}^{t_1} i_C(t) dt$$

Inductor

$$v_L = L \frac{di_L}{dt}$$



$$i_L(t_1) = i_L(t_0) + \frac{1}{L} \int_{t_0}^{t_1} v_L(t) dt$$

- Capacitors and inductors exhibit memory
 - Future capacitor voltage depends on past capacitor voltage
 - Future inductor current depends on past inductor current
- Circuits that contain capacitors and/or inductors exhibit dynamic behavior
 - Solving such circuits requires solving differential equations

State Variables

State Variables

Capacitor

Capacitor voltage is a state variable
– it has memory (remembers its previous state)

$$v_c(t)$$


Inductor

Inductor current is a state variable
– it has memory (remembers its previous state)

$$i_L(t)$$

Capacitors and Inductors Summary

Capacitor $C \equiv \frac{dq_C}{dv_C}$

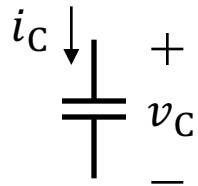

$$i_C = C \frac{dv_C}{dt}$$


$$v_C(t_1) = v_C(t_0) + \frac{1}{C} \int_{t_0}^{t_1} i_C(t) dt$$

$$v_C(t_1^+) = v_C(t_1^-) \quad \text{if } i_C(t_1) < \infty$$

Energy Stored

$$w_C = \frac{1}{2} C v_C^2$$

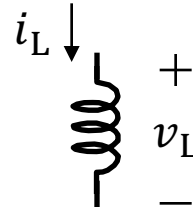Inductor $L \equiv \frac{d\lambda_L}{di_L}$



$$v_L = L \frac{di_L}{dt}$$

$$i_L(t_1) = i_L(t_0) + \frac{1}{L} \int_{t_0}^{t_1} v_L(t) dt$$

$$i_L(t_1^+) = i_L(t_1^-) \quad \text{if } v_L(t_1) < \infty$$

Energy Stored

$$w_L = \frac{1}{2} L i_L^2$$