

ECE/ENGRD 2100

Introduction to Circuits for ECE

Lecture 18

First Order RC and RL Circuits – Solution using
Intuitive Approach and ZIR/ZSR Method

Announcements

- Recommended Reading:
 - Textbook Chapter 7
- Upcoming due dates:
 - Prelab 3 due by 12:20 pm on Tuesday March 5, 2019
 - Homework 3 due by 11:59 pm on Monday March 11, 2019
 - Lab report 3 due by 11:59 pm on Friday March 15, 2019

Intuitive Approach

$$\text{Total Solution: } y(t) = y_h(t) + y_p(t)$$

$y_h(t)$ - Natural Response (Homogeneous Solution)

- Typically, dies with time
- Form depends on order of circuit
 - First-order circuits (RC, RL): exponential decay

$$K e^{-t/\tau} \quad \text{where} \quad \tau = \begin{cases} RC \\ L/R \end{cases}$$

$y_p(t)$ - Driven Response (Particular Solution)


- Continues in steady state
- Same form as the drive - $f(t)$

Determining DC Steady State

Inductor

$$v_L = L \frac{di_L}{dt}$$

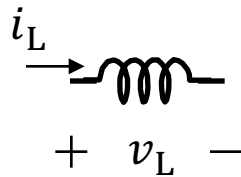$i_L = \text{constant} \xrightarrow{=dc} v_L = 0$




short circuit

Capacitor


$$i_C = C \frac{dv_C}{dt}$$

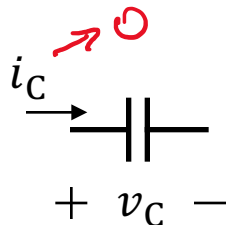$v_C = \text{constant}$ $\xrightarrow{}$ $i_C = 0$



open circuit

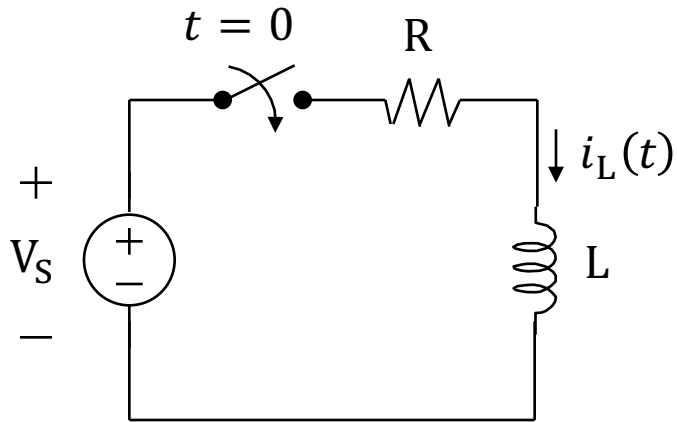RL Circuit – Solution using Intuitive Approach




$$i_L(0^-) = 0$$

$$i_L(0^+) = i_L(0^-) = 0$$


as $t \rightarrow \infty$
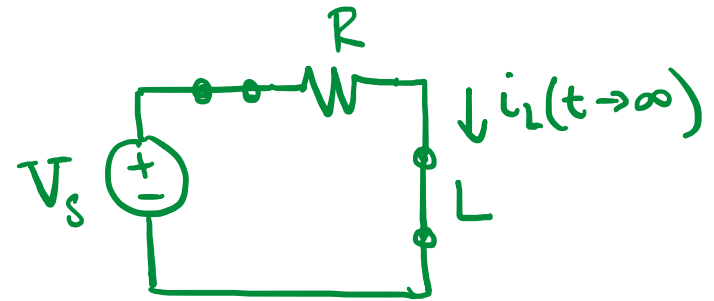
$$i_L(t \rightarrow \infty) = \frac{V_s}{R}$$





$$\tau = \frac{L}{R}$$


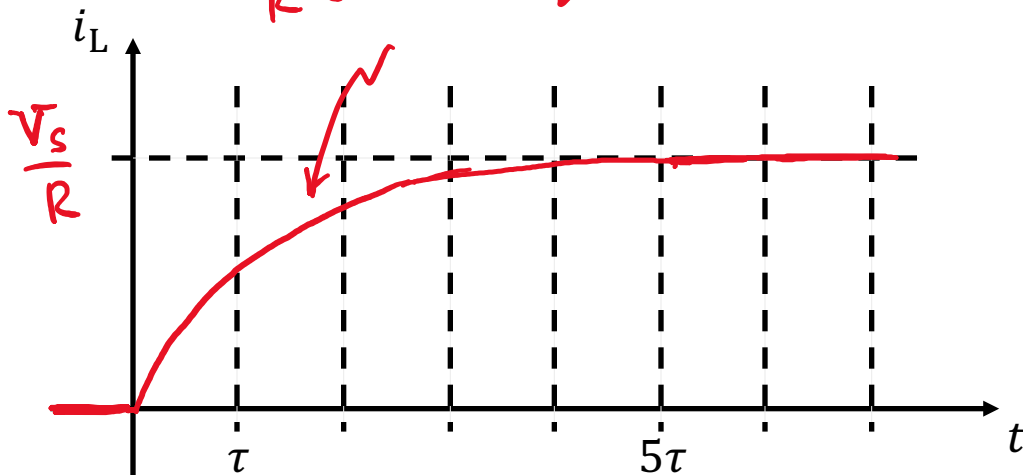
$$i_L = \frac{V_s}{R} (1 - e^{-t/\tau})$$



More Complex Circuit

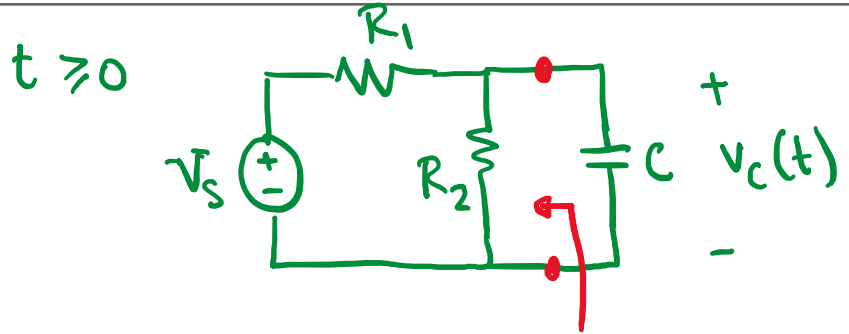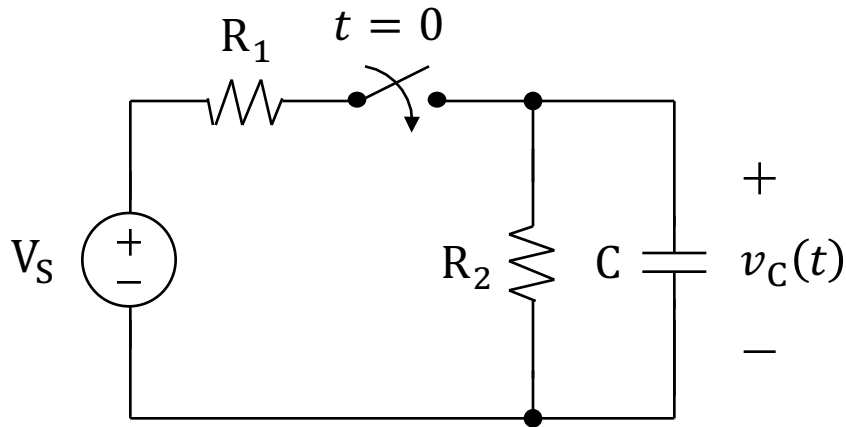


$R_1 || R_2 = R_{TH}$ \Downarrow Thevenin

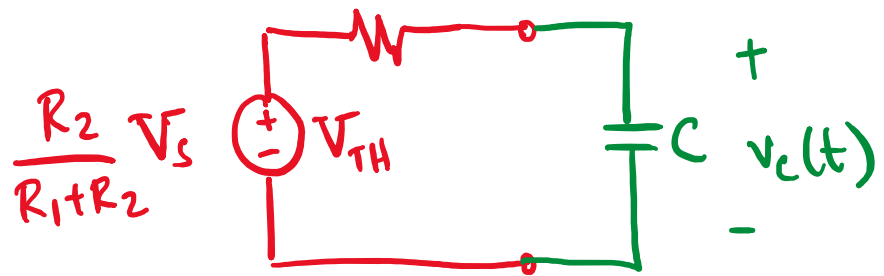
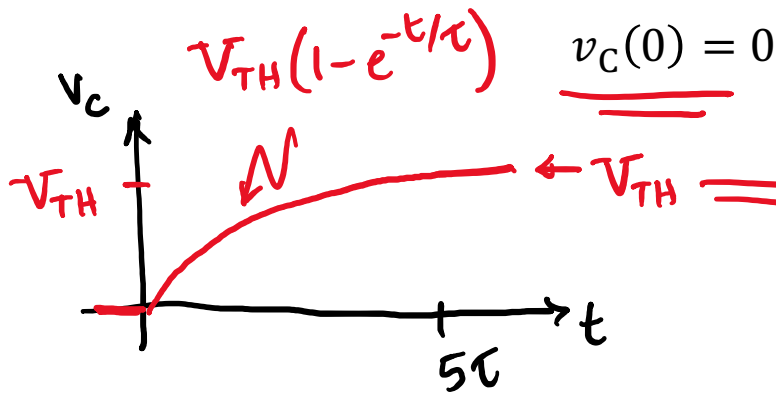


$$v_c(t) = \frac{R_2}{R_1 + R_2} V_s (1 - e^{-t/\tau})$$

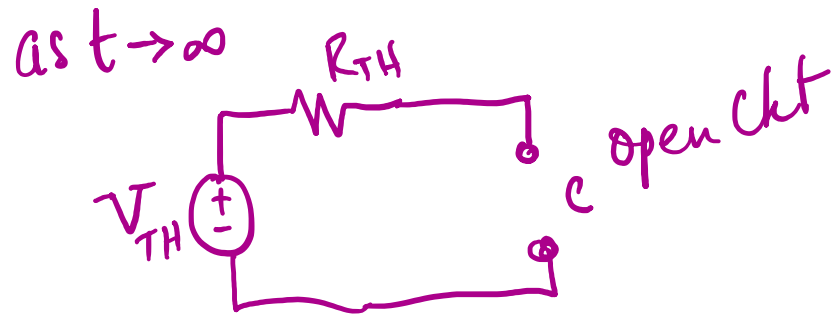
$$\tau = CR_{TH} = \frac{CR_1R_2}{R_1 + R_2}$$




Time Constants for Complex Circuits

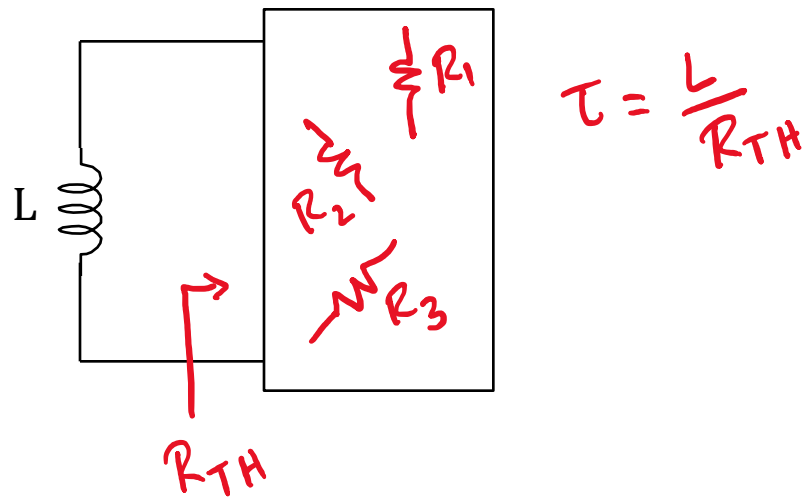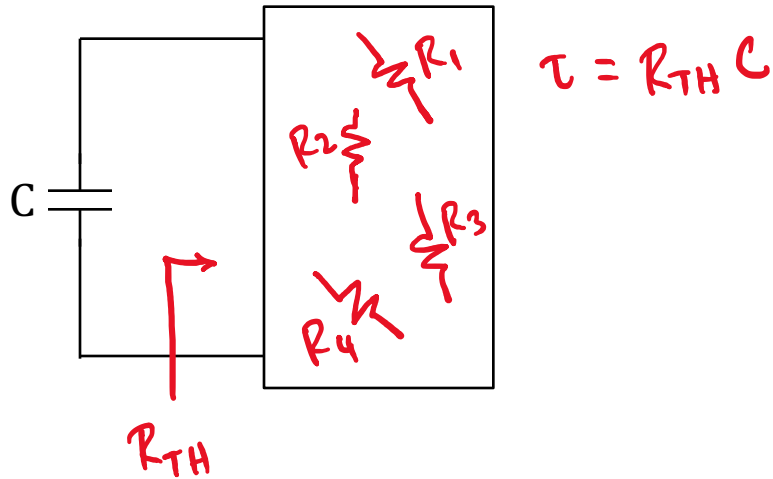


$$\tau = R C_{eq}$$

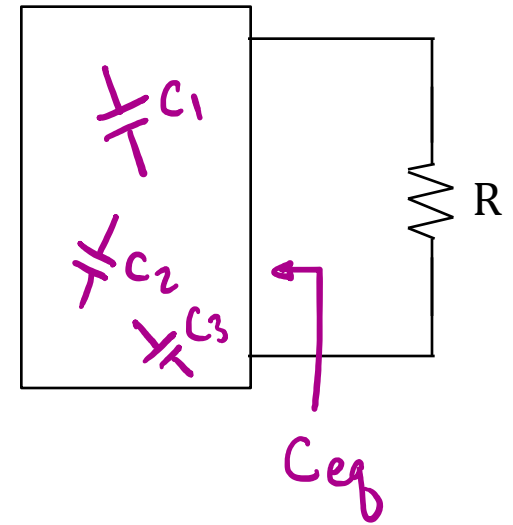

$$\tau = \frac{L_{eq}}{R}$$

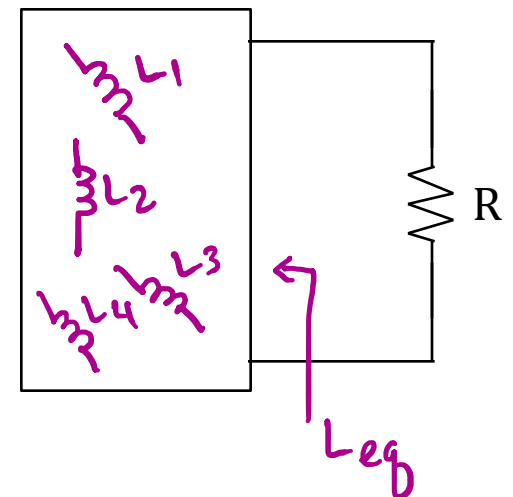


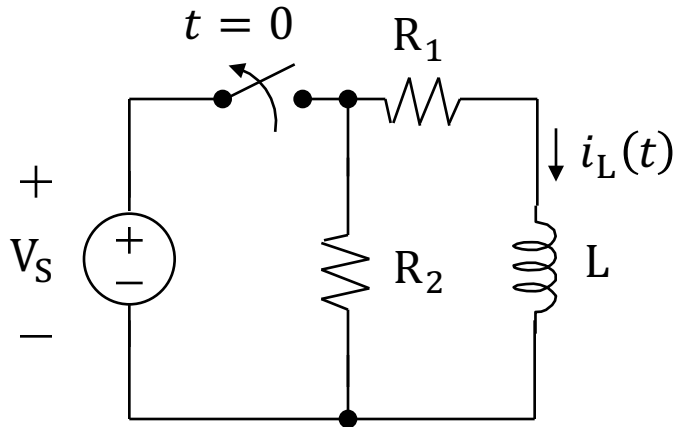Another RL Circuit Example – Intuitive Approach




Find $i_L(t)$ for $t > 0$

$t < 0$

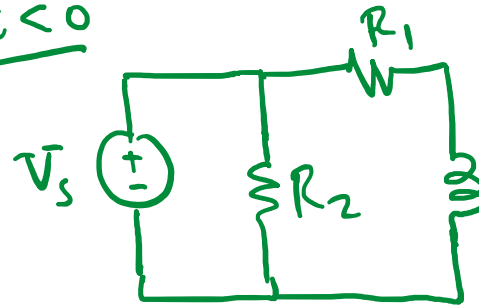



$t = 0^-$

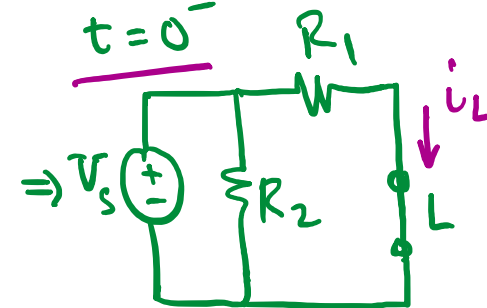

$$i_L(0^-) = \frac{V_s}{R_1}$$

Initial Condition: $i_L(0^+) = ?$
 $i_L(0^-) \rightarrow \frac{V_s}{R_1}$


$t > 0$

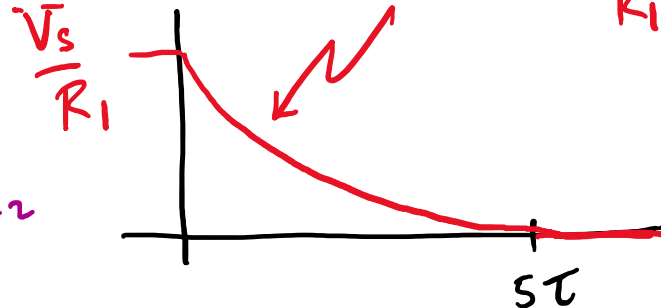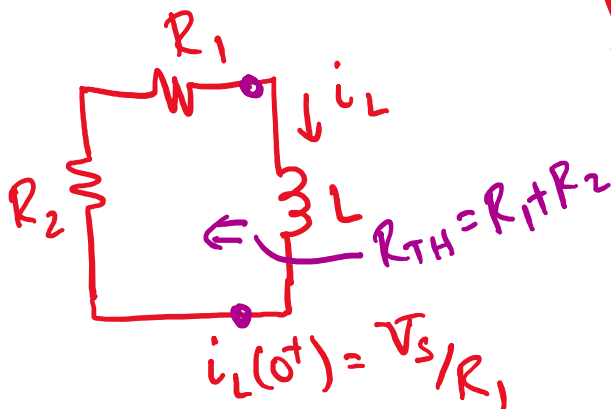

$$i_L(t) = \frac{V_s}{R_1} e^{-t/\tau}$$

$$\tau = \frac{L}{R_{TH}} = \frac{L}{R_1 + R_2}$$

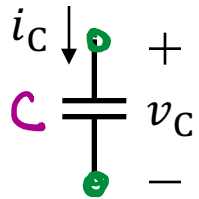Treating Initial Condition Like Input - Capacitor



$$v_c(0) = V_0$$


Same

$$i_c = C \frac{dv_c}{dt} \Rightarrow v_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(t') dt'$$

$$\Rightarrow v_c(t) = \frac{1}{C} \int_0^t i_c(t') dt' + v_c(0)$$

$$v_c(t) = \frac{1}{C} \int_0^t i_c(t') dt' + V_0$$

Same

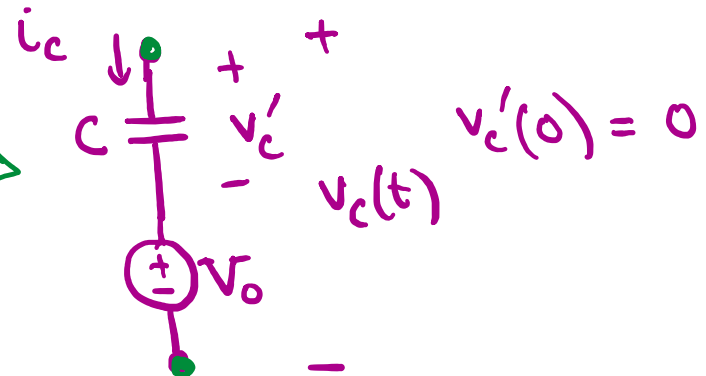


$$v'_c = \frac{1}{C} \int_0^t i_c(t') dt' + v'_c(0)$$

$$v_c = v'_c + V_0$$

$$v_c = \frac{1}{C} \int_0^t i_c(t') dt' + V_0$$

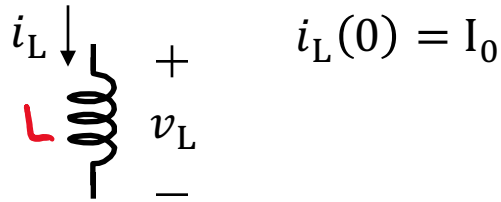
Treating Initial Condition Like Input - Inductor



$$v_L = L \frac{di_L}{dt}$$

➔
$$i_L(t) = \frac{1}{L} \int_0^t v_L(t') dt' + i_L(0)$$

same


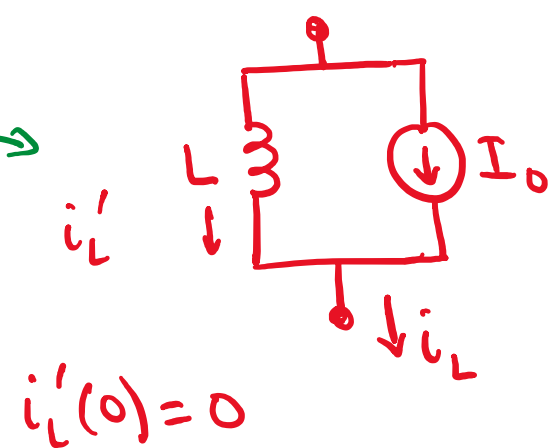


$$i_L = i'_L + I_0$$



Same

$$i_L = \frac{1}{L} \int_0^t v_L(t') dt' + \underline{\underline{i'_L(0)}} + I_0$$

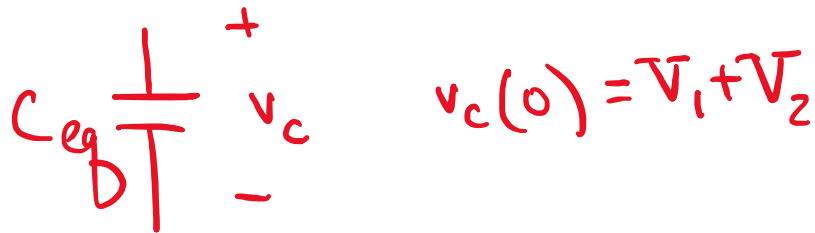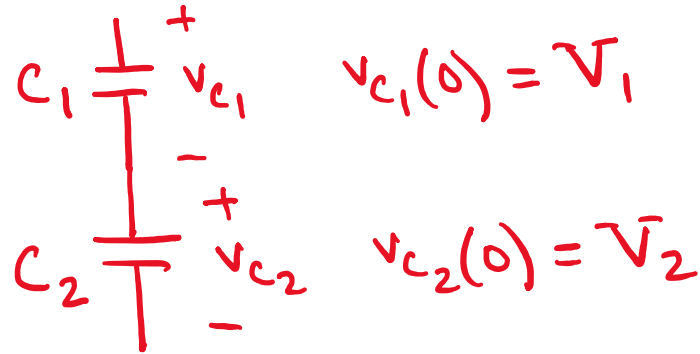More on Combining Capacitors and Inductors


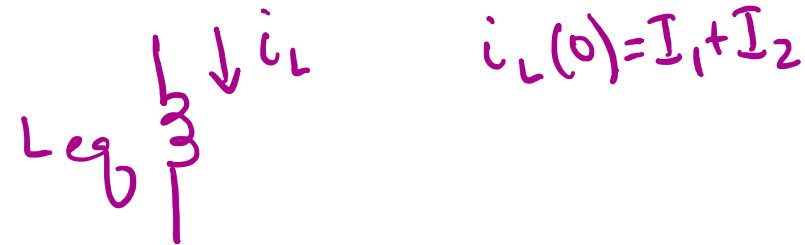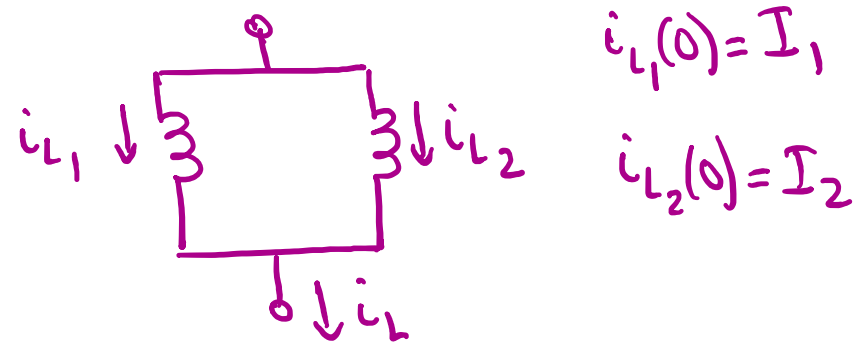
$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$$



$$L_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2} \right)^{-1}$$



ZIR and ZSR Approach (Superposition)

ZIR – Zero Input Response

ZSR – Zero State Response

No initial condition

No drive

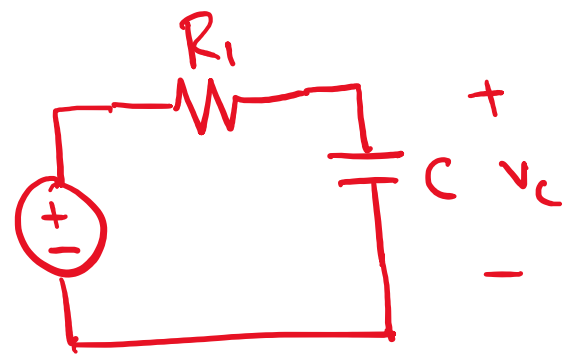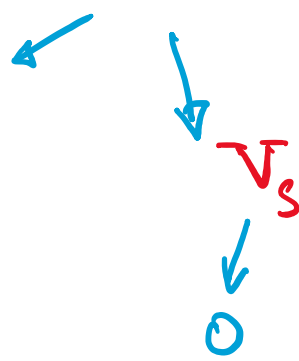


$v_c(0) = V_0$

$v'_c(0) = 0$


Total Response = ZIR + ZSR

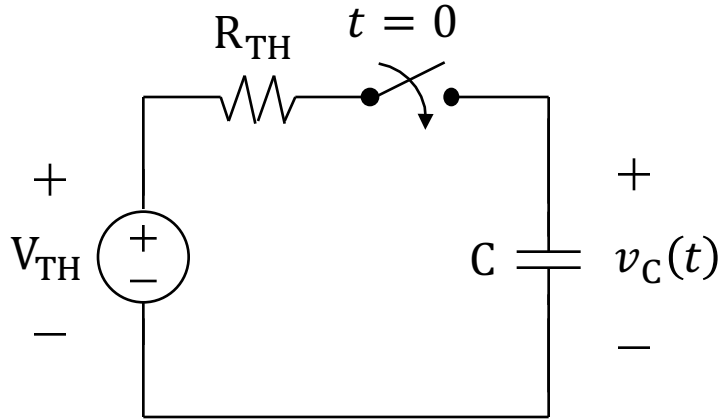RC Circuit with Non-Zero Initial Condition




$v_C(0^-) = V_0$

ZSR

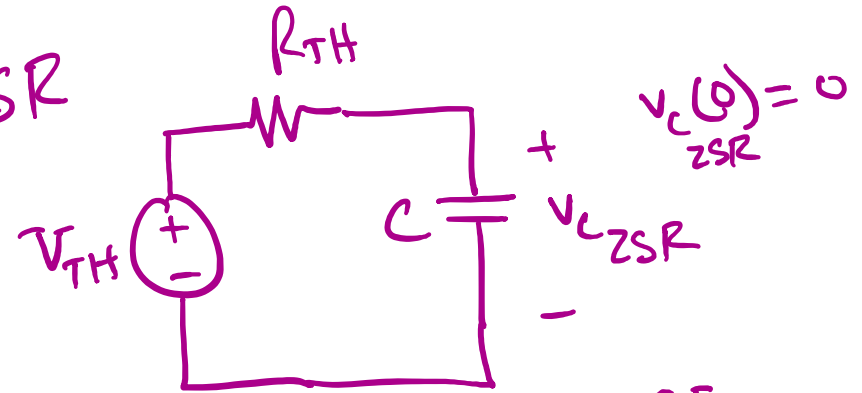


$v_{CZSR}(t) = V_{TH}(1 - e^{-t/\tau})$


$\tau = R_{TH} C$

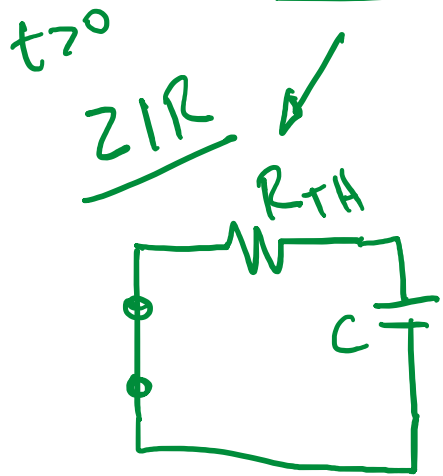

v_{CZIR}
 $v_C(0) = V_0$

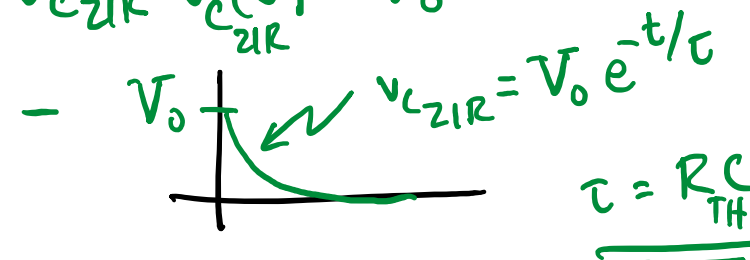

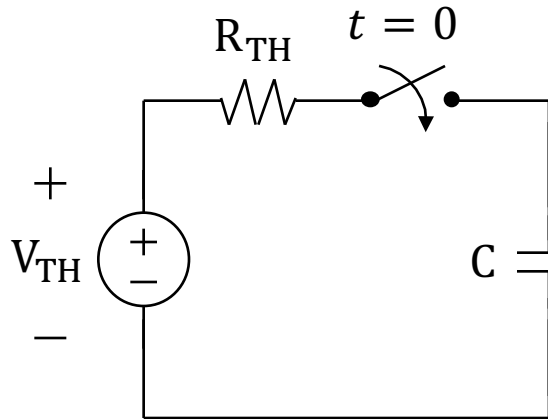RC Circuit with Non-Zero Initial Condition (Cont.)



$$v_C = v_{CZIR} + v_{CZSR}$$

$$v_C = V_0 e^{-t/\tau} + V_{TH}(1 - e^{-t/\tau})$$

$$v_C(0^-) = V_0$$



Natural Response
 Driven Response

Total Response \rightarrow $v_C(t) = V_0 e^{-t/\tau} + V_{TH}(1 - e^{-t/\tau})$

ZIR \rightarrow $V_0 e^{-t/\tau}$

ZSR \rightarrow $V_{TH}(1 - e^{-t/\tau})$
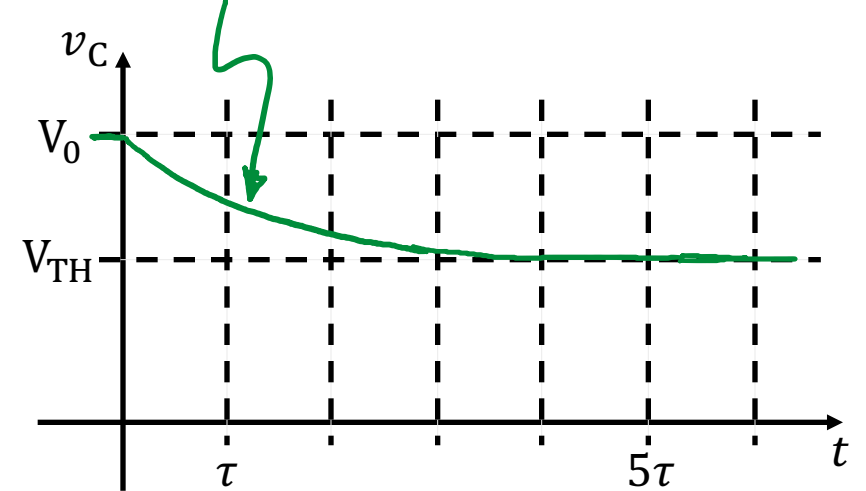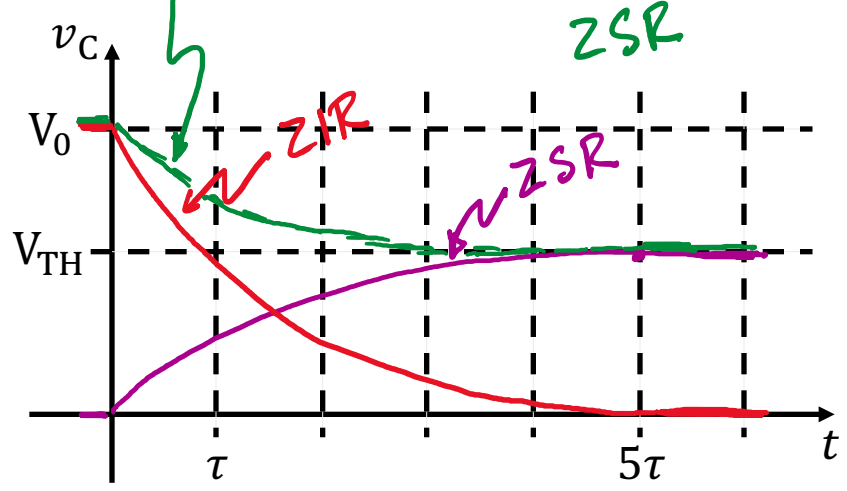
$$\Rightarrow v_C(t) = (V_0 - V_{TH})e^{-t/\tau} + V_{TH}$$



Total Response = ZIR + ZSR

Intuitive Approach with DC Drives - Summary

- Determine time constant $\tau = \begin{cases} R_{TH}C_{eq} \\ L_{eq}/R_{TH} \end{cases}$
- Determine initial value, using state variable continuity condition
- Determine final value, using steady state circuit
- Connect initial and final values with exponential $(Y_I - Y_F)e^{-t/\tau}$

$$v_C(t) = V_F + (V_I - V_F)e^{-t/\tau}$$

