

ECE/ENGRD 2100

Introduction to Circuits for ECE

Lecture 2

Circuit Laws and Circuit Analysis

Announcements

- Recommended Reading:
 - Textbook Chapter 3
- Lab 1 is next week (starting Tuesday January 29, 2019)
- Upcoming due dates:
 - Prelab 1 due by 12:20 pm on Tuesday January 29, 2019
 - Homework 1 due by 11:59 pm on Friday February 1, 2019
 - Lab report 1 due by 11:59 pm on Friday February 8, 2019

Discussion Sections


- Option A: Wed 1:25-2:15 pm and Fri 1:25-2:15 pm
- Option B: Wed 12:20-1:10 pm and Fri 1:25-2:15 pm
- Option C: Wed 1:25-2:15 pm and Thu 1:25-2:15 pm
- Option D: Thu 1:25-2:15 pm and Fri 1:25-2:15 pm

Option E: Tue 1:25-2:15pm and Fri 1:25-2:15pm


Both Discussions Sections cover the same material

Constitutive Relationships of Basic Circuit Elements


Voltage Source

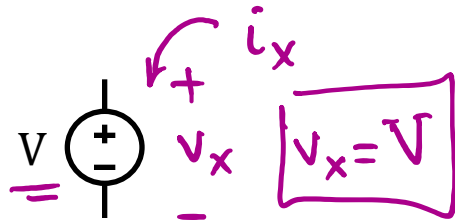

Current Source

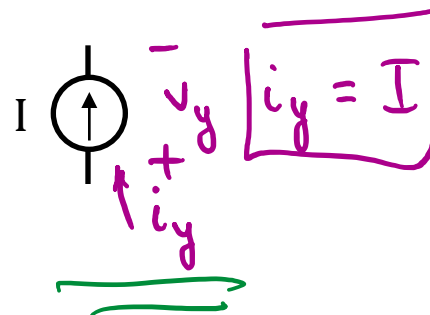


Resistor

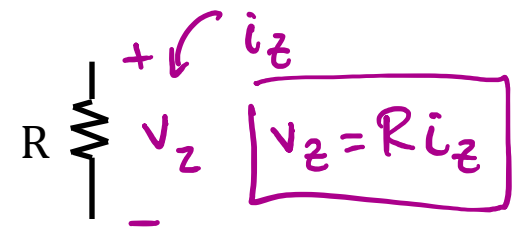

We could have defined the circuit variables with the opposite polarity as long as we follow the associated variables convention

Example

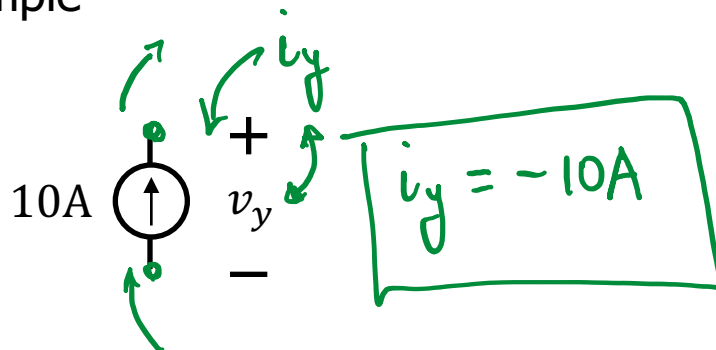

$$P = v \cdot i$$

if $P = +ve$

Power going in element


if $P = -ve$

Power coming out of element

Kirchhoff's Circuit Law

- To analyze circuits we need additional relations between the terminal variables of the circuit elements
- These additional relationships come from **Kirchhoff's Voltage Law (KVL)** and **Kirchhoff's Current Law (KCL)** that account for how the elements are interconnected

Kirchhoff's Voltage Law (KVL)

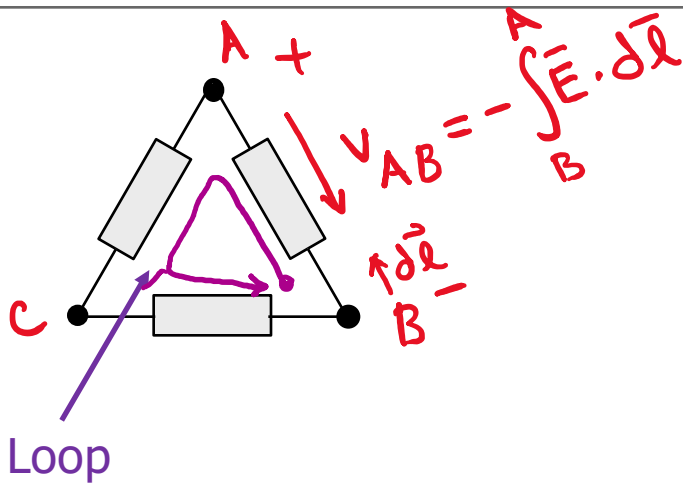

$$\oint \vec{E} \cdot d\vec{l} = -\frac{\partial}{\partial t} \iint \vec{B} \cdot d\vec{s} = -\frac{\partial \Phi}{\partial t} \quad \text{Faraday's Law}$$

$\frac{\partial \Phi}{\partial t} = 0$ through loops (not outside elements)

$$\oint \vec{E} \cdot d\vec{l} = 0$$

$$\Rightarrow \underbrace{\int_B^A \vec{E} \cdot d\vec{l}}_{-V_{AB}} + \underbrace{\int_A^C \vec{E} \cdot d\vec{l}}_{-V_{CA}} + \underbrace{\int_C^B \vec{E} \cdot d\vec{l}}_{-V_{BC}} = 0$$

$$\Rightarrow V_{AB} + V_{CA} + V_{BC} = 0$$

$$\Rightarrow \text{in general } \sum_{k=1}^N V_k = 0$$


Sum of voltages around a loop is zero

KVL (Cont.)

- In applying KVL, be careful about signs
- Good approach to remember: While traversing a loop, add with sign that one hits first (or add with sign that one hits second)


$$-v_1 - v_2 - v_3 = 0$$

$$v_1 + v_2 + v_3 = 0$$

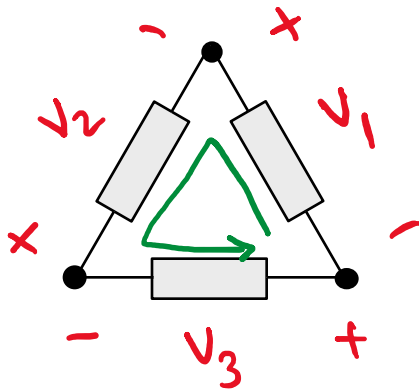

- You can go around the loop in either direction

Kirchhoff's Current Law (KCL)

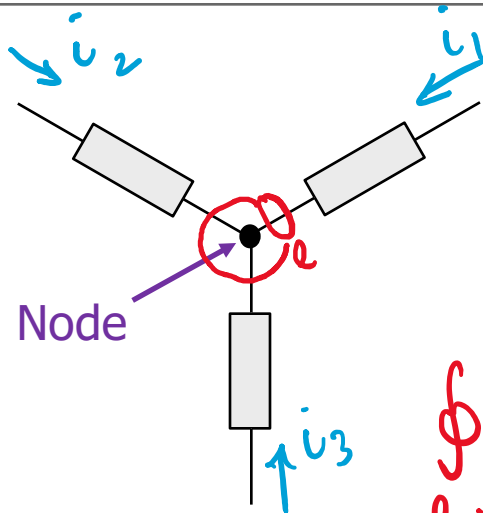

$$\oint_L \vec{H} \cdot d\vec{l} = \iint_S \vec{J} \cdot d\vec{s} + \frac{\partial}{\partial t} \iint_S \vec{D} \cdot d\vec{s} \quad \text{Ampere's Law}$$

$$\oiint_S \vec{D} \cdot d\vec{s} = \iiint_V \rho \, dv = q \quad \text{Gauss' Law}$$

$$\oint_L \vec{H} \cdot d\vec{l} = 0$$

$\frac{dq}{dt} = 0$ inside elements & at nodes

$$\underbrace{\oint_L \vec{H} \cdot d\vec{l}}_{=0} = \iint_S \vec{J} \cdot d\vec{s} + \underbrace{\frac{\partial}{\partial t} \iint_S \vec{D} \cdot d\vec{s}}_{=0}$$

$$\Rightarrow \iint_S \vec{J} \cdot d\vec{s} = 0$$


$$\Rightarrow i_1 + i_2 + i_3 = 0$$

$$\sum_{k=1}^M i_k = 0 \quad \text{KCL}$$

Sum of currents going into a node is zero

KCL (Cont.)

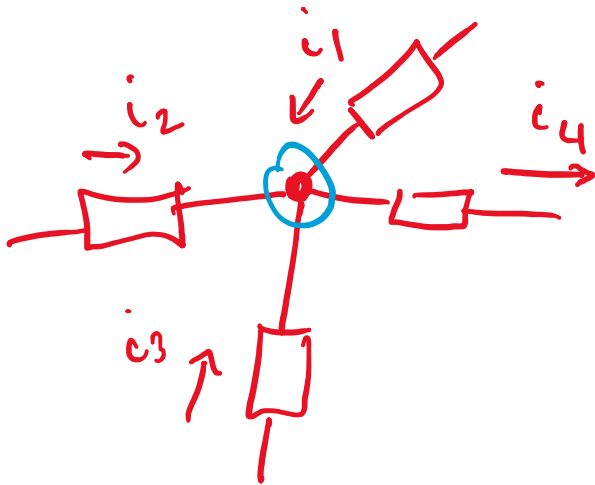- In applying KCL, be careful about signs
- Good approach to remember: **Either use all currents going out of the node, or all currents going into the node**




$$i_1 + i_2 + i_3 - i_4 = 0$$

- KCL also holds for any closed region of a circuit

KVL and KCL Examples

KVL: $\sum_{k=1}^N v_k = 0$

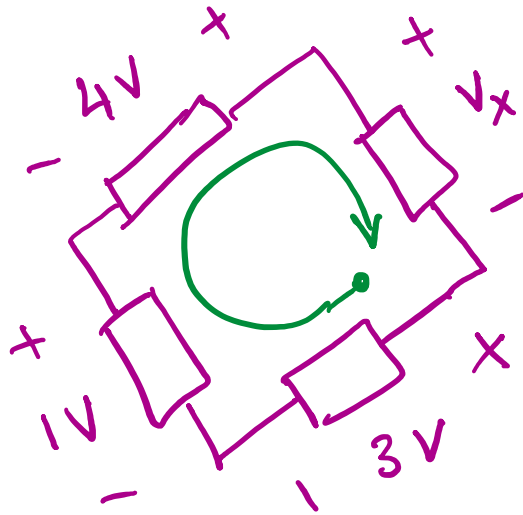


$$+3 - 1 - 4 + v_x = 0$$

$$v_x = \underline{\underline{2V}}$$

KCL: $\sum_{k=1}^M i_k = 0$

Our First Circuit Analysis

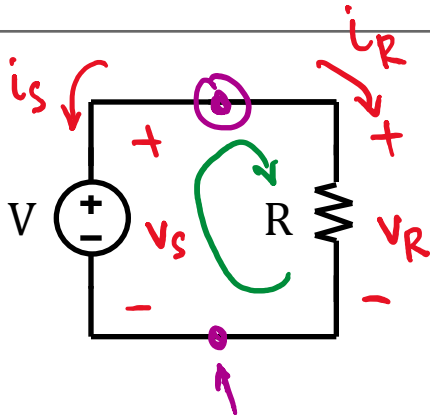

Analyzing (or “solving”) a circuit means finding the voltage across and the current through each element (“branch”)

Unknowns: v_s, i_s, v_R, i_R

Constitutive Relationships:

$$v_s = V \quad \text{--- (1)}$$

$$v_R = R i_R \quad \text{--- (2)}$$

Circuit Relationships:

$$-v_s + v_R = 0 \Rightarrow v_s = v_R \quad \text{--- (3) KVL}$$

$$\underline{-i_s - i_R = 0} \Rightarrow i_s = -i_R \quad \text{--- (4) KCL}$$


$$v_s = V$$

$$v_R = v_s = V$$

$$i_R = \frac{v_R}{R} = \frac{V}{R}$$

$$i_s = -i_R = -\frac{V}{R}$$

Graphical Solution

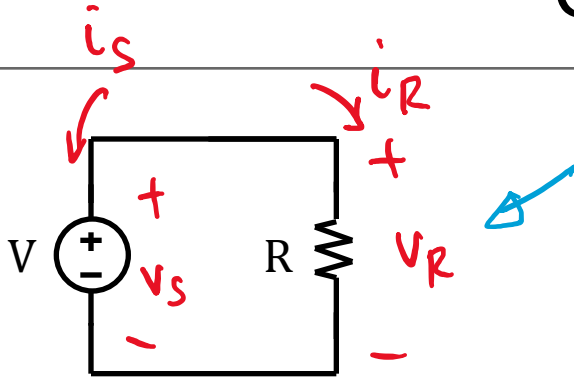

Constitutive Relationships:

$$v_S = V$$


$$v_R = Ri_R$$

Circuit Relationships:

$$\underline{v_R = v_S}$$


$$i_R = -i_S$$

Power Calculation

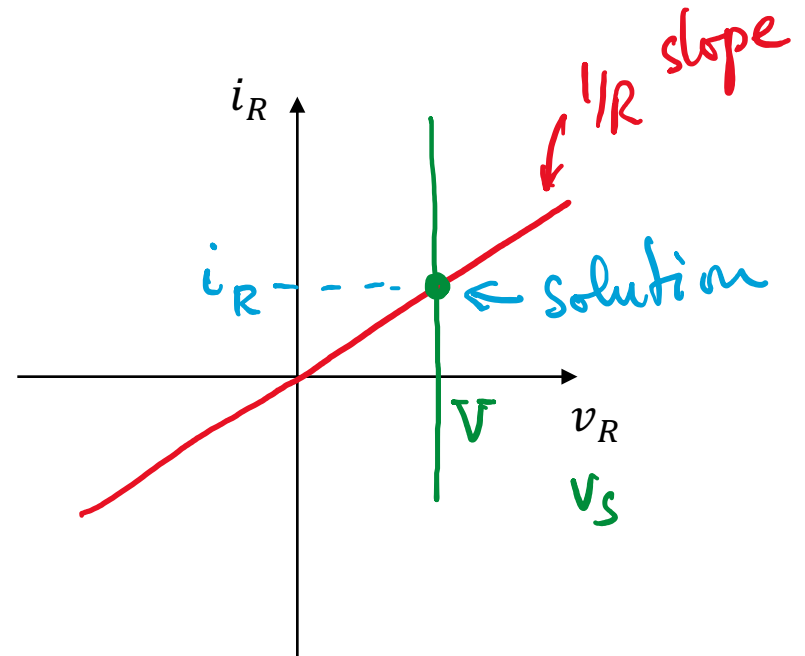

$$\underline{\underline{i_S = -i_R}}$$

Another Circuit Analysis Example

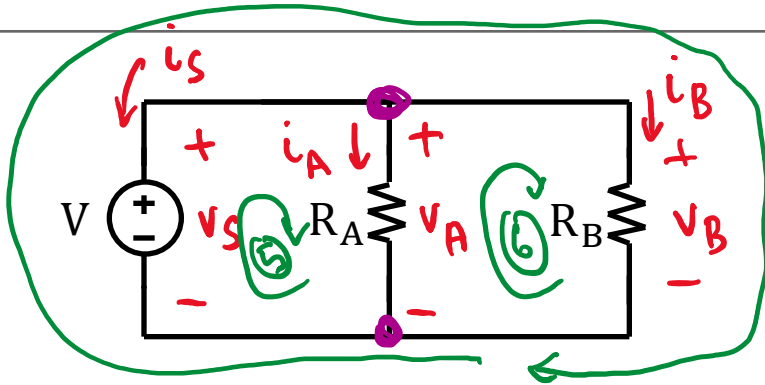

Unknowns: 6

Constitutive Relationships:

$$v_S = V \quad - \textcircled{1}$$

$$v_A = R_A i_A \quad - \textcircled{2}$$

$$v_B = R_B i_B \quad - \textcircled{3}$$

Circuit Relationships:

$$\text{KCL: } -i_S - i_A - i_B = 0 \quad - \textcircled{4}$$

$$\text{KVL: } -v_S + v_A = 0 \quad - \textcircled{5}$$

$$-v_A + v_B = 0 \quad - \textcircled{6}$$

Want to learn
easier ways
to solve
circuits

Another Circuit Analysis Example - Discussion

In general:

- For B branches (elements), there are $2B$ unknowns ←
- For B branches, there are B independent element equations ←
- For N nodes, there are $(N-1)$ independent KCL equations ←
- For N nodes and B branches, there are $(B-N+1)$ independent KVL equations

$$2B - (B + N - 1)$$

- In our example, we have six unknowns and six equations, so we can find a solution
- While this approach is good enough for a computer, it is too laborious for humans, especially when circuits become large
- So we need techniques and tricks to make solving circuits easier