

ECE/ENGRD 2100

Introduction to Circuits for ECE

Lecture 21


Undamped and Damped Second Order Circuits

Natural and Driven Response

Announcements

- Recommended Reading:
 - Textbook Chapter 8
- Upcoming due dates:
 - Lab report 3 due by 11:59 pm on Friday March 15, 2019
 - Prelab 4 due by 12:20 pm on Tuesday March 19, 2019
 - Homework 4 due by 11:59 pm on Friday March 22, 2019
 - Lab report 4 due by 11:59 pm on Friday March 29, 2019
- Prelim 2 on Thursday March 28, 2019 from 7:30 – 9 pm in 203 Phillips
 - Email afриди@cornell.edu if have conflict
 - Will cover material through Lecture 24
 - Prelim is closed-book and closed-notes
 - Two double-sided page formula sheet is allowed
 - Bring a calculator

Undriven LC Circuit – Intuitive Approach


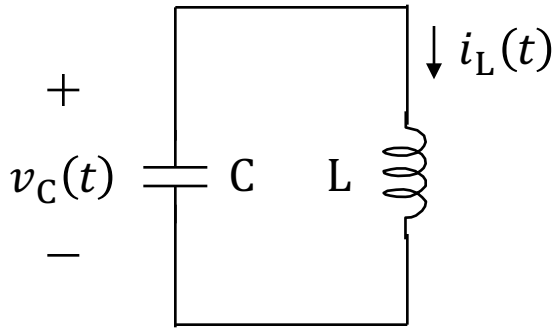


- Since there is no energy dissipating element in the circuit, $v_C(t)$ and $i_L(t)$ will oscillate without damping
- For total energy to remain constant, $v_C(t)$ and $i_L(t)$ oscillations must remain 90° out of phase
- ELI the ICE man: Voltage of inductor leads its current, $v_L (= v_C)$ leads i_L , i.e., if v_C oscillation is \cos then i_L oscillation is \sin (as \cos leads \sin by 90°)
- To determine dc value $v_C(t)$ and $i_L(t)$ will oscillate around: V_C, I_L , assume circuit has a little damping, then ask what values of $v_C(t)$ and $i_L(t)$ would the circuit settle down to – $v_C(t)$ and $i_L(t)$ will oscillate around these values.
- Frequency of oscillation, $\omega_0 = 1/\sqrt{LC}$
- Relationship between amplitudes of oscillations of v_C and i_L is given by $\Delta V_C = Z_0 \Delta I_L$ where $Z_0 = \sqrt{L/C}$

$$v_C(t) = \underline{B} \cos(\omega_0 t + \underline{\phi})$$


$$i_L(t) = \frac{B}{Z_0} \sin(\omega_0 t + \phi)$$

Driven LC Circuit – Impulse Input

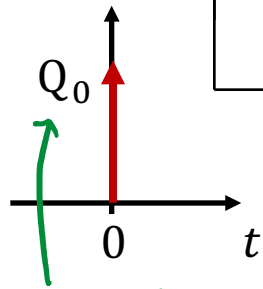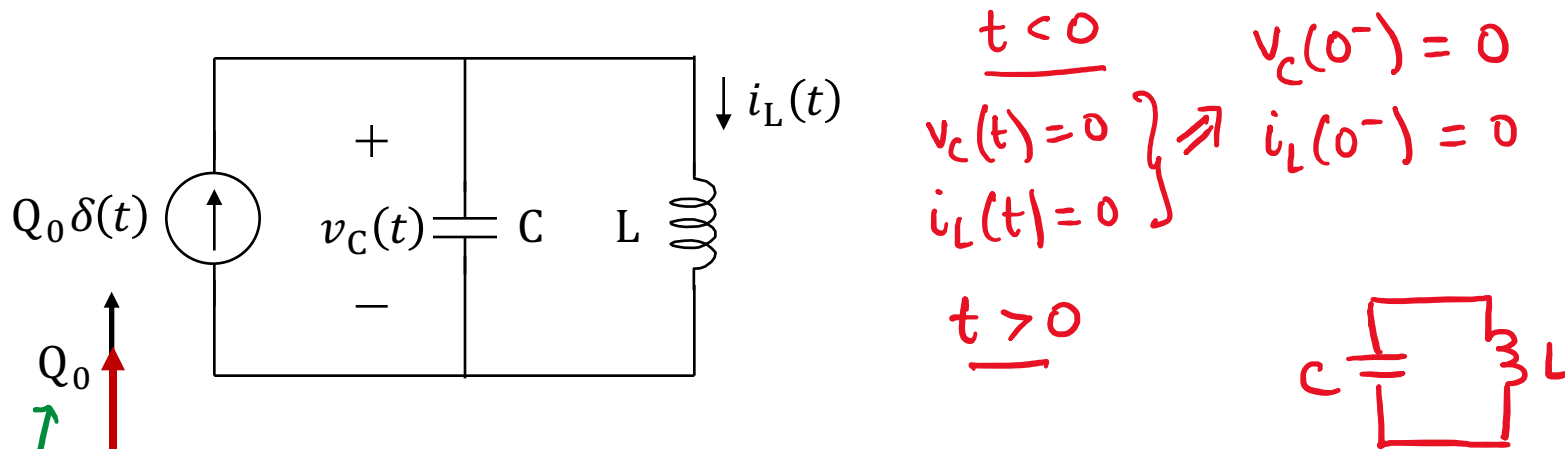

charge
 $[A \cdot s]$


$t = 0$
 $v_C(0^+) \neq i_L(0^+)$

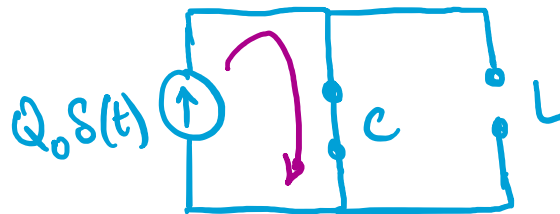

$$v_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(t') dt' \Rightarrow \underline{\underline{v_C(0^+)}} = \frac{1}{C} \int_{-\infty}^{0^+} i_C(t') dt' = \frac{1}{C} \int_{0^-}^{0^+} Q_0 \delta(t') dt' = \underline{\underline{\frac{Q_0}{C}}}$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(t') dt' \Rightarrow \underline{\underline{i_L(0^+)}} = \frac{1}{L} \int_{-\infty}^{0^+} v_L(t') dt' = \frac{1}{L} \int_{0^-}^{0^+} \frac{Q_0}{2C} dt' = \underline{\underline{0}}$$

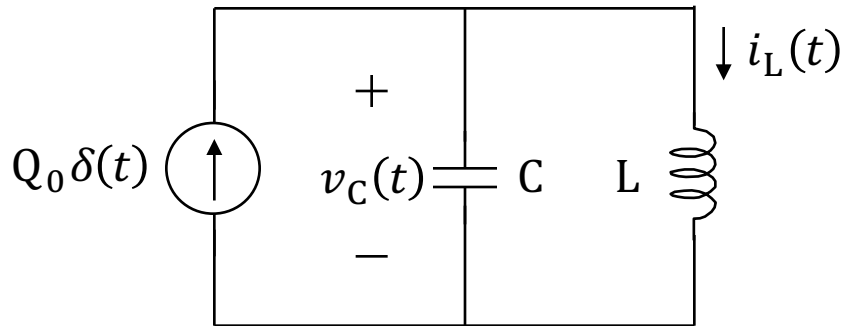Driven LC Circuit – Impulse Input (Cont.)



Initial Conditions

$$v_C(0^+) = \frac{Q_0}{C}$$

$$i_L(0^+) = 0$$

$$v_C(t) = B \cos(\omega_0 t + \phi) \Rightarrow v_C(0^+) = B \cos \phi = \frac{Q_0}{C}$$





$$i_L(t) = \frac{B}{Z_0} \sin(\omega_0 t + \phi) \Rightarrow i_L(0^+) = \frac{B}{Z_0} \sin \phi = 0 \Rightarrow \boxed{\phi = 0}$$

$$\Rightarrow B \cos(0) = \frac{Q_0}{C} \Rightarrow B = \frac{Q_0}{C}$$


$$v_C(t) = \frac{Q_0}{C} \cos \omega_0 t$$

$$i_L(t) = \frac{Q_0}{C Z_0} \sin \omega_0 t$$

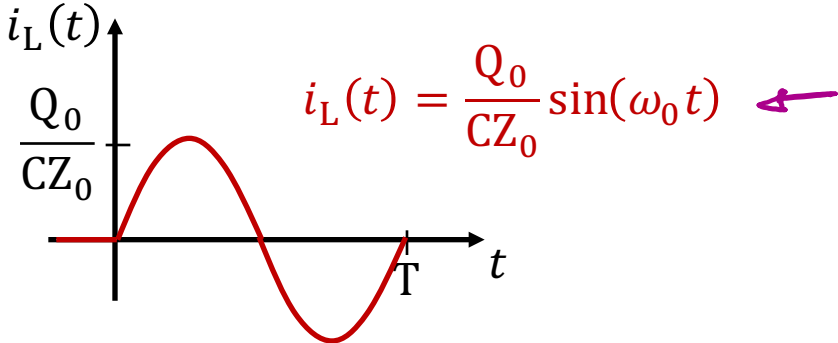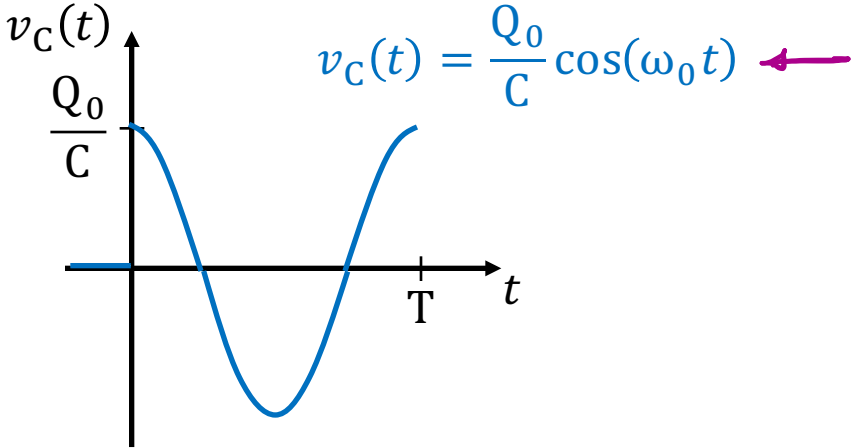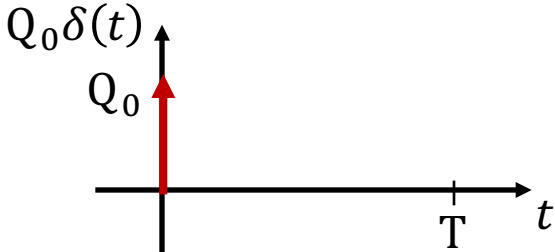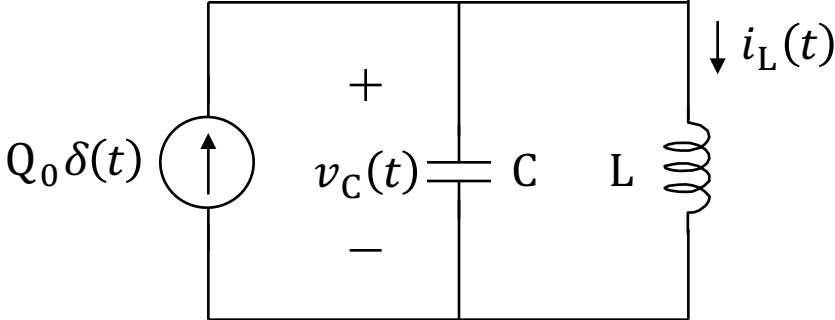Driven LC Circuit – Impulse Input – Waveforms



Driven LC Circuit – Step Input

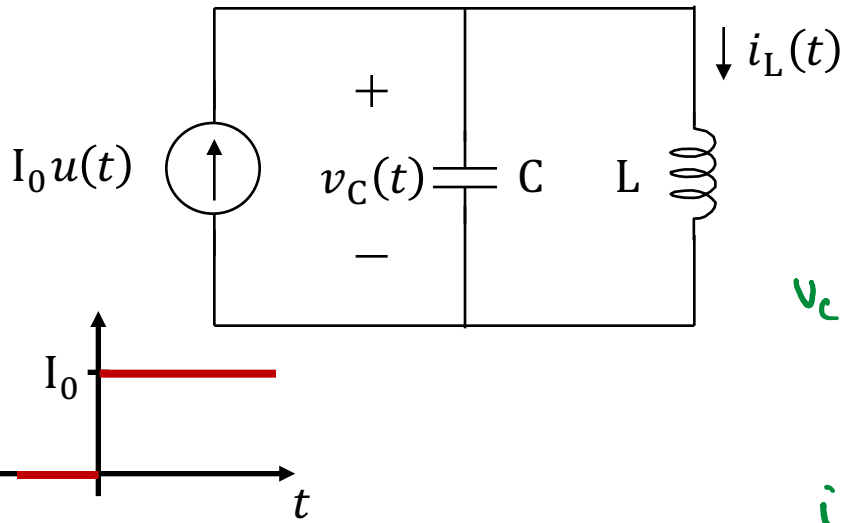

Total Response

= Natural Response + Driven Response

$$v_C(t) = v_{C,h} + v_{C,p}$$


$$v_C(t) = B \cos(\omega_0 t + \phi) + V_{DC}$$

$$i_L(t) = i_{L,h} + i_{L,p}$$

$$i_L(t) = \frac{B}{Z_0} \sin(\omega_0 t + \phi) + I_{DC}$$

"constant"
since
drive is
constant
for $t > 0$

DC Circuit ($t \rightarrow \infty$)

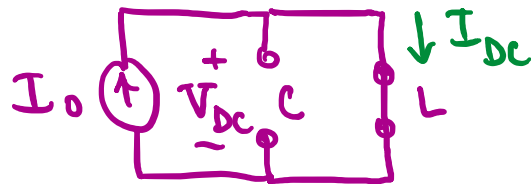


$$V_{DC} = 0$$

$$I_{DC} = I_0$$

$$v_C(t) = B \cos(\omega_0 t + \phi) + 0$$

$$i_L(t) = \frac{B}{Z_0} \sin(\omega_0 t + \phi) + I_0$$

Driven LC Circuit – Step Input (Cont.)

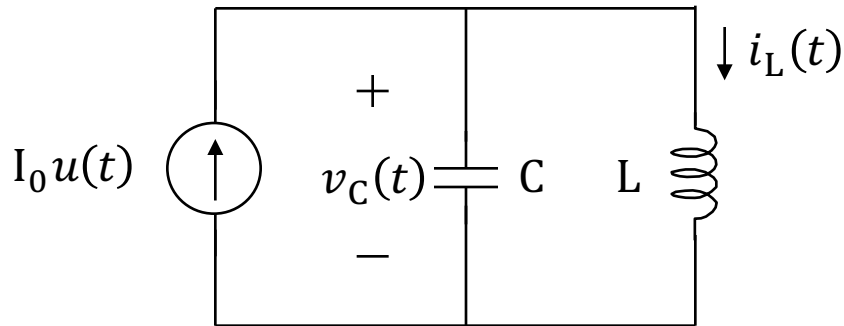

$$v_C(t) = B \cos(\omega_0 t + \phi) \quad \leftarrow$$

$$i_L(t) = \frac{B}{Z_0} \sin(\omega_0 t + \phi) + I_0$$

for $t > 0$ $v_C(0^+)$ $i_L(0^+)$

$$v_C(0^-) = 0 \quad i_L(0^-) = 0$$

$$\Rightarrow v_C(0^+) = v_C(0^-) = 0$$

$$i_L(0^+) = i_L(0^-) = 0$$

No impulse
so continuity
applies




$$v_C(0^+) = B \cos \phi = 0 \Rightarrow \phi = \pi/2$$

$$i_L(0^+) = \frac{B}{Z_0} \sin \phi + I_0 = 0 \Rightarrow \frac{B}{Z_0} = -I_0 \Rightarrow B = -I_0 Z_0$$

$$v_C(t) = -I_0 Z_0 \cos(\omega_0 t + \pi/2) = I_0 Z_0 \sin(\omega_0 t)$$


$$i_L(t) = -I_0 \sin(\omega_0 t + \pi/2) + I_0 = I_0 (1 - \cos(\omega_0 t))$$

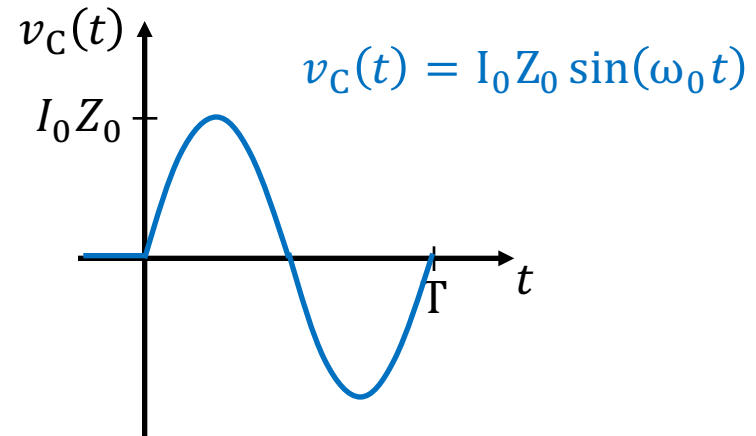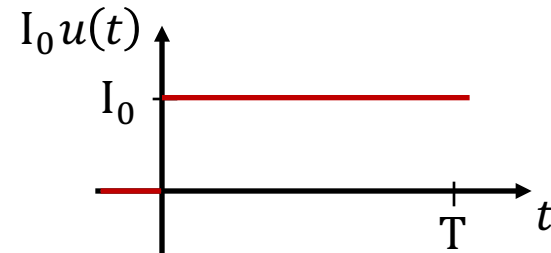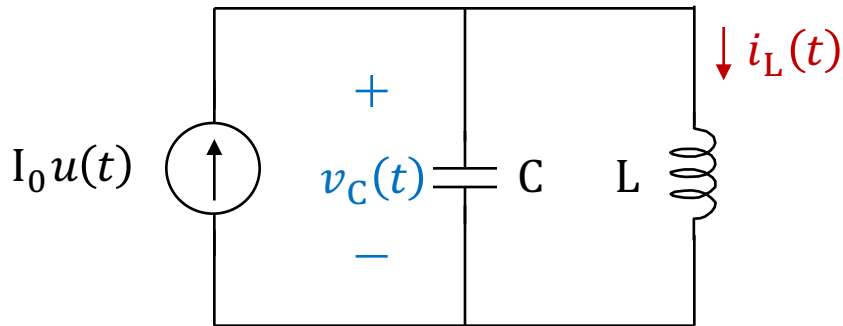Driven LC Circuit – Step Input – Waveforms



$$v_C(t) = -I_0 Z_0 \cos\left(\omega_0 t + \frac{\pi}{2}\right)$$


$$= I_0 Z_0 \sin(\omega_0 t)$$

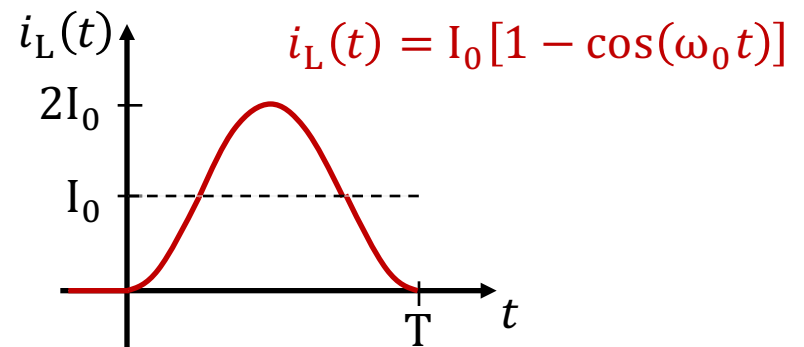

$$i_L(t) = I_0 \left[1 - \sin\left(\omega_0 t + \frac{\pi}{2}\right)\right]$$

$$= I_0 [1 - \cos(\omega_0 t)]$$

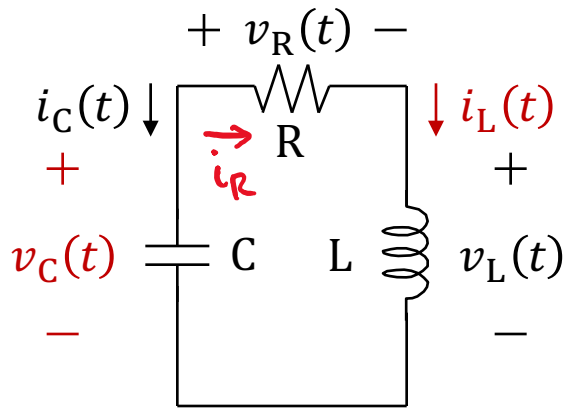Damped LC (RLC) Circuit – Natural Response



Series RLC Circuit

KVL

$$v_C = v_R + v_L$$

$$\Rightarrow v_C = -RC \frac{dv_C}{dt} - LC \frac{d^2 v_C}{dt^2}$$

$$i_C = C \frac{dv_C}{dt} = -i_L$$

$$v_L = L \frac{di_L}{dt} = -LC \frac{d^2 v_C}{dt^2}$$

$$v_R = Ri_R = Ri_L = -RC \frac{dv_C}{dt}$$

$$\Rightarrow \boxed{\frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{v_C}{LC} = 0}$$


Diff. Eq.

Damping Factor, $\alpha = \frac{R}{2L}$

Undamped Natural Radial Freq, $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\frac{d^2 v_C}{dt^2} + 2\alpha \frac{dv_C}{dt} + \omega_0^2 v_C = 0$$

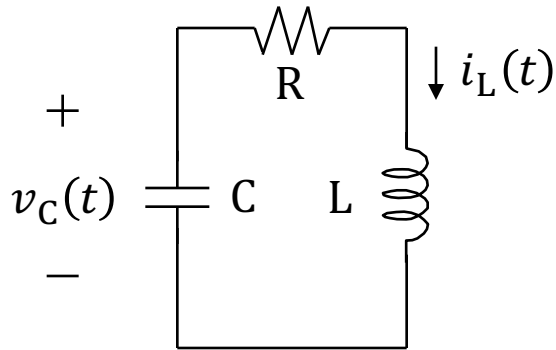Series RLC Circuit – Differential Equation



Series RLC Circuit

$$\frac{d^2 v_C}{dt^2} + 2\alpha \frac{dv_C}{dt} + \omega_0^2 v_C = 0$$

Particular Soln
!!
0

$$\alpha = \frac{R}{2L} \quad \text{Damping Factor}$$


$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{Undamped Natural Radial Frequency}$$

Homogeneous Soln $v_{C,h} = A e^{st}$

$$\Rightarrow \cancel{A s^2 e^{st}} + 2\alpha \cancel{A s e^{st}} + \omega_0^2 \cancel{A e^{st}} = 0$$

$$\Rightarrow \boxed{s^2 + 2\alpha s + \omega_0^2 = 0} \quad \leftarrow \text{Characteristic Eqn.}$$

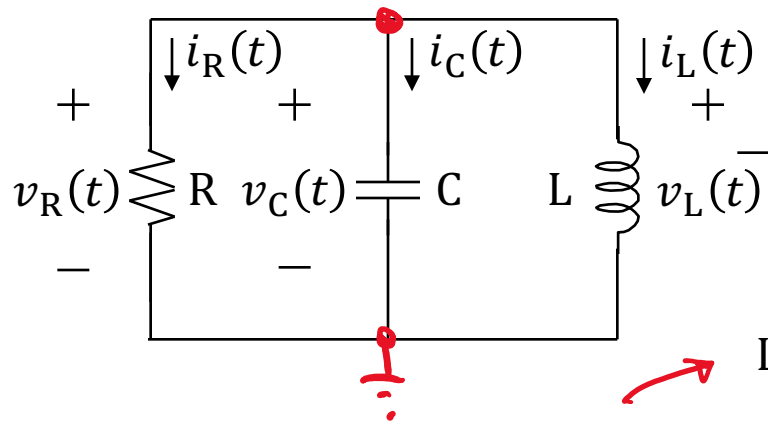Parallel RLC Circuit – Differential Equation



KCL

$$i_C + i_R + i_L = 0$$

$$LC \frac{d^2 i_L}{dt^2} + \frac{L}{R} \frac{di_L}{dt} + i_L = 0$$

Diff. Equ.

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = 0$$

$$v_L = L \frac{di_L}{dt} = v_C$$

$$i_C = C \frac{dv_C}{dt} = LC \frac{d^2 i_L}{dt^2}$$

$$i_R = \frac{v_R}{R} = \frac{v_C}{R} = \frac{L}{R} \frac{di_L}{dt}$$


$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$i_{L,h} = A e^{st} \Rightarrow \cancel{As^2 e^{st}} + 2\alpha \cancel{A s e^{st}} + \omega_0^2 \cancel{A e^{st}} = 0$$

$$\Rightarrow s^2 + 2\alpha s + \omega_0^2 = 0$$

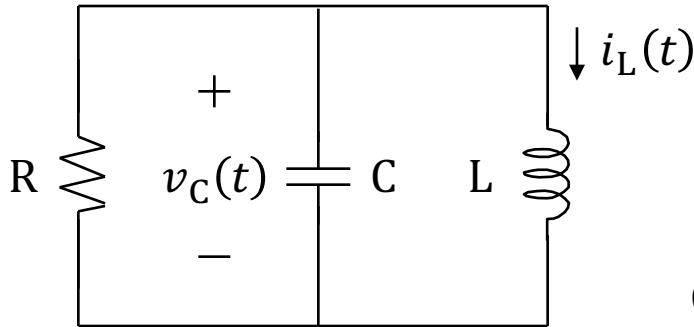RLC Circuit: Characteristic Equation - General Form



Parallel RLC Circuit

$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Ae^{st}

Characteristic equation

$$s^2 + 2\alpha s + \omega_0^2 = 0$$




$$s = \frac{-2\alpha \pm \sqrt{4\alpha^2 - 4\omega_0^2}}{2}$$

$$\Rightarrow s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

or
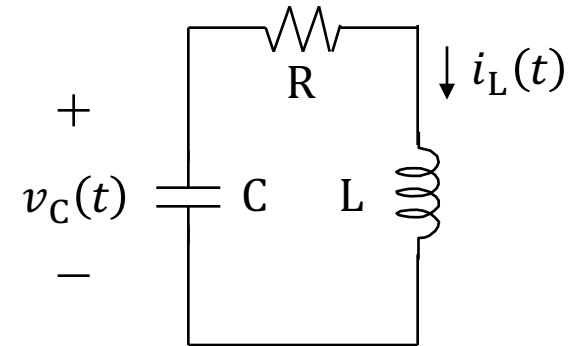
$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$



Series RLC Circuit

$$\alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Characteristic Equation – Possible Solution – Case 1

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


Case 1: $\alpha > \omega_0$

$$\Rightarrow s_1 = -\alpha + \underbrace{\sqrt{\alpha^2 - \omega_0^2}}_{+ve}$$


$$s_2 = -\alpha - \underbrace{\sqrt{\alpha^2 - \omega_0^2}}_{+ve}$$

Two real solutions
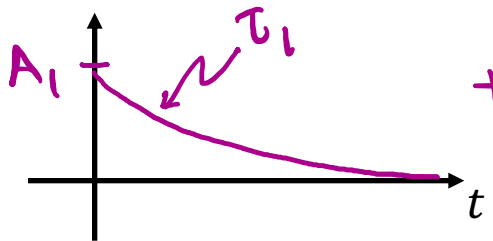
$$v_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} = A_1 e^{-t/\tau_1} + A_2 e^{-t/\tau_2}$$



+

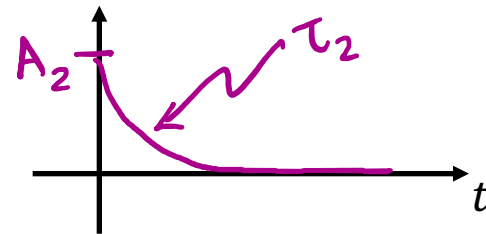

Characteristic Equation – Possible Solution – Case 2

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


Case 2: $\alpha = \omega_0$

$$s_1 = -\alpha$$


$$s_2 = -\alpha$$

$$v_c(t) = A_1 e^{-\alpha t} + \underline{A_2 t e^{-\alpha t}}$$

Only when $\alpha = \omega_0$

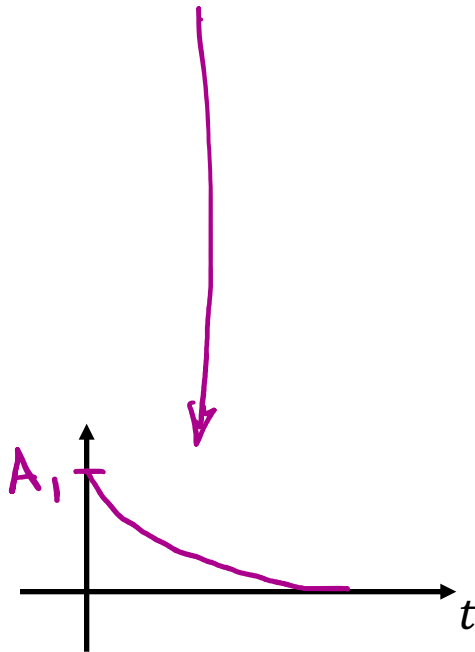

+

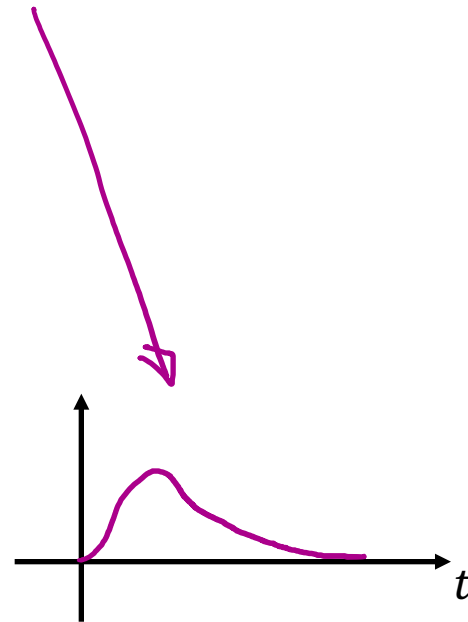

Characteristic Equation – Possible Solution – Case 3

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Case 3: $\alpha < \omega_0$

$$s_1 = -\alpha - j\sqrt{\omega_0^2 - \alpha^2}$$

$$s_2 = -\alpha + j\sqrt{\omega_0^2 - \alpha^2}$$

Damped Natural Radial Frequency, ω_d

$$v_c(t) = A_1 e^{(-\alpha - j\omega_d)t} + A_2 e^{(-\alpha + j\omega_d)t} = e^{-\alpha t} [A_1 e^{-j\omega_d t} + A_2 e^{+j\omega_d t}]$$

$$v_c(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$

