

ECE/ENGRD 2100

Introduction to Circuits for ECE


Lecture 22

Driven Damped Second Order LC Circuits

Announcements

- Recommended Reading:
 - Textbook Chapter 8
- Upcoming due dates:
 - Lab report 3 due by 11:59 pm on Friday March 15, 2019
 - Prelab 4 due by 12:20 pm on Tuesday March 19, 2019
 - Homework 4 due by 11:59 pm on Monday March 25, 2019
 - Lab report 4 due by 11:59 pm on Monday April 8, 2019
- Prelim 2 on Thursday March 28, 2019 from 7:30 – 9 pm in 203 Phillips
 - Email afridi@cornell.edu if have conflict
 - Will cover material through Lecture 24
 - Prelim is closed-book and closed-notes
 - Two double-sided page formula sheet is allowed
 - Bring a calculator

RLC Circuit – Natural Response – Summary

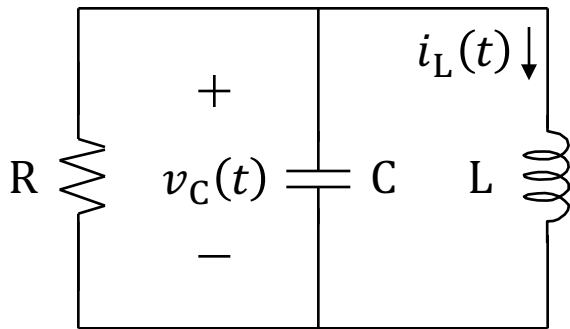

Parallel RLC Circuit

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Characteristic equation: $s^2 + 2\alpha s + \omega_0^2 = 0$ ←

→ $s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$ ←

$\alpha > \omega_0$ Overdamped

$$A_1 e^{-\left(\alpha - \sqrt{\alpha^2 - \omega_0^2}\right)t} + A_2 e^{-\left(\alpha + \sqrt{\alpha^2 - \omega_0^2}\right)t}$$

$\alpha = \omega_0$ Critically damped


$$A_1 e^{-\alpha t} + A_2 t e^{-\alpha t}$$

$\alpha < \omega_0$ Underdamped

$$\omega_d \equiv \sqrt{\omega_0^2 - \alpha^2}$$

$$A_1 e^{-\alpha t} \cos(\omega_d t) + A_2 e^{-\alpha t} \sin(\omega_d t)$$
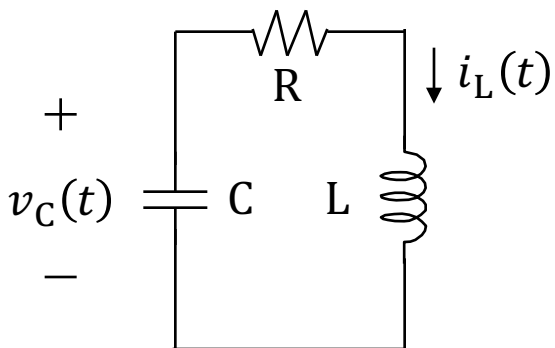
$$= B e^{-\alpha t} \cos(\omega_d t + \phi)$$



Series RLC Circuit


$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Quality Factor


Characteristic equation: $s^2 + 2\alpha s + \omega_0^2 = 0$

Quality factor: $Q \equiv \frac{\omega_0}{2\alpha}$

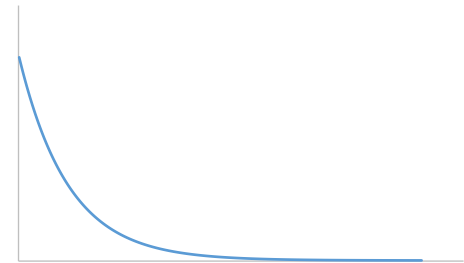
Overdamped: $\alpha > \omega_0$ \Rightarrow $Q < \frac{1}{2}$



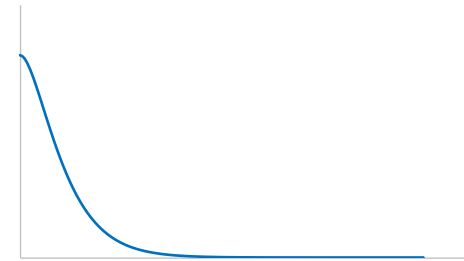
Critically damped: $\alpha = \omega_0$ \Rightarrow $Q = \frac{1}{2}$



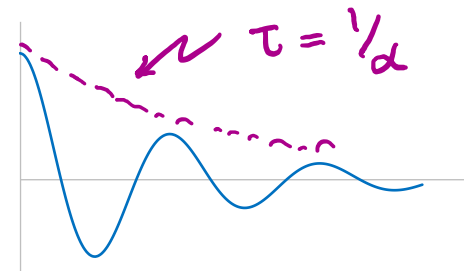Underdamped: $\alpha < \omega_0$ \Rightarrow $Q > \frac{1}{2}$



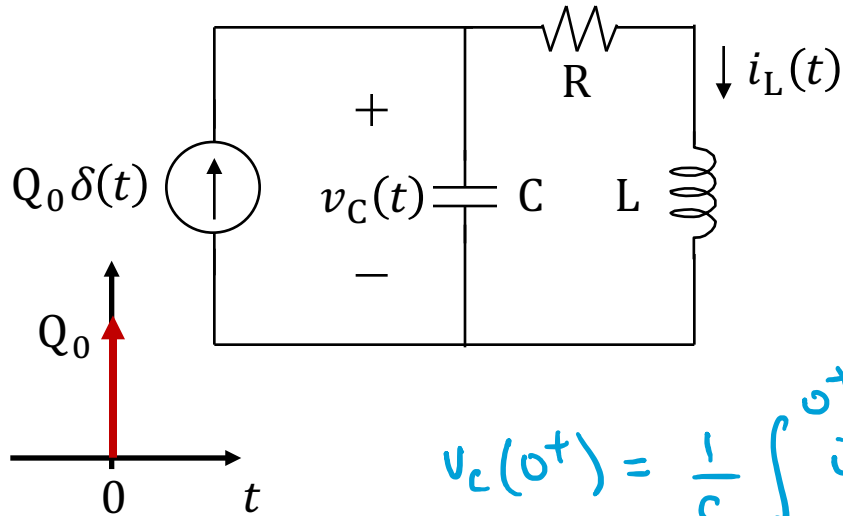Underdamped Series RLC Circuit - Impulse Response




$$v_C(0^+) = ?$$

$$i_L(0^+) = ?$$

$$v_C(0^+) = \frac{1}{C} \int_{-\infty}^{0^+} i_C(t') dt' = \frac{1}{C} \int_{0^-}^{0^+} Q_0 \delta(t') dt' = \frac{Q_0}{C}$$

$$i_L(0^+) = \frac{1}{L} \int_{0^-}^{0^+} v_L(t') dt' = 0$$

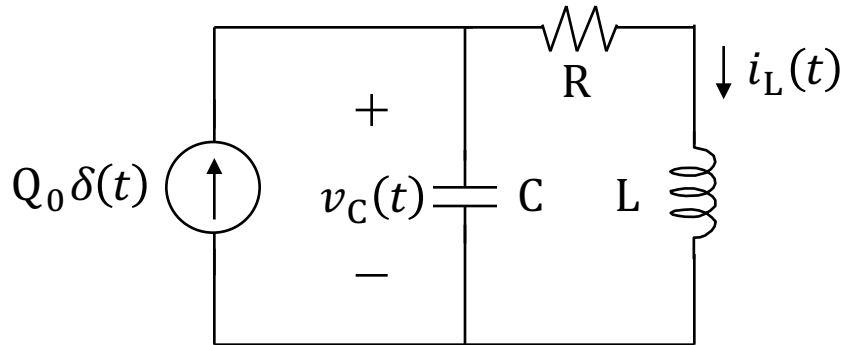Underdamped RLC – Impulse Response (Cont.)



$$v_C(0^+) = \frac{Q_0}{C} \quad i_L(0^+) = 0$$


Assuming Underdamped

$t > 0$


$$v_C(t) = B e^{-\alpha t} \cos(\omega_d t + \phi)$$

$$i_L = -i_C = -C \frac{dv_C}{dt}$$
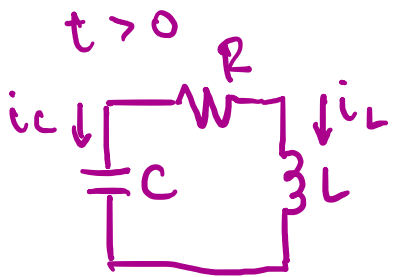
$$i_L = -CB \left[-\alpha e^{-\alpha t} \cos(\omega_d t + \phi) - \omega_d e^{-\alpha t} \sin(\omega_d t + \phi) \right]$$



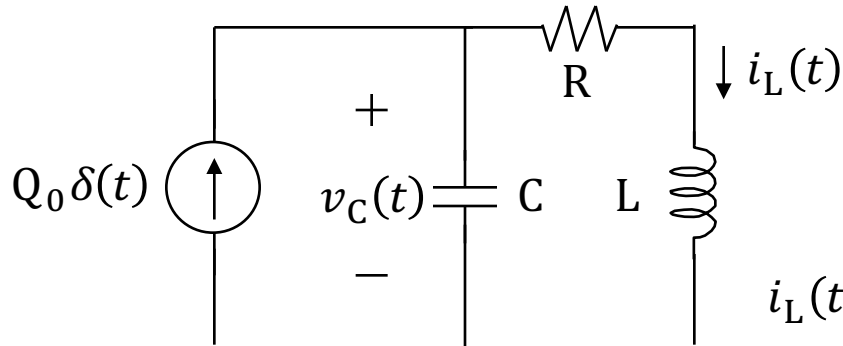Underdamped RLC – Impulse Response (Cont.)



$$\underline{v_C(t) = e^{-\alpha t} B \cos(\omega_d t + \phi)}$$

$$\underline{i_L(t) = e^{-\alpha t} B C [\omega_d \sin(\omega_d t + \phi) + \alpha \cos(\omega_d t + \phi)]}$$

Use Trigonometric Identity:

$$\underline{a \sin(x) + b \cos(x) = \sqrt{a^2 + b^2} \sin(x + \tan^{-1}(b/a))}$$

$$\Rightarrow i_L(t) = e^{-\alpha t} B C \underbrace{\sqrt{\omega_d^2 + \alpha^2}}_{\omega_0} \sin(\omega_d t + \phi + \tan^{-1}(\alpha/\omega_d))$$


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$\sqrt{\omega_d^2 + \alpha^2} = \omega_0$$

$$C \omega_0 = C \frac{1}{\sqrt{LC}} = \sqrt{\frac{C}{L}} = \frac{1}{Z_0}$$

$$i_L(t) = e^{-\alpha t} \frac{B}{Z_0} \sin(\omega_d t + \phi + \tan^{-1}(\alpha/\omega_d))$$

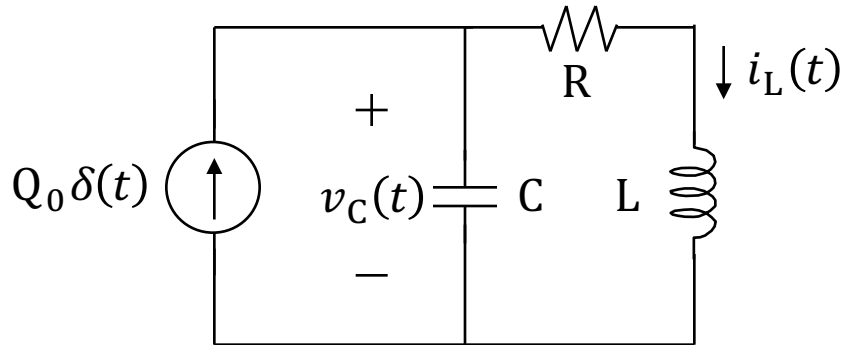Underdamped RLC – Impulse Response (Cont.)



$$v_C(t) = e^{-\alpha t} B \cos(\omega_d t + \phi)$$

$$i_L(t) = e^{-\alpha t} \frac{B}{Z_0} \sin(\omega_d t + \phi + \tan^{-1}(\alpha/\omega_d))$$


$$v_C(0^+) = \frac{Q_0}{C} \quad i_L(0^+) = 0$$

$$v_C(0^+) = B \cos \phi = \frac{Q_0}{C}$$





$$i_L(0^+) = \frac{B}{Z_0} \sin(\underbrace{\phi + \tan^{-1}(\alpha/\omega_d)}_{=0}) = 0 \Rightarrow \phi = -\tan^{-1}(\alpha/\omega_d)$$

$$\tan \phi = -\alpha/\omega_d$$

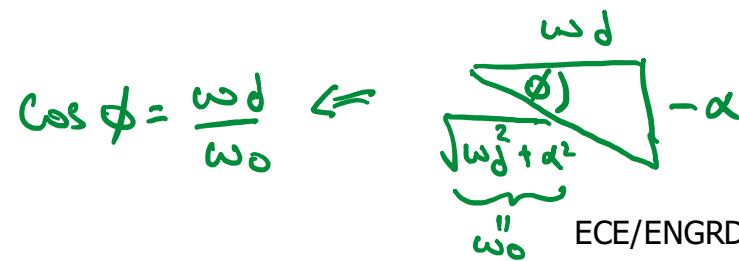
$$\Rightarrow B = \frac{Q_0}{C} \frac{1}{\cos \phi} = \frac{\omega_0}{\omega_d} \frac{Q_0}{C}$$



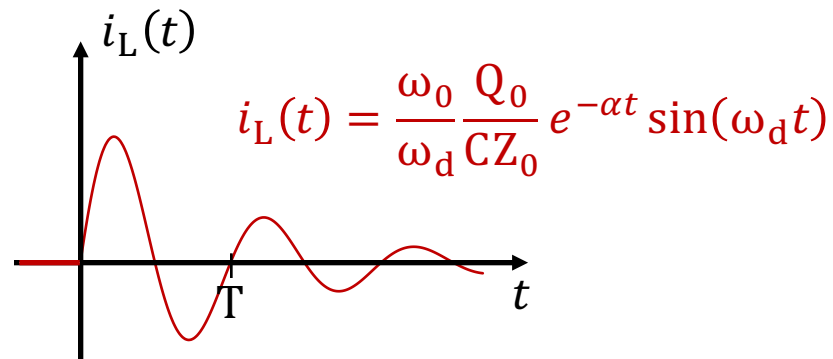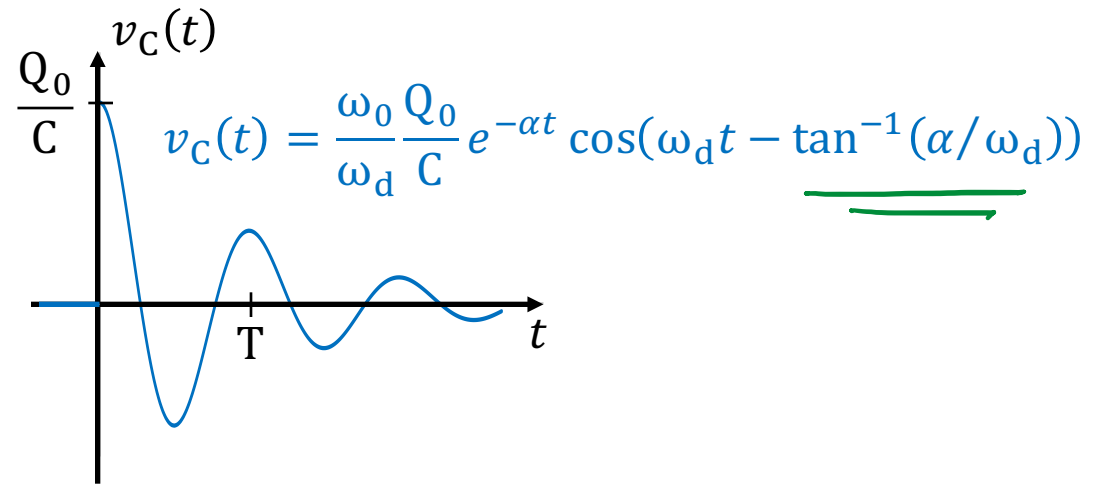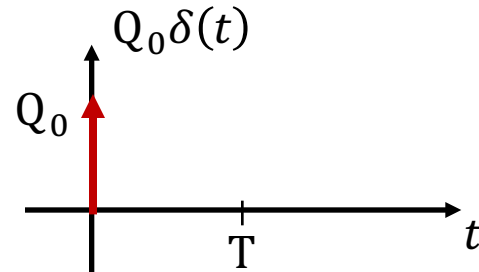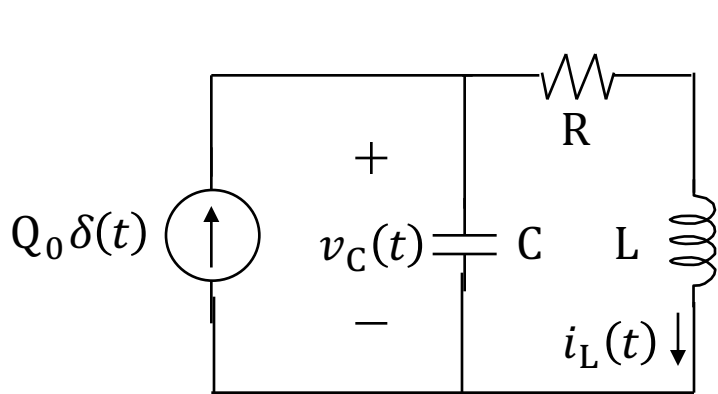Underdamped RLC – Impulse Response - Waveforms



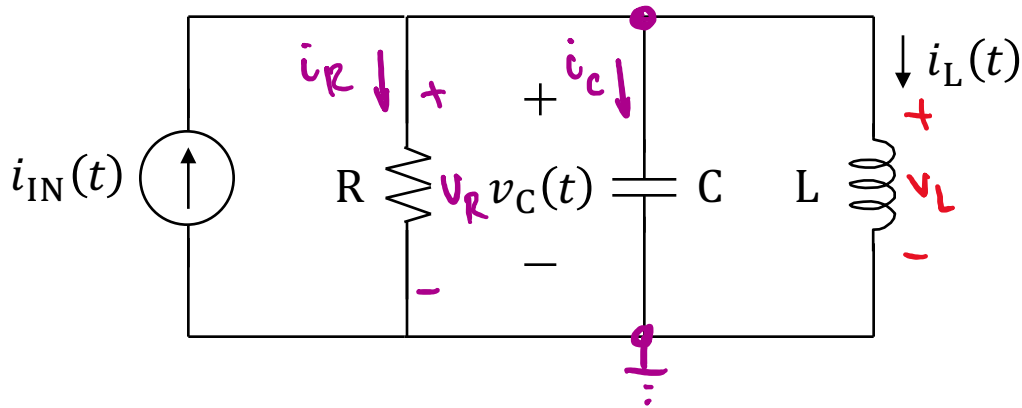Driven Parallel RLC Circuit – Differential Equation



$$i_{IN} = i_R + i_C + i_L$$

$v_L = L \frac{di_L}{dt}$

$$i_C = C \frac{dv_C}{dt} = C \frac{dv_L}{dt} = LC \frac{d^2 i_L}{dt^2}$$


$$i_R = \frac{v_R}{R} = \frac{v_L}{R} = \frac{L}{R} \frac{di_L}{dt}$$

$$\Rightarrow LC \frac{d^2 i_L}{dt^2} + \frac{L}{R} \frac{di_L}{dt} + i_L = i_{IN}$$

$$\Rightarrow \frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{i_{IN}}{LC}$$


Diff. Equ

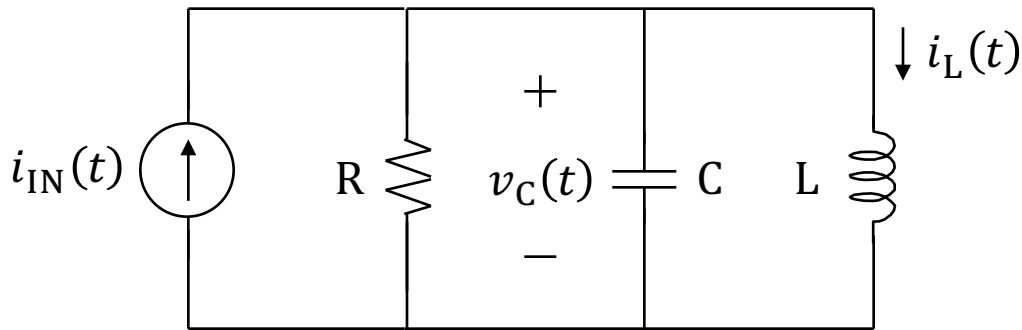Driven Parallel RLC Circuit – Step Response



$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{i_{IN}}{LC}$$

$$i_{IN}(t) = I_0 u(t)$$

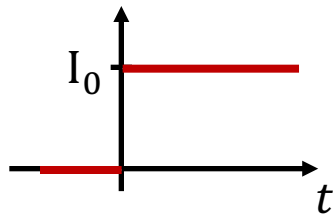


Natural Response

$$i_L(t) = i_{L,h} + i_{L,p}$$

Driven Response
(Particular Solution)

t > 0

t → ∞

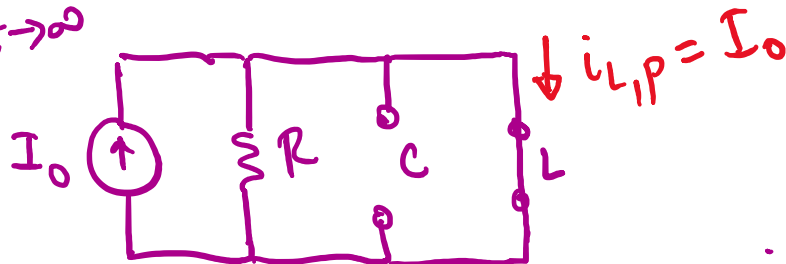

Initial Conditions


$$i_L(0^-) = 0$$

$$v_C(0^-) = 0$$

$$i_L(0^+) = i_L(0^-) = 0$$

$$v_C(0^+) = v_C(0^-) = 0$$

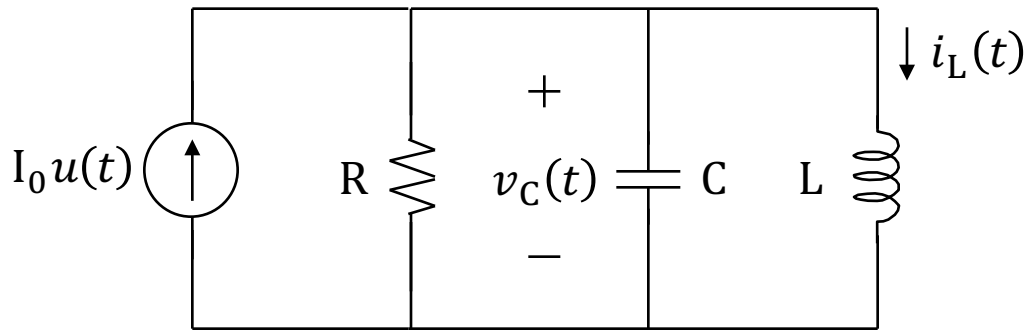Parallel RLC Circuit – Step Response (Cont.)



$$C = 1 \mu\text{F} \quad L = 1 \mu\text{H} \quad R = 5 \Omega$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10^6 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = 10^5 \text{ rad/s}$$


$\omega_0 > \alpha \Rightarrow$ Under damped

$$i_L(t) = \underline{B} e^{-\alpha t} \cos(\omega_d t + \underline{\phi})$$

$$v_C(t) = v_L(t) = L \frac{di_L}{dt} = BL \left[-\alpha e^{-\alpha t} \cos(\omega_d t + \phi) - \omega_d e^{-\alpha t} \sin(\omega_d t + \phi) \right]$$

$$\omega_d \equiv \sqrt{\omega_0^2 - \alpha^2} = 9.95 \times 10^5 \text{ rad/s}$$

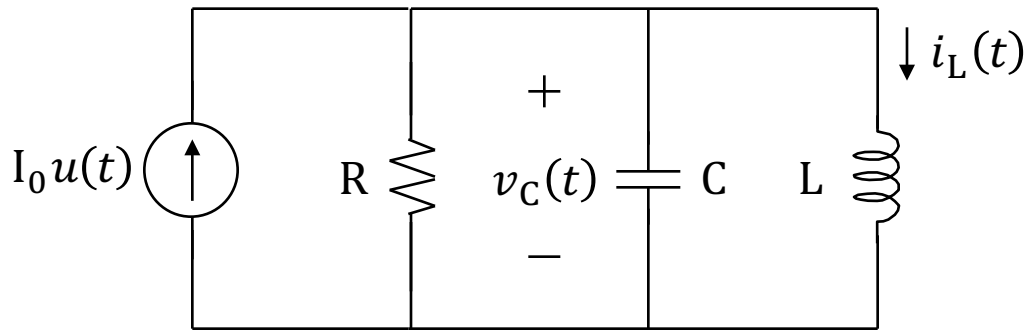Parallel RLC Circuit – Step Response (Cont.)



$$v_C(0^+) = 0$$

$$i_L(0^+) = 0$$

$$i_L(t) = e^{-\alpha t} B \cos(\omega_d t + \phi) + I_0$$

$$v_C(t) = -e^{-\alpha t} B L [\omega_d \sin(\omega_d t + \phi) + \alpha \cos(\omega_d t + \phi)]$$


$$i_L(0^+) = B \cos \phi + I_0 = 0$$

$$v_C(0^+) = -B L [\omega_d \sin \phi + \alpha \cos \phi] = 0$$

$$\Rightarrow \phi = -\tan^{-1}(\alpha/\omega_d) \Rightarrow \cos \phi = \frac{\omega_d}{\omega_0}$$

$$\Rightarrow B = -I_0 \frac{\omega_0}{\omega_d}$$

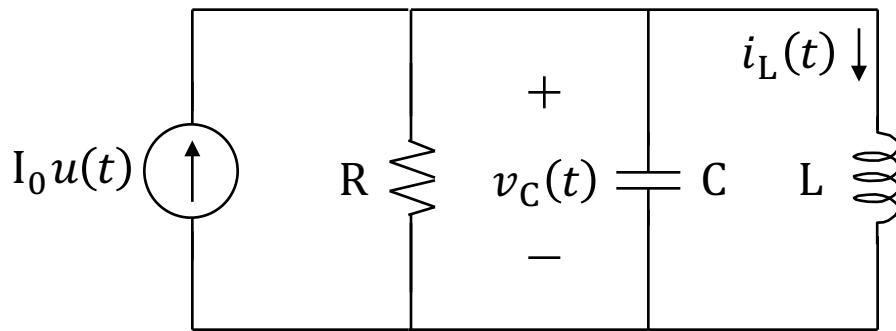
Parallel RLC Circuit – Step Response (Cont.)



$$B = -\frac{I_0 \omega_0}{\omega_d} \quad \phi = -\tan^{-1}(\alpha/\omega_d)$$

$$i_L(t) = e^{-\alpha t} B \cos(\omega_d t + \phi) + I_0$$

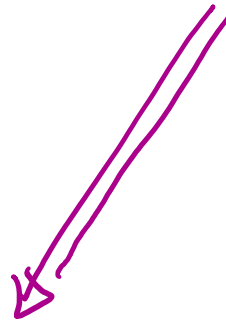
$$v_C(t) = -e^{-\alpha t} B L [\omega_d \sin(\omega_d t + \phi) + \alpha \cos(\omega_d t + \phi)]$$



$$i_L(t) = I_0 \left[1 - \frac{\omega_0}{\omega_d} e^{-\alpha t} \cos \left(\omega_d t - \tan^{-1} \left(\frac{\alpha}{\omega_d} \right) \right) \right]$$

$$v_C(t) = I_0 Z_0 \frac{\omega_0}{\omega_d} e^{-\alpha t} \sin(\omega_d t)$$

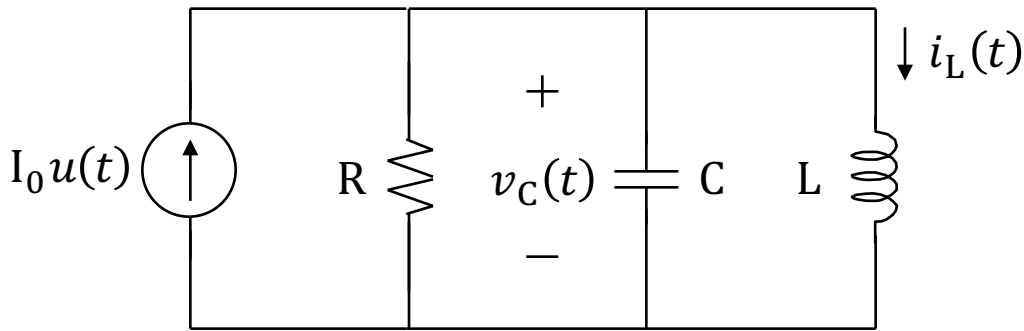Parallel RLC Circuit – Step Response – Waveforms



$$C = 1 \mu\text{F} \quad L = 1 \mu\text{H} \quad R = 5 \Omega$$

$$\omega_0 = 10^6 \text{ rad/sec}$$

$$\alpha = 10^5 \text{ rad/sec}$$

$$\omega_d = 9.95 \times 10^5 \text{ rad/s}$$

$$f_d = \frac{\omega_d}{2\pi} = 158 \text{ kHz}$$

$$Z_0 = \sqrt{\frac{L}{C}} = 1 \Omega$$

$$Q_0 = \frac{\omega_0}{2\alpha} = 5$$

