

ECE/ENGRD 2100

Introduction to Circuits for ECE


Lecture 26

Sinusoidal Steady State Analysis Using Phasors


Announcements

- Recommended Reading:
 - Textbook Chapter 9
- Upcoming due dates:
 - Homework 4 due by 11:59 pm on Monday March 25, 2019
 - Lab report 4 due by 11:59 pm on Monday April 8, 2019
- Prelim 2 on Thursday March 28, 2019 from 7:30 – 9 pm in 203 Phillips
 - Email afridi@cornell.edu if have conflict
 - Will cover material through Lecture 24
 - Prelim is closed-book and closed-notes
 - Two double-sided page formula sheet is allowed
 - Bring a calculator

Dynamic Circuit with Sinusoidal Drive

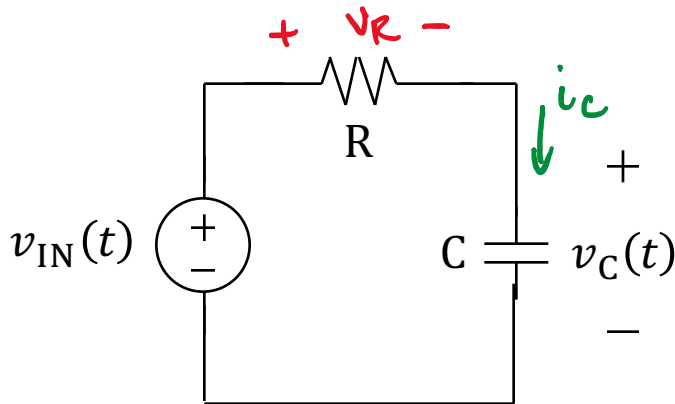
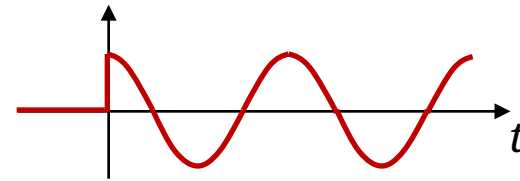
$$v_{IN}(t) = V_I \cos(\omega t + \phi_I) u(t)$$



$$v_{IN} = v_R + v_C = R i_C + v_C$$

$$i_C = C \frac{dv_C}{dt}$$

$$\Rightarrow \boxed{RC \frac{dv_C}{dt} + v_C = v_{IN}} \quad \text{Diff. Equ.}$$

$$t < 0 \Rightarrow v_C(t) = 0$$


$$\underline{t > 0} \Rightarrow v_C(t) = v_{C,h}(t) + v_{C,p}(t) = \underline{A} e^{-t/\tau} + \underline{B} \cos(\omega t + \delta)$$

$\overset{v_{C,p}(t)}{\parallel}$
 \swarrow unknowns \searrow

where $\tau = RC$

Initial Condition: $v_C(0^+) = v_C(0^-) = 0$

Particular Solution

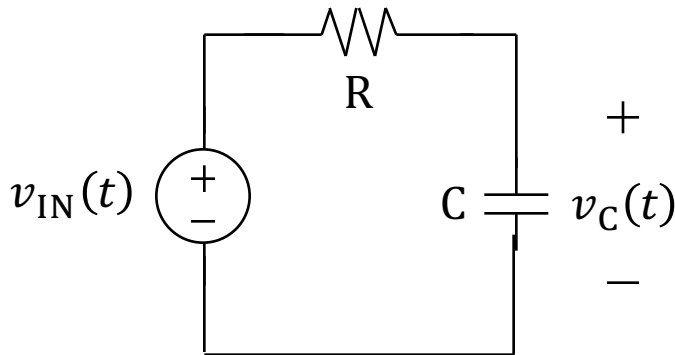

For $t > 0$:

$$RC \frac{dv_C}{dt} + v_C = V_I \cos(\omega t + \phi_I)$$

Diff. Eqn

Guess:

$$v_{C,p}(t) = B \cos(\omega t + \gamma)$$

Particular Soln

Substitute guess into differential equation:

$$\underline{-RC\omega B \sin(\omega t + \gamma) + B \cos(\omega t + \gamma) = V_I \cos(\omega t + \phi_I)}$$


True for all time

$$\begin{aligned} \Rightarrow -RC\omega B [\sin(\omega t) \cos(\gamma) + \cos(\omega t) \sin(\gamma)] + B [\cos(\omega t) \cos(\gamma) - \sin(\omega t) \sin(\gamma)] \\ = V_I [\cos(\omega t) \cos(\phi_I) - \sin(\omega t) \sin(\phi_I)] \end{aligned}$$

Match $\sin(\omega t)$ and $\cos(\omega t)$ terms:

$$\begin{cases} -RC\omega B \cos(\gamma) - B \sin(\gamma) = -V_I \sin(\phi_I) & \text{--- (A)} \\ -RC\omega B \sin(\gamma) + B \cos(\gamma) = V_I \cos(\phi_I) & \text{--- (B)} \end{cases}$$

Particular Solution (Cont.)

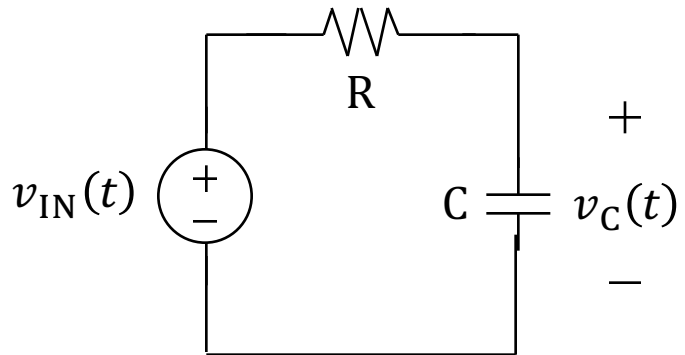

$$\left\{ \begin{array}{l} RC\omega B \cos(\gamma) + B \sin(\gamma) = V_I \sin(\phi_I) \quad \text{--- (A)} \\ -RC\omega B \sin(\gamma) + B \cos(\gamma) = V_I \cos(\phi_I) \quad \text{--- (B)} \end{array} \right.$$

Square and add:

$$\begin{aligned} & (RC\omega)^2 B^2 \cos^2(\gamma) + B^2 \sin^2(\gamma) + 2RC\omega B^2 \cos(\gamma) \sin(\gamma) \\ & + (RC\omega)^2 B^2 \sin^2(\gamma) + B^2 \cos^2(\gamma) - 2RC\omega B^2 \cos(\gamma) \sin(\gamma) \\ & = V_I^2 \sin^2(\phi_I) + V_I^2 \cos^2(\phi_I) \end{aligned}$$


$$\Rightarrow (RC\omega)^2 B^2 [\underbrace{\cos^2(\gamma) + \sin^2(\gamma)}_{=1}] + B^2 [\underbrace{\cos^2(\gamma) + \sin^2(\gamma)}_{=1}] = V_I^2 [\underbrace{\sin^2(\phi_I) + \cos^2(\phi_I)}_{=1}]$$

$$\Rightarrow \underline{(RC\omega)^2 B^2 + B^2 = V_I^2}$$



$$B = \frac{V_I}{\sqrt{1 + (RC\omega)^2}}$$

Particular Solution (Cont.)

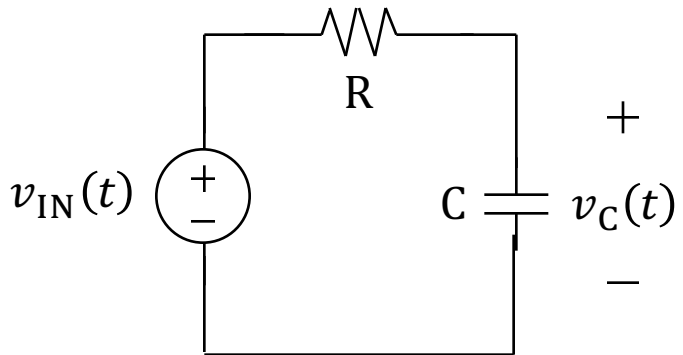


$$RC\omega B \cos(\gamma) + B \sin(\gamma) = V_I \sin(\phi_I) \quad \leftarrow$$

$$B = \frac{V_I}{\sqrt{1 + (RC\omega)^2}}$$

$$\Rightarrow \frac{RC\omega B}{\sqrt{1 + (RC\omega)^2}} \cos(\gamma) + \frac{B}{\sqrt{1 + (RC\omega)^2}} \sin(\gamma) = \frac{V_I}{\sqrt{1 + (RC\omega)^2}} \sin(\phi_I)$$

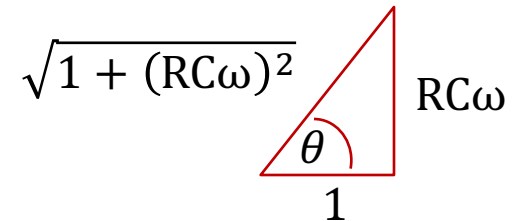
$$\Rightarrow B \sin(\theta) \cos(\gamma) + B \cos(\theta) \sin(\gamma) = B \sin(\phi_I)$$



$$\Rightarrow \sin(\theta + \gamma) = \sin(\phi_I) \quad \text{where } \theta = \tan^{-1}(RC\omega)$$

$$\Rightarrow \theta + \gamma = \phi_I \quad \Rightarrow \gamma = \phi_I - \tan^{-1}(RC\omega)$$

Total Solution

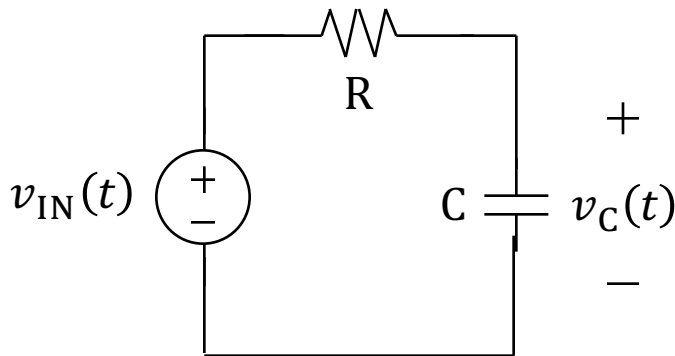

$$v_C(t) = v_{C,h}(t) + v_{C,p}(t)$$

$$v_{C,h}(t) = Ae^{-t/\tau} \quad \text{where } \tau = RC$$

$$v_{C,p}(t) = \frac{V_I}{\sqrt{1 + (RC\omega)^2}} \cos(\omega t + \phi_I - \tan^{-1}(RC\omega))$$

$$\Rightarrow v_C(t) = Ae^{-t/\tau} + \frac{V_I}{\sqrt{1 + (RC\omega)^2}} \cos(\omega t + \phi_I - \tan^{-1}(RC\omega))$$


Apply initial condition:

$$\Rightarrow v_C(0^+) = A + \frac{V_I}{\sqrt{1 + (RC\omega)^2}} \cos(\phi_I - \tan^{-1}(RC\omega)) = 0$$


$$\Rightarrow A = \frac{-V_I}{\sqrt{1 + (RC\omega)^2}} \cos(\phi_I - \tan^{-1}(RC\omega))$$

$$\Rightarrow v_C(t) = \frac{-V_I}{\sqrt{1 + (RC\omega)^2}} \cos(\phi_I - \tan^{-1}(RC\omega)) e^{-t/\tau} + \frac{V_I}{\sqrt{1 + (RC\omega)^2}} \cos(\omega t + \phi_I - \tan^{-1}(RC\omega))$$

Sinusoidal Steady State

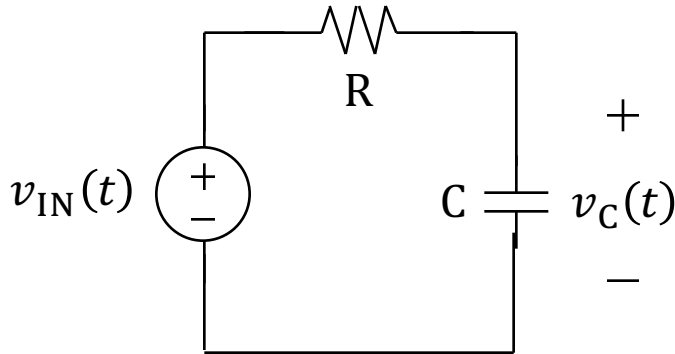
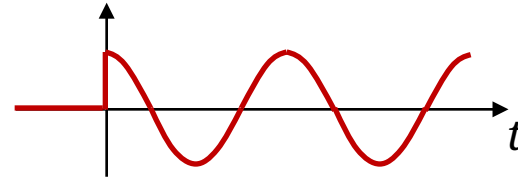
$$v_{IN}(t) = V_I \cos(\omega t + \phi_I) u(t)$$



For $t > 0$:

$$v_C(t) = \frac{-V_I}{\sqrt{1 + (RC\omega)^2}} \cos(\phi_I - \tan^{-1}(RC\omega)) e^{-t/\tau}$$

goes to zero
as $t \rightarrow \infty$
(in 5τ 's)

$$+ \frac{V_I}{\sqrt{1 + (RC\omega)^2}} \cos(\omega t + \phi_I - \tan^{-1}(RC\omega))$$

Stays for $t \rightarrow \infty$
Sinusoidal Steady State

Focus on this
↓

Review of Complex Numbers in Polar Form

$$z = a + jb$$

$$j \equiv \sqrt{-1}$$

Imaginary Axis


$$a = |z| \cos(\angle z)$$

$$b = |z| \sin(\angle z)$$

$$z = |z| (\cos(\angle z) + j \sin(\angle z))$$

$$\text{Euler's Formula: } e^{j\theta} = \cos \theta + j \sin \theta$$

$$z = |z| e^{j\angle z}$$

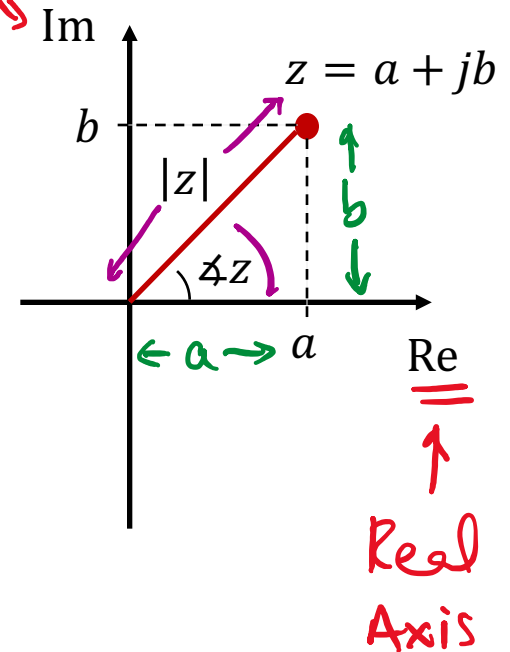

$$|z| = \sqrt{a^2 + b^2}$$

$$\angle z = \tan^{-1}\left(\frac{b}{a}\right)$$


$$z = \sqrt{a^2 + b^2} e^{j \tan^{-1}(b/a)}$$

Polar Form Complex Number Useful Relationships

$$z = a + jb = \sqrt{a^2 + b^2} e^{j \tan^{-1}(b/a)}$$

$$\operatorname{Re}\{z\} = \operatorname{Re}\{a + jb\} = a \quad \leftarrow \text{Real part of } z$$
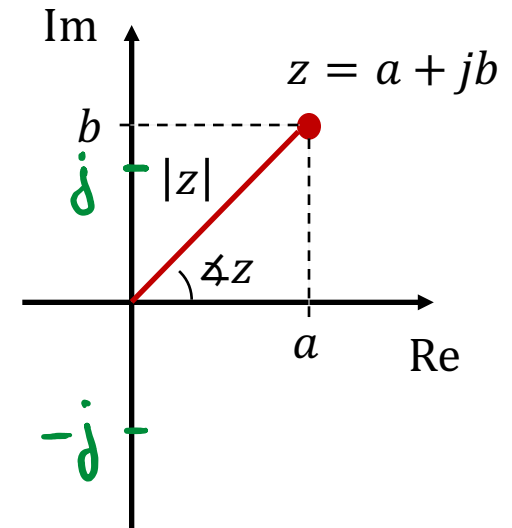
$$\operatorname{Im}\{z\} = \operatorname{Im}\{a + jb\} = b \quad \leftarrow \text{Imaginary part of } z$$



$$z_1 = |z_1| e^{j\angle z_1}$$

$$z_2 = |z_2| e^{j\angle z_2}$$

$$z_1 z_2 = |z_1| |z_2| e^{j(\angle z_1 + \angle z_2)}$$

$$\frac{z_1}{z_2} = \frac{|z_1|}{|z_2|} e^{j(\angle z_1 - \angle z_2)}$$

$$(z_1)^n = |z_1|^n e^{jn\angle z_1}$$

$$e^{j\frac{\pi}{2}} = j$$


$$e^{-j\frac{\pi}{2}} = -j$$

Sinusoid as Complex Number in Polar Form

$$\underline{v_X(t) = V_X \cos(\omega t + \phi_X)}$$

Using Euler's Formula: $e^{j\theta} = \underbrace{\cos(\theta)}_{\text{Real part}} + j \underbrace{\sin(\theta)}_{\text{Imaginary part}}$
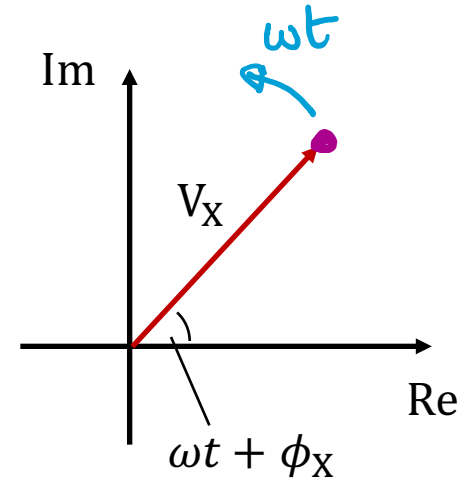
$$\underline{V_X e^{j(\omega t + \phi_X)} = V_X \cos(\omega t + \phi_X) + j V_X \sin(\omega t + \phi_X)}$$



$$\text{Re}\{V_X e^{j(\omega t + \phi_X)}\} = V_X \cos(\omega t + \phi_X)$$

Rotating Phasor

$$\underline{V_X \cos(\omega t + \phi_X)} = \text{Re}\{\underline{V_X e^{j(\omega t + \phi_X)}}\} = \text{Re}\{\underbrace{V_X e^{j\phi_X}}_{\hat{V}_X} e^{j\omega t}\} = \text{Re}\{\hat{V}_X e^{j\omega t}\}$$

$\hat{V}_X \leftarrow$ Phasor


Phasor

Phasor

$$\hat{V}_X = V_X e^{j\phi_X}$$

Phasor has magnitude and phase
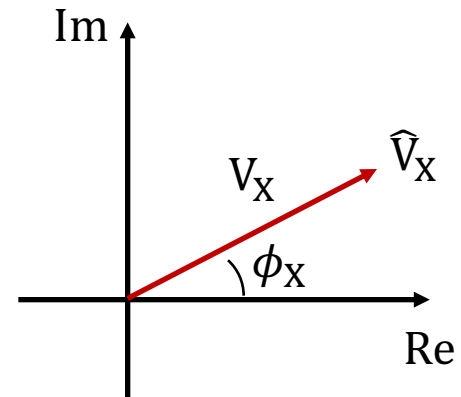
$$\text{Alternate notation } \hat{V}_X = V_X \angle \phi_X$$



Rotating Phasor (Complex Exponential)

$$\hat{V}_X e^{j\omega t} = V_X e^{j\phi_X} e^{j\omega t}$$

Using Phasors to Solve Circuits in Sinusoidal Steady State




Drive: $v_{IN}(t) = V_I \cos(\omega t + \phi_I)$ ←

$$V_I e^{j(\omega t + \phi_I)} = \underbrace{V_I \cos(\omega t + \phi_I)}_{"a"} + j \underbrace{V_I \sin(\omega t + \phi_I)}_{"b"} = \underline{a + jb}$$

$$a = V_I \cos(\omega t + \phi_I) = \text{Re}\{V_I e^{j(\omega t + \phi_I)}\}$$

$$b = V_I \sin(\omega t + \phi_I) = \text{Im}\{V_I e^{j(\omega t + \phi_I)}\}$$
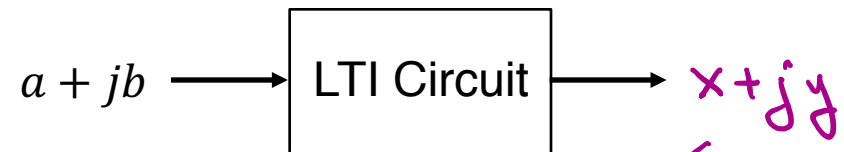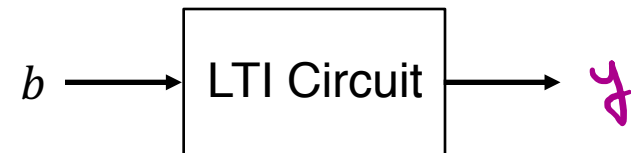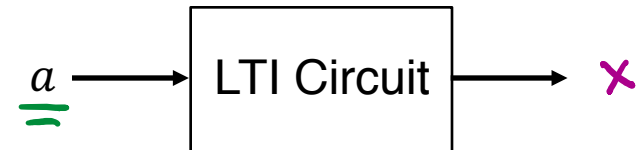
$$a + jb = V_I e^{j(\omega t + \phi_I)}$$



$$x = \text{Re}\{x + jy\} =$$


LTI ≡ Linear Time-Invariant

Phasor Analysis Method

1. Express drive as real part of a rotating phasor (phasor $\times e^{j\omega t}$)

$$v_{IN}(t) = V_I \cos(\omega t + \phi_I) = \operatorname{Re}\{V_I e^{j(\omega t + \phi_I)}\} = \operatorname{Re}\{V_I e^{j\phi_I} e^{j\omega t}\} = \operatorname{Re}\{\underline{\underline{\hat{V}_I e^{j\omega t}}}\}$$

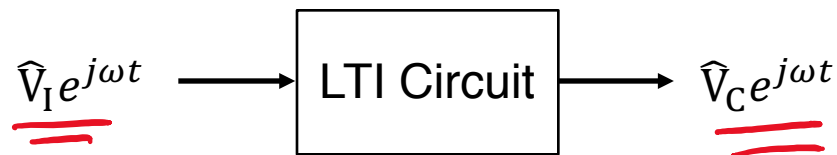
2. Calculate response to the rotating phasor



3. Take real part of the response to the rotating phasor

$$v_C(t) = \operatorname{Re}\{\underline{\underline{\hat{V}_C e^{j\omega t}}}\} = \operatorname{Re}\{V_C e^{j\phi_C} e^{j\omega t}\} = \underline{\underline{V_C \cos(\omega t + \phi_C)}}$$

Phasor Analysis Example

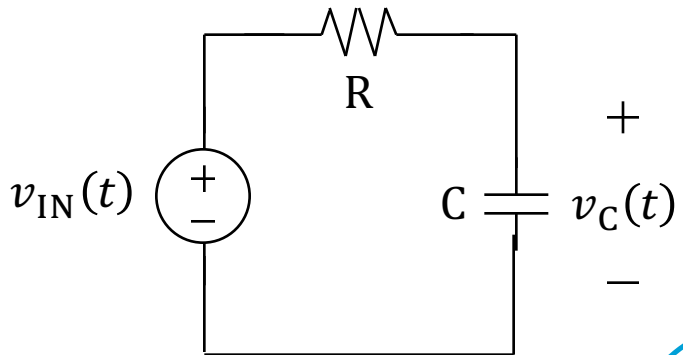

$$v_{IN}(t) = V_I \cos(\omega t + \phi_I) u(t)$$

$$RC \frac{dv_C}{dt} + v_C = v_{IN}$$

$t > 0$

$$\tilde{v}_{IN}(t) = V_I e^{j(\omega t + \phi_I)}$$


Particular Solu: $\tilde{v}_{C,p}(t) = V_C e^{j(\omega t + \phi_{V_C})}$
 $= \hat{V}_C e^{j\omega t}$

$$\hat{V}_C = V_C e^{j\phi_{V_C}}$$

~~$$RC \hat{V}_C j\omega e^{j\omega t} + \hat{V}_C e^{j\omega t} = V_I e^{j\phi_I} e^{j\omega t}$$~~

$$\hat{V}_C = \frac{V_I e^{j\phi_I}}{1 + jRC\omega}$$

Phasor Analysis Example (Cont.)

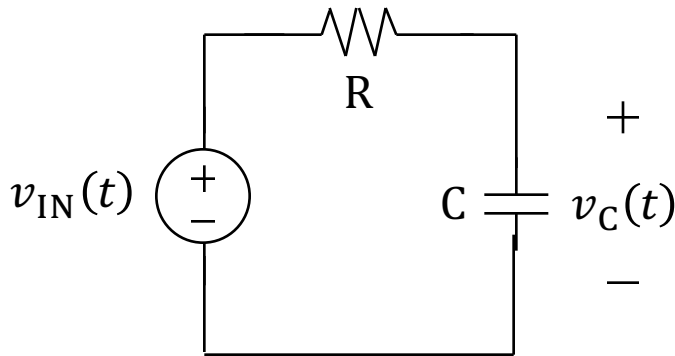

$$\hat{V}_C = \frac{V_I e^{j\phi_I}}{1 + jRC\omega}$$

$$\hat{V}_C = \frac{V_I e^{j\phi_I}}{\sqrt{1 + (RC\omega)^2} e^{j \tan^{-1}(RC\omega)}}$$

$$\hat{V}_C = \frac{V_I}{\sqrt{1 + (RC\omega)^2}} e^{j(\phi_I - \tan^{-1}(RC\omega))}$$

Particular Solu

$$v_C(t) = \text{Re} \left\{ \hat{V}_C e^{j\omega t} \right\} = \frac{V_I}{\sqrt{1 + (RC\omega)^2}} \cos(\omega t + \phi_I - \tan^{-1}(RC\omega))$$