

ECE/ENGRD 2100

Introduction to Circuits for ECE

Lecture 27

Sinusoidal Steady State Analysis Using Impedances

Announcements

- Recommended Reading:
 - Textbook Chapter 9
- Upcoming due dates:
 - Lab report 4 due by 11:59 pm on Monday April 8, 2019
 - Prelab 5 due by 12:20 pm on Tuesday April 9, 2019
 - Homework 5 due by 11:59 pm on Friday April 12, 2019
 - Lab report 5 due by 11:59 pm on Friday April 19, 2019
- Prelim 2 on Thursday March 28, 2019 from 7:30 – 9 pm in 203 Phillips
 - Make up exams today (Wednesday March 27):
 - 3:30 – 5 pm in 354 Duffield
 - 5 – 6:30 pm in 354 Duffield
 - Will cover material through Lecture 24
 - Prelim is closed-book and closed-notes
 - Two double-sided page formula sheet is allowed
 - Bring a calculator


Phasors

Phasor

$$\hat{V}_X = V_X e^{j\phi_X}$$


Phasor has magnitude and phase

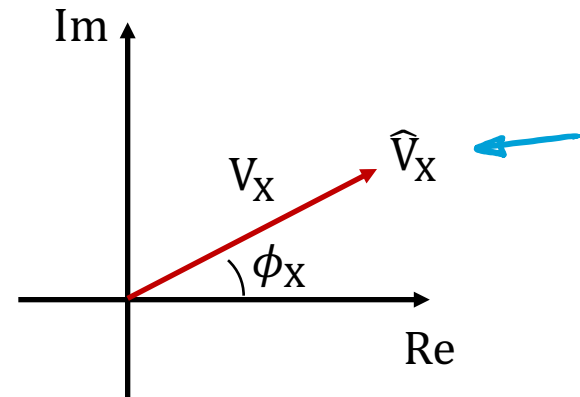Alternate notation: $\hat{V}_X = V_X \angle \phi_X$



Rotating Phasor (Complex Exponential)
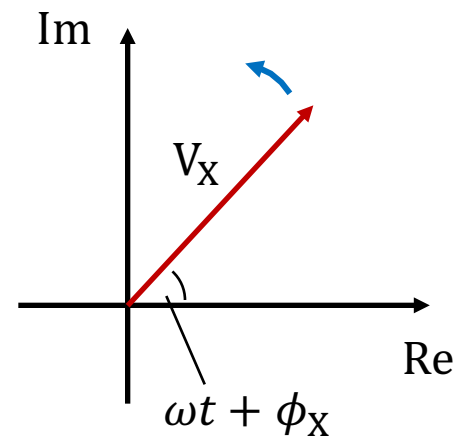
$$\hat{V}_X e^{j\omega t} = V_X e^{j\phi_X} e^{j\omega t}$$




Sinusoidal Steady State Analysis using Phasors

1. Express drive as real part of a rotating phasor (phasor $\times e^{j\omega t}$)

$$v_{\text{IN}}(t) = V_{\text{I}} \cos(\omega t + \phi_{\text{I}}) = \text{Re}\{V_{\text{I}}e^{j(\omega t + \phi_{\text{I}})}\} = \text{Re}\{V_{\text{I}}e^{j\phi_{\text{I}}}e^{j\omega t}\} = \text{Re}\{\widehat{V}_{\text{I}}e^{j\omega t}\}$$

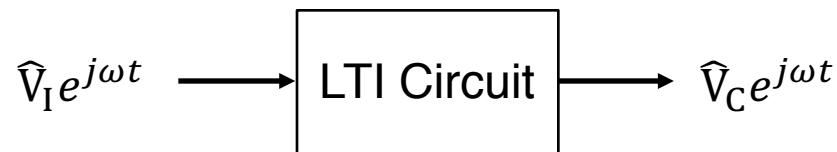
2. Calculate response to the rotating phasor



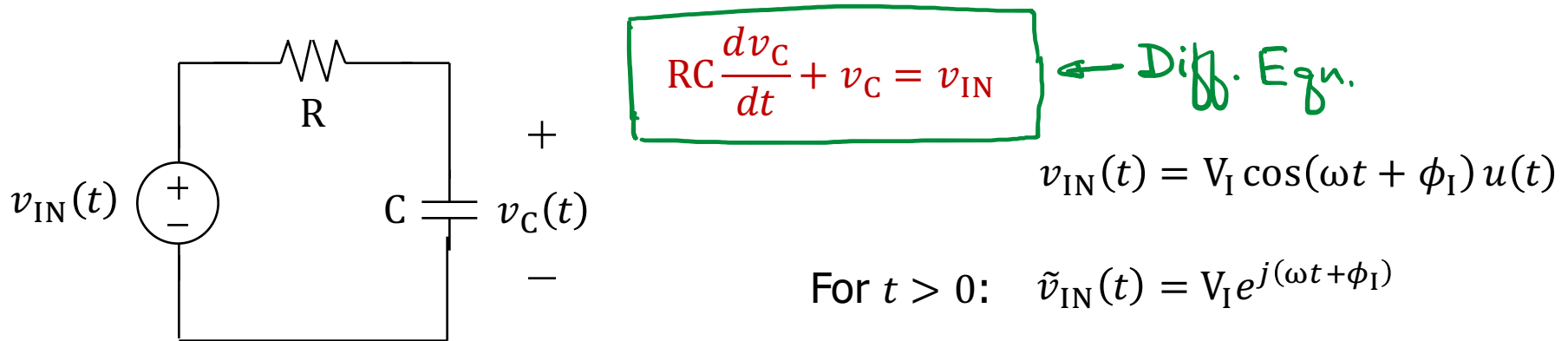3. Take real part of the response to the rotating phasor

$$v_{\text{C}}(t) = \text{Re}\{\widehat{V}_{\text{C}}e^{j\omega t}\} = \text{Re}\{V_{\text{C}}e^{j\phi_{\text{C}}}e^{j\omega t}\} = V_{\text{C}} \cos(\omega t + \phi_{\text{C}})$$

Phasor Analysis using Circuit's Differential Equation



Sinusoidal Steady State Solution (Particular Solution): $\tilde{v}_{C,p}(t) = \hat{V}_C e^{j\omega t}$


$$RC \frac{d\tilde{v}_{C,p}}{dt} + \tilde{v}_{C,p} = \tilde{v}_{IN} \Rightarrow RCj\omega \hat{V}_C e^{j\omega t} + \hat{V}_C e^{j\omega t} = V_I e^{j\phi_I} e^{j\omega t} \Rightarrow \hat{V}_C = \frac{V_I e^{j\phi_I}}{1 + jRC\omega}$$

$$\Rightarrow \hat{V}_C = \frac{V_I e^{j\phi_I}}{\sqrt{1 + (RC\omega)^2} e^{j \tan^{-1}(RC\omega)}} \Rightarrow \hat{V}_C = \frac{V_I}{\sqrt{1 + (RC\omega)^2}} e^{j(\phi_I - \tan^{-1}(RC\omega))}$$

$$\Rightarrow v_{C,p}(t) = \text{Re}\{\hat{V}_C e^{j\omega t}\} = \text{Re}\left\{ \frac{V_I}{\sqrt{1 + (RC\omega)^2}} e^{j(\omega t + \phi_I - \tan^{-1}(RC\omega))} \right\}$$

$$\Rightarrow v_{C,p}(t) = \frac{V_I}{\sqrt{1 + (RC\omega)^2}} \cos(\omega t + \phi_I - \tan^{-1}(RC\omega))$$

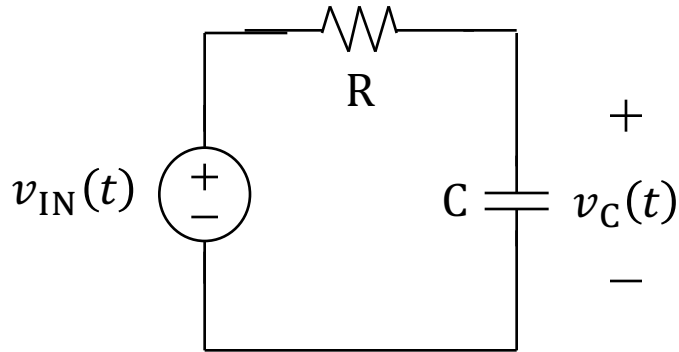Sinusoidal Steady State Analysis – Alternate Approach



⇓ Diff. Egn.

$$RC \frac{dv_C}{dt} + v_C = v_{IN}$$

⇓ Applied Phasor


$$\tilde{v}_{IN}(t) = V_I e^{j(\omega t + \phi_I)}$$

⇓ Phasor Equation


Phasor Response

⇓ Real World

Phasor World

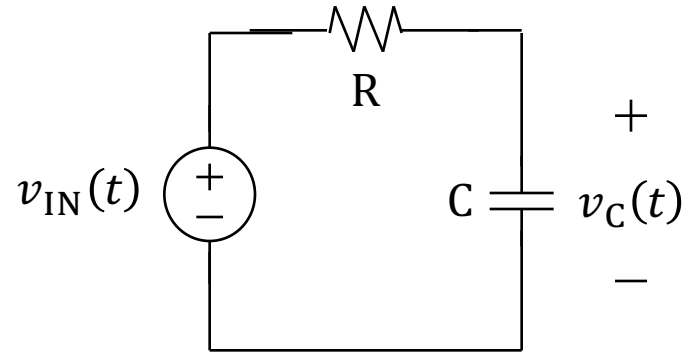

⇓

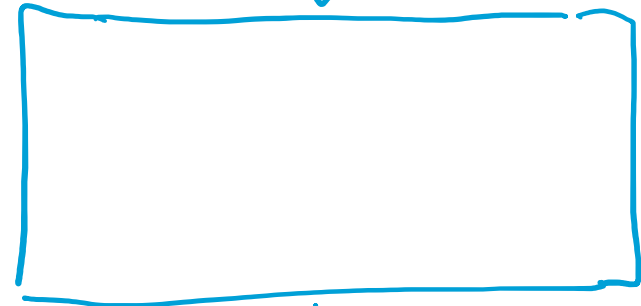


Phasor world

⇓ Egn

Solve

Phasor Response of Components – Impedance

Resistor

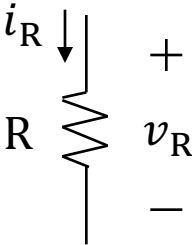


$v_R = Ri_R$

$i_R(t) \rightarrow \hat{I}_R e^{j\omega t} = I_R e^{j\phi_{I_R}} e^{j\omega t}$
 $v_R(t) \rightarrow \hat{V}_R e^{j\omega t} = V_R e^{j\phi_{V_R}} e^{j\omega t}$

~~$\hat{V}_R e^{j\omega t} = R \hat{I}_R e^{j\omega t}$~~ $\Rightarrow \hat{V}_R = R \hat{I}_R \Rightarrow$ Define Impedance
 $\underline{Z}_R \equiv \frac{\hat{V}_R}{\hat{I}_R} = R$

Inductor

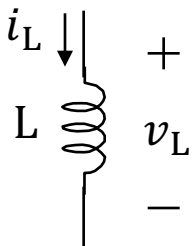


$v_L = L \frac{di_L}{dt}$

$i_L(t) \rightarrow \hat{I}_L e^{j\omega t}$
 $v_L(t) \rightarrow \hat{V}_L e^{j\omega t}$

~~$\hat{V}_L e^{j\omega t} = L j\omega \hat{I}_L e^{j\omega t}$~~ $\Rightarrow \hat{V}_L = j\omega L \hat{I}_L \Rightarrow \underline{Z}_L \equiv \frac{\hat{V}_L}{\hat{I}_L} = j\omega L$

Capacitor

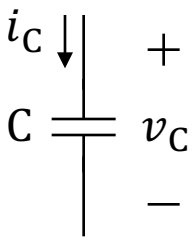


$i_C = C \frac{dv_C}{dt}$

$v_C(t) \rightarrow \hat{V}_C e^{j\omega t}$
 $i_C(t) \rightarrow \hat{I}_C e^{j\omega t}$

~~$\hat{I}_C e^{j\omega t} = C j\omega \hat{V}_C e^{j\omega t}$~~ $\Rightarrow \hat{V}_C = \frac{1}{j\omega C} \hat{I}_C \Rightarrow \underline{Z}_C \equiv \frac{\hat{V}_C}{\hat{I}_C} = \frac{1}{j\omega C}$

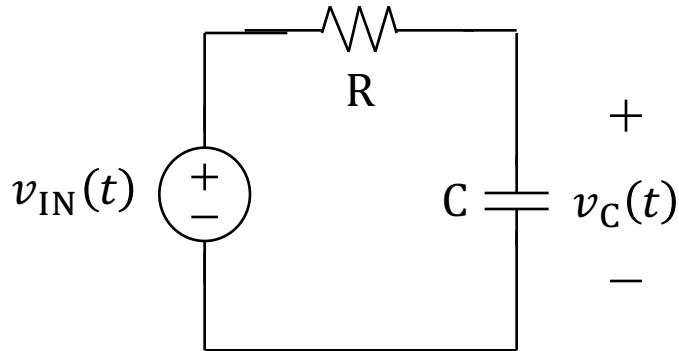Sinusoidal Steady State Analysis – Alternate Approach



⇓ Diff. Egn.

$$RC \frac{dv_C}{dt} + v_C = v_{IN}$$

⇓ Applied Phasor

$$\tilde{v}_{IN}(t) = V_I e^{j(\omega t + \phi_I)}$$


⇓ Phasor Equation

Phasor Response


⇓

Real World

Phasor World

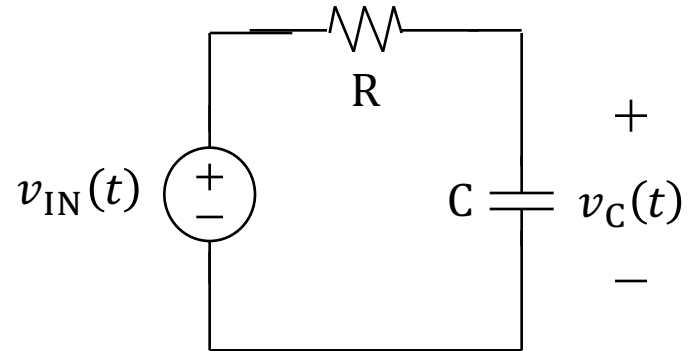

$$\hat{V}_R = Z_R \hat{I}_R$$

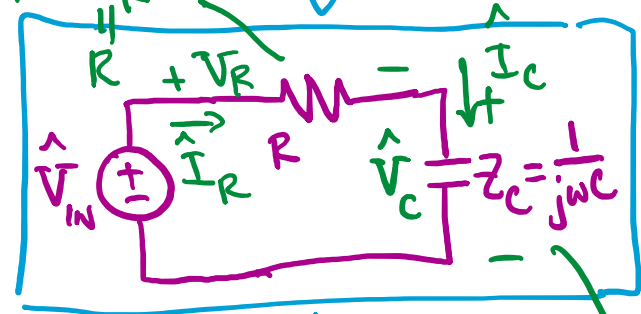

Phasor world

⇓ Egn

Solve

$$\hat{V}_C = Z_C \hat{I}_C$$

Impedance Summary



- In phasor (frequency) domain, for linear R, L and C, phasor voltage \hat{V} and phasor current \hat{I} are related by algebraic expressions
 - In time domain, for linear L and C, voltage $v(t)$ and current $i(t)$ related by differentials

- Impedance $Z \equiv \frac{\hat{V}}{\hat{I}}$
 - Impedance has units of ohms [Ω]
 - In general, Z is a complex number: $Z = R + jX = |Z|e^{j\angle Z}$
 - R is "resistance"; X is called "reactance"
 - Inverse of Impedance is called "admittance" $Y = \frac{1}{Z} = G + jB$
 - G is "conductance"; B is called "susceptance"

- Impedances can be treated the same way resistances are treated

Combining Impedance

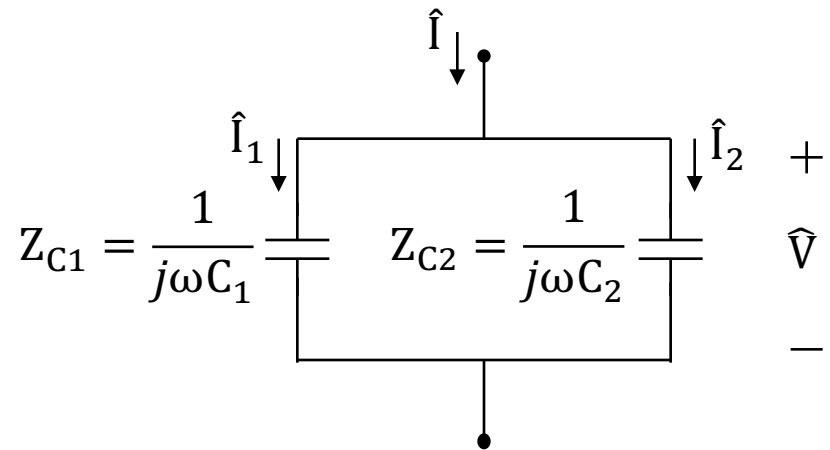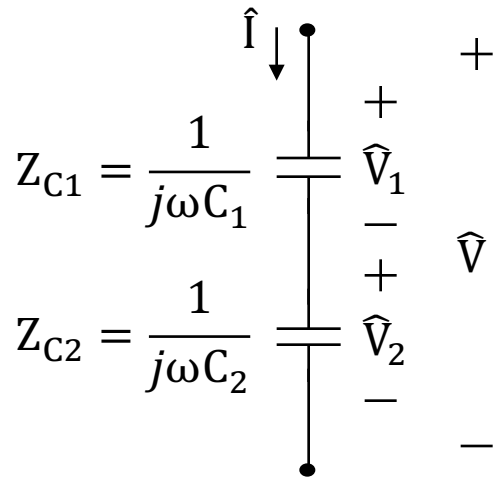- Impedances follow the same combination rules as resistors
 - Impedances in series add
 - Admittances in parallel add



$$\hat{V} = \hat{V}_1 + \hat{V}_2 = Z_{C1} \hat{I} + Z_{C2} \hat{I}$$


$$Z_{eff} = Z_{TH} \equiv \frac{\hat{V}}{\hat{I}} = Z_{C1} + Z_{C2}$$

$$\hat{I} = \hat{I}_1 + \hat{I}_2 = \frac{\hat{V}}{Z_{C1}} + \frac{\hat{V}}{Z_{C2}}$$

$$\Rightarrow \frac{1}{Z_{eff}} = \frac{\hat{I}}{\hat{V}} = \frac{1}{Z_{C1}} + \frac{1}{Z_{C2}}$$

Voltage and Current Division with Impedances

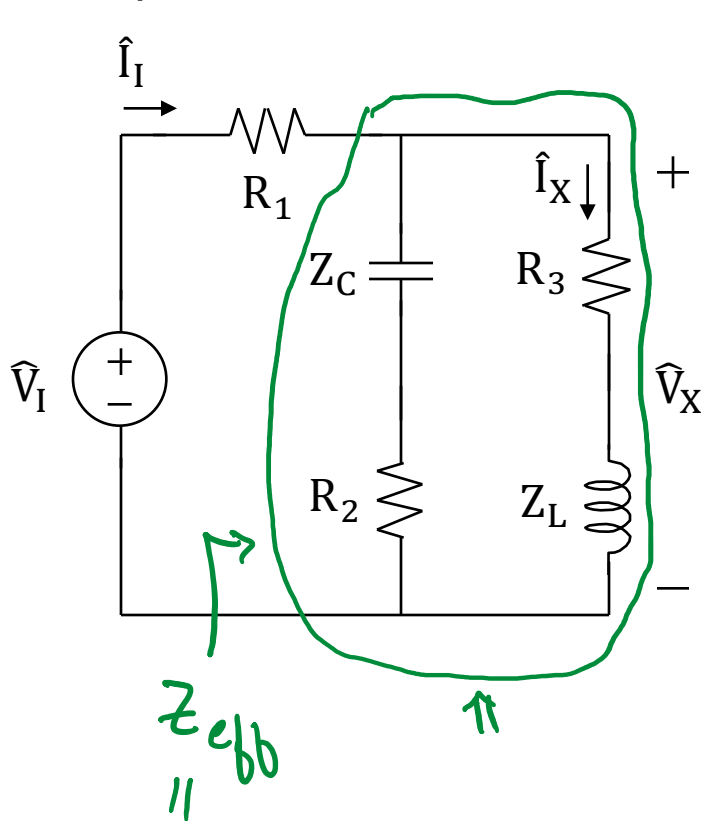- Impedances follow the same voltage and current division rules as resistors






$$\hat{V}_x = \frac{(Z_C + R_2) \parallel (R_3 + Z_L)}{R_1 + (Z_C + R_2) \parallel (R_3 + Z_L)} \cdot \hat{V}_I$$

$$v_x(t) = \text{Re} \{ \hat{V}_x e^{j\omega t} \}$$

Z_{TH} ← Thevenin Impedance

Can also create Thevenin and Norton Equivalents in frequency domain

Impedance – Dependence on Frequency

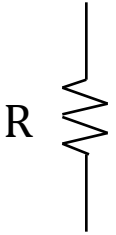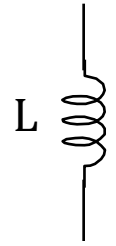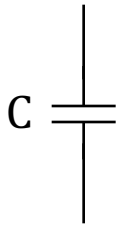	$\omega = 0$	$\omega \rightarrow \infty$
<p>Resistor</p>  <p>$Z_R = R$</p>	<p>$Z_R = R$</p>	<p>$Z_R = R$</p>
<p>Inductor</p>  <p>$Z_L = j\omega L$</p>	<p>No change</p> <p>$Z_L = 0$</p>	<p>Fast Change</p> <p>$Z_L \rightarrow \infty$</p>
<p>Capacitor</p>  <p>$Z_C = \frac{1}{j\omega C}$</p>	<p>No change</p> <p>$Z_C \rightarrow \infty$</p>	<p>Fast Change</p> <p>$Z_C = 0$</p>

Sinusoidal Steady State Analysis using Impedances

1. Create impedance (frequency domain) model of the circuit

- Replace sinusoidal sources by the equivalent phasor

$$v_{IN}(t) = V_I \cos(\omega t + \phi_I) \rightarrow V_I e^{j\phi_I}$$

- Replace circuit elements by their impedances models

$$R \rightarrow R$$

$$L \rightarrow j\omega L$$

$$C \rightarrow \frac{1}{j\omega C}$$


2. Solve frequency domain circuit (with algebraic constitutive relationships) for phasors of interest

Solve it like a resistive circuit

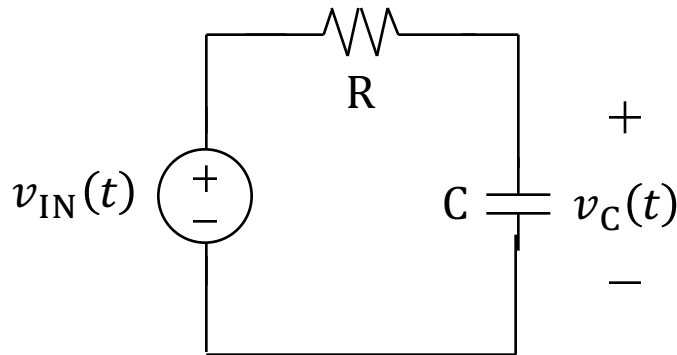
3. Convert phasors of interest into time domain by multiplying by $e^{j\omega t}$ and taking the real part

$$v_C(t) = \text{Re} \{ \widehat{V}_C e^{j\omega t} \} = \text{Re} \{ V_C e^{j\phi_C} e^{j\omega t} \} = V_C \cos(\omega t + \phi_C)$$

Circuit Analysis using Impedances – Example 1


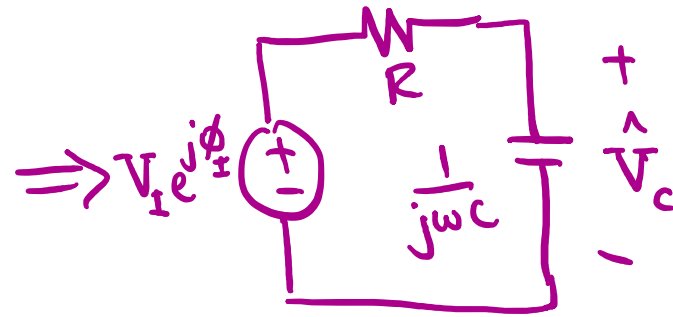
$$v_{IN}(t) = V_I \cos(\omega t + \phi_I) u(t)$$



$$\hat{V}_C = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \cdot V_I e^{j\phi_I}$$

$$\Rightarrow \hat{V}_C = \frac{V_I e^{j\phi_I}}{1 + jRC\omega} = \frac{V_I e^{j\phi_I}}{\sqrt{1 + (RC\omega)^2} e^{j \tan^{-1}(RC\omega)}} = \frac{V_I e^{j(\phi_I - \tan^{-1}(RC\omega))}}{\sqrt{1 + (RC\omega)^2}}$$

$$v_C(t) = \text{Re}\{ \hat{V}_C e^{j\omega t} \} = \frac{V_I}{\sqrt{1 + (RC\omega)^2}} \cos(\omega t + \phi_I - \tan^{-1}(RC\omega))$$