

ECE/ENGRD 2100

Introduction to Circuits for ECE

Lecture 29

Magnitude and Phase versus Frequency Plots

Announcements

- Recommended Reading:
 - Textbook Chapter 9 and Chapter 14
- Upcoming due dates:
 - Lab report 4 due by 11:59 pm on Monday April 8, 2019
 - Prelab 5 due by 11:59 pm on Monday April 15, 2019
 - Homework 5 due by 11:59 pm on Wednesday April 17, 2019
 - Lab report 5 due by 11:59 pm on Friday April 19, 2019

Sinusoidal Steady State Analysis using Impedances

1. Create impedance (frequency domain) model of the circuit 

– Replace sinusoidal sources by the equivalent phasor


$$v_{IN}(t) = V_I \cos(\omega t + \phi_I) \rightarrow V_I e^{j\phi_I} \quad \leftarrow$$

– Replace circuit elements by their impedances models



$$R \rightarrow R \qquad L \rightarrow j\omega L \qquad C \rightarrow \frac{1}{j\omega C}$$

2. Solve frequency domain circuit (with algebraic constitutive relationships) for phasors of interest


– Solve frequency domain circuit like a resistive circuit

 \hat{V}_C

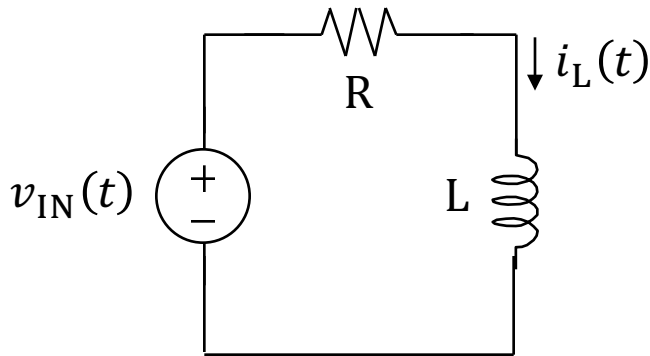3. Convert phasors of interest into time domain by multiplying by $e^{j\omega t}$ and taking the real part


$$v_C(t) = \text{Re} \{ \hat{V}_C e^{j\omega t} \} = \text{Re} \{ V_C e^{j\phi_C} e^{j\omega t} \} = \underline{V_C} \cos(\omega t + \underline{\phi_C})$$


Circuit Analysis using Impedances – Example 2



$$v_{IN}(t) = V_I \cos(\omega t + \phi_I)$$

Freq.
Domain

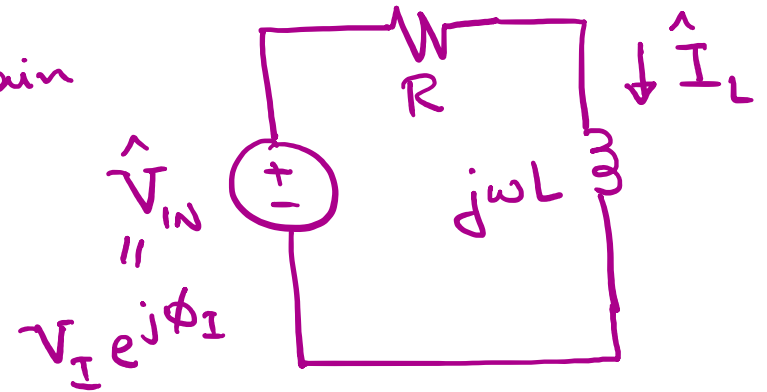


$$\hat{I}_L = \frac{\hat{V}_{IN}}{R + j\omega L} = \frac{V_I e^{j\phi_I}}{\sqrt{R^2 + (\omega L)^2}} e^{-j \tan^{-1}(\frac{\omega L}{R})}$$

$$i_L(t) = \text{Re} \left\{ \hat{I}_L e^{j\omega t} \right\} = \text{Re} \left\{ \frac{V_I e^{j(\omega t + \phi_I - \tan^{-1}(\frac{\omega L}{R}))}}{\sqrt{R^2 + (\omega L)^2}} \right\}$$

$$i_L(t) = \frac{V_I}{\sqrt{R^2 + (\omega L)^2}} \cos(\omega t + \phi_I - \tan^{-1}(\frac{\omega L}{R}))$$

Circuit Behavior in Frequency Domain

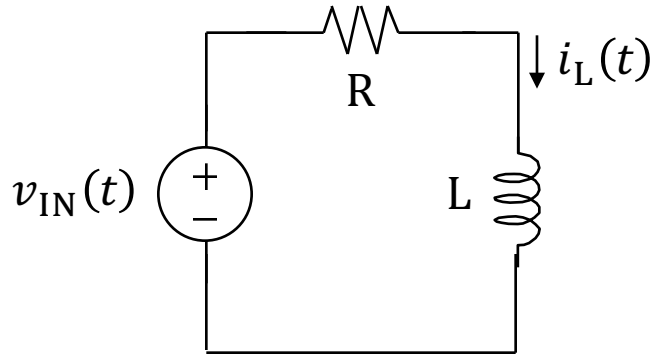


$$\hat{I}_L = \frac{\hat{V}_{IN} e^{-j \tan^{-1}(\omega L/R)}}{\sqrt{R^2 + (\omega L)^2}}$$

$$v_{IN}(t) = V_I \cos(\omega t + \phi_I)$$

Quite often we are not interested in going back into the time domain and simply interested in the behavior of the output as a function of the frequency of the driving sinusoid (e.g., when designing filters)

Frequency Domain Circuit Analysis

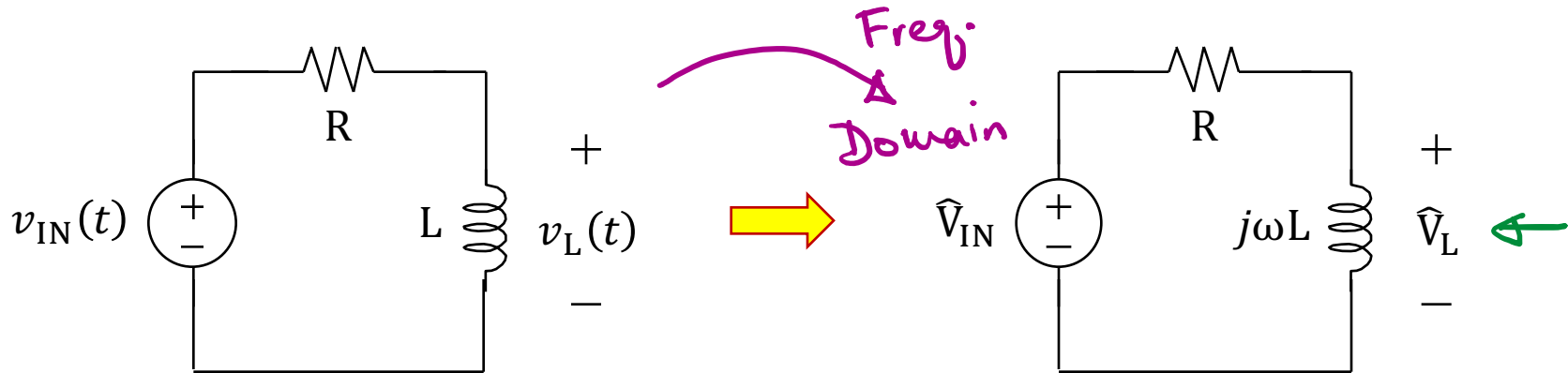

$$v_{IN}(t) = V_I \cos(\omega t + \phi_I)$$


$$+ V_2 \cos(\omega_2 t + \phi_2)$$

$$+ V_3 \cos(\omega_3 t + \phi_3)$$

$$\hat{V}_L = \frac{j\omega L}{R + j\omega L} \hat{V}_{IN}$$

Transfer Function $H(j\omega) \equiv \frac{\hat{V}_L}{\hat{V}_{IN}} = \frac{j\omega L}{R + j\omega L}$

Transfer Function

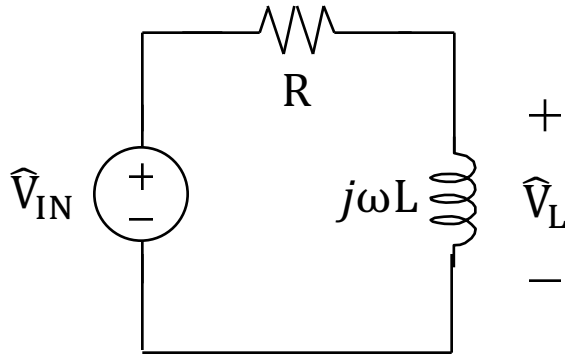

$$\hat{V}_L = \frac{j\omega L}{R + j\omega L} \hat{V}_{IN}$$


$$H(j\omega) \equiv \frac{\hat{V}_L}{\hat{V}_{IN}} = \frac{j\omega L}{R + j\omega L}$$

Low Freq: $H(j\omega) \approx \frac{j\omega L}{R}$ if $R \gg \omega L \Rightarrow \omega \ll \frac{R}{L}$

Corner Freq: $\omega = R/L$ $H(j\omega) = \frac{j\omega L}{\omega L + j\omega L} = \frac{j}{1+j}$ if $R = \omega L \Rightarrow \omega = \frac{R}{L}$


High Freq: $H(j\omega) \approx \frac{j\omega L}{j\omega L} = 1$ if $R \ll \omega L \Rightarrow \omega \gg \frac{R}{L}$

Transfer Function Magnitude and Phase
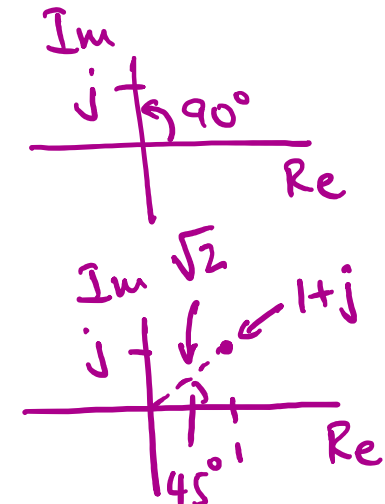
$$H(j\omega) = \begin{cases} \frac{j\omega L}{R} = \frac{\omega L}{R} e^{j90^\circ} & \omega \ll \frac{R}{L} \\ \frac{j}{1+j} = \frac{e^{j90^\circ}}{\sqrt{2} e^{j45^\circ}} = \frac{1}{\sqrt{2}} e^{j45^\circ} & \omega = \frac{R}{L} \\ 1 = 1 e^{j0^\circ} & \omega \gg \frac{R}{L} \end{cases}$$

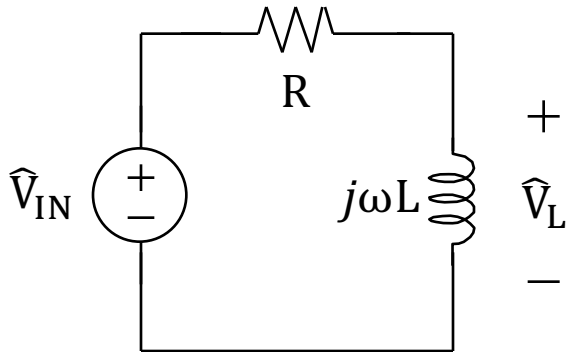
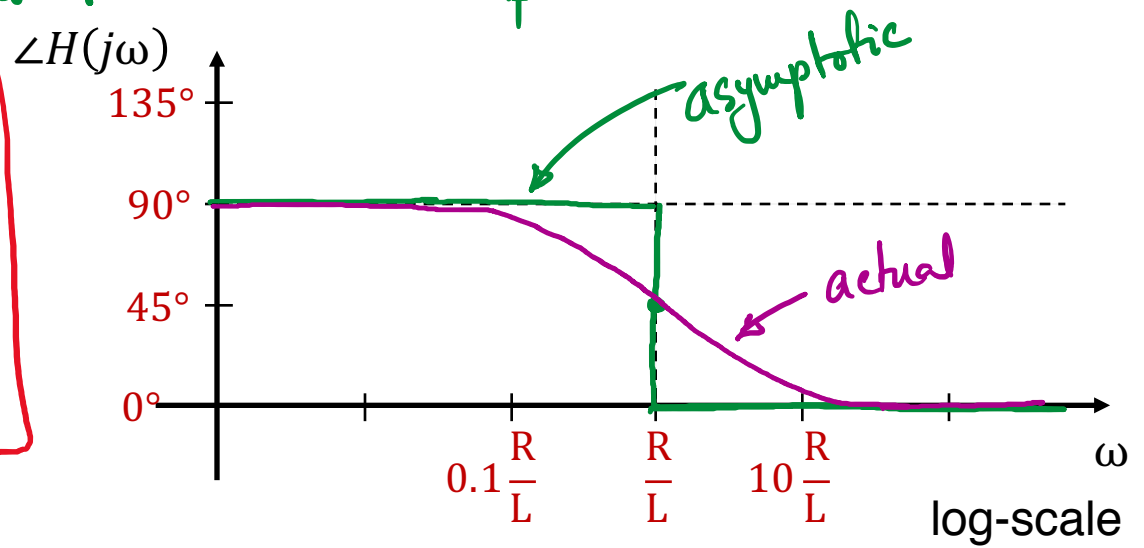
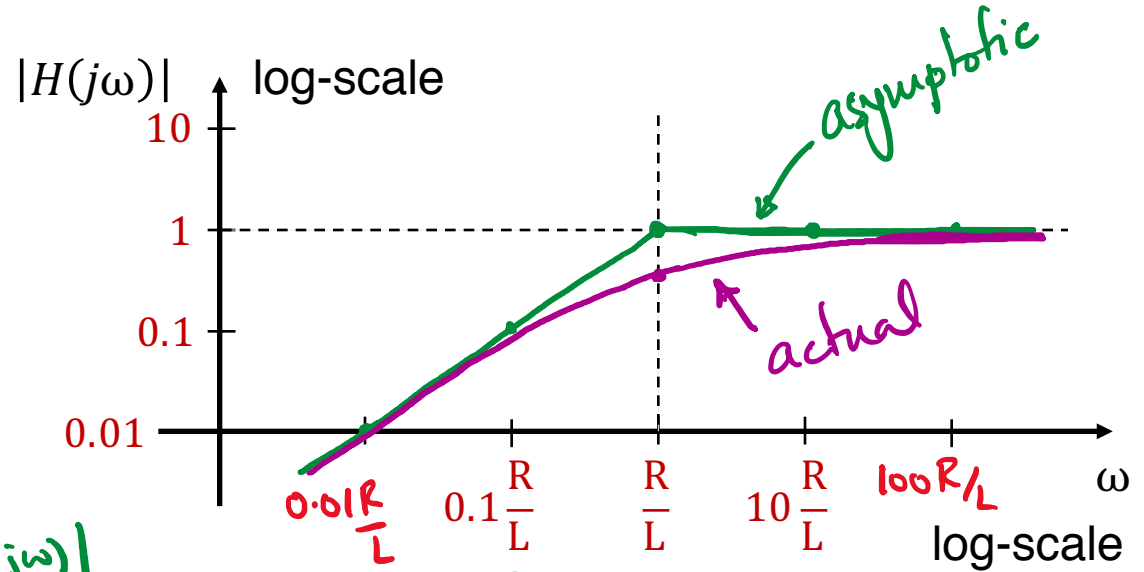
The diagrams illustrate the phase response of the transfer function. The top diagram shows a vector of length 1 along the positive imaginary axis, representing a phase of 90 degrees. The bottom diagram shows a vector of length $\frac{1}{\sqrt{2}}$ at a 45-degree angle in the first quadrant, representing a phase of 45 degrees. The horizontal component is labeled '1' and the vertical component is labeled 'j'.

Magnitude and Phase versus Frequency Plots



$$H(j\omega) \equiv \frac{\hat{V}_L}{\hat{V}_{IN}} = \frac{j\omega L}{R + j\omega L}$$

$$H(j\omega) = \begin{cases} \frac{\omega L}{R} e^{j90^\circ} & \omega \ll R/L \\ \frac{1}{\sqrt{2}} e^{j45^\circ} & \omega = R/L \\ 1 e^{j0^\circ} & \omega \gg R/L \end{cases}$$





Impedance Plots


$$Z_R = R = R e^{j0^\circ}$$

$$Z_L = j\omega L = \omega L e^{j90^\circ}$$
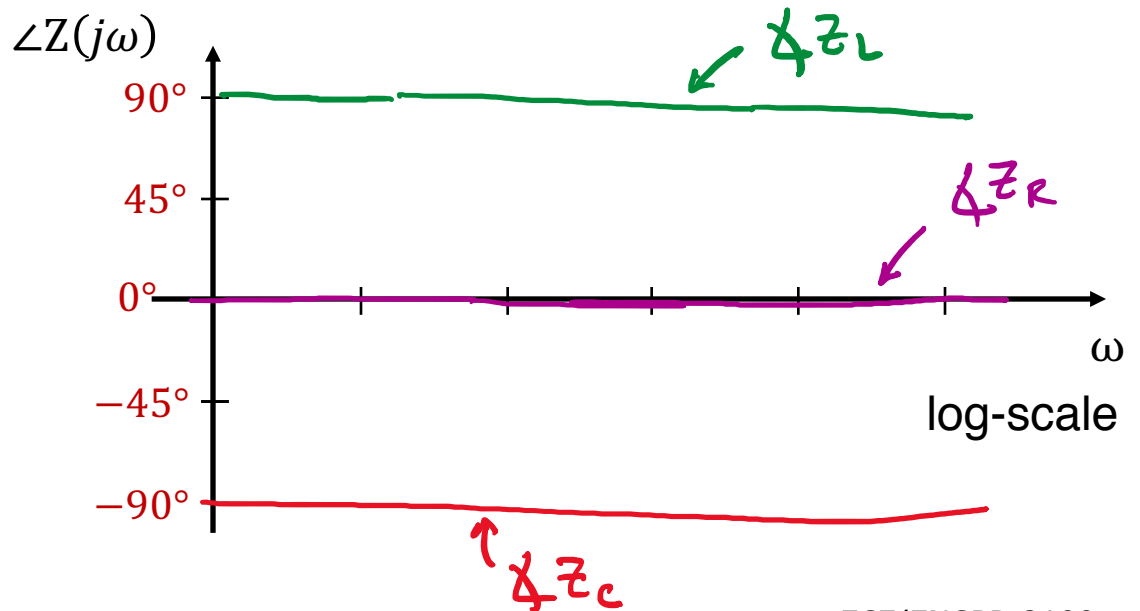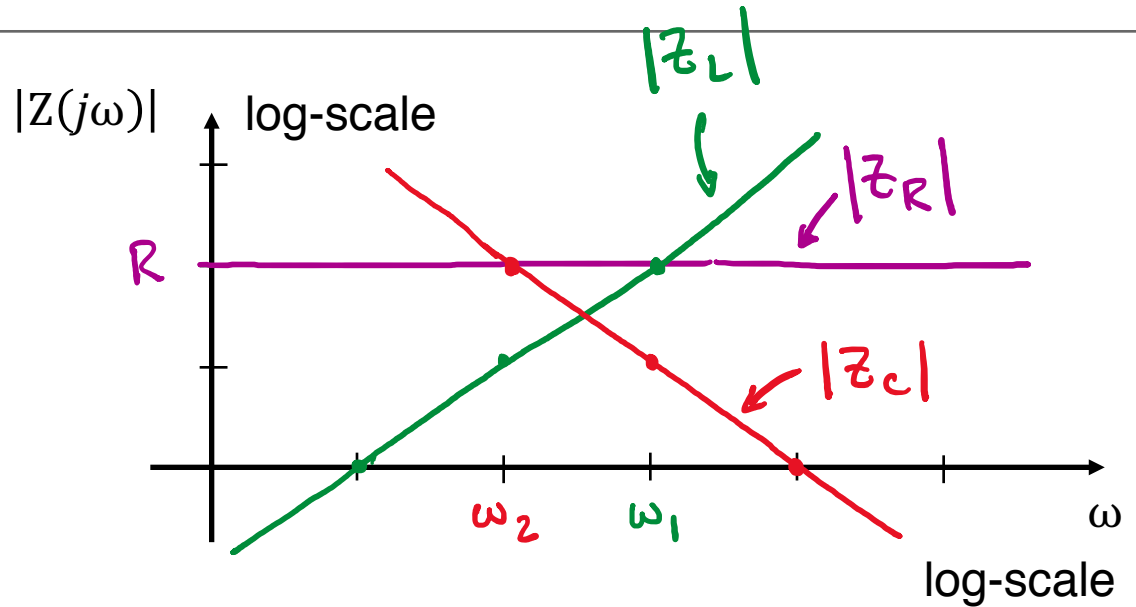
$$Z_C = \frac{1}{j\omega C} = \frac{1}{\omega C} e^{-j90^\circ}$$



Impedance of Parallel L-C Circuit

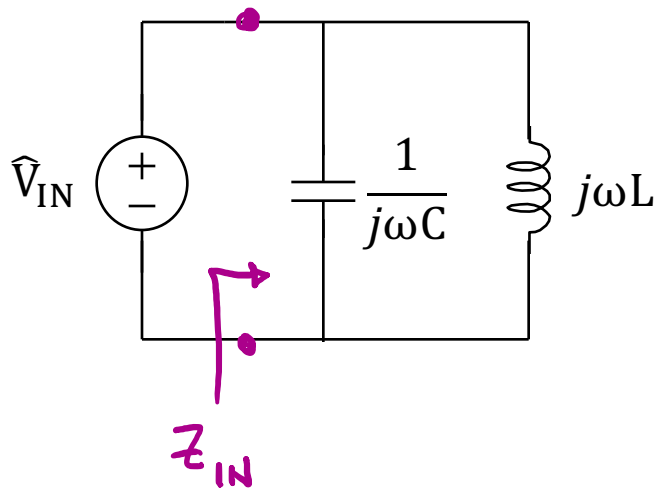

$$Z_{IN} = \frac{1}{j\omega C} \parallel j\omega L$$

$$Z_{IN} = \frac{\frac{1}{j\omega C} \cdot j\omega L}{\frac{1}{j\omega C} + j\omega L} = \frac{j\omega L}{1 - \omega^2 LC}$$

$$Z_{IN} = \begin{cases} \frac{j\omega L}{1} = j\omega L \\ \frac{j\omega L}{-\omega^2 LC} = \frac{1}{j\omega C} \end{cases}$$

low Freq (looks like L)

Hig Freq (looks like C)

at ω where $\frac{1}{j\omega C} = j\omega L$