

ECE/ENGRD 2100

Introduction to Circuits for ECE


Lecture 30

Second Order Systems in Frequency Domain

Announcements

- Recommended Reading:
 - Textbook Chapter 14
- Upcoming due dates:
 - Prelab 5 due by 11:59 pm on Monday April 15, 2019
 - Homework 5 due by 11:59 pm on Wednesday April 17, 2019
 - Lab report 5 due by 11:59 pm on Friday April 19, 2019

Impedance of Parallel L-C Circuit

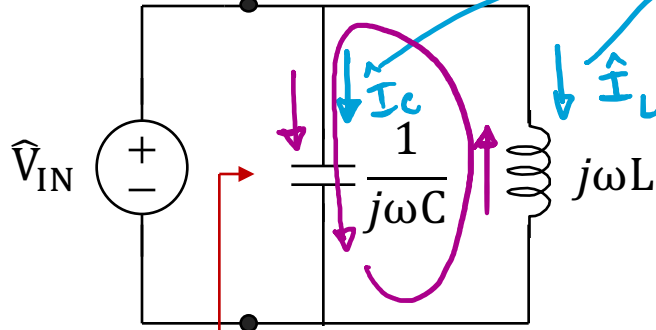

Currents are equal in magnitude but opposite in phase

$$Z_{IN} = \frac{1}{j\omega C} \parallel j\omega L$$

$$\hat{I}_L = \frac{\hat{V}_{IN}}{Z_0 e^{j90^\circ}} = \frac{\hat{V}_{IN}}{Z_0} e^{-j90^\circ}$$

$$\Rightarrow Z_{IN} = \frac{j\omega L}{1 - \omega^2 LC}$$

$$\hat{I}_C = \frac{\hat{V}_{IN}}{Z_0 e^{-j90^\circ}} = \frac{\hat{V}_{IN}}{Z_0} e^{j90^\circ}$$

$$Z_{IN}(j\omega) = \begin{cases} j\omega L & \omega \text{ low} & \omega \ll \frac{1}{\sqrt{LC}} = \omega_0 \\ 1 & \\ j\omega C & \omega \text{ high} & \omega \gg \frac{1}{\sqrt{LC}} = \omega_0 \end{cases}$$

$$\omega L e^{j90^\circ}$$



$$1 = \omega^2 LC \Rightarrow \omega = \frac{1}{\sqrt{LC}} = \omega_0$$

$$\text{@ } \omega = \omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow Z_{IN}(j\omega) = \frac{j\omega L}{0} \rightarrow \infty$$


$$\text{@ } \omega = \omega_0 \Rightarrow \omega L = \omega_0 L = \frac{L}{\sqrt{LC}} = \sqrt{\frac{L}{C}} = Z_0$$

$$\text{@ } \omega = \omega_0 \Rightarrow \frac{1}{\omega C} = \frac{1}{\omega_0 C} = \frac{\sqrt{LC}}{C} = \sqrt{\frac{L}{C}} = Z_0$$

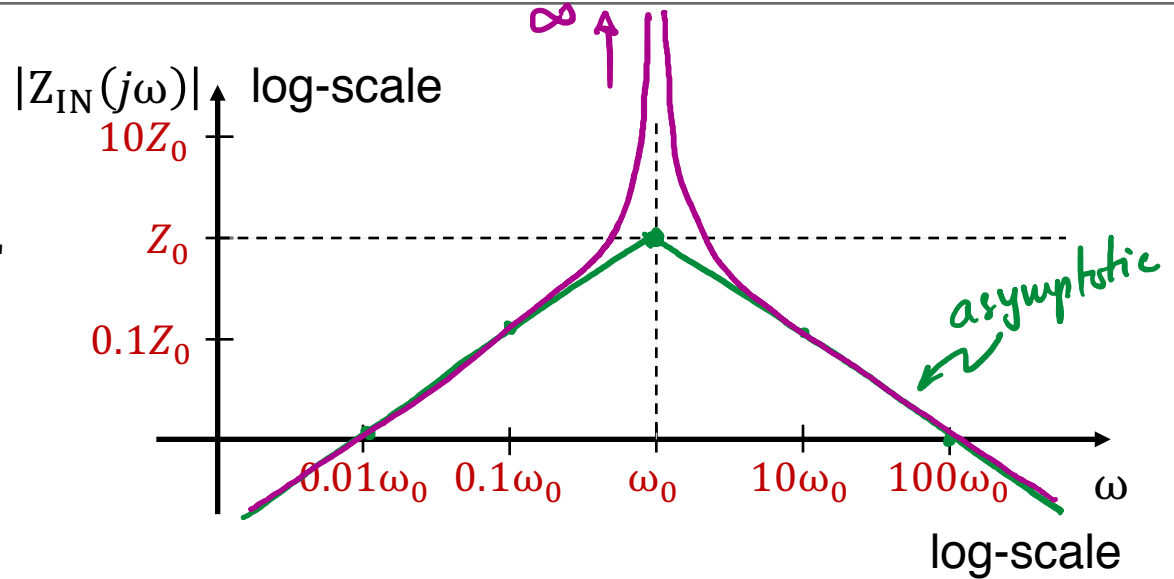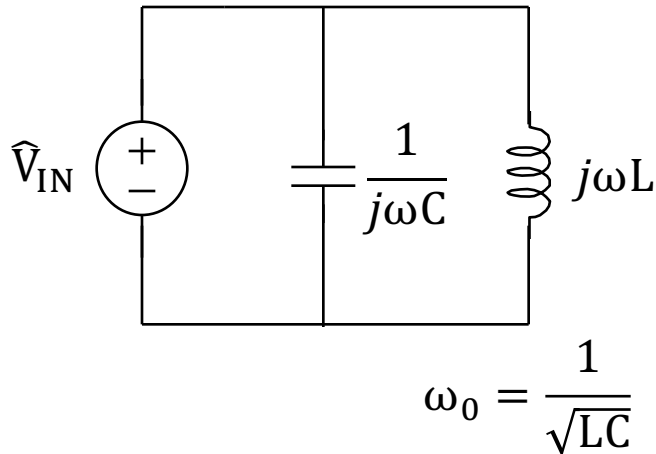
Impedance of Parallel L-C Circuit (Cont.)


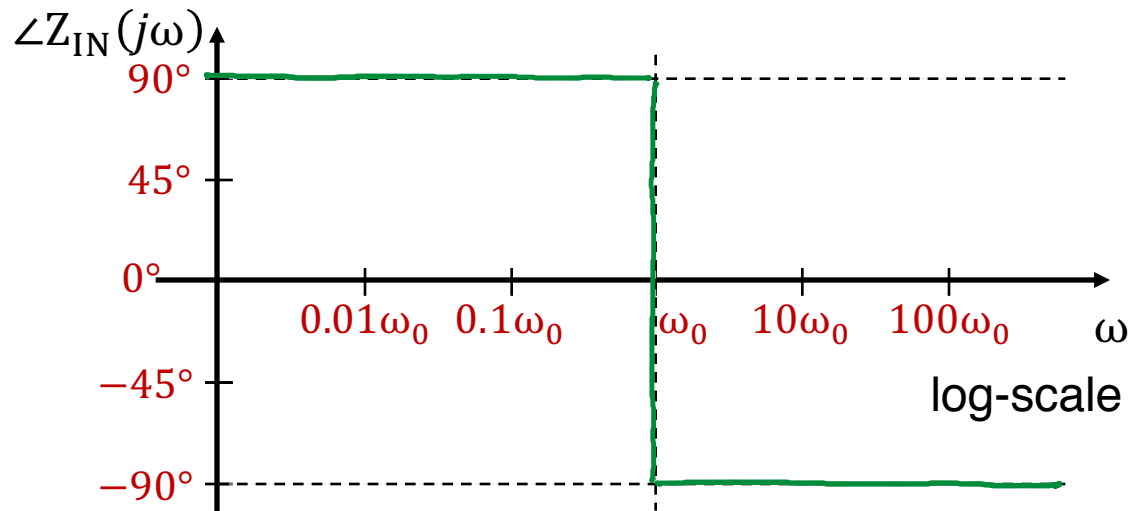
$$Z_{IN}(j\omega) = \begin{cases} \omega L e^{j90^\circ} & \omega \ll \omega_0 \\ \infty & \omega = \omega_0 \\ \frac{1}{\omega C} e^{-j90^\circ} & \omega \gg \omega_0 \end{cases}$$



Impedance of Series L-C Circuit

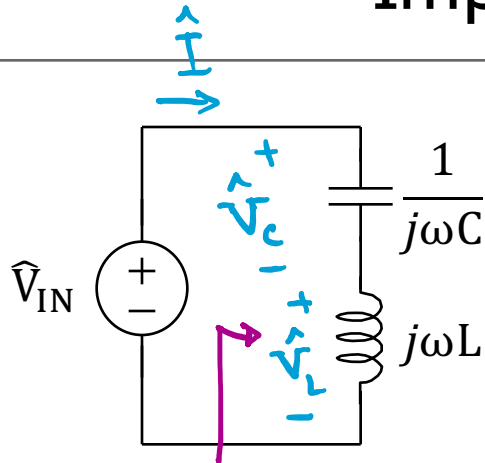

$$Z_{IN} = \frac{1}{j\omega C} + j\omega L = \frac{1 - \omega^2 LC}{j\omega C}$$

$$Z_{IN} = \begin{cases} \frac{1}{j\omega C} = \frac{1}{\omega C} e^{-j90^\circ} \\ 0 \\ j\omega L = \omega L e^{+j90^\circ} \end{cases}$$

$$\omega \ll \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega = \omega_0$$

$$\omega \gg \omega_0 = \frac{1}{\sqrt{LC}}$$




@ $\omega = \omega_0$ Z_{IN}

$$\hat{V}_C = \frac{1}{j\omega_0 C} \hat{I} = Z_0 \hat{I} e^{-j90^\circ}$$



$$\hat{V}_L = j\omega_0 L \hat{I} = Z_0 \hat{I} e^{+j90^\circ}$$

Same magnitude } so cancel
but opposite phase }


Impedance of Series L-C Circuit (Cont.)

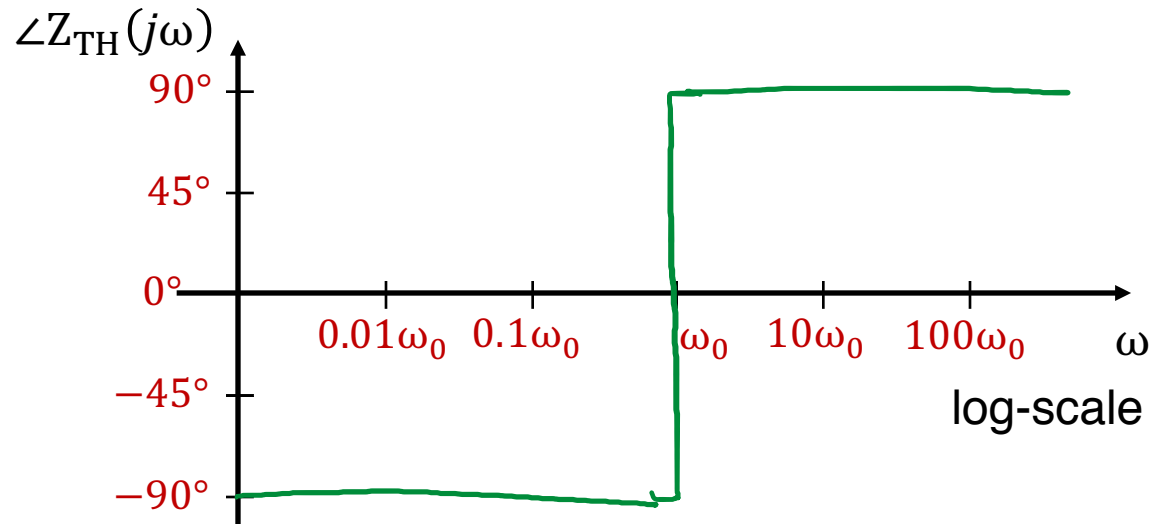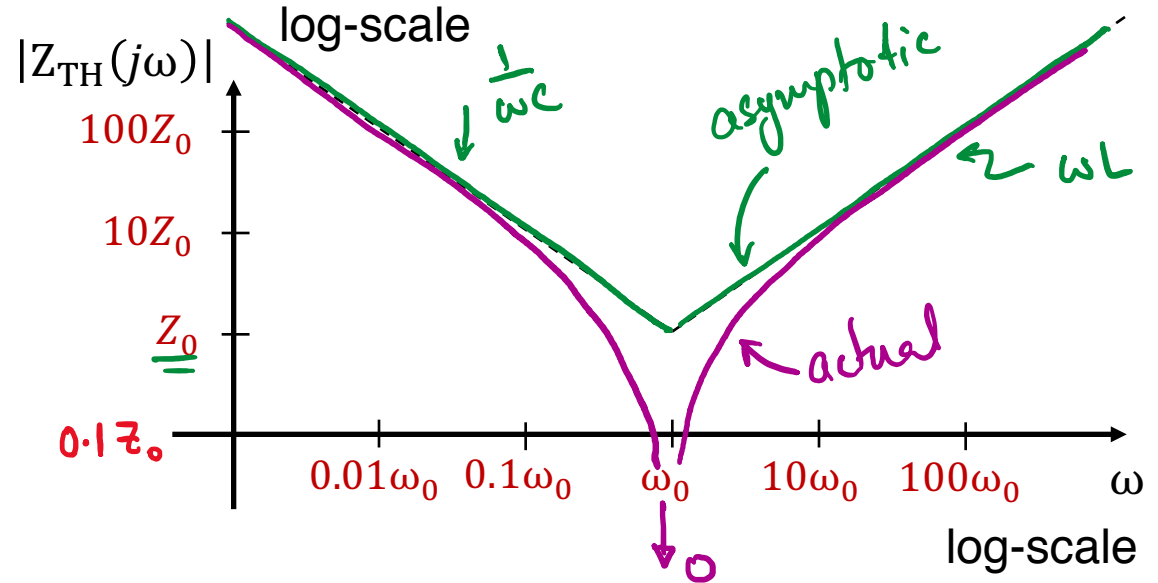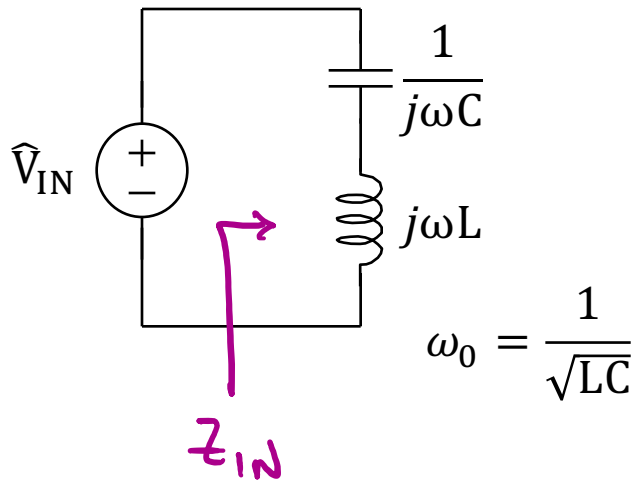


Admittance of Series L-C Circuit

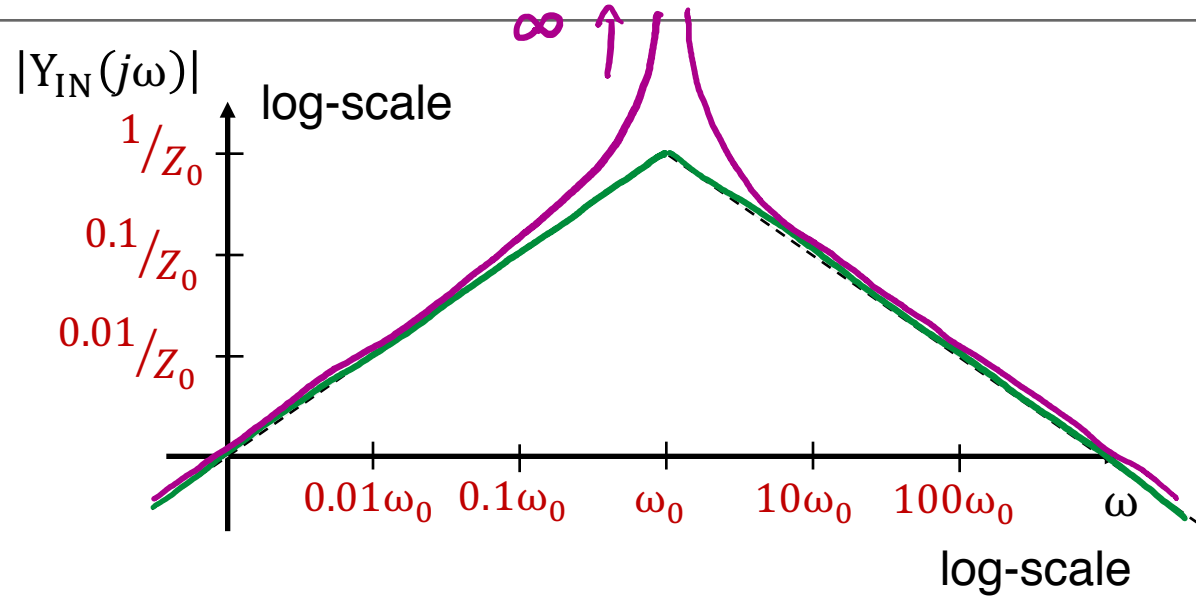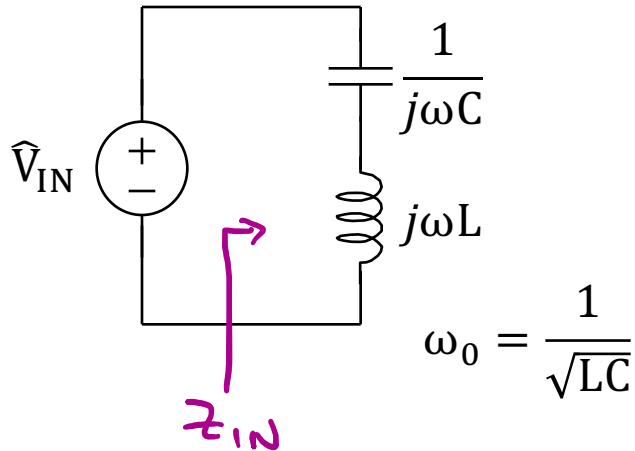

$$Y_{IN} \equiv \frac{1}{Z_{IN}}$$

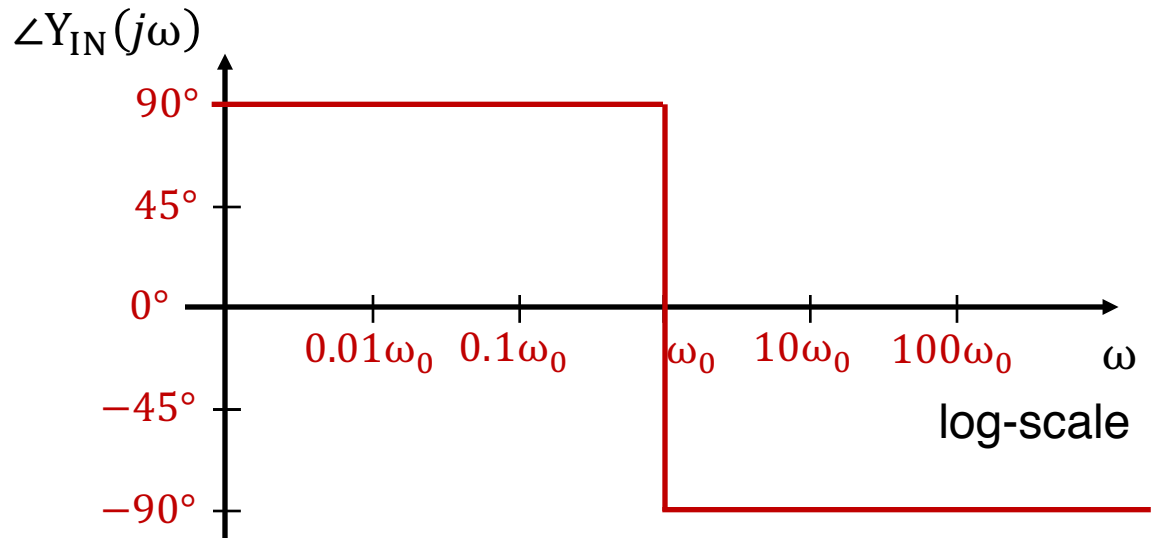


Series L-C Circuit with Damping

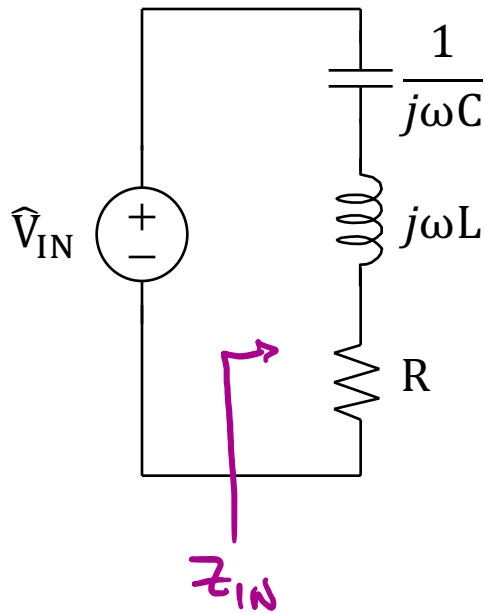

$$Z_{IN} = \frac{1}{j\omega C} + R + j\omega L = \frac{1 + j\omega RC - \omega^2 LC}{j\omega C}$$

$$Z_{IN} = \begin{cases} \frac{1}{j\omega C} = \frac{1}{\omega C} e^{-j90^\circ} & \omega < \omega_0 = \frac{1}{\sqrt{LC}} \\ \frac{\cancel{1} + j\omega_0 R \cancel{C} - \cancel{1}}{\cancel{j\omega_0 C}} = R & \omega = \omega_0 \\ \frac{-\omega^2 LC}{j\omega C} = j\omega L = \omega L e^{+j90^\circ} & \omega \gg \omega_0 = \frac{1}{\sqrt{LC}} \end{cases}$$



Case 1 – Overdamped

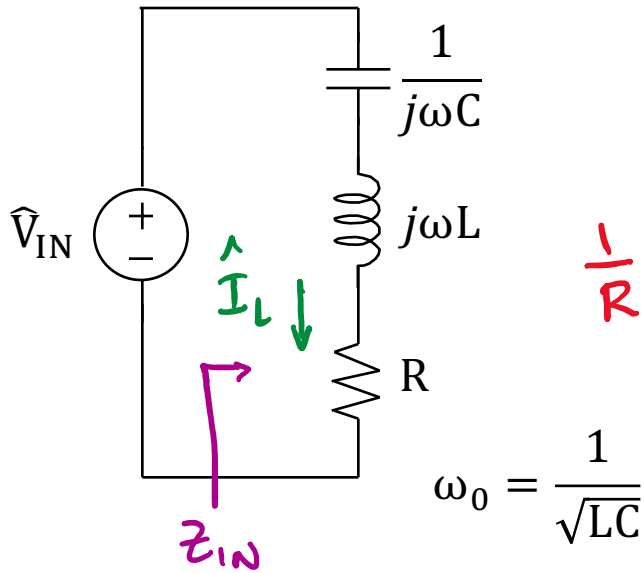



$$Y_{IN} \equiv \frac{1}{Z_{IN}}$$

$$R_0 > 2Z_0$$


$$\hat{I}_L = \frac{\hat{V}_{IN}}{Z_{IN}} = Y_{IN} \hat{V}_{IN}$$

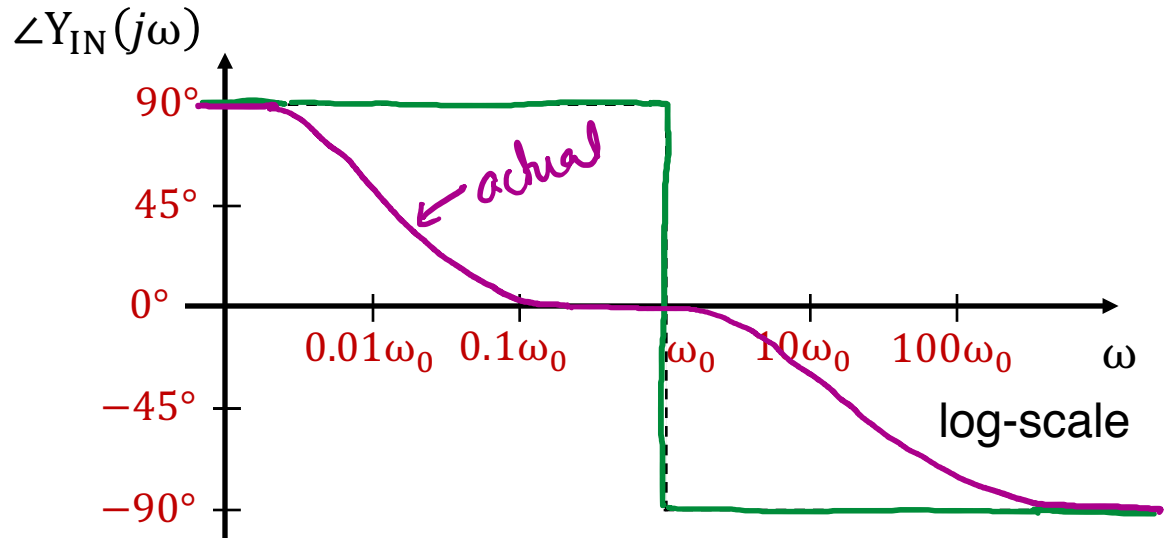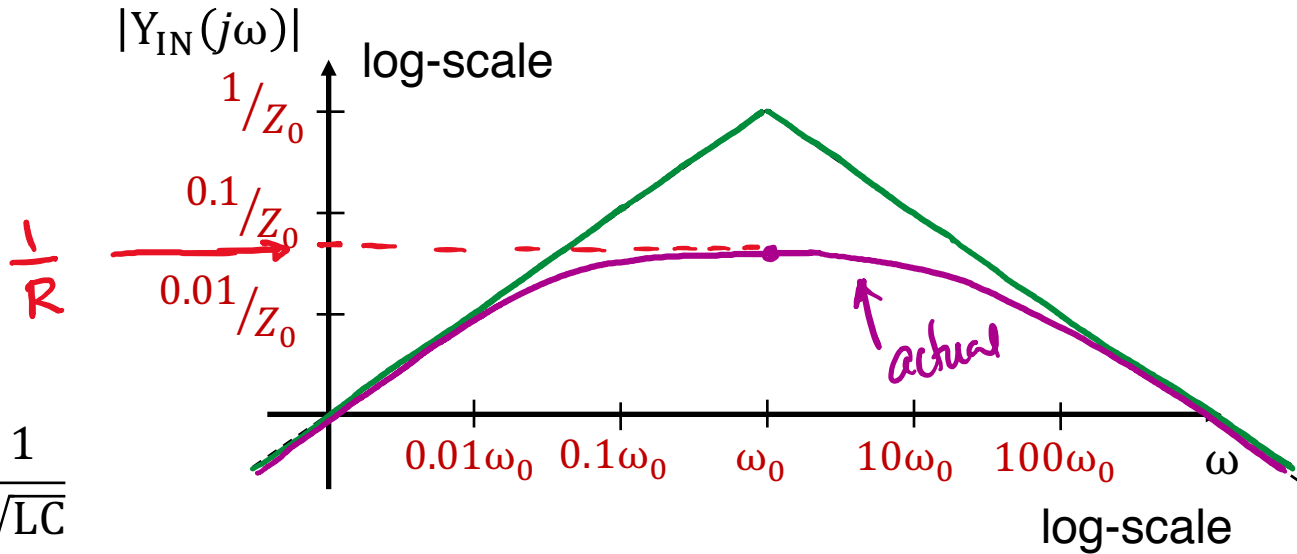


Case 2 – Critically Damped

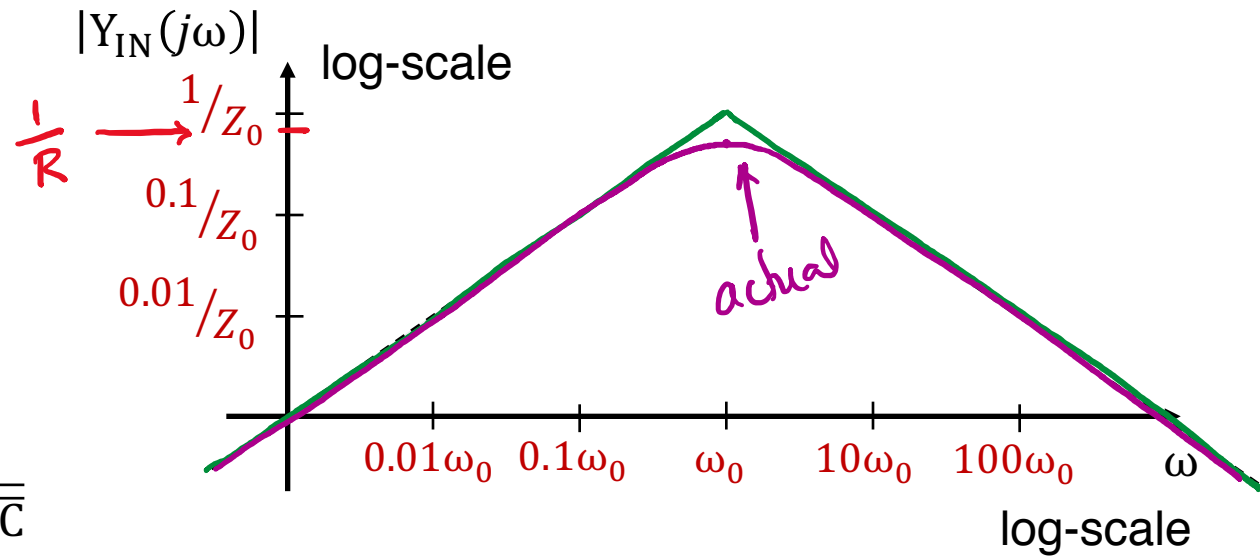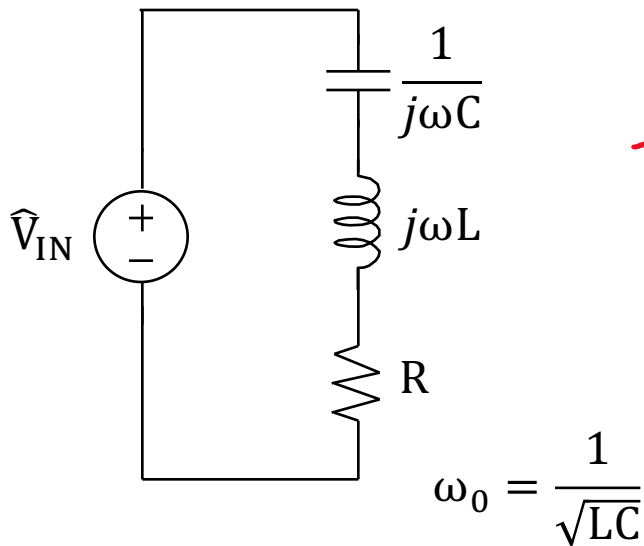

$R = 2Z_0$


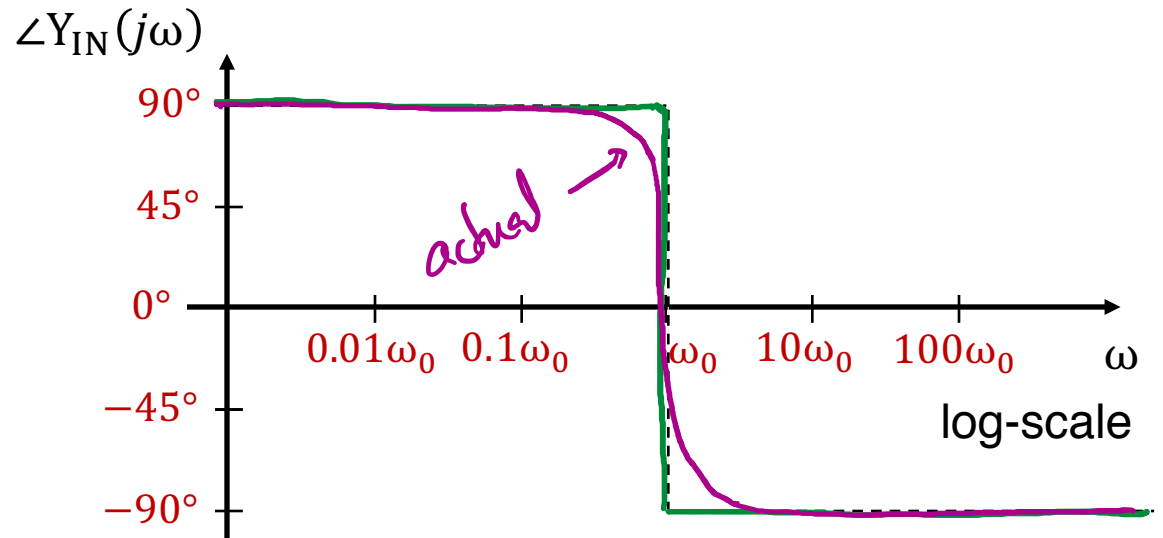


Case 3 – Underdamped

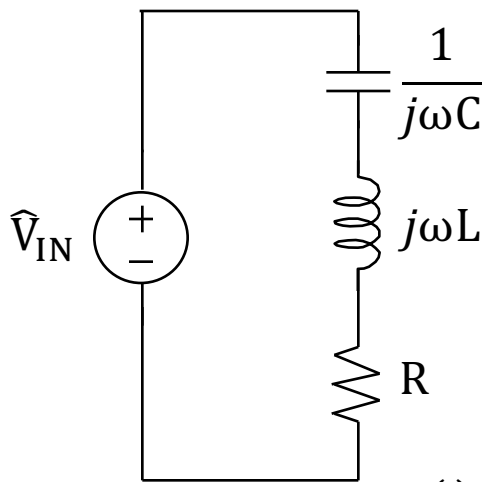


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$R < 2Z_0$$

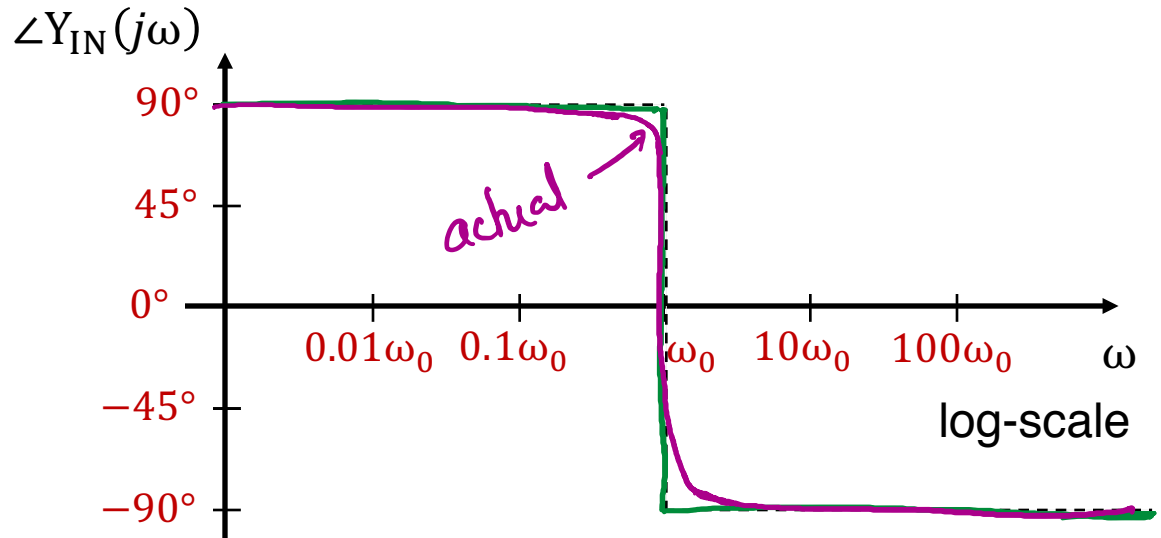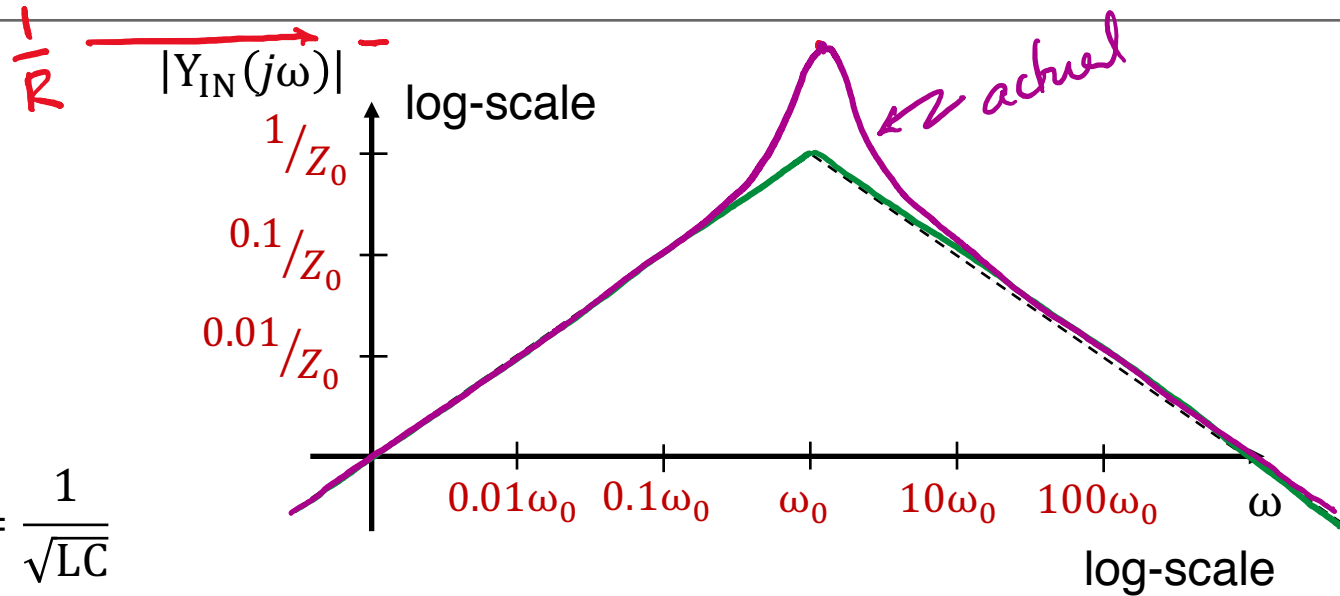

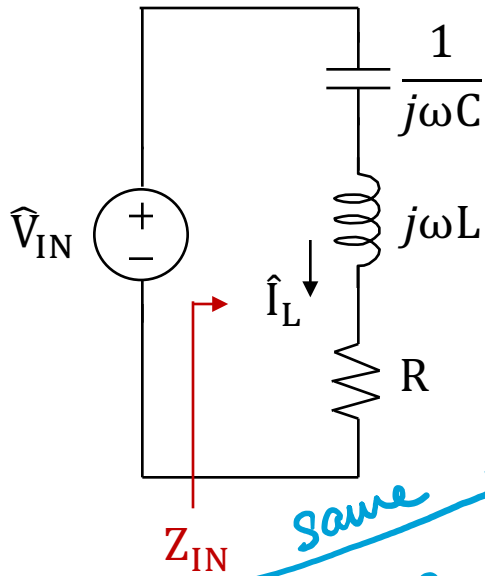Connection Between Frequency & Time Domain



$$\hat{I}_L = \frac{\hat{V}_{IN}}{Z_{IN}} \quad \Rightarrow \quad \frac{\hat{V}_{IN}}{\hat{I}_L} = Z_{IN} = \frac{1}{j\omega C} + R + j\omega L$$

$$\hat{V}_{IN} = \frac{1 + j\omega RC + (j\omega)^2 LC}{j\omega C} \hat{I}_L$$

$$(j\omega)^2 LC \hat{I}_L + j\omega RC \hat{I}_L + \hat{I}_L = j\omega C \hat{V}_{IN}$$

Diff. Eq.

$$LC \frac{d^2 i_L}{dt^2} + RC \frac{di_L}{dt} + i_L = C \frac{dv_{IN}}{dt}$$

$$(j\omega)^2 LC \hat{I}_L e^{j\omega t} + (j\omega) RC \hat{I}_L e^{j\omega t} + \hat{I}_L e^{j\omega t} = (j\omega) C \hat{V}_{IN} e^{j\omega t}$$

Plug in Diff Eqn

$$v_{IN} \rightarrow \hat{V}_{IN} e^{j\omega t}$$

$$i_L \rightarrow \hat{I}_L e^{j\omega t}$$

$$\alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$Q \equiv \frac{\omega_0}{2\alpha}$$

$$Q = \frac{Z_0}{R}$$

Frequency Response and Natural Response

Overdamped

$$R > 2Z_0$$

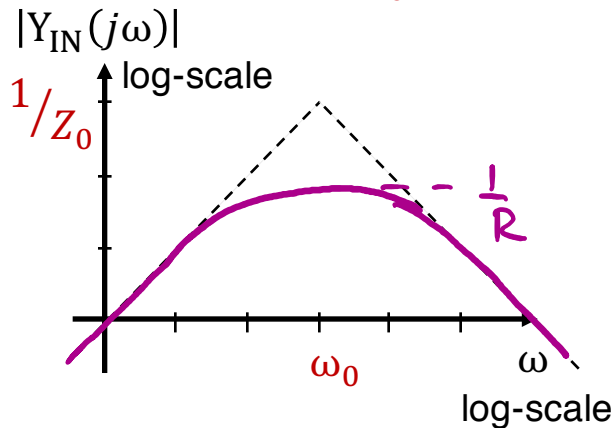


$$Q \equiv \frac{\omega_0}{2\alpha} = \frac{Z_0}{R} < \frac{1}{2}$$

$$\Rightarrow \alpha > \omega_0$$

$$A_1 e^{-(\alpha - \sqrt{\alpha^2 - \omega_0^2})t} + A_2 e^{-(\alpha + \sqrt{\alpha^2 - \omega_0^2})t}$$

Critically damped

$$R = 2Z_0$$

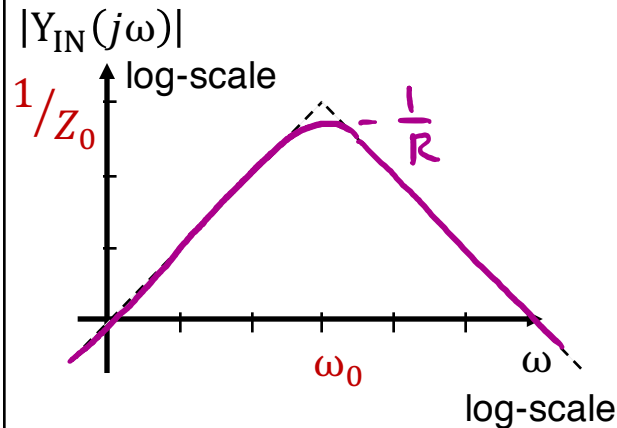


$$Q \equiv \frac{\omega_0}{2\alpha} = \frac{Z_0}{R} = \frac{1}{2}$$

$$\Rightarrow \alpha = \omega_0$$

$$A_1 e^{-\alpha t} + A_2 t e^{-\alpha t}$$

Underdamped

$$R < 2Z_0$$

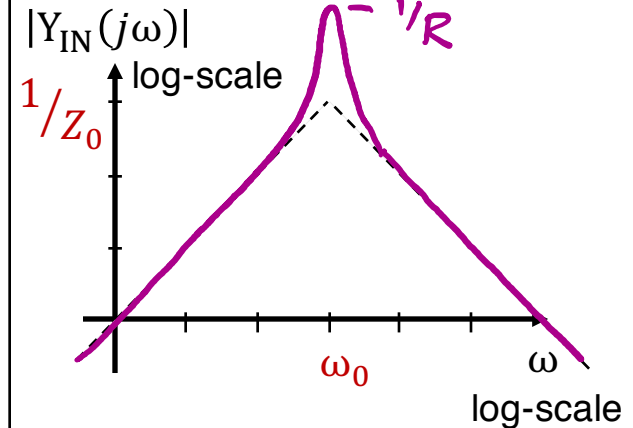

$$Q \equiv \frac{\omega_0}{2\alpha} = \frac{Z_0}{R} > \frac{1}{2}$$

$$\Rightarrow \alpha < \omega_0$$

$$A_1 e^{-\alpha t} \cos(\omega_d t) + A_2 e^{-\alpha t} \sin(\omega_d t)$$

$$\omega_d \equiv \sqrt{\omega_0^2 - \alpha^2}$$