

ECE/ENGRD 2100

Introduction to Circuits for ECE


Lecture 31

Passive and Active Filters


Announcements

- Recommended Reading:
 - Textbook Chapter 14 and Chapter 15
- Upcoming due dates:
 - Prelab 5 due by 11:59 pm on Monday April 15, 2019
 - Homework 5 due by 11:59 pm on Friday April 19, 2019
 - Lab report 5 due by 11:59 pm on Friday April 19, 2019


Filters

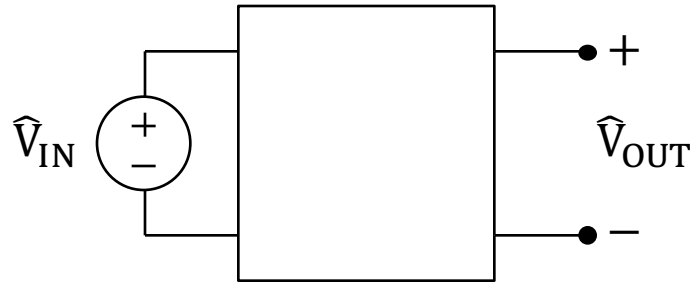


Low Pass Filter

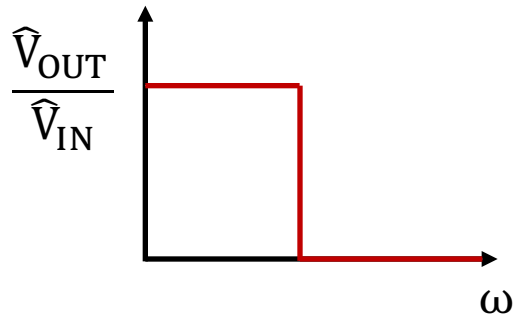


High Pass Filter

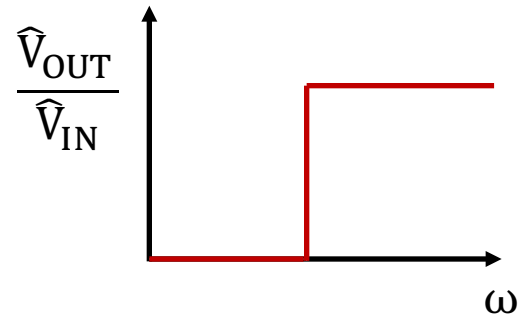


Band Pass Filter

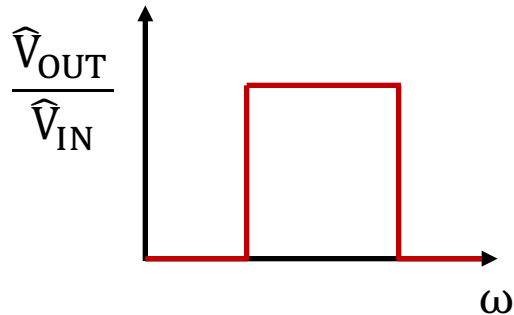

Band Stop Filter

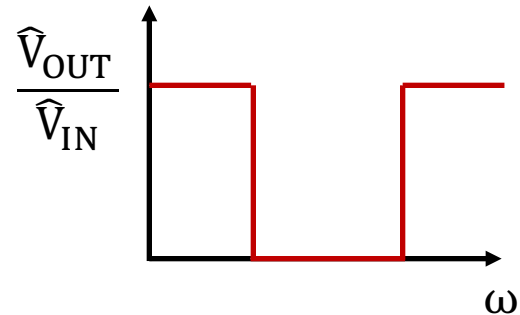

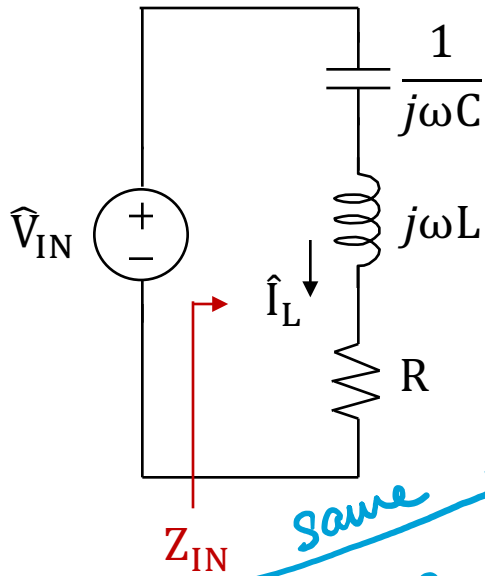Connection Between Frequency & Time Domain



$$\hat{I}_L = \frac{\hat{V}_{IN}}{Z_{IN}} \quad \Rightarrow \quad \frac{\hat{V}_{IN}}{\hat{I}_L} = Z_{IN} = \frac{1}{j\omega C} + R + j\omega L$$

$$\hat{V}_{IN} = \frac{1 + j\omega RC + (j\omega)^2 LC}{j\omega C} \hat{I}_L$$

$$(j\omega)^2 LC \hat{I}_L + j\omega RC \hat{I}_L + \hat{I}_L = j\omega C \hat{V}_{IN}$$

Diff. Eq.

$$LC \frac{d^2 i_L}{dt^2} + RC \frac{di_L}{dt} + i_L = C \frac{dv_{IN}}{dt}$$

Plug in Diff Eqn

$$v_{IN} \rightarrow \hat{V}_{IN} e^{j\omega t}$$

$$i_L \rightarrow \hat{I}_L e^{j\omega t}$$

$$(j\omega)^2 LC \hat{I}_L e^{j\omega t} + (j\omega) RC \hat{I}_L e^{j\omega t} + \hat{I}_L e^{j\omega t} = (j\omega) C \hat{V}_{IN} e^{j\omega t}$$

$$\alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$Q \equiv \frac{\omega_0}{2\alpha}$$

$$Q = \frac{Z_0}{R}$$

Frequency Response and Natural Response

Overdamped

$$R > 2Z_0$$

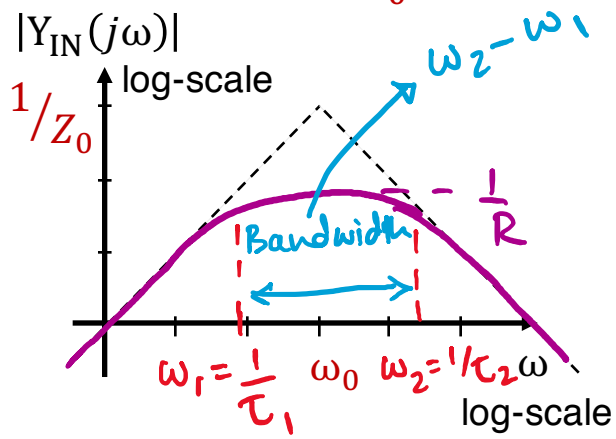


$$Q \equiv \frac{\omega_0}{2\alpha} = \frac{Z_0}{R} < \frac{1}{2}$$

$$\Rightarrow \alpha > \omega_0$$

$$A_1 e^{-(\alpha - \sqrt{\alpha^2 - \omega_0^2})t} + A_2 e^{-(\alpha + \sqrt{\alpha^2 - \omega_0^2})t} = A_1 e^{-t/\tau_1} + A_2 e^{-t/\tau_2}$$

Critically damped

$$R = 2Z_0$$

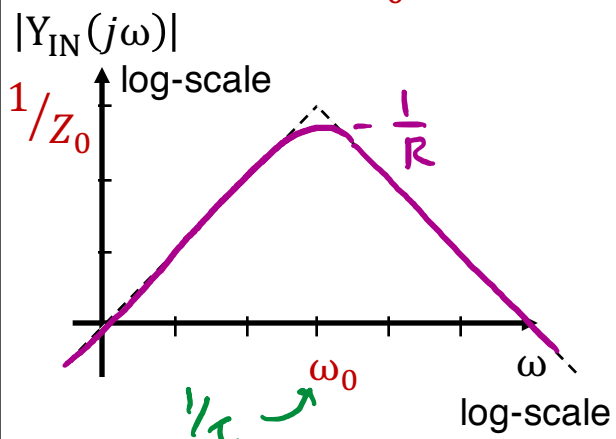


$$Q \equiv \frac{\omega_0}{2\alpha} = \frac{Z_0}{R} = \frac{1}{2}$$

$$\Rightarrow \alpha = \omega_0$$

$$A_1 e^{-at} + A_2 t e^{-at} = A_1 e^{-t/\tau} + A_2 t e^{-t/\tau}$$

Underdamped

$$R < 2Z_0$$

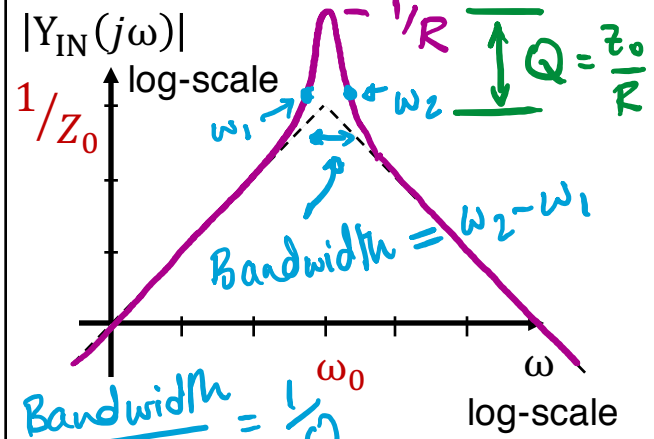


$$Q \equiv \frac{\omega_0}{2\alpha} = \frac{Z_0}{R} > \frac{1}{2}$$

$$\Rightarrow \alpha < \omega_0$$


$$A_1 e^{-\alpha t} \cos(\omega_d t) + A_2 e^{-\alpha t} \sin(\omega_d t)$$

$$\omega_d \equiv \sqrt{\omega_0^2 - \alpha^2}$$


Passive Filter Synthesis

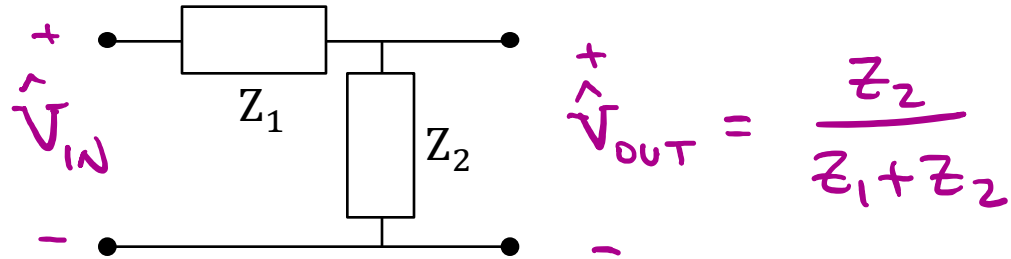

Low Pass Filter

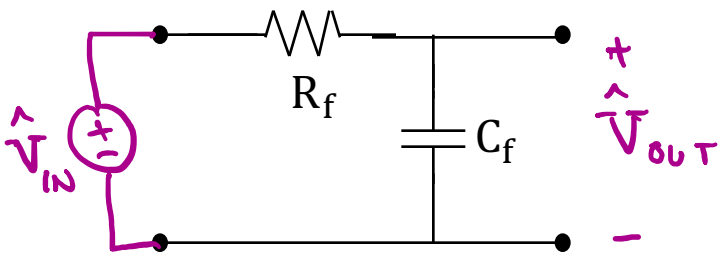


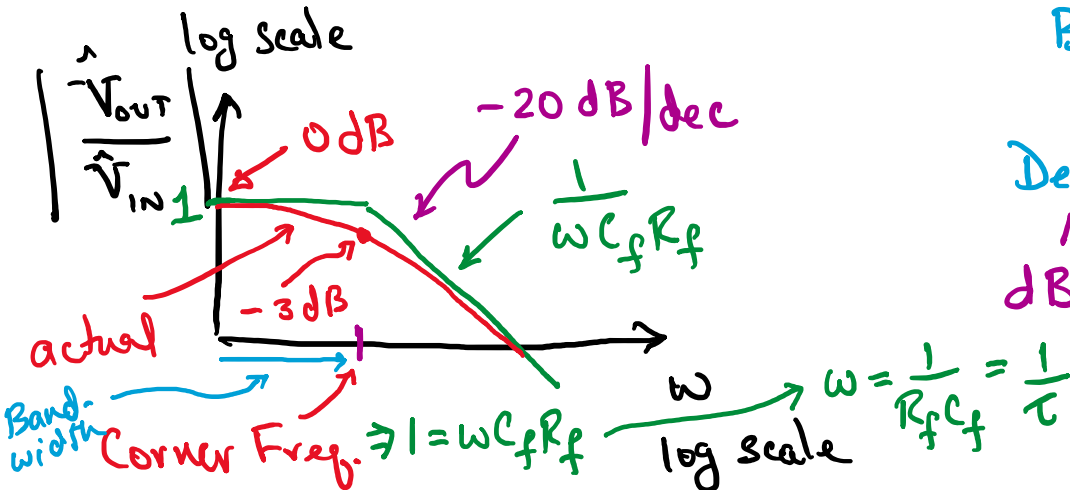
$$\frac{\hat{V}_{OUT}}{\hat{V}_{IN}} = \frac{\frac{1}{j\omega C_f}}{\frac{1}{j\omega C_f} + R_f} = \frac{1}{1 + j\omega C_f R_f}$$






$$\text{Bel} = \log_{10} \left(\frac{P_{OUT}}{P_{IN}} \right)$$

$$\begin{aligned}
 \text{Decibel} &= 10 \log_{10} \left(\frac{P_{OUT}}{P_{IN}} \right) \\
 &= 10 \log_{10} \left(\frac{V_{OUT}^2 / R}{V_{IN}^2 / R} \right) \\
 &= 20 \log_{10} \left(\frac{V_{OUT}}{V_{IN}} \right)
 \end{aligned}$$




Passive Filter Synthesis (Cont.)

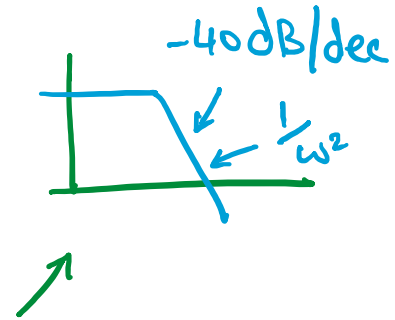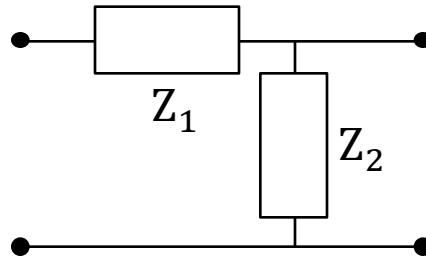


Low Pass Filters

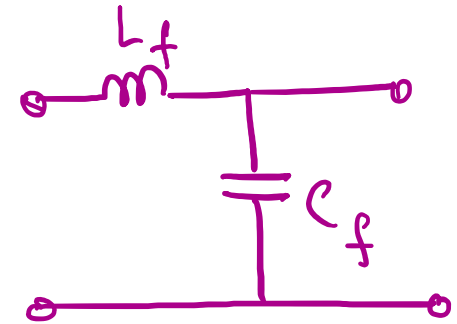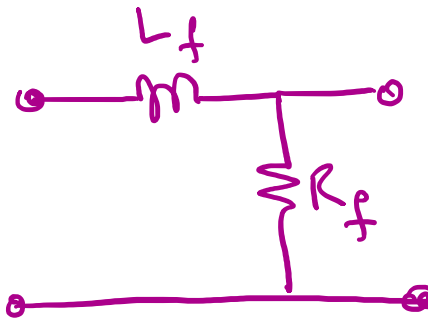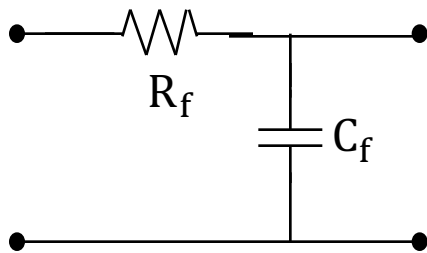



High Pass Filters

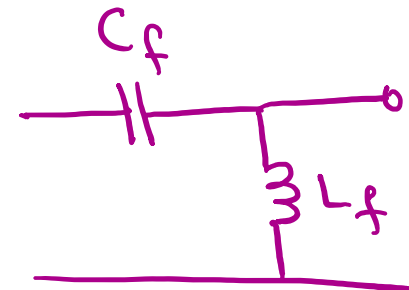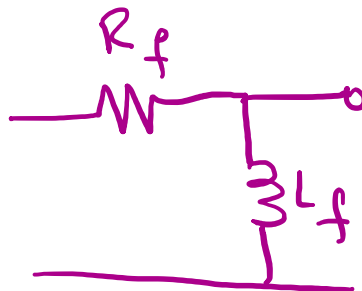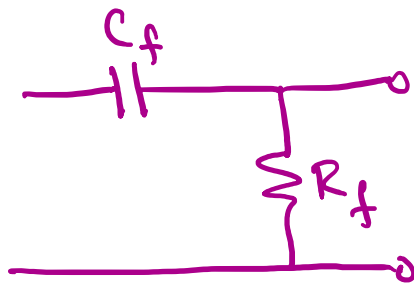



Passive Filter Synthesis (Cont.)

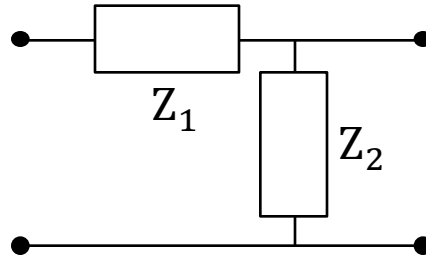


Band Pass Filters

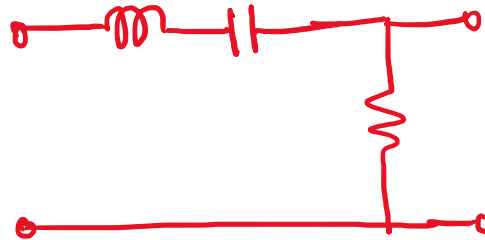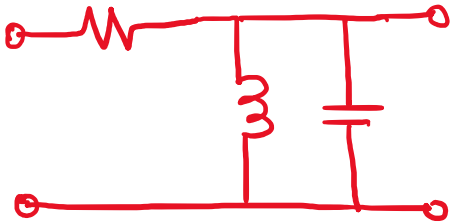


Band Stop Filters

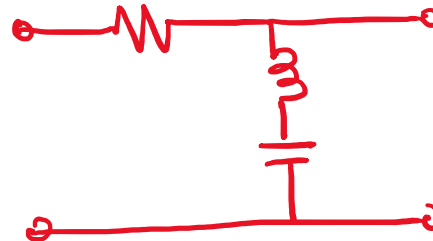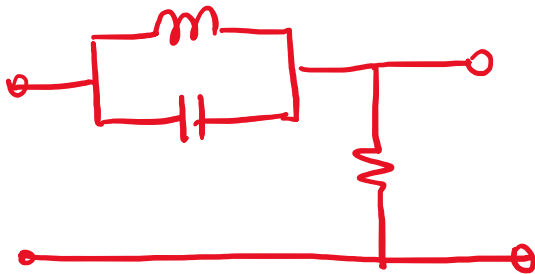

Limitations of Passive Filters

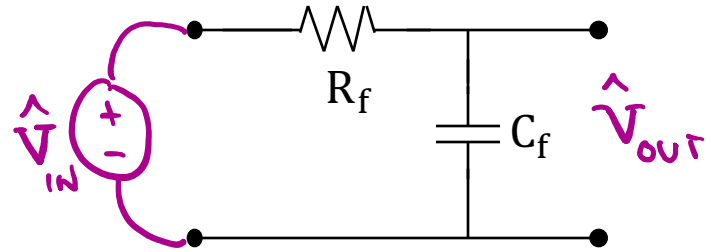

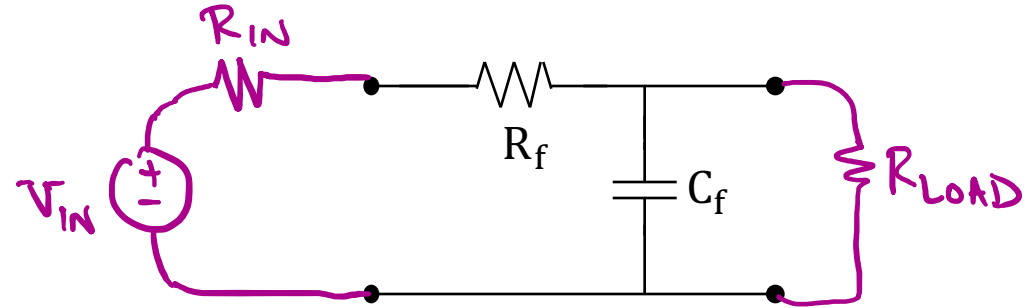
$$\text{Corner Freq} = \frac{1}{R_f C_f}$$



$$\text{Corner Freq} = \frac{1}{R_{TH} C_f}$$


$$R_{TH} = (R_{IN} + R_f) \parallel R_{LOAD}$$

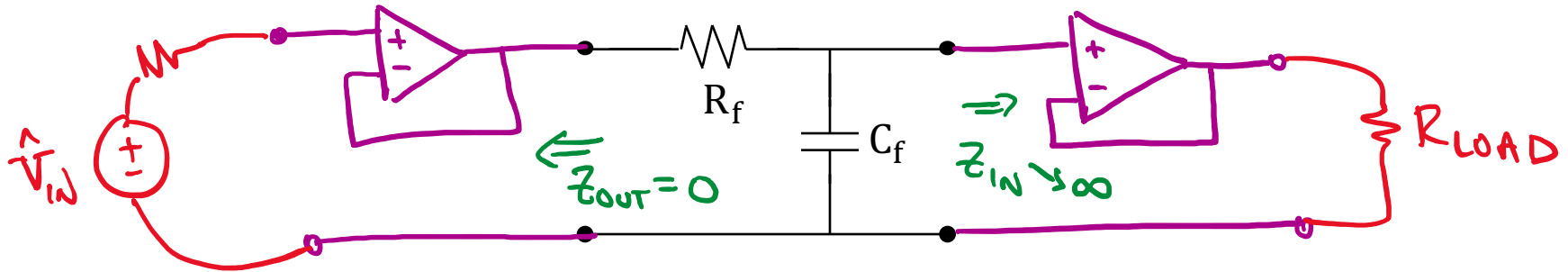Active Op Amp Filters – Brute Force Approach



$$\text{Corner Freq} = \frac{1}{R_f C_f}$$

Active Filters – Elegant Approach

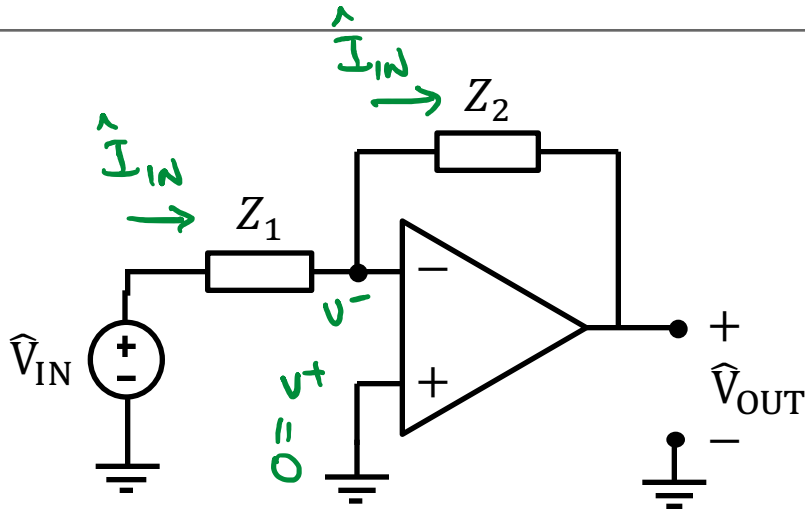

$$v^+ \approx v^-$$

$$\hat{I}_{IN} = \frac{\hat{V}_{IN}}{Z_1}$$

$$\hat{V}_{OUT} = 0 - \hat{I}_{IN} Z_2$$

$$\hat{V}_{OUT} = -\frac{Z_2}{Z_1} \hat{V}_{IN}$$