

# **ECE/ENGRD 2100**

Introduction to Circuits for ECE

Lecture 32


Active Filters

# Announcements

---

- Recommended Reading:
  - Textbook Chapter 15
- Upcoming due dates:
  - Prelab 5 due by 11:59 pm on Monday April 15, 2019
  - Homework 5 due by 11:59 pm on Monday April 22, 2019
  - Lab report 5 due by 11:59 pm on Friday April 19, 2019

# Active Filters – Elegant Approach

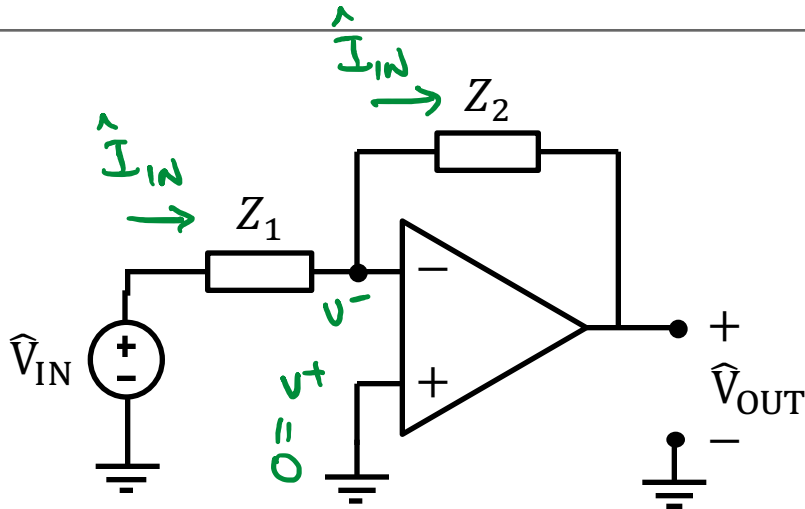


$$v^+ \approx v^-$$

$$\hat{I}_{IN} = \frac{\hat{V}_{IN}}{Z_1}$$


$$\hat{V}_{OUT} = 0 - \hat{I}_{IN} Z_2$$

$$\hat{V}_{OUT} = -\frac{Z_2}{Z_1} \hat{V}_{IN}$$


# Low Pass Active Filter Synthesis

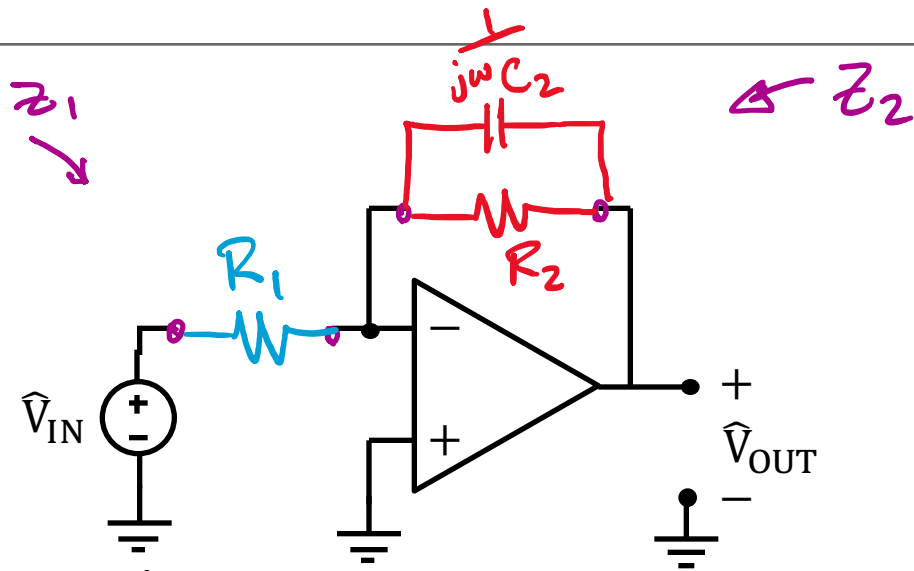

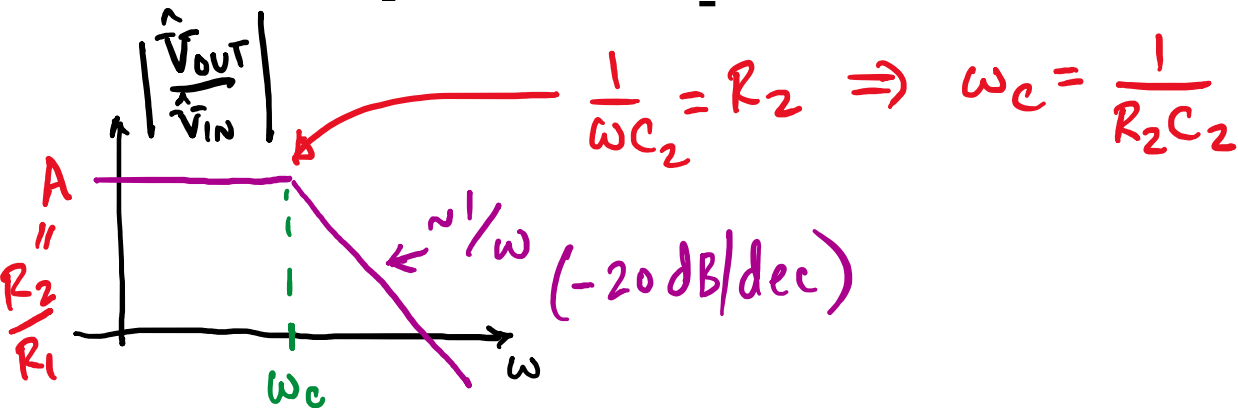
$$\frac{\hat{V}_{OUT}}{\hat{V}_{IN}} = -\frac{Z_2}{Z_1}$$



# High Pass Active Filter Synthesis

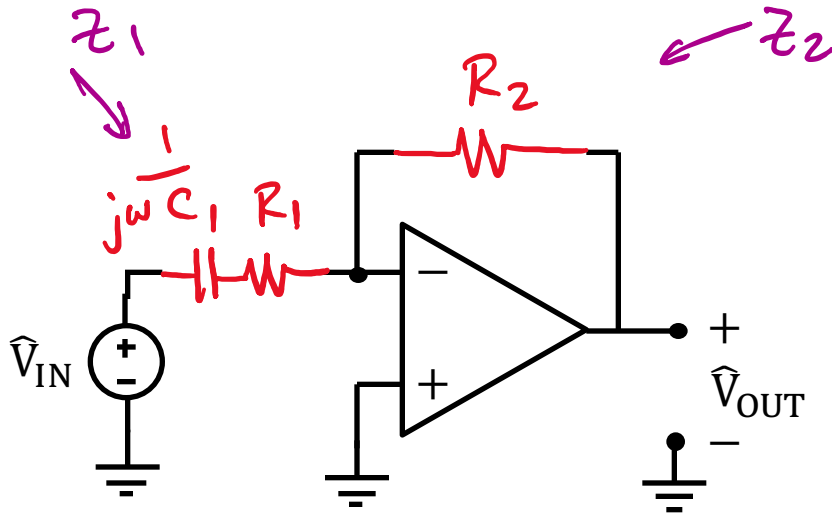

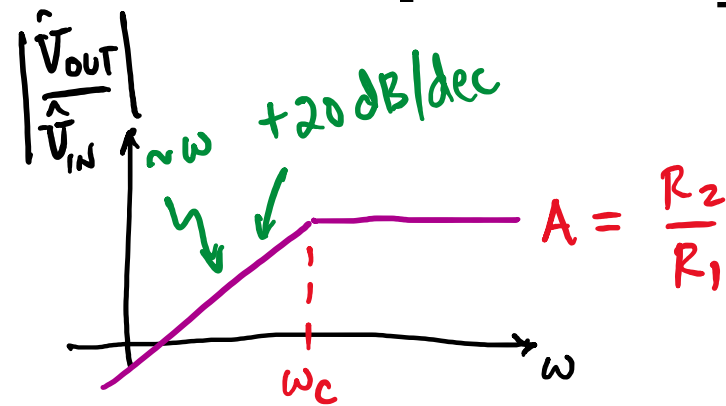
$$\frac{\hat{V}_{OUT}}{\hat{V}_{IN}} = -\frac{z_2}{z_1}$$



$$\omega_c: \frac{1}{\omega C_1} = R_1 \Rightarrow \omega_c = \frac{1}{R_1 C_1}$$


$$\frac{\hat{V}_{OUT}}{\hat{V}_{IN}} = -\frac{R_2}{\frac{1}{j\omega C_1} + R_1} = \frac{-j\omega R_2 C_1}{1 + j\omega R_1 C_1}$$

# Band Pass Active Filter Synthesis

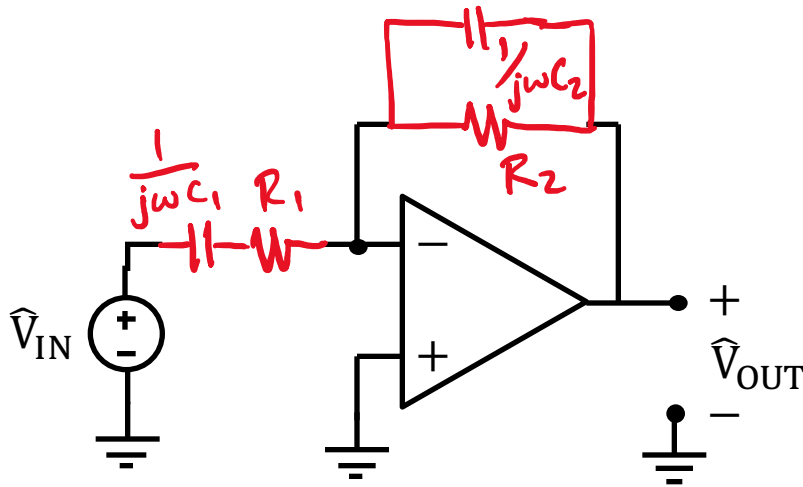

$$\frac{\hat{V}_{OUT}}{\hat{V}_{IN}} = -\frac{z_2}{z_1}$$

Need:  $\omega_{c1} < \omega_{c2}$

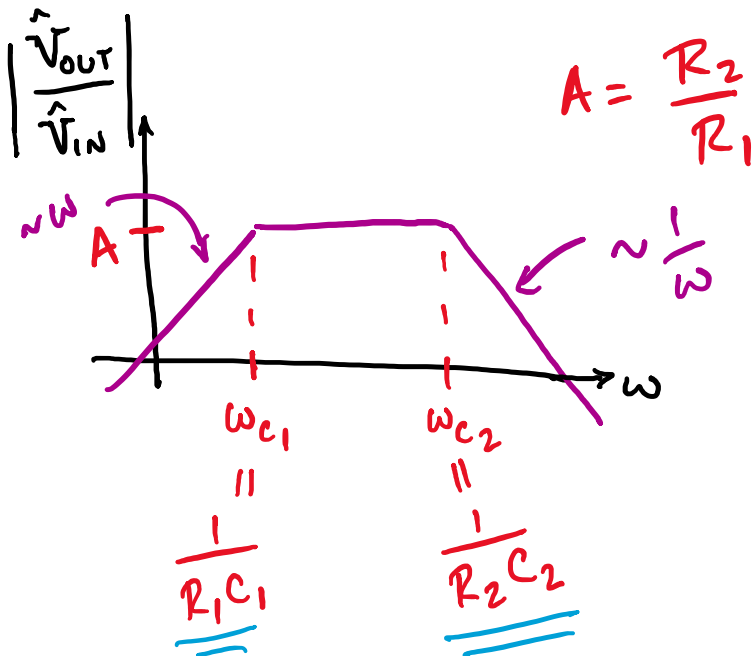

$$\begin{aligned} \frac{\hat{V}_{OUT}}{\hat{V}_{IN}} &= -\frac{\frac{R_2/j\omega C_2}{R_2 + 1/j\omega C_2}}{\frac{1}{j\omega C_1} + R_1} \\ &= -\frac{R_2}{1 + j\omega R_2 C_2} \frac{j\omega C_1}{1 + j\omega R_1 C_1} \end{aligned}$$

# Band Pass Active Filter – Quality Factor

$$\frac{\hat{V}_{OUT}}{\hat{V}_{IN}} = \frac{-j\omega R_2 C_1}{(1+j\omega R_2 C_2)(1+j\omega R_1 C_1)} = \frac{-j\omega R_2 C_1}{(1+j\omega/\omega_{c2})(1+j\omega/\omega_{c1})}$$

$$\left[ \frac{(j\omega)^2}{\omega_{c1}\omega_{c2}} + j\omega \left( \frac{1}{\omega_{c1}} + \frac{1}{\omega_{c2}} \right) + 1 \right] \hat{V}_{OUT} = -j\omega R_2 C_1 \hat{V}_{IN}$$

$$\frac{1}{\omega_{c1}\omega_{c2}} \frac{d^2 v_{out}}{dt^2} + \left( \frac{1}{\omega_{c1}} + \frac{1}{\omega_{c2}} \right) \frac{dv_{out}}{dt} + v_{out} = -R_2 C_1 \frac{dv_{in}}{dt}$$

homogeneous  
diff. eqn

$$v_{out} \sim e^{st} \Rightarrow \frac{s^2}{\omega_{c1}\omega_{c2}} + \left( \frac{1}{\omega_{c1}} + \frac{1}{\omega_{c2}} \right) s + 1 = 0$$

$$s^2 + \frac{2\alpha}{(\omega_{c1} + \omega_{c2})} s + \frac{\omega_0^2}{\omega_{c1}\omega_{c2}} = 0$$

← Characteristic Eqn

$$Q \equiv \frac{\omega_0}{2\alpha} = \frac{\sqrt{\omega_{c1}\omega_{c2}}}{\omega_{c1} + \omega_{c2}}$$

# Band Pass Active Filter – Quality Factor (Cont.)

$$Q = \frac{\sqrt{\omega_{c1} \omega_{c2}}}{\omega_{c1} + \omega_{c2}} \Rightarrow \frac{dQ}{d\omega_{c1}} = 0$$


Maximum at  
 $\Rightarrow \omega_{c1} = \omega_{c2}$

$$Q_{\max} = \frac{\sqrt{\omega_{c2} \omega_{c2}}}{\omega_{c2} + \omega_{c2}} = \frac{\omega_{c2}}{2\omega_{c2}} = \frac{1}{2}$$

$$Q_{\max} = \frac{1}{2}$$




# Band Stop Active Filter Synthesis

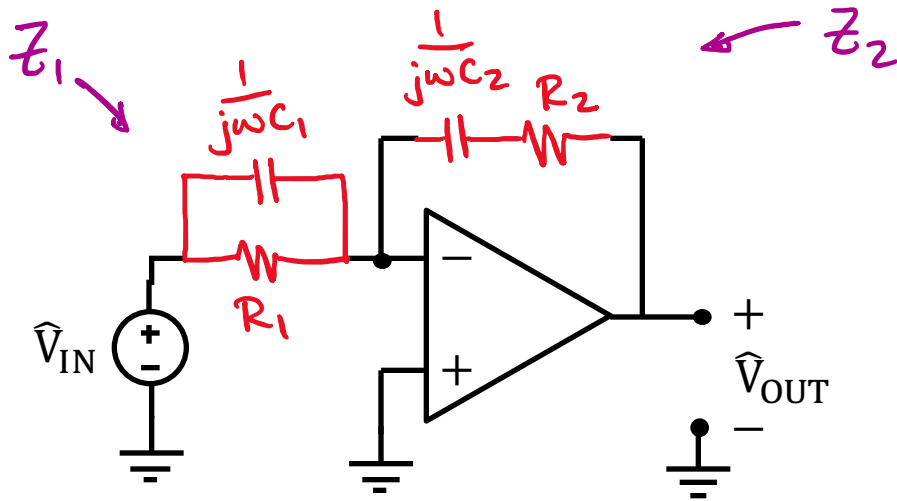


$$\frac{\hat{V}_{OUT}}{\hat{V}_{IN}} = -\frac{Z_2}{Z_1}$$

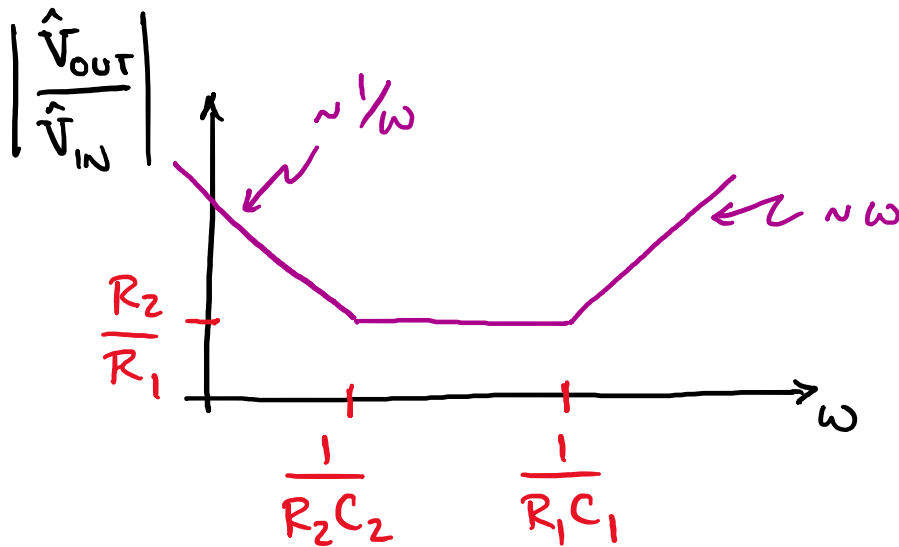swap  $Z_1$  &  $Z_2$  of band pass filter to create band stop filter



# Sallen-Key Low Pass Active Filter

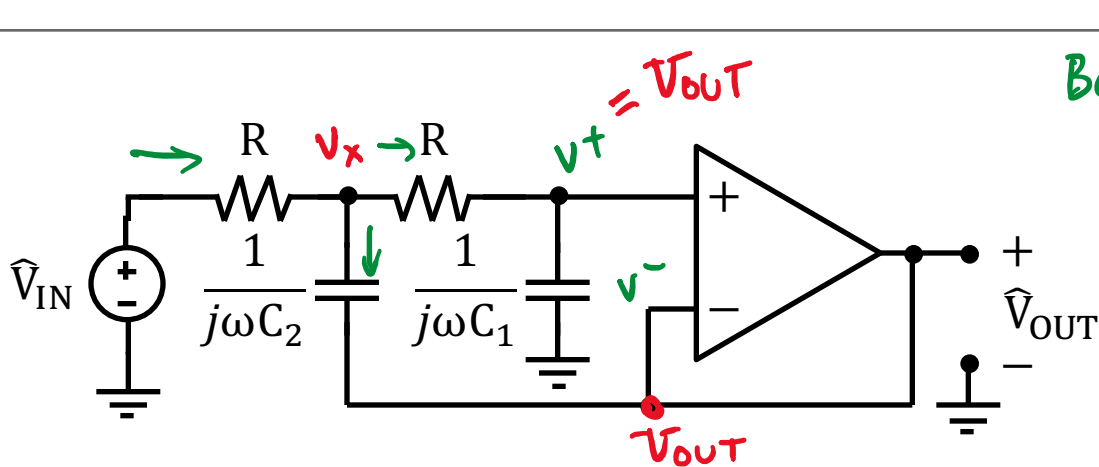


Because  $\hat{V}_{OUT}$  is finite (system stable)  
 $v^+ \approx v^- = \hat{V}_{OUT}$

$$\hat{V}_{OUT} \parallel v^+ = \frac{\frac{1}{j\omega C_1} v_X}{\frac{1}{j\omega C_1} + R} = \frac{1}{1 + j\omega RC_1} v_X \Rightarrow v_X = (1 + j\omega RC_1) \hat{V}_{OUT}$$

$$\frac{\hat{V}_{IN} - v_X}{R} = \frac{v_X - \hat{V}_{OUT}}{1/j\omega C_2} + \frac{v_X - \hat{V}_{OUT}}{R} \quad \rightarrow \text{Do algebra}$$

$$\hat{V}_{IN} = (j\omega 2RC_1 + 2 + (j\omega)^2 R^2 C_1 C_2 - 1) \hat{V}_{OUT}$$
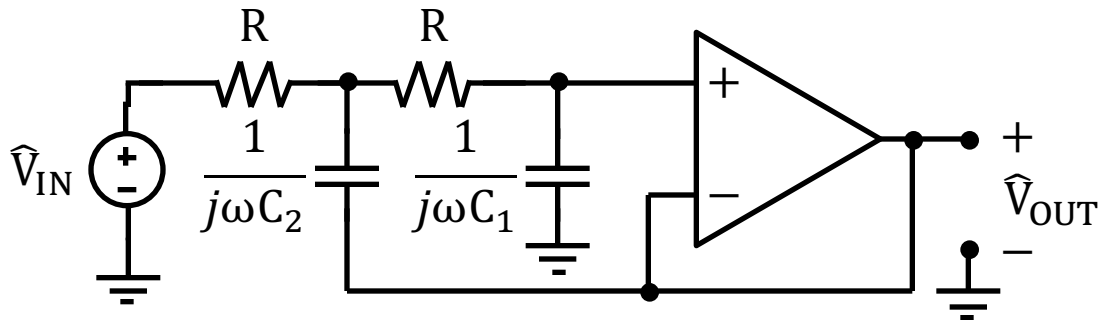
# Sallen-Key Low Pass Active Filter (Cont.)



$$\frac{\hat{V}_{OUT}}{\hat{V}_{IN}} = \frac{1}{(j\omega)^2 (R^2 C_1 C_2) + (j\omega)(2RC_1) + 1}$$


Char Eqn:  $s^2 R^2 C_1 C_2 + s 2RC_1 + 1 = 0$

$$\Rightarrow s^2 + \frac{2s}{RC_2} + \frac{1}{R^2 C_1 C_2} = 0$$

$$Q = \frac{\omega_0}{2\alpha} = \frac{1}{2} \sqrt{\frac{C_2}{C_1}}$$

← Can get Q values greater than 1/2 by making C<sub>2</sub> greater than C<sub>1</sub>

# Sallen-Key High Pass Active Filter

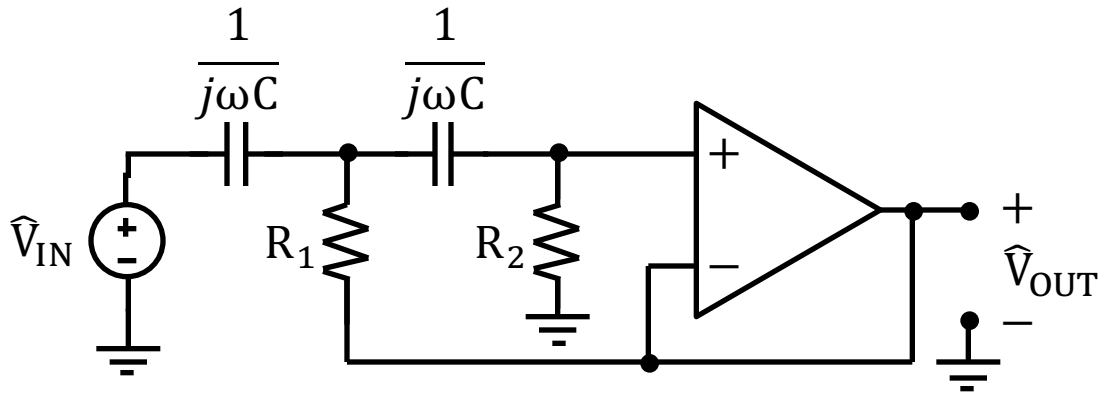

Swap R's and C's  
to go from Low Pass  
Filter to High Pass  
Filter