

# **ECE/ENGRD 2100**

## Introduction to Circuits for ECE

### Lecture 35


#### Circuit Analysis using the Laplace Transform

# Announcements



---

- Recommended Reading:
  - Textbook Chapter 12 and Chapter 13
- Upcoming due dates:
  - Homework 5 due by 11:59 pm on Friday April 26, 2019
  - Prelab 6 due by 11:59 pm on Friday April 26, 2019
  - Lab report 6 due by 11:59 pm on Friday May 3, 2019
  - Homework 6 due by 11:59 pm on Friday May 3, 2019

# Complete Solution for Arbitrary Drives

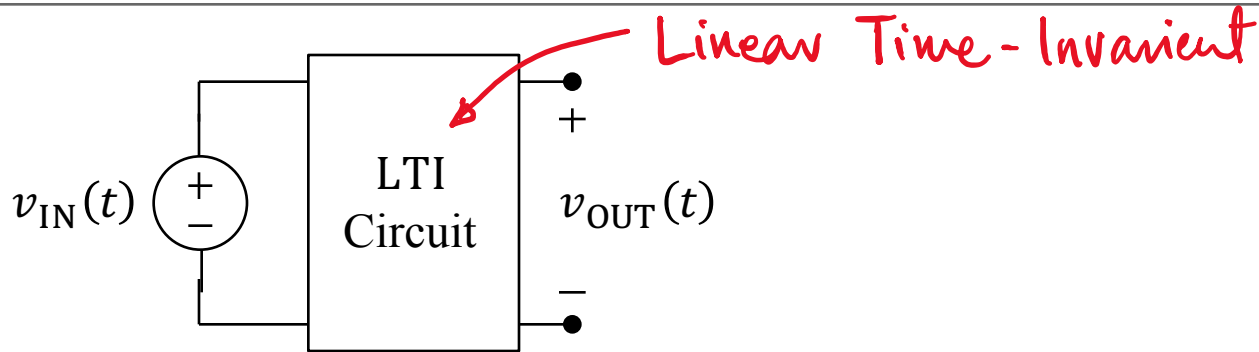


## Example


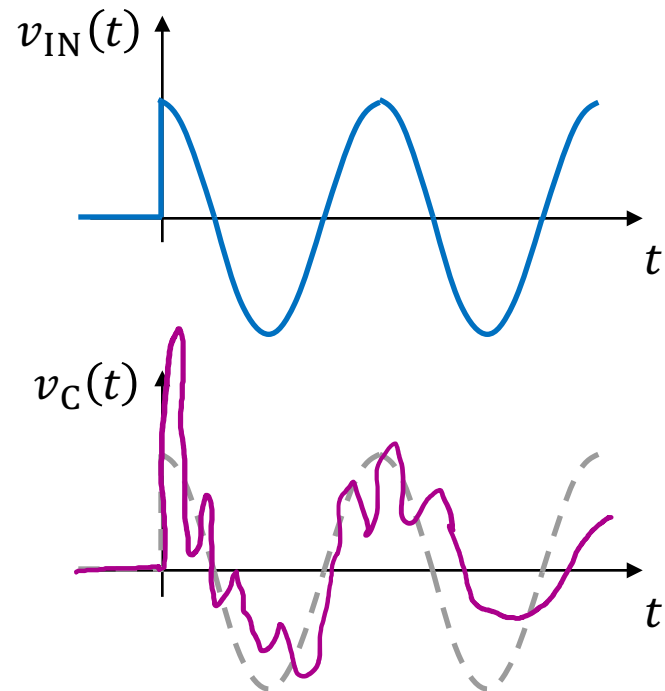
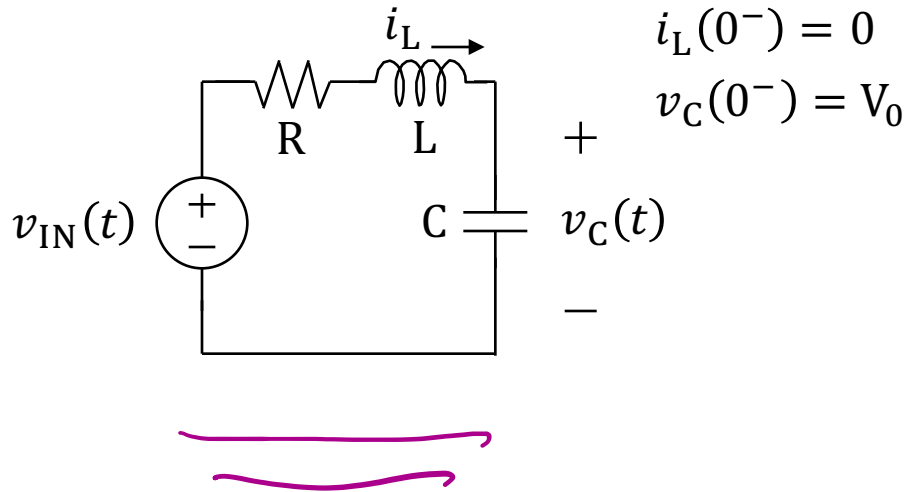


# Complete Solution in Frequency Domain

Time Domain

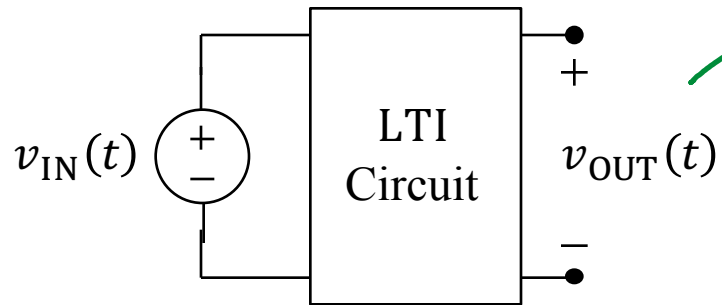

Frequency Domain

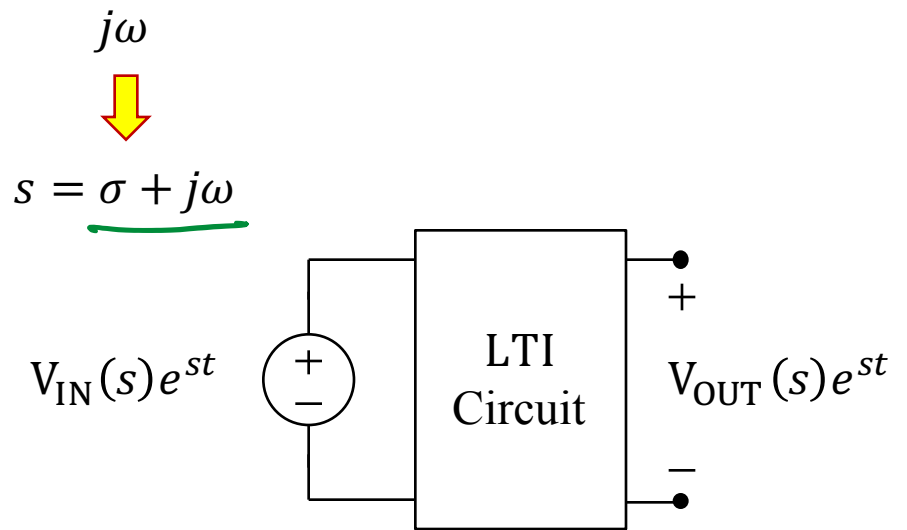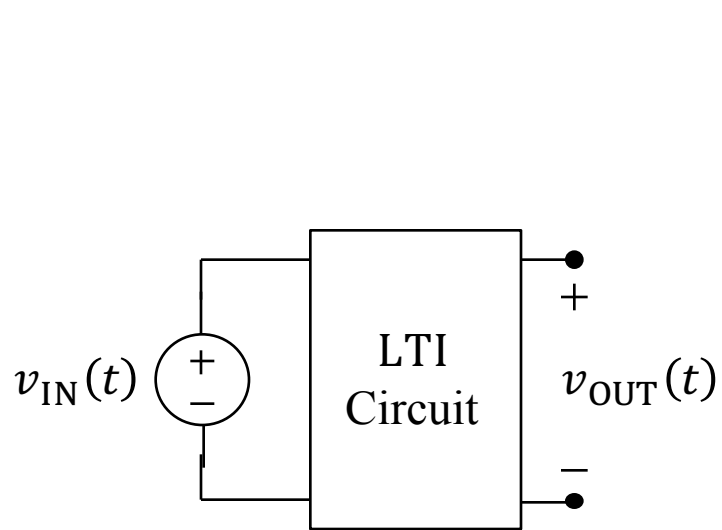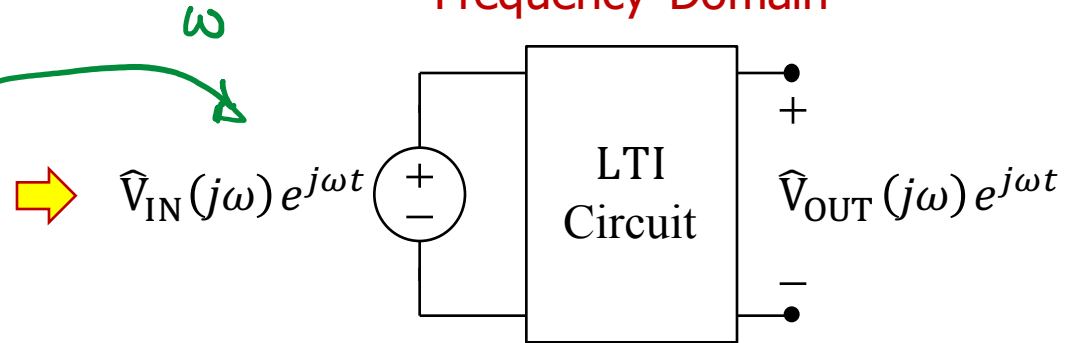

$\sigma$	$\omega$	$Ae^{st}$
0	0	A
$\sigma_1$	0	$Ae^{\sigma_1 t}$
$\sigma_1$	$\omega_1$	$Ae^{\sigma_1 t} e^{j\omega_1 t}$

$$\int V_{IN}(s)e^{st} ds \quad \longrightarrow \quad \int V_{OUT}(s)e^{st} ds$$

# Laplace Transform

## Unilateral Laplace Transform

$$\mathcal{L}\{f(t)\} = \int_{0^-}^{\infty} f(t) e^{-st} dt = F(s)$$



where  $s = \sigma + j\omega$

$$s = \sigma_0 + j\omega \Rightarrow ds = j d\omega$$

## Inverse Laplace Transform

$$\mathcal{L}^{-1}\{F(s)\} = \frac{1}{2\pi j} \int_{\sigma_0 - j\infty}^{\sigma_0 + j\infty} F(s) e^{st} ds = f(t)$$

Time Domain

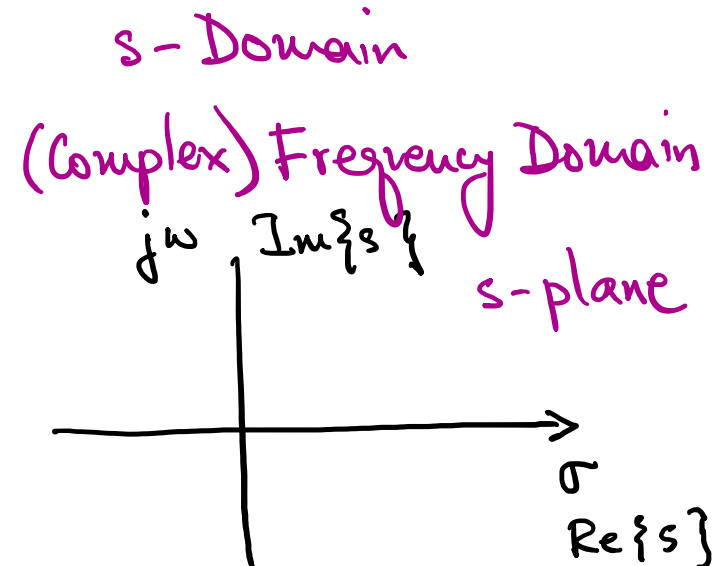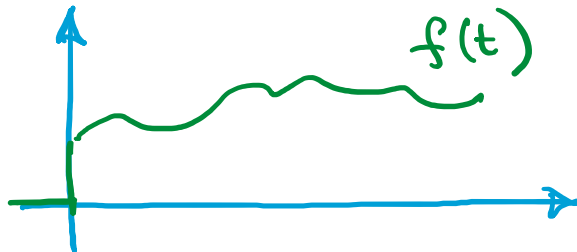

# Laplace Transform – Linearity Property

$$\mathcal{L}\{f(t)\} = \int_{0^-}^{\infty} f(t) e^{-st} dt = F(s)$$

$$f(t) = K_1 f_1(t) + K_2 f_2(t)$$

$$\mathcal{L}\{K_1 f_1(t) + K_2 f_2(t)\} = \int_{0^-}^{\infty} (K_1 f_1(t) + K_2 f_2(t)) e^{-st} dt$$

$$= K_1 \int_{0^-}^{\infty} f_1(t) e^{-st} dt + K_2 \int_{0^-}^{\infty} f_2(t) e^{-st} dt$$

$$= K_1 \mathcal{L}\{f_1(t)\} + K_2 \mathcal{L}\{f_2(t)\}$$

$$\mathcal{L}\{K_1 f_1(t) + K_2 f_2(t)\} = K_1 \mathcal{L}\{f_1(t)\} + K_2 \mathcal{L}\{f_2(t)\}$$

# Laplace Transform – Differentiation Property

$$\mathcal{L}\{f(t)\} = \int_{0^-}^{\infty} f(t) e^{-st} dt = F(s)$$

$$\mathcal{L}\left\{\frac{df}{dt}\right\} = \int_{0^-}^{\infty} \frac{df}{dt} e^{-st} dt$$

$$= \left[ f(t) e^{-st} \right]_{0^-}^{\infty} + \int_{0^-}^{\infty} f(t) s e^{-st} dt$$

$$= 0 - f(0^-) + s \underbrace{\int_{0^-}^{\infty} f(t) e^{-st} dt}_{F(s)} = sF(s) - f(0^-)$$

$$\mathcal{L}\left\{\frac{df}{dt}\right\} = sF(s) - f(0^-)$$

$$v' = \frac{dv}{dt}$$

$$(uv)' = u'v + uv'$$

$$\Rightarrow \int_{0^-}^{\infty} u'v dt = [uv]_{0^-}^{\infty} - \int_{0^-}^{\infty} uv' dt$$

$$u' = \frac{df}{dt} \Rightarrow u = f$$

$$v = e^{-st} \Rightarrow v' = -s e^{-st}$$

# Laplace Transform Properties

	Time Domain		Frequency Domain	
Linear	$K_1 f_1(t) + K_2 f_2(t)$	$\longleftrightarrow$	$K_1 F_1(s) + K_2 F_2(s)$	$\leftarrow$
Differentiation	$\frac{df(t)}{dt}$	$\longleftrightarrow$	$sF(s) - f(0^-)$	$\leftarrow$
	$\frac{d^2 f(t)}{dt^2}$	$\longleftrightarrow$	$s^2 F(s) - sf(0^-) - f'(0^-)$	$\leftarrow$
	$\int_{-\infty}^t f(t) dt$	$\longleftrightarrow$	$\frac{F(s)}{s} + \frac{1}{s} \int_{-\infty}^{0^-} f(t) dt$	
	$f(t - t_0)u(t - t_0)$	$\longleftrightarrow$	$e^{-t_0 s} F(s)$	
	$e^{-\alpha t} f(t)$	$\longleftrightarrow$	$F(s + \alpha)$	
	$f(0^+)$	$\longleftrightarrow$	$\lim_{s \rightarrow \infty} sF(s)$	$\leftarrow$
	$f(\infty)$	$\longleftrightarrow$	$\lim_{s \rightarrow 0} sF(s)$	$\leftarrow$




# Laplace Transform of $u(t)$

$$f(t) = u(t)$$


$$F(s) = \int_{0^-}^{\infty} f(t) e^{-st} dt = \int_{0^-}^{\infty} u(t) e^{-st} dt = \int_{0^-}^{\infty} e^{-st} dt$$

$$= \left[ \frac{e^{-st}}{-s} \right]_{0^-}^{\infty} = \frac{0 - 1}{-s} = \frac{1}{s}$$


for  $\text{Re}\{s\} > 0$

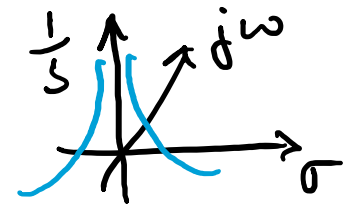

$$u(t) \longleftrightarrow \frac{1}{s}$$

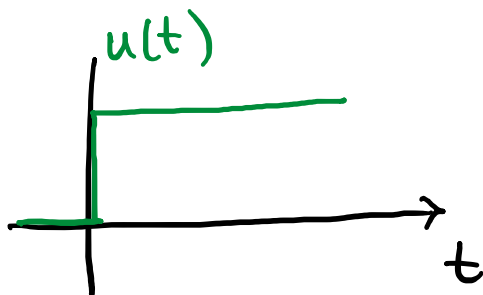
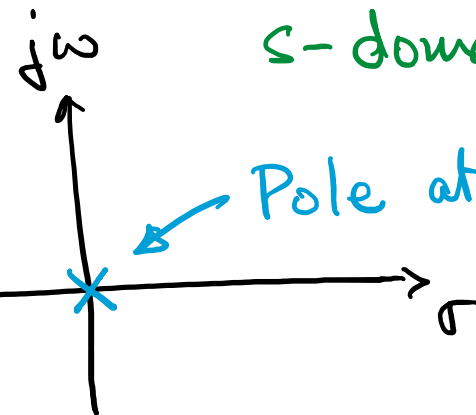
$$\frac{1}{s} = \frac{1}{\sigma + j\omega}$$



Pole at  $s=0$

# Laplace Transform of $e^{-\alpha t}$


$$f(t) = e^{-\alpha t}$$

$$\begin{aligned} F(s) &= \int_{0^-}^{\infty} f(t) e^{-st} dt = \int_{0^-}^{\infty} e^{-\alpha t} e^{-st} dt = \int_{0^-}^{\infty} e^{-(s+\alpha)t} dt \\ &= \left[ \frac{e^{-(s+\alpha)t}}{-(s+\alpha)} \right]_{0^-}^{\infty} = \frac{0 - 1}{-(s+\alpha)} = \frac{1}{s+\alpha} \quad \text{Re}\{s\} > -\alpha \end{aligned}$$

$$e^{-\alpha t} u(t) \iff \frac{1}{s+\alpha}$$

$$\frac{1}{\sigma + j\omega + \alpha}$$

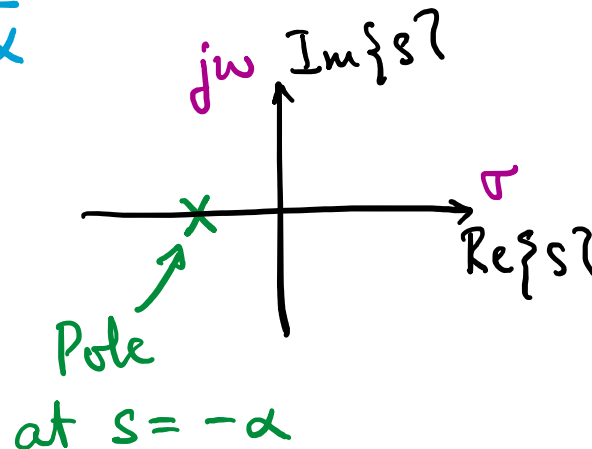
$\Rightarrow \sigma = -\alpha \text{ \& } \omega = 0$



# Laplace Transform Pairs

Time Domain		Frequency Domain	
$\delta(t)$	$\longleftrightarrow$	1	
$u(t)$	$\longleftrightarrow$	$\frac{1}{s}$	$\leftarrow$
$tu(t)$	$\longleftrightarrow$	$\frac{1}{s^2}$	
$e^{-\alpha t}u(t)$	$\longleftrightarrow$	$\frac{1}{s + \alpha}$	$\leftarrow$
$\sin(\omega t) u(t)$	$\longleftrightarrow$	$\frac{\omega}{s^2 + \omega^2}$	
$\cos(\omega t) u(t)$	$\longleftrightarrow$	$\frac{s}{s^2 + \omega^2}$	
$te^{-\alpha t}u(t)$	$\longleftrightarrow$	$\frac{1}{(s + \alpha)^2}$	
$e^{-\alpha t} \sin(\omega t) u(t)$	$\longleftrightarrow$	$\frac{\omega}{(s + \alpha)^2 + \omega^2}$	
$e^{-\alpha t} \cos(\omega t) u(t)$	$\longleftrightarrow$	$\frac{s + \alpha}{(s + \alpha)^2 + \omega^2}$	
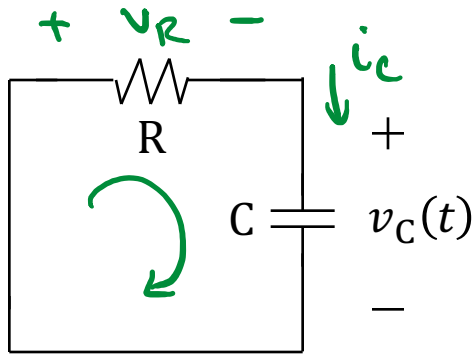
# Laplace Transform based Analysis - Example 1



$$v_C(0^-) = V_0$$

$$v_R + v_C = 0$$

$$RC \frac{dv_C}{dt} + v_C = 0$$

Diff Eqn

$$\mathcal{L} \left\{ RC \frac{dv_C}{dt} + v_C \right\} = 0$$


$$\Rightarrow RC(sV_C(s) - v_C(0^-)) + V_C(s) = 0$$

$$\Rightarrow (sRC + 1)V_C(s) = RCv_C(0^-) \Rightarrow V_C(s) = \frac{RCv_C(0^-)}{sRC + 1}$$

$$\Rightarrow \underline{V_C(s)} = \frac{v_C(0^-)}{s + 1/RC} = v_C(0^-) \cdot \frac{1}{s + 1/RC}$$

$$\Rightarrow v_C(t) = v_C(0^-) e^{-t/RC} u(t)$$

## Example 2

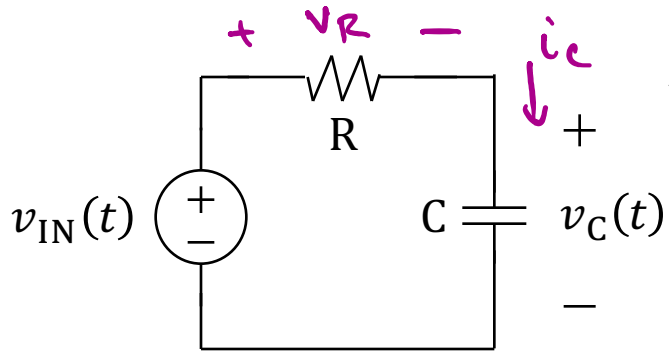

$$v_R + v_C = v_{IN}$$

$$RC \frac{dv_C}{dt} + v_C = V_I u(t)$$

↓  $\mathcal{L}$

$$v_{IN}(t) = V_I u(t)$$

$$RC(sV_C(s) - v_C(0^-)) + V_C(s) = \frac{V_I}{s}$$

$$\Rightarrow (RCs + 1)V_C(s) = \frac{V_I}{s} + RCv_C(0^-)$$

$$V_C(s) = \frac{V_I/RC}{s(s + 1/RC)} + \frac{v_C(0^-)}{s + 1/RC}$$

$$V_C(s) = \frac{A_1}{s} + \frac{A_2}{s + 1/RC} + \frac{v_C(0^-)}{s + 1/RC}$$