

ECE/ENGRD 2100

Introduction to Circuits for ECE


Lecture 37

Transfer Functions and Bode Plots Revisited

Announcements

- Recommended Reading:
 - Textbook Chapter 13 and Appendix E
- Upcoming due dates:
 - Homework 5 due by 11:59 pm on Monday April 29, 2019
 - Prelab 6 due by 11:59 pm on Monday April 29, 2019
 - Lab report 6 due by 11:59 pm on Friday May 3, 2019
 - Homework 6 due by 11:59 pm on Tuesday May 7, 2019

Transfer Function in s-Domain

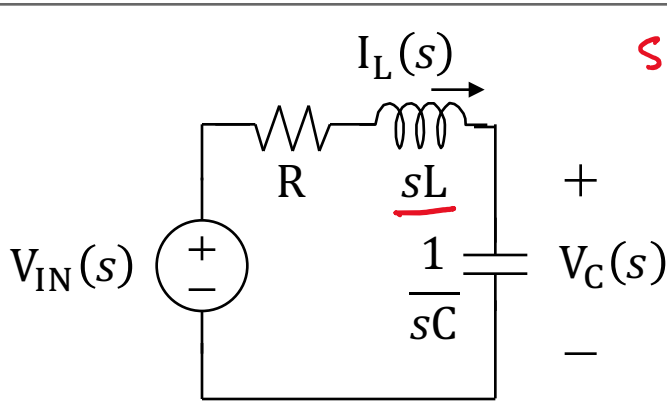

$$s = \sigma + j\omega$$

$$H(s) \equiv \frac{Y(s)}{X(s)}$$

← output (any variable of interest)
 with initial conditions = 0
 ← input (drive)

$$H_{IL}(s) \equiv \frac{I_L(s)}{V_{IN}(s)} = \frac{\frac{s}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$H_{VC}(s) \equiv \frac{V_C(s)}{V_{IN}(s)} = \frac{\frac{1}{sC}}{sL + R + \frac{1}{sC}} = \frac{1}{s^2 LC + sRC + 1} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

All Transfer Functions of a circuit have the same denominator

The denominator set equal to zero is the characteristic equation of the circuit: $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$ ← Solutions of this give information about natural response of circuit

Poles and Zeros of the Transfer Function

$$H(s) \equiv \frac{Y(s)}{X(s)} = \frac{N(s)}{D(s)} = \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}$$

$$H(s) = \frac{a_n (s + z_1)(s + z_2) \dots (s + z_n)}{b_m (s + p_1)(s + p_2) \dots (s + p_m)}$$

Poles are the roots of the denominator polynomial – $D(s) \Rightarrow s = -p_1, -p_2, \dots, -p_m$

Zeros are the roots of the numerator polynomial – $N(s) \Rightarrow s = -z_1, -z_2, \dots, -z_n$

$$Y(s) = H(s)X(s) = \frac{N(s)}{D(s)}X(s)$$

By applying an impulse, we are getting the natural response of the circuit


Impulse Response:

$$X(s) = 1$$



$$Y(s) = H(s) = \frac{N(s)}{D(s)}$$

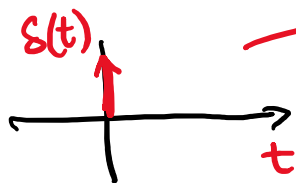The poles of the transfer function determine the natural response of the circuit



$$\mathcal{L}\{\delta(t)\} = 1$$

$$D(s) = b_m (s + p_1)(s + p_2) \dots (s + p_m) = 0$$


$$s = -\alpha \pm j\sqrt{\alpha^2 - \omega^2}$$

Pole Location and Natural Response

$$s = \underline{\underline{\sigma}} + j\omega$$

$$e^{st} = e^{\sigma t} e^{j\omega t}$$

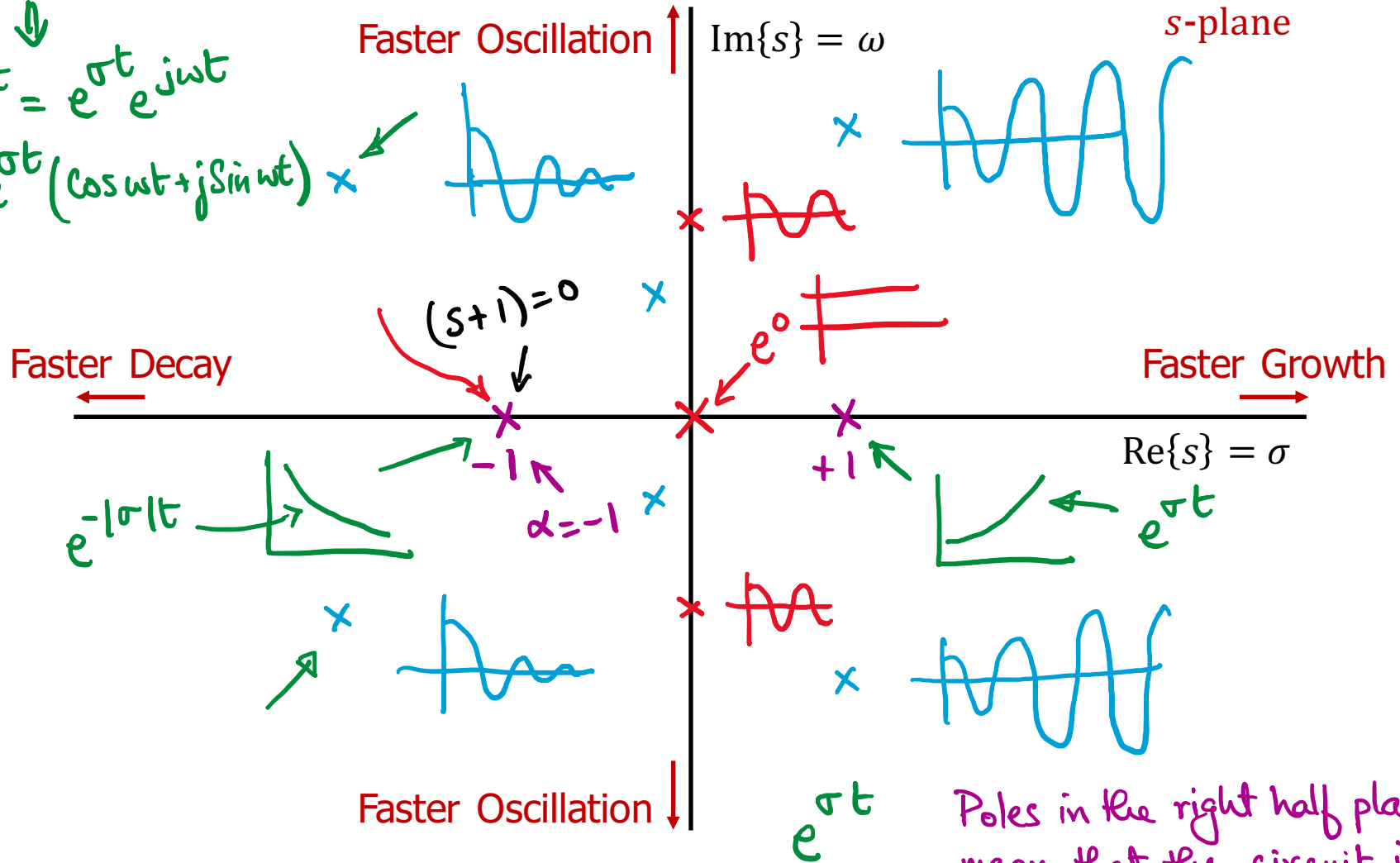
$$= e^{\sigma t} (\cos \omega t + j \sin \omega t)$$




Poles in the right half plane mean that the circuit is unstable

Sinusoidal Steady-State Frequency Response


s-Domain

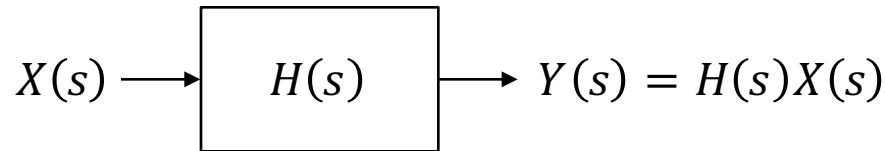

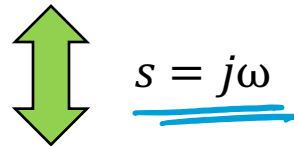The s-domain transfer function can also be used to find the sinusoidal steady-state response of the circuit. Simply replace "s" by "j ω "




Phasor-Domain

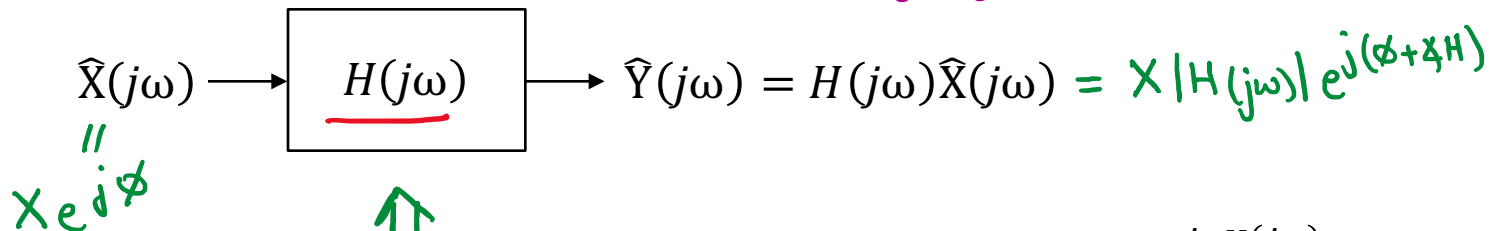

$$H(j\omega) = |H(j\omega)| e^{j\angle H(j\omega)}$$

Time-Domain

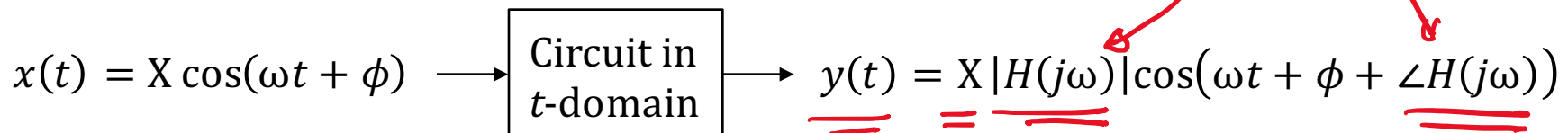

Bode Plots (Revisited)

$$H(s) = H_1(s)H_2(s)$$

$$\updownarrow s = j\omega$$

$$\underline{H(j\omega)} = \underline{H_1(j\omega)}\underline{H_2(j\omega)} \quad \Rightarrow \quad H(j\omega) = \overbrace{|H_1(j\omega)|e^{j\angle H_1(j\omega)}}^{H_1(j\omega)} \overbrace{|H_2(j\omega)|e^{j\angle H_2(j\omega)}}^{H_2(j\omega)}$$

$$\Rightarrow |H(j\omega)|e^{j\angle H(j\omega)} = \underbrace{|H_1(j\omega)||H_2(j\omega)|}_{|H(j\omega)|} e^{j(\angle H_2(j\omega) + \angle H_1(j\omega))}$$

$$\underline{|H(j\omega)|} = \underline{|H_1(j\omega)||H_2(j\omega)|} \quad \Rightarrow \quad \underline{|H(j\omega)|_{dB}} = \underline{20 \log_{10}(|H_1(j\omega)||H_2(j\omega)|)}$$

$$|H(j\omega)|_{dB} = 20 \log_{10}|H_1(j\omega)| + 20 \log_{10}|H_2(j\omega)|$$

$$\underline{\angle H(j\omega)} = \underline{\angle H_2(j\omega)} + \underline{\angle H_1(j\omega)}$$

Bode Plot Example 1

$$H(s) = \frac{10^5(s + 10^3)}{(s + 10^1)(s + 10^5)}$$

$$\updownarrow s = j\omega$$

$$H(j\omega) = \frac{10^5(j\omega + 10^3)}{(j\omega + 10^1)(j\omega + 10^5)} \Rightarrow H(j\omega) = \frac{10^2(1 + j\omega/10^3)}{(1 + j\omega/10^1)(1 + j\omega/10^5)}$$

$$H(j\omega) = H_1(j\omega)H_2(j\omega)H_3(j\omega)H_4(j\omega)$$

$$H_1(j\omega) = 10^2$$

$$H_2(j\omega) = (1 + j\omega/10^3)$$

$$H_3(j\omega) = \frac{1}{(1 + j\omega/10^1)}$$

$$H_4(j\omega) = \frac{1}{(1 + j\omega/10^5)}$$


Bode Plot Example 1 (Cont.)

$$H_1(j\omega) = 10^2 \rightarrow 20 \log_{10} 10^2 = 40 \text{ dB} \quad |H(j\omega)|_{\text{dB}}$$

$$H_2(j\omega) = (1 + j\omega/10^3)$$

$$H_3(j\omega) = \frac{1}{(1 + j\omega/10^1)}$$

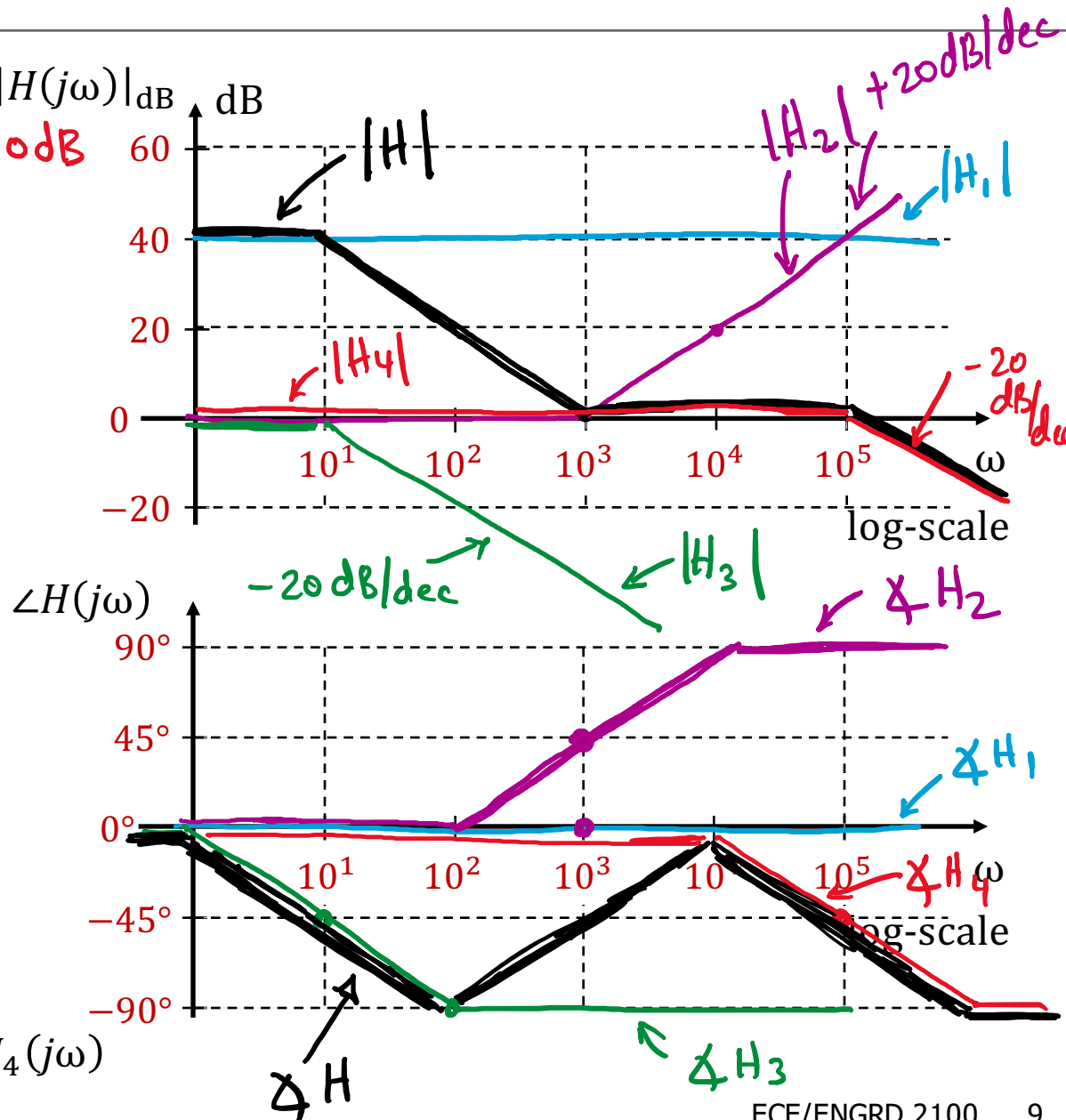
$$H_4(j\omega) = \frac{1}{(1 + j\omega/10^5)}$$



$$H(j\omega) = H_1(j\omega)H_2(j\omega)H_3(j\omega)H_4(j\omega)$$

Bode Plot Example 1 – Using Poles and Zeros
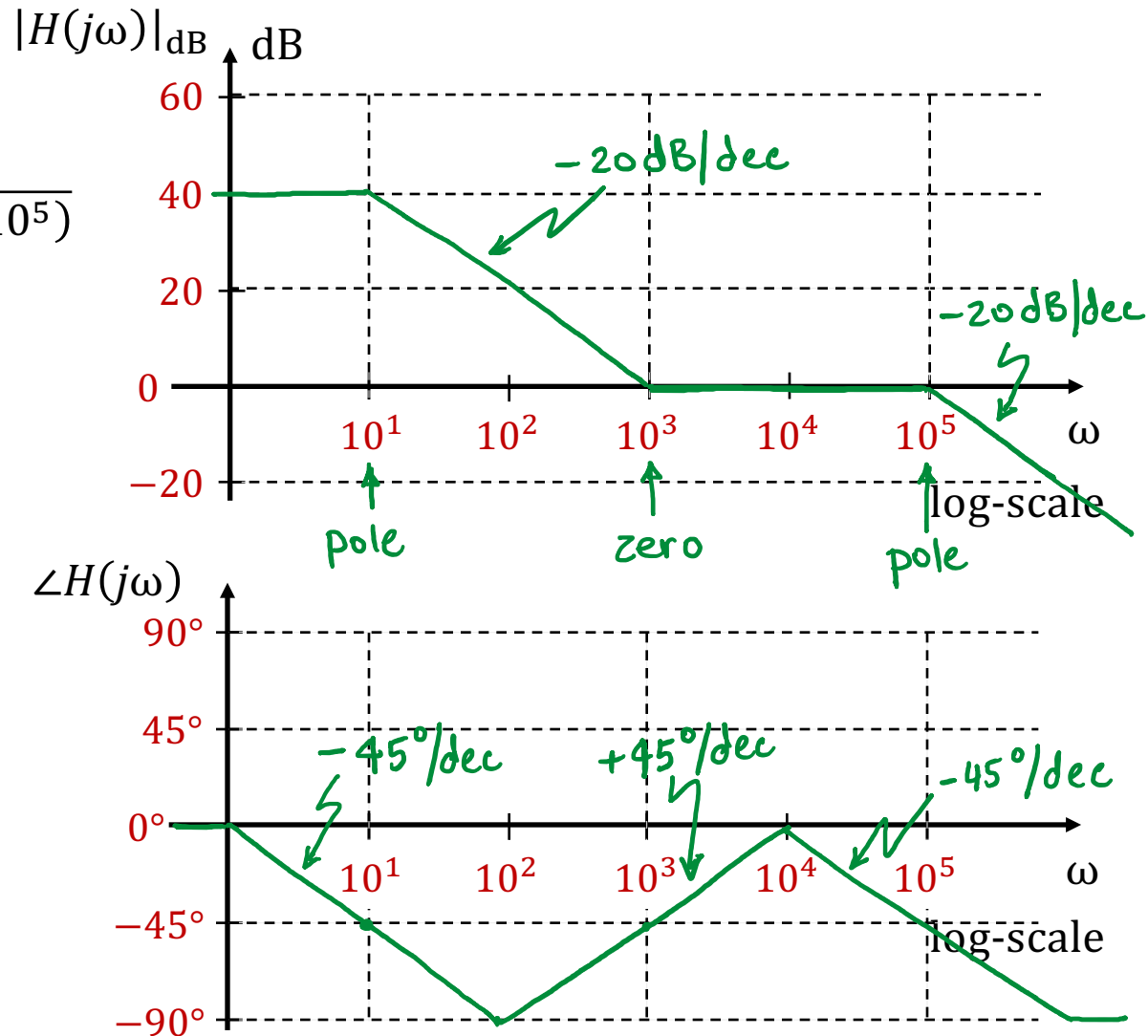
$$H(j\omega) = \frac{10^2(1 + j\omega/10^3)}{(1 + j\omega/10^1)(1 + j\omega/10^5)}$$



Bode Plot Example 2

$$H(s) = \frac{10^7}{s^2 + 10s + 10^6}$$

↕ $s = j\omega$

$$H(j\omega) = \frac{10^7}{-\omega^2 + 10j\omega + 10^6}$$

$2\alpha = 10$ $\omega_0^2 = 10^6$

$$= \frac{10}{1 + j\omega/10^5 - (\omega/10^3)^2}$$

$\omega_0 = 10^3 \text{ rad/s}$

$\alpha = 5 \text{ rad/s}$

Since $\omega_0 > \alpha \Rightarrow$ underdamped

$Q = \frac{\omega_0}{2\alpha} = 10^2$

$\Rightarrow Q_{dB} = 40 \text{ dB}$

